

Google Little-Box Reloaded

Advances In Ultra-Compact GaN
Based Single-Phase DC/AC Power Conversion



Dominik Neumayr



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Google Little-Box Reloaded

Advances In Ultra-Compact GaN
Based Single-Phase DC/AC Power Conversion



D. Neumayr, J. W. Kolar, D. Bortis, M. Guacci, J. Azurza



Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Outline

- ▶ The Google Little Box Challenge
- ▶ *Little Box 1.0*
- ▶ *Concepts & Performances of Other Finalists*
- ▶ *Optimization & Advanced Analysis*
- ▶ *Little Box 2.0*
- ▶ Conclusions



Acknowledgement

O. Knecht
F. Krismer
M. Guacci
L. Camurca
M. Kasper
E. Hatipoglu

Google Little Box Challenge


Requirements
The Grand Prize
Finalists & Finals



LITTLE BOX CHALLENGE

Google | IEEE

 - Design / Build the 2kW 1- Φ Solar Inverter with the Highest Power Density in the World
- Power Density > 3kW/dm³ (> 50W/in³, multiply kW/dm³ by Factor 16)
- Efficiency > 95%
- Case Temp. < 60°C
- EMI FCC Part 15 B



■ Push the Forefront of New Technologies in R&D of High Power Density Inverters



The Grand Prize

- Highest Power Density ($> 50\text{W}/\text{in}^3$)
- Highest Level of Innovation



\$1,000,000


■ Timeline

- Challenge Announced in Summer 2014
- **2000+ Teams Registered** Worldwide
- 100+ Teams Submitted a Technical Description until July 22, 2015
- **18 Finalists (3 No-Shows)**



LITTLE BOX CHALLENGE Finalists

* and FH IZM /
Fraza d.o.o.

 


- 5 Companies
- 6 Consultants
- 4 Universities

15 Teams/Participants in the Final @ NREL



LITTLE BOX CHALLENGE

Final Presentations

 

- Finalists Invited to NREL / USA
- **Presentations on Oct. 21, 2015**
- **Subsequent Testing by NREL**




Little Box 1.0

Converter Topology
Modulation & Control
Technologies /Components
Mechanical Concept
Exp. Analysis


Acknowledgement



*Derivation of
Converter Concept*

 


1- Φ Output Power Pulsation Buffer

 


Power Pulsation Buffer


• Parallel Buffer @ DC Input

 

• Series Buffer @ DC Input

 


 ■ Parallel Approach for Limiting Voltage Stress on Converter Stage Semiconductors



Passive Power Pulsation Buffer (1)


- Electrolytic Capacitor

 

$$\begin{aligned}
 S_0 &= 2.0 \text{ kVA} \\
 \cos \Phi_0 &= 0.7 \\
 V_{C,\max} &= 450 \text{ V} \\
 \Delta V_C / V_{C,\max} &= 3 \%
 \end{aligned}$$




5 x 493µF/450 V
C = 2.46 mF

 


 
■ $C > 2.2\text{mF} / 166 \text{ cm}^3 \rightarrow$ Consumes 1/4 of Allowed Total Volume !





Passive Power Pulsation Buffer (2)

  - Series Resonant Circuit / Used in Rectifier Input Stage of Locomotives




- * $C_r = 20 \mu\text{F}$
- * $L_r = 127 \text{ mH} @ v_{Lr} = 400 \text{ V}$

■ Unacceptably Large Inductor Volume !




→ Electronic Inductor

 

Partial Active Power Pulsation Buffer

 - Coupling Capacitor & “Electronic Inductor” Processing Only *Partial Power*




Electronic Inductor




- * Ertl (1999)
- * Enslin (1991)
- * Pilawa (2015)

 - Low $U_{C,aux}$ → Low Converter Losses
- High Values of C_k, C_{aux} Required for Low $U_{C,aux}$
- Full-Bridge Aux. Converter Allows Lower $U_{C,aux}$





Partial Active Power Pulsation Buffer

 
- Coupling Capacitor & “Electronic Inductor”



  - Low $U_{C,aux}$ → Low Converter Losses
- High Values of C_k, C_{aux} Required for Low $U_{C,aux}$
- Full-Bridge Aux. Converter Allows Lower $U_{C,aux}$



Properties of Full-Bridge Aux. Conv.

 


Full Active Power Pulsation Buffer



* Kyritsis (2007)

 - Large Voltage Fluctuation Foil or Ceramic Capacitor
- Buck- or Boost-Type DC/DC Interface Converter
- Buck-Type allows Utilizing 600V Technology



CeraLink
TDK




108 x 1.2 μF / 400 V
 $C_k \approx 140 \mu\text{F}$
 $V_{Ck} = 23.7 \text{ cm}^3$

- Significantly Lower Overall Volume Compared to Electrolytic Capacitor





*Output Stage
Topology / Modulation*

 


Symmetric PWM Full-Bridge AC/DC Conv. Topology

  - Symmetric PWM Operation of Both Bridge Legs
- No Low-Frequency CM Output Voltage Component



 - DM Component of u_1 and u_2 Defines Output u_o
- CM Component of u_1 and u_2 Represents Degree of Freedom of the Modulation (!)







ZVS of Output Stage / TCM Operation



* Henze (1988)

    - TCM Operation for Resonant Voltage Transition @ Turn-On/Turn-Off







- Requires Only Measurement of Current Zero Crossings, $i = 0$
- Variable Switching Frequency Lowers EMI



4D-Interleaving




    - Interleaving of 2 Bridge Legs per Phase - Volume / Filtering / Efficiency Optimum
- Interleaving in Space & Time – Within Output Period
- Alternate Operation of Bridge Legs @ Low Power
- Overlapping Operation @ High Power



 - Opt. Trade-Off of Conduction & Switching Losses / Opt. Distribution of Losses






Remark: iTCM Inverter Topology


- TCM : Challenging Inductor Design $\rightarrow$ Superposition of HF & LF Currents
- iTCM: Adding LC-Circuit between Bridge Legs $\rightarrow$ Separation of LF & HF Currents $\rightarrow L \gg L_B$

– TCM

 

- Low Output Current Ripple
- PWM Modulation Applicable
- Dedicated LF and HF Inductor Designs Possible


– iTCM

 

- $\rightarrow$ Reduced Filtering Effort
- $\rightarrow$ Simple Control Strategy
- $\rightarrow$ Improved Converter Efficiency


* P. Jain (2015)



 


Selection of Switching Frequency

 - Significant Reduction in EMI Filter Volume for Increasing Sw. Frequency



 
- Doubling Sw. Frequ. f_s Cuts Filter Volume in Half
- Upper Limit due to Digital Signal Processing Delays / Inductor & Sw. Losses – Heatsink Volume



EMI Filter Topology (1)

Conventional Filter Structure

 
- DM Filtering Between the Phases
- CM Filtering Between Phases and PE




- CM Cap. Limited by Earth Current Limit – Typ. 3.5mA for PFC Rectifiers (GLBC: 5mA then 50mA !)
- Large CM Inductor Needed – Filter Volume Mainly Defined by CM Inductors

EMI Filter Topology (2)

 - Filter Structure with Internal CM Capacitor Feedback
- Filtering to DC- (and optional to DC+)



 
- No Limitation of CM Capacitor C_1 Due to Earth Current Limit $\rightarrow \mu\text{F}$ Instead of nF Can be Employed
- Allows Downsizing of CM Inductor and/or Total Filter Volume



Final Converter Topology

- Interleaving of 2 Bridge Legs per Phase
- Active DC-Side Buck-Type Power Pulsation Buffer
- 2-Stage EMI AC Output Filter

 - (1) Heat Sink
- (2) EMI Filter
- (3) Power Pulsation Buffer
- (4) Enclosure




- ZVS of All Bridge Legs @ Turn-On/Turn-Off in Whole Operating Range (4D-TCM-Interleaving)
- Heatsinks Connected to DC Bus / Shield to Prevent Cap. Coupling to Grounded Enclosure

Technologies




 
Power Semiconductors
Cooling
DSP/FPGA
Auxiliary






Evaluation of Power Semiconductors (1)

    - Accurate Measurement of ZVS Losses Using Calorimetric Approach
- High Sw. Frequency for Large Ratio of Sw. and Conduction Losses




 - Direct Measurement of the Sum of Sw. and Conduction Losses
- Subtraction of the Conduction Losses Known from Calibration
- Fast Measurement by $C_{th} \cdot \Delta T / \Delta t$ Evaluation




Evaluation of Power Semiconductors (2)

 - Comparison of Soft-Switching Performance of $\sim 60\text{m}\Omega$, 600V/650V/900V GaN, SiC, Si MOSFETs
- Measurement of Energy Loss per Switch and Switching Period





 
- GaN MOSFETs Feature Highest Soft-Switching Performance
- Similar Soft-Switching Performance Achieved with Si and SiC
- Almost No Voltage-Dependency of Soft-Switching Losses for Si-MOSFET




Selected Power Semiconductors

- 600V IFX Normally-Off GaN GIT - ThinPAK8x8
- 2 Parallel Transistors / Switch
- Antiparallel CREE SiC Schottky Diodes

   
- 1.2V typ. Gate Threshold Voltage
- 55 m Ω $R_{DS(on)}$ @ 25°C, 120m Ω @ 150°C
- 5 Ω Internal Gate Resistance



$dv/dt = 500kV/\mu s$

 


 - CeraLink Capacitors for DC Voltage Buffering




High dv/dt -Immunity Gate Drive (1)

 - Low Threshold-Voltage of GaN GIT Devices → Negative Gate Voltage During Off-State Needed
- Internal Diode Characteristic → Gate Current Limitation During On-State Needed
- State-of-the-Art Gate Drive with Additional RC-Circuit




– C_s Enables High Gate Current for Fast Turn-On

– R_3 Discharges C_s During Off-State

 

 
- Duty Cycle and Frequency Dependent Gate Voltage
- Risk of Parasitic Turn-on Due to Switching of Complementary Switch






High dv/dt -Immunity Gate Drive (2)

 - Improved Gate Drive Circuit with RC-Circuit and **Added Clamping Diodes**
- High Current for Fast Turn-On as Conventional Approach



– Diode **ZD_2** Quickly Discharges C_s to V_{ZD2} @ Turn-Off

 – Diode **ZD_1** Prevents C_s from Complete Discharge During Off-State




- Fixed Neg. Turn-Off Gate Voltage Independent of Duty Cycle and @ Start-Up






High dv/dt -Immunity Gate Drive (3)

 - Improved Gate Drive Circuit with RC-Circuit and **Added Clamping Diodes**
- High Current for Fast Turn-On as Conventional Approach



– Diode **ZD_2** Quickly Discharges C_s to V_{ZD2} @ Turn-Off

 – Diode **ZD_1** Prevents C_s from Complete Discharge During Off-State





- Fixed Neg. Turn-Off Gate Voltage Independent of Duty Cycle and @ Start-Up
- RC-Circuit in Neg. Rail Enables Precharge of C_s with R_4



Final Advanced Gate Drive

  - **Fixed Negative Turn-off Gate Voltage** - Independent of Sw. Frequency and Duty Cycle
- **Extreme dv/dt Immunity ($500\text{ kV}/\mu\text{s}$)** - Due to CM Choke at Signal Isolator Input




- **Total Prop. Delay $< 30\text{ ns}$** incl. Signal Isolator, Gate Drive, and Switch Turn-On Delay


High Frequency Inductors (1)

- Multi-Airgap Inductor with Multi-Layer Foil Winding Arrangement Minim. Prox. Effect
- Very High Filling Factor / Low High Frequency Losses
- Magnetically Shielded Construction Minimizing EMI
- Intellectual Property of F. Zajc / Fraza

 - $L = 10.5 \mu\text{H}$
- 2 x 8 Turns
- 24 x 80 μm Airgaps
- Core Material DMR 51 / Hengdian
- 0.61mm Thick Stacked Plates
- 20 μm Copper Foil / 4 in Parallel
- 7 μm Kapton Layer Isolation
- 20m Ω Winding Resistance / $Q \approx 600$
- Terminals in No-Leakage Flux Area




■ Dimensions - 14.5 x 14.5 x 22mm³

 

High Frequency Inductors (2)

 - High Resonance Frequency → Inductive Behavior up to High Frequencies
- Extremely Low AC-Resistance → Low Conduction Losses up to High Frequencies
- High Quality Factor



- Shielding Eliminates HF Current through the Ferrite → Avoids High Core Losses
- Shielding Increases the Parasitic Capacitance


High Frequency Inductors (3)




* Knowles (1975!)

- Cutting of Ferrite Introduces Mech. Stress
- Significant Increase of the Loss Factor
- Reduction by Polishing / Etching (5 μm)


 
■ Comparison of Temp. Increase of a Bulk and a Sliced Sample @ 70mT / 800kHz



 


Thermal Management

  - 30°C max. Ambient Temperature
- 60°C max. Allowed Surface and Air Outlet Temperature
- Evaluation of Optimum Heatsink Temperature for Thermal Isolation of Converter



 
- Minimum Volume Achieved w/o Thermal Isolation with Heatsink @ max. Allowed Surface Temp.





Thermal Management

- Overall Cooling Performance Defined by Selected Fan Type and Heatsink


– Radial Blower

 



– Axial Fan

  

 
– Square Cross Section of Heatsink for Using a Fan



– Flat and Wide Heatsink for Blower

  


 
- Optimal Fan and Heat Sink Configuration Defined by Total Cooling System Length
- Cooling Concept with Blower Selected → Higher CSPI for Larger Mounting Surface




Final Thermal Management Concept (1)

- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters

  - 200um Fin Thickness
- 500um Fin Spacing
- 3mm Fin Height
- 10mm Fin Length
- $CSPI = 37 \text{ W}/(\text{dm}^3 \cdot \text{K})$
- 1.5mm Baseplate



 - $CSPI_{eff} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$ Considering Heat Distribution Elements
- Two-Side Cooling $\rightarrow$ Heatsink Temperature = 52°C @ 80W (8W by Natural Convection)





$i=0$ Detection

- Analyzed Methods**
 - Shunt Current Measurement
 - Measurement of the $R_{ds,on}$
 - Two Antiparallel Diodes
 - Giant Magneto-Resistive Sensor
 - Hall Element
- Saturable Inductor**

Various Drawbacks

  
Losses, No Galvanic Isolation, Low Signal-to-Noise Ratio (SNR), Size, Bandwidth, Realization Effort




- Galvanic Isolation, High SNR, Small Size, High Bandwidth, Simple Design**
- Min. Core Volume/Cross Section for Min. Core Losses**

$i=0$ Detection

 
- Saturable Inductor
 - Toroidal Core R4 x 2.4 x 1.6, EPCOS (4mm Diameter)
 - Core Material N30, EPCOS



 Digital Signal v_o
Induced Voltage v_i
Current i






 - Operation Tested up to 2.5MHz Switching Frequency




$i=0$ Detection

   - Saturable Inductor – Toroidal Core R4 x 2.4 x 1.6, EPCOS (4mm Diameter)
- Core Material N30, EPCOS




 
- Operation Tested up to 2.5MHz Switching Frequency




Control Board & $i=0$ Detection

- Fully Digital Control - Overall Control Sampling Frequency of 25kHz
- TI DSC TMS320F28335 / 150MHz / 179-pin BGA / 12mm x 12mm
- Lattice FPGA LFXP2-5E / 200MHz / 86-pin BGA / 8mm x 8mm

  - TCM Current / Induced Voltage / Comparator Output





 - $i=0$ Detection of TCM Currents Using R4/N30 Saturable Inductors
- Galv. Isolated / Operates up to 2.5MHz Switching Frequency / <10ns Delay




Active Power Pulsation Buffer Capacitor

  - **Electrolytic Capacitors** – Limited by Lifetime-Relevant Current Limit
- **2.2 μ F, 450 V Class II X6S MLCC** – Highest Energy Density but Cap. Decreases with DC Bias
- **Novel 1 μ F / 2 μ F, 650 V CeraLink™ Cap. (PLZT Ceramic) Features High Cap. @ High DC Bias**
- **Allows 125°C Operating Temp. & Shows Very Low ESR @ High Frequencies**




 
- **CeraLink Resonance Frequency at Several MHz**
- **Small-Signal ESR of CeraLink in MHz Frequ. Range Sign. Lower Comp. to X6S MLCC**




Final Active Power Pulsation Buffer

- High Energy Density 2nd Gen. 400VDC CeraLink Capacitors Utilized as Energy Storage
- Highly Non-Linear Behavior → Optimal DC Bias Voltage of 280VDC
- Losses of 6W @ 2kVA Output Power

  - 108 x 1.2 μ F / 400 V
- 23.7cm³ Capacitor Volume




 - Effective Large Signal Capacitance of $C \approx 160\mu$ F




Active Power Pulsation Buffer Control (1)

- New Cascaded Control Structure

 

 
- P-Type Resonant Controller
- Feedforward of Output Power Fluctuation
- Underlying Input Current (i_i) / DC Link Voltage (u_c) Control





Active Power Pulsation Buffer Control (2)

 - Multiple Controller Outputs Combined in a Single Current Reference







- Regulation of Mean Buffer Voltage (Bias Voltage)
- Tight Control of Inverter DC Link Voltage also During Transients
- Active Power Decoupling – Rejection of 2 x Line-Frequ. Ripple in Inverter DC Input Voltage




Auxiliary Supply

    - Constant 50% Duty Cycle Half Bridge w. Diode Rect. or Synchr. Rectification (SR)
- ZVS → Compact / Efficient / Low EMI





@ $V_{in} = 380V$, $P_{out} = 10W$

 - Only Marginal Eff. Gain with Synchr. Rectification for Output Power Levels > 5W




Auxiliary Supply & Measurement Circuits

  
- Constant 50% Duty Cycle Half Bridge with Synchr. Rectification
- ZVS → Compact / Efficient / Low EMI ($f_s=465$ kHz)
- 10W Max. Output Power
- 390V...450V Input Operating Range
- 13.8V...16.8V DC Output in Full Inp. Voltage / Output Power Range
- 90% Efficiency @ P_{max}



■ 19mm x 24mm x 4.5mm (2cm³ Volume)

 


3D-CAD Construction →

 


Mechanical Construction (1)

 - Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$




 ■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$




Mechanical Construction (2)

 - Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$




 ■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$




Mechanical Construction (3)

 - Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$




 ■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$




Mechanical Construction (4)

 - Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$




 ■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$



Mechanical Construction (5)

 - Built to the Power Density Limit @ $\eta = 95\%$ / $T_c < 60^\circ\text{C}$



■ $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$ (14.8in^3) $\rightarrow 8.2\text{ kW/dm}^3$

Experimental Results

Hardware
Output Voltage/Input Current Quality
Thermal Behavior
Efficiency
EMI →

Little Box 1.0 - Prototype

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

- 8.2 kW/dm³
- 8.9cm x 8.8cm x 3.1cm
- 96,3% Efficiency @ 2kW
- $T_c=58^\circ\text{C}$ @ 2kW


- $\Delta u_{\text{DC,pp}} = 1.1\%$
- $\Delta i_{\text{DC,pp}} = 2.8\%$
- $\text{THD}+N_u = 2.6\%$
- $\text{THD}+N_I = 1.9\%$

- Compliant to All *Original* Specifications (!)

- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



★ 135 W/in³

 

Little Box 1.0 - Prototype

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

- 8.2 kW/dm³
- 8.9cm x 8.8cm x 3.1cm
- 96,3% Efficiency @ 2kW
- $T_c=58^\circ\text{C}$ @ 2kW


- $\Delta u_{DC} = 1.1\%$
- $\Delta i_{DC} = 2.8\%$
- $THD+N_U = 2.6\%$
- $THD+N_I = 1.9\%$

■ Compliant to All *Original* Specifications (!)

- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



★ 135 W/in³


 





Little Box 1.0 Measurement Results (1)

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

- Ohmic Load / 2kW

  


- Compliant to All Specifications

 


Little Box 1.0 Measurement Results (2)

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

 Buffer Cap Voltage (50V/div)
 Output Voltage (50V/div)
 Buffer Cap. Current (5A/div)
 Ind. Curr. Bridge Leg 1-1 (5A/div)



 
- Start-up and Shut-Down (No Load Operation)




Little Box 1.0 Measurement Results (3)

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

 Buffer Cap. Voltage (50V/div)
 Buffer Cap. Current (10A/div)
 Conv. Inp. Curr. (AC Coupl. 500mA/div)
 DC Link Voltage (AC Coupl. 1V/div)



 
- Stationary Operation @ 2kW Output Power




Little Box 1.0 Measurement Results (4)

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

 DC Link Voltage (50 V/div)
 Buffer Cap. Voltage (50 V/div)
 Buffer Cap. Current (10 A/div)
 Conv. Input Current (2 A/div)



 
- Transient Response for Load-Step of 0 Watt $\rightarrow$ 700 Watt



Little Box 1.0 Measurement Results (5)

- System Employing Active Ceralink 1- Φ Power Pulsation Buffer

 DC Link Voltage (20V/div)
 Buffer Cap. Voltage (20V/div)
 Buffer Cap. Current (5A/div)
 Conv. Input Current (1A/div)




- Transient Response for Load-Step of 700 Watt $\rightarrow$ 0 Watt




Little Box 1.0 Measurement Results (6)

 - System Employing Active Ceralink 1- Φ Power Pulsation Buffer




- Compliant to All Specifications

 


Little Box 1.0 - Measurement Results (6)


 
- $\text{CSPI} = 37 \text{ W}/(\text{dm}^3 \cdot \text{K})$
- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters



 
- $\text{CSPI}_{\text{eff}} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$ Considering Heat Distribution Elements
- Two-Side Cooling → Heatsink Temperature = 52°C @ 2kW Output Power (74 W Loss)



Little Box 1.0 Measurement Results (7)

  


■ Compliant to All Specifications

 


Little Box 1.0 Volume and Loss Distribution

Volume Distribution (240cm³)

 

Loss Distribution (75W)

 

- Large Heatsink (incl. Heat Conduction Layers)
- Large Losses in Power Fluctuation Buffer Capacitor (!)
- TCM Causes Relatively High Conduction & Switching Losses @ Low Power
- Relatively Low Switching Frequency @ High Power – Determines EMI Filter Volume

■ *Other Finalists*

Topologies
Switching Frequencies
Power Density / Efficiency Comparison →



Detailed Descriptions:
www.LittleBoxChallenge.com



Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

Note: Numbering of Teams is Arbitrary

  



- 70...300 W/in^3
- 35 kHz... 500kHz... 1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps or Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)



Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

Note: Numbering of Teams is Arbitrary

  

- (1) Virginia Tech
- (2) Schneider Electric
- (3) EPRI (Univ. of Tennessee)
- (4) Venderbosch
- (5) Energy Layer

- (6) ETH Zurich
- (7) Rompower
- (8) Tommasi-Bailly
- (9) Red Electric Devils
- (10) AHED


- (11) FH IISB
- (12) Univ. of Illinois
- (13) AMR
- (14) OKE
- (15) Cambridge Magnetics



Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

Note: Numbering of Teams is Arbitrary

 

- (1) Virginia Tech
- (2) Schneider Electric
- (3) EPRI (Univ. of Tennessee)
- (4) Venderbosch
- (5) Energy Layer
- (6) ETH Zurich
- (7) Rompower
- (8) Tommasi-Bailly
- (9) Red Electric Devils
- (10) AHED
- (11) FH IISB
- (12) Univ. of Illinois
- (13) AMR


- 70...300 W/in³
- 35 kHz... 500kHz... 1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps or Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)



Red Electric Devils

★ 145 W/in³

 - No Low-Frequ. Common-Mode Output Voltage Comp. → $i_{\text{gnd}} < 5\text{mA}$ (!)
- Buck-Type DC-Side Active Power Pulsation Filter (MLCC Cap. $< 150\mu\text{F}$, 200V_{pp})




- 2 x Interleaved Bridge Legs for Each Half-Bridge
- DM Inductors (L_1/L_2 and L_4/L_5) and Series Connected CM Inductor (L_7/L_8)
- Single Open-Loop Hall Sensor Outp. Curr. Measurement + Observer-Based Curr. Reconstruction



Red Electric Devils

★ 145 W/in³

 - No Low-Frequ. Common-Mode Output Voltage Comp. → $i_{\text{gnd}} < 5\text{mA}$ (!)
- Buck-Type DC-Side Active Power Pulsation Filter (MLCC Cap. $< 150\mu\text{F}$, 200V_{pp})





- DSP & CPLD Control
- GaN Systems @ ZVS (35kHz ... 240kHz)
- Shielded Multi-Stage EMI Filter @ DC Input & AC Output



Red Electric Devils

★ 145 W/in³

  - 3D Sandwich Assembly
- Single Ultra-Thin PCB – Power / Control / Aux.
- Honeycomb Cu-Heatsink & Al Oxide Inductor Cooling
- MLCC Storage Caps Rows Utilized as Heatsink “Fins” (1mm Gaps)





- 145 W/in³
- 95.4 % CEC Efficiency
- $i_{\text{gnd}} < 5\text{mA}$ (!)
- CSPI = 22.6 W/(dm³.K) - Heatsink & Axial Fan



Red Electric Devils

★ 145 W/in³

  - 3D Sandwich Assembly
- Single Ultra-Thin PCB – Power / Control / Aux.
- Honeycomb Cu-Heatsink & Al Oxide Inductor Cooling
- MMLC Storage Caps Rows Utilized as Heatsink “Fins” (1mm Gaps)





- 145 W/in³
- 95.4 % CEC Efficiency
- $i_{\text{gnd}} < 5\text{mA}$ (!)
- CSPI = 22.6 W/(dm³.K) - Heatsink & Axial Fan



Schneider Global Team
Electric

★ 100 W/in³

  - High Efficiency & Robustness Preferred → Larger Size
- DC-Side Series (!) Active Power Puls. Filter → Compensates 120Hz DC Link Volt. Variation



- $C_{DC} = 400\mu\text{F} / 450\text{V}$
- 1/5 Volume Comp. to only Bulk Capacitors
- $V_{dcinput}$ Ripple <10% (<30V_{pp}) @ Full Load

- Nanocrystalline CM Choke
- DC-Side & AC-Side EMI/RF Filter
- Q_{5...8} - T0247 SiC MOSFETs, 45kHz of Both Legs




Schneider Global Team


Electric

★ 100 W/in³

 
- High Efficiency & Robustness Preferred → Larger Size
- PWM of Both Legs of Output Full-Bridge → No Low. Freq. CM Output Voltage Comp.
- DC-Side Series (!) Active Power Puls. Filter → Compensates 120Hz DC Link Volt. Variation



 - $i_{\text{gnd}} < 25\text{mA}$ (!)
- 97.2 % CEC Efficiency



 
- $C_{\text{DC_RF}} = 2 \times 1500\mu\text{F}/25\text{V}$, $U_{\text{DC_RF}} = 15\text{V}$
- Only 52VA Processed Ripple Filter Power @ Rated Output (!)
- Q_1/Q_2 & Q_3/Q_4 - $R_{\text{ds,on}} = 2.2\text{m}\Omega$ MOSFETs (40V, 100A), w/o Heatsink, $f_s = 130\text{kHz}$ of Both Legs
- TI Piccolo DSP Control of Entire System / Open Loop Control of 120Hz Comp. Filter




ILLINOIS
UNIVERSITY OF ILLINOIS AT URBANA, CHAMPAIGN

Prof. Pilawa-Podgurski & Team

 - 7-Level Flying Capacitor Converter
- Series-Stacked Active Power Buffer



 
- 216 W/in³
- 100V GaN
- Integrated Switching Cell
- 720kHz Eff. Sw. Frequ. (7 x 120kHz)



ILLINOIS
UNIVERSITY OF ILLINOIS AT URBANA, CHAMPAIGN

Prof. Pilawa-Podgurski & Team

 
- 7-Level Flying Capacitor Converter
- Series-Stacked Active Power Buffer



- 216 W/in³
- 100V GaN
- Integrated Switching Cell
- 720kHz Eff. Sw. Frequ. (7 x 120kHz)

Y. Lei, C. Barth, S. Qin, W.-C. Liu, I. Moon, A. Stillwell, D. Chou, T. Foulkes, Z. Ye, Z. Liao and R.C.N. Pilawa-Podgurski "A 2 kW, Single-Phase, 7-Level, GaN Inverter with an Active Energy Buffer Achieving 216 W/in³ Power Density and 97.6% Peak Efficiency", IEEE Applied Power Electronics Conference, Long Beach, CA, 2016

 ■ ***Competition
Conclusions***
*Key Technologies
Power Density Limit* →



Google Little Box Challenge Summary

■ Overall

- Engineering “Jewels”
- No (Fundamentally) New Approach / Topology
- Passives & 3D-Packaging are Finally Defining the Power Density
- Careful Heat Management (Adv. Heat Sink, Heat Distrib., 2-Side Integr. Cooling, etc.)
- Careful Mechanical Design (3D-CAD, Single PCB, Avoid Connectors, etc.)
- Clear Power Density / Efficiency Trade-Off

■ 200W/in³ (12kW/dm³) Achievable


- $f_s < 150\text{kHz}$ (Constant)
- SiC (Not GaN)
- ZVS (Partial, i.e. Around $i=0$)
- Full-Bridge Output Stage
- Active Power Pulsation Buffer (Buck-Type, X6S Cap.)
- Conv. EMI Filter Structure
- Multi-Airgap Litz Wire Inductors
- DSP Only (No FPGA)

100+ Teams
3 Members / Team, 1 Year
300 Man-Years
3300 USD / Man-Year



Optimization & Advanced Analysis



 
Adv. Modulation / Circuit Concepts
Measurement of Buffer Cap. Performance
Measurement of GaN ZVS & On-State Losses
Measurement of Multi-Airgap Core Losses




Eff. Optimal f_s -Modulation



   - TCM $\rightarrow$ ZVS but Large Current Ripple & Wide Frequency Variation
- PWM $\rightarrow$ Const. Sw. Frequency but Hard Sw. @ Current Maximum
- Opt. Combination of TCM & PWM $\rightarrow$ Optim. Frequ. Variation Over Output Period
- Exp. Determination of Loss-Opt. Sw. Frequency f_{OFM} Considering DC/DC Conv. Stage





 
- DC/AC Properties Calculated Assuming Local DC/DC Operation
- Loss-Optimal Local Sw. Frequ. f_{OFM} for Given V_{DC} & Local i_o & v_{CO}




Eff. Optimal f_s -Modulation



   - TCM $\rightarrow$ ZVS but Large Current Ripple & Wide Frequency Variation
- PWM $\rightarrow$ Const. Sw. Frequency but Hard Sw. @ Current Maximum
- Opt. Combination of TCM & PWM $\rightarrow$ Optim. Frequ. Variation Over Output Period
- Exp. Determination of Loss-Opt. Sw. Frequency f_{OFM} Considering DC/DC Conv. Stage




 - DC/AC Properties Calculated Assuming Local DC/DC Operation
- Loss-Optimal Local Sw. Frequ. f_{OFM} for Given V_{DC} & Local i_o & v_{C0}



Eff. Optimal f_s -Modulation

 
- Resulting Time-Dependency of Optimal Sw. Frequ. & Power Loss
- Comparison with 140 kHz Const. Sw. Frequency PWM



- Higher Average Switching Frequency f_s @ Light Loads
- Reduction of f_s @ Mains Voltage Peak (for Ohmic Load) for Sustaining ZVS

Eff. Optimal f_s -Modulation

 
- Optimal Inductor Current Envelope for Diff. Output Power Levels



- Higher Average Switching Frequency f_s @ Light Loads
- Reduction of f_s @ Mains Voltage Peak (for Ohmic Load) for Sustaining ZVS



Measurements

 Buffer Capacitor Losses / Cap.
Power Semicond. ZVS & On-State Losses
Ferrite Multi-Airgap Core Losses



CeraLink vs. X6S

 
 
- Electrolytic Capacitors → Limited by Lifetime Current Limit
- X6S MLCC, 2.2 μ F, 450 V Class II → Highest Energy Density but Low Cap. @ High DC Bias
- CeraLink™, 1 μ F / 2 μ F, 650 V → PLZT Ceramic, High Cap. @ High DC Bias
- CeraLink™ Allows Op. @ 125°C → Very Low ESR @ High Frequencies




- PPB Design Optimiz. Requires Large-Signal Capacitance and Power Loss Data in All Operating Points

CeraLink vs. X6S

  - Electrolytic Capacitors → Limited by Lifetime Current Limit
- X6S MLCC, 2.2 μ F, 450 V Class II → Highest Energy Density but Low Cap. @ High DC Bias
- CeraLink™, 1 μ F / 2 μ F, 650 V → PLZT Ceramic, High Cap. @ High DC Bias
- CeraLink™ Allows Op. @ 125°C → Very Low ESR @ High Frequencies



 ■ Experimental Setup for Generation of DC Bias & Superimposed AC Voltage





CeraLink vs. X6S



- Variation of DC Bias and Superimposed AC Voltage @ 60°C Operating Temp.

✗ Designed Op. Point

EPCOS/TDK
CeraLink™ 2μF, 600V

  



TDK Class II
X6S MLCC 2.2μF, 450V

  

- PPB Design Optimiz. Requires Large-Signal Capacitance and Power Loss Data in All Operating Points


 
Measurement of GaN ZVS & On-State Losses →



 


Analysis of GaN Power Transistor ZVS Losses

  - Little-Box 1.0 Experiments Indicated *Residual ZVS Losses of GaN Power Transistors*
- Losses Cannot be Explained by Remaining i_D , u_{DS} Overlap / Non-Ideal Gate Drive etc.





 - Potentially Large Measurement Error for Electric Double-Pulse Sw. Loss Measurement
- Accuracy only Guaranteed by **Direct Loss Measurement** → **Calorimetric Approach**




Analysis of GaN Power Transistor ZVS Losses

  - Little-Box 1.0 Experiments Indicated *Residual ZVS Losses* of GaN Power Transistors
- Losses Cannot be Explained by Remaining i_D , u_{DS} Overlap / Non-Ideal Gate Drive






 - Potentially Large Measurement Error for Electrical Double-Pulse Sw. Loss Measurement
- Accuracy only Guaranteed by Direct Loss Measurement $\rightarrow$ Calorimetric Approach




Calorimetric Measurement of ZVS Losses

   - “Inductor in the Box” → Accurate DC Inp. & Outp. Power Measurement, Subtr. on Ind. Losses
- “Bridge Leg in the Box” → Direct Measurement of the Sum of Cond. & Sw. Losses






 - “Bridge Leg in the Box” & Fast Measurement by $C_{th} \cdot \Delta T / \Delta t$ Evaluation
- DC/DC Operation @ High Sw. Frequency for Large Ratio of Sw. and Conduction Losses
- Subtraction of the Cond. Losses from Datasheet or Dir. Measurement




Calorimetric Measurement of ZVS Losses

   - “Bridge Leg in the Box” & Fast Measurement by $C_{th} \cdot \Delta T / \Delta t$ Evaluation
- Subtraction of the Cond. Losses from Datasheet or Direct Measurement
- DC/DC Operation @ High Sw. Frequency for Large Ratio of Sw. and Conduction Losses





 - Isolated Temp. Measurement with Optical Fiber (GaAs Crystal) Instead of Thermocouple
- Calibration by On-State of T_1 and T_2 & DC Current Operation / DC Power Loss Measurement




Calibration of “Bridge Leg in the Box” Setup

  - Calibration by On-State of T_1 and T_2 & DC Current Operation / DC Power Loss Measurement
- Identification of Thermal Cap. C_{th} and Thermal Resistance R_{th}




 - DC Power Loss Measurement Ensures High Accuracy
- Thermal Behavior for Short Measurement Times Mainly Determined by C_{th}



Accurate On-State Voltage Measurement


 
- Clamping Diode for Limiting the On-State Voltage Measurement (OVM) to 2V
- Subtraction of the SiC Diode Forward Voltage Drop for High Accuracy (2mV)




- Only 50ns Blanking Time – OVM Circuit Can also be Used for Dynamic $R_{DS,on}$ Measurement

Accurate On-State Voltage Measurement

  - **Clamping Diode for Limiting the On-State Voltage Measurement (OVM) to 2V**
- **Subtraction of the SiC Diode Forward Voltage Drop for High Accuracy (2mV)**






 - Only 50ns Blanking Time – OVM Circuit Can also be Used for Dynamic $R_{DS(on)}$ Measurement




ZVS Loss Measurement Results (1)

   - Measurement of Energy Loss per Switch and Switching Period
- GaN Enhancement Mode Power Transistor (600V, 70mΩ@25°C)
- Antiparallel CREE SiC Schottky Freewheeling Diode (600V, 3.3A)





 - Switching w/ and w/o 100pF Parallel Low-Loss SMD Multilayer Ceramic Chip Capacitor (450V)
- dv/dt Measured in 10%...90% of Turn-off Voltage, Behavior @ at Low dv/dt Still to be Clarified




ZVS Loss Measurement Results (2)

  - Analysis of a *Permanently-Off Half-Bridge* Excited with Switch Node Voltage
- Measurement of Energy Loss per Switch and Switching Period





 - Heating Indicates Losses in the Permanently-Off Devices
- Losses Comparable to the Losses of the Switching Half Bridge for Same dv/dt




ZVS Loss Measurement Results (2)

  
- Analysis of a *Permanently-Off Half-Bridge* Excited with Switch Node Voltage
- Measurement of Energy Loss per Switch and Switching Period



- Heating Indicates Losses in the Permanently-Off Devices
- Losses Comparable to the Losses of the Switching Half Bridge for Same dv/dt



 
Measurement of Ferrite Multi-Airgap Core "Mystery" Losses



 

Multi-Airgap Inductor

   - Ferrite E-Core with **50 x 0.3mm Thick Stacked Plates** as Center Post
- Power Loss of TCM Inductors Sign. Higher than Expected




- Analysis by **Fraunhofer IZM** Shows Up to Factor 10 High Core Losses (!) → “Mystery” Losses



– Machining Increases Core Losses


- 1964 - E. Stern & D. Temme

 → Machining / Compressive Stress Changes BH-Loop of NiZn Ferrite




- 1974 - J. Knowles, E. Snelling

 → Compressive Stress Incr. Loss Fact., Reduces μ ,



- 1984 - E. Klokholm & H. Wolfe

 → 40 μm Magn. Dead Surface Layer of MnZn Ferrite




- 1987 - S. Chandrasekar et al.

→ Lapping Causes Greater Residual Stress than Grinding

Ferrite Machining Process


- Cutting of Thin Plates from Ferrite Rod with Diamond Saw
- Abrasive Machining Introduces Mech. Stress into Surface

Diamond Blade
5000rpm

 


Machined
Core


SEM Image of
Machined MnZn
Ferrite (3F4)

 

laboratory for
lmm
nanometallurgy

 

 - Ferrite Properties in Surface Altered → Increase of Loss Factor





Subsurface Condition of Machined Ferrite




Materials Science and Technology

  - **Focused Ion Beam (FIB) Cut into Ferrite (3F4) Sample & Scanning Electron Microscopy (SEM)**
- **Polishing of Surface with Grain Sizes 2400 SiC → 4000 SiC → Colloidal Silica SiO_2**




 - **Polishing Removes 500µm of Surface** → **Bulk Material Exposed**
- **Bulk Ferrite also Exhibits Cavities** → **Result of (Imperfect) Sintering Process**




Thermometric Surface Loss Measurement

 - Impression of Homogeneous Sin. Flux Density of Desired Ampl. / Frequ.
- Cap. Series Comp. for Lowering Impedance @ High Frequencies
- Measurement of *Transient Temp. Change* → Calc. of Losses






 - Temperature Rise of $\Delta T = 1.5^{\circ} \dots 5^{\circ}\text{C}$ Sufficient (Accuracy $\pm 0.2^{\circ}\text{C}$), Fast Measurement (!)




Test Fixture / Magnetic Circuit

   - **E-Type Fixture** for Swift Installation of Diff. Samples (7mm x 6.4mm x 21.6mm)
- **FEM Optimiz. of Dimensions** – Large Core Cross Section / Tapered Outer Limbs






 - **Therm. Insul. & Airgap Lattice Ensure Low Heat Flux to Ambient**
- **Measurement of Temp. Increase Over Time Allows to Verify Homog. Flux Density in Sample**




Identification of Therm. Parameters R_{th} , C_{th}

   - DC Current Impressed in Ferrite, Voltage Control for Const. Power Dissipation as $R_{DC}=R_{DC}(Temp.)$
- Temperature Response of Sample Recorded (FLIR A655sc W with Close-Up Lens)
- Emissivity of Ferrite Determined Using Heat Plate ($\varepsilon=0.86$)




 
- $R_{th} = 37.8 \text{ K/W}$ Can be Neglected
- Obtained Parameter $C_{th} = 3.83 \text{ J/K}$ Close to C_{th} Calc. Based on Vendor Data ($C_{th} = 3.6 \text{ J/K}$)



Surface Loss Measurement Principle



  
- Hypothesis: Core Loss Density in Surface Layer Higher than in Bulk
- Thinner Plates $\rightarrow$ Higher Average Losses / Faster Temp. Rise
- Stacking of Plates Does NOT Affect Temperature Rise (!)



- Surface Loss Density Can be Directly Calc. from Mat. Parameters / Geometry & Δt_A and Δt_B

Temperature Rise Recording

 - Comparison of Solid 3F4 Sample (1 x 21.6mm) and Stacked Plates Sample (7 x 3mm)
- Sinusoidal Excitation *100mT / 400kHz*




3F4 Solid Sample / 21.6mm



7 Plates 3F4 / 3mm





 - Thermal Image shown *25 Seconds After Turn-On* of Magnetic Excitation




Measurement Results – Bulk Losses

  - Comparison of Measurement Results and Datasheet Values, 3F4 @ 25°C
- Measurement Error Approx. $\pm 10\%$ (Worst Case)



 - Good Agreement with Datasheet Values / Vendor Steinmetz Parameters





Measurement Results – Surface Losses


- Measurement Error Approx. $\pm 25\%$ (Worst Case)
- Error Determined by Meas. Time & Temp. Reading Accuracy


  
$$p_{Surf} = 0.0615 \times \left(\frac{f}{1\text{Hz}}\right)^{1.13} \times \left(\frac{\hat{B}}{1\text{T}}\right)^{3.47} \left(\frac{\text{mW}}{\text{cm}^2}\right)$$






 - Comp. of Steinmetz Parameters of Surface Losses & Bulk Losses $BS > B$, $aS < a$




“Critical Thickness” of Ferrite Plates

   - “Critical Thickness” Reached for **Equal Losses in Bulk & Surface**
- Critical Plate Thickness is **INDEPENDENT** of Cross Section (!)



- Dependence on Flux Density Ampl. & Frequency !
- Dependence on Material / Machining Process / Power Processing Treatment

Little Box 2.0

 



240 W/in³

DC/ | AC | Converter + Unfolder
PWM vs. TCM Optimization
 η p-Pareto Limits
Hardware Prototype
Experimental Results





Little Box 2.0 – New Converter Topology (1)

  - **Alternative Converter Topology** → Only Single HF Bridge Leg + 60Hz-Unfolder
- **DC/AC - Buck Converter + Full-Bridge Unfolder** OR **HF Half-Bridge & Half-Bridge Unfolder**



  - v_{C0} Easy to Generate/Control
- Higher Conduction Losses Due to FB-Unfolder
- Lower CM-Noise (DC & $n \times 120\text{Hz}$ -Comp.)
- $C_{CM}=700\text{nF}$ Allowed for 50mA Gnd Current




- v_{AC1} More Difficult to Generate/Control
- Lower Conduction Losses
- Higher CM-Noise (DC and $n \times 120\text{Hz}$ -Comp.)
- $C_{CM}=150\text{nF}$ Allowed for 50mA Gnd Current



Little Box 2.0 – New Converter Topology (2)

- **Alternative Converter Topology** - DC/ | AC | - Buck Converter + Unfolder
- **60Hz-Unfolder** (Temporary PWM for Ensuring Continuous Current Control)
- **TCM or PWM** of DC/ | AC | - Buck-Converter


 


- **Full Optimization** of All Converter Options for **Real Switches** / X6S Power Pulsation Buffer



Little Box 2.0 – Multi-Objective Optimization

  
- **DC/AC - Buck Converter (Single Bridge Leg) + Unfolder & PWM Shows Best Performance**
- **Full-Bridge Would Employ 2 Switching Bridge Legs - Larger Volume & Losses**
- **Interleaving Not Advantageous – Lower Heatsink Vol. but Larger Total Vol. of Switches and Inductors**



■ **$\rho = 250\text{W/in}^3$ (15kW/dm³) @ $\eta = 98\%$ Efficiency Achievable for Full Optimization**



Little Box 2.0 – Control Structure

 

- Each Stage (Buck & Unfolder) Controlled with Cascaded Current and Voltage Loop
- Without Switching of Unfolder Control Like for Conventional Boost PFC Rectifier


*3D-CAD Construction
of the Final System*



240 W/in³



 
Little Box 2.0 – Final Mechanical Construction (1)



■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2 in³) → 14.8 kW/dm³ (243 W/in³)



 
Little Box 2.0 – Final Mechanical Construction (2)



■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2 in³) → 14.8 kW/dm³ (243 W/in³)



 
Little Box 2.0 – Final Mechanical Construction (3)



■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2 in³) → 14.8 kW/dm³ (243 W/in³)



 
Little Box 2.0 – Final Mechanical Construction (4)



■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)



 Little Box 2.0 – Final Mechanical Construction (5)



■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2in³) → 14.8 kW/dm³ (243 W/in³)



Experimental Results

*Hardware Prototype
Output Voltage/Input Current Quality
Steady-State / Step-Response Waveforms
Efficiency
EMI Measurements
Operating Temperature* →




Little Box 2.0 -- Demonstrator

★ 240 W/in³

Output Filter

Inductors
(Buck-Stage &
Unfolder)

Power Board
Control Board

 

PPB Capacitor

Heat Sink + Fans

■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2 in³) → 14.8 kW/dm³ (243 W/in³)




Little Box 2.0 -- Demonstrator

★ 240 W/in³

PPB Capacitor

Heat Sink + Fans

 

PPB Capacitor

Inductors
(Buck-Stage &
Unfolder)



Power Board

Control Board

■ 60 mm x 50 mm x 45 mm = 135 cm³ (8.2 in³) → 14.8 kW/dm³ (243 W/in³)

Analysis of DC/ | AC | -Buck Converter & Unfolder

  - Voltage Zero Crossing Behavior With (Right) & Without (Left) Switching of Unfolder




Output Voltage (200V/div)
Output Current (10A/div)
Buck Inductor Current (10A/div)
Unfolder Output Voltage (200V/div)

- Output Voltage & Current Fully Controlled Around Voltage Zero Crossings
- Slope of Buck Conv. Outp. Curr. can be Decreased – Adv. for React. Loads (No Step-Change of DC Curr.)




Little Box 2.0 – Measured Waveforms (1)


- DC/|AC| Buck-Stage Output Voltage & Inductor Current

 

■ Resistive Load

 

■ Inductive Load

 


■ Capacitive Load



Little Box 2.0 – Measured Waveforms (2)

- Step-Response Waveforms for 600 W Load Step

 AC current (5 A/div)
AC voltage (200 V/div)
Buck Inductor Current (10 A/div)




- Good Performance of Output Voltage Controller



Little Box 2.0 – Measured Waveforms (3)

 - Step-Response Waveforms for 600 W Load Step
- DC-Side and PPB Waveforms




- Transients Settle Within 50 ms



Little Box 2.0 – Efficiency Measurements (1)

 - Performance of LB 2.0 with X6S Power Pulsation Buffer
- 140 kHz PWM
- High Speed Fan for Improved Cooling




 - 97.4 Peak Efficiency @ 2kW
- 96.12 % CEC Efficiency with Conv. Fans



Little Box 2.0 – Efficiency Measurements (2)

- Performance of X6S Power Pulsation Buffer
- Performance of Inverter with Electrolytic Capacitors




- 99.1% Peak Efficiency of PPB
- ≈98% Peak Efficiency of Inverter




Little Box 2.0 – Thermal Management

- Steady-State Operating Temperature @ 2 kW
- CSPI = 53 W/(dm³.K)

Power Stage

 



Control PCB

 


- 60°C - 65°C of Exposed Surfaces
- 85°C Winding Temperature
- CSPI = 37.5 W/(dm³.K) Including Air Duct



Little Box 2.0 – EMI Measurements

  


 - Compliant to FCC Part 15 B EMI Limits
- Compliant to Revised 50 mA Ground Current Limit




Little Box Comparison - Volume and Loss Distribution


 
■ Cooling
 ■ Housing
 ■ Others
 ■ Power Transistor
 ■ Output Filter
 ■ Electronics
 ■ Inductor
 ■ Buffer Capacitor




Tot. Volume: 240.5 cm³

 

Tot. Losses: 74.4 W

  

Tot. Volume: 137.9 cm³

 


Tot. Losses: 56.4 W




Finalists - Performance Overview Revisited

 - 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities



- 70...300 W/in^3
- 35 kHz... 500kHz... 1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps of Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)

 

Source: whiskeybehavior.info

Overall Summary



Performance Limits / Future Requirements

- 220...250W/in³ for Two-Level Bridge Leg + Unfolder
- 250...300W/in³ for Highly Integrated Multi-Level Approach
- Isol. Distance Requirements Difficult to Fulfill
- Fulfilling Industrial Inp. Overvoltage Requirem. would Signific. Reduce Power Density
- Low Frequency (20kHz...120kHz) SiC vs. HF (200kHz...1.2MHz) GaN
- Multi-Cell Concepts for LV Si (or GaN) vs. Two-Level SiC (or GaN)
- New Integr. Control Circuits and $i=0$ Detection for Sw. Frequency >1MHz
- Integrated Gate Drivers & Switching Cells
- High Frequency Low Loss Magnetic Materials
- High Bandwidth Low-Volume Current Sensors
- Low Loss Ceramic Capacitors Tolerating Large AC Ripple
- Passives w. Integr. Heat Management and Sensors
- 3D Packaging
- New U-I-Probes Required for Ultra-Compact Conv. R&D
- Specific Systems for Testing → Devices Equipped with Integr. Measurement Functions
- Convergence of Sim. & Measur. Tools → Next Gen. Oscilloscope
- New Multi-Obj. Multi-Domain Simulation/Optim. Tools

References

ETH Zurich
Other Finalists
Non-Finalists
General

► Publications of ETH Zurich

D. Neumayr, D. Bortis, E. Hatipoglu, J. W. Kolar, G. Deboy, *New Efficiency Optimal Frequency Modulation (OFM) for High Power Density DC/AC Converter Systems*, to be published in Proc. of the International Future Energy Electronics Conference (IFEEC-ECCE Asia), Kaohsiung, Taiwan, June 3-7, 2017.

D. Neumayr, M. Guacci, D. Bortis, J. W. Kolar, *Novel Temperature-Gradient based Calorimetric Measurement Principle to Obtain Soft-Switching Benchmark of GaN and SiC Power Devices*, Proceedings of the 29th IEEE International Symposium on Power Semiconductor Devices and ICs (ISPSD), Sapporo, Japan, May 28 - June 1, 2017.

D. Rothmund, D. Bortis, J. Huber, D. Biadene, J. W. Kolar, *10kV SiC-Based Bidirectional Soft-Switching Single-Phase AC/DC Converter for Medium-Voltage Solid-State Transformer Applications*, Proceedings of the 8th International Symposium on Power Electronics for Distributed Generation Systems (PEDG), Florianopolis, Brazil, April 17-20, 2017.

M. Guacci, D. Neumayr, D. Bortis, J. W. Kolar, G. Deboy, *Analysis and Design of a Multi-Tapped High-Frequency Auto-Transformer Based Inverter System*, Proceedings of the 17th IEEE Workshop on Control and Modeling for Power Electronics (COMPEL), Trondheim, Norway, June 27-30, 2016.

D. Neumayr, D. Bortis, J. W. Kolar, *Comprehensive Large-Signal Performance Analysis of Ceramic Capacitors for Power Pulsation Buffers*, Proceedings of the 17th IEEE Workshop on Control and Modeling for Power Electronics (COMPEL), Trondheim, Norway, June 27-30, 2016.

D. Bortis, D. Neumayr, J. W. Kolar, *η -Pareto Optimization and Comparative Evaluation of Inverter Concepts considered for the GOOGLE Little Box Challenge*, Proceedings of the 17th IEEE Workshop on Control and Modeling for Power Electronics (COMPEL), Trondheim, Norway, June 27-30, 2016.

J. W. Kolar, D. Bortis, D. Neumayr, *The Ideal Switch is Not Enough*, Proceedings of the 28th IEEE International Symposium on Power Semiconductor Devices and ICs (ISPSD), Prague, Czech Republic, June 12-16, 2016.

D. Bortis, O. Knecht, D. Neumayr, J. W. Kolar, *Comprehensive Evaluation of GaN GIT in Low- and High-Frequency Bridge Leg Applications*, Proceedings of the 8th International Power Electronics and Motion Control Conference (IPEMC-ECCE Asia), Hefei, China, May 22-25, 2016.

D. Neumayr, D. Bortis, J. W. Kolar, *Ultra-Compact Power Pulsation Buffer for Single-Phase DC/AC Converter Systems*, Proceedings of the 8th International Power Electronics and Motion Control Conference (IPEMC-ECCE Asia), Hefei, China, May 22-25, 2016.

► Publications of Other Finalists

F. Frebel, O. Bomboir, P. Bleus, D. Rixhon, *Transformer-less 2kW Non-Isolated 400VDC/230VAC Single-Stage Micro-Inverter*, Proc. of the IEEE Intern. Telecommunications Energy Conference (INTELEC), 2016.

R. Ghosh, M. Srikanth, D. Klikic, M. Wang, R. Mitova, *Novel Active Ripple Filtering Schemes used in the Little Box Inverter*, to be published in Proc. of the Intern. Conf. on Power Conv. and Intelligent Motion (PCIM Europe), 2017.

I. Zhang, R. Born, X. Zhao, J.S. Lai, *A High Efficiency Inverter Design for Google Little Box Challenge*, Proc. of the IEEE Workshop on Wide Bandgap Power Devices and Applications (WiPDA), 2015.

C. Zhao, B. Trento, L. Jiang, E. A. Jones, B. Liu, Z. Zhang, D. Costinett, F. Wang, L. M. Tolbert, J. F. Jansen, R. Kress, R. Langley, *Design and Implementation of GaN-Based 100-kHz 102-W/in³ Single-Phase Inverter*, IEEE Journal of Emerging and Selected Topics in Power Electronics, vol. 4, no. 3, pp. 824–840.

S. Qin, Y. Lei, C. Barth, W. C. Liu, R. C. N. Pilawa-Podgurski, *A High Power Density Series-Stacked Energy Buffer for Power Pulsation Decoupling in Single-Phase Converters*, to be published in the IEEE Transactions on Power Electronics.

T. Menrath, S. Matlok, S. Endres, S. Zelter, B. Eckardt, *Mechatronic Design of 2kW SiC DC/AC Converter with 200W/in³*, to be published in Proc. of the Intern. Conf. on Power Conv. and Intelligent Motion (PCIM Europe), 2017.

► General Publications

Solaredge Technologies Ltd., *Multi-level Inverter*, European Patent Application EP 2779410A2 (Inventor: I. Yoscovitch), filed March 14, 2014, published Sept. 17, 2014.

C. P. Henze, H. C. Martin, D. W. Parsley, *Zero-voltage Switching in High Frequency Power Converters using Pulse Width Modulation*, Proc. of the IEEE Applied Power Electronics Conference (APEC), 1988, pp. 33-40.

R. W. Erickson, A. P. Rogers, *A Microinverter for Building-Integrated Photovoltaics*, Proc. of the IEEE Applied Power Electronics Conference (APEC), 2009, pp. 911-917.

M. Pahlevaninezhad, P. Jain, *Zero Voltage Switching Interleaved Boost AC/DC Converter*, US Patent US 8723487B2 (May 13, 2014), filed March 9, 2012.

J. E. Knowles, *The Origin of Increase in Magnetic Losses Induced by Machining Ferrites*, IEEE Trans. on Magnetics, vol. 11, pp. 1–5, 1975.

K. A. Kim, Y. C. Liu, M. C. Chen, H. J. Chiu, *Opening the Box: Survey of High Power Density Inverter Techniques From the Little Box Challenge*, CPSS Transactions on Power Electronics and Applications, vol. 2, no. 2, pp. 131-139, 2017.

Biographies of the Authors

kolar@lem.ee.ethz.ch
neumayr@lem.ee.ethz.ch
bortis@lem.ee.ethz.ch



Johann W. Kolar (F'10) received his Ph.D. degree (summa cum laude) from the Vienna University of Technology, Austria. He is currently a Full Professor and the Head of the Power Electronic Systems Laboratory at the Swiss Federal Institute of Technology (ETH) Zurich. He has proposed numerous novel PWM converter topologies, and modulation and control concepts and has supervised over 60 Ph.D. students. He has published over 750 scientific papers in international journals and conference proceedings, 3 book chapters, and has filed more than 140 patents. He has presented over 20 educational seminars at leading international conferences, has served as IEEE PELS Distinguished Lecturer from 2012 through 2016, and has received 25 IEEE Transactions and Conference Prize Paper Awards, the 2014 IEEE Power Electronics Society R. David Middlebrook Achievement Award, the 2016 IEEE William E. Newell Power Electronics Award, the 2016 IEEE PEMC Council Award, and the ETH Zurich Golden Owl Award for excellence in teaching. He has initiated and/or is the founder of 4 ETH Spin-off companies. The focus of his current research is on ultra-compact and ultra-efficient SiC and GaN converter systems, wireless power transfer, Solid-State Transformers, Power Supplies on Chip, as well as ultra-high speed and ultra-light weight drives, bearingless motors, and energy harvesting.



Dominik Neumayr (SM10) started his academic education at the University of Applied Sciences (FH) for Automation Engineering in Wels and received the Dipl.-Ing. (FH) degree in 2008. He was with the Center for Advanced Power Systems (CAPS) in Tallahassee/Florida working on Power/Controller Hardware-in-the-Loop simulations and control systems design for AC/DC/AC PEBB based converter systems from ABB. He continued his academic education at the Swiss Federal Institute of Technology in Zurich (ETH Zurich) and received the M.Sc. degrees in electrical engineering and information technology in 2015. Since spring 2015 he is a PhD student at the Power Electronic Systems (PES) Laboratory, ETH Zurich. His current research focuses on ultra-high power density converter systems.



Dominik Bortis (M'08) received the M.Sc. degree in electrical engineering and the Ph.D. degree from the Swiss Federal Institute of Technology (ETH) Zurich, Switzerland, in 2005 and 2008, respectively. In May 2005, he joined the Power Electronic Systems Laboratory (PES), ETH Zurich, as a Ph.D. student. From 2008 to 2011, he has been a Postdoctoral Fellow and from 2011 to 2016 a Research Associate with PES, co-supervising Ph.D. students and leading industry research projects. Since January 2016 Dr. Bortis is heading the newly established research group Advanced Mechatronic Systems at PES.

Thank You !

