**ETH** zürich



### Monolithic Bi-Directional Switches — Opening New Horizons in Power Electronics

Johann W. Kolar et al.



Swiss Federal Institute of Technology (ETH) Zurich Power Electronic Systems Laboratory www.pes.ee.ethz.ch

Sept. 16, 2022







### Monolithic Bi-Directional Switches — Opening New Horizons in Power Electronics

Johann W. Kolar | Jonas E. Huber | Daifei Zhang



Swiss Federal Institute of Technology (ETH) Zurich Power Electronic Systems Laboratory www.pes.ee.ethz.ch

Sept. 16, 2022





#### Monolithic Bi-Directional Switches — Opening New Horizons in Power Electronics

**Abstract** — Power Electronics is a key technology for all forms of generation and utilization of electric power in modern societies, ranging from renewable energy systems and highly diverse power supply applications including fast-charging of EVs and hyperscale datacenters to variable frequency drives for industry automation.

The progress in the area has been driven over the past 40 years by new power semiconductor device concepts and corresponding circuit topologies with a focus on voltage-source converter (VSC) structures and/or the application of switching elements limited to unipolar voltage blocking capability. With reference to recently intensifying R&D activities on two-gate monolithic bi-directional switches (M-BDSs) featuring bipolar voltage blocking and bidirectional current control capability, the talk contemplates on the potential advantages of M-BDSs for the realization of ultra-compact three-phase PFC rectifier systems and next generation inverter systems with low motor insulation stress. In this context the performance gain achievable utilizing three-level T-type VSC topologies and the unique features of current-source converter approaches – today solely employed in thyristor-based high-power medium-voltage motor drives - and AC/AC matrix converter concepts over state-of-the-art VSC systems are highlighted.

Final considerations are on the paramount importance of advanced integration and packaging technologies for a next disruptive performance improvement of power electronics systems.







## **Outline**



#### ► Introduction


→ 3-Φ AC/DC Grid Interfaces
 → 3-Φ Motor Drive Inverters
 → SiC/GaN M-BDS R&D Activities

► Outlook

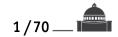M. Guacci M. Haider F. Krismer J. Miniböck N. Nain L. Schrittwieser F. Vollmaier **Acknowledgement** G. Zulauf








# **Driving Applications**


**Global** Megatrends  $\rightarrow$  Industry Automation | Renewable Energy | Sustainable Mobility | Urbanization etc.

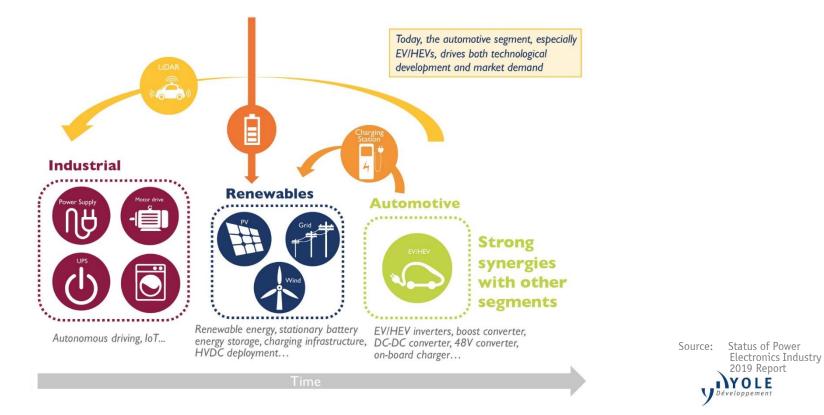

● Clean Energy Transition → "All-Electric" Society




**ETH** zürich

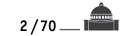


#### **Power Electronic Systems** Laboratory
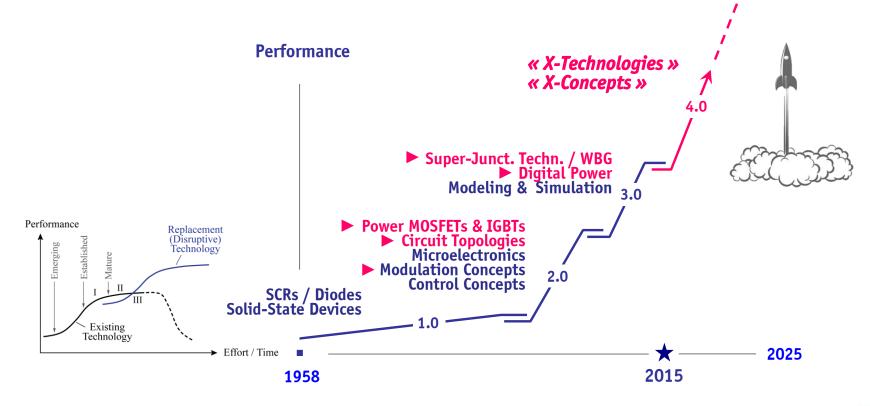
### **S-Curve of Power Electronics**

- « X-Technologies » / "Moon-Shot" Technologies
   « X-Concepts » → Full Utilization of Basic Scaling Laws & X-Technologies
   Power Electronics 1.0 → Power Electronics 4.0
- 2...5...10x Improvement NOT Only 10% !



**ETH** zürich

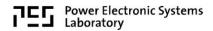







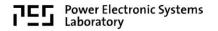Renewable Energy Digitalization Sustainable Mobility Industry Automation Etc.









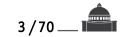
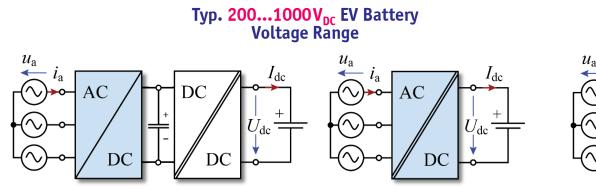
## $3-\Phi$ AC/DC Converter Application Areas

- Electric Vehicle Battery Charging
- Datacenter Power Supply
- Renewable Energy Applications



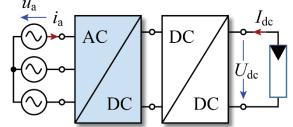


MPP Tracking in 60...90% of Max. Open Circuit Voltage

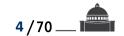320...530V<sub>rms</sub> Line-to-Line

- Non-Isolated OR Isolated Output
- Wide AC Input &/OR DC Output Voltage Range
- Unidirectional OR Bidirectional Power Transfer








#### **Power Electronic Systems** Laboratory
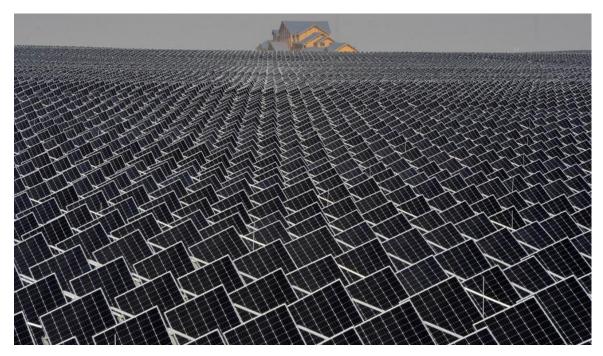
### **Renewable Energy – Photovoltaics**

- 3-Φ DC/AC Mains Interface
   Lower Costs / Higher Efficiency / Lower Weight
   20 Years Lifetime / Life-Cycle Assessment





Source: REUTERS/Stringer

**Globally Installed** PV Capacity Forecasted to 2.7 Terawatt by 2030 (IEA)



**ETH** zürich

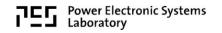

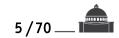

### **Digitalization** — **Datacenters**

- Medium-Voltage 
   Power-Supplies-on-Chip (0.6 ... 0.8V) Power Conversion

   Trend Towards 380V DC Power Distribution
- Short Innovation Cycles
- Modularity / Scalability

Server-Farms up to 450 MW 99.9999%/<30s/a \$1.0 Mio./Outage


> Since 2006 Running Costs > Initial Costs



- Higher Availability
- Higher Efficiency
   Higher Power Density
- Lower Costs




**ETH** zürich

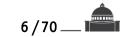

### History of 3- $\Phi$ Diode Bridge Rectifiers

- L. Kallir @ Techn. Hochschule Wien (25. Dec. 1898)
- Extension of 1-⊕ Wilke/Pollak/Graetz Rectifier


### Zeitschrift für Elektrotechnik.

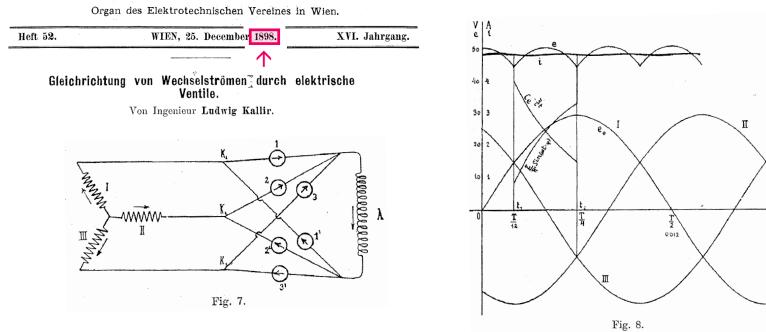

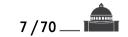• Electrolytic Cells, Sparc Gaps, Discharge Tubes as "Valves"








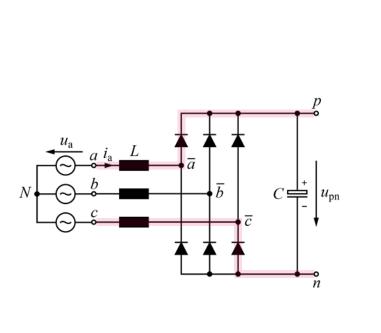
### **3-Diode Bridge Rectifier**

- Conduction States Defined by Line-to-Line Mains Voltages Intervals with Zero Phase Current / LF Harmonics No Output Voltage Control




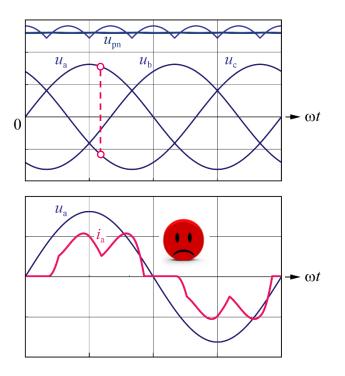

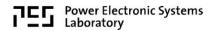→ Active Mains Current Shaping / Simultaneous Current Flow in All Phases
















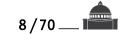
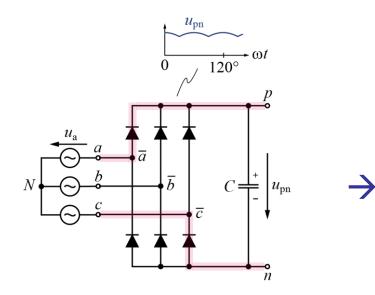
### **Integrated Active Filter (IAF) PFC Rectifier**

- **3<sup>rd</sup> Harmonic Current Injection** into Phase with Lowest Voltage Phase Selector AC Switches Operated @ Mains Frequency 3-Φ Unfolder



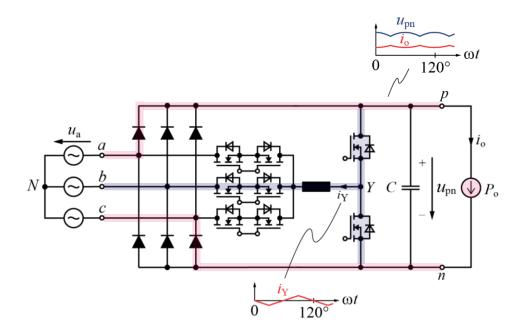


Non-Sinusoidal Mains Current

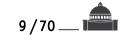 $\rightarrow$  P<sub>0</sub>= const. Required  $\rightarrow$  Sinusoidal Mains Current  $\rightarrow$  NO (!) DC Voltage Control








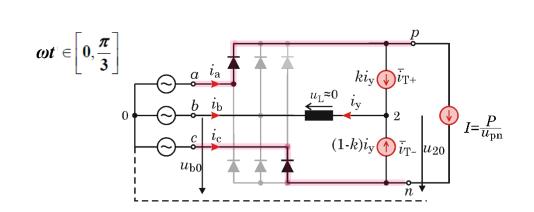
# **IAF Rectifier (1)**

- Low Complexity Low Transistor Current Stress / Sw. Losses Sinusoidal Mains Current @ Const. Power Load
- No Output Voltage Control




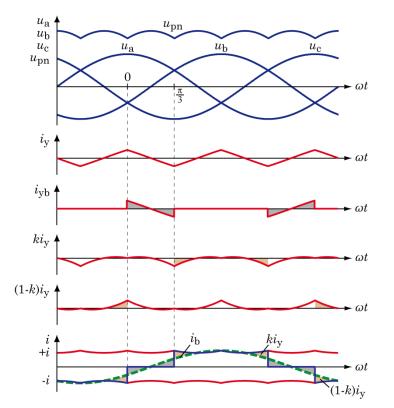

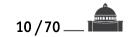• Transistors T<sub>+</sub>, T<sub>-</sub> Could be Replaced by Passive Network








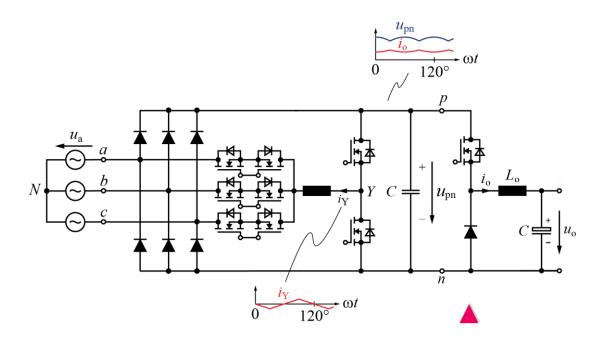
# **IAF Rectifier (2)**

- **Buck-Output Stage**  $\rightarrow$   $P_0$ = const. & Output Voltage Control Sinusoidal Mains Current




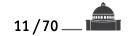• Buck-Stage Could be Replaced by Isolated DC/DC Conv. or Inverter





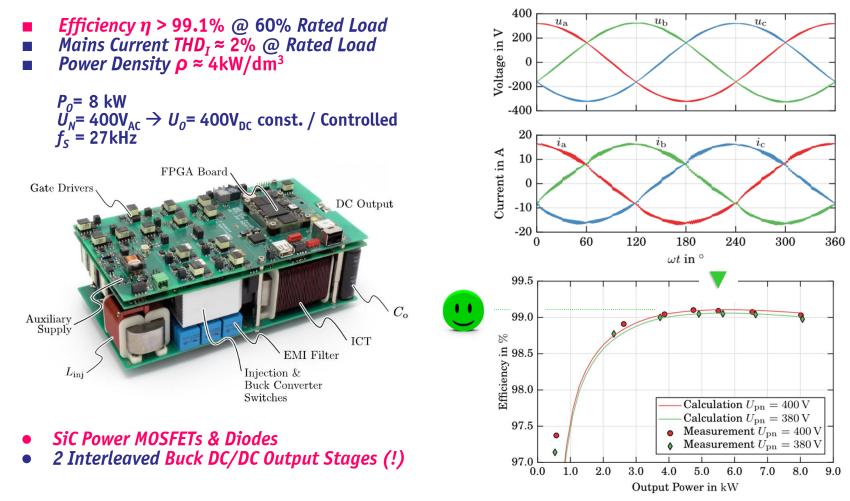
### **IAF Rectifier & Buck Output Stage**



ETH zürich


**Power Electronic Systems** Laboratory

> ICSCRM 2022 D\_VOS, Switzerland

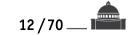



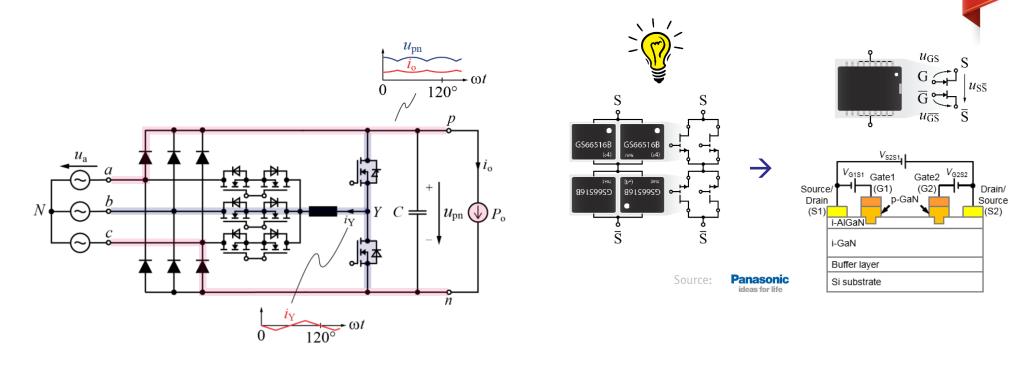
M-BDS — <u>Monolithic Bidirectional / Bipolar Switch</u> Realization of the Phase Selector Switches of 3<sup>rd</sup> Harmonic Inj. PFC Rectifiers Bipolar Voltage Blocking / Current Carrying Capability



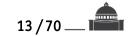• M-BDS  $\rightarrow$  Factor of 4 Reduction of Chip Area Comp. to Discrete Realization of Same  $R_{(on)}$  (!)










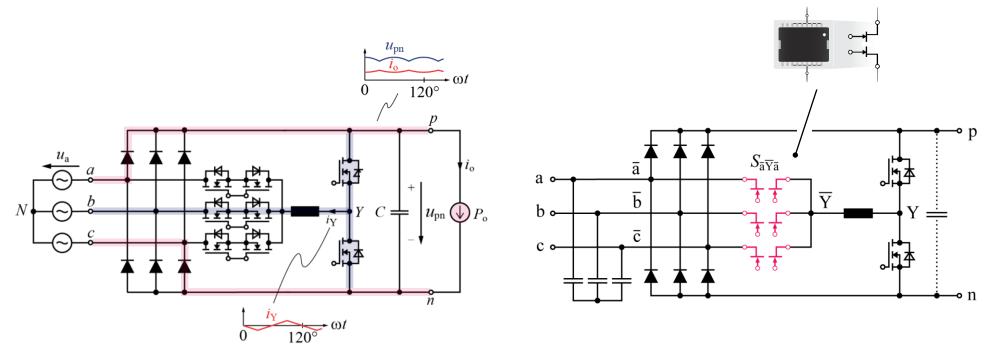
- Realization of the Phase Selector Switches of 3<sup>rd</sup> Harmonic Inj. PFC Rectifiers
   Bipolar Voltage Blocking / Current Carrying Capability
   Low Sw. Frequ. / Mains Frequ. Operation



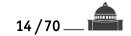• M-BDS  $\rightarrow$  Factor of 4 Reduction of Chip Area Comp. to Discrete Realization of Same  $R_{(on)}$  (!)








### **Experimental Analysis of 1<sup>st</sup> Gen. 600V GaN M-BDS**

- A PowerAmerica Program Based on Infineon's CoolGaN™ HEMT Technology
- Dual-Gate Device / Controllability of Both Current Directions

Bipolar Voltage Blocking Capability | Normally On or Off

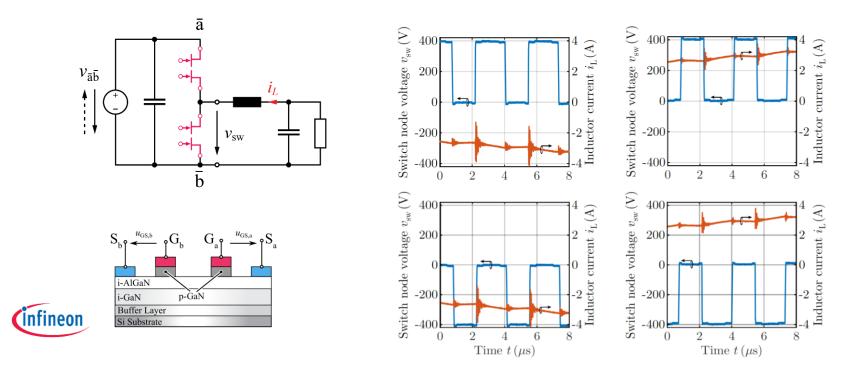


• Analysis of 4-Quardant Operation of  $R_{DS(on)} = 140m\Omega \mid 600V$  Sample @  $\pm 400V$ 


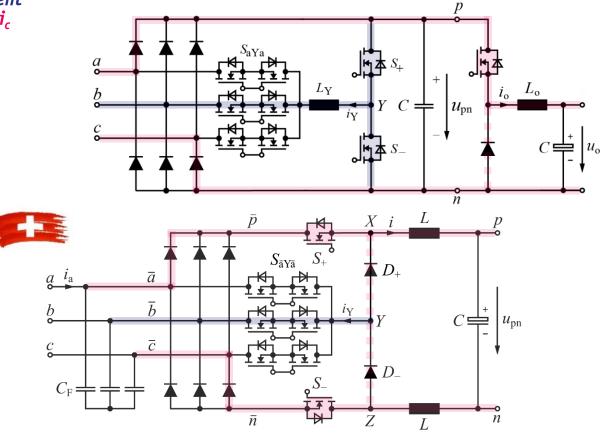
### **Swiss Rectifier**


- **Integration** of 3<sup>rd</sup> Harmonic Injector Switches & Buck Output Stage
- Controlled Output Voltage Sinusoidal Mains Current
- $i_y$  Def. by KCL: E.g.  $i_a$   $i_c$



• Low Complexity

**ICSCRM 2022** DAVOS, Switzerland




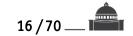


**ETH** zürich
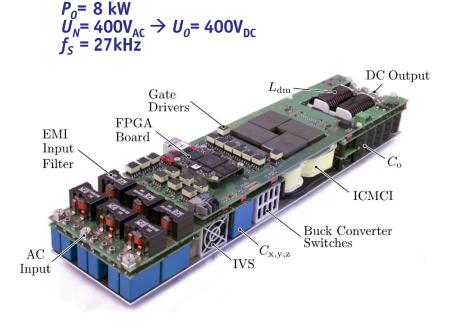
### **Swiss Rectifier Demonstrator**


- **Efficiency**  $\eta = 99.26\%$  @ 60% Rated Load Mains Current THD<sub>I</sub>  $\approx 0.5\%$  @ Rated Load Power Density  $\rho \approx 65W/in^3$



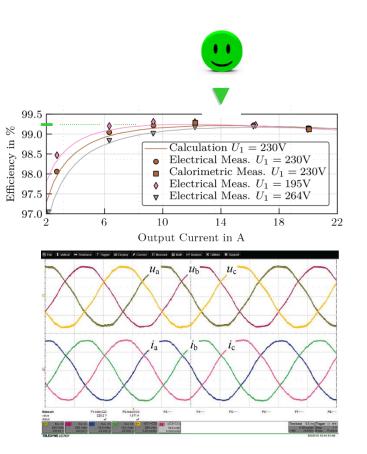- SiC Power MOSFETs & Diodes
- Integr. CM & Output Coupling Inductors (ICMCI)






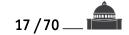



Bipolar Voltage Blocking / Current Carrying Capability

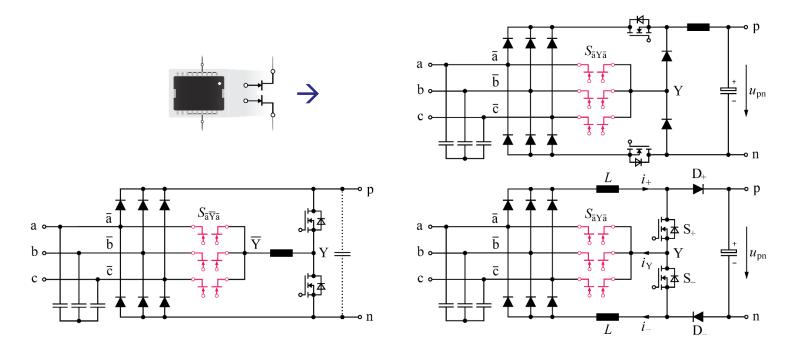Factor of 4 Reduction of Chip Area Comp. to Discrete Realization of Same R<sub>(on)</sub>




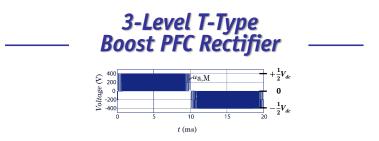• Mains Frequ. Operation of the Phase Selector Switches  $\rightarrow$  Conduction Losses Only















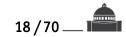
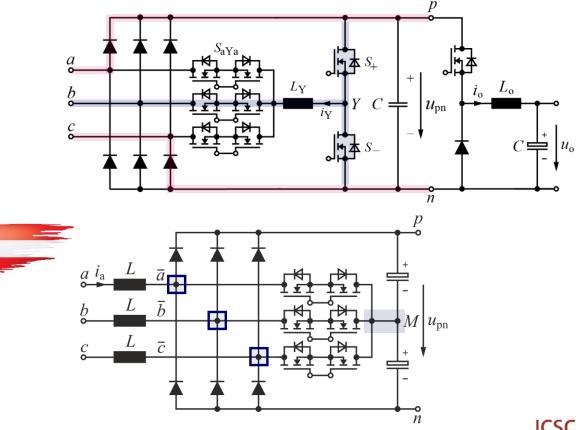
### 3-Level T-Type PFC (Vienna) Rectifier


- 3<sup>rd</sup> Harm. Inj. Inductor Shifted to AC-Side & PWM of DC-Midpoint Ref. Inj. Switches
- **3-Level Diode Bridge Input Voltage**
- Sinusoidal Input Current
- Controlled Output Voltage



- Low Sw. Voltage Stress
- Low AC-Side Inductance
- Low Conduction Losses
- Bridge-Leg & Phase Symmetry

**ETH** zürich


ICSCRM 2022 D\_VOS, Switzerland

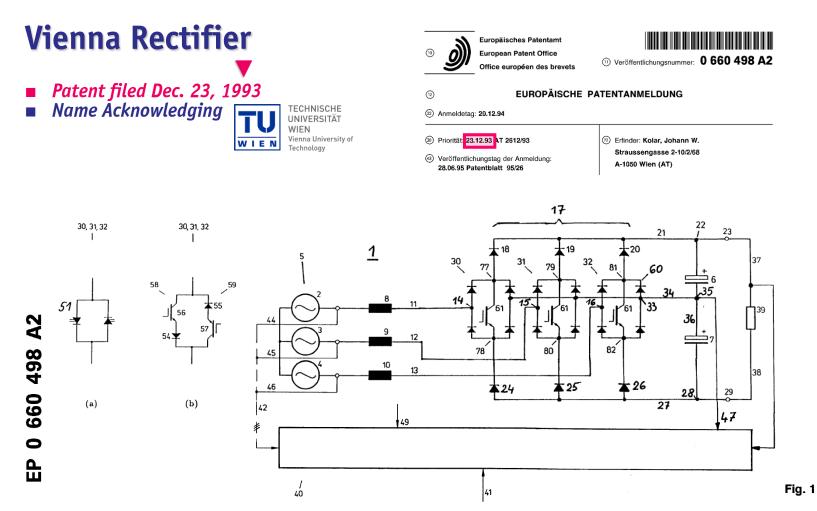

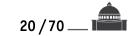• First Ind. Demonstrator for High-Power Telecom Rectifiers in 2001








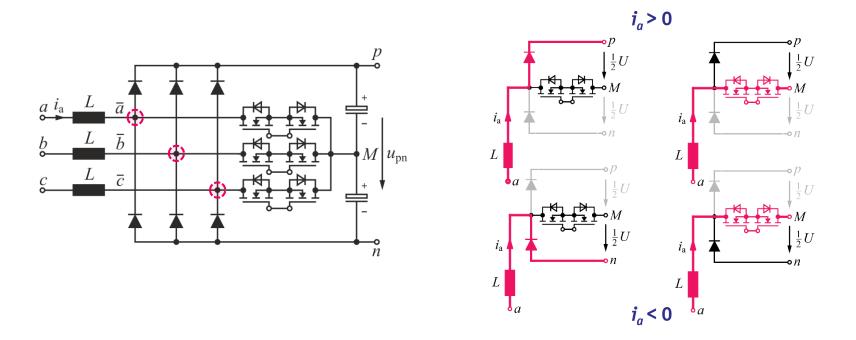
### 3-Level T-Type PFC (Vienna) Rectifier

- Control of Diode Bridge Input Voltage  $\rightarrow$  Sinusoidal Input Current Shaping
- Controlled Output Voltage > Mains Line-to-Line Voltage Amplitude  $\rightarrow$  Boost Type Low Conduction Losses Compared to Alternative 3-Level Topologies



• Voltage Stress of T-Type Switches Defined by Half (!) DC-Link Voltage



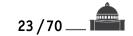


**ICSCRM 2022** 

D\_VOS, Switzerland

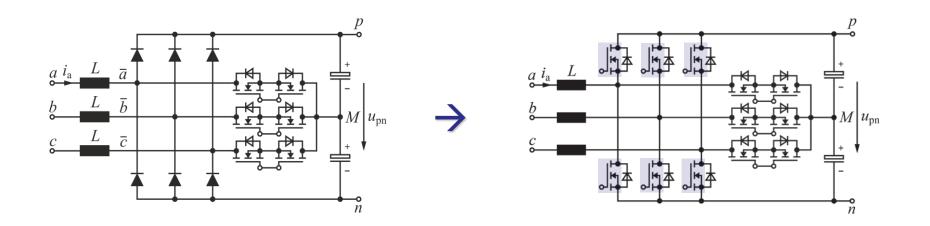
### **Vienna Rectifier – Bidirectional Extension**


- **Rectifier Diodes Replaced w/ SiC MOSFETs** Full DC-Link Voltage Blocking Capability Sw. Voltage Stress Still Def. by Half (!) DC-Link Voltage Synchronous Rectification



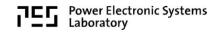• Voltage Stress of T-Type Switches Defined by Half (!) DC-Link Voltage






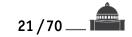

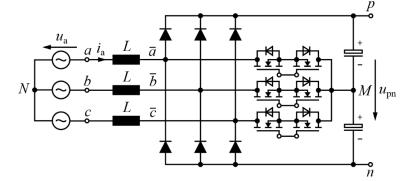
### **Vienna Rectifier Demonstrator (1)**

- Design for More Electric Aircraft Application
   650V CoolMOS & 1200V SiC Diodes
- Coldplate Cooling

 $P_0$  = 10 kW  $U_N$  = 400V<sub>AC</sub> ± 10%  $f_N$  = 50Hz or 360...800Hz  $U_0$  = 800V<sub>DC</sub>




η =96.8%

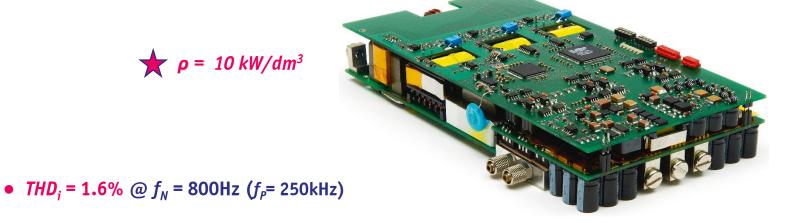

**ICSCRM 2022** D\_VOS, Switzerland



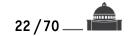


### **Vienna Rectifier Demonstrator (2)**

- Design for More Electric Aircraft Application
   650V CoolMOS & 1200V SiC Diodes
- Coldplate Cooling

 $P_0$  = 10 kW  $U_N$  = 400V<sub>AC</sub> ± 10%  $f_N$  = 50Hz or 360...800Hz  $U_0$  = 800V<sub>DC</sub>

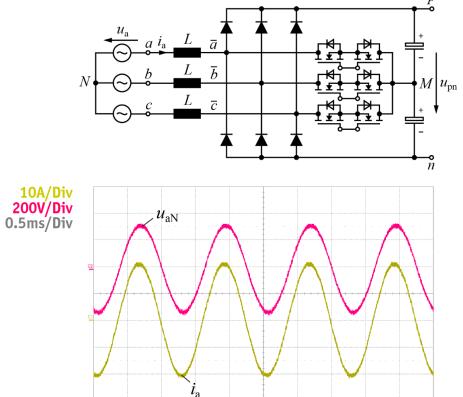
η =96.8%  $\dot{\rho} = 165 W/in^3 (10 kW/dm^3)$  $f_P = 250 kHz$ 



- *THD<sub>i</sub>* = 1.6% @ *f<sub>N</sub>* = 800Hz
   *System Allows 2-Φ Operation*




**ETH** zürich

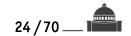




• *M-BDS-Realization of the Midpoint-Switches* 

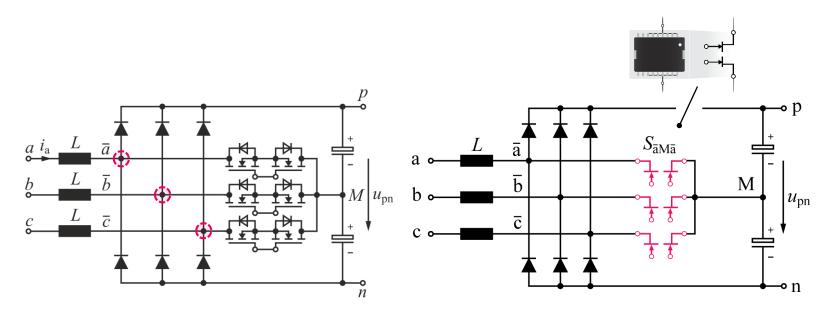Significant Reduction of Cond. Losses @ Given Chip Area



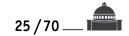
• 600 V M-BDSs @ U<sub>pn</sub>= 800 V<sub>DC</sub> in Combination w/ 1200 V SiC Diodes / MOSFETs








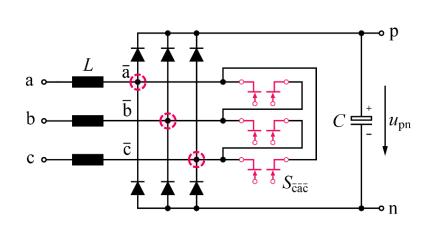- Δ-Switch Rectifier Control of Rectifier Stage Line-to-Line Inp. Voltage w/ 2 Switches M-BDSs Voltage Stress Def. by Full DC-Link Voltage Low Conduction Losses / No DC-Link Midpoint Required




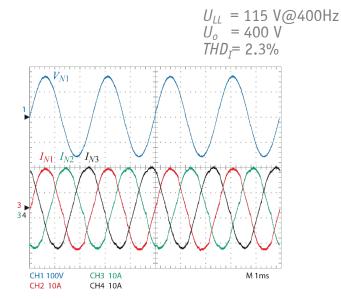

- 600V M-BDSs for 115V / 360...800Hz Aircraft Applications
- Only 2 Switches are Active @ a Time/ Phase Curr. Controller Outputs Transf. into  $\triangle$ -Quantities

**ICSCRM 2022** D\_VOS, Switzerland



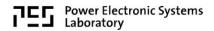


### Global Megatrends



Digitalization Renewable Energy Sustainable Mobility Industry Automation Etc.




**ETH** zürich

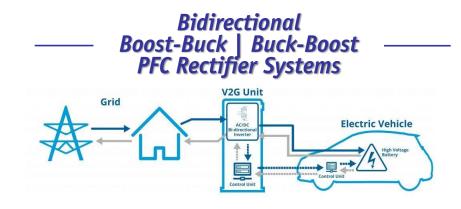

Source: www.zhaw.ch





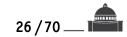

### **Ultra-Fast / High-Power EV Charging**

- Modular Mains Interfaces | Future Non-Isolated Virtually Grounded Systems
   Very Wide Output Voltage Range (200...800V)




ChargePoint stations (projected growth)

53,000 2019 2025 Source: ChargePoint




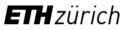- Local Battery Buffer
- $320kW \rightarrow 400km$  Range in 20min




**Power Electronic Systems** Laboratory



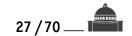


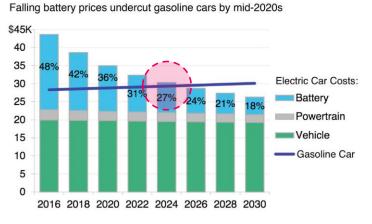
#### **Electric Vehicle Outlook 2019**

 Bloomberg NEF — By 2040 — 57% of All Passenger Vehicle Sales 30% of Global Passenger Vehicle Fleet




**Electric Cars Will Win on Price** 

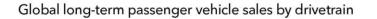

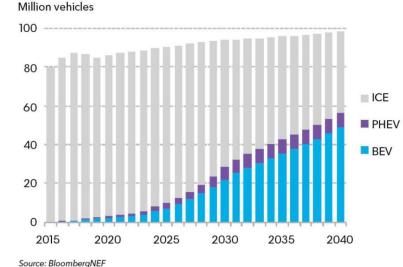

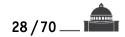• Falling Battery Costs  $\rightarrow$  Price Parity of EVs & ICE-V by Mid-2020s  $\rightarrow$  Tipping Point for EV Industry





#### **Disruptive Innovations**

- **Example** Rapid Change of Transportation Enabled by New Technology (ICE) & Business Model Tony Seba: "All New Vehicles, Globally, will be Electric by 2030"
- NY City, 5<sup>th</sup> Av., Easter Parade  $\rightarrow$  Year 1900: One Motor Cycle / Year 1913: One Horse & Carriage (!)




Source: Tony Seba

- Further Examples Digital / Analogue Photography, VHS Cassette Tape System / DVD etc.
   The Stone Age Didn't End for the Lack of Stone (Disrupted by Bronze Tools)





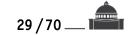


**ICSCRM 2022** 

D\_VOS, Switzerland

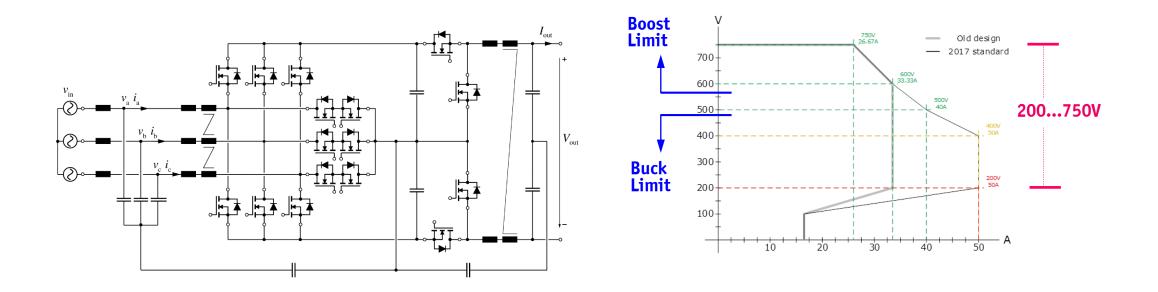
#### **Bidirectional** *Boost-Buck* **PFC Rectifier Concepts**

- Vienna Rectifier Type Bidirectional Boost PFC AC/DC Front-End & DC/DC Buck Output Stage
- Coordinated "Synergetic Control" of AC/DC and DC/DC Converter Stage for Min. Sw. Losses



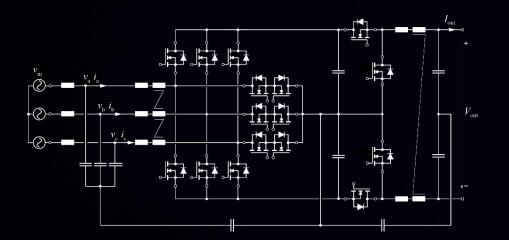• Future Non-Isolated EV-Charging → Earth Leakage Curr. Limited Using "Virtual Ground Modulation"








Boost-Buck


Buck-Boost

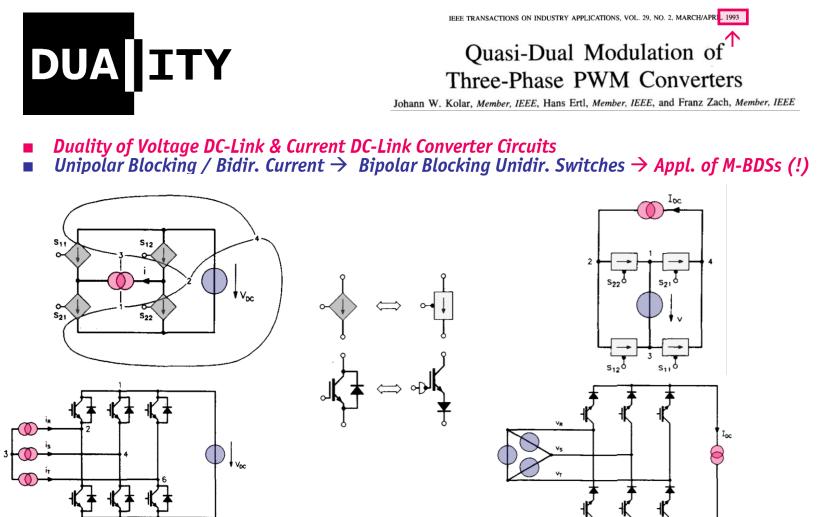


• "Boost-Buck" Translated into "Buck-Boost" Functionality / Lower # of Ind. Components





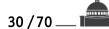

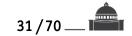


**ICSCRM 2022** 

D\_VOS, Switzerland

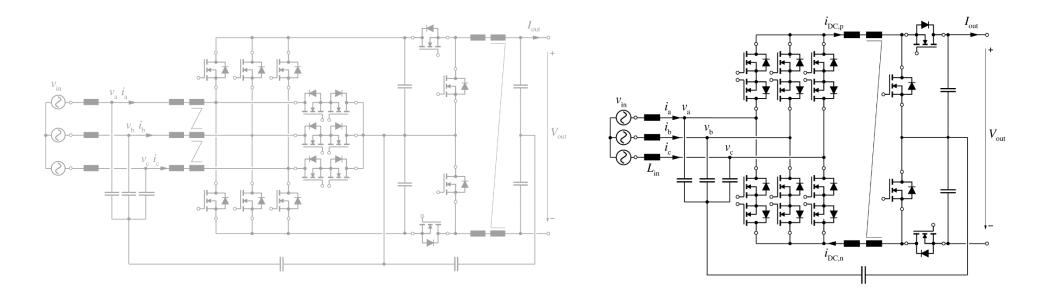
#### **Bidirectional** *Buck-Boost* **PFC Rectifier Concepts**

- **Boost**—Buck OR Buck—Boost Combination
- Closed Loop vs. Open Loop Mains Current Control & Active Input Filter Damping
   "Synergetic Control" of AC/DC and DC/DC Converter Stage



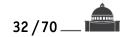AC/DC Buck-Stage Output Inductor Utilized as DC/DC Boost Inductor  $\rightarrow$  Min. # of Inductive Components 






#### **Boost-Buck** | Buck-Boost Demonstrator Systems

- 10 kW @ 400...800 V<sub>DC</sub> @  $3-\Phi$  400 V<sub>rms</sub> Mains  $U_{out} = 200 \dots 800 V_{DC}$   $\eta = 98.8\%$  @ 5.4 kW/dm<sup>3</sup>

- $AC/DC f_{sw} = 100 \text{ kHz}$   $DC/DC f_{sw} = 2 \times 100 \text{ kHz}/200 \text{ kHz} \text{ eff.}$

- =  $10 \text{ kW} @ 400...1000 \text{ V}_{\text{DC}} @ 3-\Phi 400 \text{ V}_{\text{rms}}$  Mains =  $U_{out} = 200 ... 1000 \text{ V}_{\text{DC}}$ =  $\eta = 98.6\% @ 6.4 \text{ kW/dm}^3$

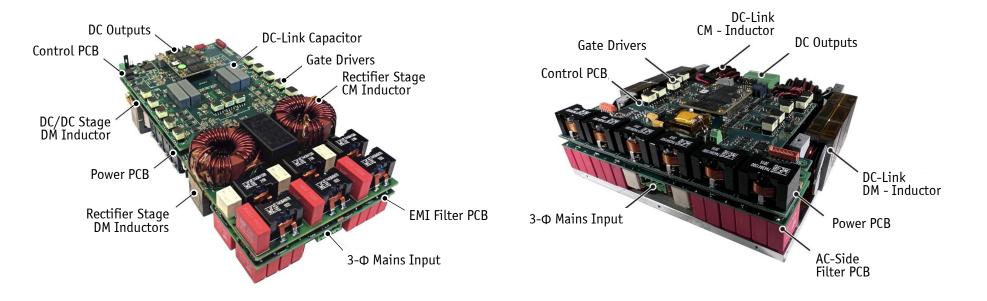
- $AC/DC f_{sw} = 100 \text{ kHz}$   $DC/DC f_{sw} = 2 \times 50 \text{ kHz}/100 \text{ kHz} \text{ eff.}$



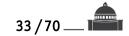- **Boost-Buck** Voltage DC-Link PFC Rectifier
- **Buck-Boost** Current DC-Link PFC Rectifier







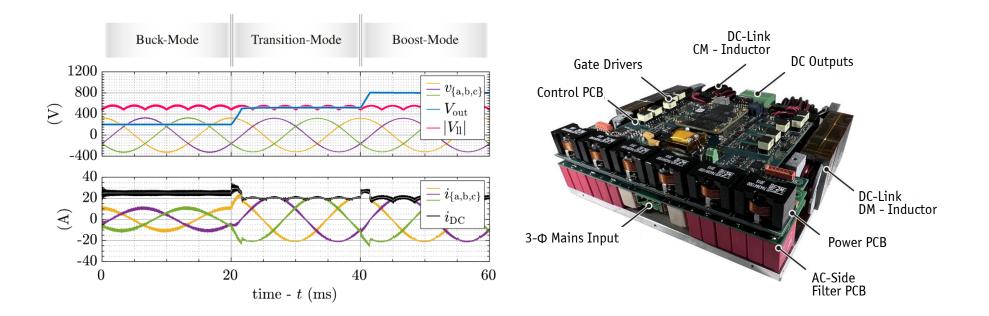
#### **Buck-Boost Demonstrator System**

- *"Synergetic" Control of CSR-Stage & Boost-Stage*  $\rightarrow$  *6-Pulse*  $i_{DC}$  / *Significant Red. of Sw. Losses* Seamless Transition from Full Boost Operation @ 6-Pulse  $i_{DC}$  to Buck Operation @  $i_{DC}$ =const.




• "Virtual Ground" Control of Output Voltage Midpoint  $\rightarrow$  Non-Isolated EV Charger (!)





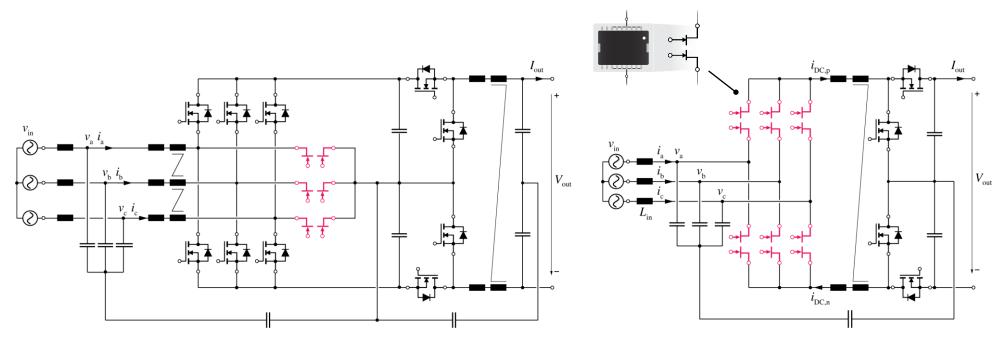- Boost—Buck OR Buck—Boost Combination
- Closed Loop vs. Open Loop Mains Current Control & Active Input Filter Damping
- "Synergetic Control" of AC/DC and DC/DC Converter Stage




• 600 V M-BDSs for Boost—Buck & 1200 V M-BDSs for Buck—Boost Combination @ 400 V<sub>rms</sub> Mains



ICSCRM 2022 D\_VOS, Switzerland






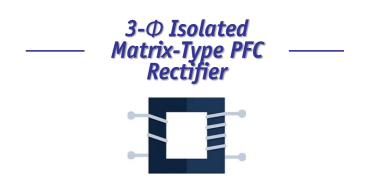






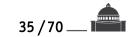
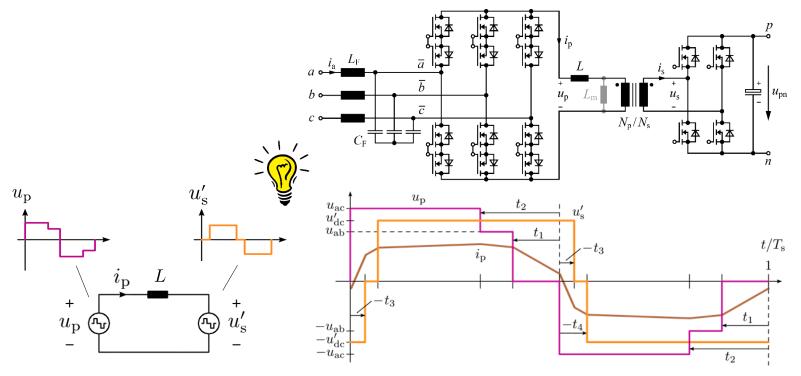
#### **Isolated Matrix-Type PFC Rectifier (1)**

- Based on Dual Active Bridge (DAB) Concept Opt. Modulation  $(t_1...t_4)$  for Min. Transformer RMS Curr. & ZVS or ZCS Allows Buck-Boost Operation



• Equivalent Circuit

• Transformer Voltages / Currents





**≈ 99%** 

٠


 $\begin{array}{l} f_{\rm sw} &= 31\,\rm kHz\\ f_{\rm sw} &= 36\,\rm kHz\\ f_{\rm sw} &= 41\,\rm kHz\\ f_{\rm sw} &= 50\,\rm kHz\\ f_{\rm sw} &= 60\,\rm kHz \end{array}$ 

22

10A/div

200V/div

18

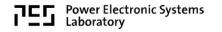

#### **Isolated Matrix-Type PFC Rectifier (2)**


- Efficiency  $\eta$  = 98.9% @ 60% Rated Load (ZVS) Mains Current THD<sub>I</sub> ≈ 4% @ Rated Load Power Density  $\rho$  ≈ 4kW/dm<sup>3</sup>

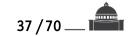99.5\$ 99.0  $P_0 = 8 \text{ kW}$   $U_N = 400 \text{V}_{AC} \rightarrow U_0 = 400 \text{V}_{DC}$   $f_S = 36 \text{kHz}$ in 98.5 98.0 98.0 97.5 98.597.0 <mark>∟</mark> **ZYNQ 7000** Gate Drivers Transformer 6 10 14System on Chip with Leakage Output Current in A Input Filter Direct Matrix Converter Heat Sink Full-Bridge  $C_{\rm dc}$ 

900V / 10mΩ SiC Power MOSFETs
 Opt. Modulation Based on 3D Look-Up Table











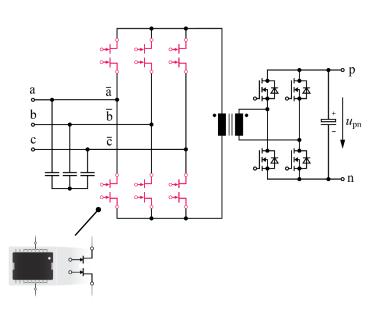- Matrix-Type Bidirectional DAB-Based Topology Unidir. Vienna Rectifier II (Boost-Type) Unidir. Vienna Rectifier III (Buck-Type)




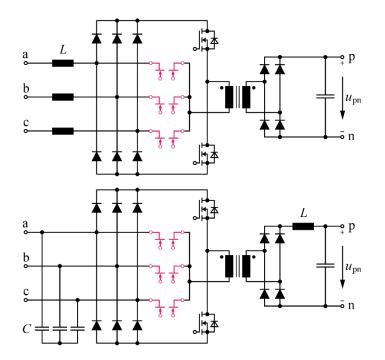

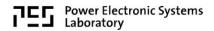• Functional Integration  $\rightarrow$  Lower Complexity BUT Limited Controllability








#### Global Megatrends







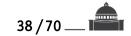

# Variable Speed Motor Drive (VSD) Systems

- Industry Automation / Robotics
- Material Machining / Processing Drilling, Milling, etc.
- Compressors / Pumps / Fans
   Transportation
- etc., etc.

.... Everywhere !



• 60...70 % of All Electric Energy Used in Industry Consumed by VSDs






**ICSCRM 2022** 

D\_VOS, Switzerland

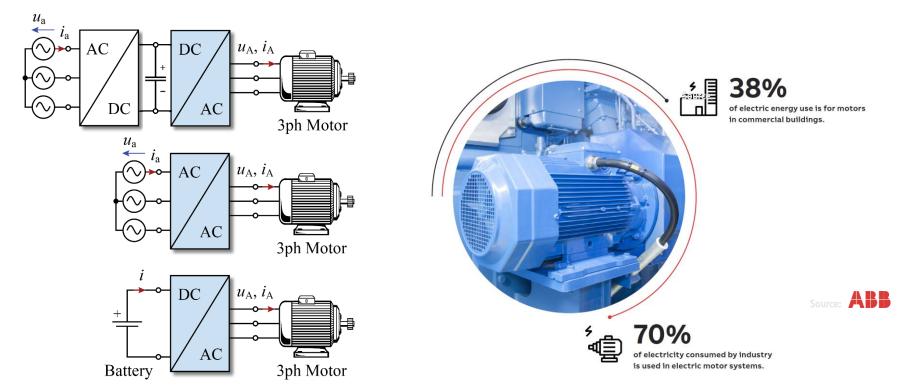
# **Variable Speed Drive Concepts**

- DC-Link Based AC/DC/AC OR Matrix-Type AC/AC Converters Battery OR Fuel-Cell Supply OR Common DC-Bus Concepts



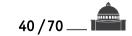
• 45% of World's Electricity Used for Motors in Buildings & Industrial Applications




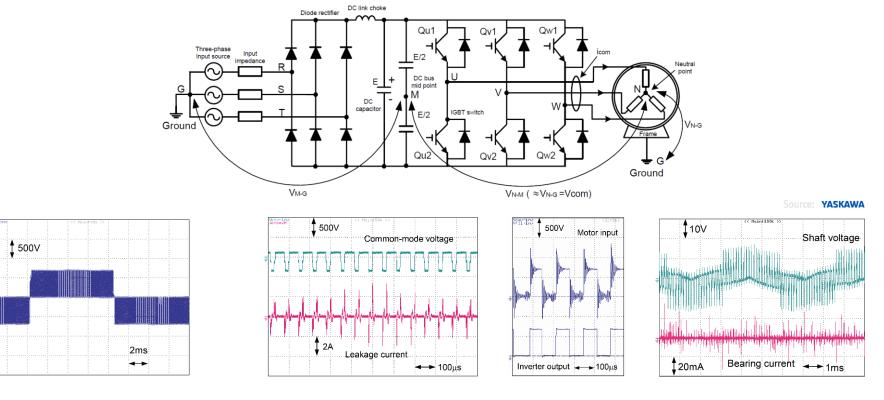
# **State-of-the-Art Drive System (1)**

- Standard 2-Level Inverter Large Motor Inductance Allows Low Sw. Frequency
- Shielded Motor Cables / Cable Length Limited / Insulated Bearings / Acoustic Noise




• Line-to-Line Voltage

**CM Leakage Current** 

| Motor Surge Voltage | Bearing Current




ICSCRM 2022 D\_VOS, Switzerland

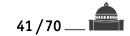

# **State-of-the-Art Drive System (2)**


- Measures Ensuring EMI Compliance / Longevity of Motor Insulation & Bearings
   Series Reactor | dv/dt-Filter | DM-Sinus Filter | Full-Sinus Filter | Multi-Level Inverter

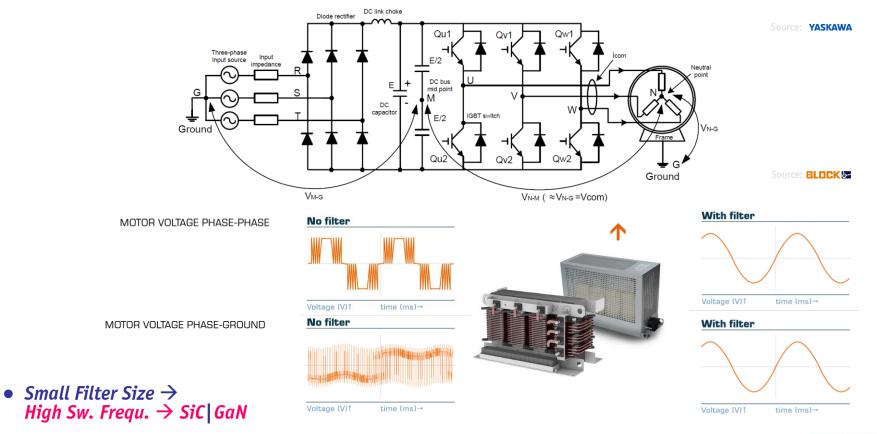




**ETH** zürich

**ETH** zürich

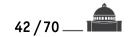
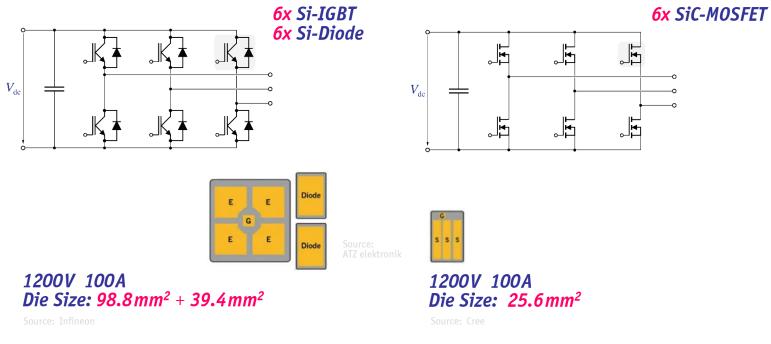
# Si vs. SiC (1)


Si-IGBT / Diode  $\rightarrow$  Const. On-State Voltage, Turn-Off Tail Current & Diode Reverse Recovery Current SiC-MOSFET  $\rightarrow$  Loss Reduction @ Part Load BUT Higher  $R_{th}$ 



- Space Saving of >30% on Module Level (!) Extremely High  $dv/dt \rightarrow$  Motor Insul. Stress / Reflections / Bearing Curr. / EMI




**ETH** zürich

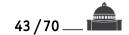

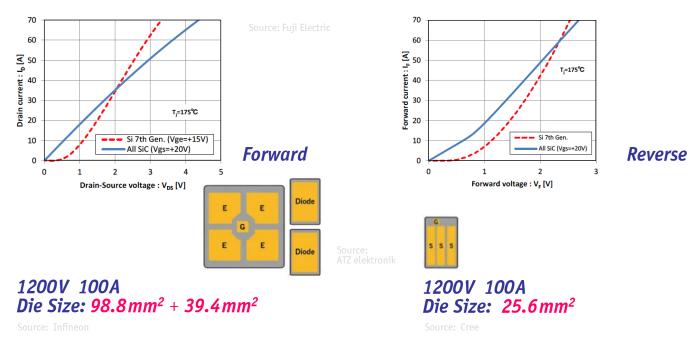
# Si vs. SiC (2)

Si-IGBT / Diode  $\rightarrow$  Const. On-State Voltage, Turn-Off Tail Current & Diode Reverse Recovery Current SiC-MOSFET  $\rightarrow$  Loss Reduction @ Part Load BUT Higher  $R_{th}$ 



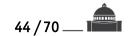
- Space Saving of >30% on Module Level (!) Extremely High  $dv/dt \rightarrow$  Motor Insul. Stress / Reflections / Bearing Curr. / EMI





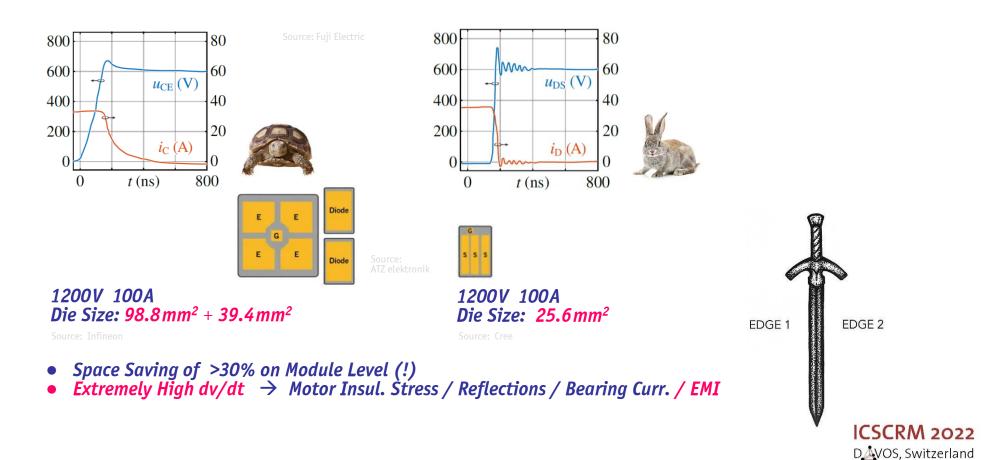
# Si vs. SiC (3)

Si-IGBT / Diode → Const. On-State Voltage, Turn-Off Tail Current & Diode Reverse Recovery Current
 SiC-MOSFET → Loss Reduction @ Part Load BUT Higher R<sub>th</sub>





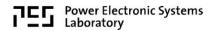



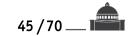
#### **Inverter Output Filters**

dv/dt-Filters — Full-Sinewave Filters ———









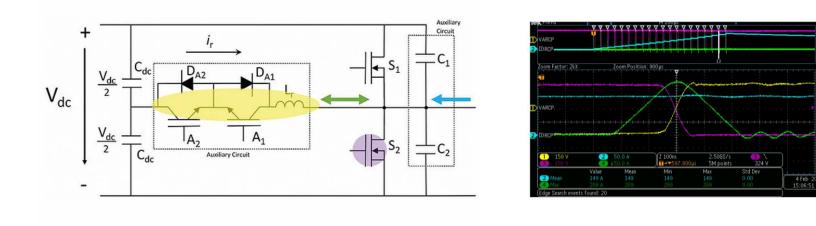
#### Aux. Resonant Commutated Pole

- dv/dt-Limitation & Sw. Loss Red. w/ Snubber Cap. & Aux. Switches → 1 ... 1.5 kV/us
   Opt. Timing of Aux. & Main Switches → Pre-Flex<sup>TM</sup> Self-Learning AI Algorithm
   Concept Proposed for BJTs by M. Lockwood & A. Fox @ IPEC 1983 (!)





Green: Lr Resonant inductor current (varies with load)

Purple: S2 Vds switch voltage (600V-0V)


Yellow: Aux + Lr ARCP and inductor voltage (-300V to +300V)


Blue: Load current varies 0-160A

- Complicated Implementation / Critical Timing for f<sub>sw</sub> > 100kHz 99.5% Half-Load | 99.35% Full-Load Eff. @ 100kW, 800V<sub>DC</sub>, f<sub>sw</sub>= 50kHz (1200V/12mΩ SiC MOSFETs)

**ICSCRM 2022** D\_VOS, Switzerland



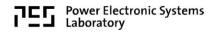

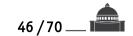


**ICSCRM 2022** 

D\_VOS, Switzerland

#### **Full-Sinewave LC Output Filter**

- 3-Level T-Type Inverter 3-Level Phase Voltage / 5-Level Line-to-Line Voltage
- Neutral Point Clamped | Flying Capacitor | T-Type Bridge-Leg Topology Lower CM Voltage Steps Compared to 2-Level Converter

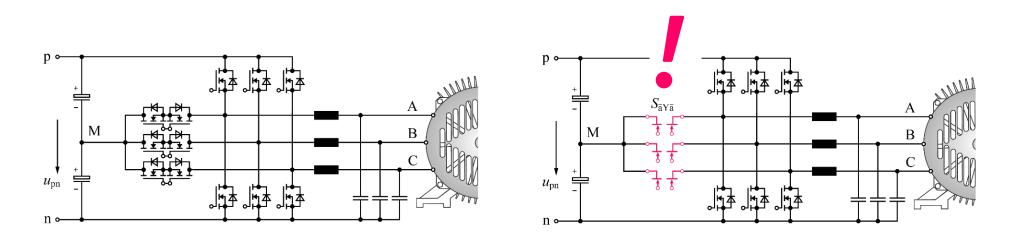

- DC-Link Referenced LC-Filter Elimination of DM & CM Sw. Frequ. Output Voltage Harmonics
- T-Type Topology Ensures Low Conduction Losses Adv. Application of M-BDSs (!)















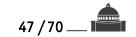

#### **Motivation**


- General / Wide Applicability
- Adaption to Load-Dependent Battery | Fuel Cell Supply Voltage
   Operation in Wide Output Voltage / Wide Motor Speed Range

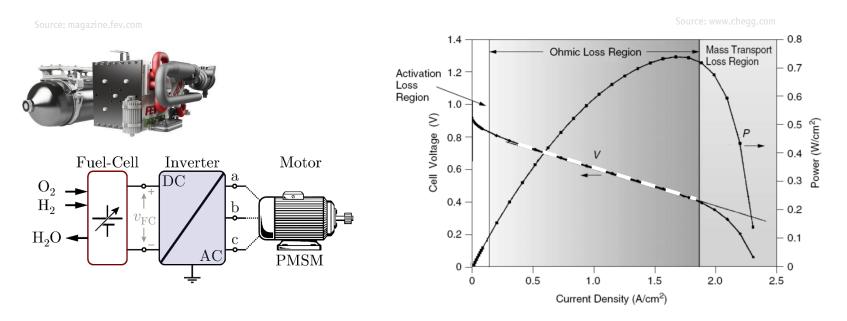

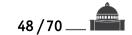- *Full-Sinewave Filtered Motor Supply Voltage* LC Output Filter Inductor Advantageously Utilized as Buck-Boost-Inductor







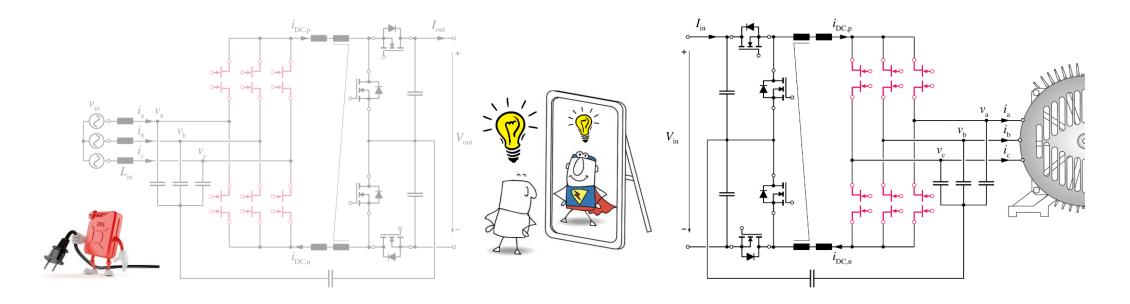
#### Current DC-Link *Buck-Boost* Inverter (1)

Derivation Based on Bidirectional Buck-Boost PFC Rectifier Topology (EV Charger)

*Lower # of Ind. Components Compared to Boost-Buck Approach* 




•

**DC/DC Buck Converter Performs Voltage**  $\rightarrow$  **Current Translation** Coordinated Control / Modulation of DC/DC & Inverter Stage for Min. Sw. Losses 


> **ICSCRM 2022** D\_VOS, Switzerland



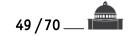

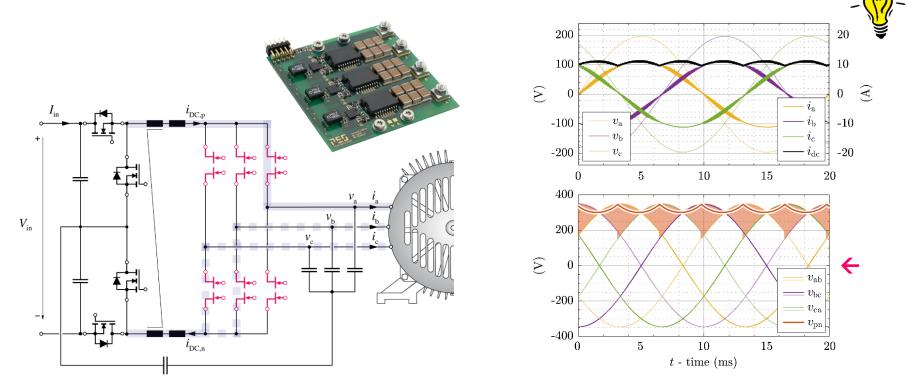
#### **Current DC-Link** *Buck-Boost* **Inverter (2)**

*"Synergetic" Control of DC/DC Buck Converter & Current DC-Link Inverter Stage 6-Pulse-Shaping of DC Current by Buck-Stage*  $\rightarrow$  *Allows Inverter Phase Clamping* 



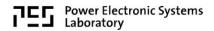Switching of Only 2 of 3 Phase Legs  $\rightarrow$  Reduction of Sw. Losses by  $\approx$  86% (!) 















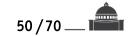

### **3-Φ** Current DC-Link AC/AC Converter (1)

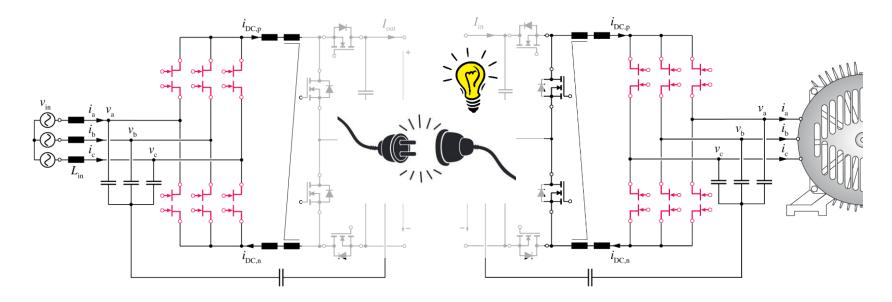**DC-Side Coupling of Buck-Boost Current DC-Link PFC Rectifier & Inverter — AC/DC/AC** 

Full Sinewave Filtering @ Input & Output w/ Single Magnetic Component




• Bipolar Blocking / Unidir. Switches / Unidir. DC-Link Current Sufficient for Bidir. Power Conversion

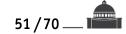• Modulation-Based Inversion of DC-Link Voltage Polarity  $\rightarrow$  Inv. of Power Flow Direction








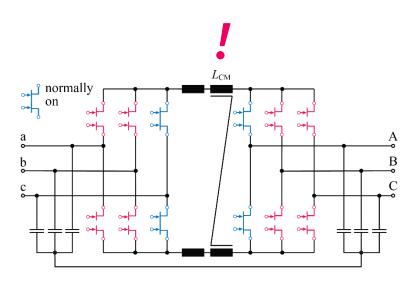
#### **3-Φ Current DC-Link AC/AC Converter (2)**

- Sinusoidal Motor Voltage Achieved w/ Single Ind. Component Unidir. Valves Sufficient for Bidir. Power Conversion M-BDSs Synchronous Rectification




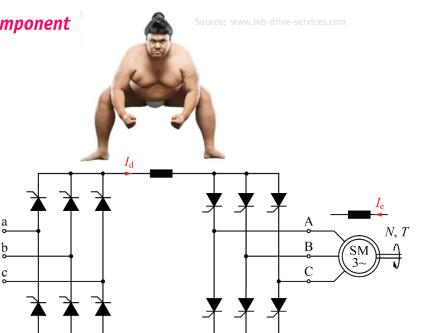

• *Relation to High-Power Thyristor-Based Medium Voltage Synchr. Machine Variable Speed Drives* 




**ICSCRM 2022** D\_VOS, Switzerland

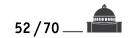

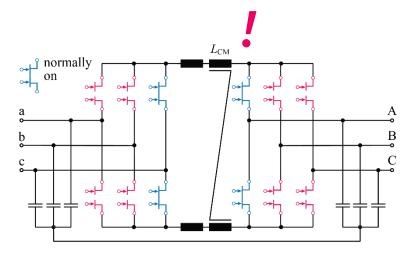
# DUA ITY

- Current DC-Link Topology
- Application of M-BDSs
- Complex 4-Step Commutation
- Low Filter Volume



- Challenging Overvoltage Protection
- Limited Control Dynamics

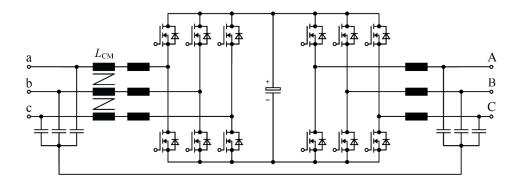- Voltage DC-Link Topology
- Standard Bridge-Legs
- Low-Complexity Commutation
- Defined Semiconductor Voltage Stress
- Facilitates DC-Link Energy Storage



<sup>•</sup> High Input / Output Filter Volume



**ETH** zürich






# $3-\Phi AC/AC$ Matrix Converter $\begin{cases} 1 0 0 \\ 0 0 0 \\ 0 1 1 \end{cases}$





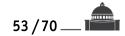


**ICSCRM 2022** 

D\_VOS, Switzerland

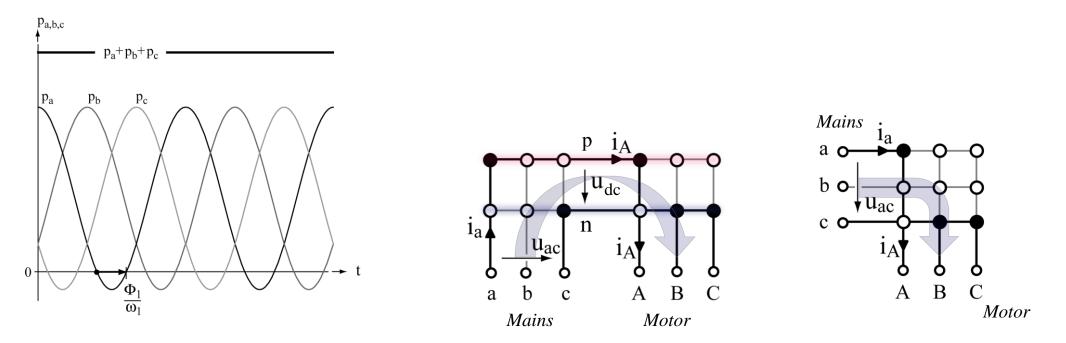
#### *Indirect* & *Direct* 3- $\Phi$ AC/AC Matrix Converter (1)

- Constant 3- $\oplus$  Instantaneous Power Flow  $\rightarrow$  No Low-Frequ. DC-Link Power Buffer Requirement (!)
- Indirect AC/DC—DC/AC OR Direct AC/AC Power Conversion  $\rightarrow$  IMC OR DMC Switch Matrix w/ Bipolar Voltage Blocking & Current Carrying Devices




Output-Side Motor Inductor  $\rightarrow$  Operation Limited to Buck-Type (Step-Down) Voltage Conversion 

**ETH** zürich

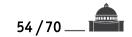

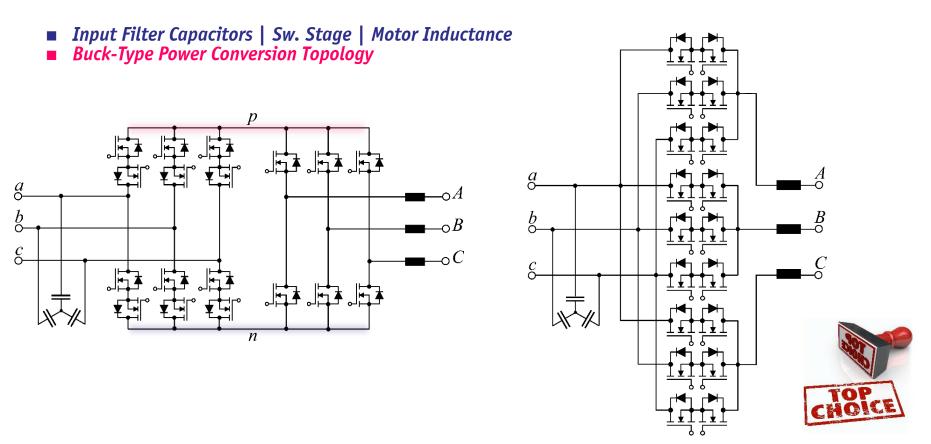
#### *Indirect* & *Direct* 3- $\Phi$ AC/AC Matrix Converter (2)




- IMC Relies on Strictly Pos. DC-Link Voltage / i=0 Input Stage Commutation
- M-BDS-Based Realization of DMC Features Lower # of Switches / 4-Step Commutation Required


ICSCRM 2022 DAVOS, Switzerland



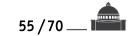

#### **4-Step Commutation of DMC**

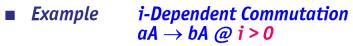

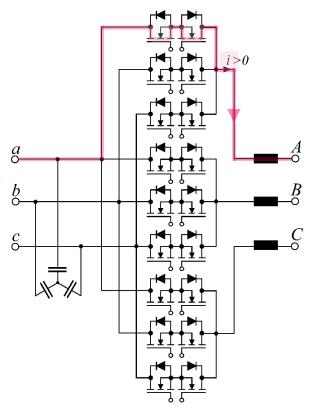


• No Mains Short Circuit

• No Load Current Interruption

Assumption  $u_{ab} < 0$ 




**ETH** zürich

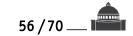

# 4-Step Commutation of DMC (1)



1<sup>st</sup> Step: Off

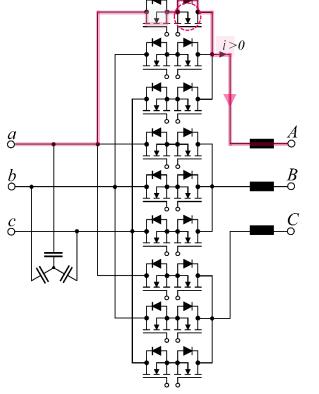


• No Mains Short Circuit

• No Load Current Interruption


Assumption  $u_{ab} < 0$ 





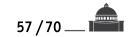

# 4-Step Commutation of DMC (2)

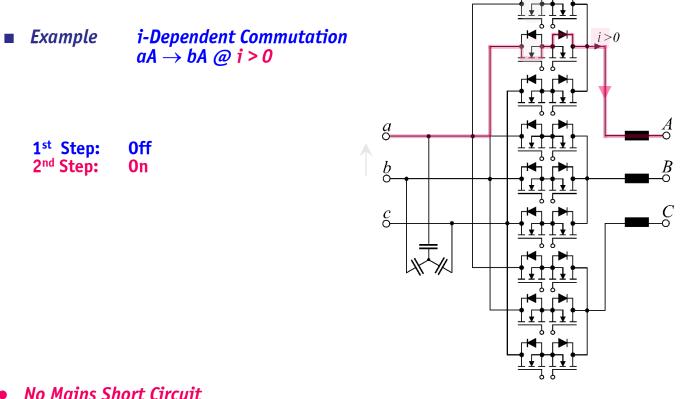


- No Mains Short Circuit
- No Load Current Interruption


Assumption  $u_{ab} < 0$ 





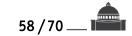


# 4-Step Commutation of DMC (3)

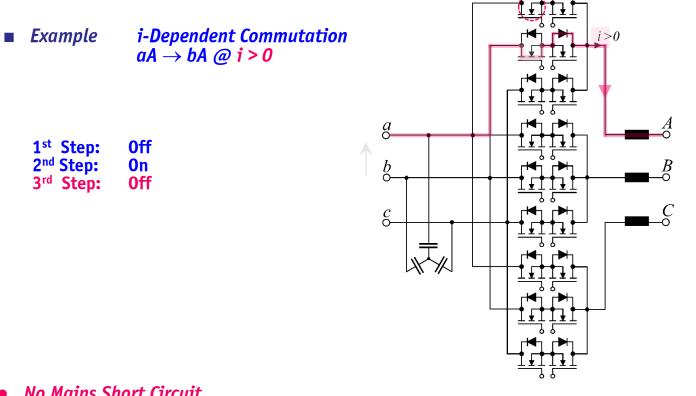


- No Mains Short Circuit
- No Load Current Interruption

Assumption  $u_{ab} < 0$ 



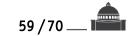

### 4-Step Commutation of DMC (4)

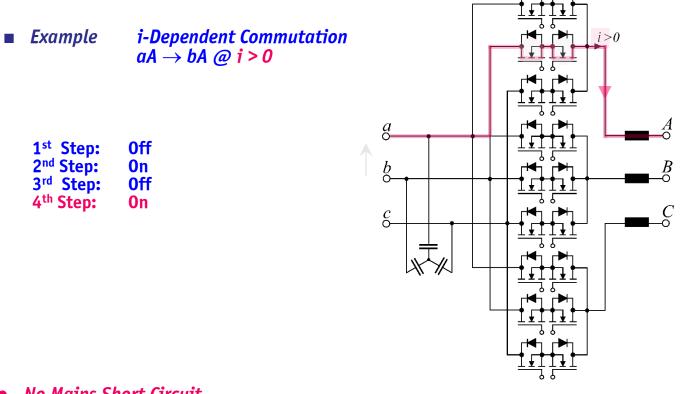

- No Mains Short Circuit
- No Load Current Interruption


Assumption  $u_{ab} < 0$ 





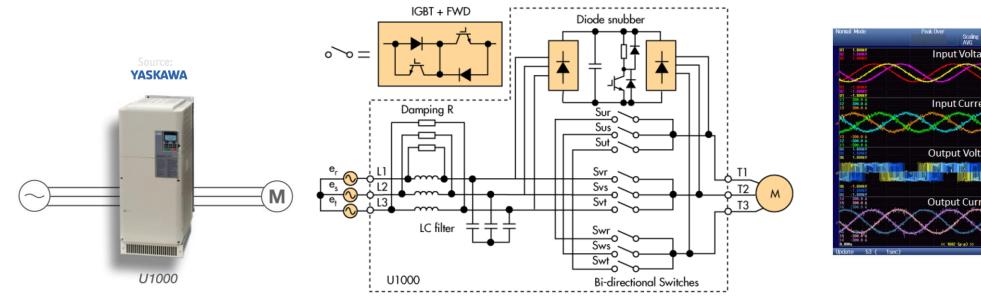
#### 

- Fully Regenerative  $\rightarrow$  e.g. Downhill Conveyor etc. Higher Power Density Compared to Voltage DC-Link System / No Front-End Boost Inductors
- Quasi Three-Level Output Characteristic No-Switching / Eco Operation for  $f_2=f_{Mains}$
- Close to Unity Power Factor




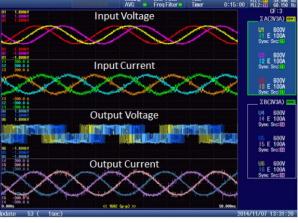

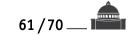- **Challenging Overvoltage Protection**
- Limited Output Voltage Range (!)











- Indirect Matrix Converter (IMC)
- GaN M-BDS AC/DC Front-End
- ZCS Commutation of AC/DC Stage @  $i_{DC}$ =0 No 4-Step Commutation

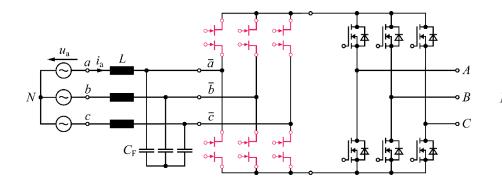- Direct Matrix Converter (CMC)
- 4-Step Commutation Exclusive Use of GaN M-BDSs



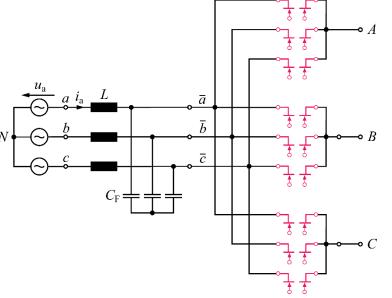
- **Higher # of Switches Compared to DMC**
- Lower Cond. Losses @ Low Output Voltage Thermally Critical @  $f_{out} \rightarrow 0$
- ٠



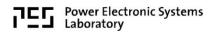• Thermally Critical @  $f_{out} \approx f_{in}$ 















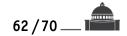


#### **Early Si-BDS Realizations**

- **Combination of Unidirectional Devices** 4x Chip Area (MOSFETs) | Costs &/OR High On-State Volt. Drop
- "True" M-BDS Single Drift Region for Blocking Voltages of Both Polarities | 2 Gates | Bidir. Curr. Cond

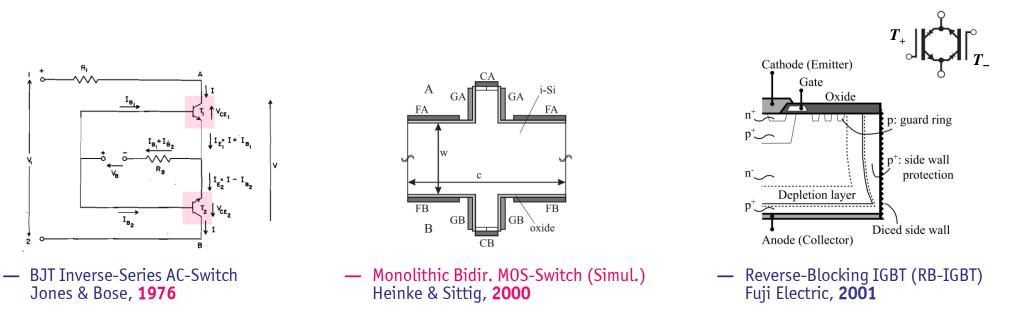


- A "Monolithic" Bidirectional Switch (M-BDS) IS NOT Necessarily a "True" M-BDS (!) "TM-BDS"
   TM-BDS Common Drift Region Formed by Back-to-Back Wafer Bonding OR 2-Side Lithography Processing

**ETH** zürich

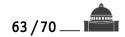

#### Monolithic 4-Terminal 1.2kV/20A SiC BiDFET

- BiDFET Two JBSFETs w/ Drains Connected via Common N<sup>+</sup> Substrate & Metallization | 50mΩ
- Junction Barrier Controlled Schottky (JBS) Diode Integr. into MOSFET Prev. Curr. Flow via Body Diode

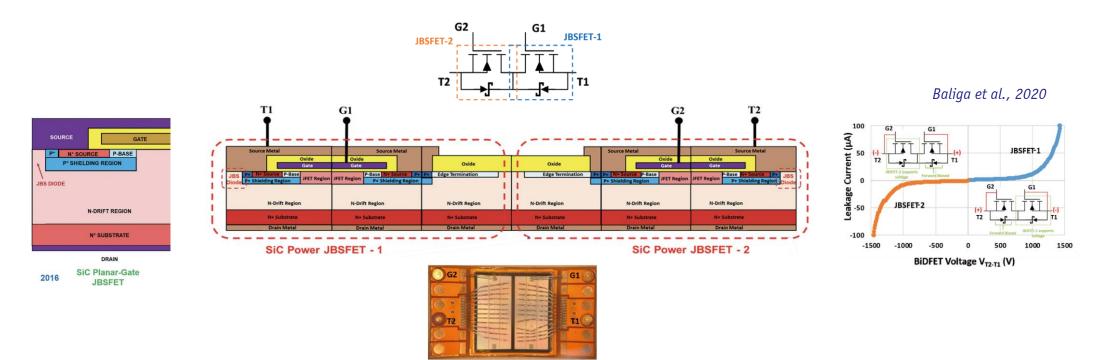


- JBSFET Low Sw. Losses & No Bipolar Degradation | Drift Layer of JBSFET-1 Blocks Pos. / JBSFET-2 Neg. Voltage
   A Monolithic Bidirectional Switch (M-BDS) IS NOT Necessarily a "True" M-BDS (!)


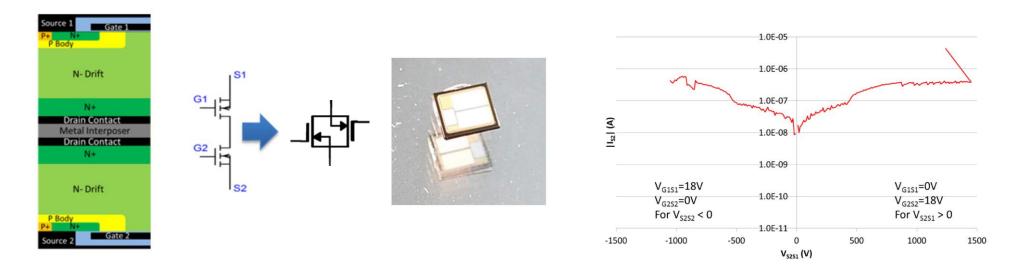
#### **Common Drain Bidirectional 1.2kV SiC MOSFET**

- Direct Drain-to-Drain Connection of 2 MOSFET Bare Dies Space-Efficient Comp. to Side-by-Side Pair
- Alternative to Semiconductor-to-Semiconductor Bonding / Low Fabrication Complexity
- Challenging Packaging & Cooling




Chow et al., 2020

- Blocking Capability Close to Rating of the Component MOSFETs
   Joining of the Existing Drain Metallizations 2 Drift Regions No "Monolithic"-BDS


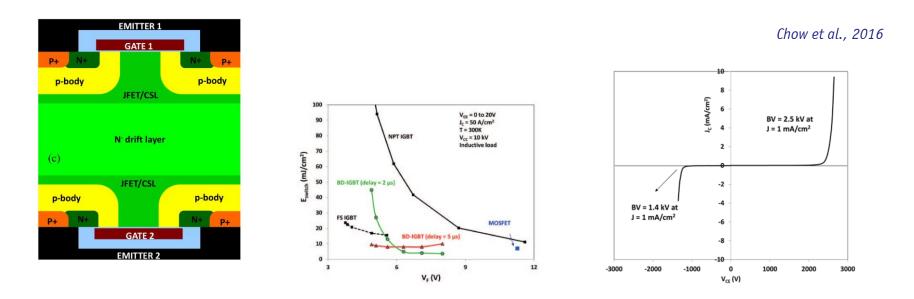
#### **Monolithically Integrated Bi-Directional SiC IGBT**

- Planar-Gate Bi-Direct. IGBT Fabricated w/ Double-Sided Lithogr. Process on Free-Standing n<sup>-</sup> Wafers
- MOS-Cells on Both Sides of Lightly Doped Drift Region / Cond. & Sw. Loss Infl. of Back-Side Gate Volt. Bias
- Challenging Packaging & Cooling




- Simul. Performance of a 15kV BD-IGBT | Blocking Characteristic (max. 7.2 kV Meas.) Epi Layer Defects etc.
   Shared Drift Region → "True" Monolithic Bidirectional Switch (TM-BDS)



Power Elect Laboratory

Power Electronic Systems


**ICSCRM 2022** D\_VOS, Switzerland

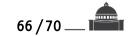

#### **1.2kV Bidir. Bipol. Junction Transistor (B-TRAN<sup>™</sup>)**


**Back-to-Back Si-BJTs with Merged Collector Regions** | Upcoming SiC Version


■ 1200 V / 25A @ 100°C Samples | Typ. 0.6 V On-State Voltage | Curr. Gain Typ. 3...4

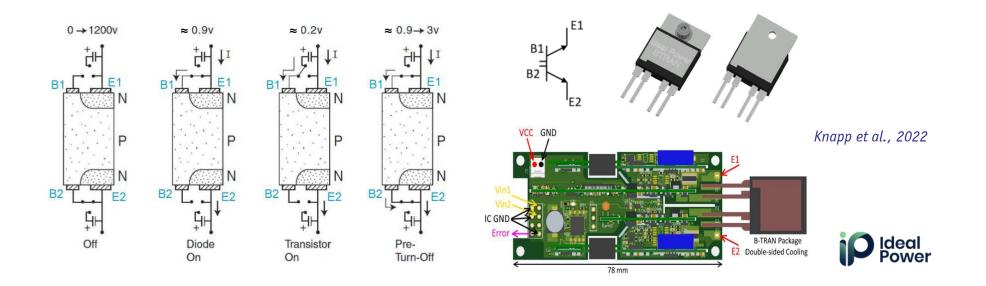

- Rel. Complex Bidir. Gate-Drive / Special 4-Terminal TO-264 Package w. Double-Sided Cooling
- Shared Collector Region → "True" Monolithic Bidirectional Switch (TM-BDS)



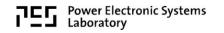

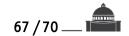


**ICSCRM 2022** 

D\_VOS, Switzerland
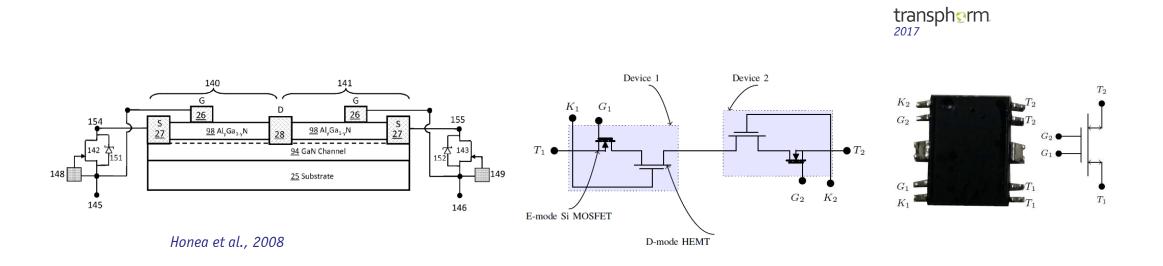
#### **Cascode GaN 4Q-Switch**


Common-Drain Arrangement of Two Cascode Switches (600 V GaN D-Mode HEMT + LV Si E-Mode MOSFET) Up to 1200 V, 200 m $\Omega$  Samples for Demonstration Purposes



• 4Q — Current Conduction Only in Quadrants I & III

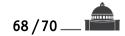
• Shared Drift Region for Blocking Pos. & Neg. Voltage & Separate (?) Cascode MOSFETs → True "Monolithic"(?)-BDS





# **Remark** Solid-State Circuit Breakers (SSCBs)

- Ultra-Fast Fault Interruption | Reduced Fault Stress | Arc-Less | Low Surge Voltage | Long Lifetime
- Software / Remote Configurable Trip Behavior / Remote-Controlled Load Switch

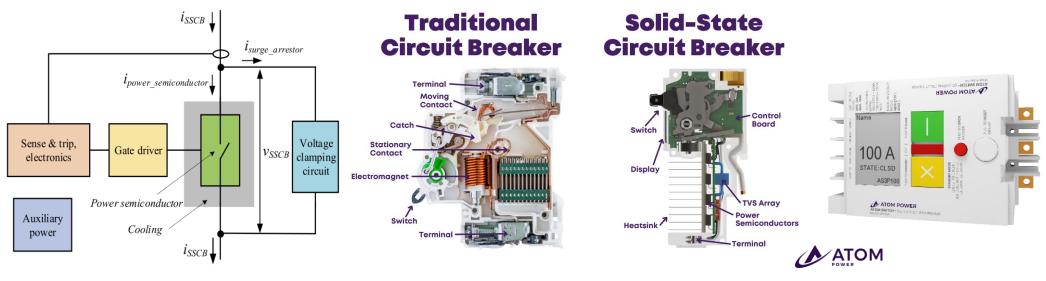


Rodrigues et al., 2021

- Recent LV Example w. Custom SiC Modules / Max. 100 A Cont. / UL Certified MBDSs Low On-Resistance Mandatory (e.g. 1100V, 22m $\Omega$  M-BDS GaN) | Low Leakage Current





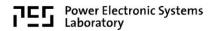











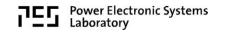

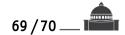

#### **Monolithic 3D-Integration**

Source: Panasonic ISSCC 2014

Isolated


dividing

DBM gate drive

transmitter chip


- M-BDS GaN 3x3 Matrix Converter with Drive-By-Microwave (DBM) Technology

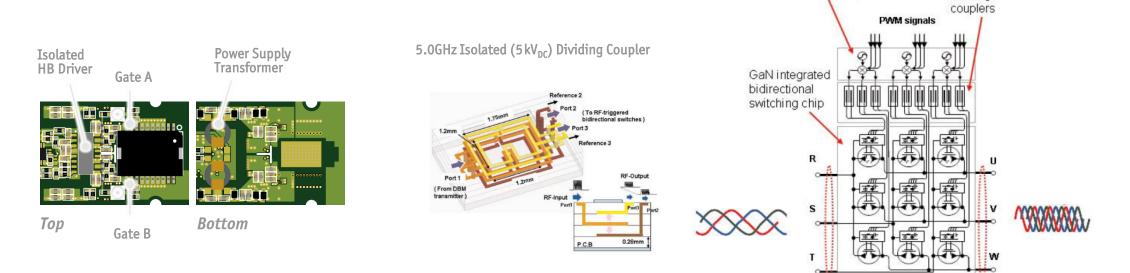- 9 Dual-Gate GaN AC-Switches / 4-Step Commutation DBM Gate Drive Transmitter Chip & Isolating Couplers Ultra Compact  $\rightarrow$  25 x 18 mm<sup>2</sup> (600V, 10A 5kW Motor) -



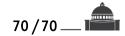
Massive Space Saving Compared to Discrete Realization (!) 







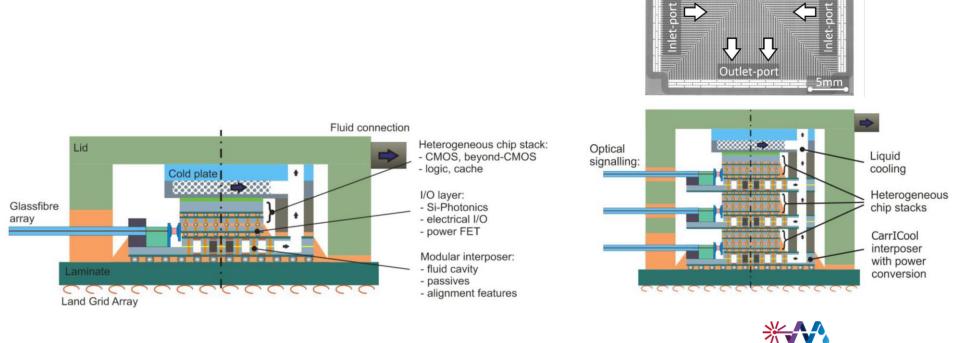- Slowing Transistor Node Scaling → Vertical & Heterogeneous Integr. of ICs for Performance Gains
   Extreme 3D-Integrated Cube-Sized Compute Nodes
   Dual Side & Interlayer Microchannel Cooling



• Interposer Supporting Optical Signaling / Volumetric Heat Removal / Power Conversion



**ICSCRM 2022** D\_VOS, Switzerland





# Thank you!



