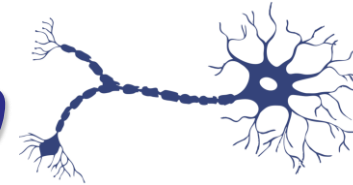


Future Power Electronics 4.0 *3- Φ SiC/GaN Converter Systems*



Johann W. Kolar & Jonas E. Huber

Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch

June 17, 2021



Outline

- ▶ *Introduction*
- ▶ *3- Φ PFC Rectifier Systems — Pt. I*
- ▶ *3- Φ VSD Inverter Systems — Pt. II*
- ▶ *Power Electronics 4.0 — Pt. III*
- ▶ *Conclusions*



M. Antivachis
J. Azurza
D. Bortis
D. Cittante
M. Guacci
M. Haider
F. Krismer
S. Miric
J. Miniböck
N. Nain
P. Niklaus
G. Rohner
F. Vollmaier
D. Zhang

Acknowledgement

Part I


3- Φ PFC Rectifier Systems

3rd Harmonic Injection
Vienna Rectifier & Buck-Boost Topologies
Two-Stage & Single-Stage Isolated Concepts



Application Areas

- *Electric Vehicle Battery Charging*
- *Datacenter Power Supply*
- *Renewable Energy Applications*

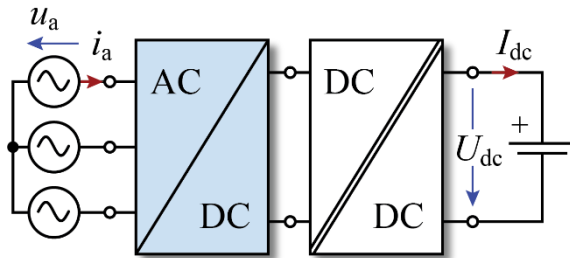Typ. $200 \dots 1000 V_{DC}$ EV Battery
Voltage Range



$320 \dots 530 V_{rms}$
Line-to-Line

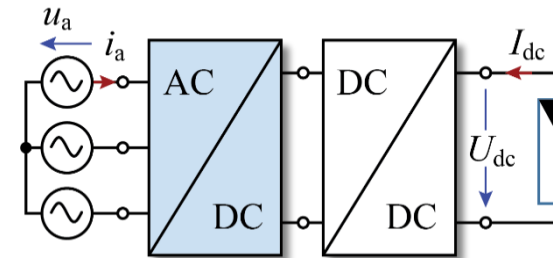
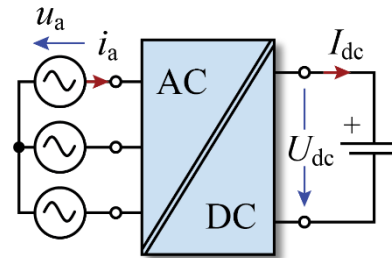


MPP Tracking in $60 \dots 90\%$ of
Max. Open Circuit Voltage

- *Isolated or Non-Isolated Output*
- *Wide AC Input / DC Output Voltage Range*
- *Unidirectional or Bidirectional Power Transfer*

3- Φ Diode Bridge Rectifier

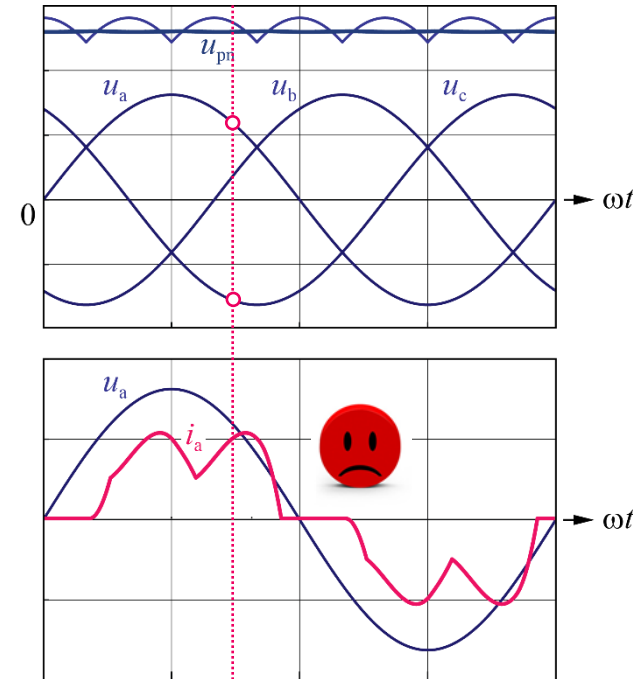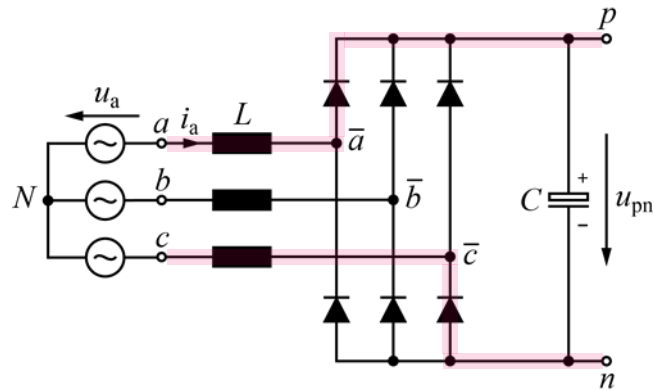- Conduction States Defined by *Line-to-Line* Mains Voltages
- Intervals with Zero Current / LF Harmonics
- No Output Voltage Control




→ Active Mains Current Shaping / Simultaneous Current Flow in All Phases

———— ***3rd Harmonic Current Injection*** ————

Integrated Active Filter (IAF) PFC Rectifier

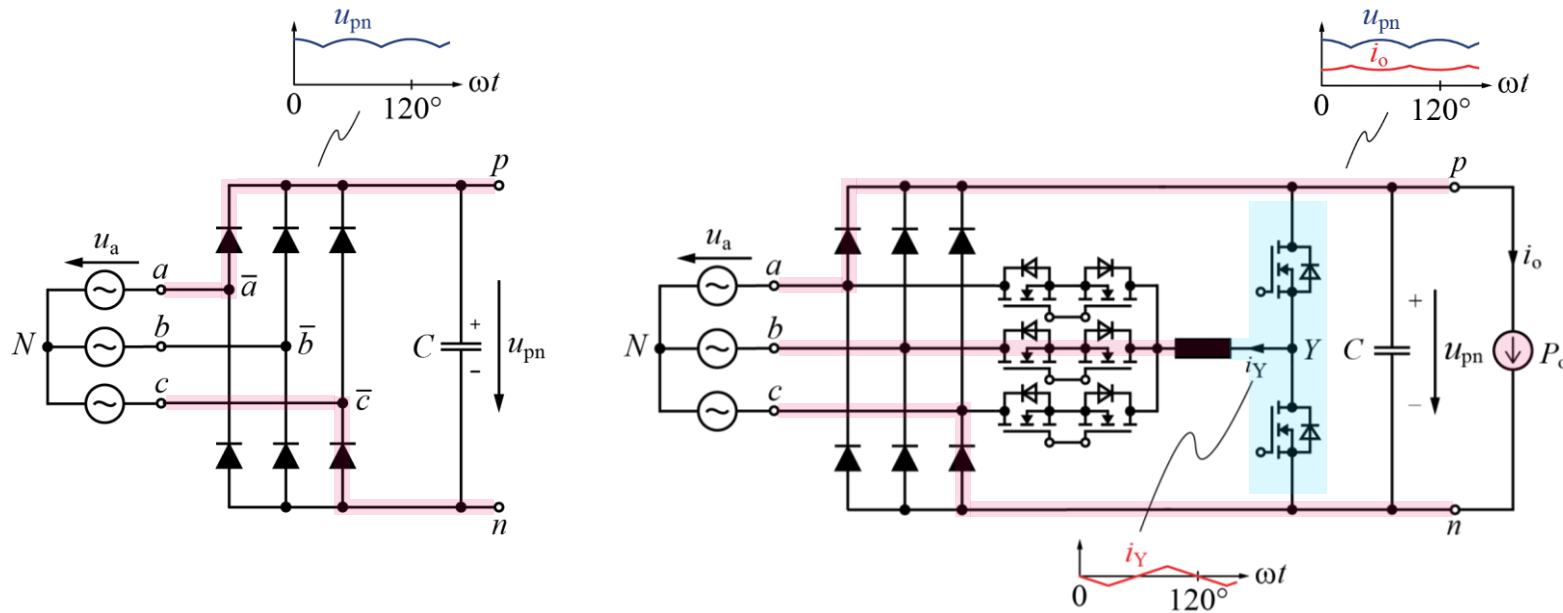- **3rd Harmonic Current Injection** into Phase with Lowest Voltage
- **Phase Selector AC Switches** Operated @ Mains Frequency




- **Non-Sinusoidal Mains Current**

- $P_0 = \text{const. Required}$
- *Sinusoidal Mains Current*
- *NO (!) DC Voltage Control*

IAF Rectifier (2)

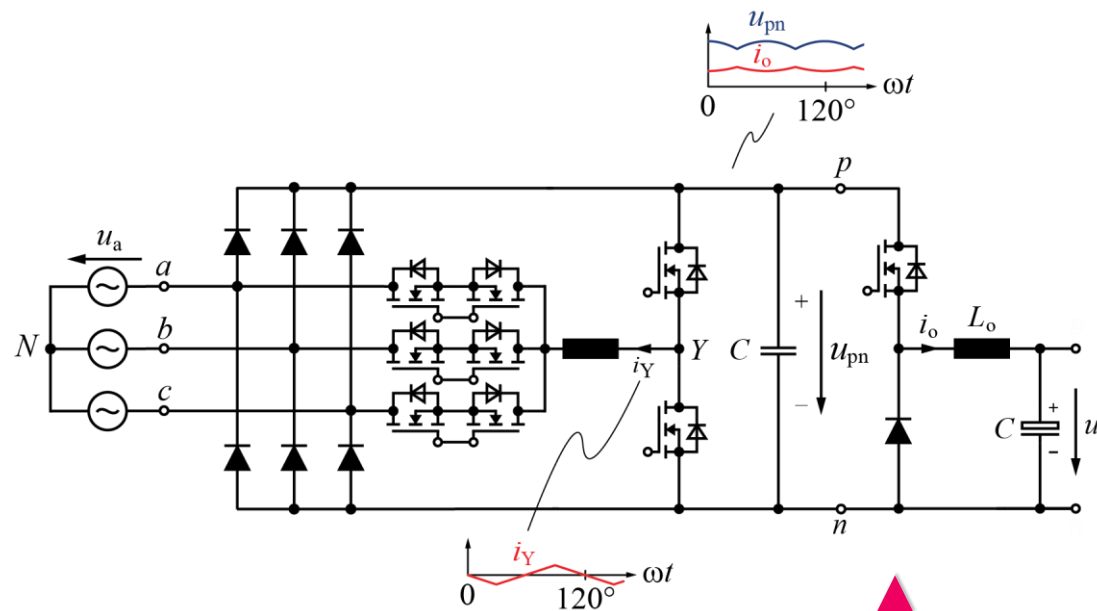- *Buck-Output Stage* → $P_o = \text{const.}$ & *Output Voltage Control*
- *Sinusoidal Mains Current*



- *Buck-Stage Could be Replaced by Isolated DC/DC Conv. or Inverter*


IAF Rectifier Demonstrator

- Efficiency $\eta > 99.1\%$ @ 60% Rated Load
- Mains Current $THD_I \approx 2\%$ @ Rated Load
- Power Density $\rho \approx 65\text{W/in}^3$



$$P_o = 8 \text{ kW}$$

$$U_N = 400\text{V}_{AC} \rightarrow U_o = 400\text{V}_{DC}$$

$$f_s = 27\text{kHz}$$


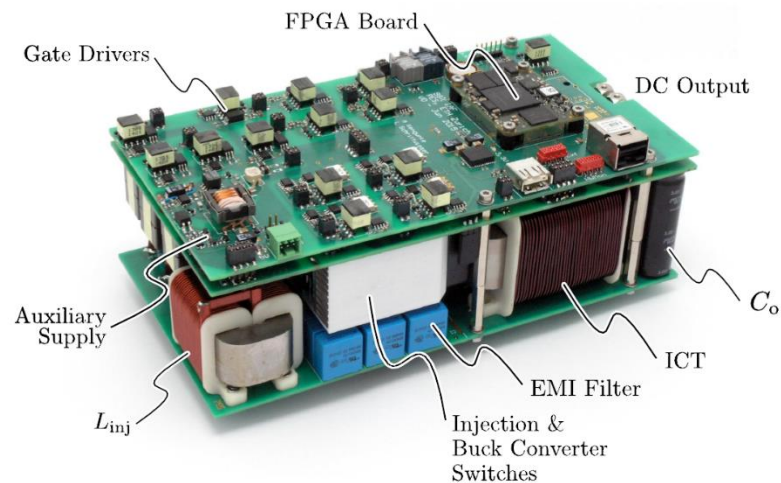


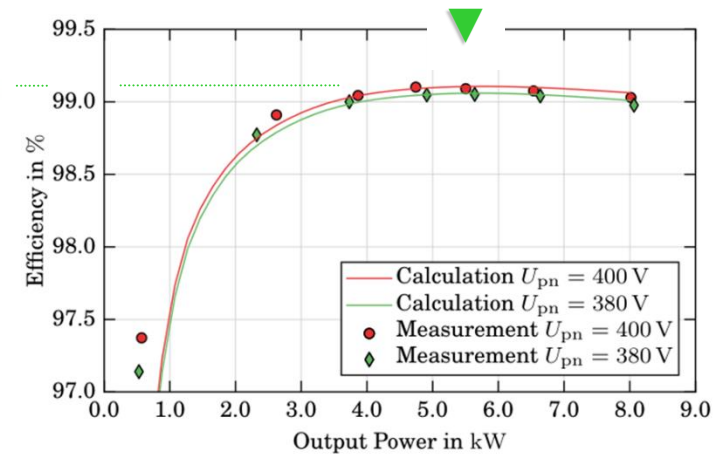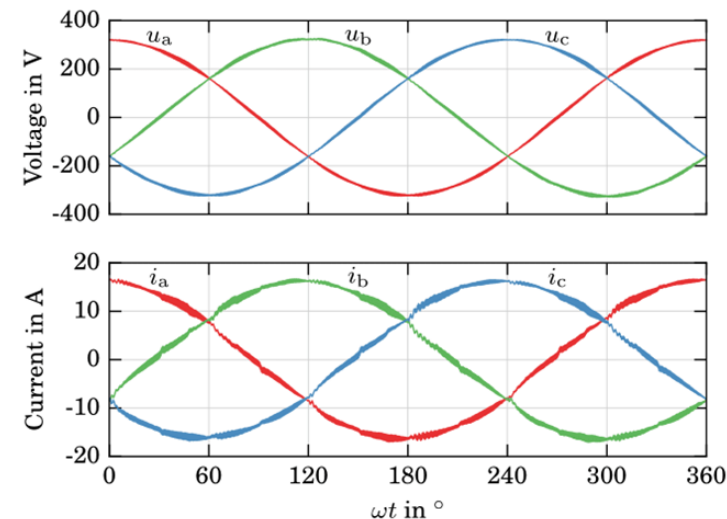- SiC Power MOSFETs & Diodes
- 2 Interleaved Buck Output Stages



Swiss Rectifier

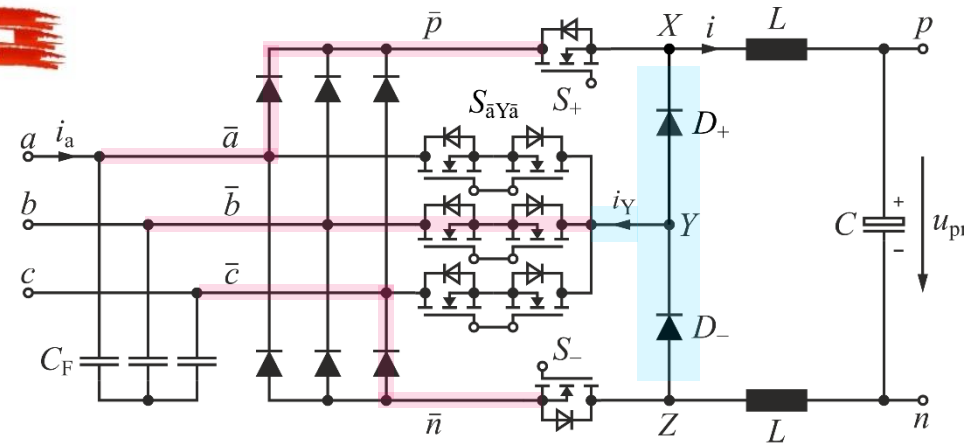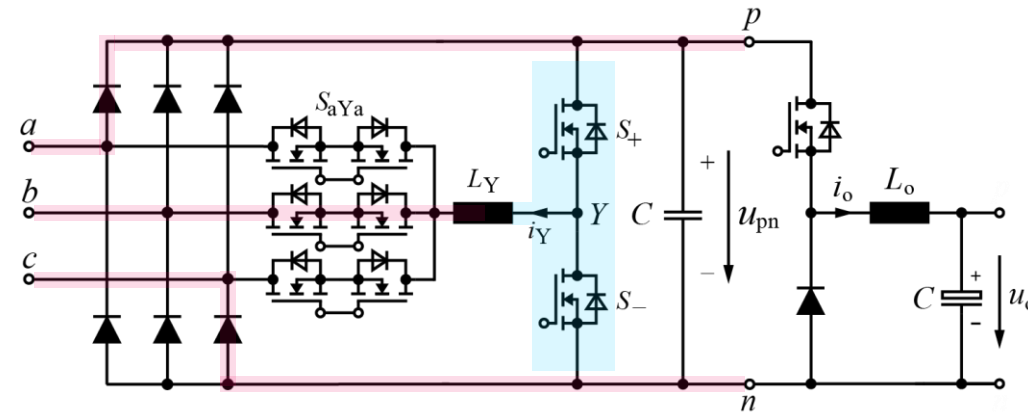- Integration of Injector Switches & Buck Output Stage
- Controlled Output Voltage
- Sinusoidal Mains Current
- i_y Def. by KCL: E.g. $i_a - i_c$




- Low Complexity


Swiss Rectifier Demonstrator

- Efficiency $\eta = 99.26\%$ @ 60% Rated Load
- Mains Current $THD_I \approx 0.5\%$ @ Rated Load
- Power Density $\rho \approx 65\text{W/in}^3$
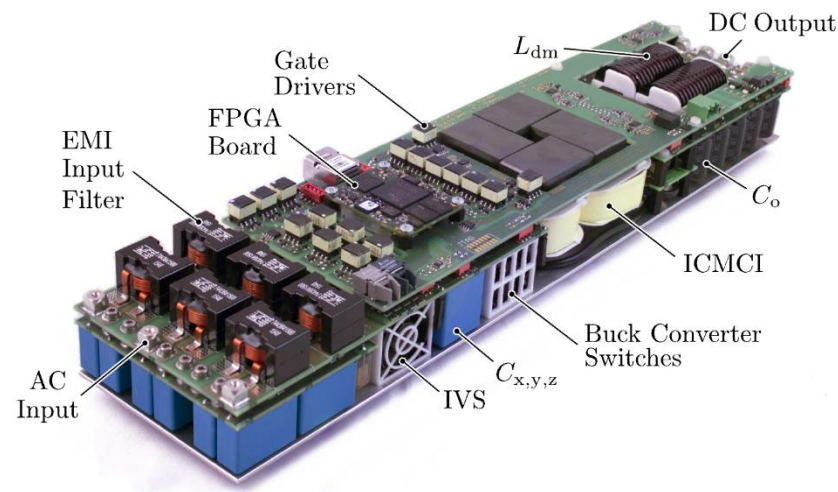
$$\begin{aligned} P_o &= 8 \text{ kW} \\ U_N &= 400\text{V}_{\text{AC}} \rightarrow U_o = 400\text{V}_{\text{DC}} \\ f_s &= 27\text{kHz} \end{aligned}$$




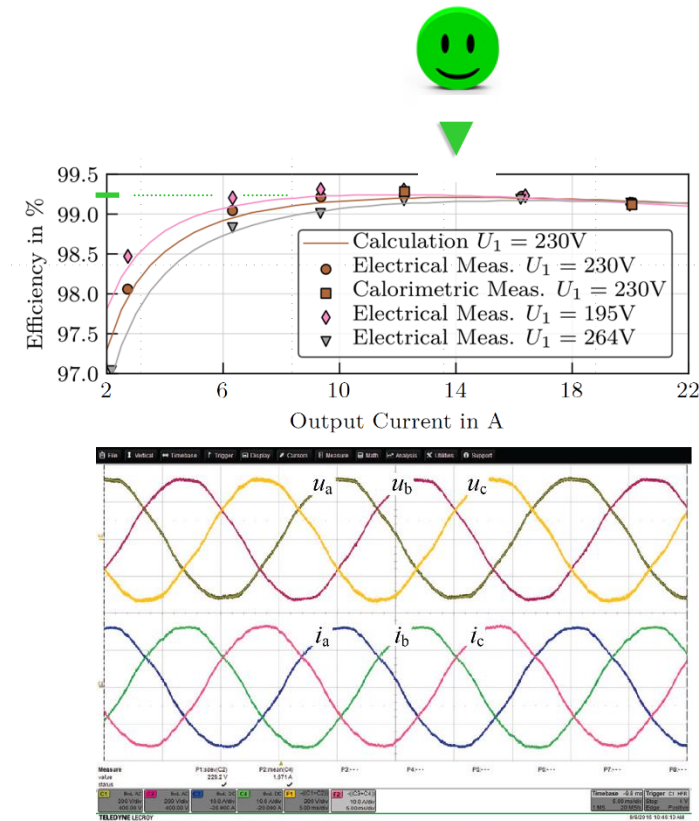- SiC Power MOSFETs & Diodes
- Integr. CM & Output Coupling Inductors (ICMCI)




Remark Monolithic GaN Bidirectional Switch

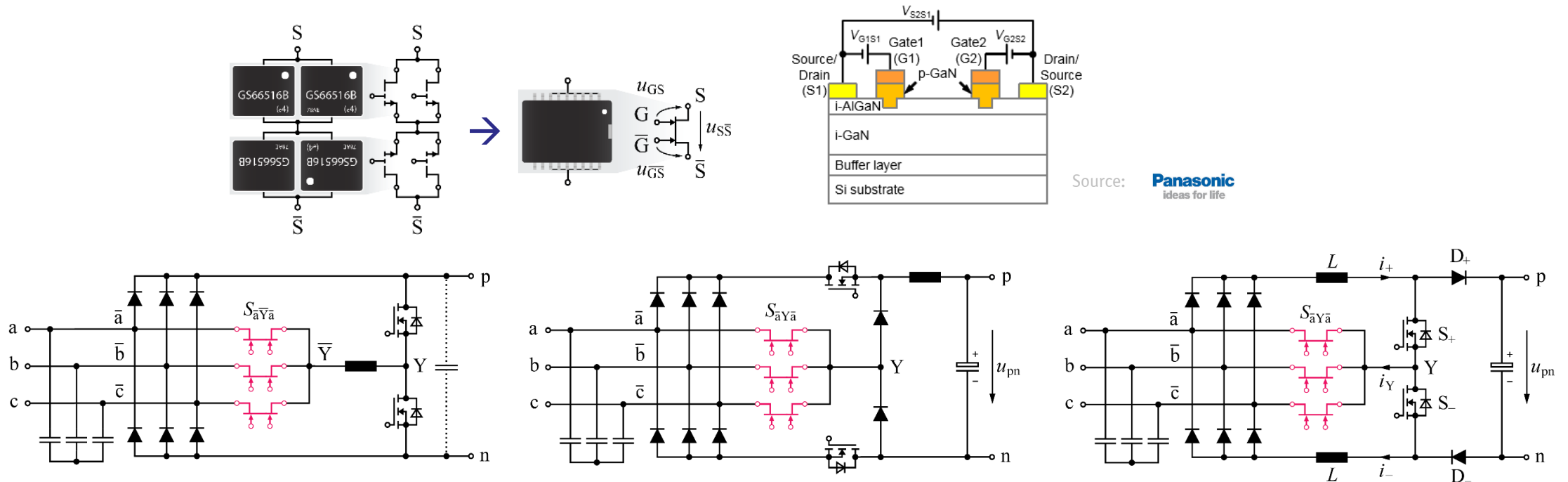- **Bipolar Voltage Blocking Capability**
- **2 Gates** → **Controllability of Both Current Directions**
- **Factor of 4 Reduction of Chip Area Comp. to Discrete Realization of Same $R_{(on)}$**









- **M-BDS Application for Phase Selector Switches of 3rd Harmonic Inj. PFC Rectifiers**

600V GaN Monolithic Bidir. Switch

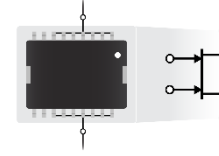

- **POWERAMERICA Project** — Based on Infineon's 600V CoolGaN™ Technology 
- **Dual-Gate Device / Controllability of Both Current Directions**
- **Bipolar Voltage Blocking Capability | Normally-On or -Off**

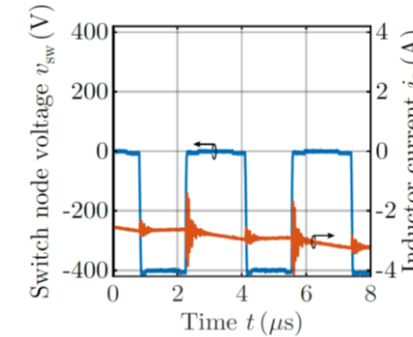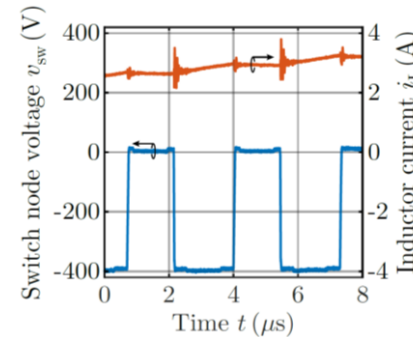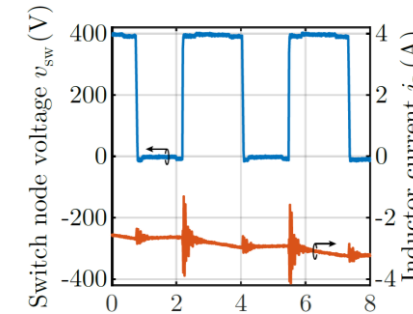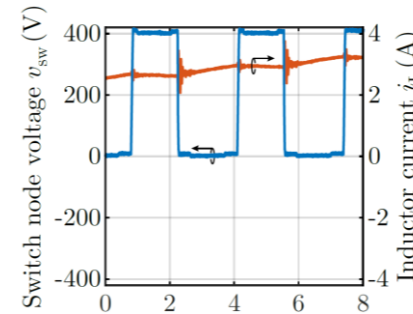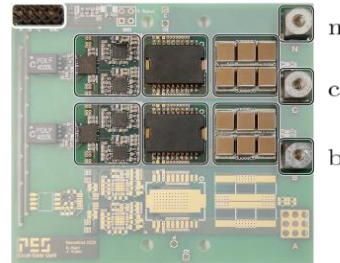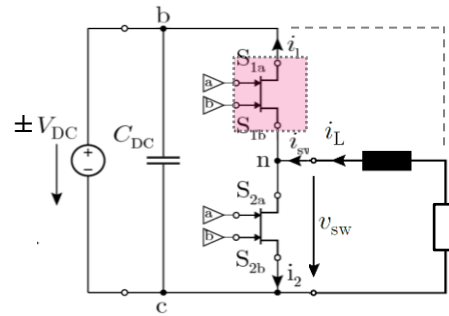


- **Analysis of 4-Quadrant Operation of $R_{(on)} = 140\text{m}\Omega$ Sample @ $\pm 400\text{V}$**

———— *Active Control of Diode Bridge
Conduction States* ————

Vienna Rectifier (1)


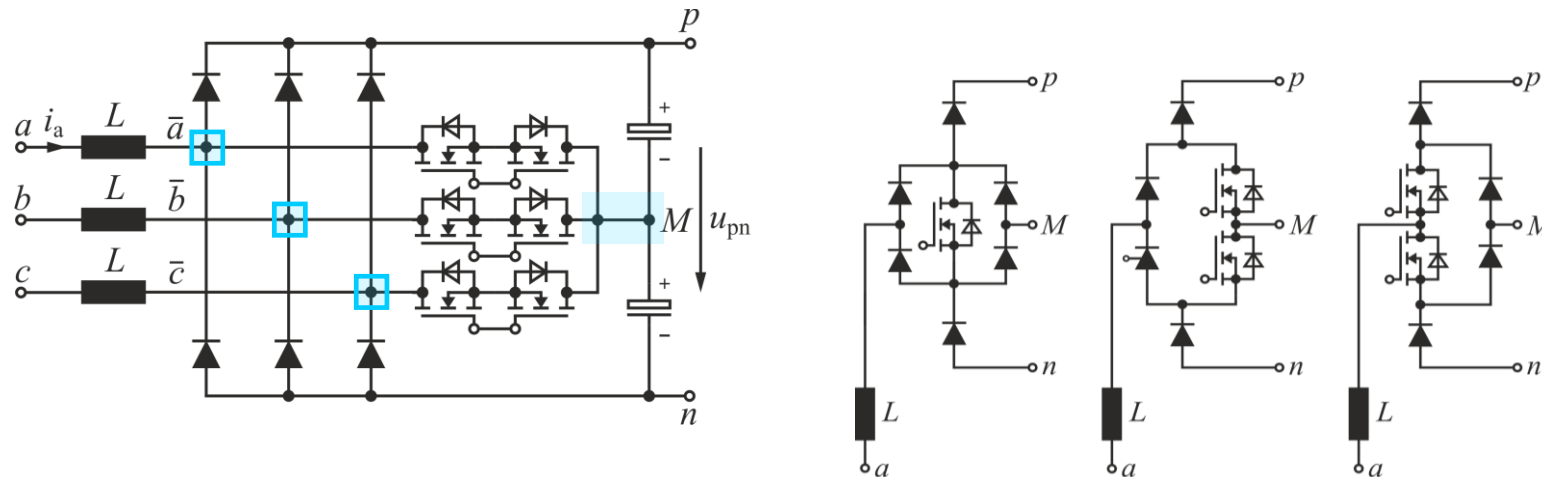
- *Active Control of Diode Bridge Conduction States / Input Voltages*
- Bridge Leg Topologies with Different Voltage Stresses / Cond. Losses
- Phase & Bridge Symmetry !



→ Analysis of Input Voltage Formation

Vienna Rectifier (2)


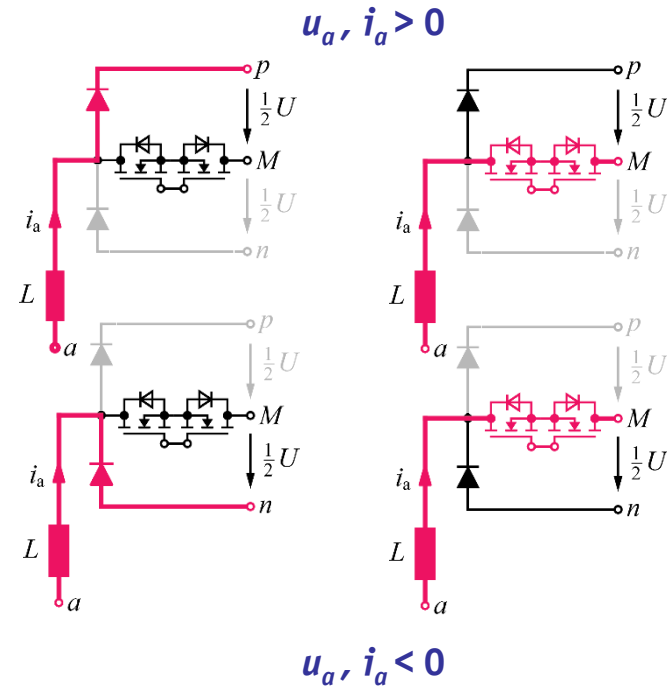
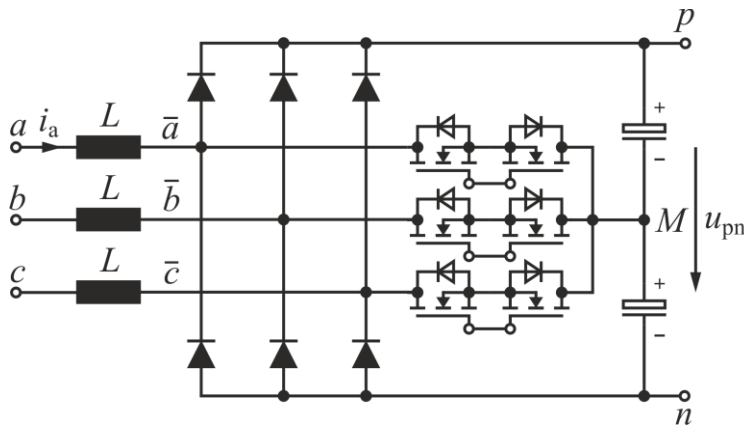
- Diode Bridge Input Voltage Formation Dependent on Current Direction & Sw. State
- Min. Output Voltage Defined by Mains Line-to-Line Voltage Amplitude
- Boost-Type



→ Sinusoidal Input Current Shaping

Vienna Rectifier (3)

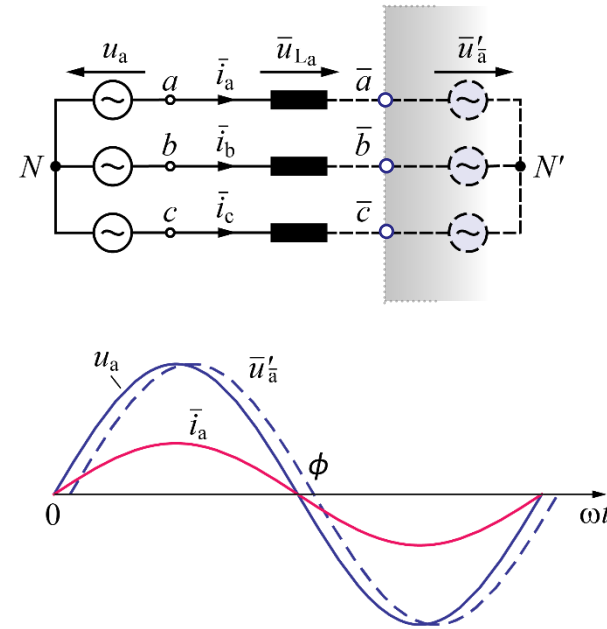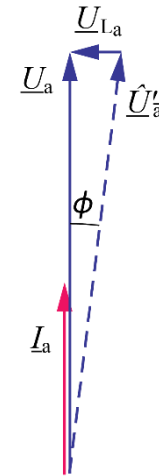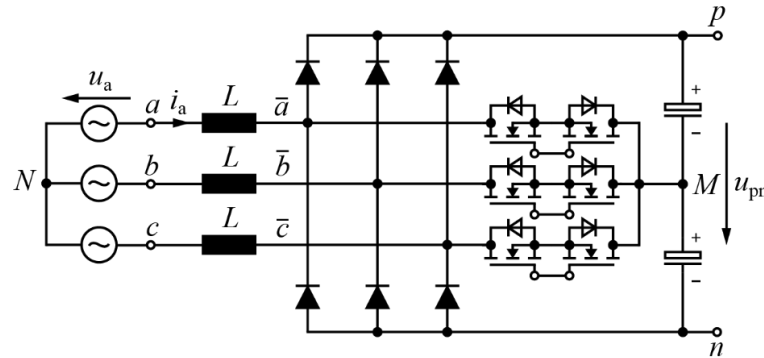
- *Input Current Impressed by Difference of Mains & Diode Bridge Input Voltage*
- $\Phi = (-30^\circ, +30^\circ)$ *Limit Due to Current-Dependent Voltage Formation*




→ Time Behavior of PWM Voltages

Vienna Rectifier (4)

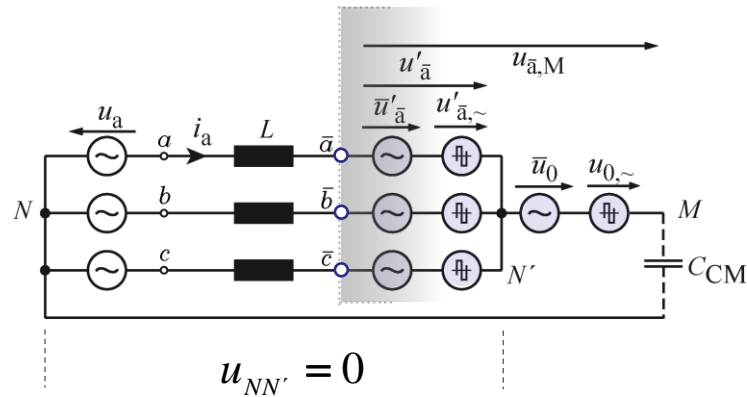- 3-Level Bridge-Leg Characteristic / 9-Level Current Impressing Phase Voltage
- Low Input Current Ripple / Low Inductance L
- Switching Frequency CM Output Voltage




→ CM EMI Filtering

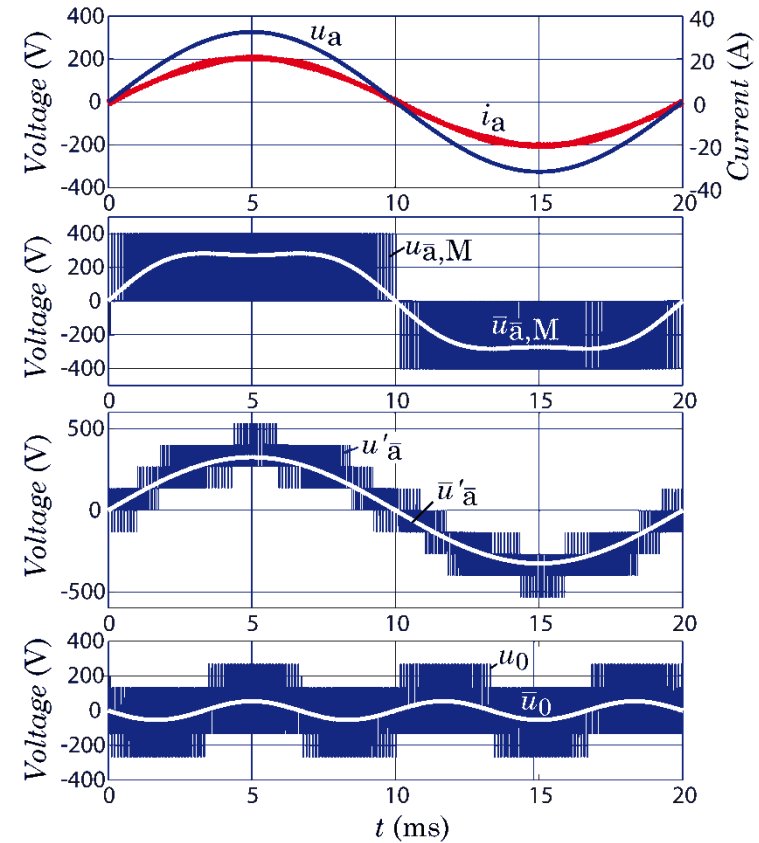

Vienna Rectifier (5)

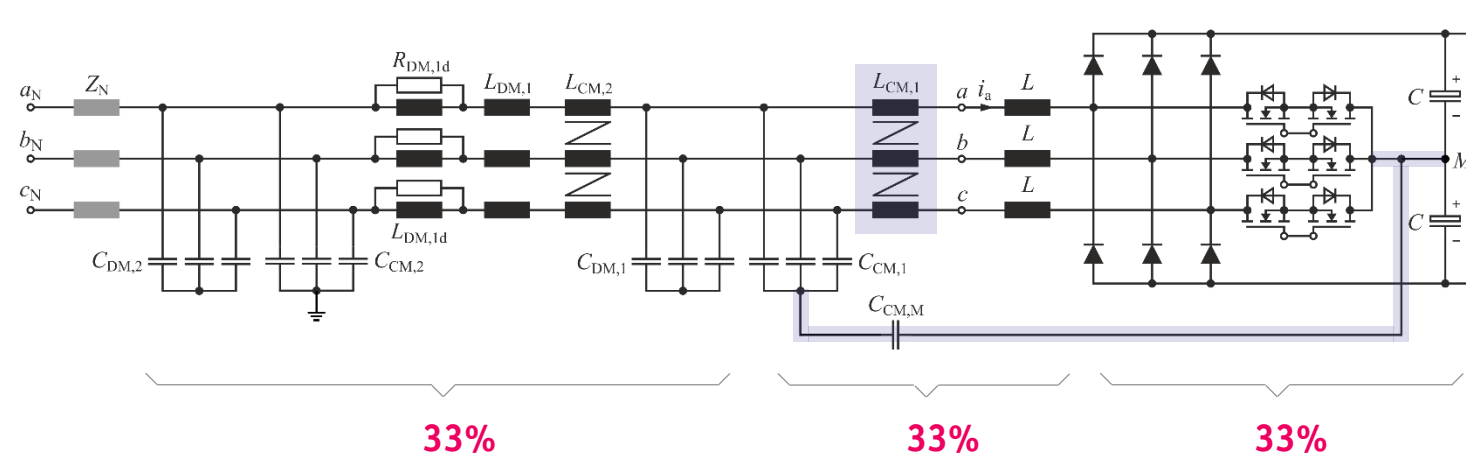- *CM EMI Filtering / Internal Cap. Connection to Virtual Star Point*
- No Limit of CM Capacitance by Max. Leakage Current
- CM Filter Stage(s) on DC-Side as Alternative



- Number of Filter Stages Dependent on Sw. Frequency

Vienna Rectifier (7)



- Highly-Compact Demonstrator System
- CoolMOS & SiC Diodes
- Coldplate Cooling

$$\begin{aligned} P_o &= 10 \text{ kW} \\ U_N &= 400\text{V}_{\text{AC}} \pm 10\% \\ f_N &= 50\text{Hz or } 360 \dots 800\text{Hz} \\ U_o &= 800\text{V}_{\text{DC}} \end{aligned}$$

$$\eta = 96.8\%$$

$$\star \rho = 165 \text{ W/in}^3$$

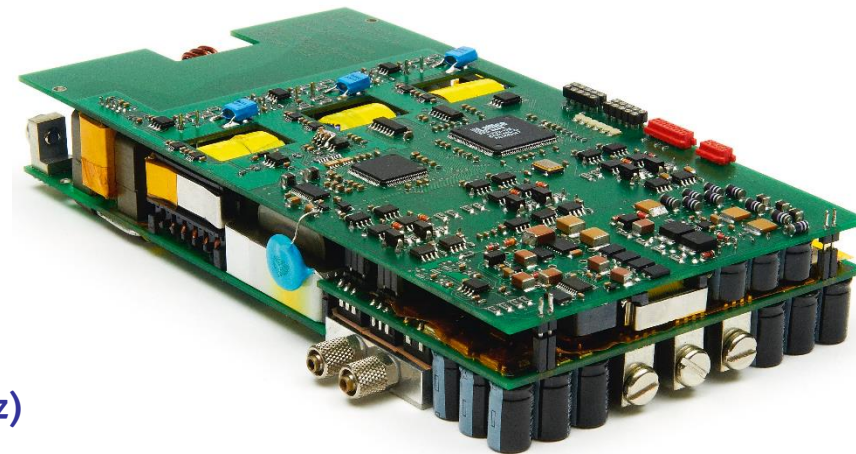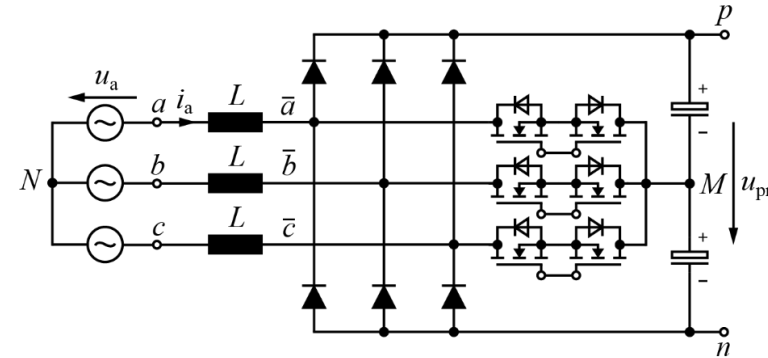- $THD_i = 1.6\% @ f_N = 800\text{Hz} (f_p = 250\text{kHz})$




Vienna Rectifier (8)

- Highly-Compact Demonstrator System
- CoolMOS & SiC Diodes
- Coldplate Cooling


$P_o = 10 \text{ kW}$
 $U_N = 400 \text{ V}_{AC} \pm 10\%$
 $f_N = 50 \text{ Hz or } 360 \dots 800 \text{ Hz}$
 $U_o = 800 \text{ V}_{DC}$

$\eta = 96.8\%$
 $\rho = 165 \text{ W/in}^3 \text{ (} 10 \text{ kW/dm}^3 \text{)}$
 $f_p = 250 \text{ kHz}$

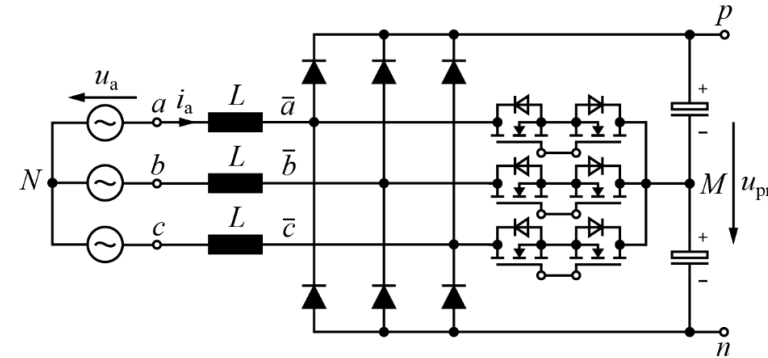- $THD_i = 1.6\% \text{ @ } f_N = 800 \text{ Hz}$
- System Allows 2- Φ Operation





10A/Div
 200V/Div
 0.5ms/Div

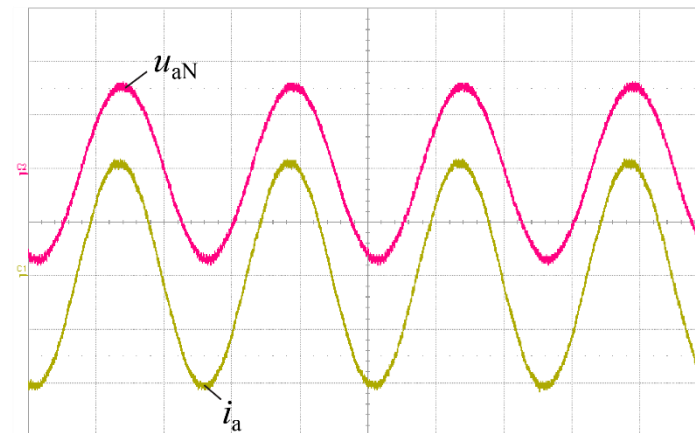

Vienna Rectifier (9)


- Dependency of Power Density on Sw. Frequency f_p
- CoolMOS & SiC Diodes
- Coldplate Cooling

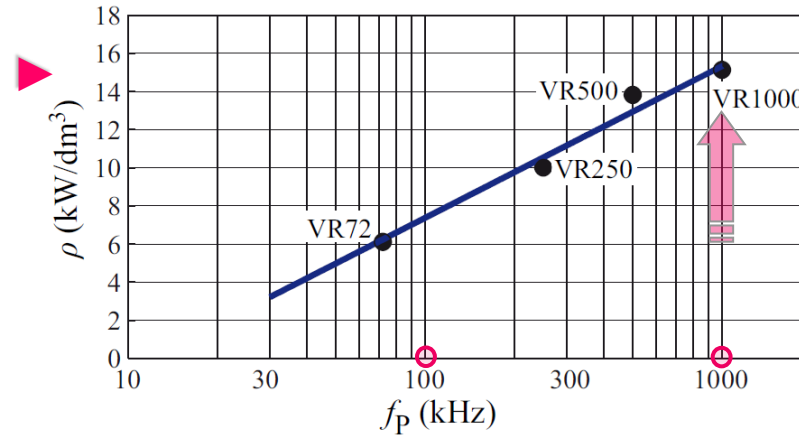
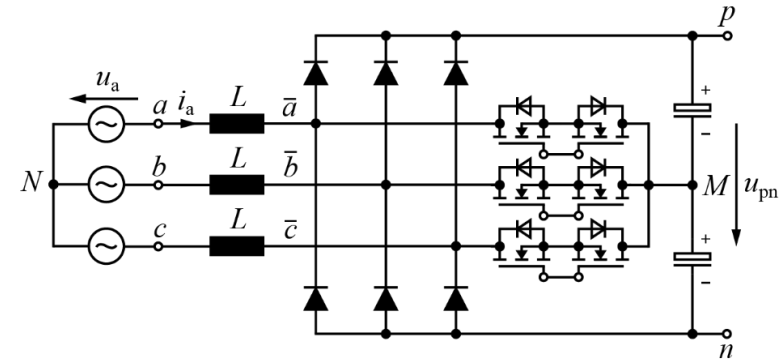
$$\begin{aligned} P_o &= 10 \text{ kW} \\ U_N &= 230V_{AC} \pm 10\% \\ f_N &= 50\text{Hz or } 360 \dots 800\text{Hz} \\ U_o &= 800V_{DC} \end{aligned}$$



- Factor 10 in $f_p \rightarrow$ Factor 2 in Power Density
- Systems with $f_p = 72/250/500/1000\text{kHz}$

Remark Application of GaN M-BDS (1)

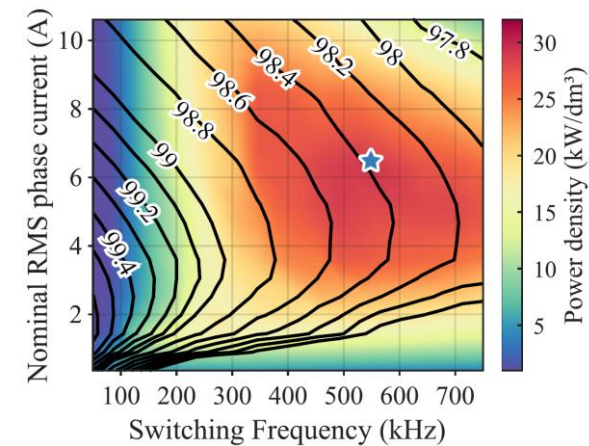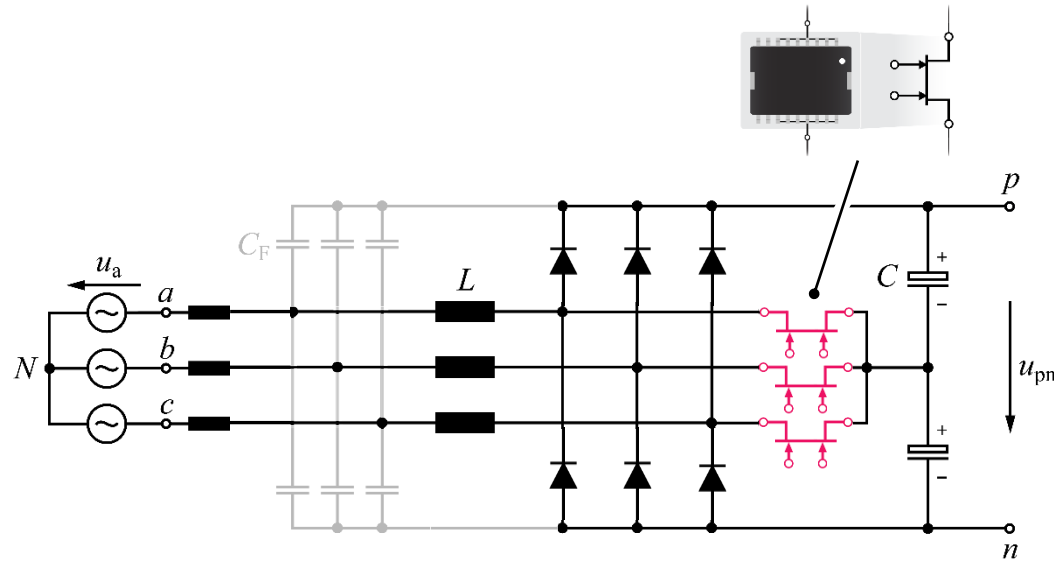
- *Vienna Rectifier*
- *600V GaN Monolithic Bidirectional Switch (M-BDS) @ $U_{pn} = 800V$, $R_{(on)} = 140m\Omega$* 
- *Continuous Current Mode, $L = 33\mu H$, $f_{sw} = 620kHz$*
- *1200V SiC Diodes*




- *Max. Power Density of $25kW/dm^3$ (w/o Full EMI Filter) @ 98.4% Efficiency*

Remark Application of GaN M-BDS (2)

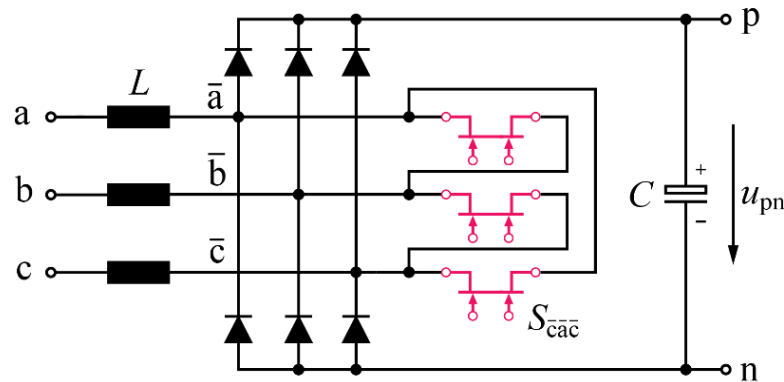- *Δ -Switch Rectifier*
- *600V M-BDSs for 115V / 360...800Hz Aircraft Applications*
- *Low Conduction Losses / No DC-Link Midpoint Required*


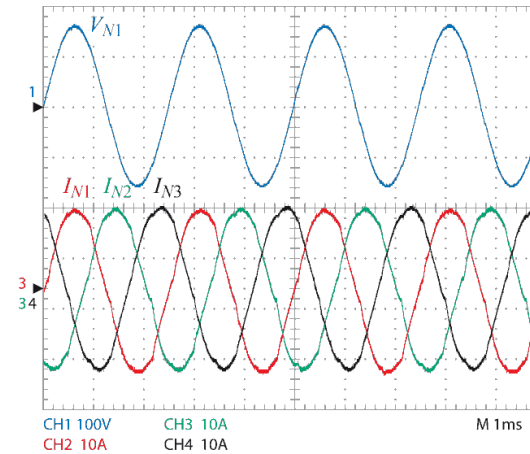
$$\begin{aligned} U_{LL} &= 115 \text{ V@400Hz} \\ U_o &= 400 \text{ V} \\ THD_I &= 2.3\% \end{aligned}$$



- *Always Only 2 Switches are Operated*
- *Phase Current Controller Outputs Transformed into Δ -Quantities*



Comparative Evaluation

—— *3L-Topology* vs. *2L-Topology* ——





Comparative Evaluation (1)

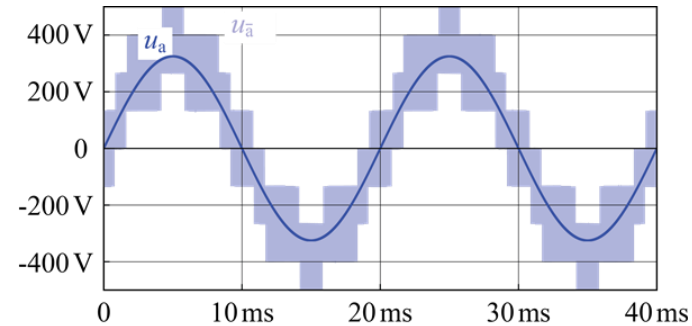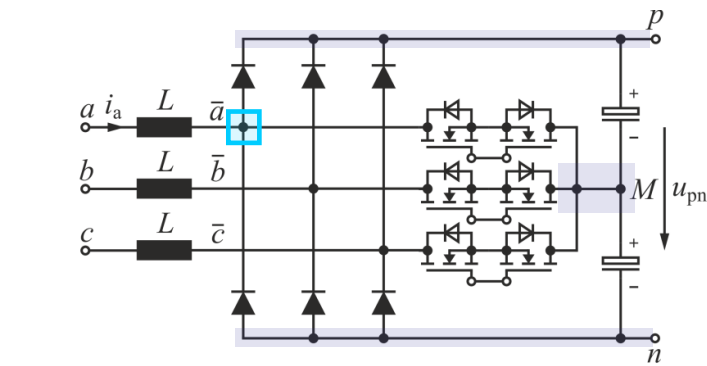- Comparison of 3-Level to Standard 2-Level PWM Rectifier
- 9 vs. 5 Volt. Levels & Factor 2...3 Lower Sw. Losses → Factor 4...6 (!) Lower L




■ Vienna Rectifier

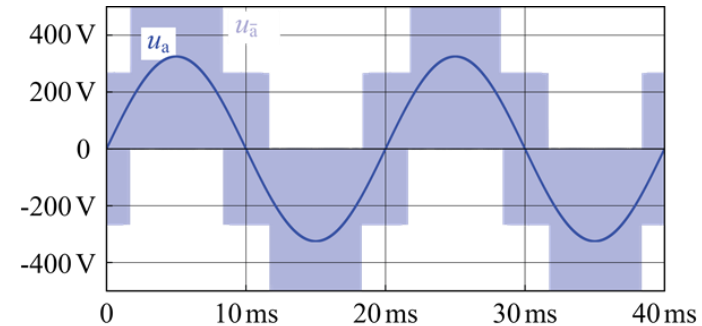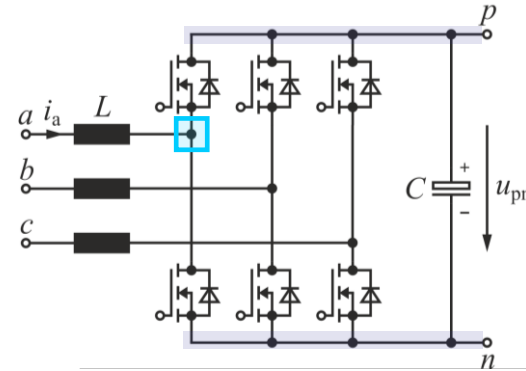


■ Standard PWM Rectifier

Comparative Evaluation (2)

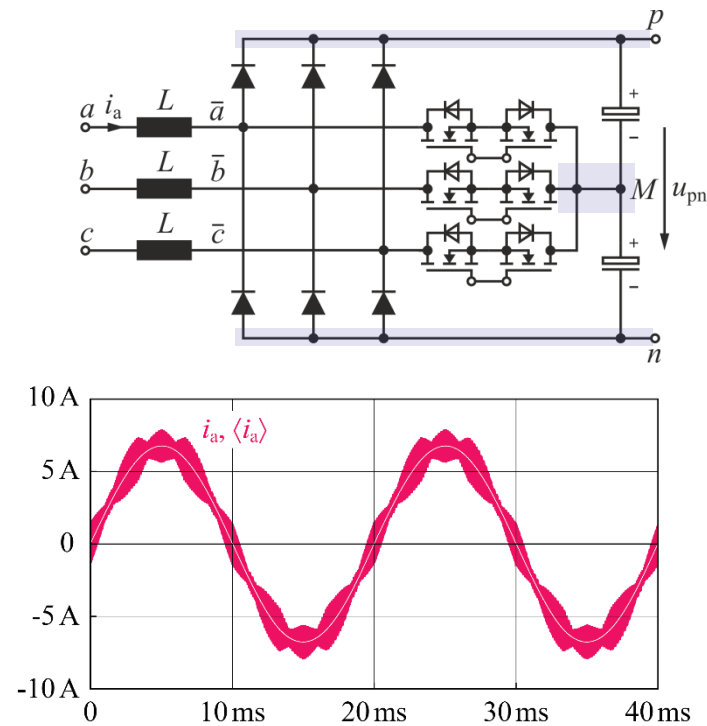- Comparison of 3-Level to Standard 2-Level PWM Rectifier
- 9 vs. 5 Volt. Levels & Factor 2..3 Lower Sw. Losses → 12 kW/dm³ vs. 8 kW/dm³ @ 22kW



■ Vienna Rectifier

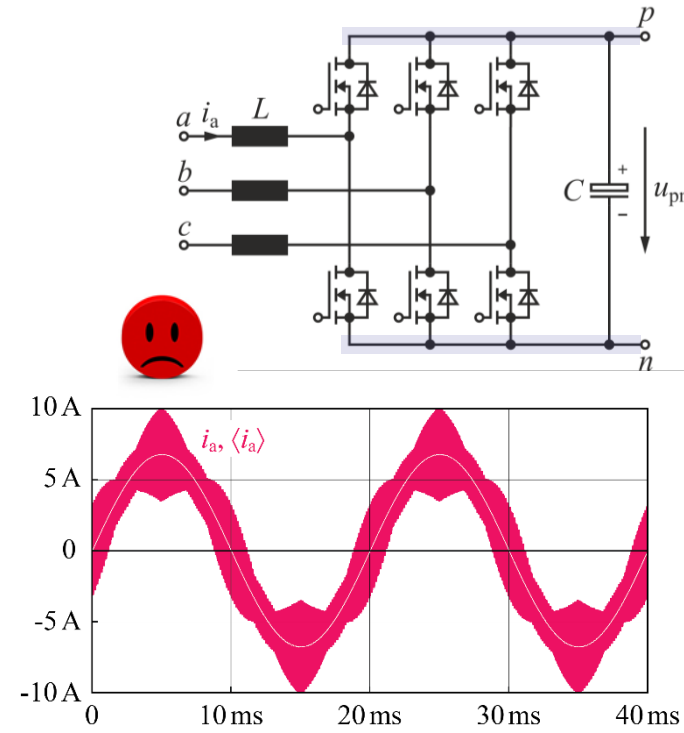


■ Standard PWM Rectifier

Vienna Rectifier — Conceptual Limits



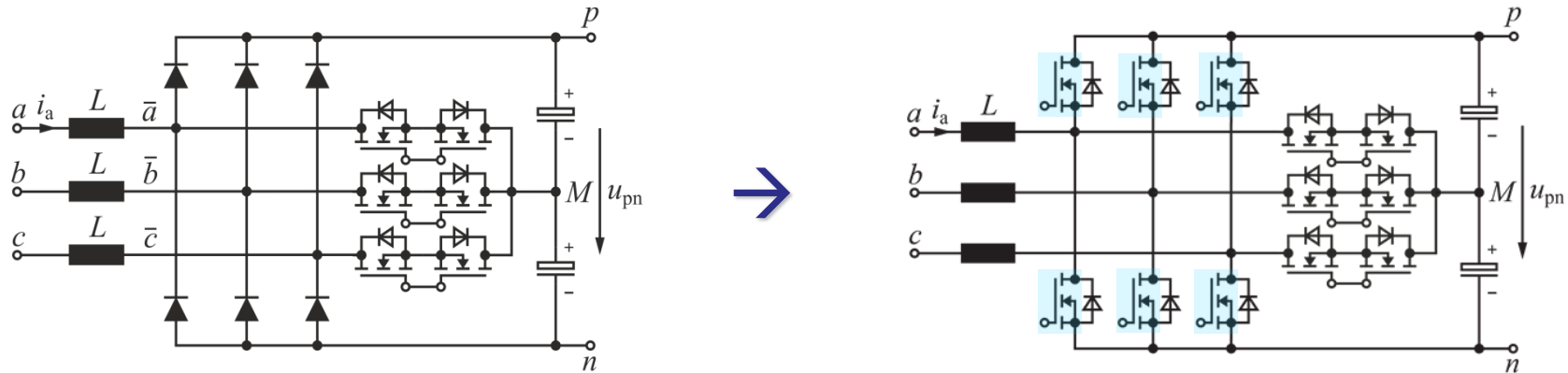- *Boost-Type*
- *No Isolation*
- *Unidirectional (in Basic Form)*



→ Buck-Boost & Buck-Type Topologies / Isolated Systems


Buck+Boost-Type

Y-Rectifier



Buck+Boost PFC Y-Rectifier


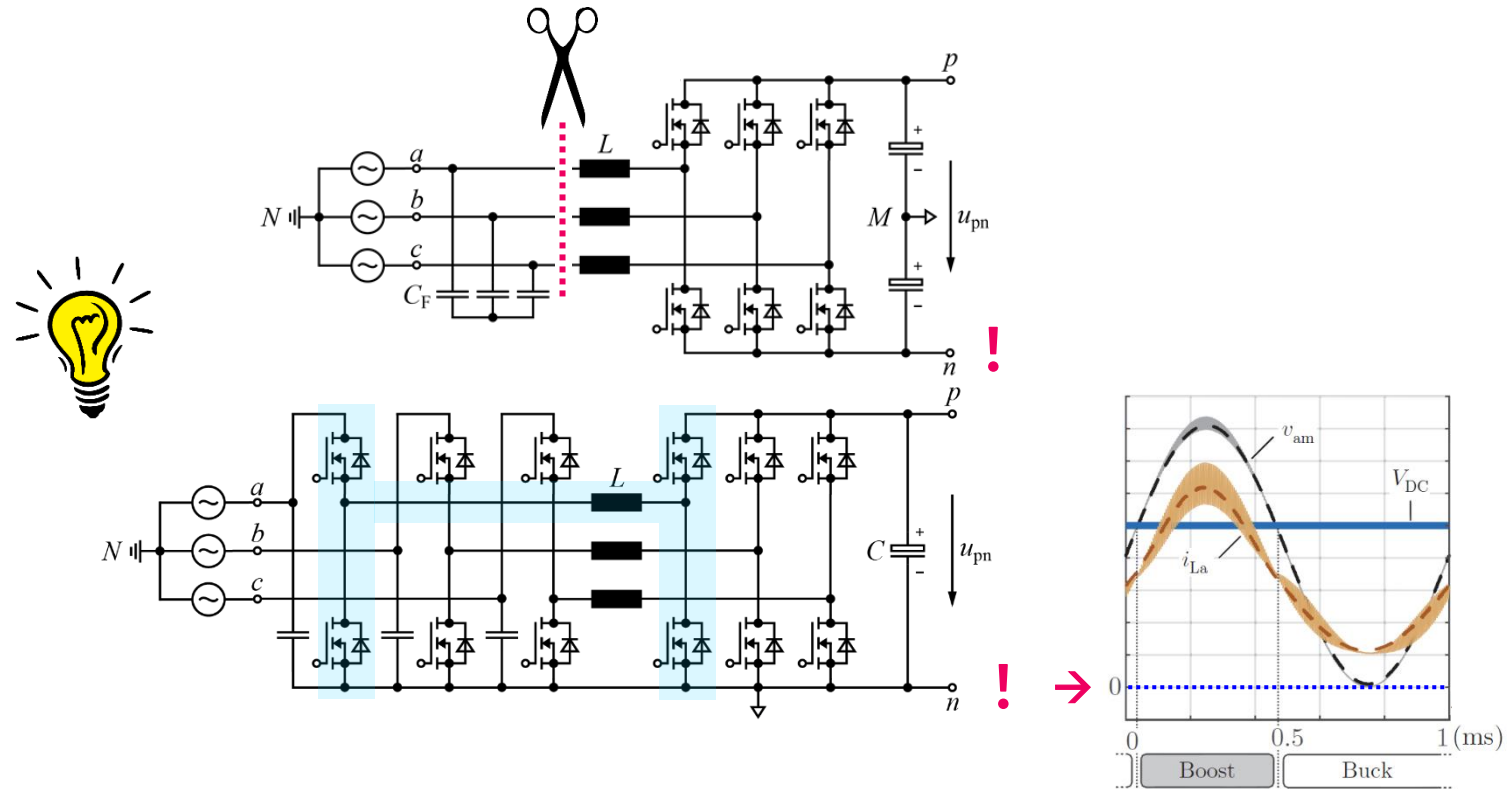
- *Switching Stage of 2-Level PFC Rectifier* → *3 DC/DC Boost-Converters w/ Ref. to Neg. DC-Link Rail*
- *Insert Front-End Buck-Stage / Phase* → *Buck+Boost Operation*



- *Bidirectional* & *Wide Input / Output Voltage Range*

Y-Rectifier

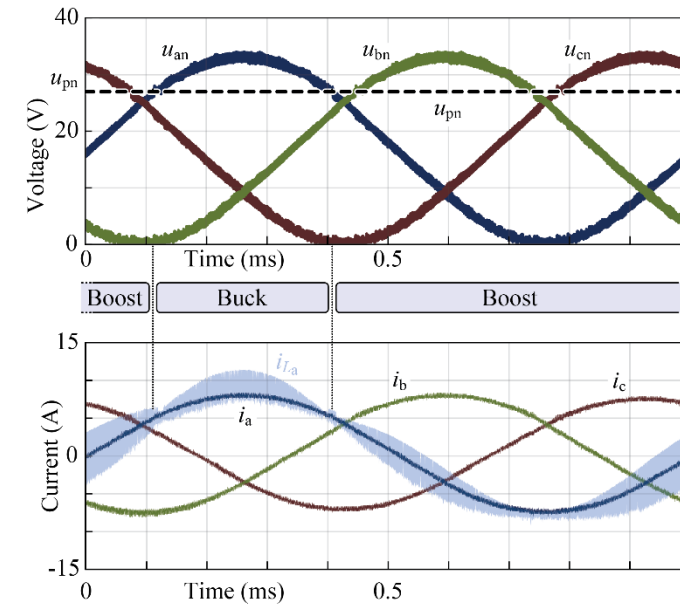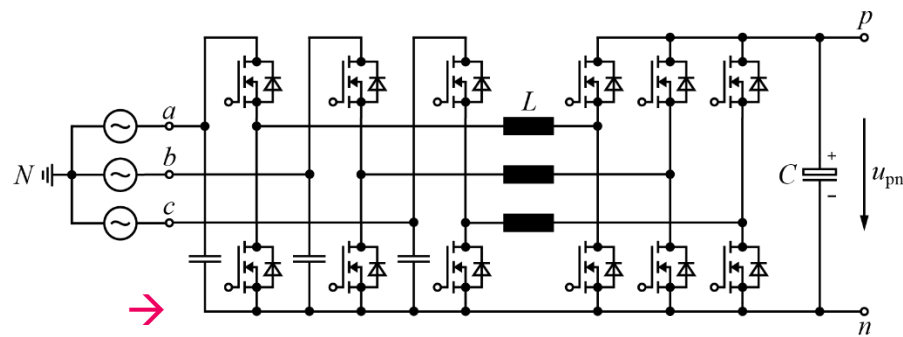
- **Rectifier Input Filter Inductor Used as Buck-Boost Inductor**
- **Allows Inverter Operation with Continuous Output Voltage (!)**
- **All-GaN Demonstrator**




- **Bidirectional & Wide Input / Output Voltage Range**

Y-Rectifier vs. 3- Φ Cuk-Type Rectifier

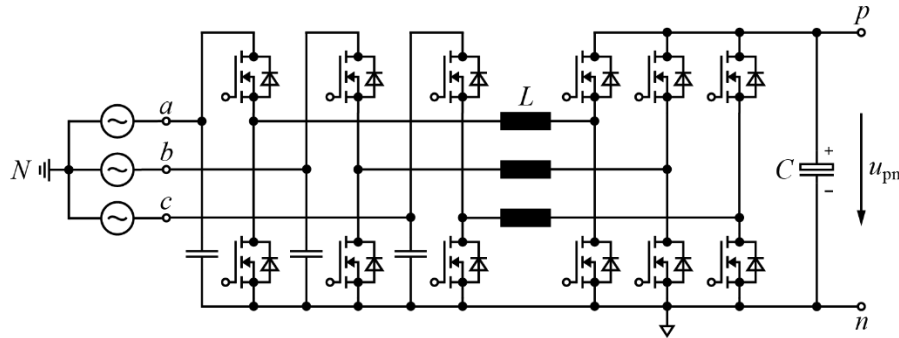- 3 Main Inductive Components
- 12 Power Transistors Blocking U_{in} OR U_{out}
- Discontinuous Input & Output Current



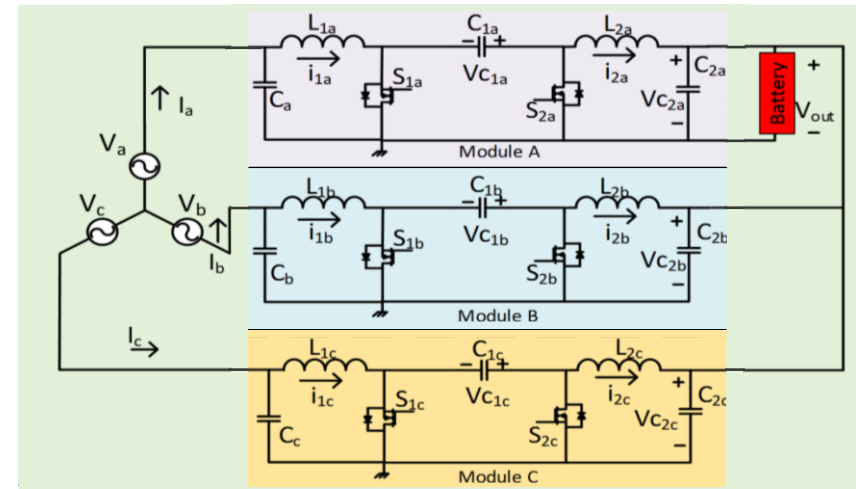- 6 Main Inductive Components
- 6 Power Transistors Blocking U_{in} AND U_{out}
- Continuous Input & Output Current





Source: N. Kumar, S. Mazumder, A. Gupta | 2018

- Bidirectional & Wide Input / Output Voltage Range

3- Φ I-DC-Link Buck-Boost Rectifier

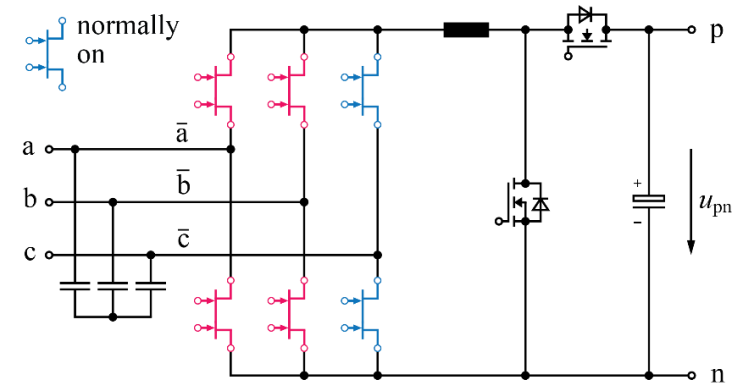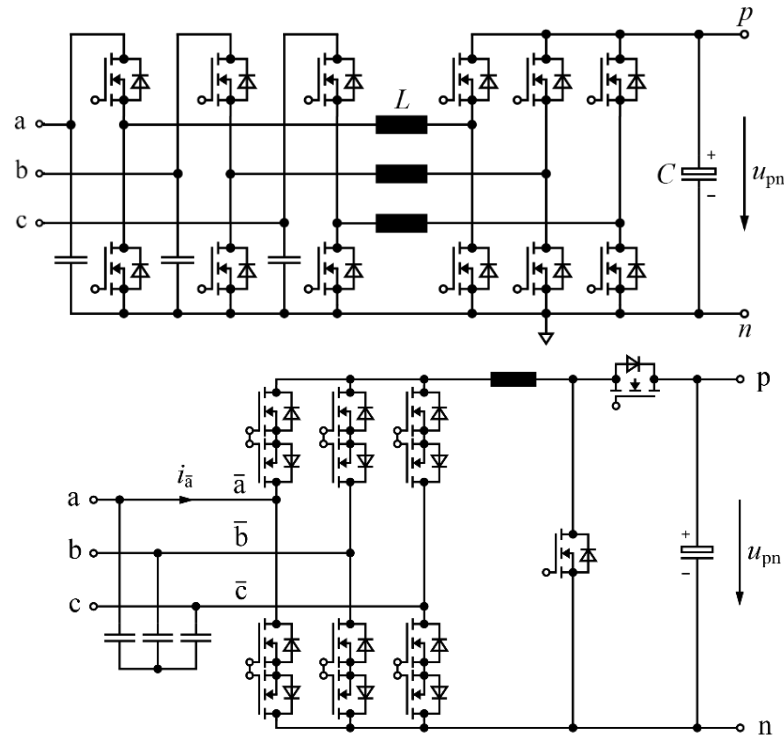- *Combination of Y-Rectifier Boost-Stages*
- *Main Power Circuit w/ Single Inductor*
- *Input-Side AC-Switches*



- *Low Complexity Realization w/ Monolithic Bidirectional Switches*

Isolated 3- Φ PFC Rectifier Systems

*Synergetic Control
Matrix-Type Isolated Topology*




Selected EV-Charger Topology

- **Isolated** Controlled Output Voltage
- **Buck-Boost** Functionality & Sinusoidal Input Current
- **Applicability of 600V GaN Semiconductor Technology**
- **High Power Density / Low Costs**




Source: SIEMENS

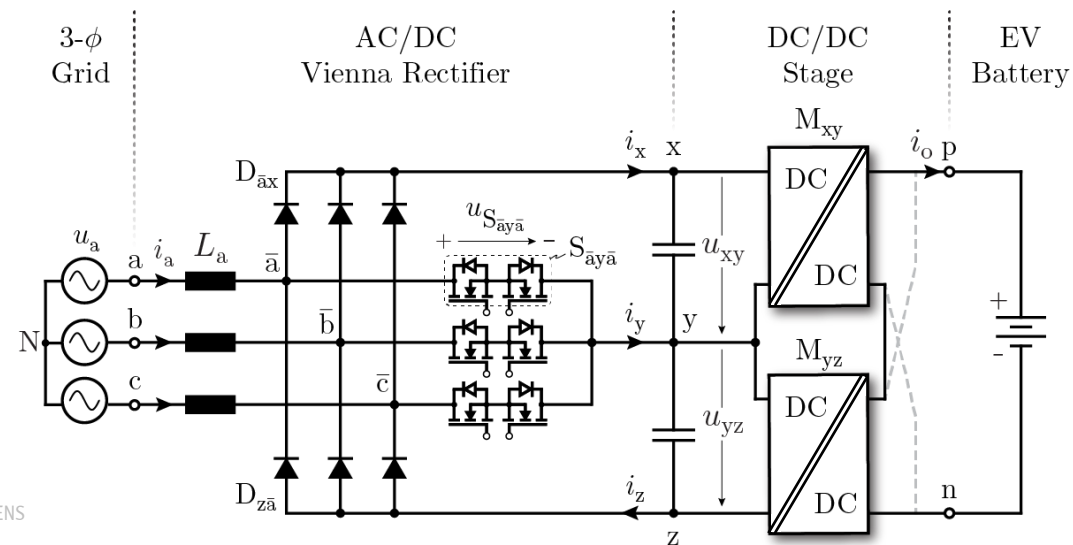


→ Conventional / Independent OR "Synergetic Control" of Input & Output Stage

Conventional Control

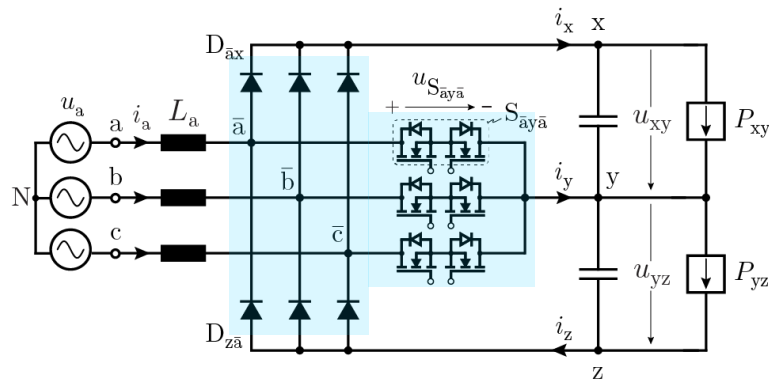- *Decoupled Control of AC/DC & DC/DC-Stage*
- *Constant DC-Link Voltage (Equally Splitted)*
- *Cont. Sw. of All 3 Phases → 3/3 PWM*





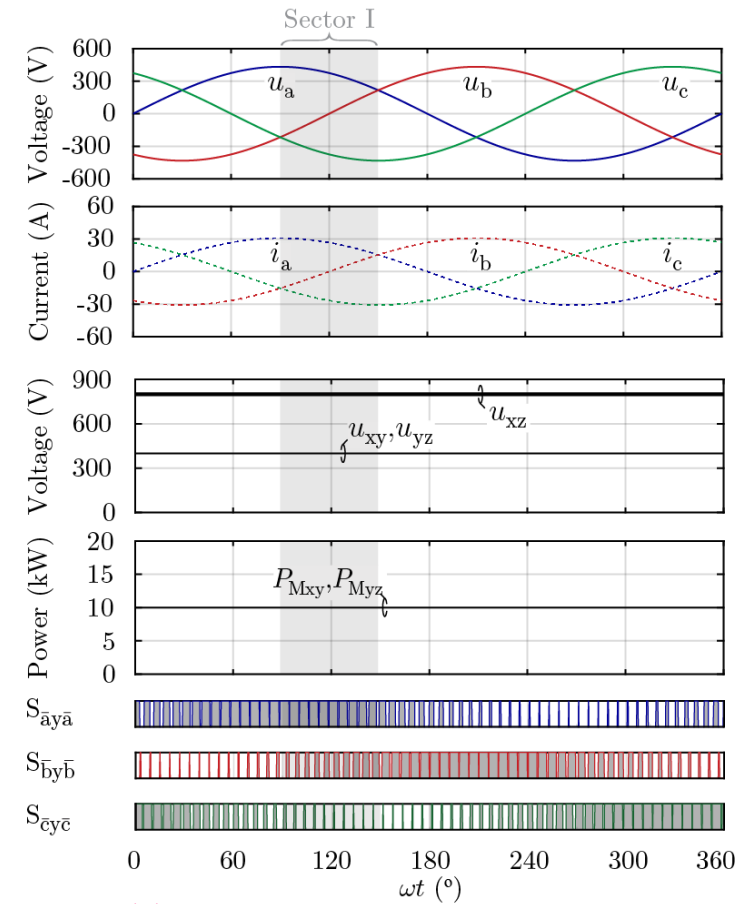→ *Control Capability & Control DOFs NOT Fully Utilized (!)*



"Synergetic" Control

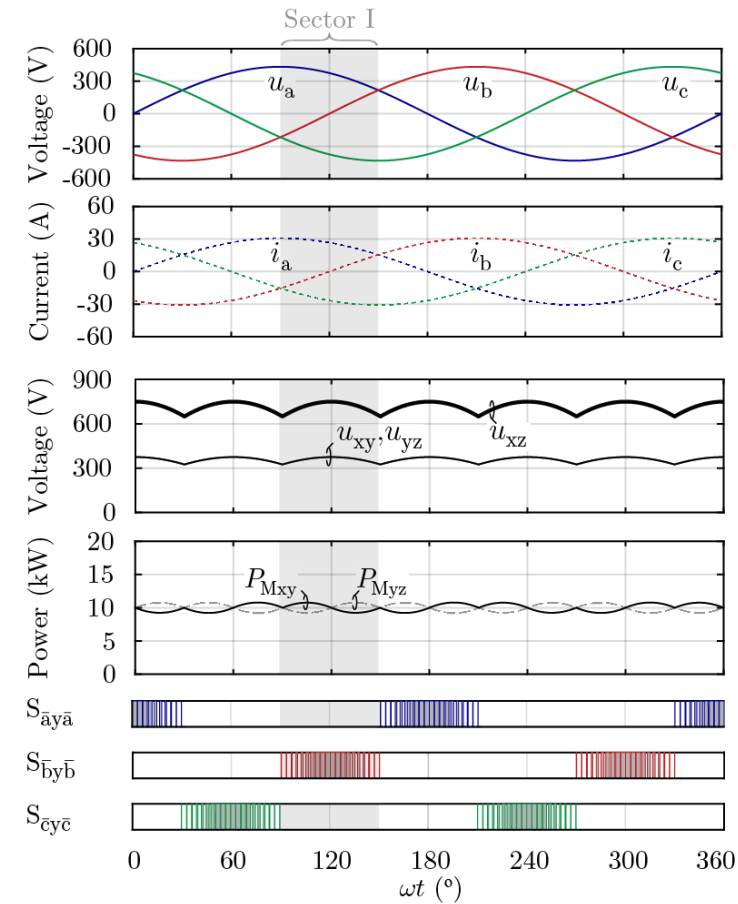
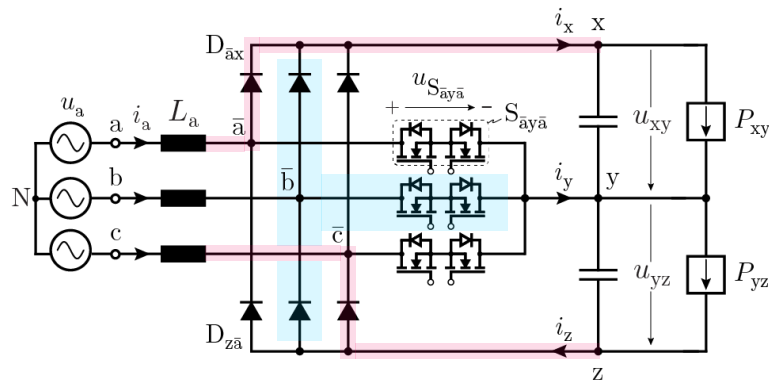
- Only Phase with Lowest Current Switched
- Control of 2 Phase Currents by DC/DC-Stage
- Low Stresses on Power Switches
- 600V GaN HEMTs Can be Used (!)



→ Boost Capability Maintained (Transition from 1/3 to 3/3-PWM)


Conventional vs. "Synergetic" Control

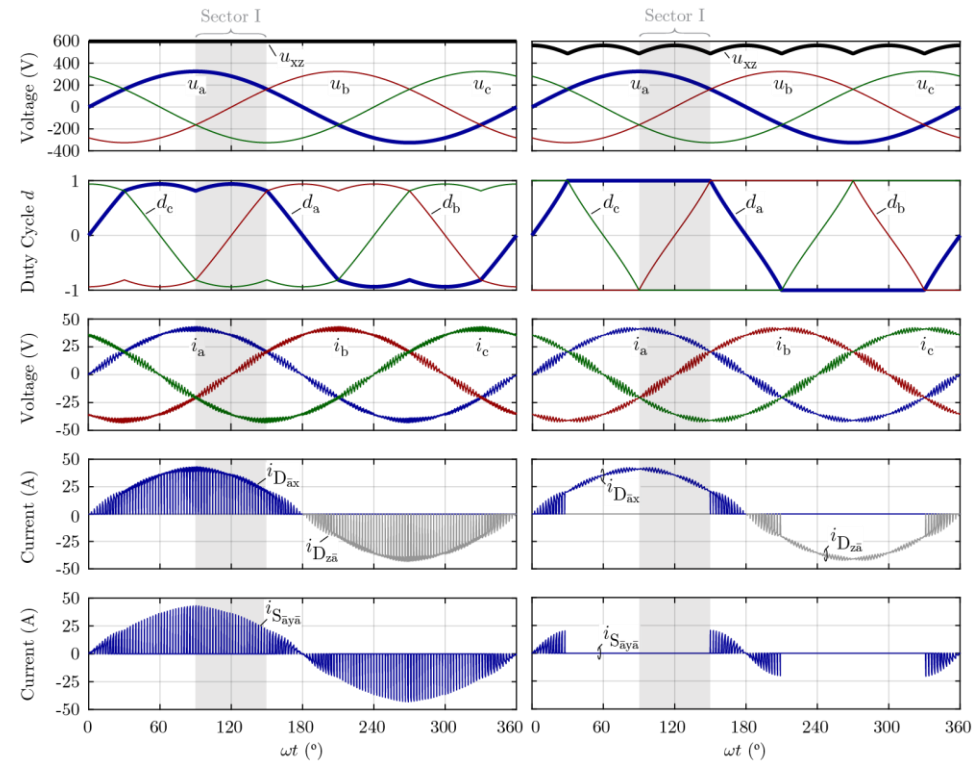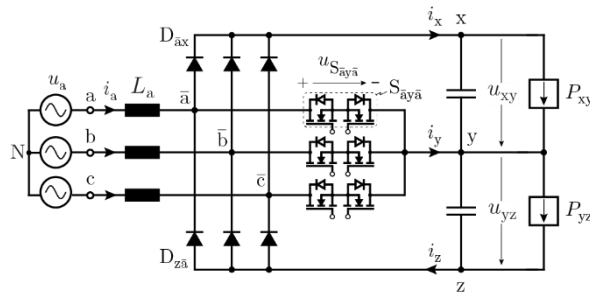- **1/3-Modulation** → **Significant Red. of Losses of the Power Switches Comp. to 3/3-PWM**
- **Conduction Losses** ≈ -80%
- **Switching Losses** ≈ -70%



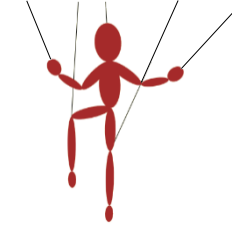→ **Operating Point Dependent Selection of 1/3-PWM OR 3/3-PWM for Min. Overall Losses**






————— ***“Synergetic” Cascaded
Control Structure*** —————

“Synergetic” Control Structure

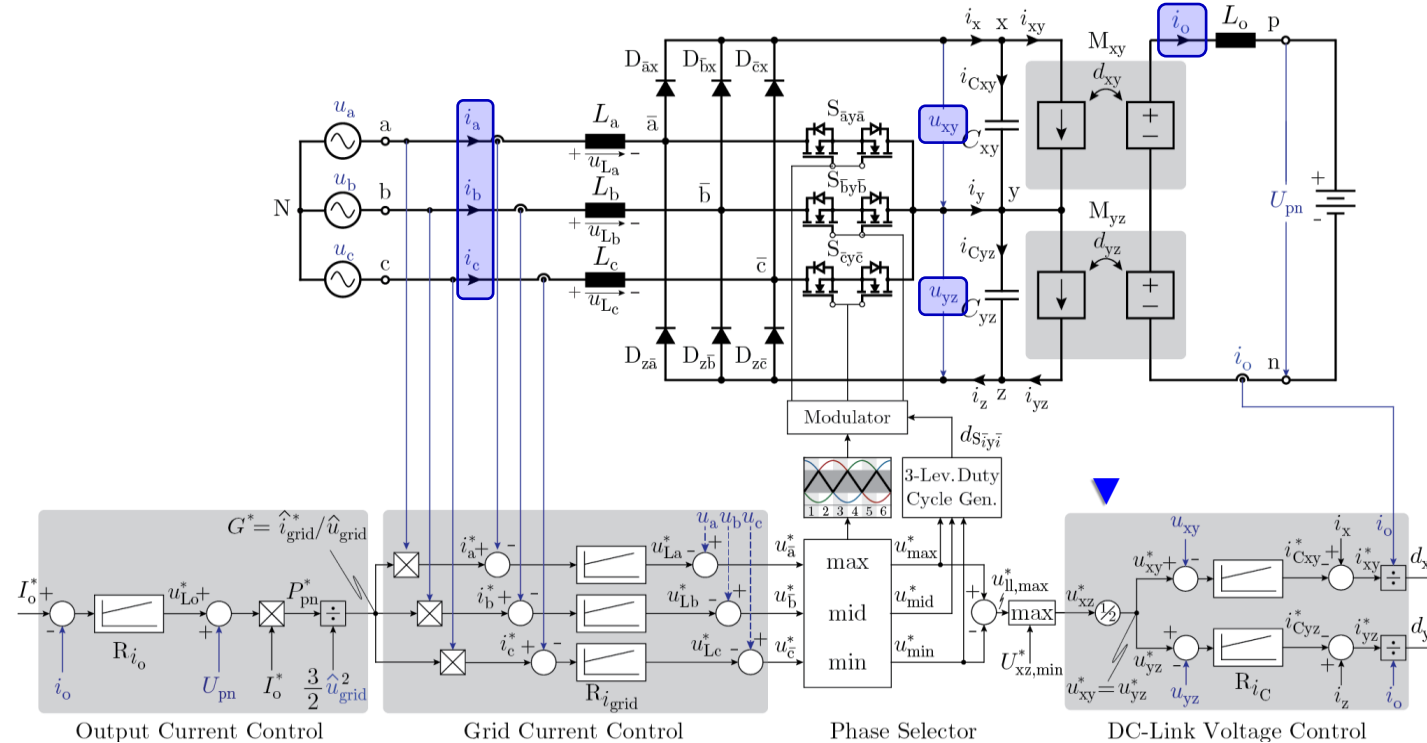- **Cascaded Control of Output & Input Current (Direct & Through DC-Link Voltage)**
- **Active Equal DC-Link Voltage Splitting**



→ Same Control Structure for 3/3-PWM (Full-Boost Mode) Using Diff. Ref. Values



AC/DC-Stage Transition to Full-Boost Operation

■ Different Operating Regimes →

Synergetic

Partial-Boost

Full-Boost

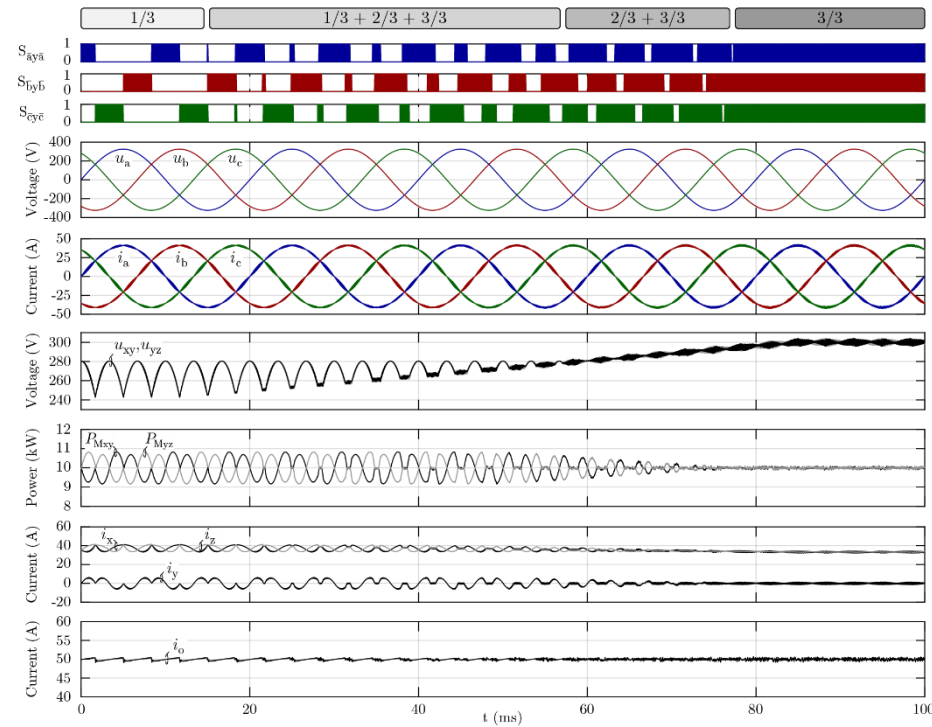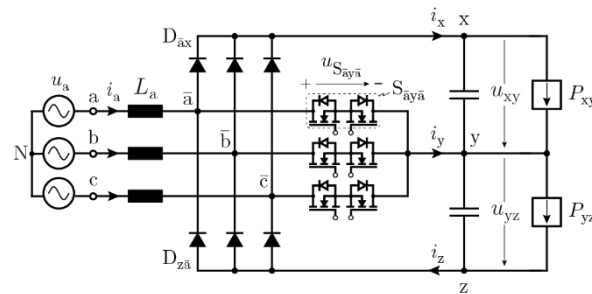



→ **Intermediate 2/3-Operation** for Limiting DC-Link Center Point Current (Low DC-Cap.)

Isolated Single-Stage PFC Rectifiers


————— *Matrix-Type PFC Rectifier* —————
Vienna - Rectifier II, III

Isolated Matrix-Type PFC Rectifier (1)

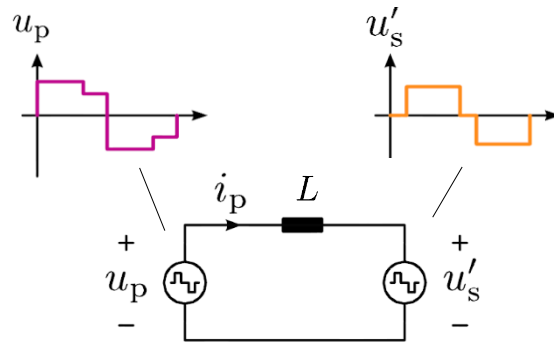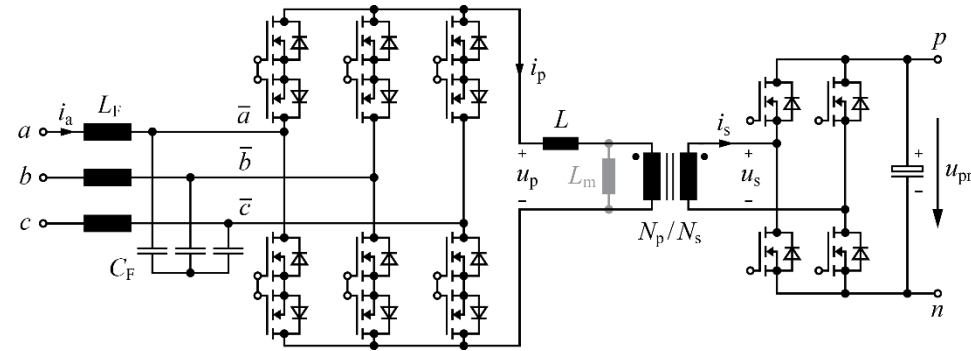- Based on Dual Active Bridge (DAB) Concept
- Optimal Modulation ($t_1 \dots t_4$) for Min. Transformer RMS Curr. & ZVS or ZCS
- Allows Buck-Boost Operation



- Equivalent Circuit

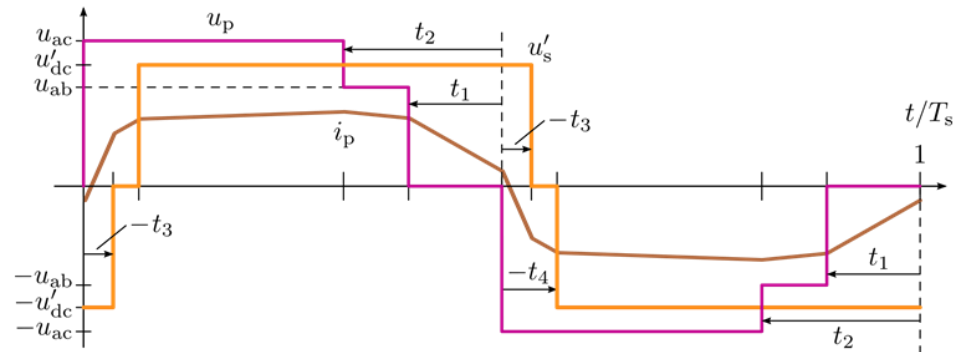

- Transformer Voltages / Currents


Isolated Matrix-Type PFC Rectifier (2)

- Efficiency $\eta = 98.9\%$ @ 60% Rated Load (ZVS)
- Mains Current $THD_I \approx 4\%$ @ Rated Load
- Power Density $\rho \approx 65\text{W}/\text{in}^3$



$$P_o = 8\text{ kW}$$

$$U_N = 400\text{V}_{\text{AC}} \rightarrow U_o = 400\text{V}_{\text{DC}}$$

$$f_s = 36\text{kHz}$$


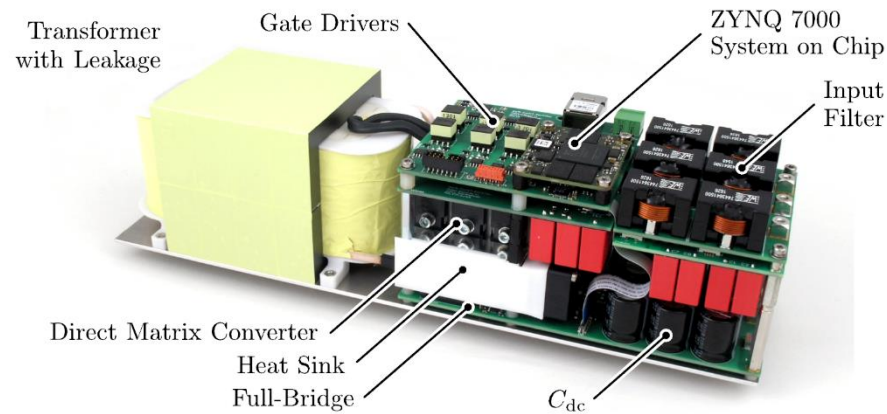


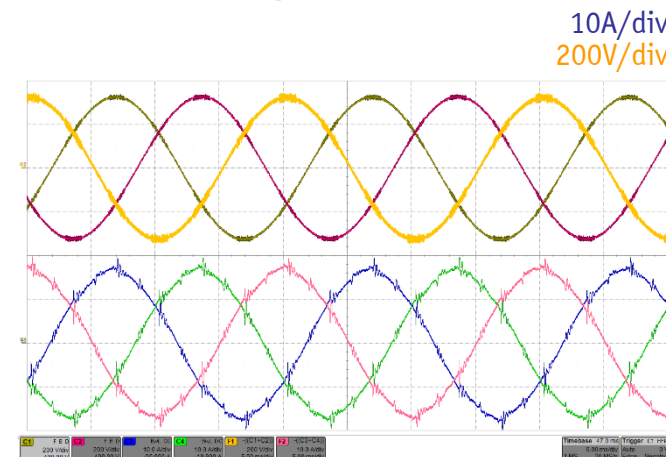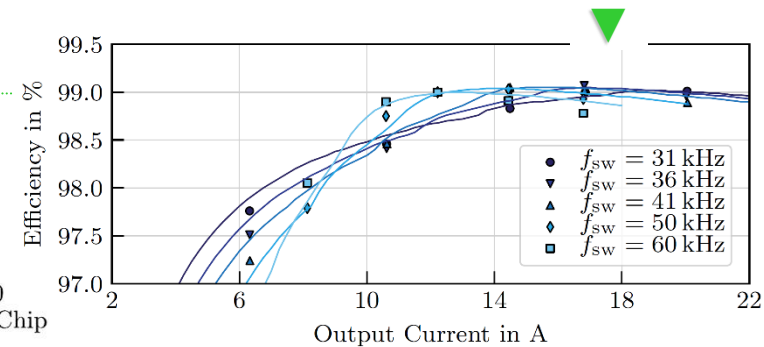- 900V / 10m Ω SiC Power MOSFETs
- Opt. Modulation Based on 3D Look-Up Table



Remark Application of M-BDS

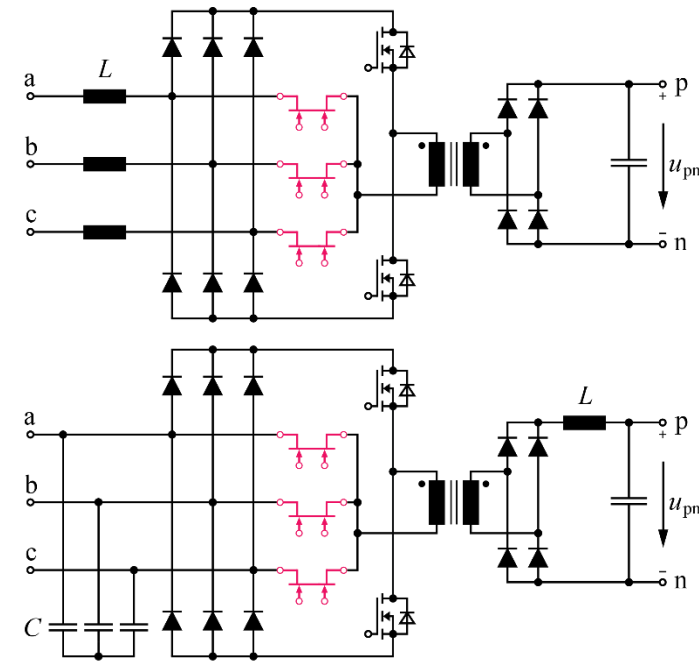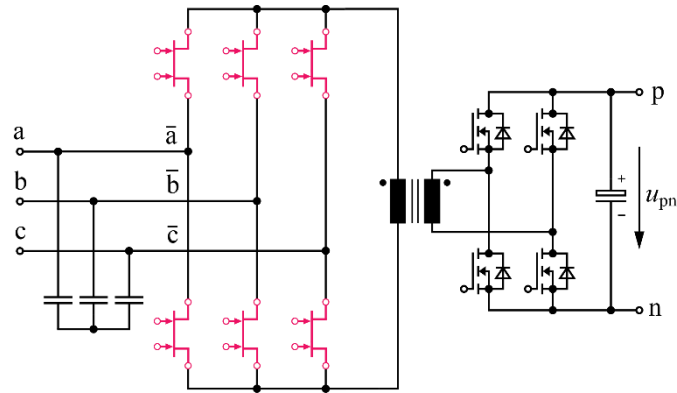- Matrix-Type Bidirectional DAB-Based Topology
- *Unidir. Vienna Rectifier II (Boost-Type)*
- *Unidir. Vienna Rectifier III (Buck-Type)*



- Integration → Lower Complexity *BUT* Limited Controllability

Part II

3- Φ Variable Speed Drive Inverter Systems


Full-Sinewave Filtering
Multi-Level Inverter Concepts
Buck-Boost Inverter
Current DC-Link Inverter



Variable Speed Drive (VSD) Systems

- Industry Automation / Robotics
- Material Machining / Processing – Drilling, Milling, etc.
- Compressors / Pumps / Fans
- Transportation
- etc., etc.

.... Everywhere !


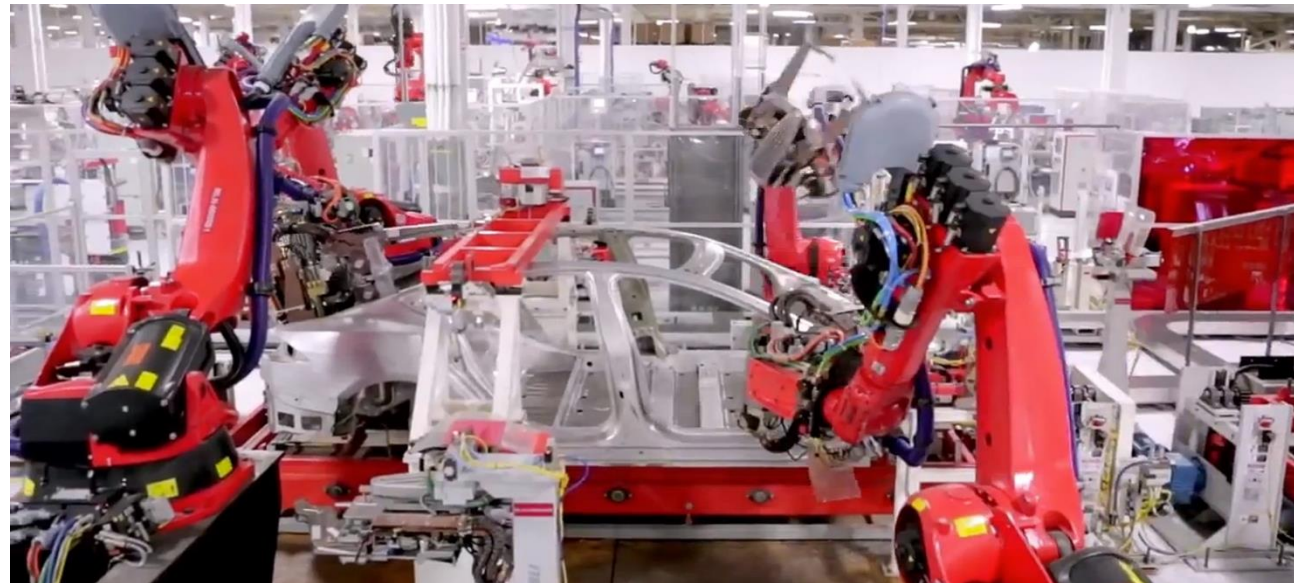


Source:  TESLA MOTORS

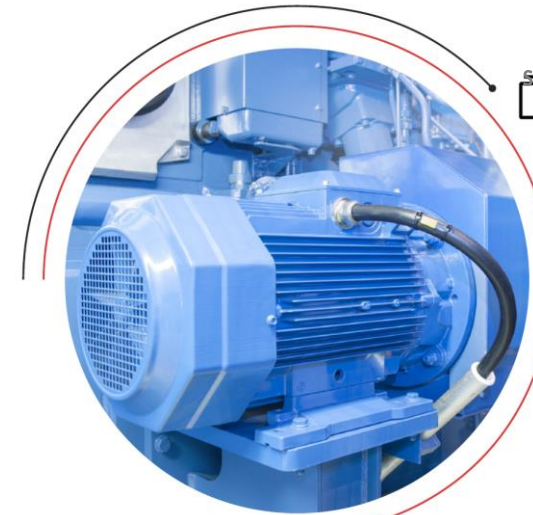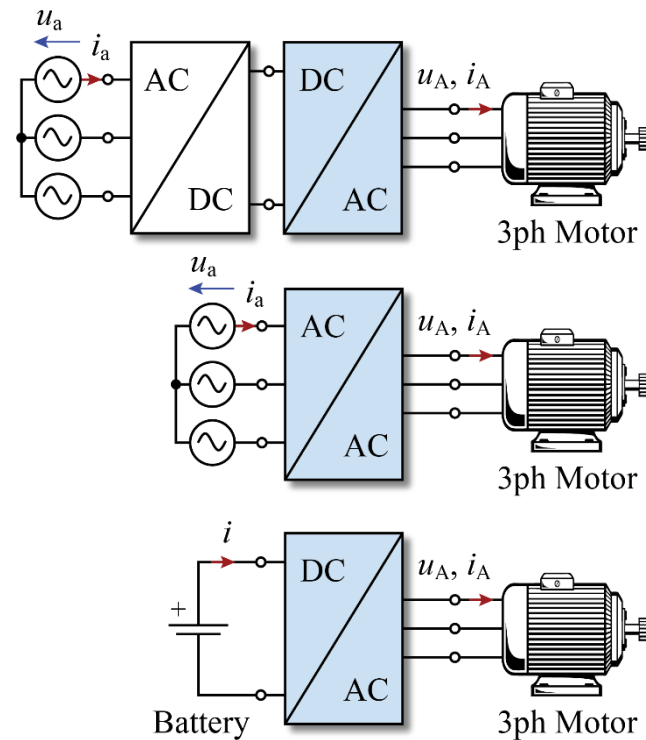- *60...70 % of All Electric Energy Used in Industry Consumed by El. Motors*

Variable Speed Drive Inverter Concepts

- *DC-Link Based OR Matrix-Type AC/AC Converters*
- *Battery OR Fuel-Cell Supply OR Common DC-Bus Concepts*



38%

of electric energy use is for motors in commercial buildings.



70%


of electricity consumed by industry is used in electric motor systems.

Source: **ABB**


- *45% of World's Electricity Used to Power Motors in Buildings & Industrial Applications*

State-of-the-Art Drive System

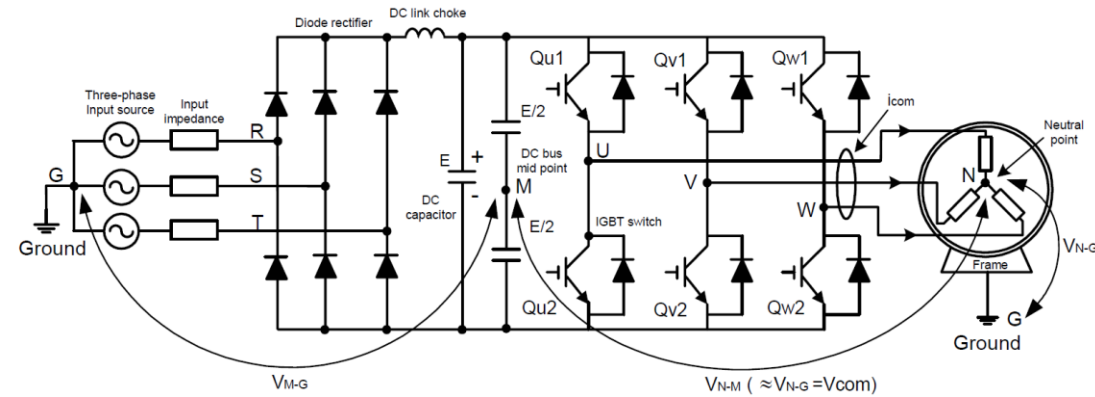
- **Standard 2-Level Inverter** — Large Motor Inductance / Low Sw. Frequency
- **Shielded Motor Cables** / Limited Cable Length / Insulated Bearings / Acoustic Noise




Source: YASKAWA

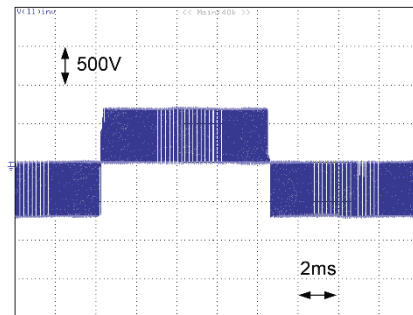


• Line-to-Line Voltage

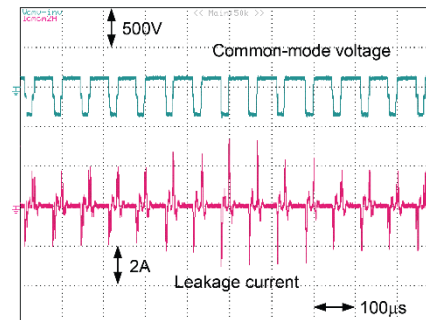

| CM Leakage Current

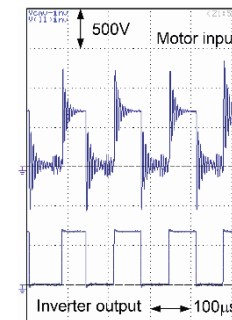



| Motor Surge Voltage

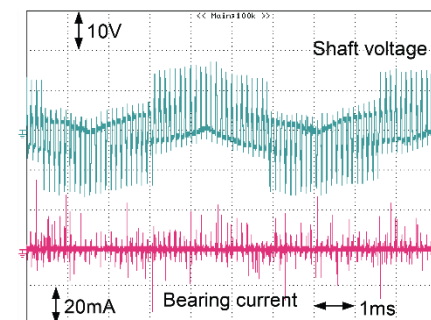

| Bearing Current

Surge Voltage Reflections

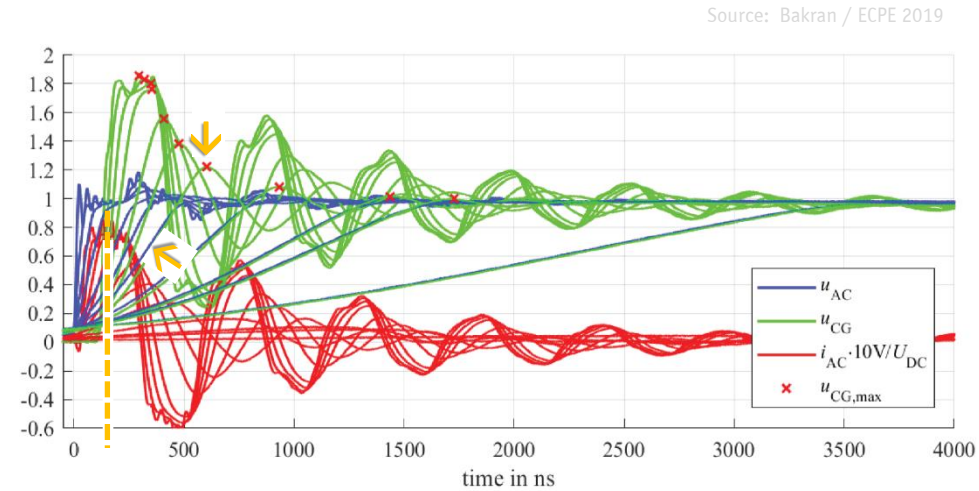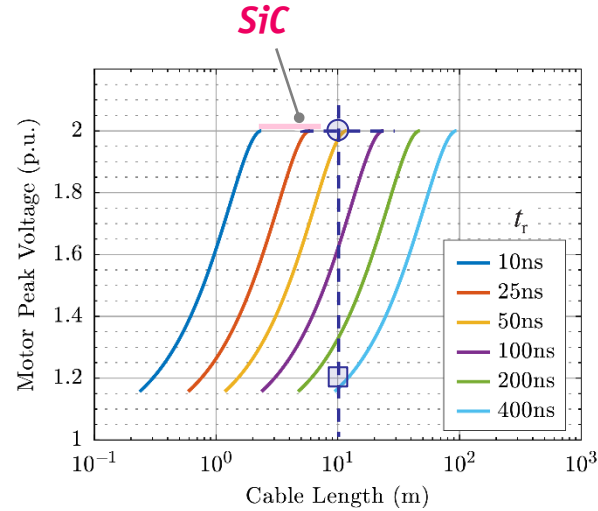
- Long Motor Cable $l_c \geq \frac{1}{2} t_r v$
- Short Rise Time of Inverter Output Voltage
- Impedance Mismatch of Cable & Motor → Reflect. @ Motor Terminals / High Insul. Stress



→ dv/dt - OR Full-Sinewave Filtering / Termination & Matching Networks etc.

Motor Bearing Currents


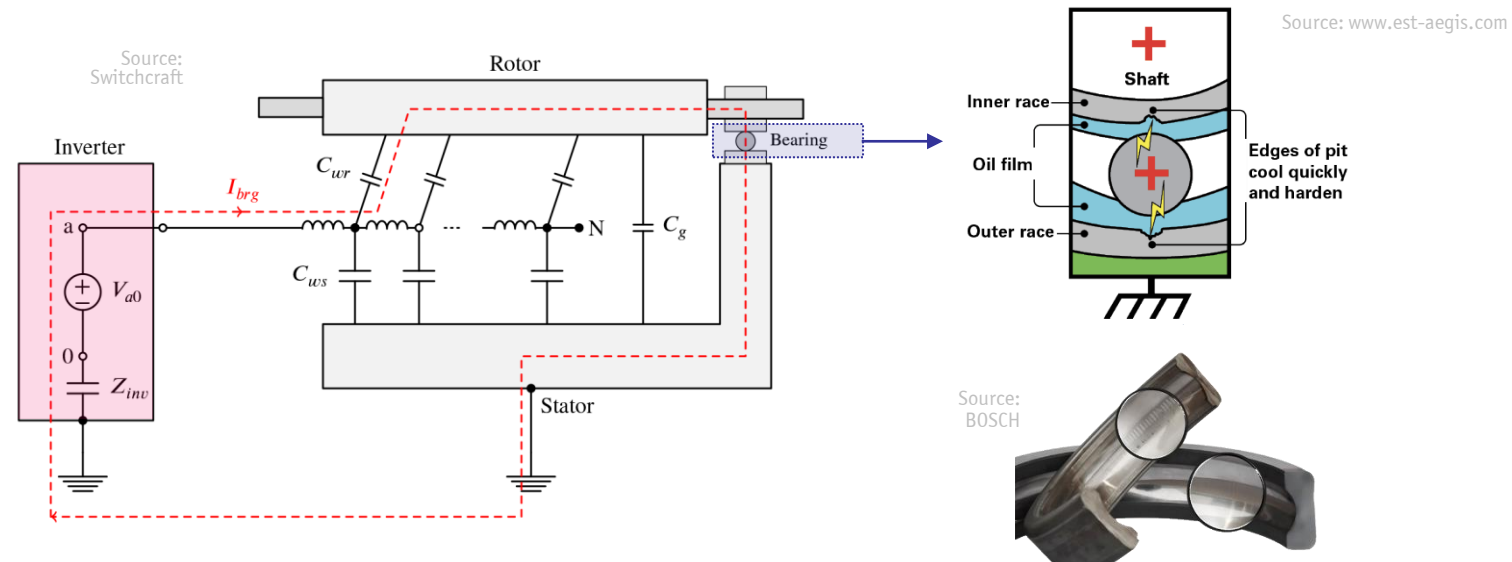
- *Switching Frequency CM Inverter Output Voltage \rightarrow Motor Shaft Voltage*
- *Electrical Discharge in the Bearing ("EDM")*



\rightarrow *Cond. Grease / Ceram. Bearings / Shaft Grndg Brushes / dv/dt - OR Full-Sinewave Filters*

VSD Inverter - Future Requirements

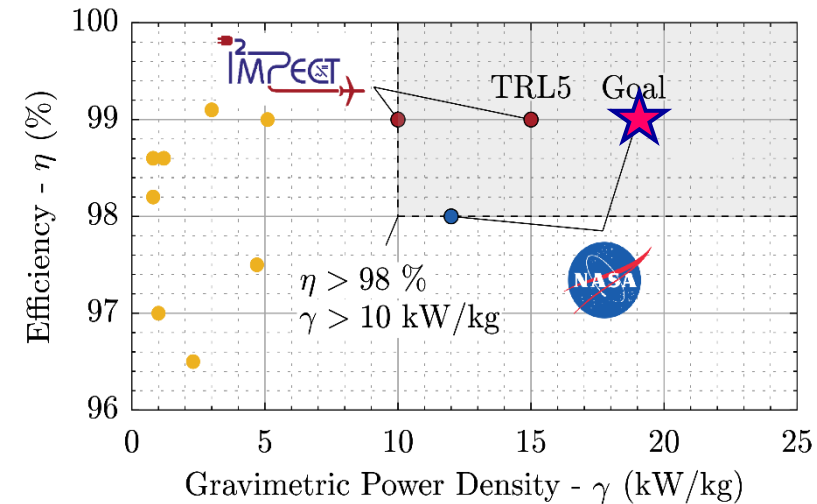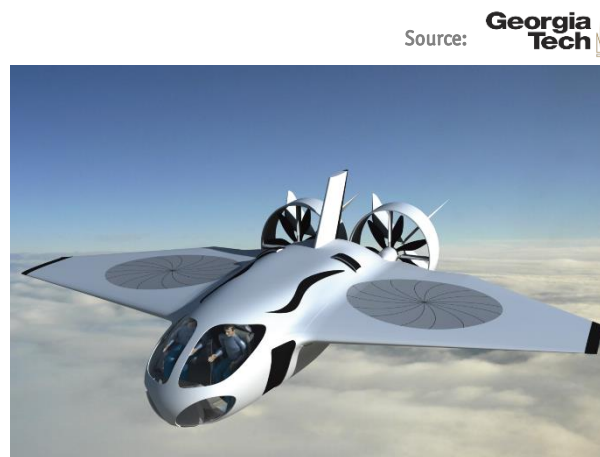- *“Sinus-Inverter” / “Non-Expert” Installation — Motor-Integrated Inverter*
- *Low Losses & Low HF Motor Losses*
- *Low Volume & Weight*
- *Wide Output Voltage Range*
- *High Output Frequencies (High-Speed Motors)*






- *Main “Enablers” → SiC/GaN Power Semiconductors & Adv. Inverter Topologies*

—— *SiC vs. Si* ——

Si vs. SiC

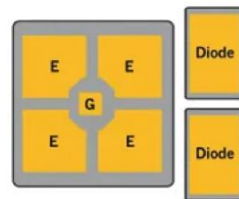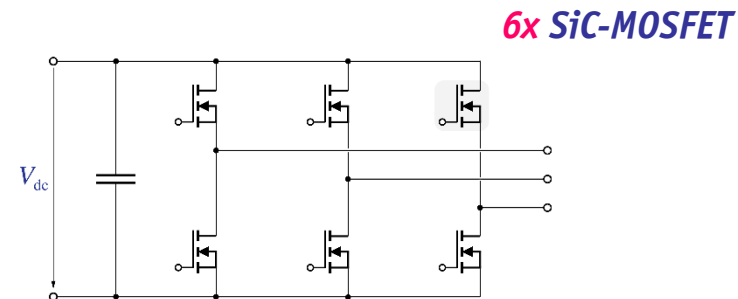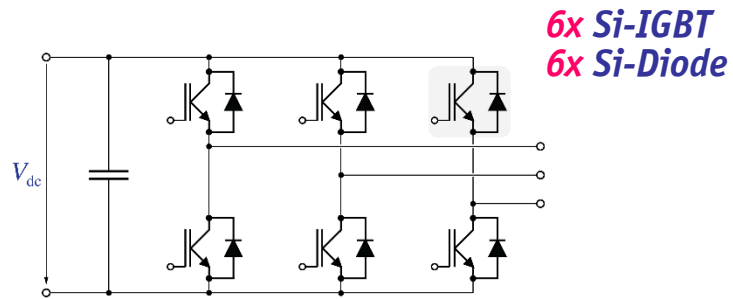
- **Si-IGBT / Diode** → Const. On-State Voltage, Turn-Off Tail Current & Diode Reverse Recovery Current
- **SiC-MOSFET** → Loss Reduction @ Part Load BUT Higher R_{th}



Source:
ATZ elektronik

1200V 100A
Die Size: $98.8\text{mm}^2 + 39.4\text{mm}^2$

Source: Infineon

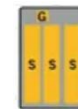

1200V 100A
Die Size: 25.6mm^2

Source: Cree

- Space Saving of **>30%** on Module Level (!)

Low $R_{DS(on)}$ High-Voltage Devices

- **Higher Critical E-Field of SiC → Thinner Drift Layer**
- **Higher Maximum Junction Temperature $T_{j,max}$**


at 300 K	Si	GaAs	4H/6H-SiC	GaN
E_g (eV)	1.12	1.4	3.0-3.2	3.4
E_c (MV/cm)	0.25	0.3	2.2-2.5	3
μ_n (cm ² /Vs)	1350	8500	100-1000	1000
ϵ_r	11.9	13	10	9.5
V_{sat} (cm/s)	1×10^7	1×10^7	2×10^7	3×10^7
λ (W/cmK)	1.5	0.5	3 - 5	1.3

© 2000 Carl-Mikael Zetterling

$$R_{on}^* = \frac{4V_B^2}{\epsilon\mu_n E_C^3} \leftarrow \text{For 1kV:}$$

	Si	SiC
W (μm)	100	10
N_D (cm ⁻³)	10^{14}	10^{16}

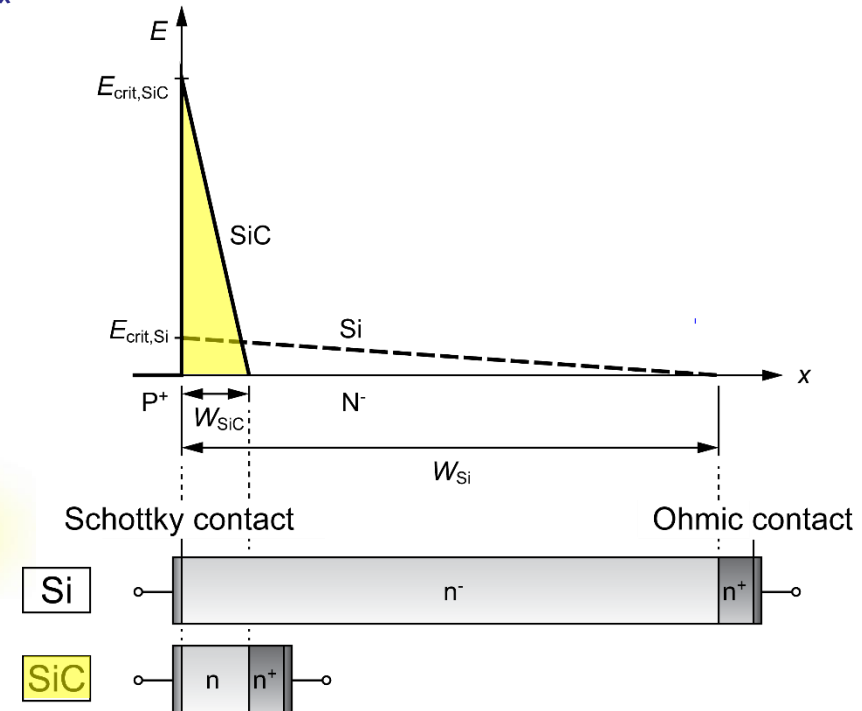
$$R_{on,SiC}^* \approx \frac{1}{300} R_{on,Si}^*$$



- **Massive Reduction of Relative On-Resistance → High Blocking Voltage Unipolar (!) Devices**


Si vs. SiC Conduction Behavior (1)

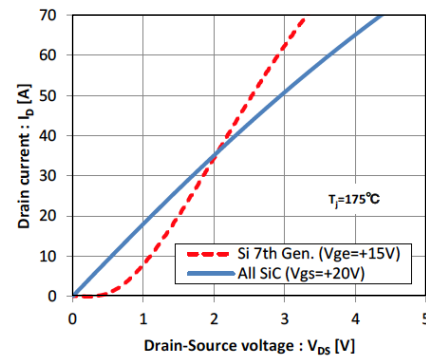- **Si-IGBT** → **Const. On-State Voltage Drop** / **Rel. Low Switching Speed**,
- **SiC-MOSFETs** → **Resistive On-State Behavior** / **Factor 10 Higher Sw. Speed**




Source: Fuji Electric

Forward

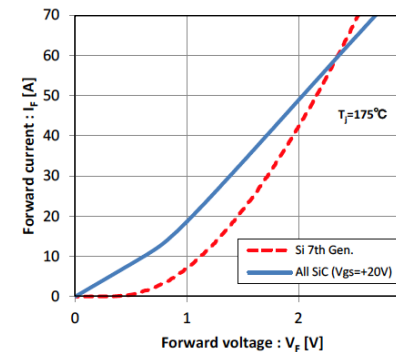


Reverse

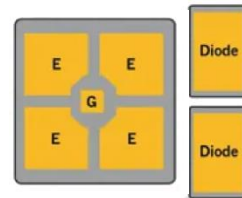

1200V 100A
Die Size: 98.8 mm² + 39.4 mm²

Source: Infineon

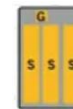



1200V 100A
Die Size: 25.6 mm²

Source: Cree

- **SiC MOSFETs Facilitate Higher Part Load Efficiency**



Si vs. SiC Conduction Behavior (2)

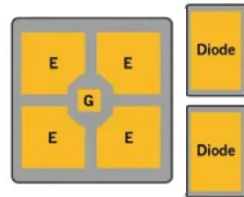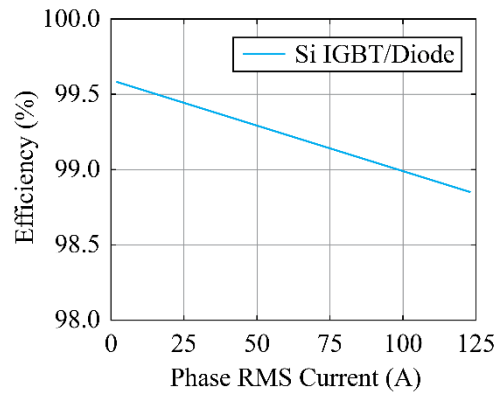- **Si-IGBT** → **Const. On-State Voltage Drop** / **Rel. Low Switching Speed**,
- **SiC-MOSFETs** → **Resistive On-State Behavior** / **Factor 10 Higher Sw. Speed**



1200V 100A
Die Size: 98.8mm² + 39.4mm²

Source: Infineon

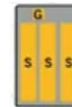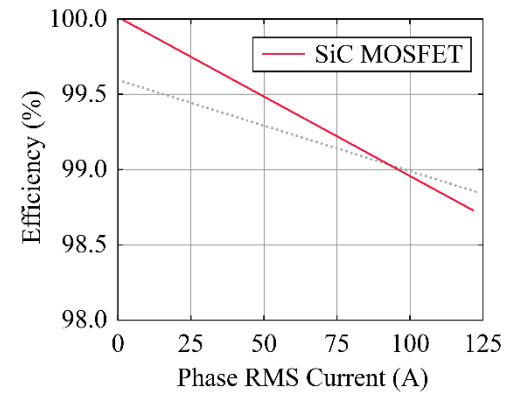


1200V 100A
Die Size: 25.6mm²

Source: Cree


- **Efficiency Characteristic Considering Only Conduction Losses**

Si vs. SiC Switching Behavior

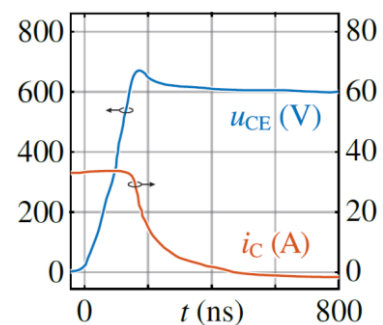- **Si-IGBT** → *Const. On-State Voltage Drop / Rel. Low Switching Speed,*
- **SiC-MOSFETs** → *Resistive On-State Behavior / Factor 10 Higher Sw. Speed*





Source: Fuji Electric

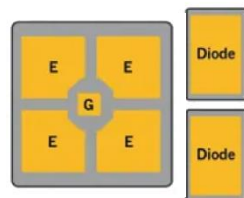

1200V 100A
Die Size: 98.8mm² + 39.4mm²

Source: Infineon

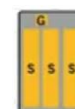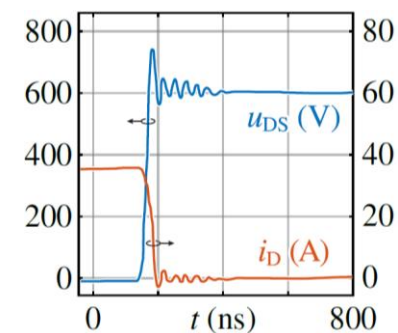


1200V 100A
Die Size: 25.6mm²

Source: Cree

- **High di/dt & dv/dt** → *Challenges in Packaging / EMI / Motor Insulation / Bearing Currents*

Challenges


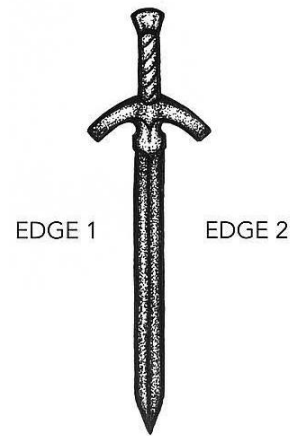


Circuit Parasitics

- *High di/dt*
- *Commutation Loop Inductance L_s*
- *Allowed L_s Directly Related to Switching Time t_s* →

$$L \frac{di}{dt} = u$$
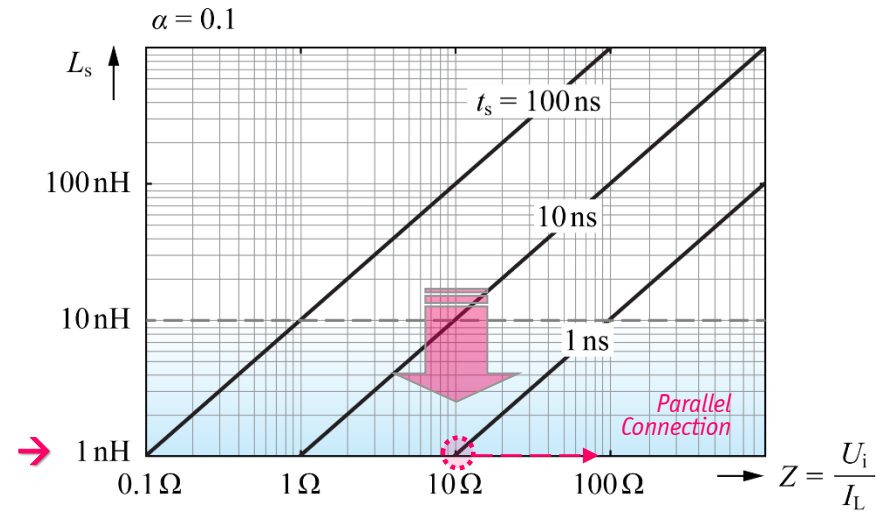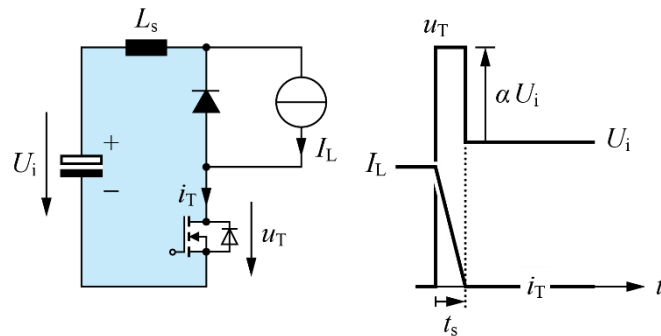
$$L_s \leq \frac{\alpha U_i}{\frac{I_L}{t_s}} = \alpha t_s \frac{U_i}{I_L}$$






- *Advanced Packaging & Parallel Interleaving for Partitioning of Large Currents (Z-Matching)*

Si vs. SiC EMI Emissions

- Higher dv/dt → Factor 10
- Higher Switching Frequencies → Factor 10
- EMI Envelope Shifted to Higher Frequencies

$f_s = 10\text{kHz}$ & 5 kV/us for (Si IGBT)
 $f_s = 100\text{kHz}$ & 50 kV/us for (SiC MOSFET)

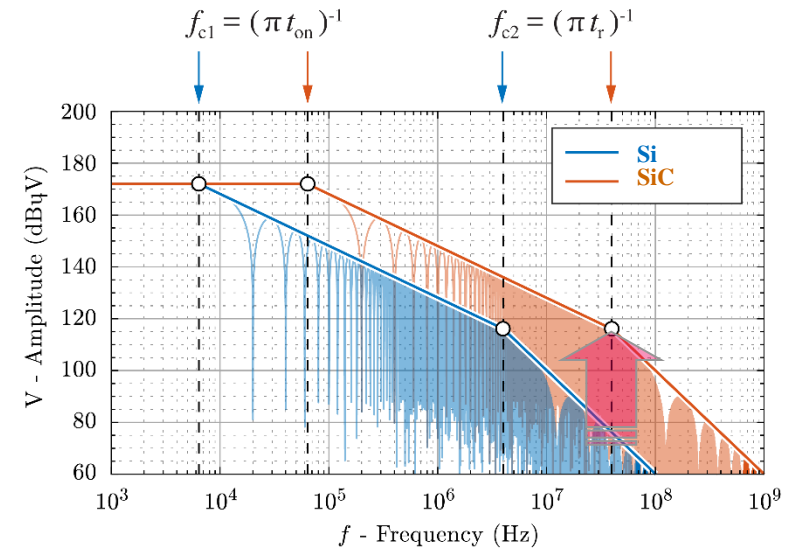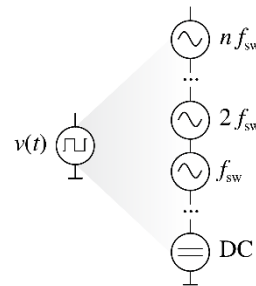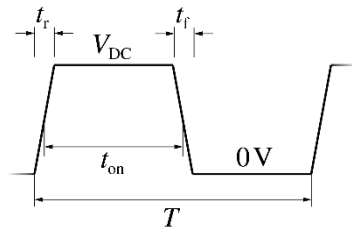$V_{DC} = 800\text{V}$
 DC/DC @ $D = 50\%$



- Higher Influence of Filter Component Parasitics & Couplings → Advanced Design

Inverter Output Filters



dv/dt-Filters
Full-Sinewave Filters



———— ***dv/dt-Control*** ————

Passive | Hybrid | Active dv/dt -Limitation

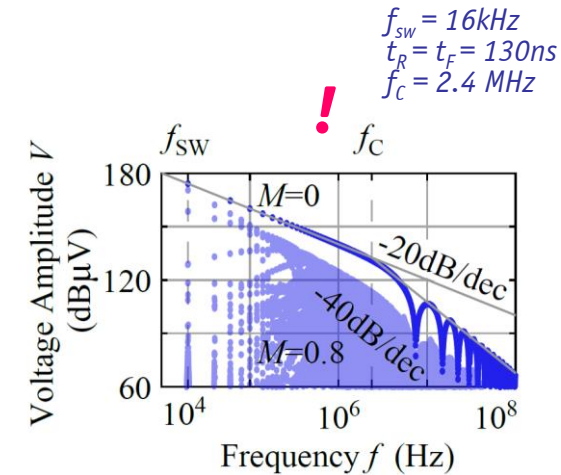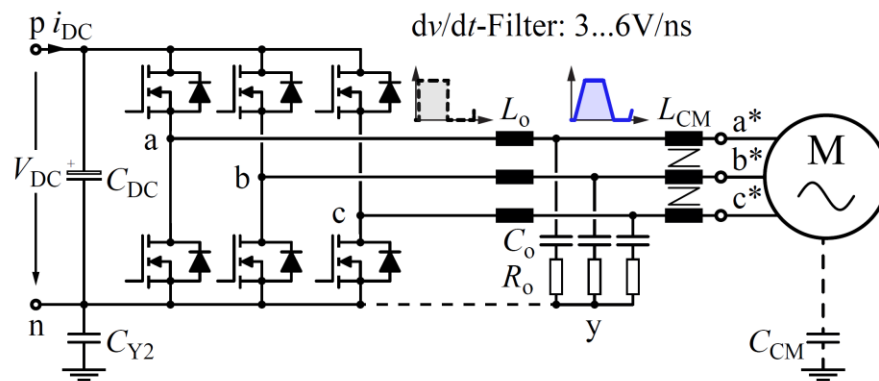- **Passive** – Damped LC-Filter $f_c > f_s$
- **Hybrid** – Undamped LC-Filter & Multi-Step Sw. Transition
- **Active** – Gate-Drive Based Shaping of Sw. Transients




- **Connection to DC-Minus & CM Inductor** → Limit CM Curr. Spikes / EMI / Bearing Currents

Comparison of dv/dt-Filtering Techniques (1)


Passive Concept

1. LCR-Filter
2. Clamped LC-Filter

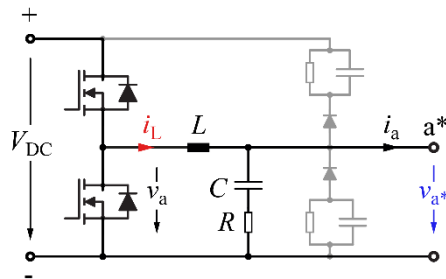


Hybrid Concept ($3f_{sw}$)

1. LC-Filter
2. Multi-Step Switching

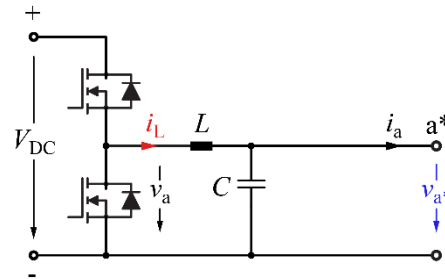


Active Concept

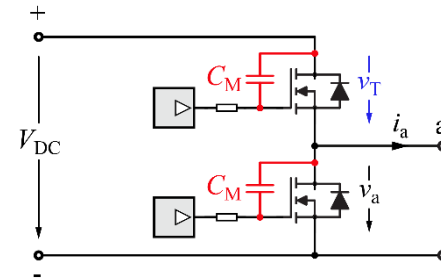
1. Miller Capacitor
2. Gate Current Control



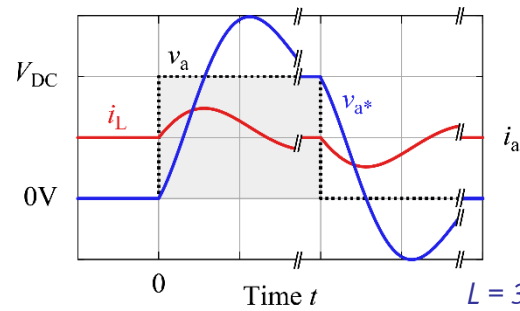
Output Voltage Waveforms — $V_{DC} = 800V$, $P_{out} = 10kW$, $6kV/us$



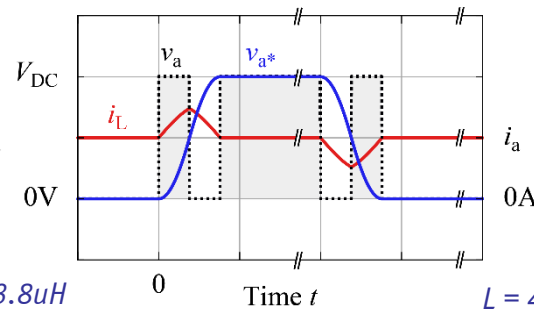$L = 3.8\mu H$
 $C = 2.7nF$
 $R = 19\Omega$





$L = 4.1\mu H$
 $C = 1.3nF$

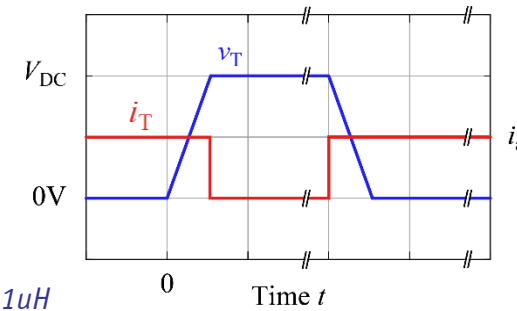

$1200V SiC / 16m\Omega$
 $C_M = 120pF$

Comparison of dv/dt-Filtering Techniques (2)

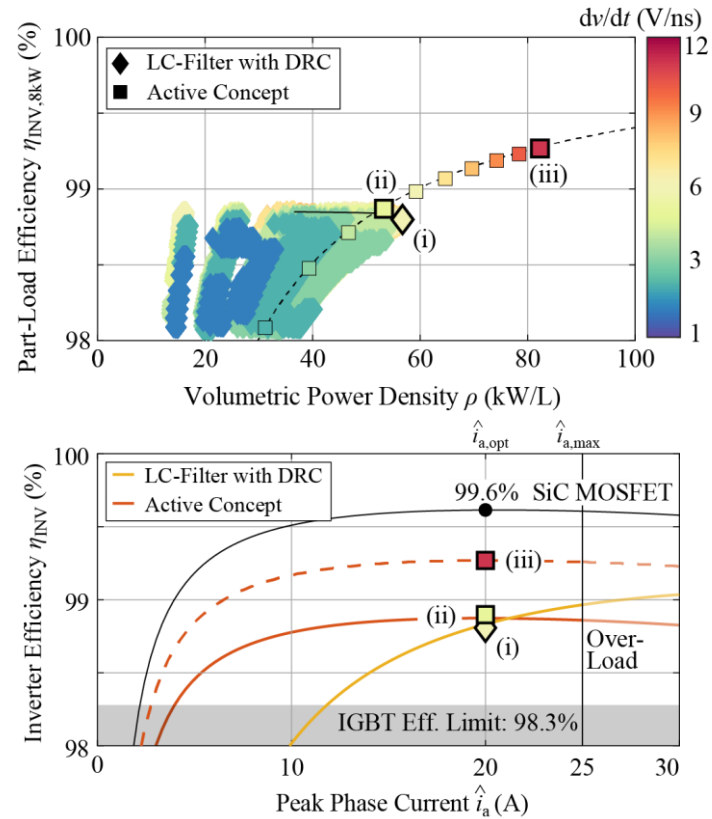
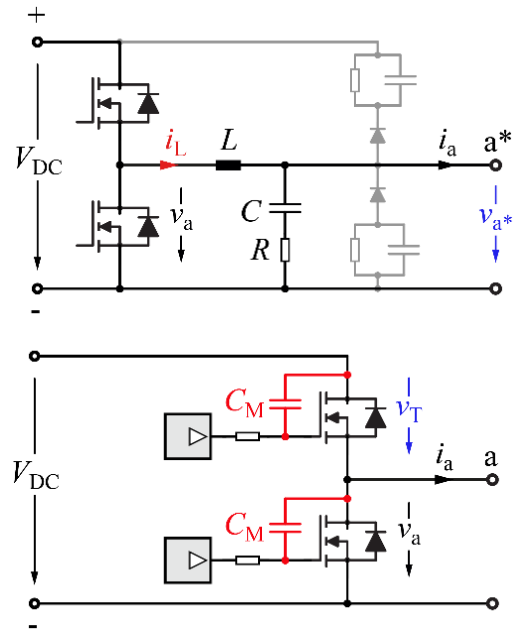
- Comparative Evaluation of Passive & Active Concept**



■ **Losses / Power Density** – $V_{DC} = 800V$, $P_{out} = 10kW$, $f_{sw} = 16kHz$, 1200V SiC-MOSFETs (16m Ω)



Multi-Bridge-Leg dv/dt-Control

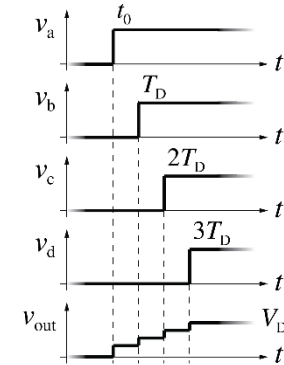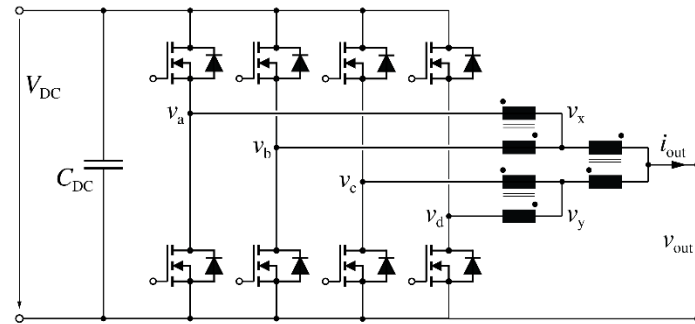■ Staggered Sw. Parallel Bridge-Legs → Non-Resonant Multi-Step Transition



Source: J. Ertl et al.
PCIM Europe 2017

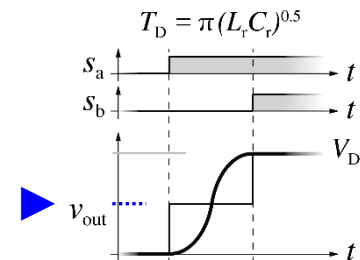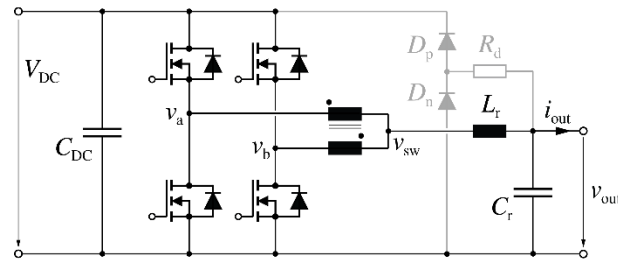■ 2-Step Switching / Resonant Transition (cf. Active dv/dt-Filter)





Source: J. Ertl et al.
PCIM Europe 2018

● Adv. for High Power / Output Curr. Syst. Employing Parallel Bridge-Legs & Local Comm. Cap.

Remark Aux. Resonant Commutated Pole

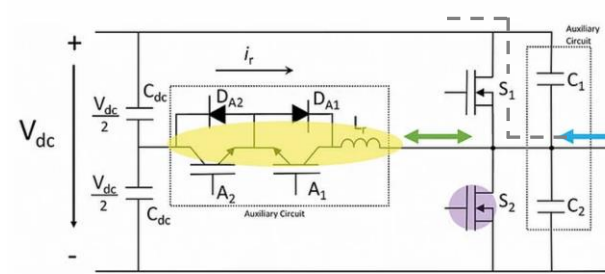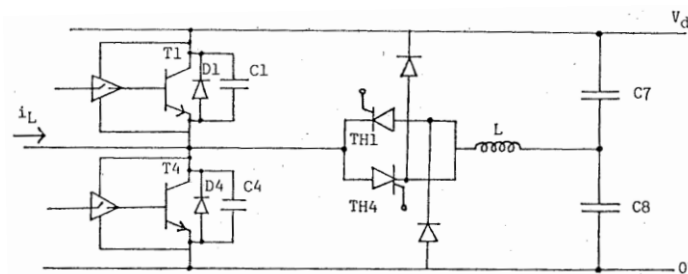- dv/dt -Limitation w/ Snubber Cap. & Aux. Switches $\rightarrow 1 \dots 1.5 \text{ kV}/\mu\text{s}$
- Opt. Timing of Aux. & Main Switches \rightarrow Pre-Flex™ Self-Learning AI Algorithm of
- Concept Proposed by M. Lockwood & A. Fox @ IPEC 1983





Green: L_r Resonant inductor current (varies with load)

Purple: S2 V_{ds} switch voltage (600V-0V)

Yellow: Aux + L_r ARCP and inductor voltage (-300V to +300V)

Blue: Load current varies 0-160A

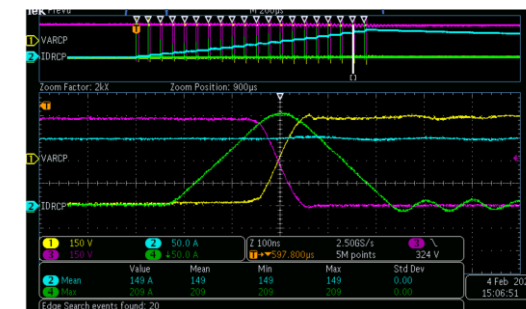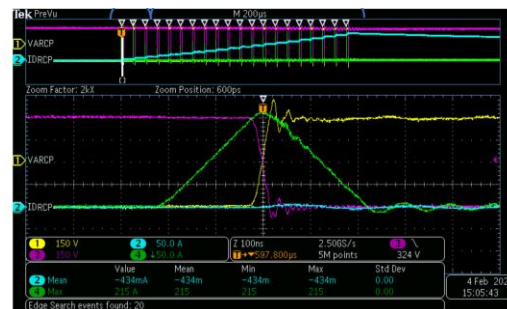


■ 99.5% Half-Load | 99.35% Full-Load (100kW/800V_{dc}) Eff. @ 50kHz (1200V/12mΩ SiC MOSFETs)

*Inverter Systems w/
Sinusoidal Output Voltages*

Output Voltage Filtering

- Measures Ensuring EMI Compliance / Longevity of Motor Insulation & Bearings
- Motor Reactor | DM-Sinus Filters | Full-Sinus (DM&CM) Filters | Multi-Level Inverters

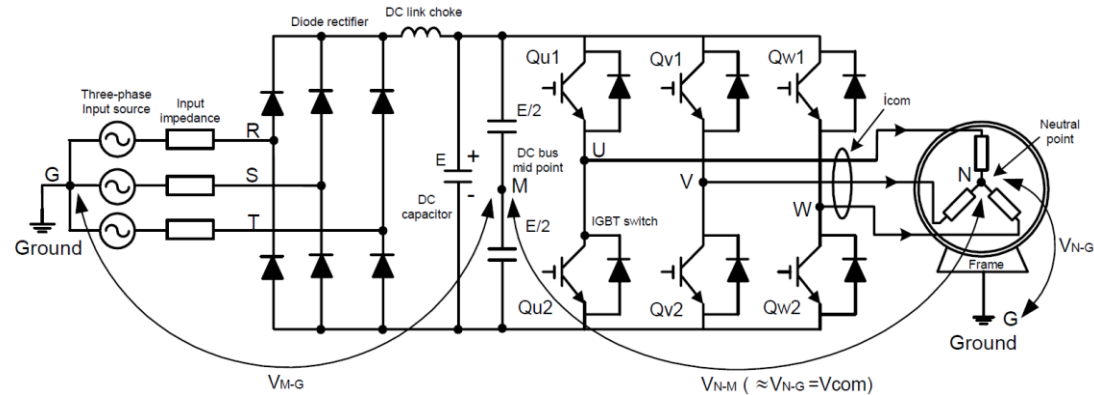

Source: YASKAWA

Source: BLOCK

MOTOR VOLTAGE PHASE-PHASE


No filter



Voltage (V)1 time (ms)→


MOTOR VOLTAGE PHASE-GROUND

No filter

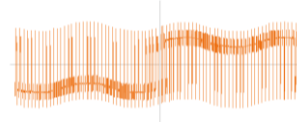


Voltage (V)1 time (ms)→

With filter

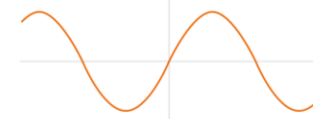


Voltage (V)1 time (ms)→

With filter

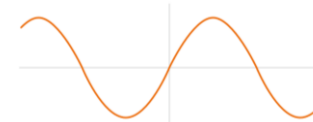


Voltage (V)1 time (ms)→

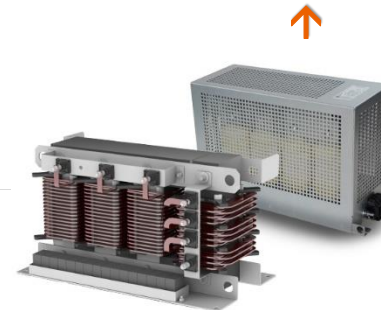

- Small Filter Size →
High Sw. Freq. → SiC | GaN

———— *Inverter DM & CM Output
Voltage Components* ————

Equivalent Circuit (1)

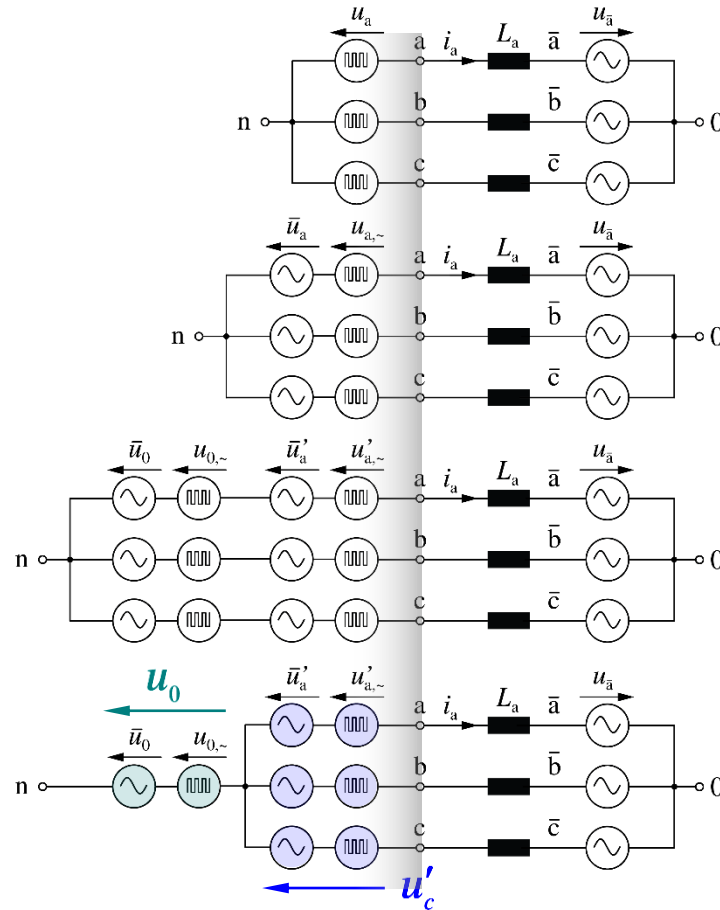

$$\begin{aligned} u_a &= \bar{u}_a + u_{a\sim} \\ u_b &= \bar{u}_b + u_{b\sim} \\ u_c &= \bar{u}_c + u_{c\sim} \end{aligned}$$



$$\begin{aligned} u_a &= u'_a + u_0 \\ u_b &= u'_b + u_0 \\ u_c &= u'_c + u_0 \end{aligned} \quad u'_a + u'_b + u'_c = 0$$

$$u_0 = \frac{1}{3}(u_a + u_b + u_c)$$

$$\begin{aligned} u_a &= \bar{u}_a + u_{a\sim} \\ u_0 &= \bar{u}_0 + u_{0\sim} \end{aligned}$$

- Active DM Voltage Component u'_c
- Inactive CM Zero Sequence Voltage u_0
- Low-Frequ. & Sw.-Frequ. Components

Equivalent Circuit (2)

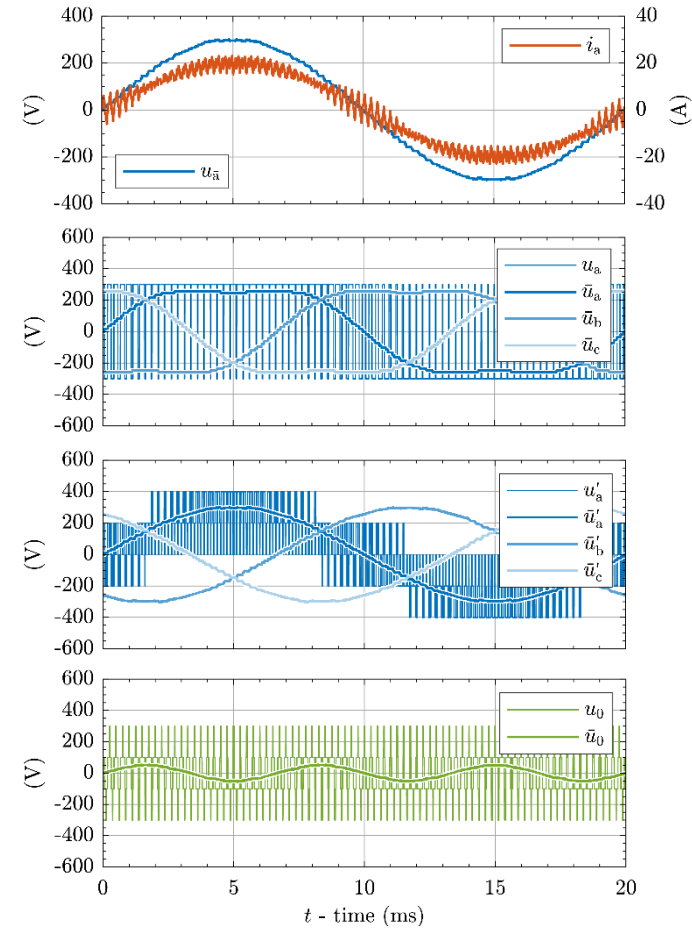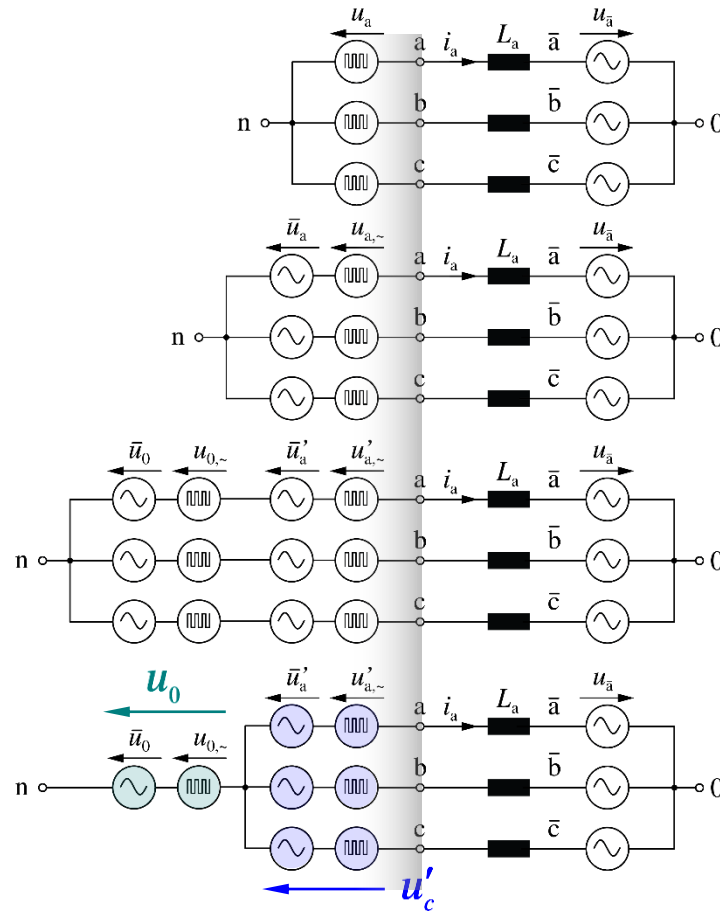

Equivalent Circuit (3)

- Active Sw.-Frequ. DM Voltage
- Inactive Sw.-Frequ. CM Voltage



$$u_0 = u_{0n} \rightarrow u_{\bar{n}0} \equiv 0$$

$$u_0 + u'_a = L \frac{di_a}{dt} + u_a + u_{0n}$$

$$u_0 + u'_b = L \frac{di_b}{dt} + u_b + u_{0n}$$


$$u_0 + u'_c = L \frac{di_c}{dt} + u_c + u_{0n}$$

$$3u_0 + 0 = 0 + 0 + 3u_{0n}$$


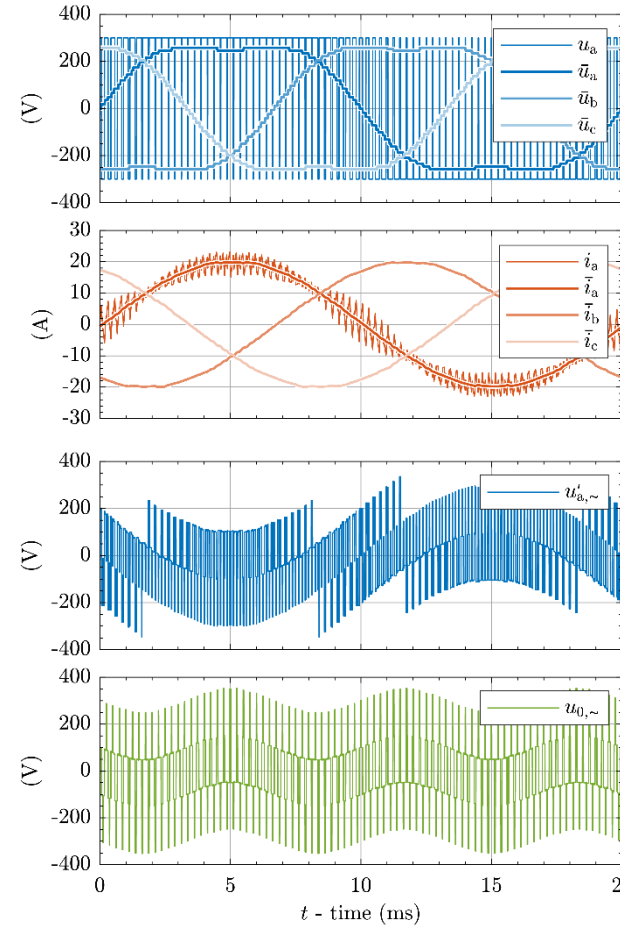
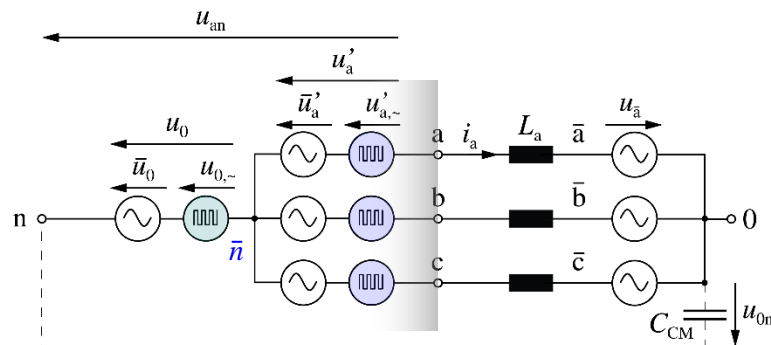


Differential- / Common-Mode Filtering

DM & CM Equivalent Circuit

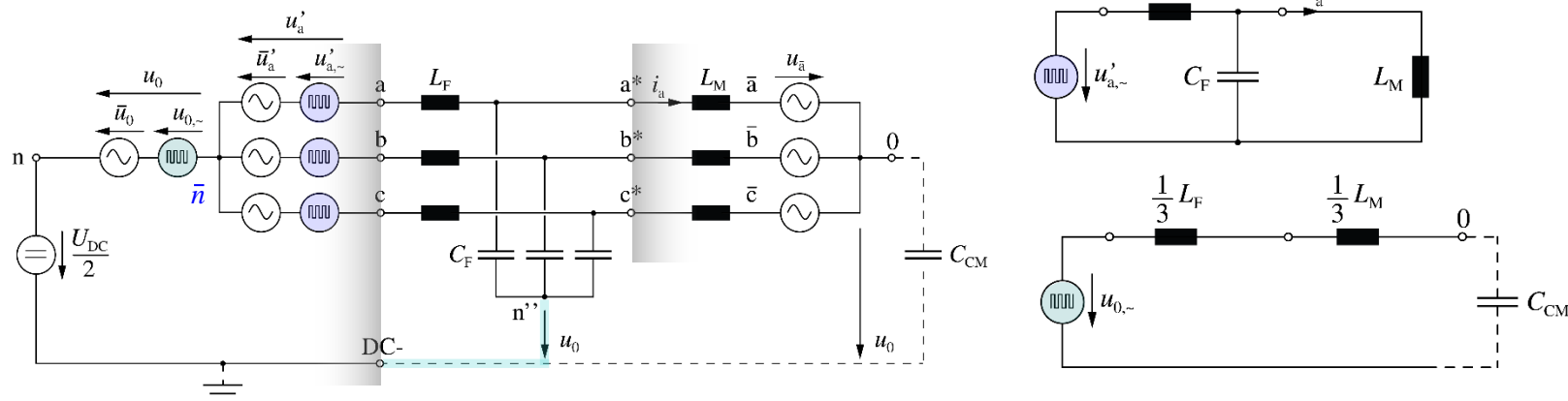

Filter Inductor Types


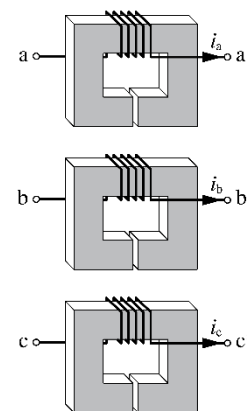
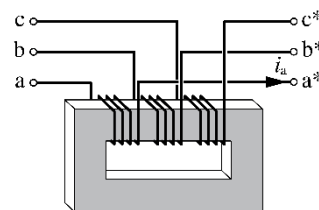
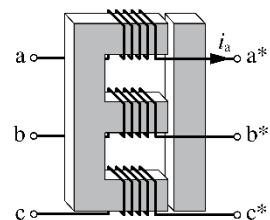


- DM Inductor / CM Inductor / Phase Inductors

———— *Triangular Current Mode (TCM)* ————
ZVS Operation

Full-Sinewave Filter & ZVS Operation

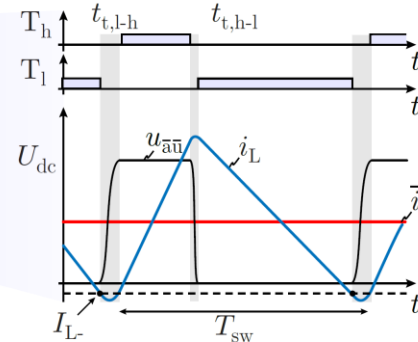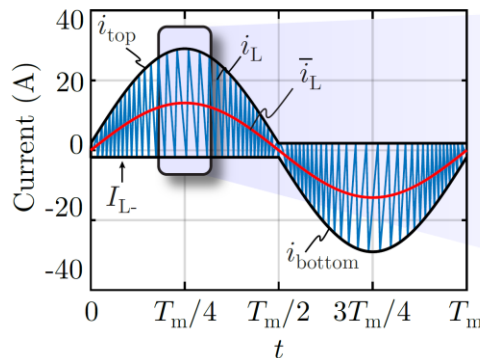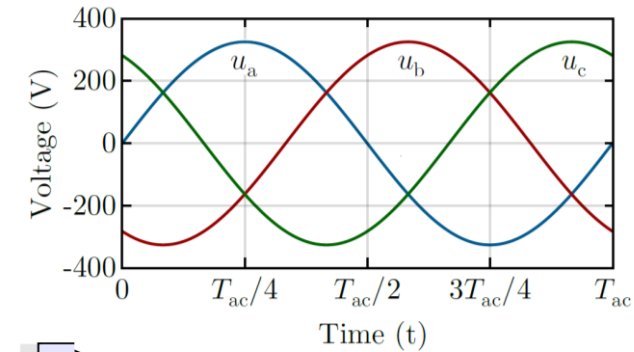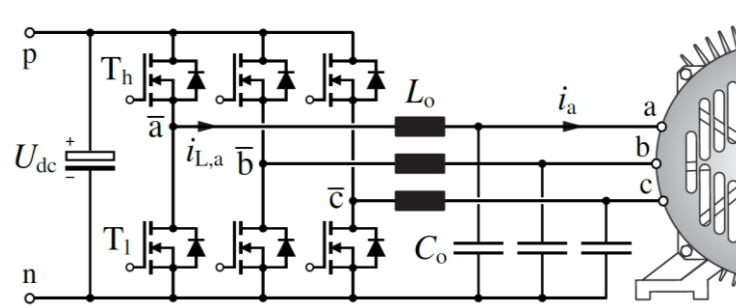- **Sinusoidal Output Voltage**
- **ZVS of Inverter Bridge-Legs**
- **High Sw. Frequency & TCM** → **Low Filter Inductor Volume**




NFO
Sinus

- **Only 33% Increase of Transistor Conduction Losses Compared to CCM (!)**
- **Very Wide Switching Frequency Variation**

Frequency-Bounded TCM \rightarrow B-TCM



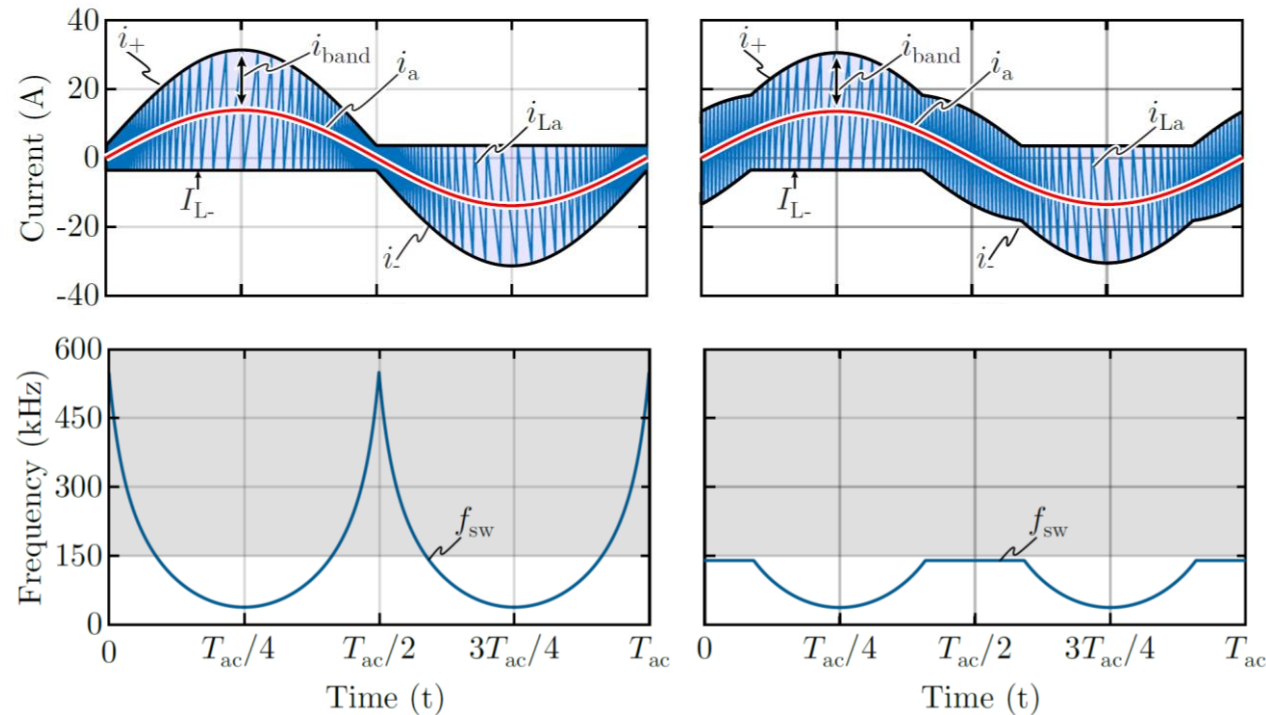
- Very Wide Switching Frequency Variation of TCM \rightarrow B-TCM



- TCM \rightarrow B-TCM — 10% Further Increase of Transistor Conduction Losses

Frequency-Bounded B-TCM \rightarrow S-TCM

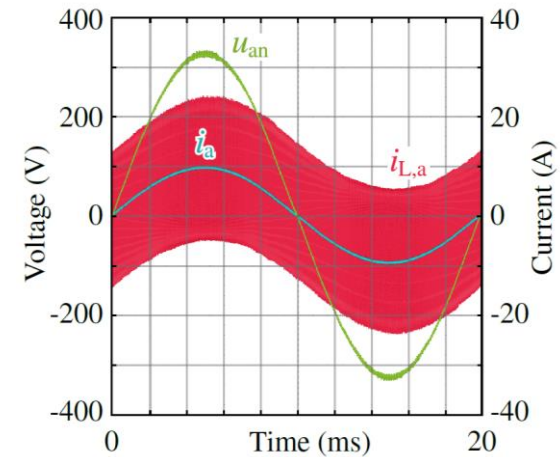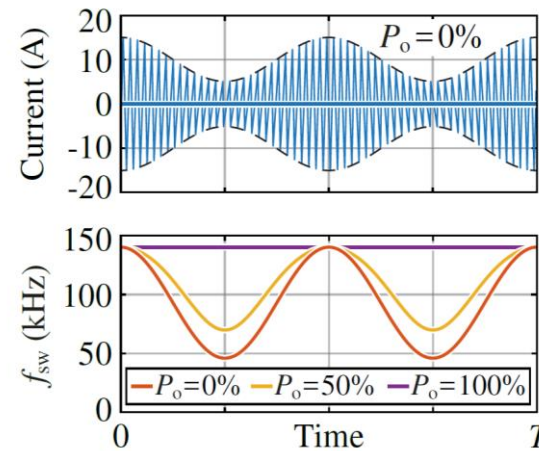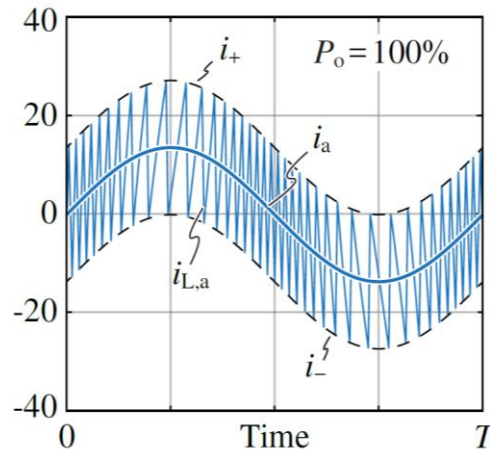
- Sinusoidal Switching Boundaries \rightarrow S-TCM
- Adaption for Low Output Power Considering $f_{sw,max} = 140\text{kHz}$



- TCM \rightarrow S-TCM \approx 10% Further Increase of Transistor Conduction Losses


Remark Residual ZVS Losses

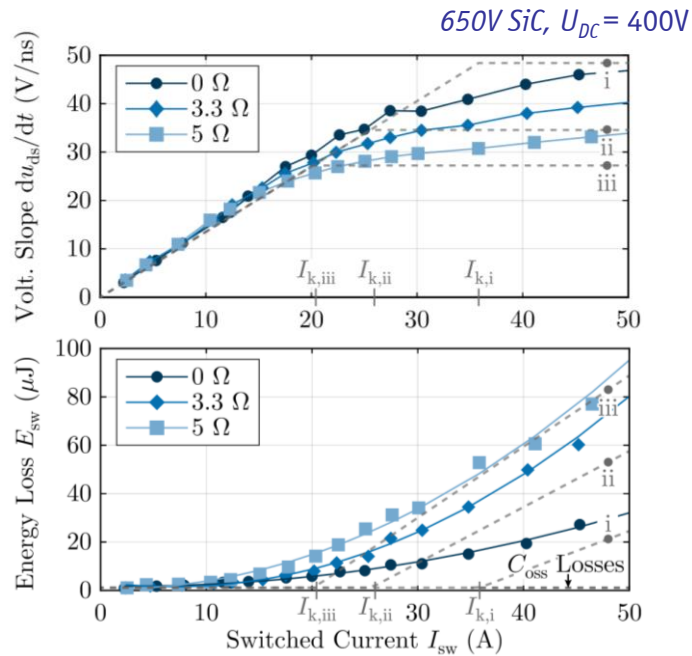- Overlap of u_{DS} & Channel Current i_{ch} @ High $I_{sw} > I_k$
- Temporary Turn-on Due to $u_{GS,i} > u_{th}$



$$\left. \frac{du_{ds}}{dt} \right|_{\max} = \frac{I_k}{C_{ds} + C_{gd}} = \frac{i_g}{C_{gd}}$$


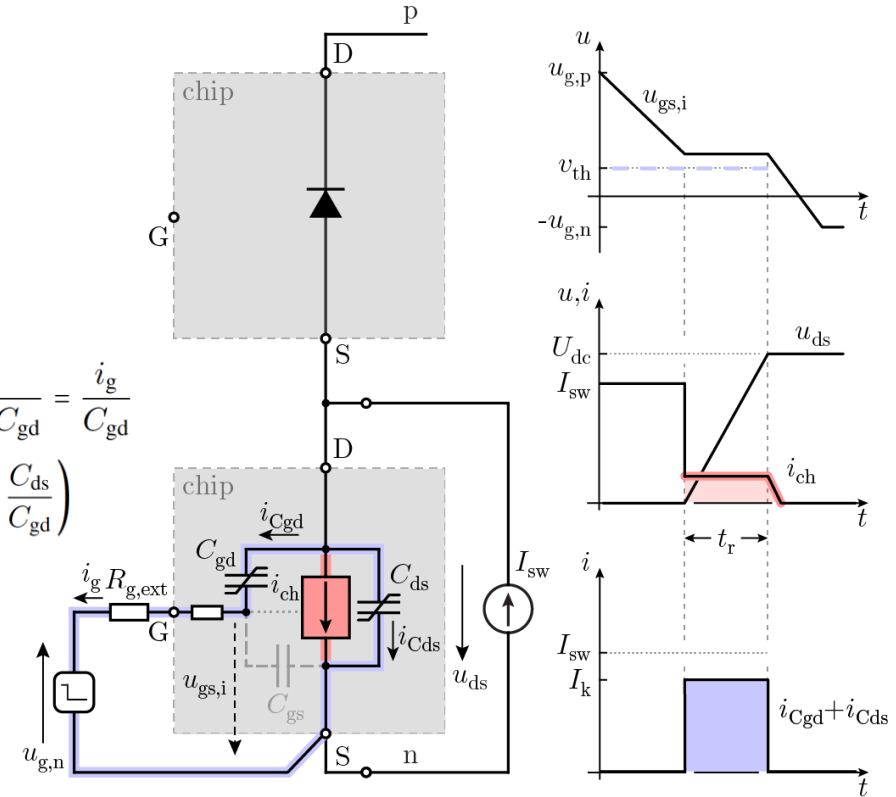
$$I_k = \frac{u_{th} + u_{g,n}}{R_g} \left(1 + \frac{C_{ds}}{C_{gd}} \right)$$



- "Kink" Current I_k Dependent on Inner & Outer Gate Resistance & $u_{g,n}$

Remark Influence of Motor Cable Capacitance

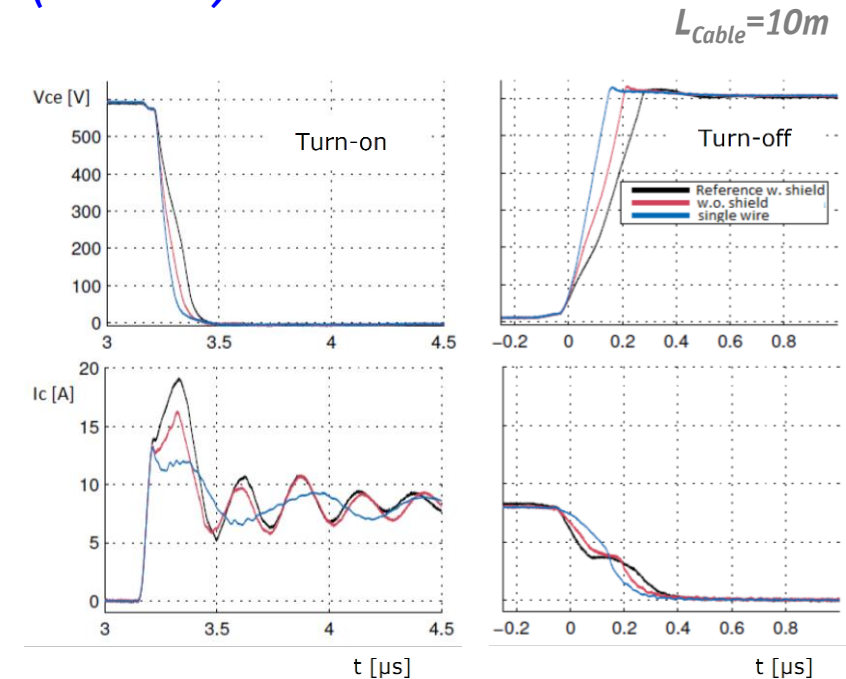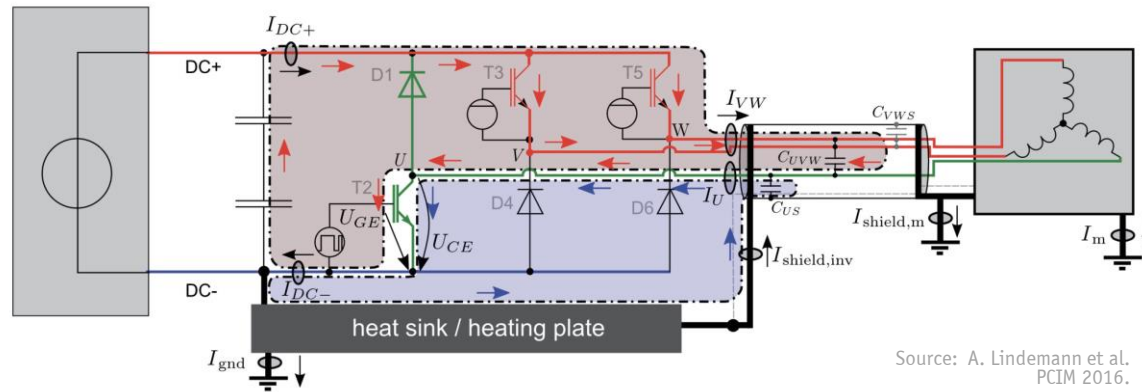- Cable Capacitance of Several 100pF/m (!)
- Large Charging / Discharging Current Peaks @ Sw. Transitions
- Increase of Turn-On / Decrease of Turn-Off Losses
- Analysis for IGBTs shows 30% Overall Increase of Sw. Losses (50m Cable)



→ Output Inductor for Decoupling OR Full-Sinewave Output Filter

Source: AN17-002 SEMIKRON
Innovation + service

———— *Continuous Current Mode (CCM) Operation* ————



Full-Sinewave 2-Stage Output Filter (1)

- Sinewave Output & IEC/EN 55011 Class-A
- Low-Loss Active Damping of 1st Filter Stage — Neg. Cap. Current Feedback
- 2kW / 400V DC-Link 3- Φ 650V GaN Inverter ($I_M=5A$), $f_{out,max} = 500Hz$
- Sw. Frequency $f_{sw} = 100kHz$

PERFECTION IN AUTOMATION
A MEMBER OF THE ABB GROUP





TU
WIEN
TECHNISCHE
UNIVERSITÄT
WIEN
Vienna | Austria

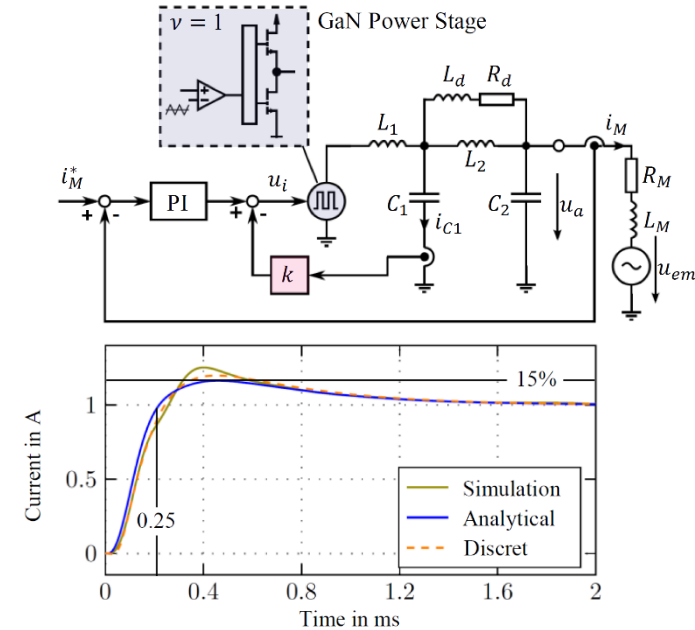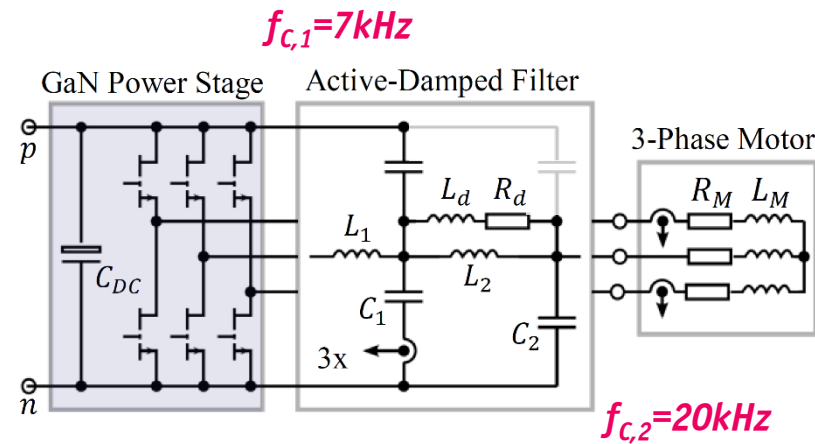

- Evaluation of Optimized Inductors — Soft Sat. Toroidal Iron Powder Cores
- $L_1=200\mu H$ / $C_1=2.5\mu F$ | $L_2=25\mu H$ / $C_2=2.5\mu F$ / $L_d=33\mu H$ / $R_d=5.6\Omega$

Full-Sinewave 2-Stage Output Filter (2)


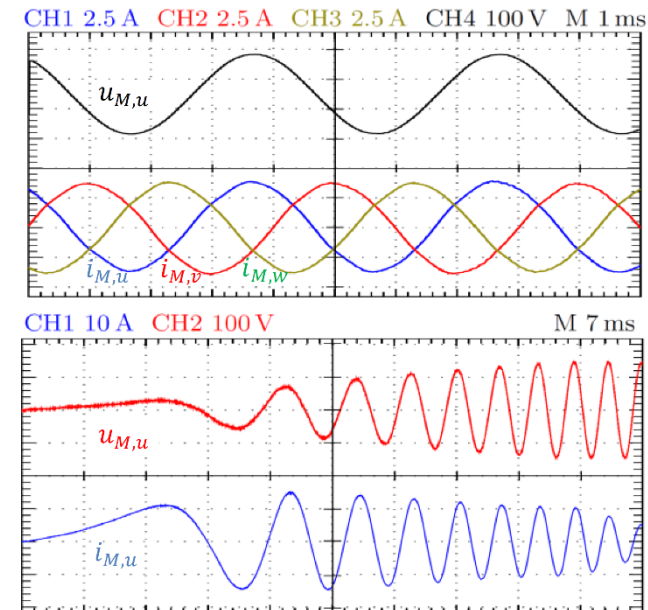
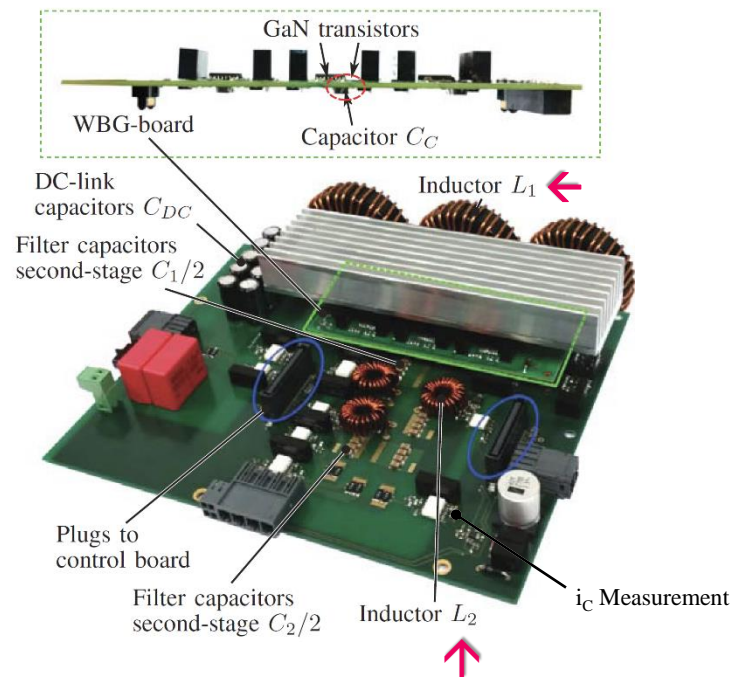
- **Exp. Verification** — **650V E-Mode GaN Systems Transistors** (50mΩ)
- **Sw. Frequency** $f_{sw} = 100\text{kHz}$, **Efficiency** $\approx 98\%$
- **200mm x 250mm**



- **Stationary Motor Phase Curr. /Voltage @ 2.5Nm & $f_{out} = 250\text{Hz}$**
- **Speed Increase from Standstill to $n = 3000\text{rpm}$ in 60ms**

Full-Sinewave 2-Stage Output Filter (3)

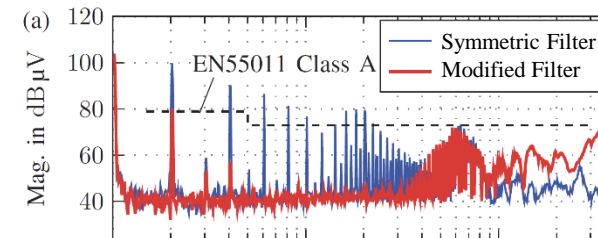
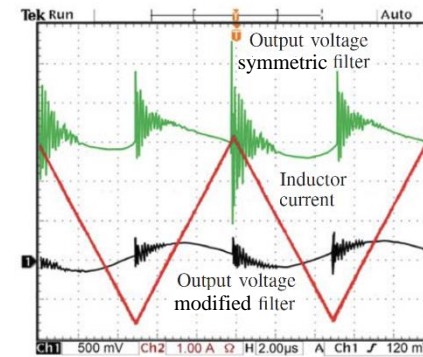
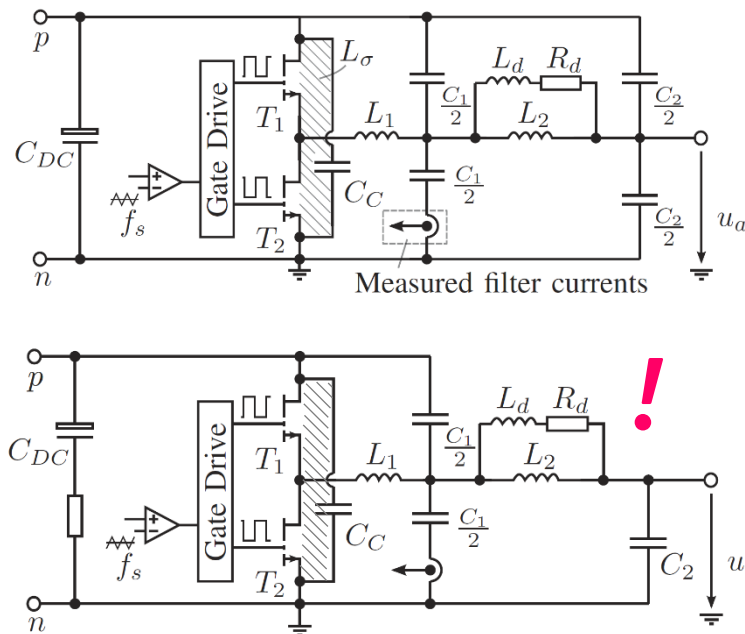
- *Modification of Output Filter Structure*
- *Elimination of Direct Cap. Coupling Between Output and Noisy (!) DC+ (Due to ESR of C_{DC})*
- *For Opt. i_c -Feedback C_1 Realized Using \approx Linear Kemet KC-Link*



- *Modified Filter \rightarrow Compliance to EMI Standard EN55011 Class-A*

GaN vs. IGBT Inverter Efficiency Comparison

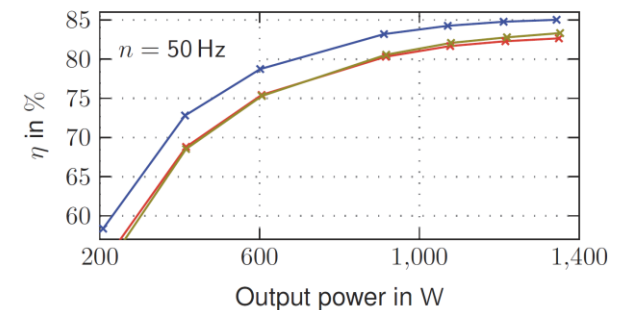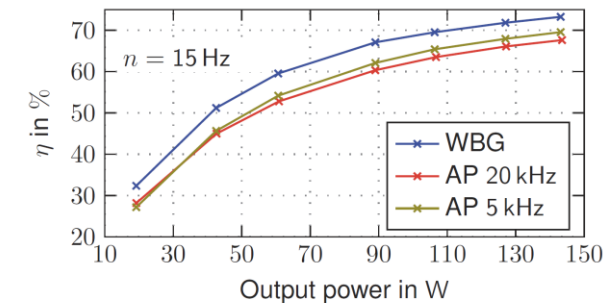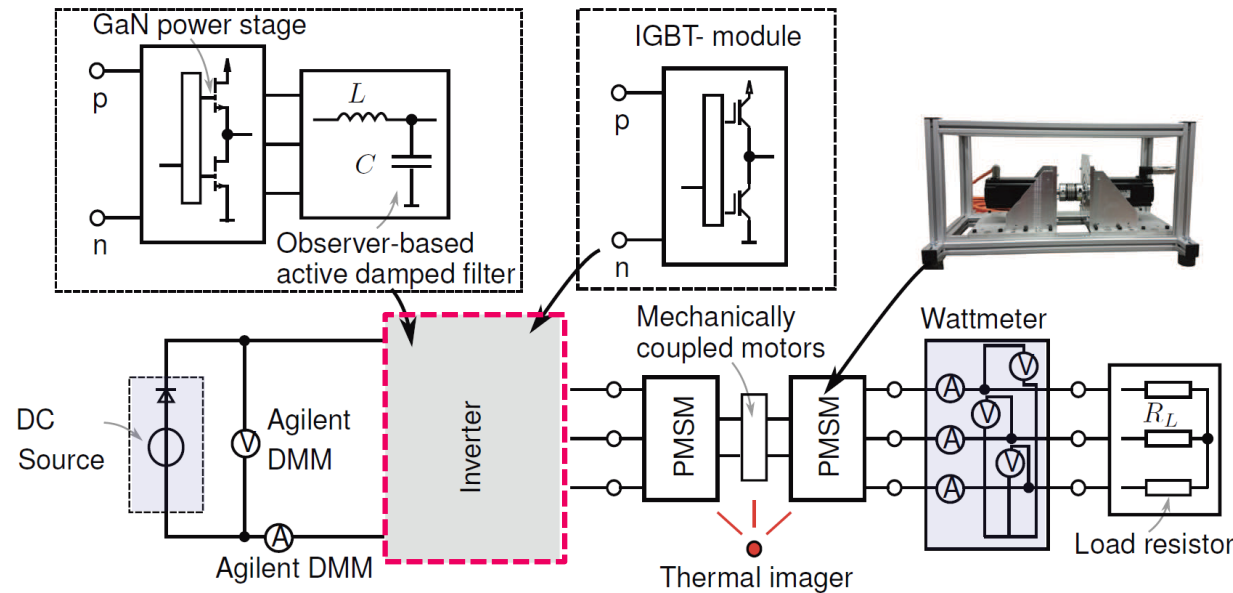- *Si Easypack 1200V/35A vs. GaN 650V/30A (50mΩ)*
- *5...20kHz Standard PWM IGBT Motor Inverter (B&R Industrial Automation)*
- *Efficiency Measurement — Inverter DC Input → Load Machine AC Output*




- *Efficiency Improvement of 2-4% in Whole Operating Range*
- *Low Sw. Losses of GaN Inverter & Low Output Filter Losses & Low Motor Iron Losses*

3- Φ 650V GaN Inverter System (1)

Source: **YASKAWA**

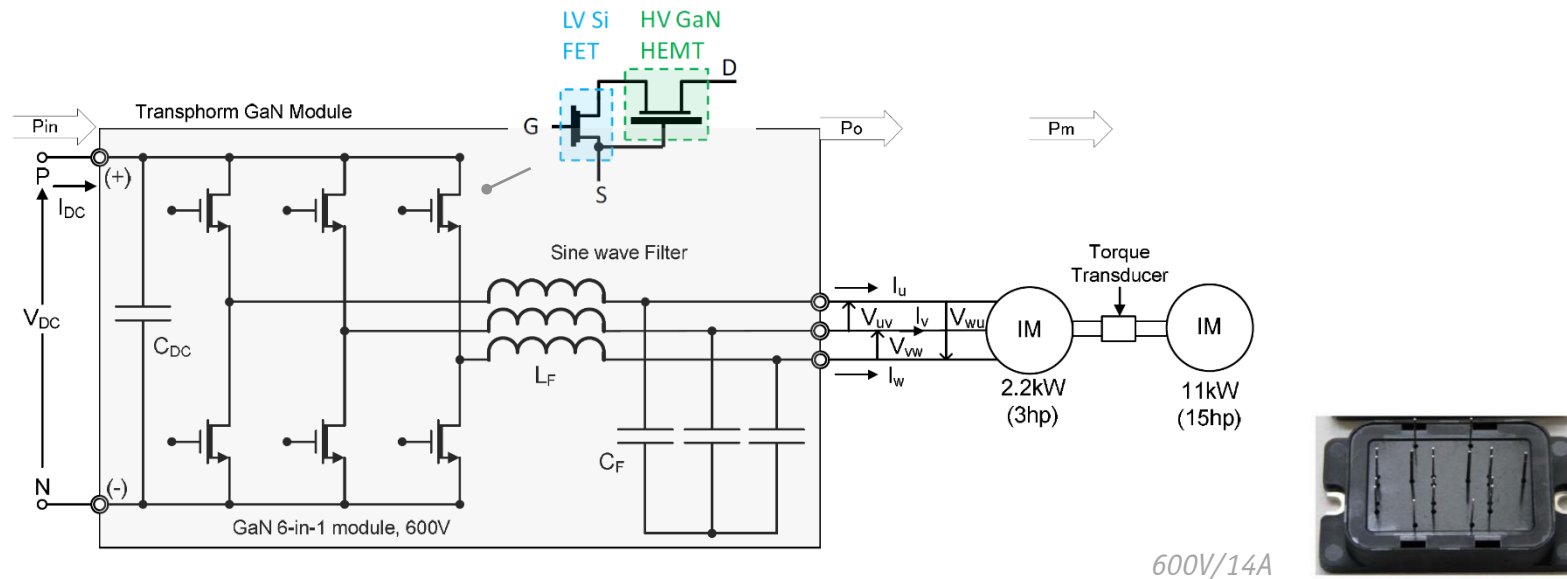- **Transphorm 650V Normally-On GaN HEMT/30V Si-MOSFET Cascode 6-in-1 Power Module**
- **Sinewave LC Output Filter** — Corner Frequency $f_c = 34\text{kHz}$ ($f_{sw} = 100\text{kHz}$)
- **No Freewheeling Diodes**




→ **Comparison to Si-IGBT Drive Systems**



3- Φ 650V GaN Inverter System (2)

Source: **YASKAWA**

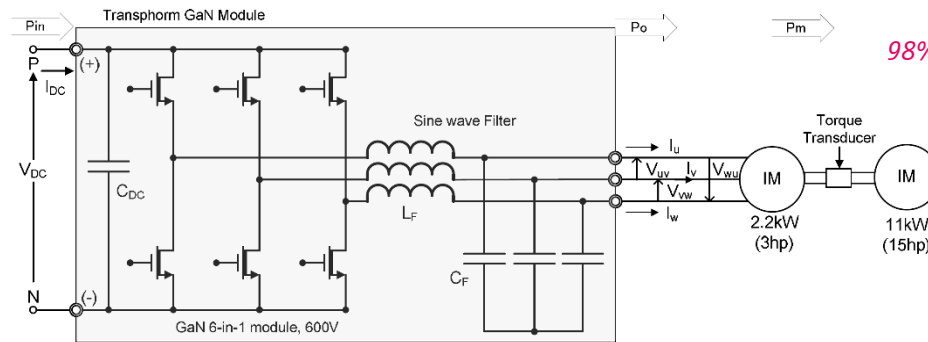
- Comparison of **GaN** Inverter w/ LC-Filter to **Si-IGBT** System (No Filter, $f_{sw}=15\text{kHz}$)
- Measurement of **Inverter Stage** & **Overall Drive Losses** @ 60Hz



98% →

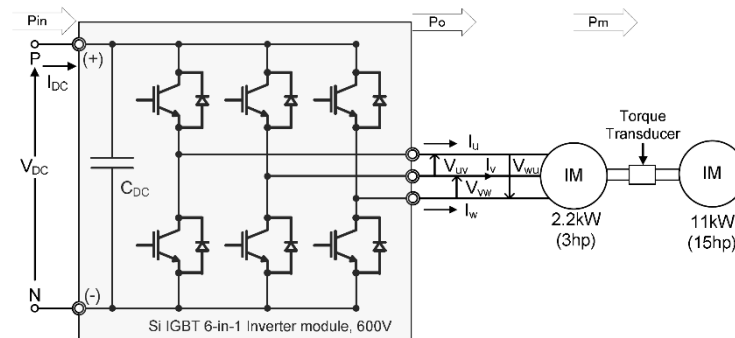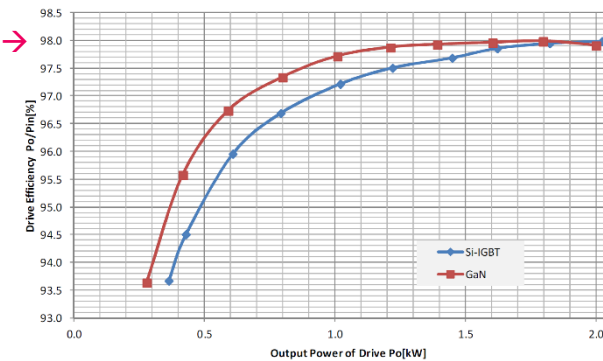

80% →


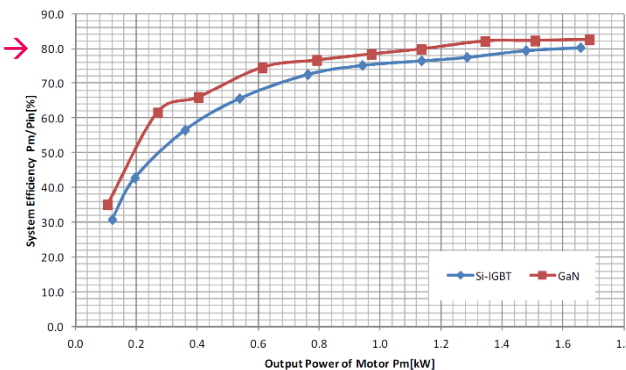


→ **2% Higher Efficiency of GaN System Despite LC-Filter (Saving in Motor Losses) !**

————— *Multi-Level / Multi-Cell
Converters & Modularity* —————


3-Level T-Type Inverter (1)

- *Higher Number of Output Voltage Levels / Lower CM Voltage Steps*
- *Neutral Point Clamped | Flying Capacitor | T-Type Bridge-Leg Topologies*

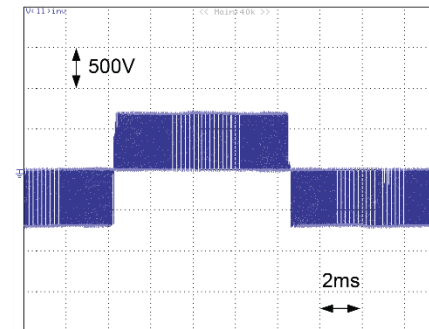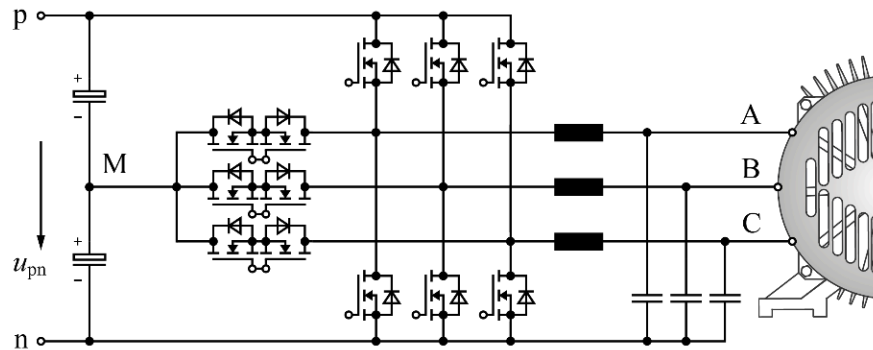

2-Level Bridge-Leg

Line-to-Line Voltage

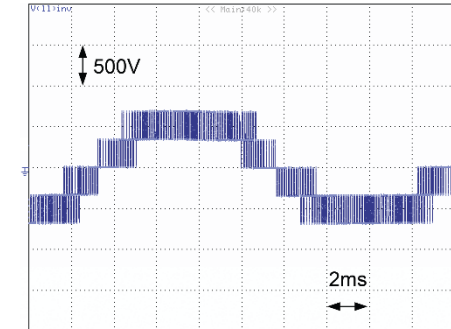


3-Level Bridge-Leg

- *More Complicated Bridge-Leg Structure*
- *On-State-Losses of Series-Connected Switches*

3-Level T-Type Inverter (2)



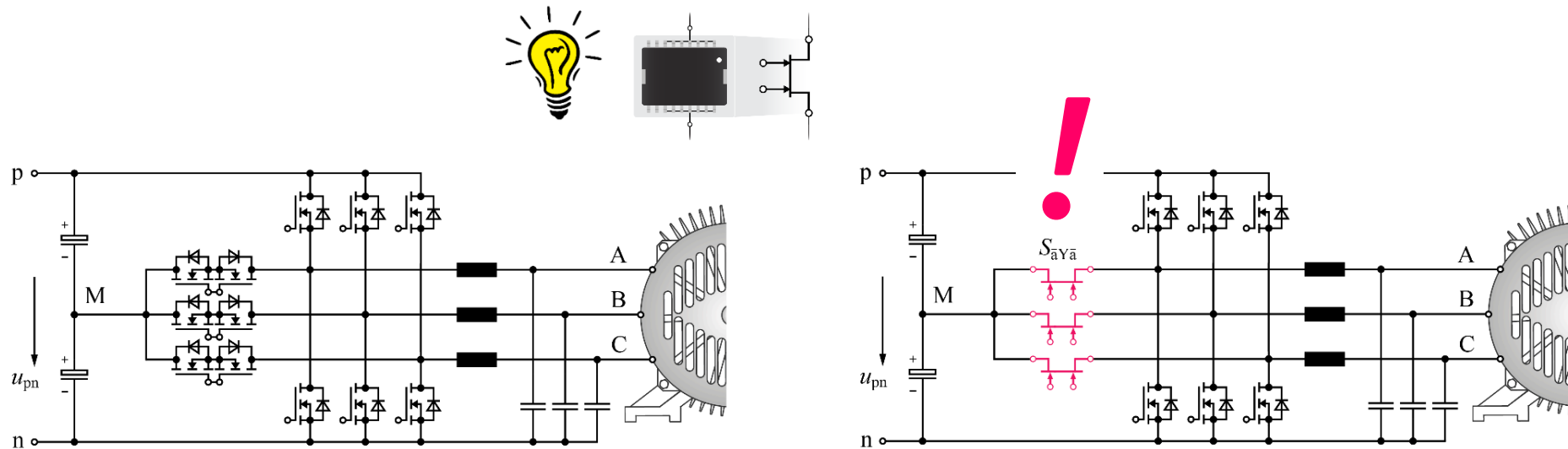
- Utilization of **600V Monolithic Bidirectional GaN Switches**
- 2-Gate Structure Provides Full Controllability



- **Factor 4 (!) Reduction of Chip Area vs. Discrete Realization @ Same $R_{(on)}$**

Flying Cap. (FC) 3-Level Converter

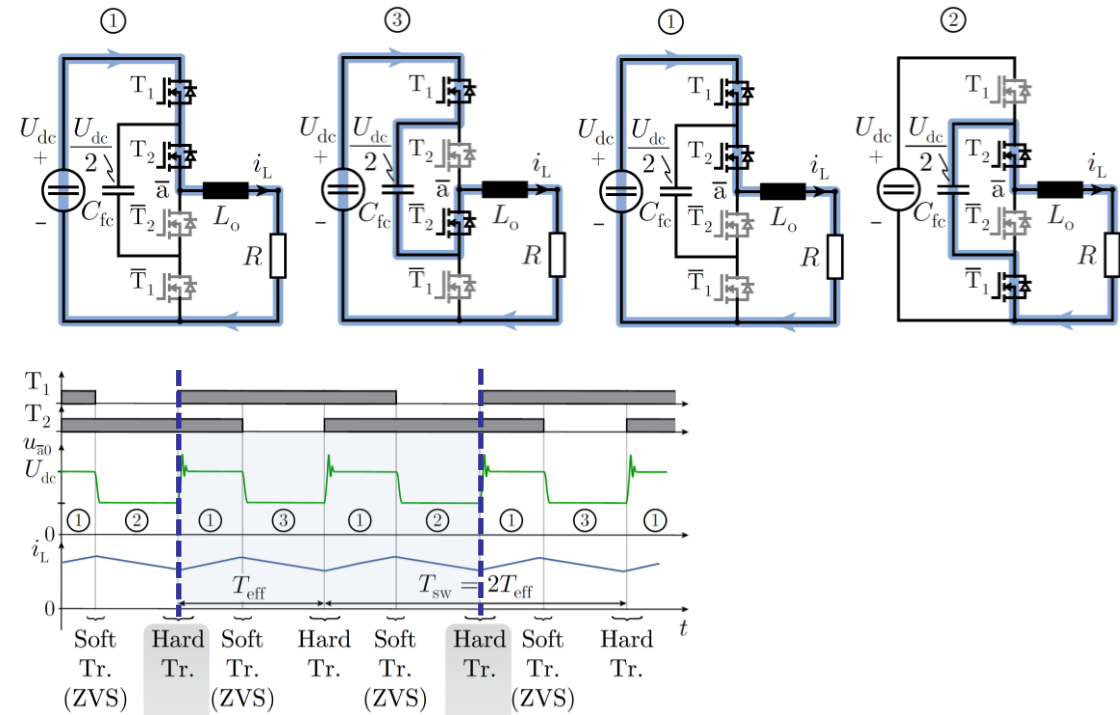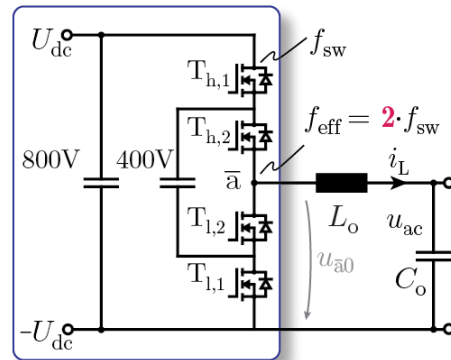
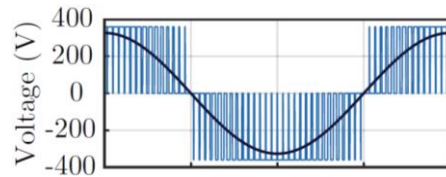
- 3-Level Flying Cap. (FC) Converter → No Connection to DC-Midpoint
- Involves All Switches in Voltage Generation → Eff. Doubles Device Sw. Frequency



- FC Voltage Balancing Possible also for DC Output

Scaling of Flying Cap. Multi-Level Concepts

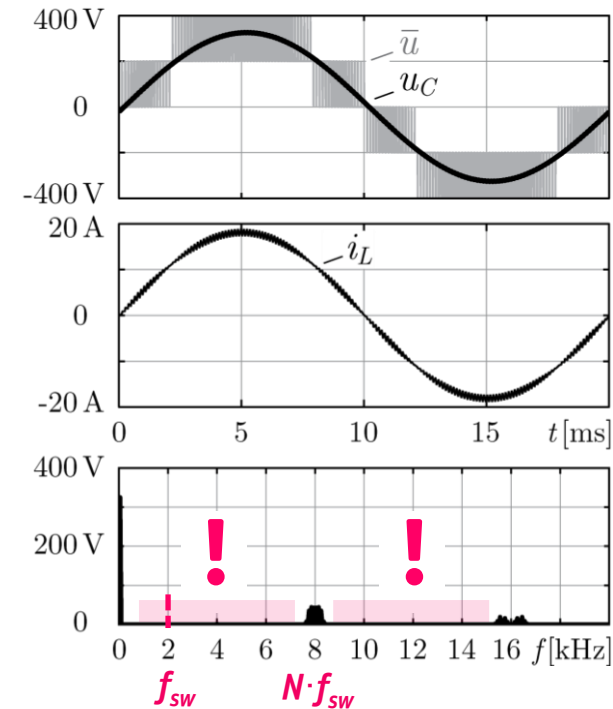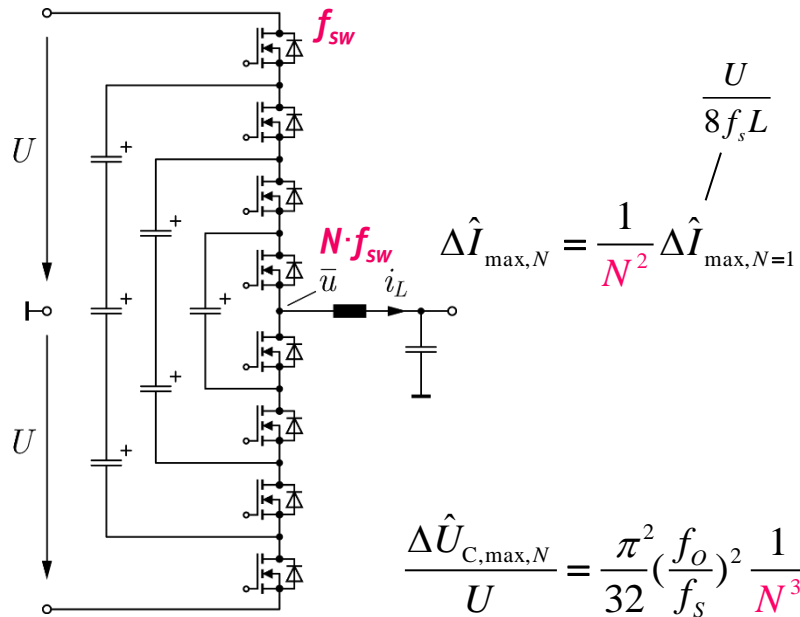
- **Series Interleaving** → **Reduced Ripple**
- $f_{sw,eff} = N \cdot f_{sw}$ @ f_{sw} -Determined (!) **Switching Losses**
- **Lower Overall On-Resistance** @ **Given Blocking Voltage**
- **Application of LV Technology** @ **HV**



- **Scalability** / **Manufacturability** / **Standardization** / **Redundancy**

SiC/GaN Figure-of-Merit



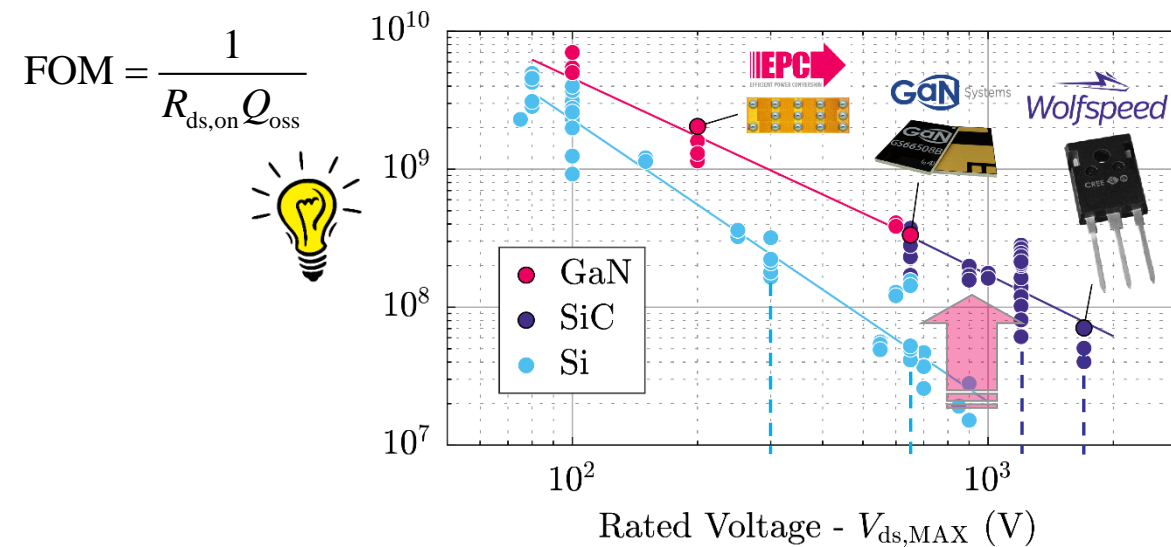
- *Figure-of-Merit (FOM) Quantifies Conduction & Switching Properties*
- *FOM Identifies Max. Achievable Efficiency @ Given Sw. Frequ.*



- *Advantage of LV over HV Power Semiconductors*
- *Advantage of Multi-Level over 2-Level Converter Topologies*

X-FOM of ML-Bridge-Legs

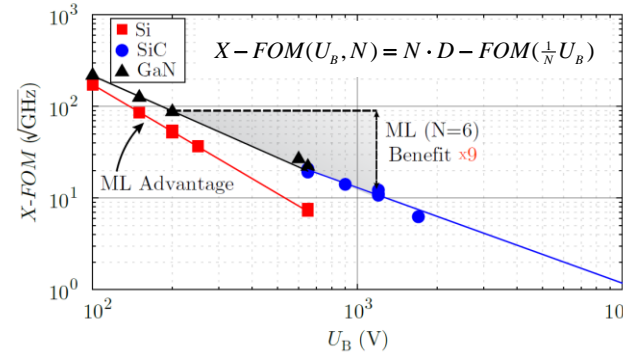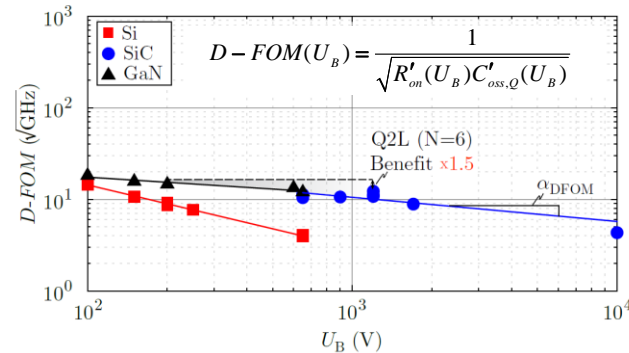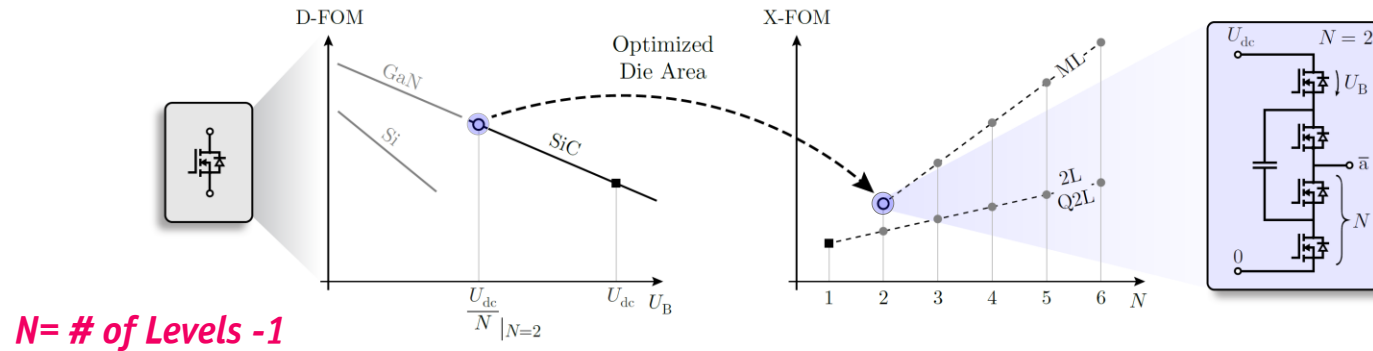- Quantifies Bridge-Leg Performance of N-Level FC Converters
- Identifies Max. Achievable Efficiency & Loss Opt. Chip Area @ Given Sw. Frequ.



- Compared to 2-Level Benchmark @ Same Filter Ind. Volt-Seconds




$$\begin{aligned} P_{semi,min,ML} &\approx \frac{1}{N^{1.2}} P_{semi,min,2L} \\ A_{chip,ML} &\approx N^{1.2} A_{chip,2L} \end{aligned}$$





7-Level Flying Cap. 200V GaN Inverter (1)

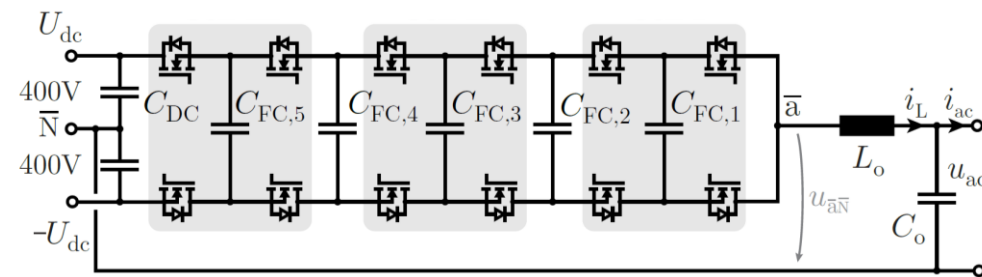- **DC-Link Voltage** 800V
- **Rated Power** 2.2 kW / Phase
- **99% Efficiency** → **Natural Convection Cooling (!)**




★ 260 W/in³

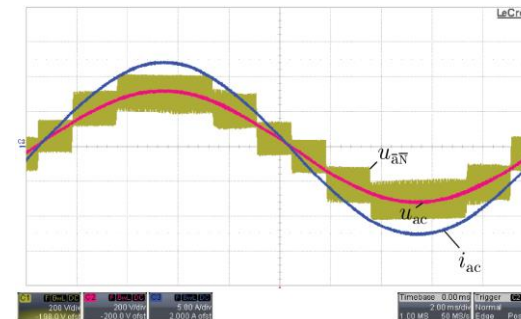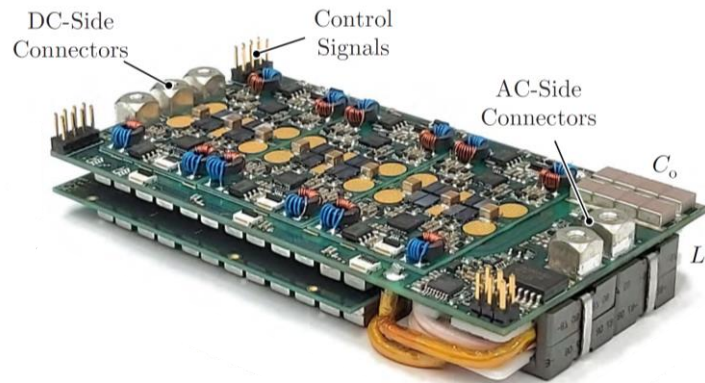


- **High Effective Sw. Frequency** ($6 \times 30\text{kHz} = 180\text{kHz}$) → **Small Filter Inductor L_o**

7-Level Flying Cap. 200V GaN Inverter (2)

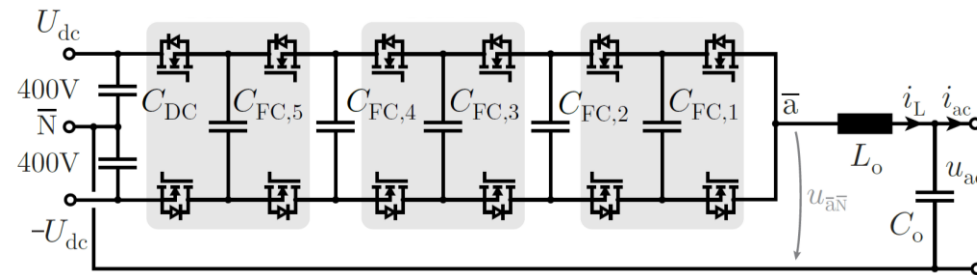- **DC-Link Voltage** 800V
- **Rated Power** 2.2 kW / Phase
- **99% Efficiency** → **Natural Convection Cooling (!)**




★ 260 W/in³

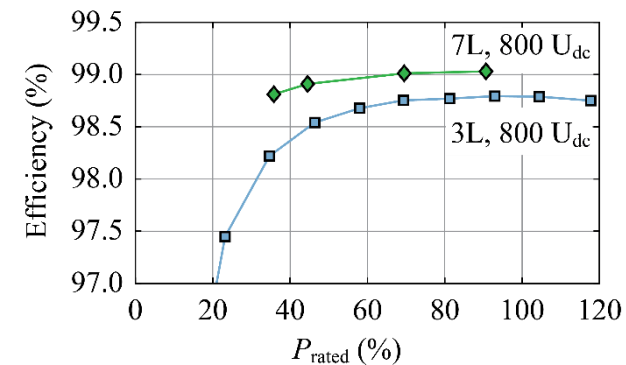

- **High Effective Sw. Frequency** ($6 \times 30\text{kHz} = 180\text{kHz}$) → **Small Filter Inductor L_o**

3- Φ Hybrid Multi-Level Inverter Demonstrator

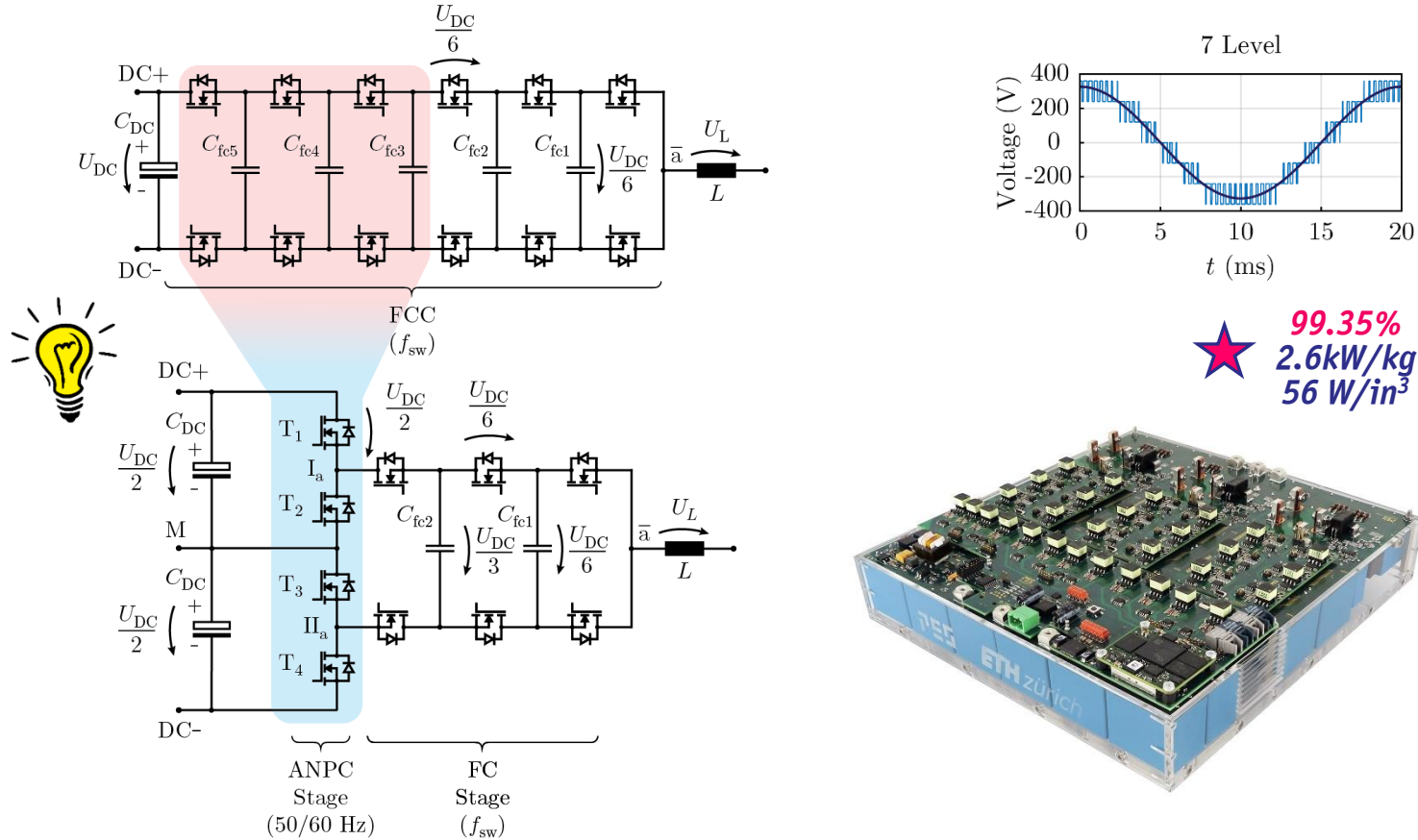- Realization of a **99%+ Efficient 10kW 3- Φ 400V_{rms,LL} Inverter System**
- **7-Level Hybrid Active NPC Topology / LV Si-Technology**



- **200V Si \rightarrow 200V GaN Technology Results in 99.5% Efficiency**


*Quasi-2L/3L
Flying Capacitor Inverter*

Quasi-2L & Quasi-3L Inverters (1)

- **Operation of N-Level Topology in 2-Level or 3-Level Mode**
- **Intermediate Voltage Levels Only Used During Sw. Transients**
- **Applicability to All Types of Multi-Level Converters**

- Schweizer (2017)

ABB

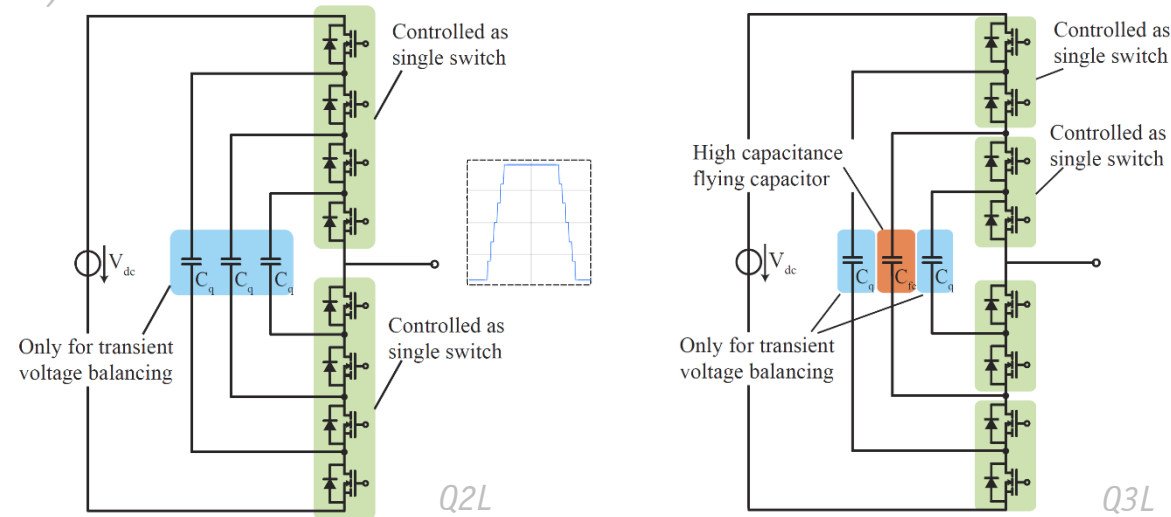

- **Reduced Avg. dv/dt → Lower EMI & Lower Overvoltages @ Motor Terminals**
- **Clear Partitioning of Overall Blocking Voltage & Small Flying Capacitors**
- **Low Voltage/Low $R_{DS(on)}$ /Low \$ MOSFETs → High Efficiency / No Heatsinks / SMD Packages**



Quasi-2L & Quasi-3L Inverters (3)

- Schweizer (2017)



- Operation of 5L Bridge-Leg Topology in Quasi-3L Mode
- Intermediate Voltage Levels Only Used During Sw. Transients
- Applicability to All Types of Multi-Level Converters

Operation @ 3.2kW

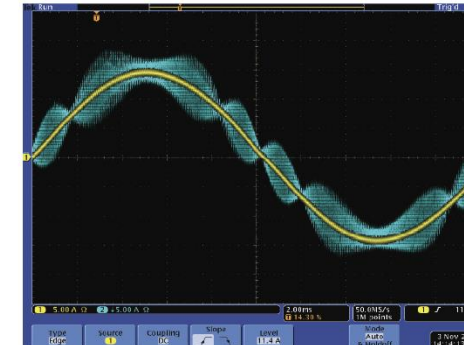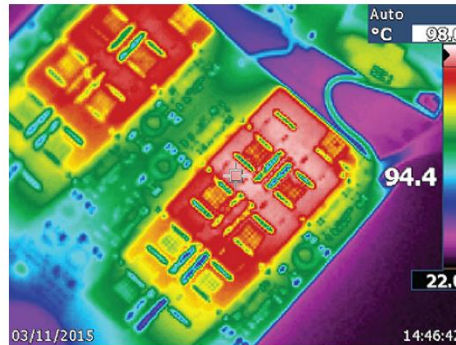

— Conv. Output Voltage
— Sw. Stage Output Voltage
— Flying Cap. (FC) Voltage
— Q-FC Voltage (Uncntrl.)

— Output Current
— Conv. Side Current

- Reduced Avg. dv/dt → Lower EMI & Lower Overvoltages @ Motor Terminals
- Clear Partitioning of Overall Blocking Voltage & Small Flying Capacitors
- Low Voltage/Low $R_{DS(on)}$ /Low \$ MOSFETs → High Efficiency / No Heatsinks / SMD Packages

***Ultra-Compact
Power Module with
Integrated Filter***

———— **650V GaN E-HEMT Technology** ————


$$f_{sw,eff} = 4.8\text{MHz}$$

$$f_{out} = 100\text{kHz}$$






Integrated Filter GaN Half-Bridge Module


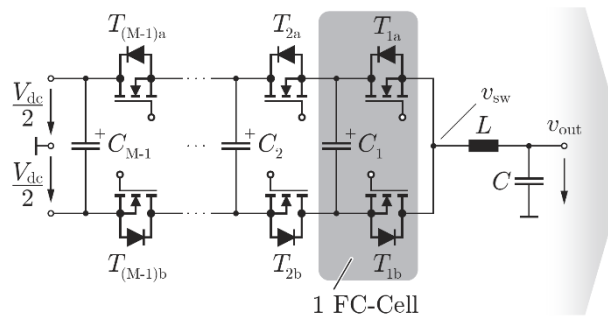
- *Minimization of Filter Volume by Series & Parallel Interleaving & Extreme Sw. Frequency*
- *Handling of DC Output Requires Flying Capacitor Approach for Series Interleaving*



$$f_{sw,eff} = (M-1) \cdot f_{sw}$$

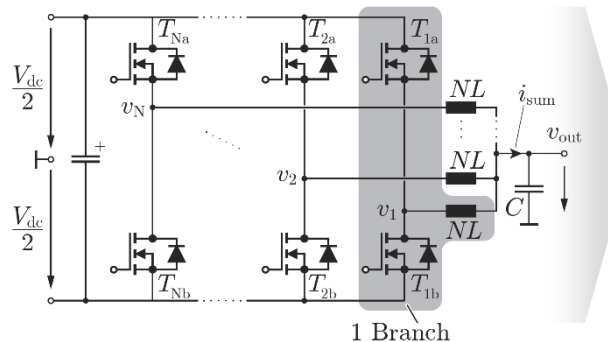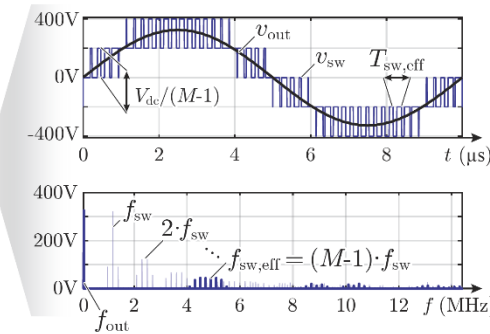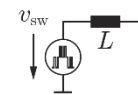



$$f_{sw,eff} = N \cdot f_{sw}$$

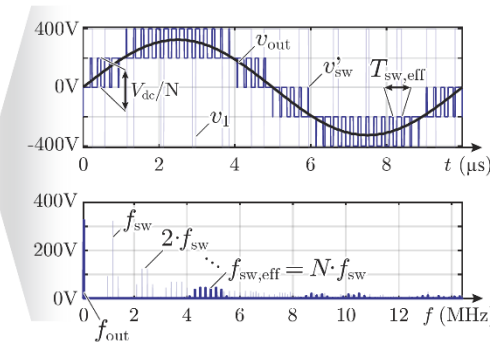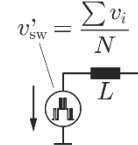


→ **Target:** *Best Combination of Multiple Levels (M) & Parallel Branches (N)*

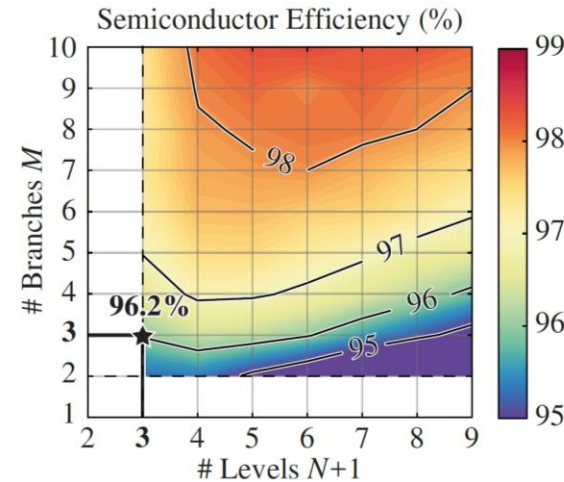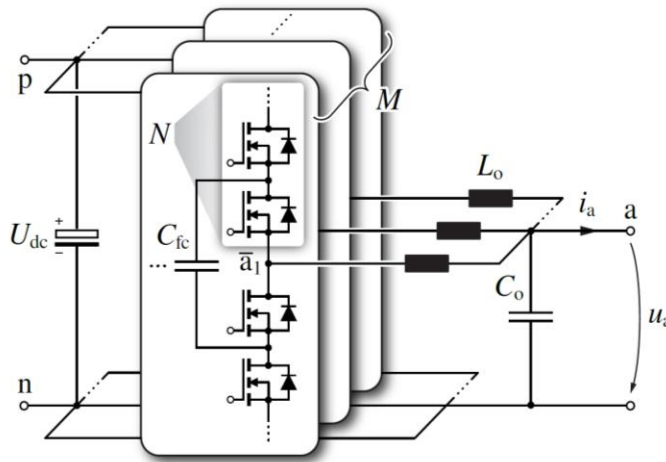4.8MHz GaN Half-Bridge Phase Module

- Combination of *Series & Parallel Interleaving*
- 600V GaN Power Semiconductors, $f_{sw} = 800\text{kHz}$
- Volume of $\approx 180\text{cm}^3$ (incl. Control etc.)
- H_2O Cooling Through Baseplate




★ 820 W/in³

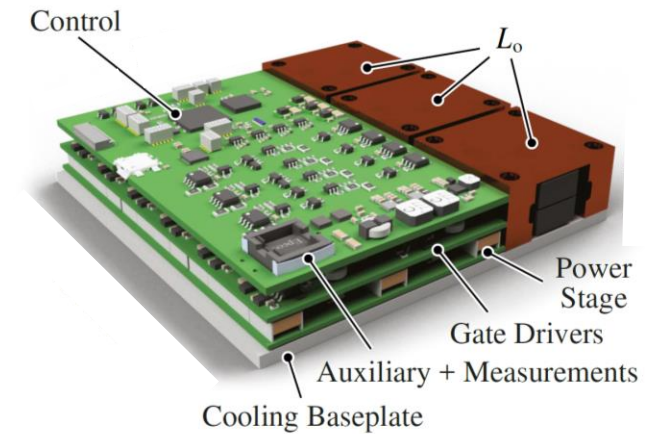

- Operation @ $f_{out} = 100\text{kHz}$ / $f_{sw,eff} = 4.8\text{MHz}$, 10kW, $U_{dc} = 800\text{V}$

Remark High-BW High-CMRR Current Measurement

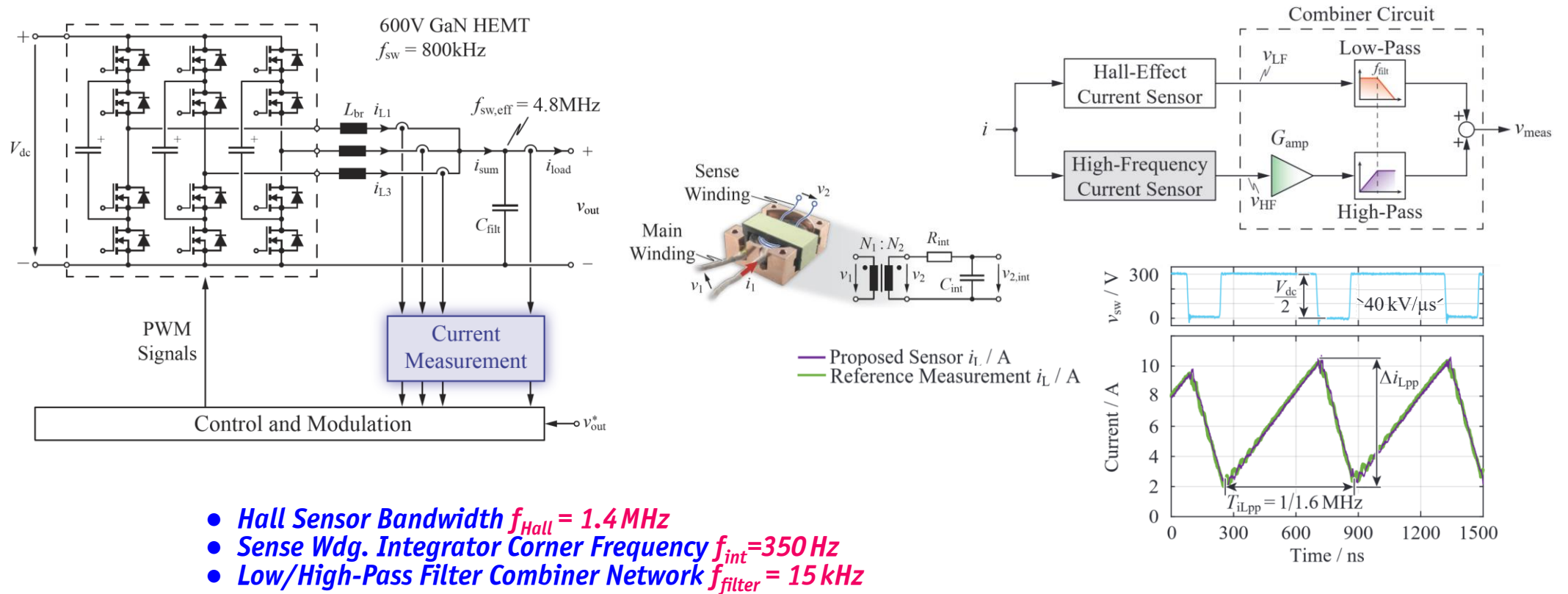- Extension of Commercial Hall Sensor DC... $f_{Hall} \approx 500\text{kHz} \rightarrow \text{DC} \dots 10\text{MHz}$
- Low-Pass & High-Pass Filter Network Combining HF-Sensor & LF Hall-Sensor



- Hall Sensor Bandwidth $f_{Hall} = 1.4\text{ MHz}$
- Sense Wdg. Integrator Corner Frequency $f_{int} = 350\text{ Hz}$
- Low/High-Pass Filter Combiner Network $f_{filter} = 15\text{ kHz}$




————— *Motor-Integrated
Inverter Systems* —————



Stacked-Multi-Cell (SMC) Inverter

- **Fault-Tolerant VSD**
- **Low-Voltage Inverter Modules**
- **Very-High Efficiency / Power Density**
- **Automated Manufacturing**

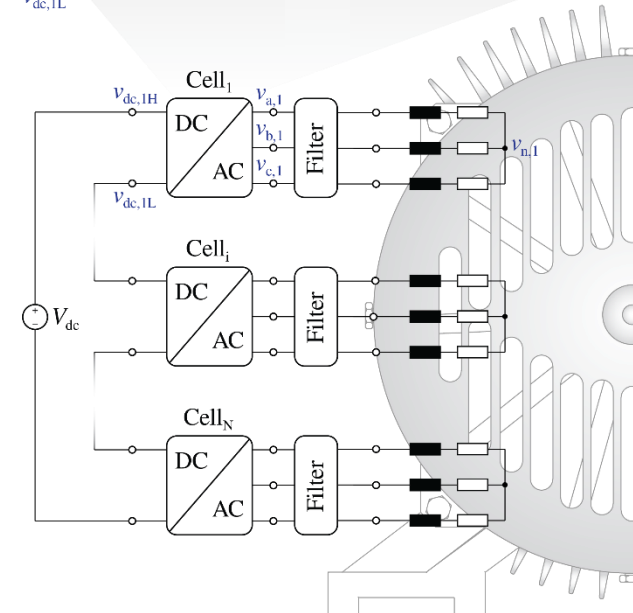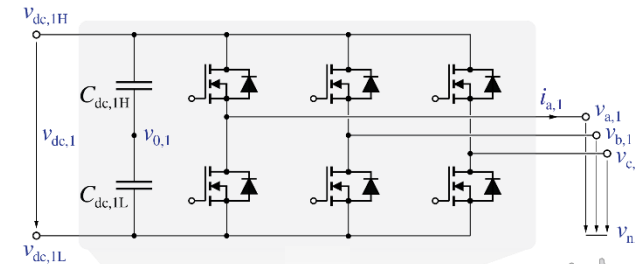
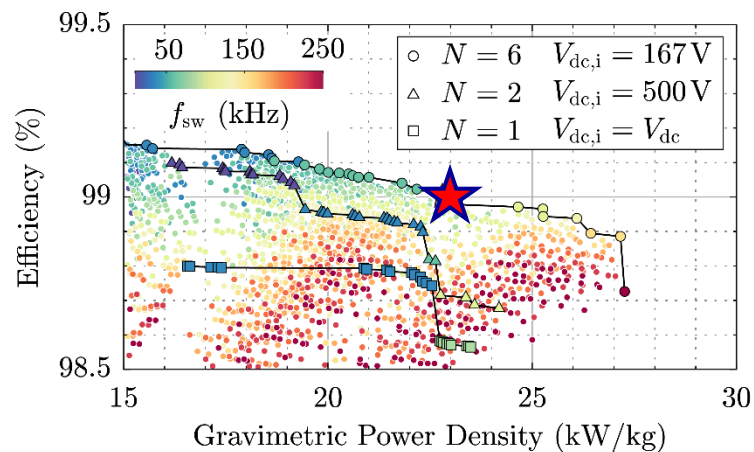
- **Rated Power** 45kW / $f_{out} = 2\text{kHz}$
- **DC-Link Voltage** 1 kV



- **Smart Motor / Plug & Play | Connected / Intelligent VSD 4.0**

Motor-Integrated SMC-Inverter

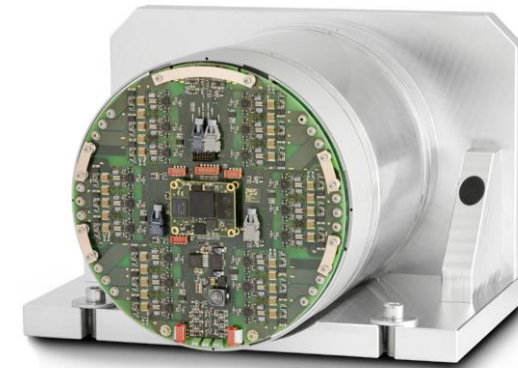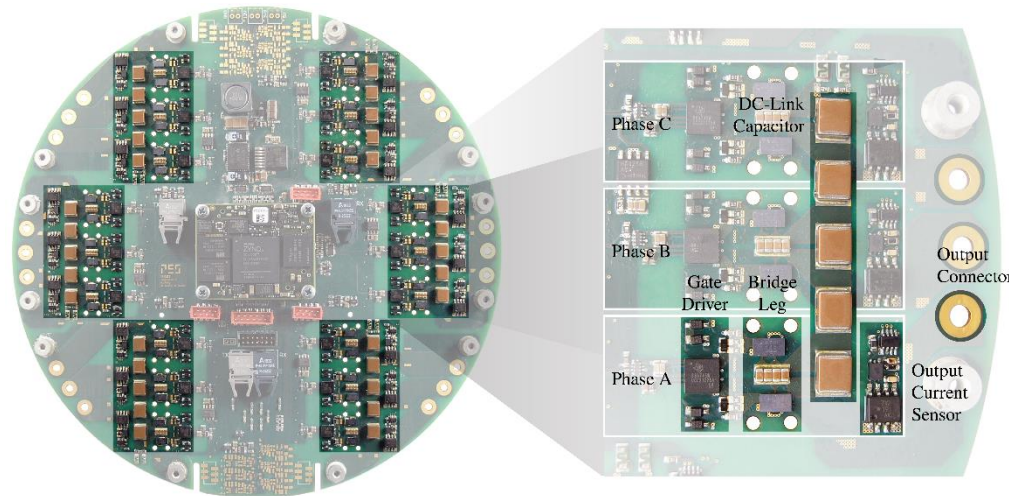- **Rated Power** **9kW @ 3700rpm**
- **DC-Link Voltage** **650V...720V**
- **3- Φ Power Cells** **5+1**
- **Outer Diameter** **220mm**





- **Axial Stator Mount**
- **200V GaN e-FETs**
- **Low-Capacitance DC-Links**
- **45mm x 58mm / Cell**

- **Main Challenge** — **Thermal Coupling/Decoupling of Motor & Inverter**

Remark Multi-Axis Drive Systems

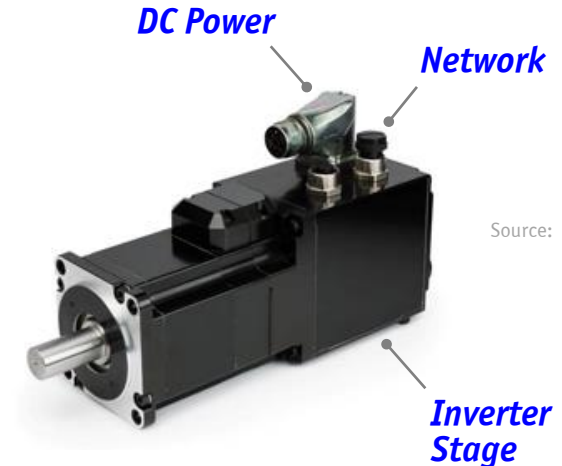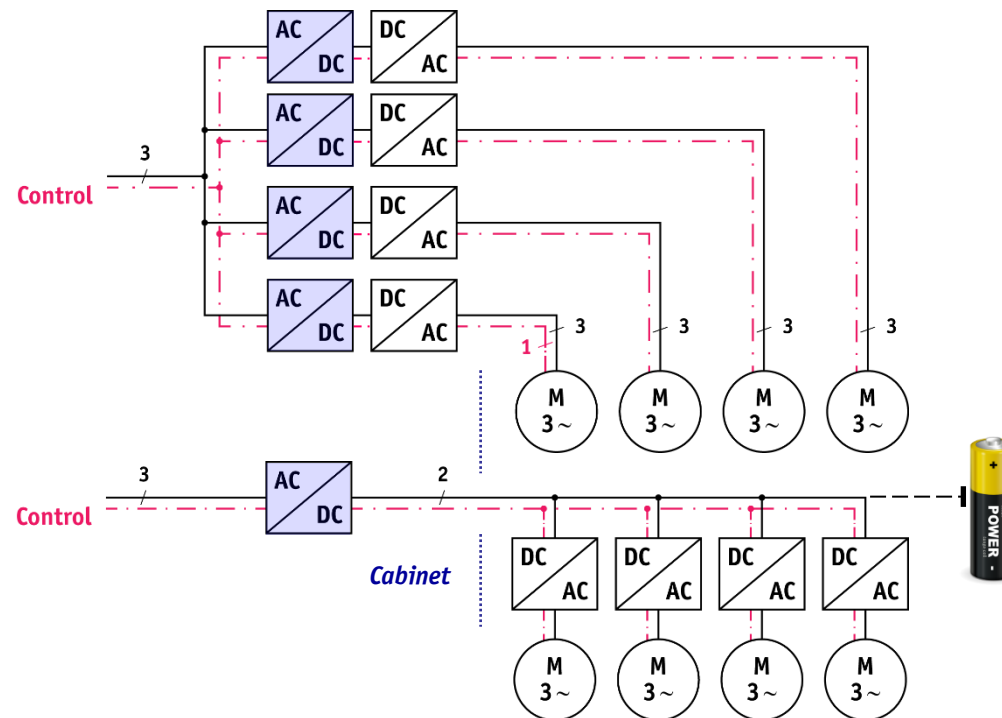- **Common DC-Bus** — **Single AC/DC Converter / Smaller Cabinet**
- **Motor Integration of DC/AC Stage** — **Massive Saving in Cabling Effort / Simplified Installation**






Source: YASKAWA

- **Facilitates DC-Bus Energy Buffer**
- **Direct Energy Exchange @ DC-Bus / Higher Efficiency / Unidir. Front-End**

———— *Double-Bridge (DB) Inverter* ————

Compressor-Integrated DB-GaN-Inverter




- *E-Mobility 5...15kW Fuel Cell Pressurized Air Supply*
- *1kW Rated Power | $U_{FC} = 40...130V$ | $f_{sw} = 300kHz$ | $n = 280'000rpm$ / $f_{out} = 4.6kHz$*
- *Low EMI / Low Cabling Effort*

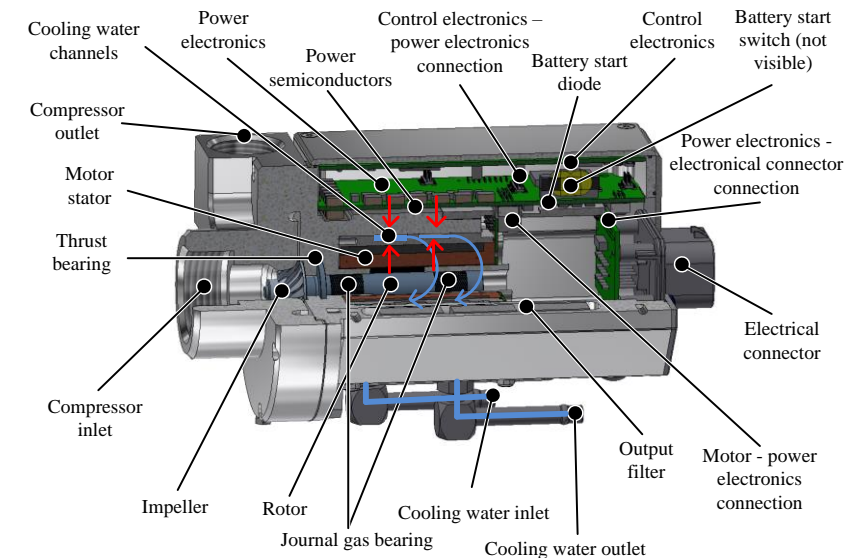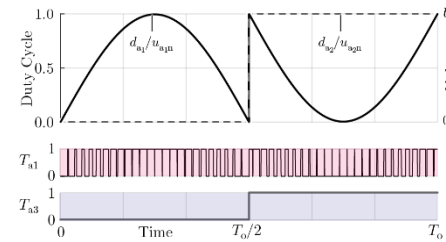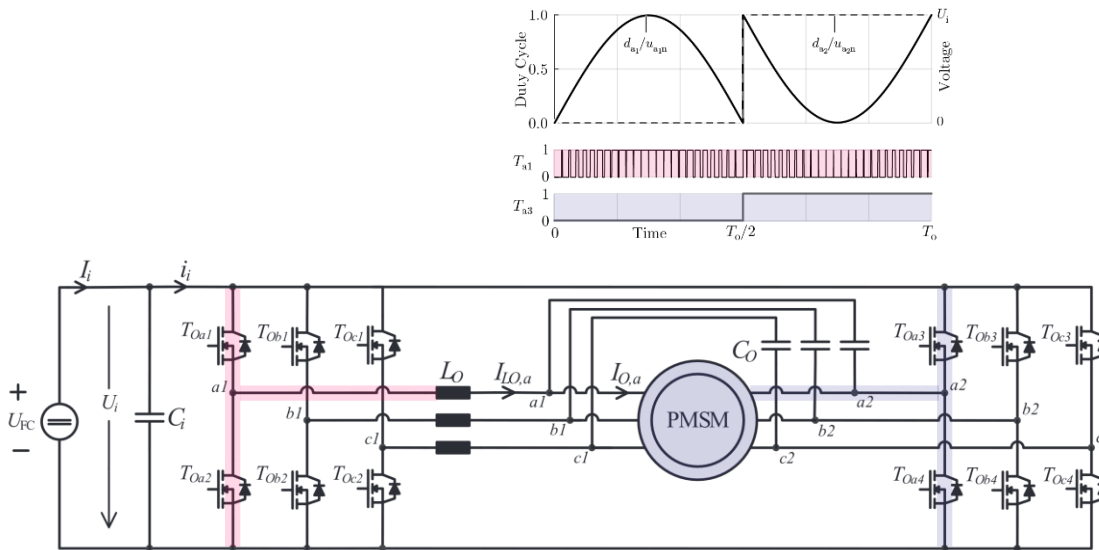

- *Integration → 2x System Power Density | 97% → 98.5% Inverter Efficiency*

Double-Bridge (DB)-Inverter Advantages

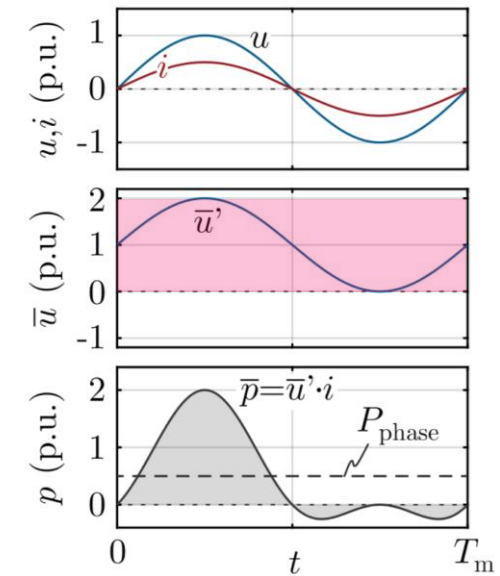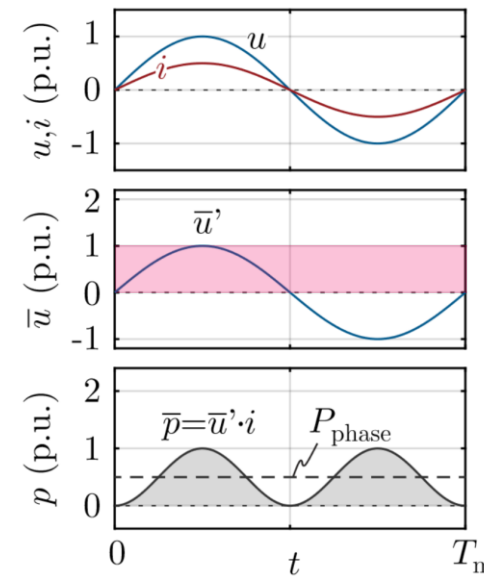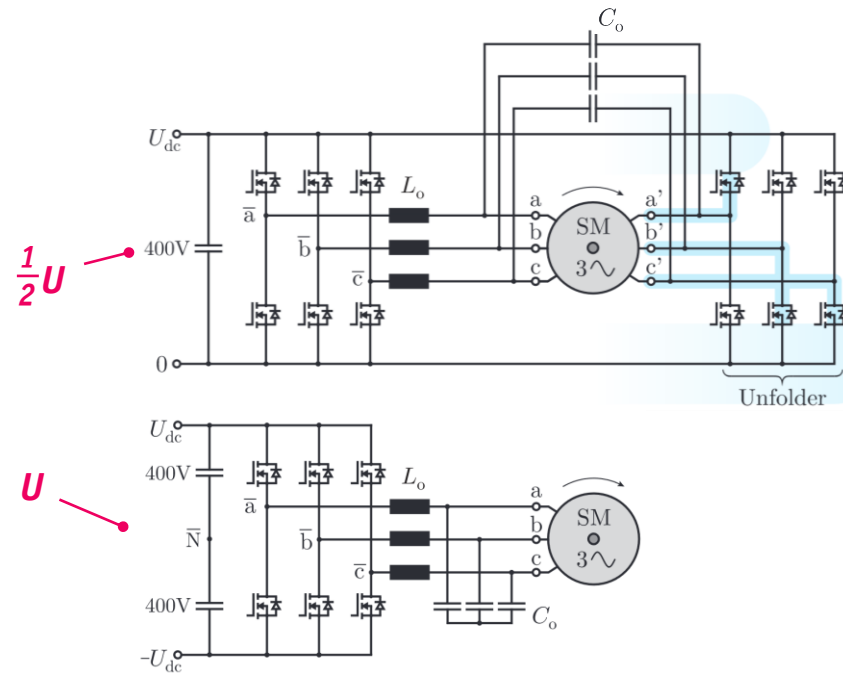- *Unfolder* → Factor 2 Lower DC-Link Voltage
- **Lower Transistor Voltage Stress / Lower Switching Losses**
- Conventional Inverter Bridge-Leg Processes 2x Instantaneous Peak Power






- Access to All Wdg. Terminals — No Problem for Inverter/Motor Integration

—— *Overload* | *Thermal Limit* ——


Remark GaN Overload Capability

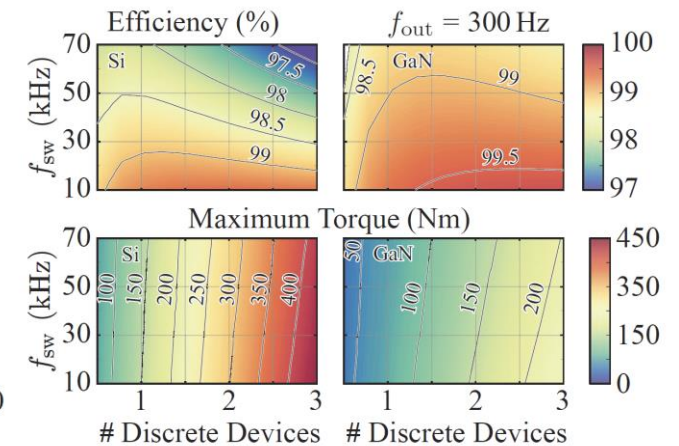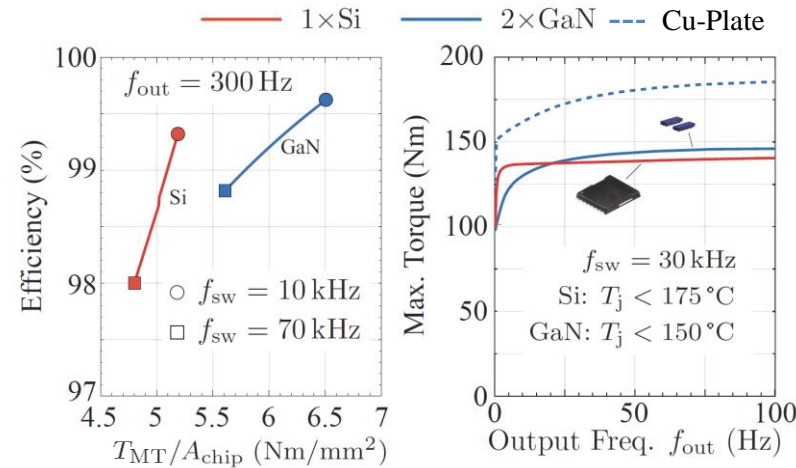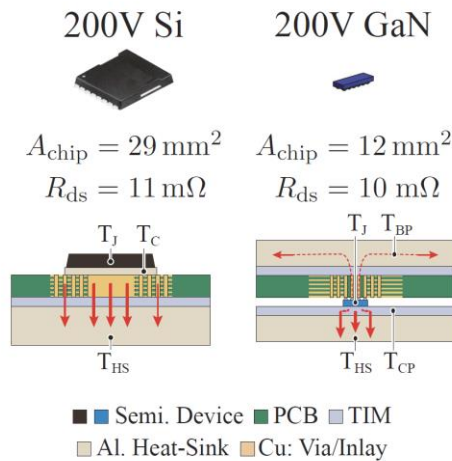- **Highly Dynamic Robotics VSDs** → **3x ... 5x Rated Torque for Seconds**
- **Smaller GaN Chip Area** → **Lower Thermal Time Constant**
- **Packaging Essentially Defines GaN Usability (!)**



- **200V GaN vs. Si (Multi-Level Inverter) Comparison**


**Buck-Boost
Y-Inverter**

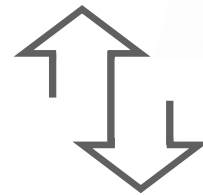

Motivation

■ General / Wide Applicability


- Adaption to Load-Dependent Battery | Fuel-Cell Supply Voltage
- VSDs → Wide Output Voltage / Speed Range

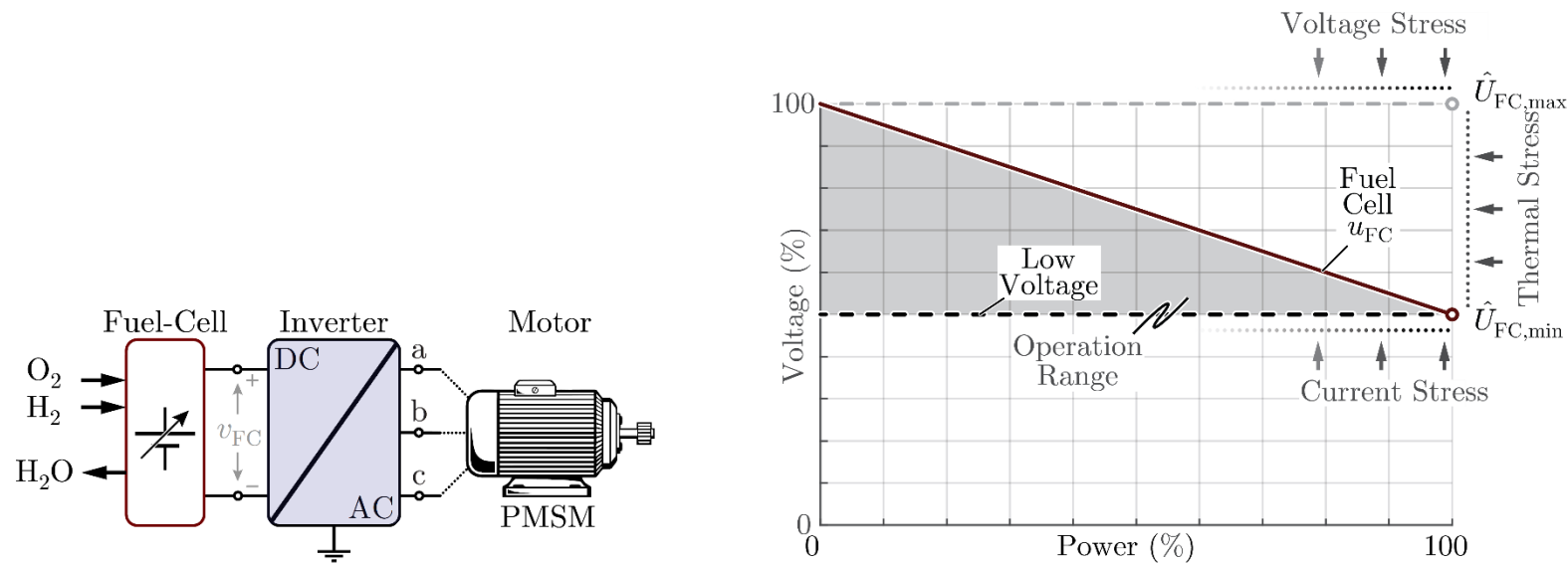

- No Additional Converter for Voltage Adaption → Single-Stage Energy Conversion

“Outside-the-Box” Topologies

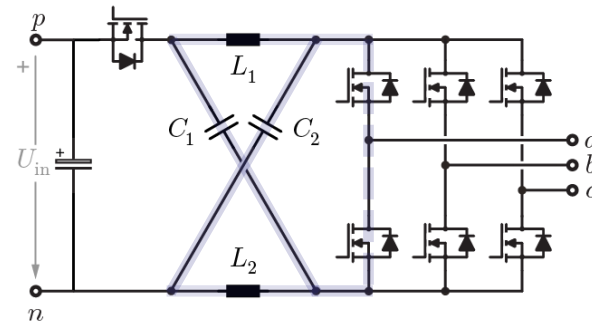
- **Z-Source Inverter** → Shoot-Through States Utilized for Boost Function
- **Higher Component Stress** Eff. Limits Boost Operation to $\approx 120\% U_{in}$



Source: F.Z. Peng / 2003
J. Rabkowski / 2007



- **3- Φ Back-End DC/AC Cuk-Converter**

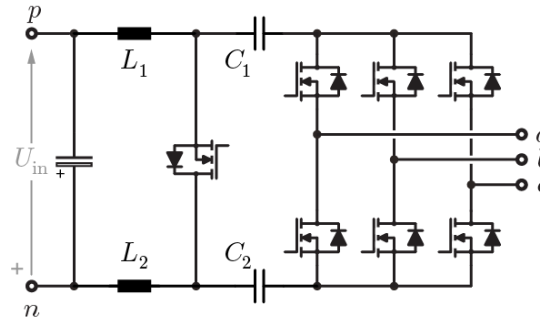


Source: T.A. Lipo
et al. / 2002 &
K.D.T Ngo / 1984

- **Integration Typ. Results in Higher Comp. Stresses & Complexity / Lower Performance**

Boost Converter DC-Link Voltage Adaption


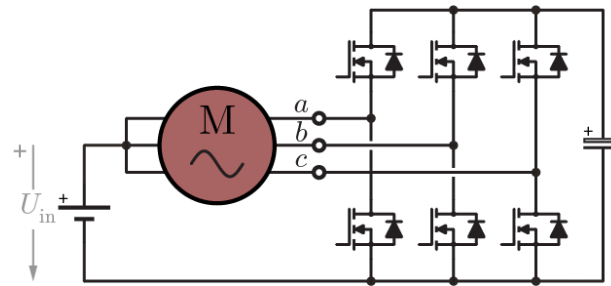
- *Inverter-Integr. DC/DC Boost Conv. → Higher DC-Link Voltage / Lower Motor Current*
- *Access to Motor Star-Point & Specific Motor Design Required*
- *No Add. Components*



Source: J. Pforr et al. / 2009

- *Explicit Front-End DC/DC Boost-Stage*

Source: www.rick-gerber.com

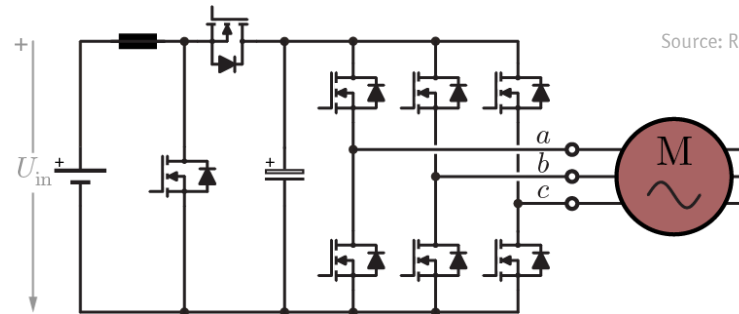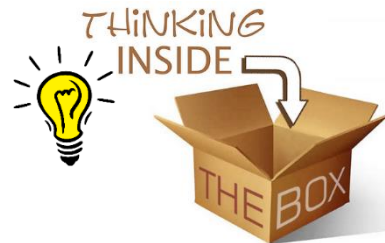


Source: R.W. Erickson et al. / 1986

→ *Coupling of the Control of Both Converter Stages → "Synergetic Control"*

Buck-Boost Y-Inverter

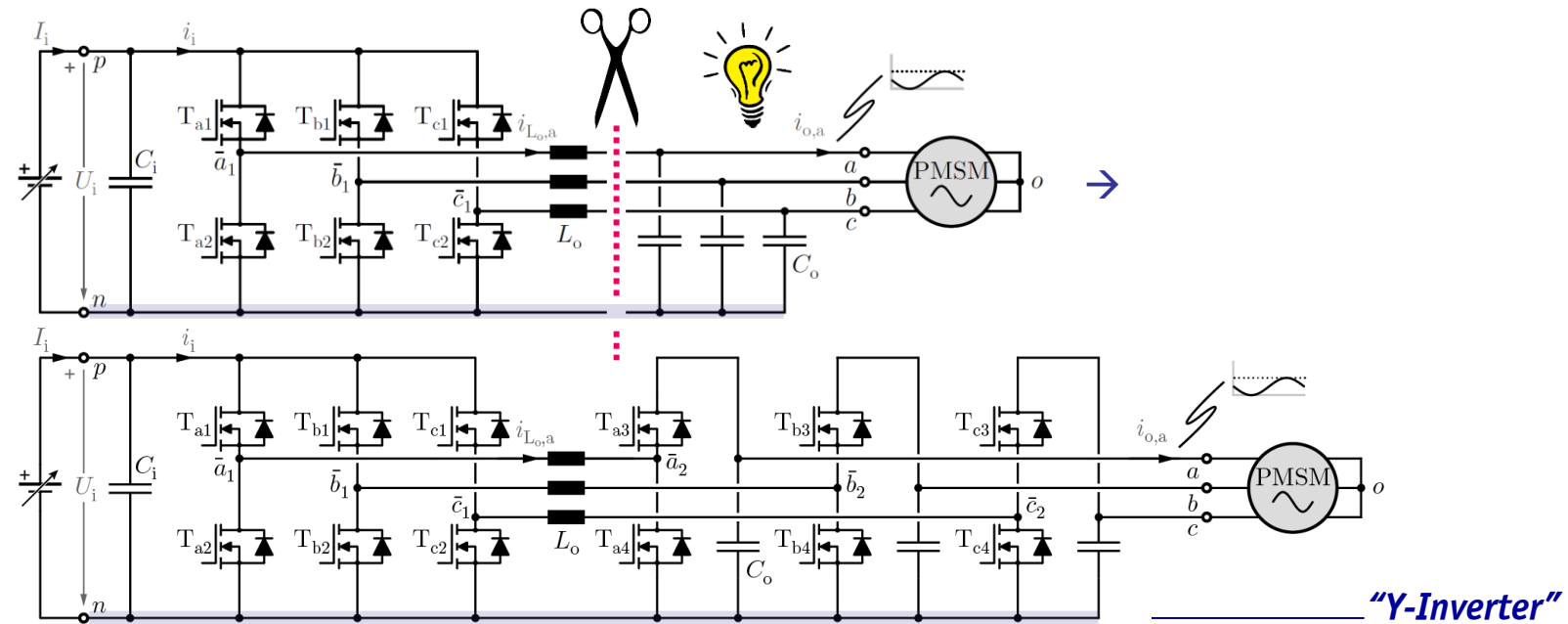
■ Generation of AC-Voltages Using Unipolar Bridge-Legs





- Switch-Mode Operation of **Buck OR Boost Stage** → **Single-Stage Energy Conversion (!)**
- 3- Φ Continuous Sinusoidal Output / Low EMI → **No Shielded Cables / No Motor Insul. Stress**

Sinusoidal Modulation

Y-Inverter

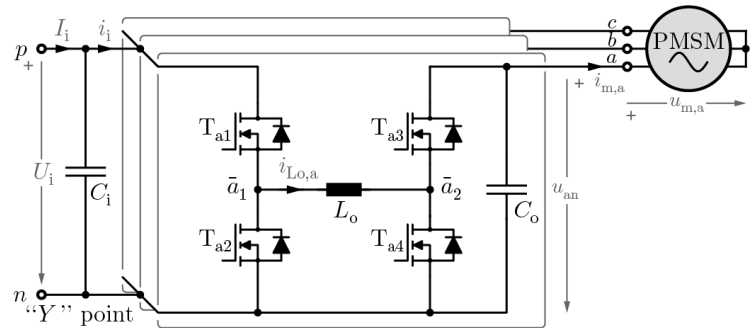


Motor Phase Voltages

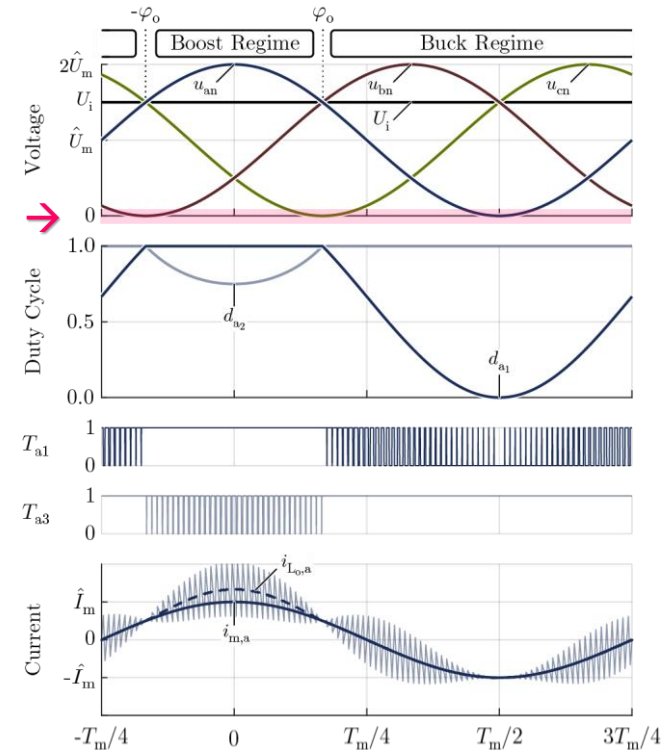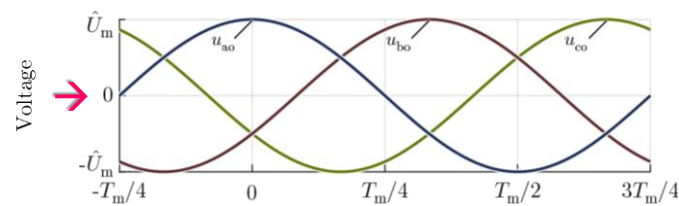



- **Const. DC Offset** → **Strictly Positive Output Voltages** u_{an} , u_{bn} , u_{cn}
- **Mutually Exclusive Operation of the Half-Bridges** → **Low Switching Losses**

Boost-Operation $u_{an} > U_i$

■ Phase-Module

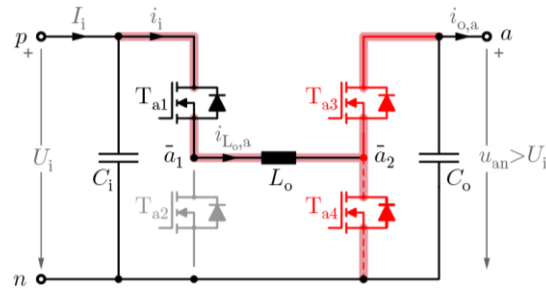


■ Motor Phase Voltages

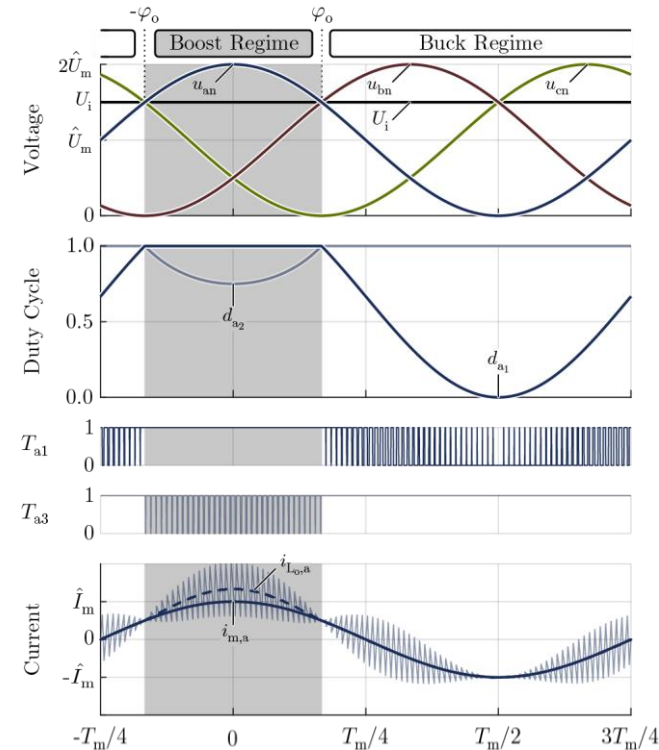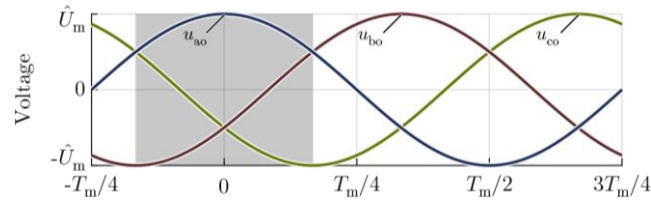



- **Current-Source-Type Operation**
- **Clamping of Buck-Bridge High-Side Switch → Quasi Single-Stage Energy Conversion**

Buck-Operation $u_{an} < U_i$

■ Phase-Module

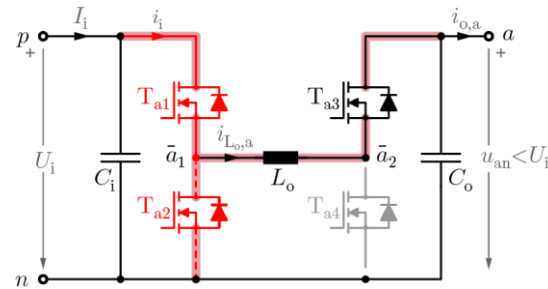

■ Motor Phase Voltages

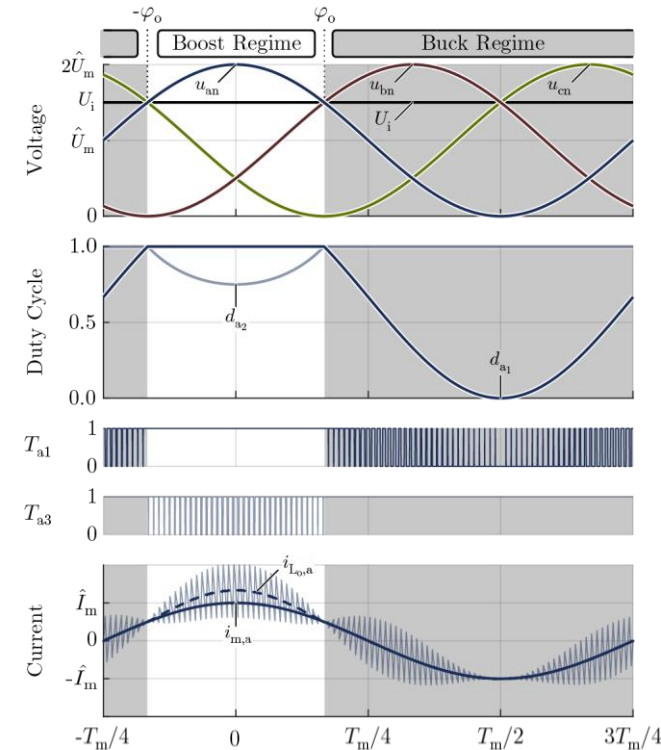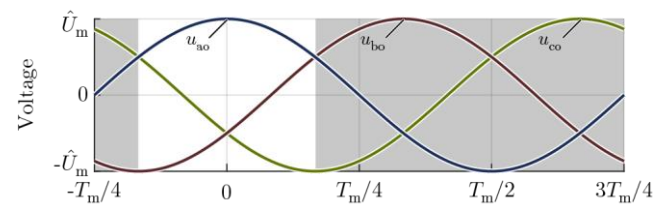


- **Voltage-Source-Type Operation**
- **Clamping of Boost-Bridge High-Side Switch → Quasi Single-Stage Energy Conversion**



Discontinuous Modulation



Y-Inverter

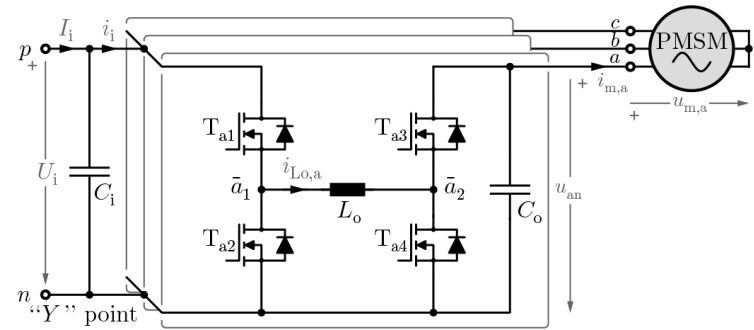


Motor Phase Voltages

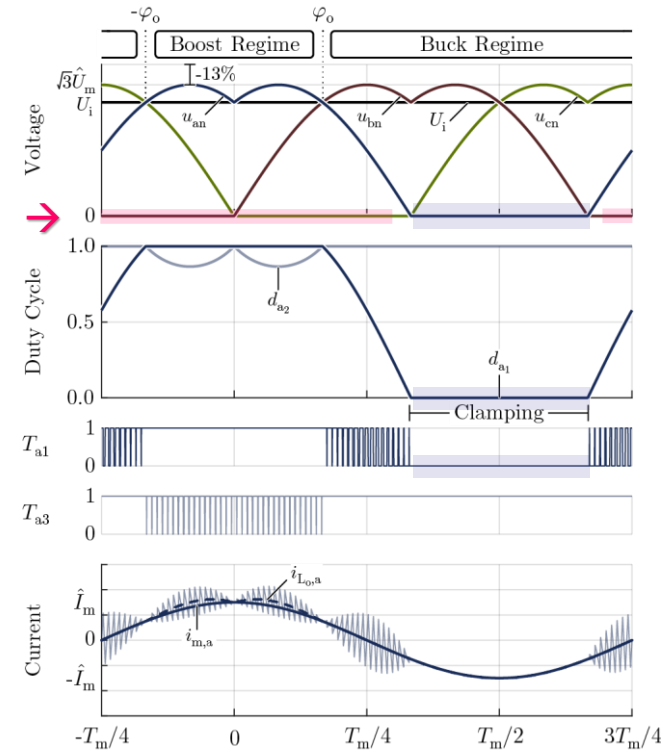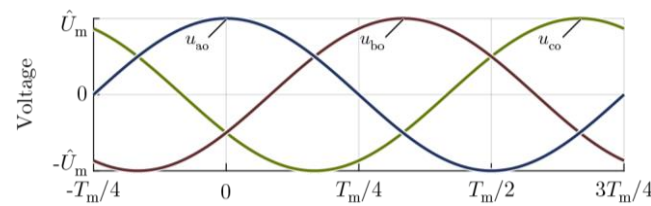

- **Clamping of Each Phase for 1/3 of the Fund. Period → Low Switching Losses (!)**
- **Non-Sinusoidal Module Output Voltages / Sinusoidal Line-to-Line Voltages**

Control Structure

- Motor Speed Control



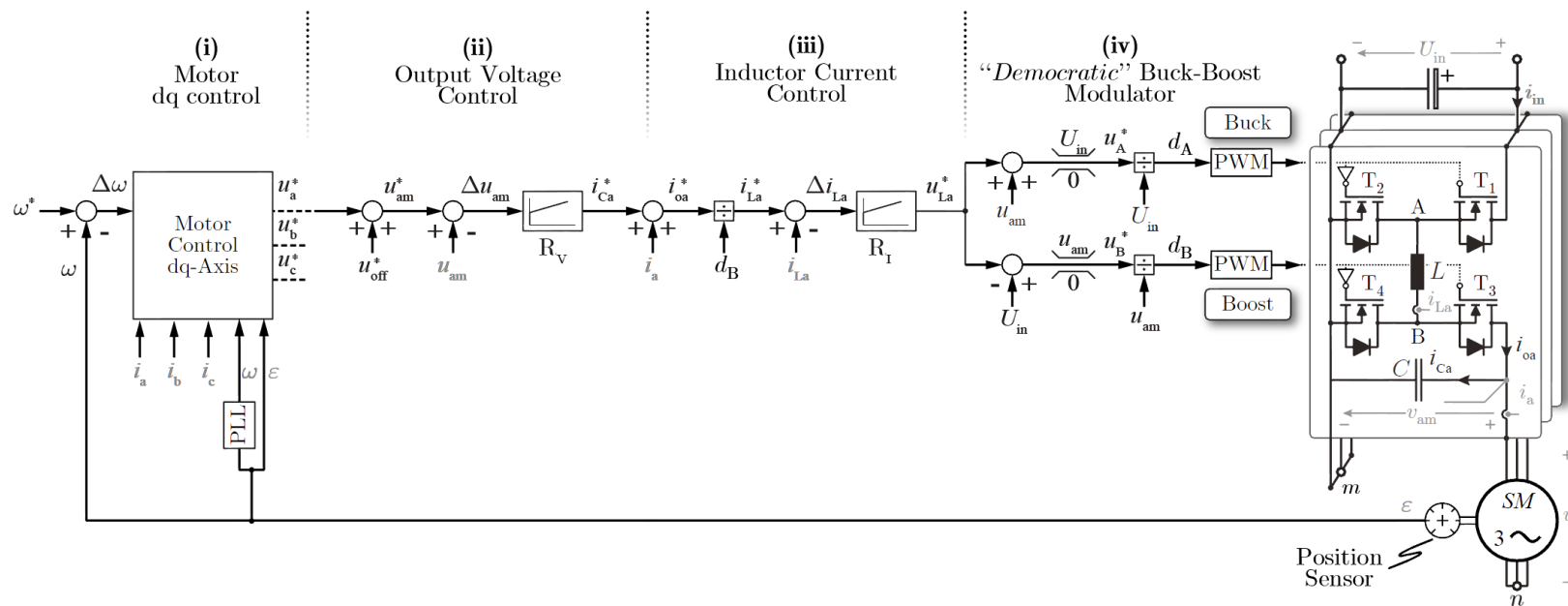


- Cascaded Current / Voltage / Current Control Loops
- Seamless Transition between Boost- & Buck-Mode → "Democratic" Control

Y-Inverter VSD

■ Demonstrator Specifications

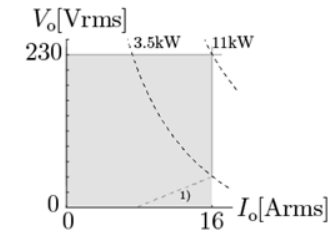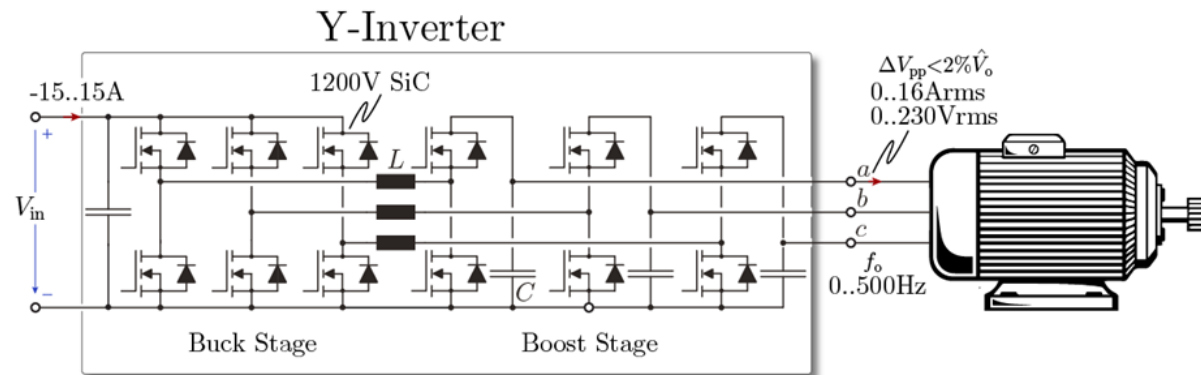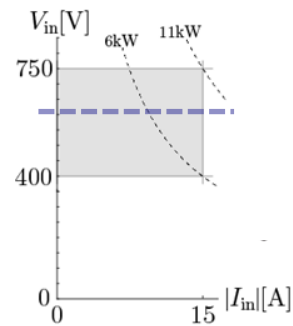
- Wide DC Input Voltage Range → **400...750V_{DC}**
- Max. Input Current → **± 15A**



- Max. Output Power → **6...11 kW**
- Output Frequency Range → **0...500Hz**
- Output Voltage Ripple → **3.2V Peak @ Output of Add. LC-Filter**

Y-Inverter Demonstrator

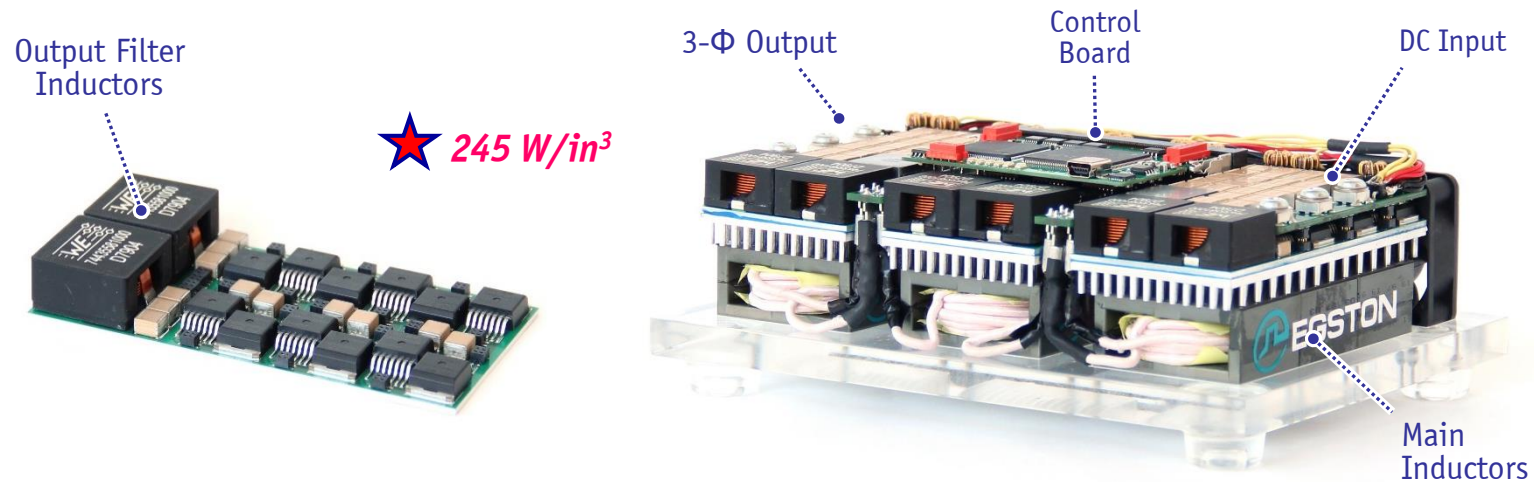- DC Voltage Range **400...750V_{DC}**
- Max. Input Current **± 15A**
- Output Voltage **0...230V_{rms} (Phase)**
- Output Frequency **0...500Hz**
- Sw. Frequency **100kHz**
- **3x SiC (75mΩ)/1200V per Switch**
- **IMS** Carrying Buck/Boost-Stage Transistors & Comm. Caps & 2nd Filter Ind.




- **Dimensions** → 160 x 110 x 42 mm³

Y-Inverter - Measurement Results


Stationary Operation

$U_{DC} = 400V$
 $U_{AC} = 400V_{rms}$ (Motor Line-to-Line Voltage)
 $f_0 = 50Hz$
 $f_{sw} = 100kHz$ / Discontinuous PWM
 $P = 6.5kW$

100V/div
10A/div

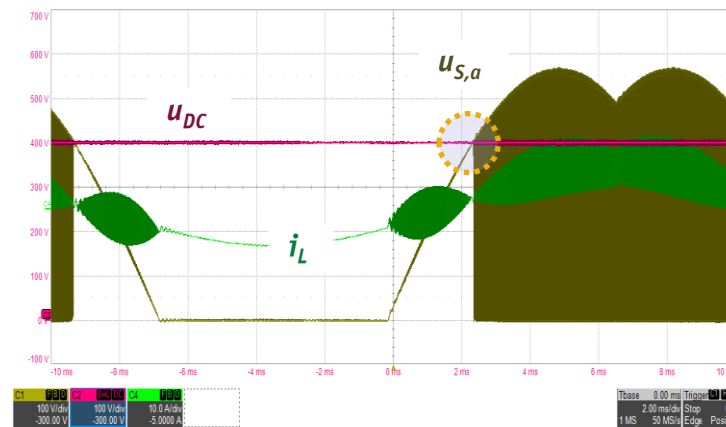

200V/div
1V/div


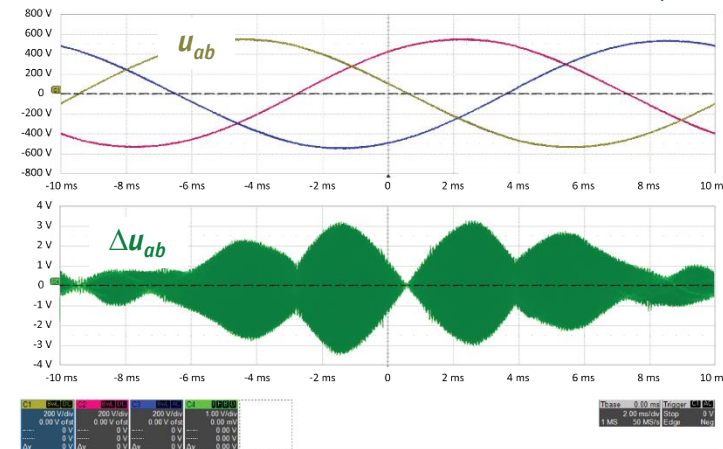


- Line-to-Line Output Voltage Ripple < 3.2V

Efficiency Measurements

- Dependency on **Input Voltage** & **Output Power Level**

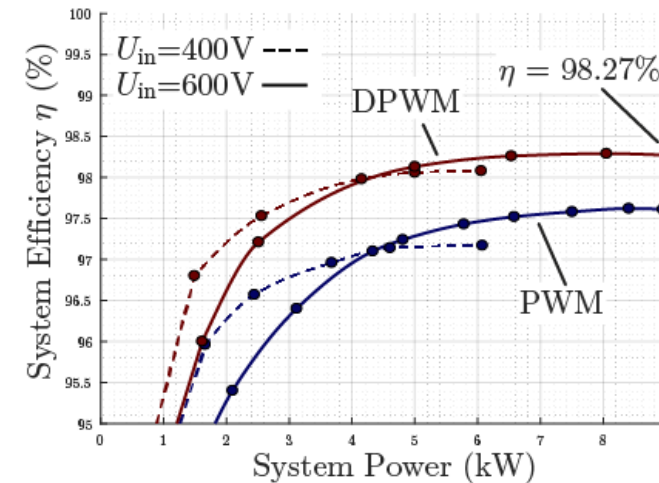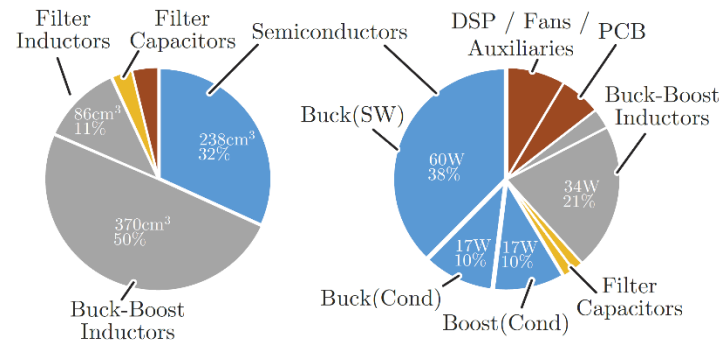
$$\begin{aligned} U_{DC} &= 400\text{V} / 600\text{V} \\ U_{AC} &= 230\text{V}_{\text{rms}} \text{ (Motor Phase-Voltage)} \\ f_{sw} &= 100\text{kHz} \end{aligned}$$



→ **Multi-Level Bridge-Leg Structure** for Increase of Power Density @ Same Efficiency

EMI-Limits (VSD Product Standard)



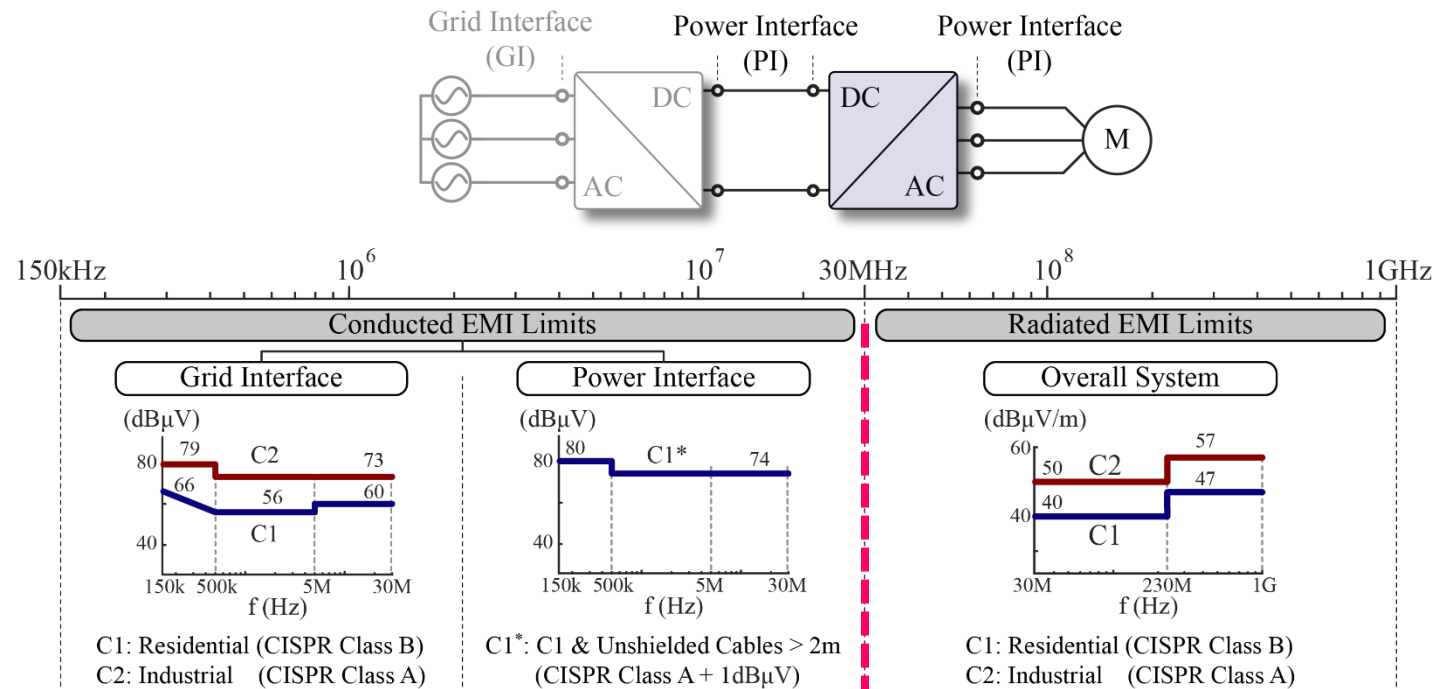
- IEC 61800-3 → Product Standard for Variable-Speed Motor Drives
- EMI Emission Limits → Grid Interface (GI) and Power Interfaces (PI)
- Application → Residential (C1) or Industrial (C2)



- EMI-Filter Design for Unshielded Cables > 2m and Resid. Applications (Cond. & Rad.)

Conducted EMI-Filter

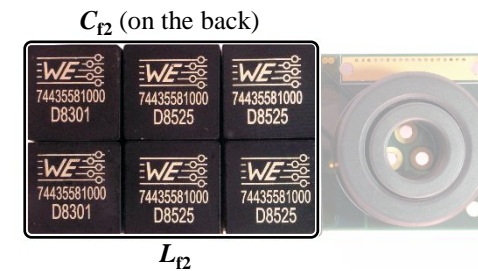
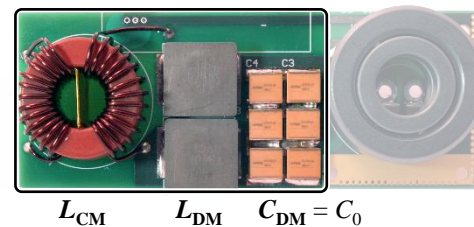
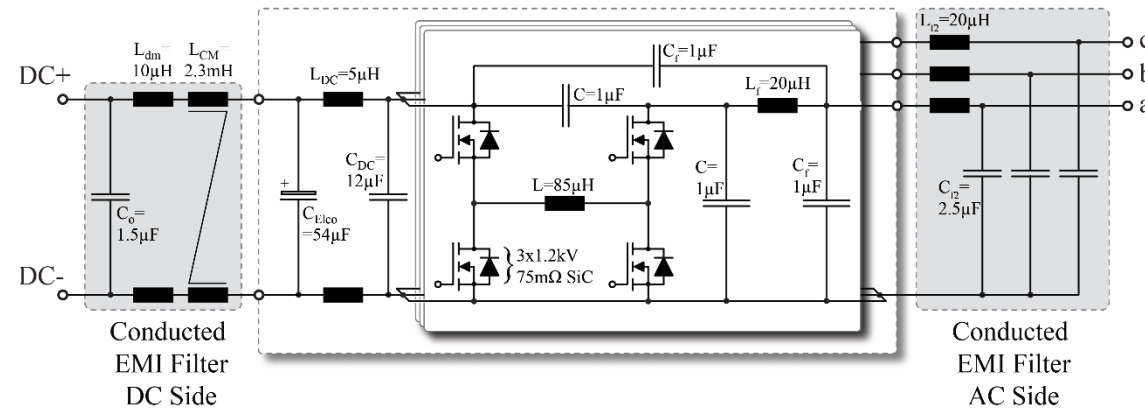
- Separate Cond. DM & CM EMI-Filter on DC-Side & DC-Minus Ref. EMI-Filter on AC-Side



- Low Add. EMI Filter Volume — $74cm^3$ for Each Filter (incl. Toroid. Radiated EMI Filter)
- Total Power Density Reduces — $15kW/dm^3$ ($740cm^3$) → $12kW/dm^3$ ($890cm^3$)

Conducted EMI - Experimental Results

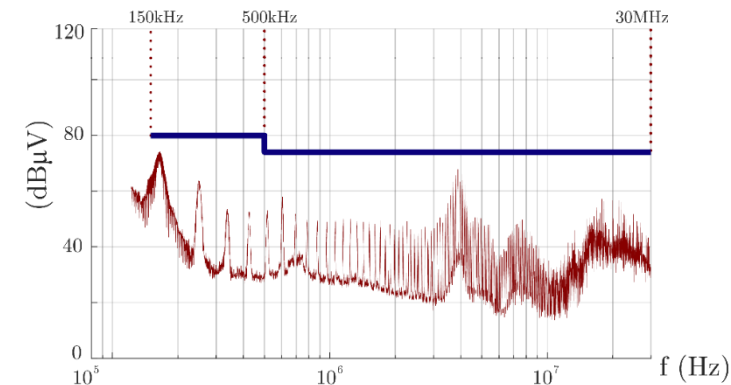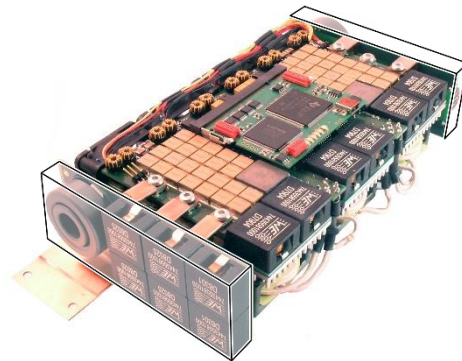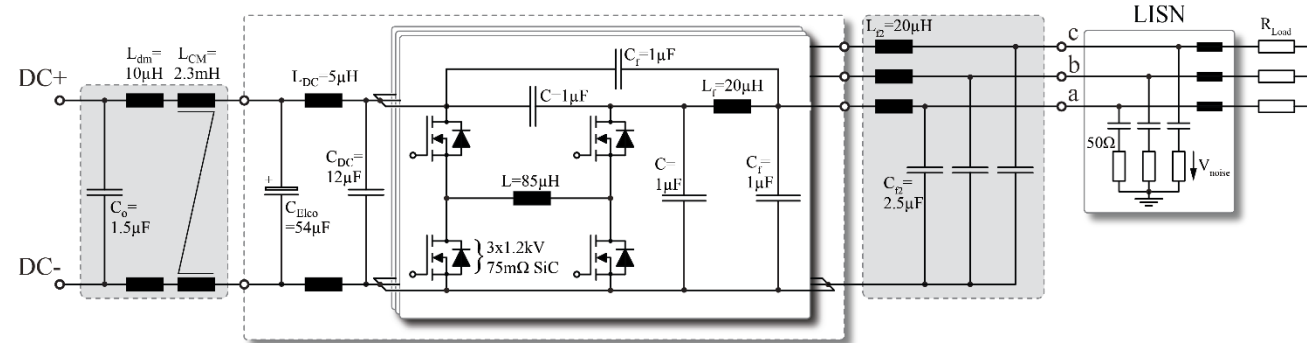
- Measurements of the Cond. EMI Noise on the AC-Side (QP, with 50Hz AC-LISN)



- Small 80uH CM-Ind. Added on AC-Side - (3cm³ of Add. Volume = 0.5% of Converter Vol.)
- Conducted EMI with Unshielded Motor Cable Fulfilled

Measurement of Radiated EMI-Noise (1)

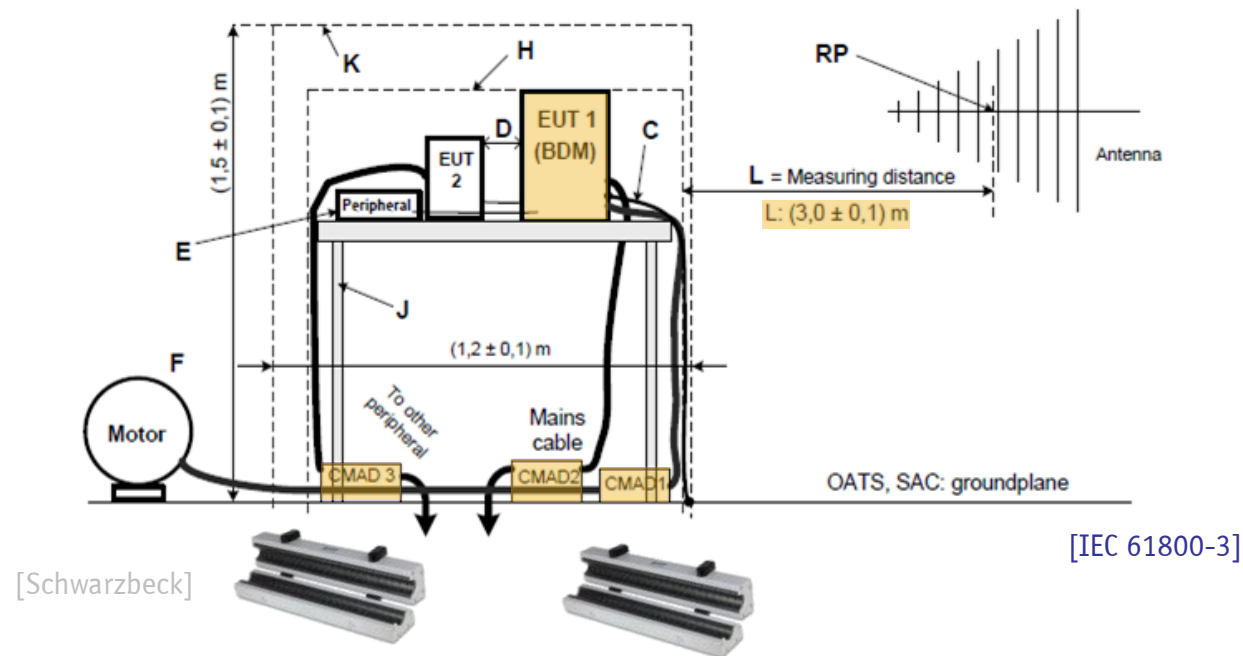
- Equipment Under Test (EUT) Placed on **Wooden Table with Specified Arrangement**
- **CM Absorption Devices (CMAD)** Terminate All Cables on AC-Side & DC-Side (Total $l_{\text{cable}} \approx 1.5\text{m}$)
- Measurement of Radiated Noise with **Antenna** in **3m Distance**



- **Either Open-Area Test Site (OATS) or Special Semi-Anechoic Chamber (SAC) Needed**
- **Alternative Pre-Compliance Measurement Method**

Measurement of Radiated EMI-Noise (2)

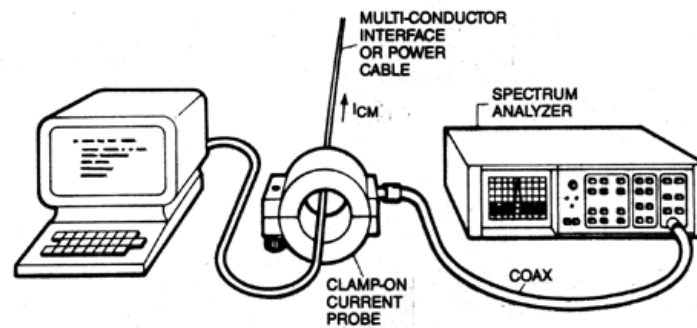
- **CM-Currents NOT Returning IN THE CABLE** are Dominant Source of Radiation
- Relation Between Radiated **Electric Field** and **CM-Currents (!)**



$$E = \begin{cases} \frac{\mu_0 \cdot f \cdot l_{cable} \cdot I_{cm}}{r} & \frac{\lambda}{4} \leq l_{cable} \\ \frac{\mu_0 \cdot \frac{c_0}{4} \cdot I_{cm}}{r} & \frac{\lambda}{4} > l_{cable} \end{cases}$$

[Electromagnetic Compatibility Engineering, H. Ott]

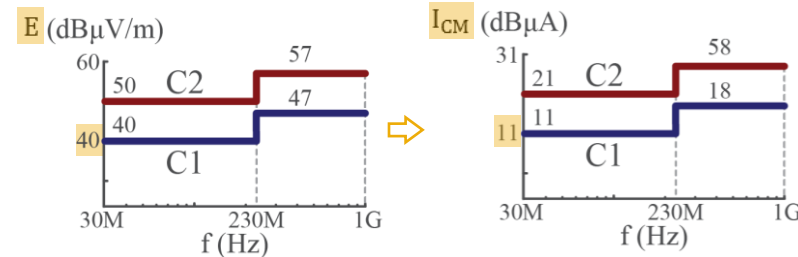[Fischer FCC F-33-1]
up to 250MHz
 $Z_{nom} = 6.3\Omega$




C1: Residential (CISPR Class B)
C2: Industrial (CISPR Class A)

- **Max. Allow. El. Field Strength of 40dBuV/m** → **Max. CM-Current of 3.5uA (11dBuA)**
- **Current Probe Impedance of 6.3Ω (F-33-1)** → **Max. Noise Volt. of 26dBuV @ Test Receiver**

Radiated EMI-Filter Design


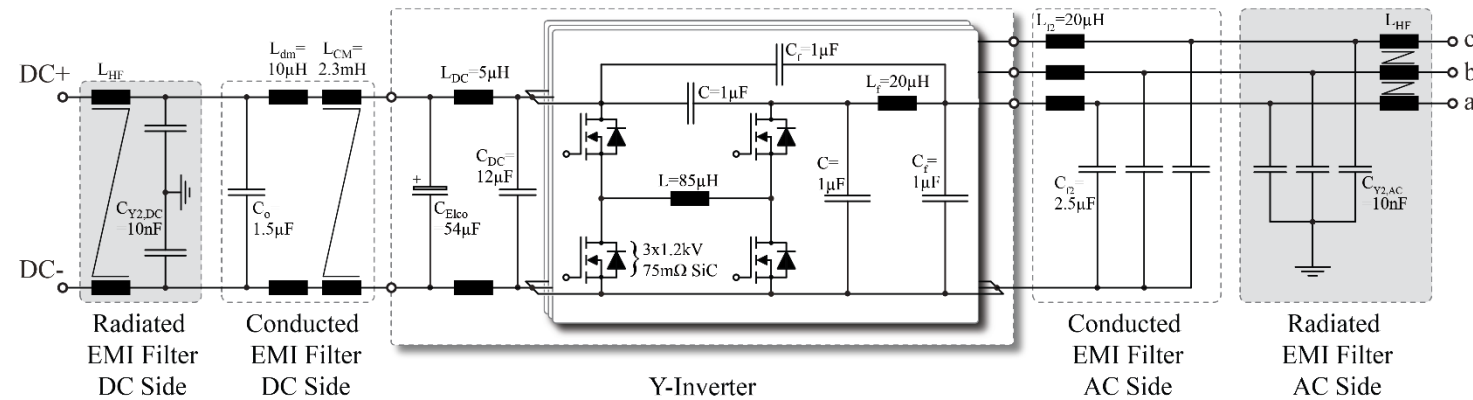
- Single-Stage HF CM-Filter on DC-Side and AC-Side
- Plug-On CM-Cores (NiZn-Ferrites) → Low Parasitics & Good HF-Att. up to 1GHz



- Additional EMI Filter Volume Already Considered with Conducted EMI Filter
- Total Power Density Slightly Reduces — $15kW/dm^3 \rightarrow 12kW/dm^3$


Experimental Results - Radiated EMI

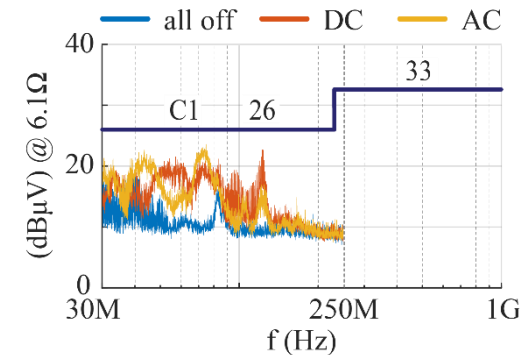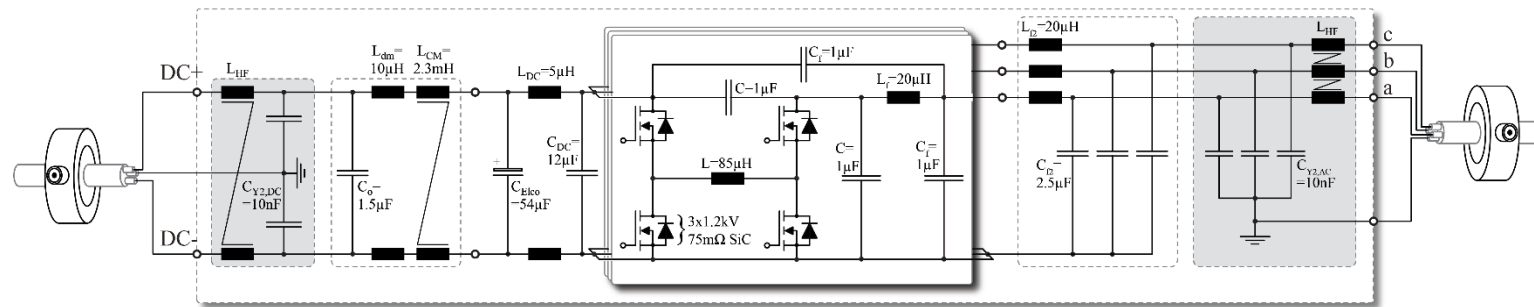- Y-Inverter Placed in Metallic Enclosure → Emulate Housing, but UNshielded Cables (!)
- Measurement Setup → According IEC 61800-3
- Alternative Measurement Principle → Conducted CM-Current Instead of Radiation




- Already Noticeable Noise Floor
- HF-Emissions Well Below Equivalent EMI-Limit → Final Step: Verification Using Antenna

***Buck-Boost
Current Source Inverter***

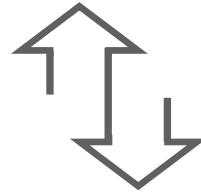

3- Φ Current Source Inverter Topology Derivation


- *Y-Inverter* \rightarrow *Phase Modules w/ Buck-Stage | Current Link | Boost-Stage*
- *3- Φ CSI* \rightarrow *Buck-Stage V-I-Converter | Current DC-Link DC/AC-Stage*

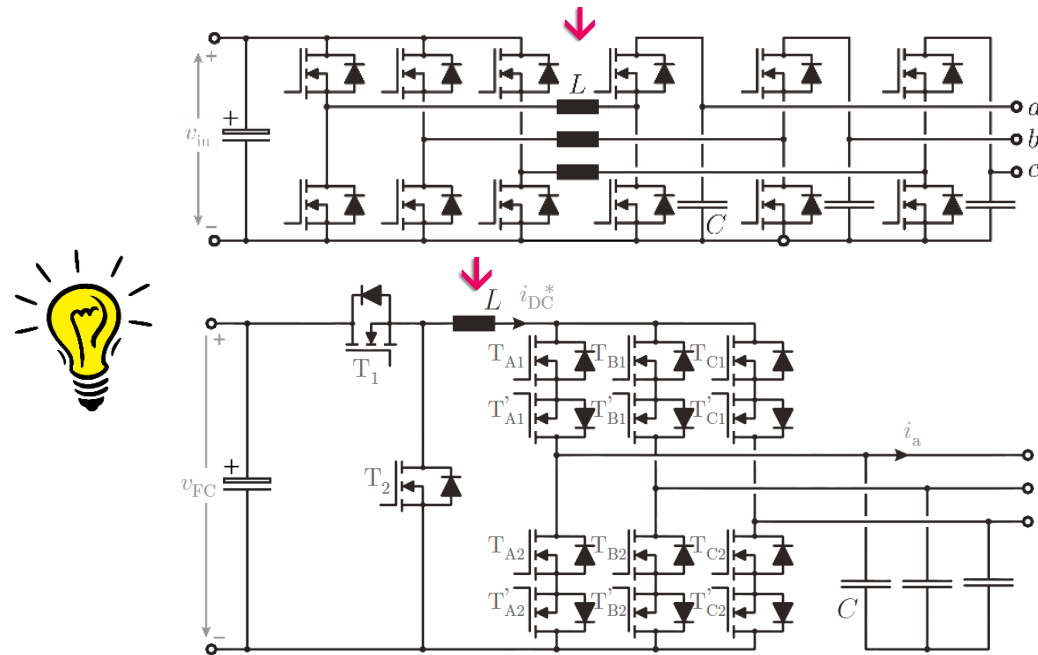

\rightarrow *Single Inductive Component & Utilization of Monolithic Bidirectional GaN Switches*

3- Φ Current Source Inverter (CSI)


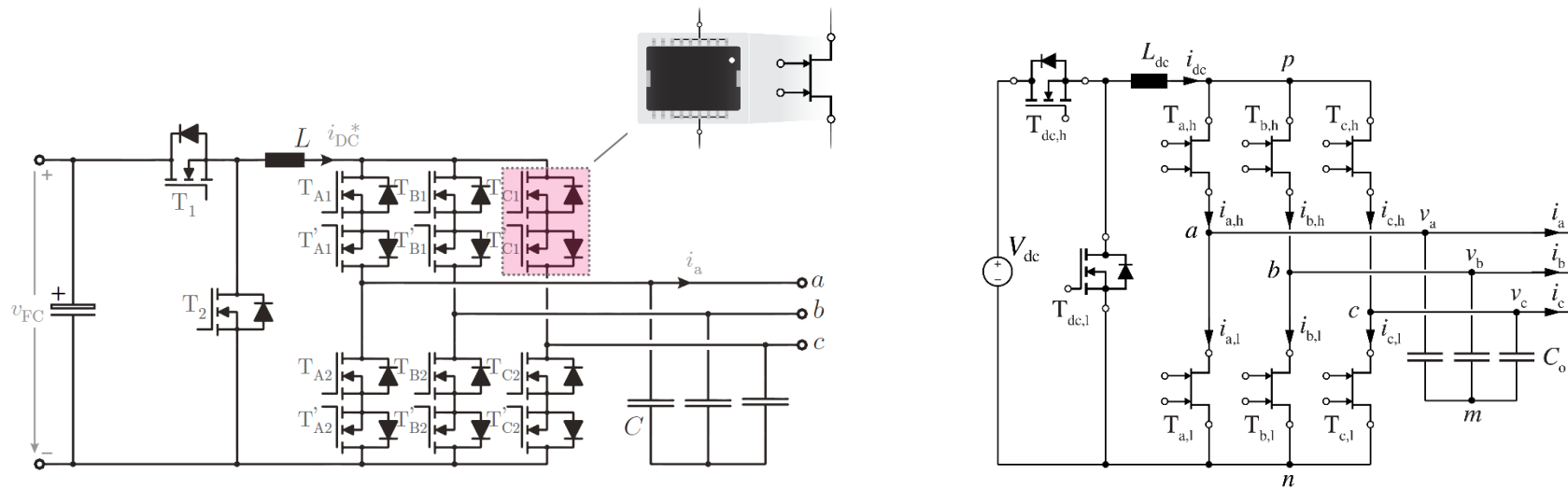
- *Bidirectional/Bipolar Switches* → *Positive DC-Side Voltage for Both Directions of Power Flow*



- *Monolithic Bidir. GaN Switches* → *Factor 4 (!) Reduction of Chip Area Comp. to Discrete Realization*

3- Φ Buck-Boost CSI (1)

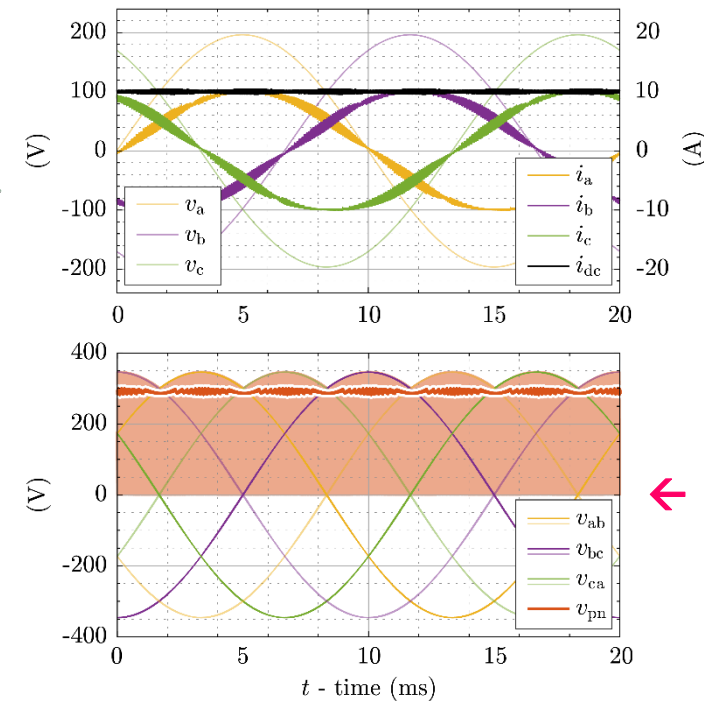
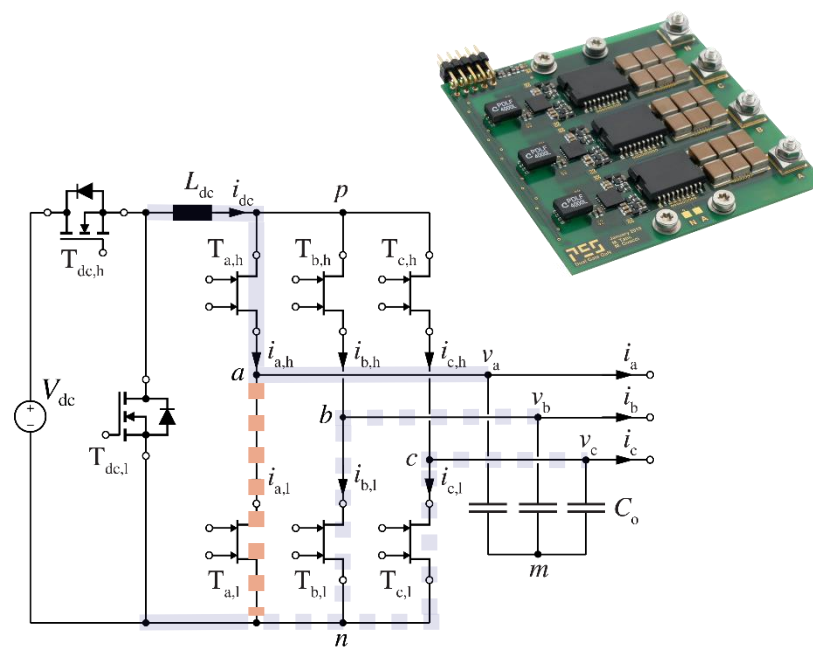
- *Monolithic Bidir. Bipolar GaN Switches Featuring 2 Gates* → Full Controllability
- *Buck-Stage for Impressing Const. DC Current / PWM of CSI for Output Voltage Control*



- *Conventional Control of Inverter Stage* → Switching of All 3 Phase Legs (3/3)

3- Φ Buck-Boost CSI (2)

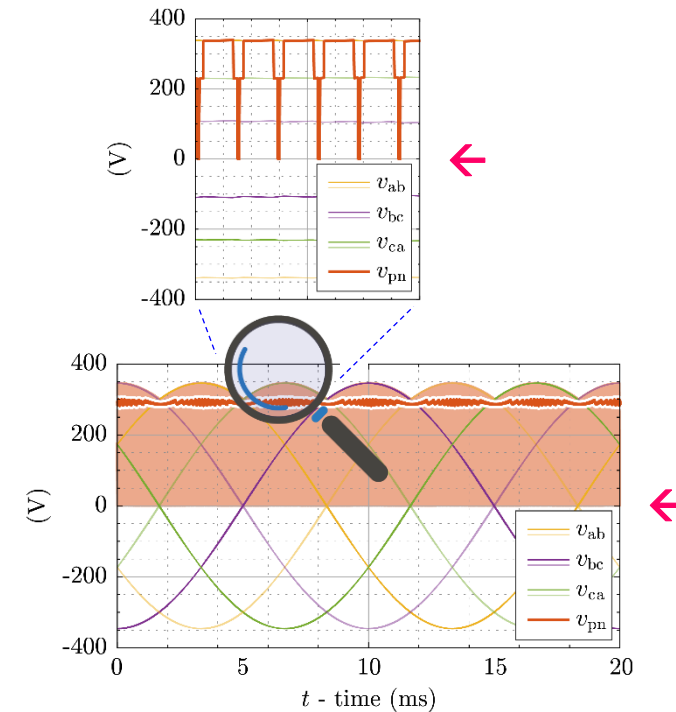
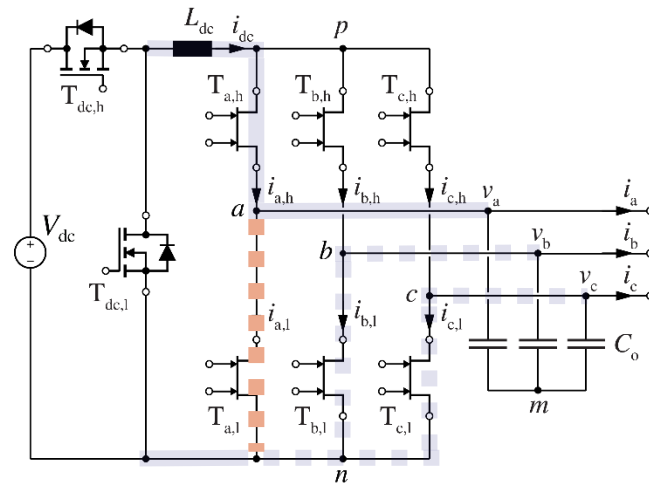
- *Monolithic Bidir. Bipolar GaN Switches Featuring 2 Gates* → Full Controllability
- *Buck-Stage for Impressing Const. DC Current / PWM of CSI for Output Voltage Control*



- *Conventional Control of Inverter Stage* → Rel. High CSI-Stage Sw. Losses

3- Φ Buck-Boost CSI (3)

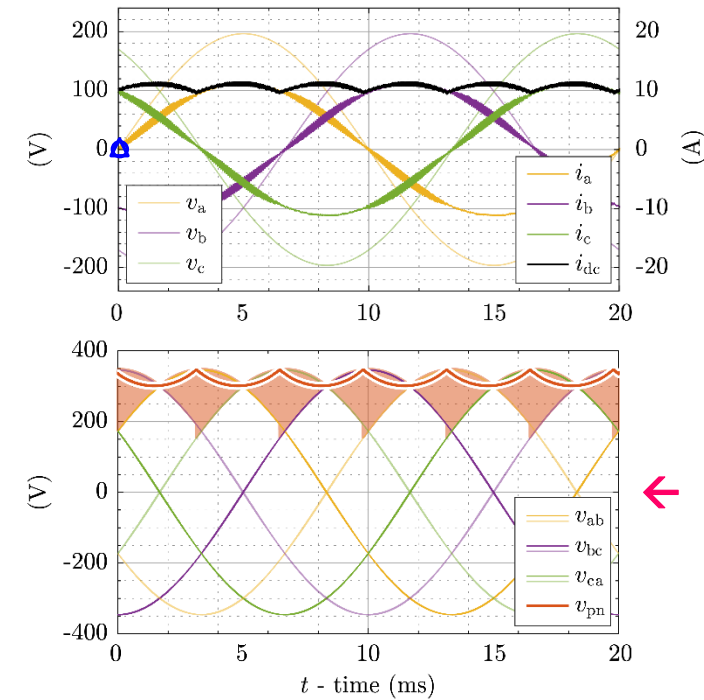
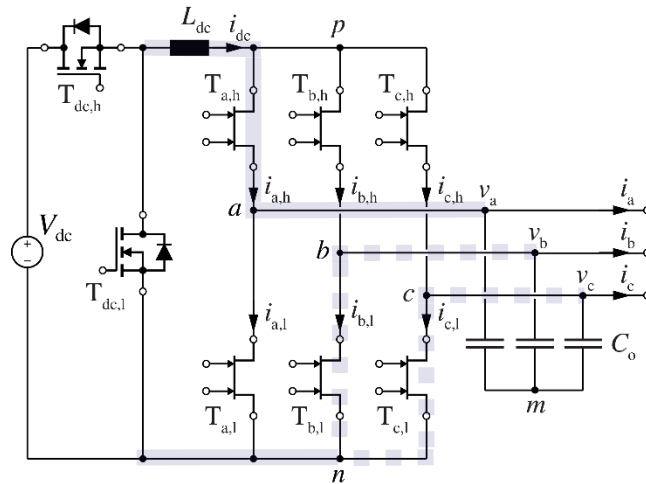
- “Synergetic” Control of Buck-Stage & CSI Stage
- 6-Pulse-Shaping of DC Current by Buck-Stage → Allows Clamping of a CSI-Phase



- Switching of Only 2 of 3 Phase Legs (2/3 Mode) → Significant Reduction of Sw. Losses

3- Φ Buck-Boost CSI (4)

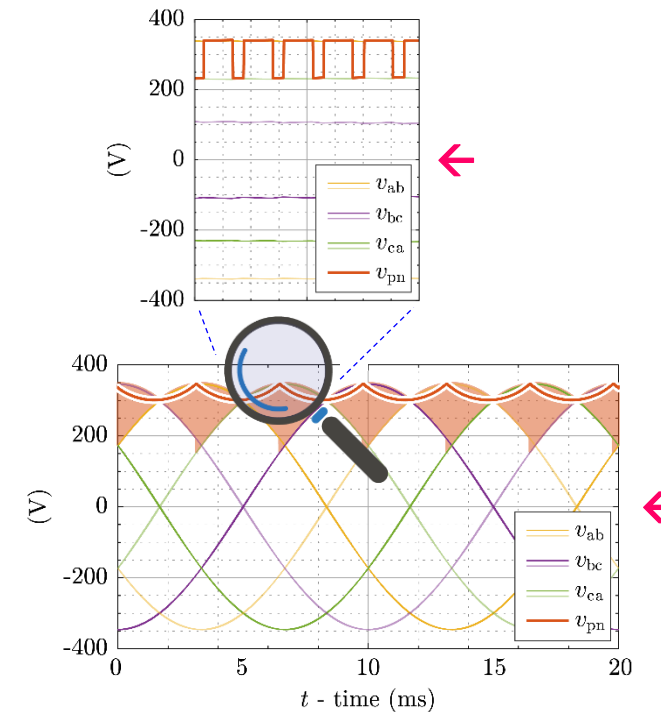
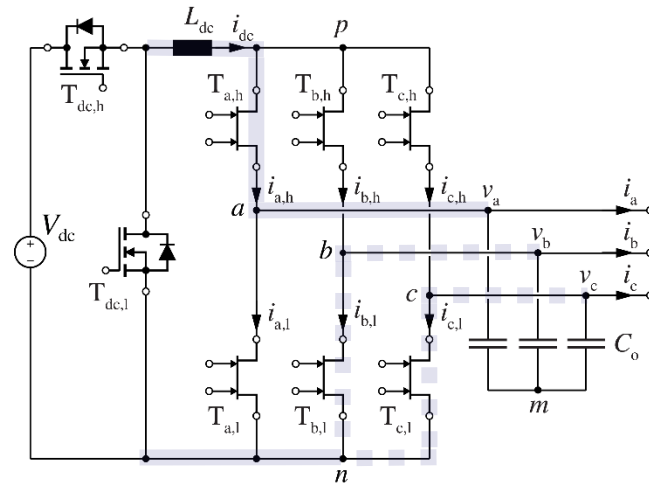
- “Synergetic” Control of Buck-Stage & CSI Stage
- 6-Pulse-Shaping of DC Current by Buck-Stage \rightarrow Allows Clamping of a CSI-Phase



- Switching of Only 2 of 3 Phase Legs \rightarrow Significant Red. of Sw. Losses (\approx -86% for R-Load)

3- Φ Buck-Boost CSI (5)

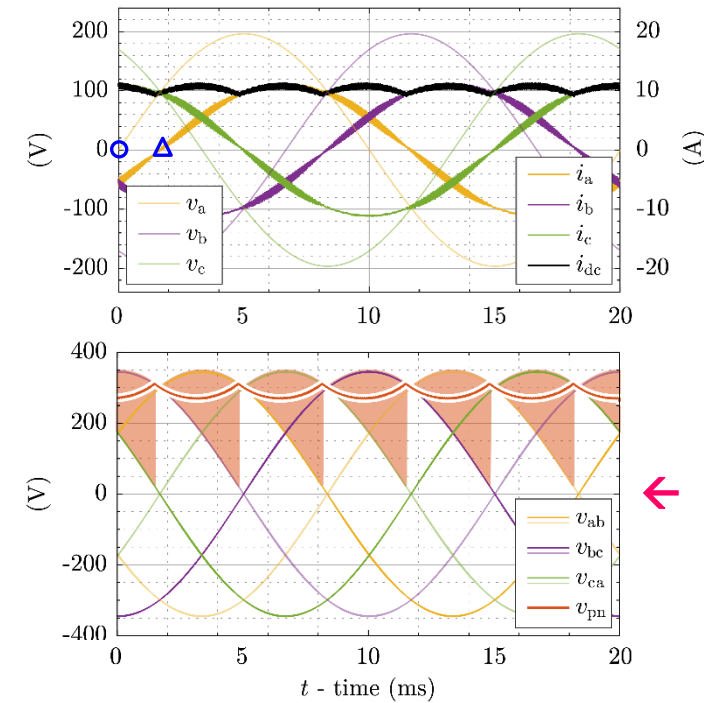
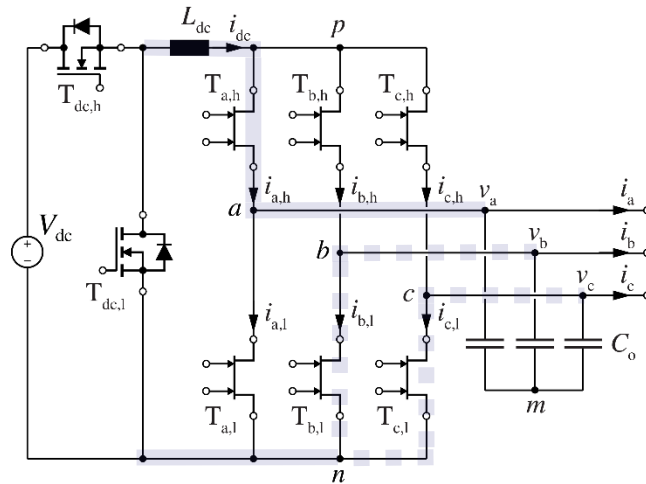
- “Synergetic” Control of Buck-Stage & CSI Stage
- 6-Pulse-Shaping of DC Current by Buck-Stage \rightarrow Allows Clamping of a CSI-Phase



- Operation for 30° Phase Shift of AC-Side Voltage & Current

3- Φ Buck-Boost CSI (6)

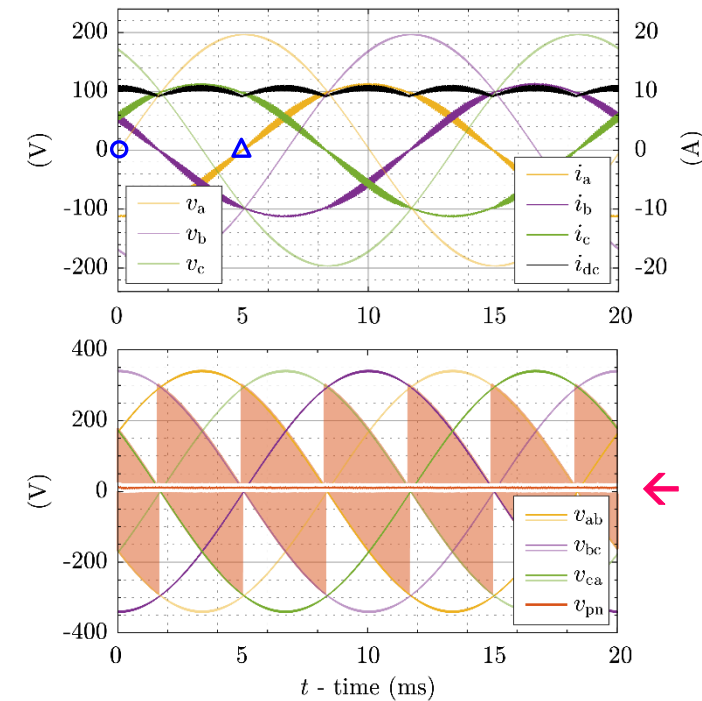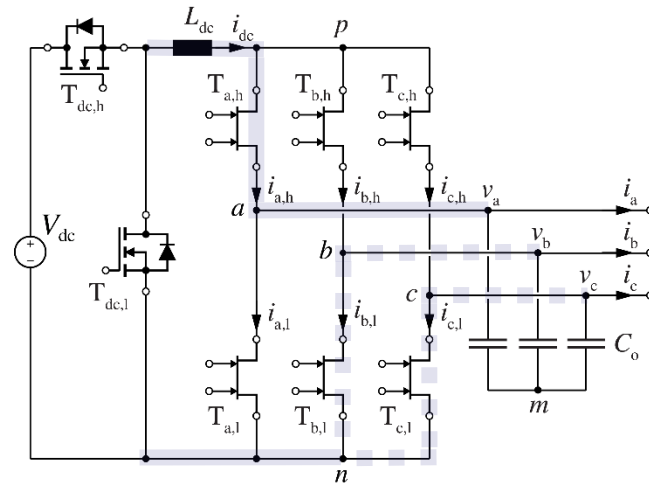
- “Synergetic” Control of Buck-Stage & CSI Stage
- 6-Pulse-Shaping of DC Current by Buck-Stage \rightarrow Allows Clamping of a CSI-Phase



- Operation for 90° Phase Shift ($\pm 90^\circ$ — Limit Case for Buck-Stage Current Control)


3- Φ Buck-Boost CSI (7)

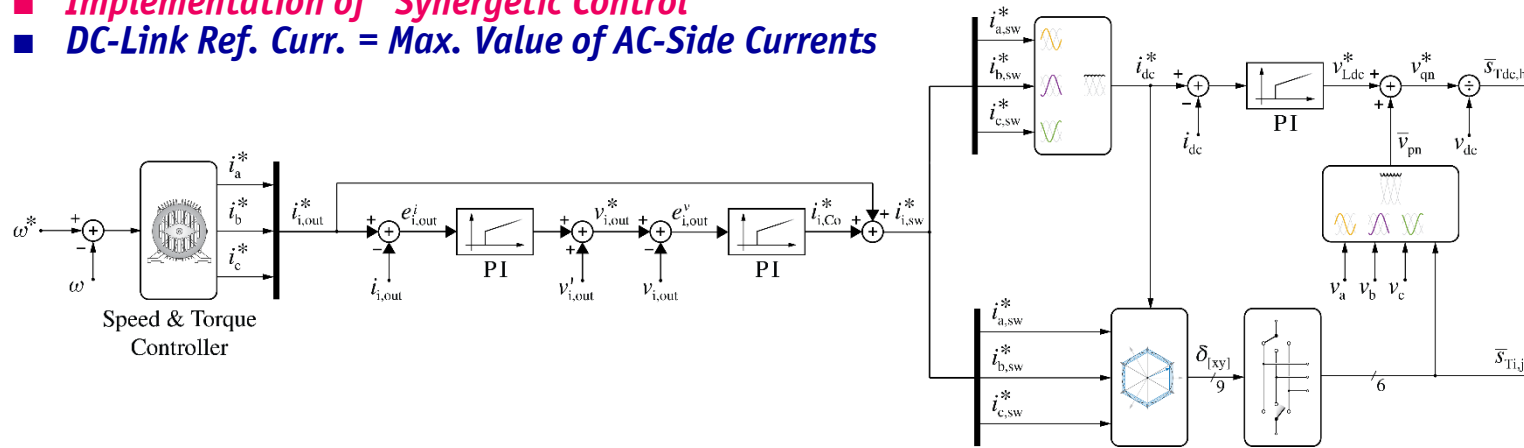- *Implementation of “Synergetic Control”*
- *DC-Link Ref. Curr. = Max. Value of AC-Side Currents*



3/3 Mod. ($i_{DC} = \text{const.}$) \rightarrow
 2/3 Mod. (6-Pulse i_{DC}) \rightarrow
 Partial 2/3 Mod. \rightarrow
 Full-Boost Operation

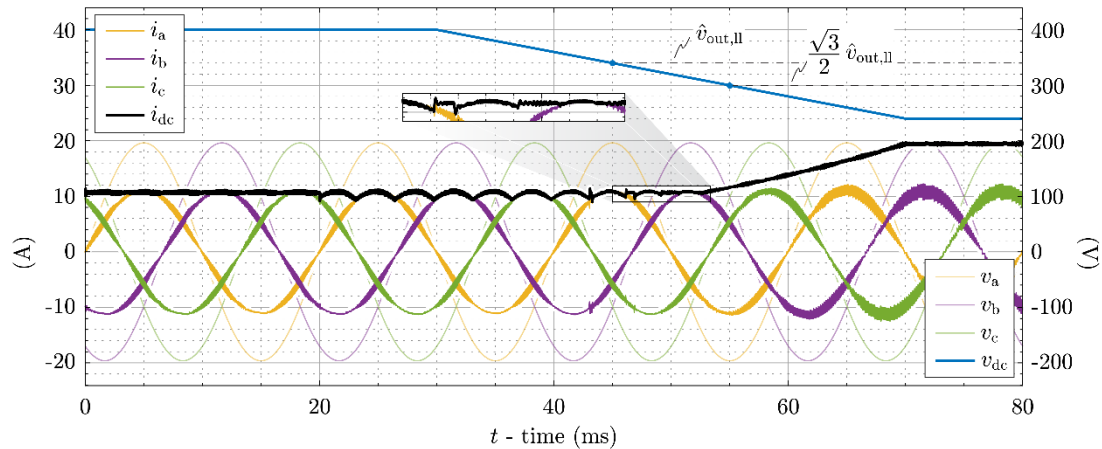
- *Seamless Transition from Buck to Boost Operation*



3- Φ DC-Link AC/AC Converter Topologies

■ Current DC-Link Topology

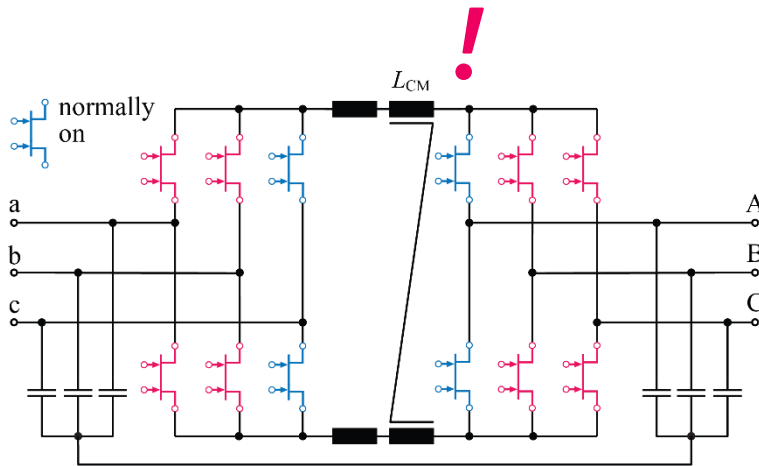
- Application of *M-BDSs*
- Complex 4-Step Commutation
- Low Filter Volume



- Challenging Overvoltage Protection
- Lower Control Dynamics

■ Voltage DC-Link Topology

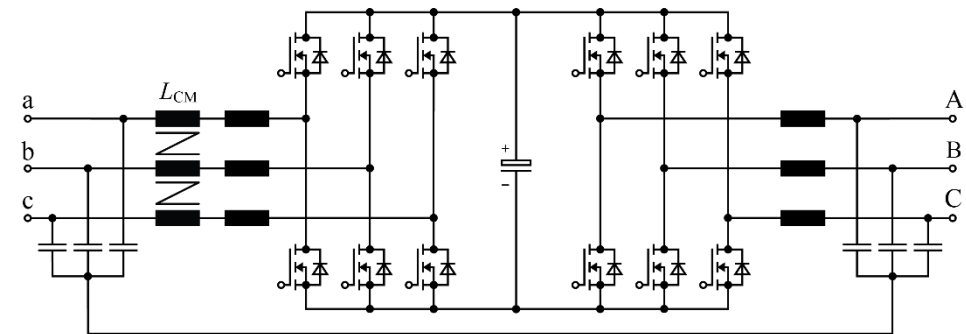
- Standard Bridge-Legs
- Low-Complexity Commutation
- Defined Semiconductor Voltage Stress
- Facilitates DC-Link Energy Storage



- High Input / Output Filter Volume

200kHz SiC Current DC-Link AC/AC Converter (1)

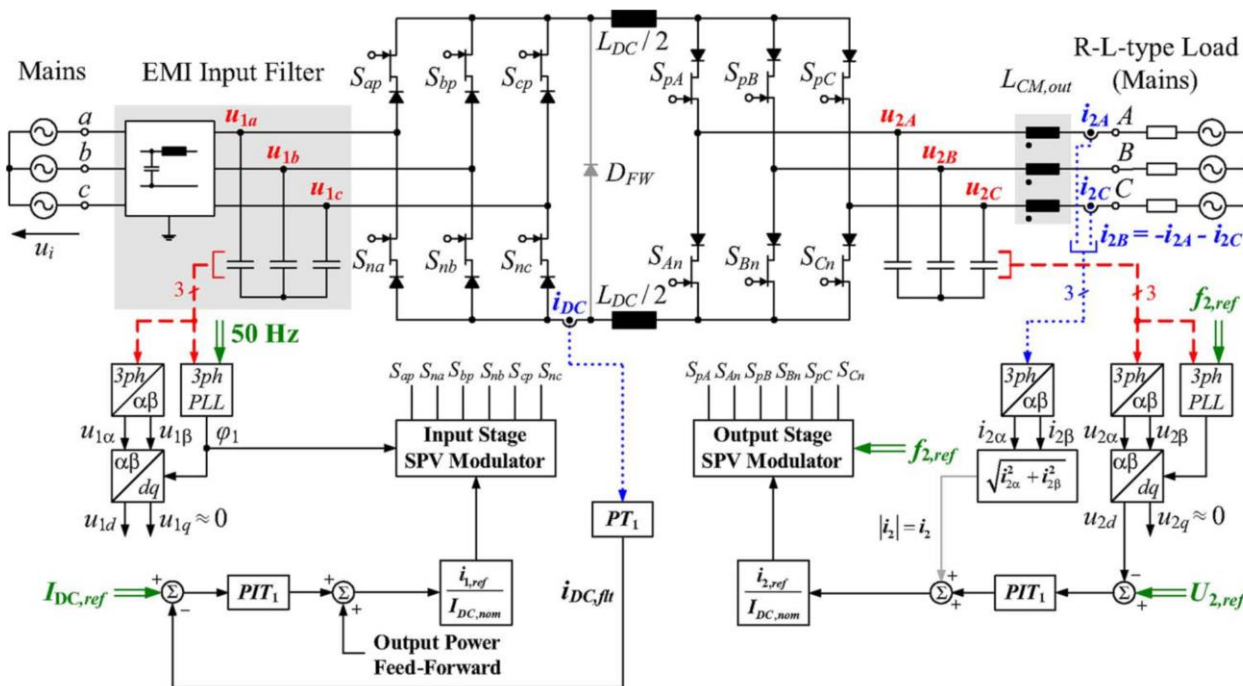- *Normally-On T0-220 1200V/6A SiC J-FETs — Built in 2008 (!)*
- *1200V/10A SiC Schottky Series Diodes*
- *X7R Ceramic Filter Capacitors*






- *Natural Free-Wheeling Current Path for Gate Driver Power Supply Loss*

200kHz SiC Current DC-Link AC/AC Converter (2)

- **7kHz DC-Link Current Control Bandwidth**
- **PCB-Stack Construction — Power | Gate-Drive | Control Board**
- **Coldplate Cooling**

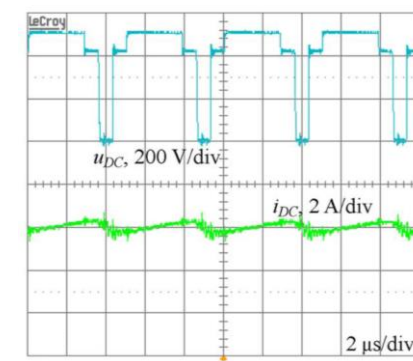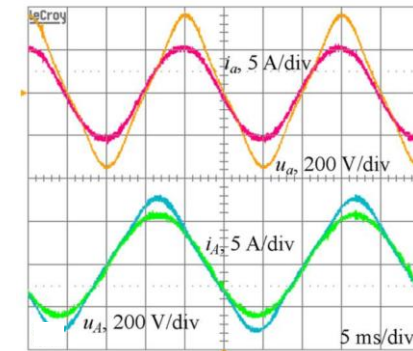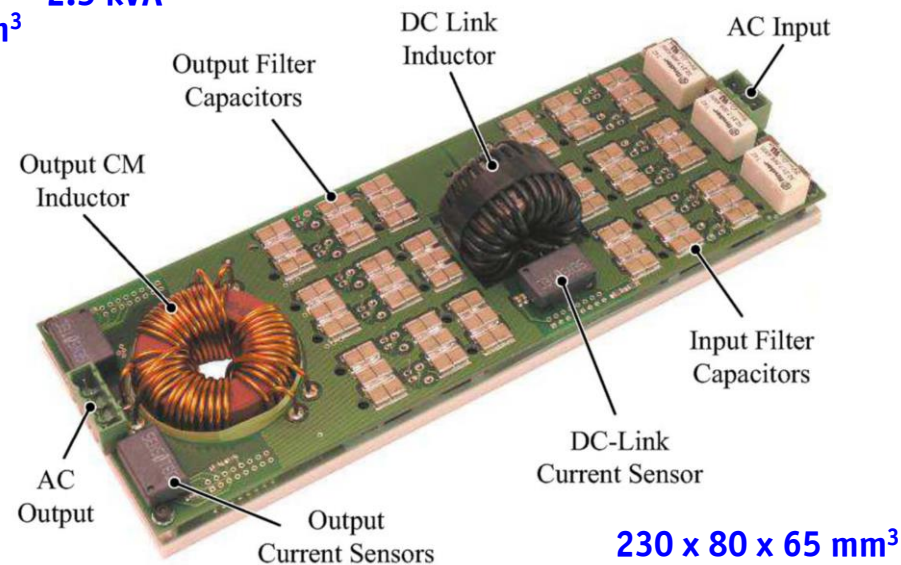Input **400V_{rms} Line-to-Line**
 Output **0...300Hz**
 Rated Power **2.5 kVA**
2.4 kVA / dm³
(40 W/in³)





- **Low Volume Powder Core DC-Link Inductor (320μH)**

200kHz SiC Current DC-Link AC/AC Converter (3)

- **7kHz DC-Link Current Control Bandwidth**
- **PCB-Stack Construction — Power | Gate-Drive | Control Board**
- **Coldplate Cooling**

— **Conducted EMI | EMI Filter**

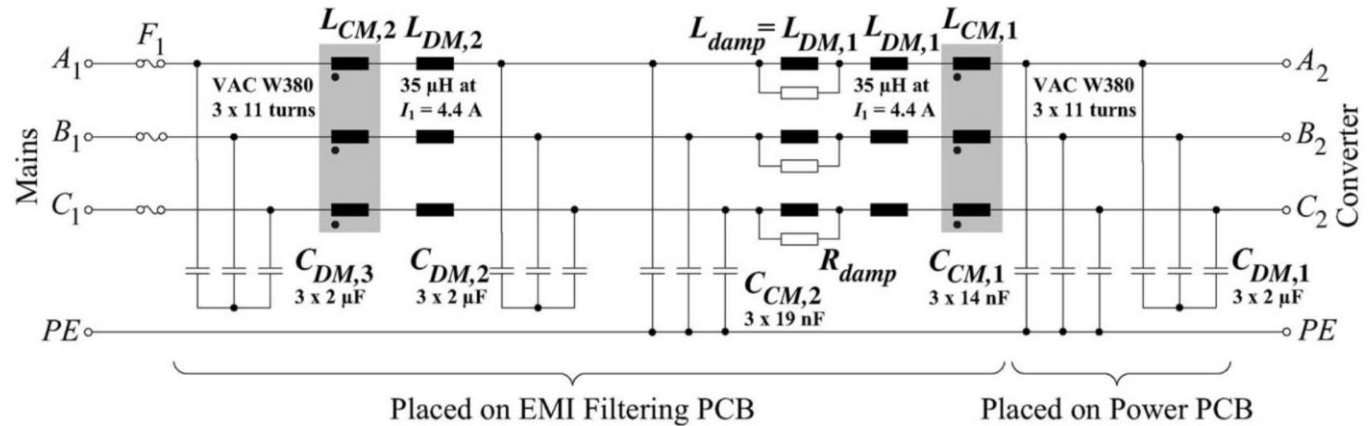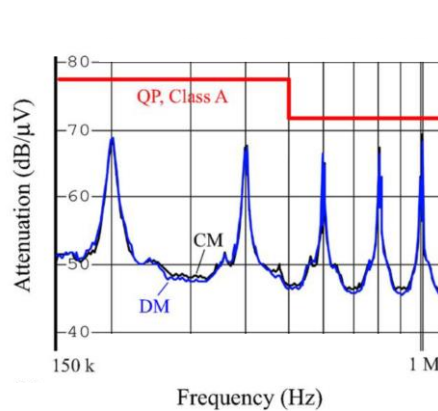


- **Low Volume Powder Core DC-Link Inductor (320uH)**

Remark 3- Φ AC/AC Matrix Converter

■ Indirect Matrix Converter (IMC)

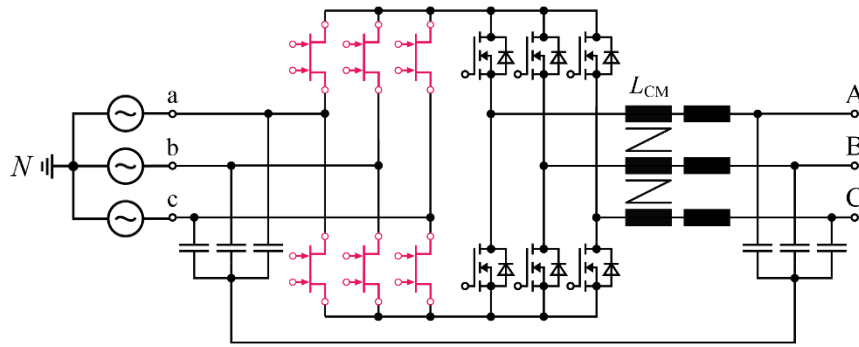
- CSI-Type GaN M-BDS AC/DC Front-End
- ZCS Commutation of CSI-Stage @ $i_{DC}=0$
- No 4-Step Commutation



- Higher # of Switches Compared to CMC
- Lower Cond. Losses @ Low Output Voltage
- Thermally Critical @ $f_{out} \rightarrow 0$

■ Direct Matrix Converter (CMC)

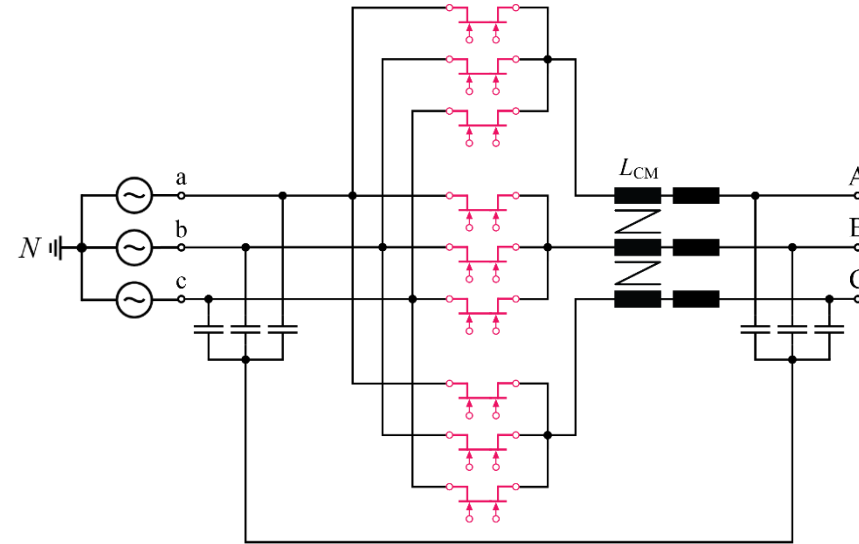- 4-Step Commutation
- Exclusive Use of GaN M-BDSs




- Thermally Critical @ $f_{out} \approx f_{in}$

3- Φ AC/AC Converter Comparison

■ Current DC-Link Topology


- Application of M-BDSs | 12 Switches
- 4-Step Commutation
- Buck-Boost Functionality
- Low Filter Volume

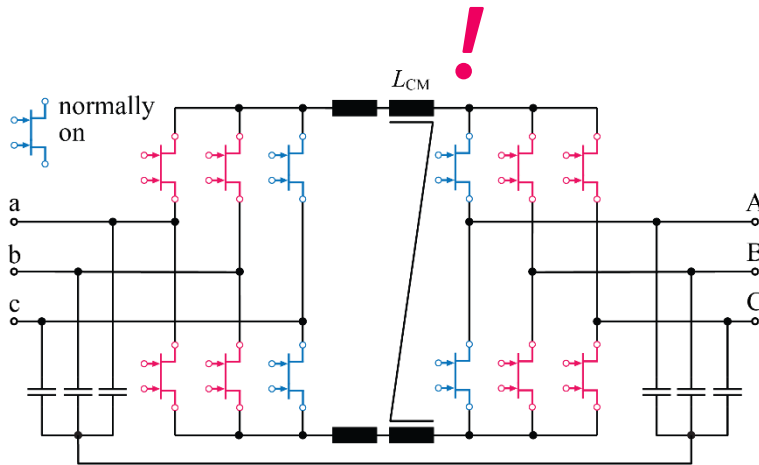

- Challenging Overvoltage Protection

■ Direct Matrix Converter

- Application of M-BDSs | 9 Switches
- 4-Step Commutation
- Complex Space Vector Modulation
- Limited to Buck-Operation (!)

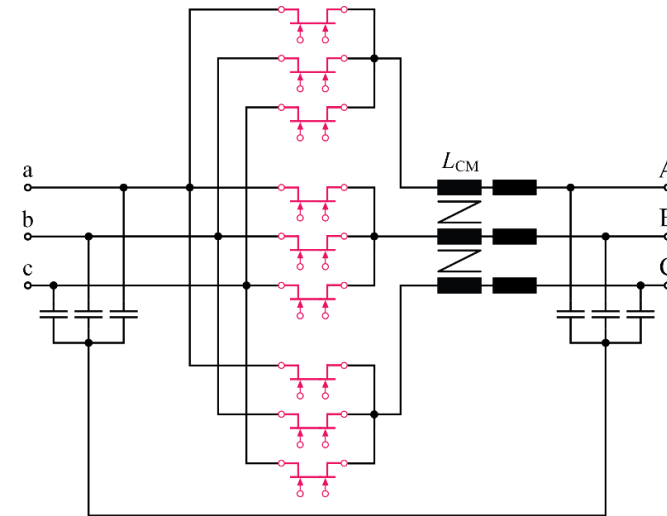



- Challenging Overvoltage Protection

Matrix Converter Monolithic 3D-Integration

- *GaN 3x3 Matrix Converter Chipset with Drive-By-Microwave (DBM) Technology*
 - *9 Dual-Gate GaN AC-Switches*
 - *DBM Gate Drive Transmitter Chip & Isolating Couplers*
 - *Ultra-Compact → 25 x 18 mm² (600V, 10A – 5kW Motor)*

Source: **Panasonic** ISSCC 2014

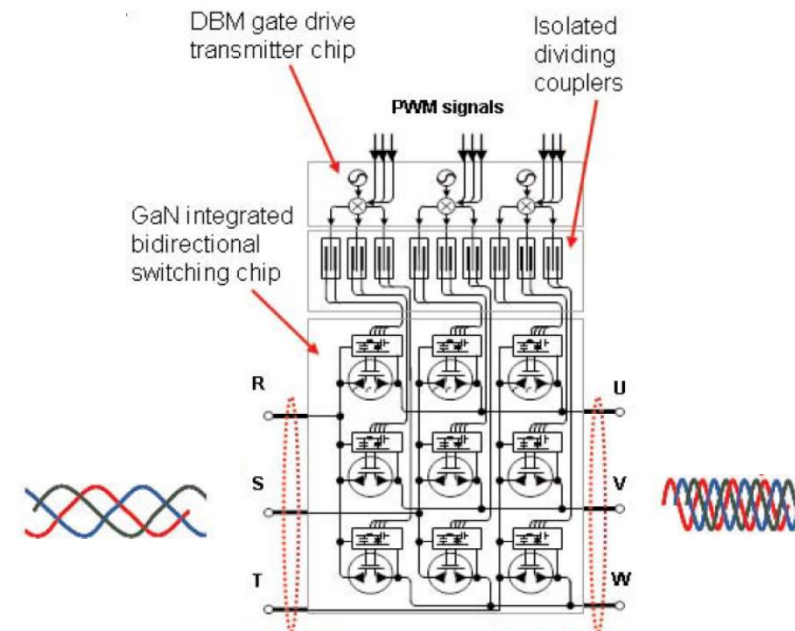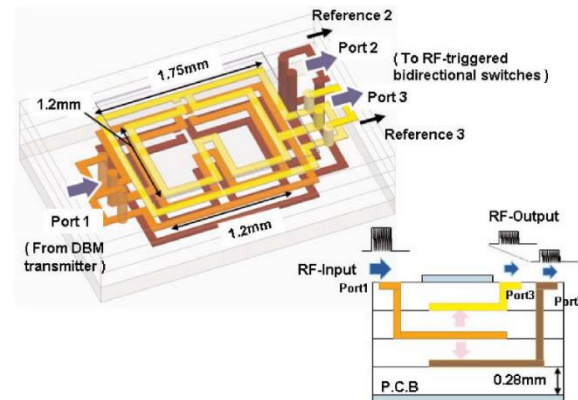
5.0GHz Isolated (5kV_{DC}) Dividing Coupler



— Conclusion —


Future Development

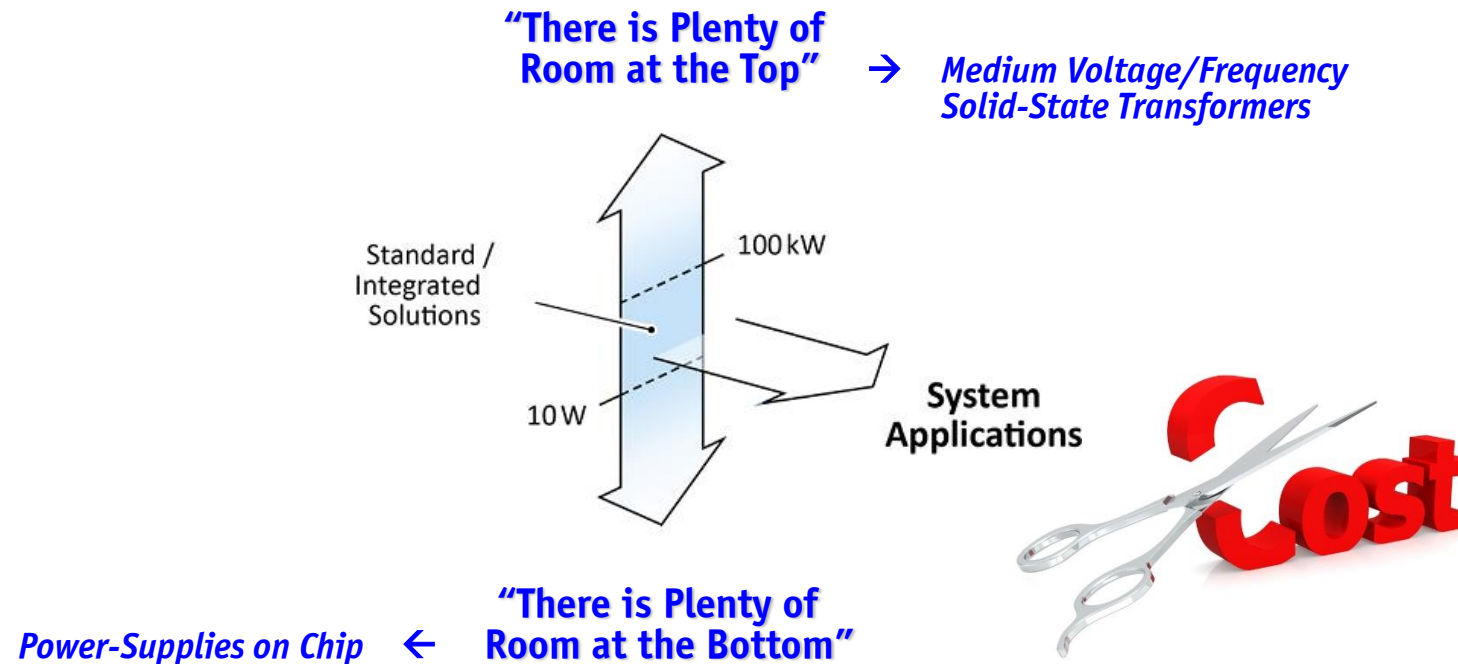- Commoditization / Standardization
- Extreme Cost Pressure (!)




- *Key Importance of Technology Partnerships of Academia & Industry*

Smart Converter Concept

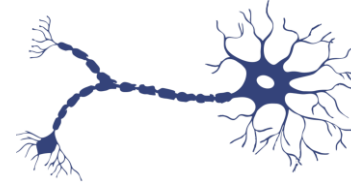

- Utilize High Computing Power & Network Effects in the Cloud → **Cognitive Power Electronics**

Source: Dr. R. Sommer
SIEMENS

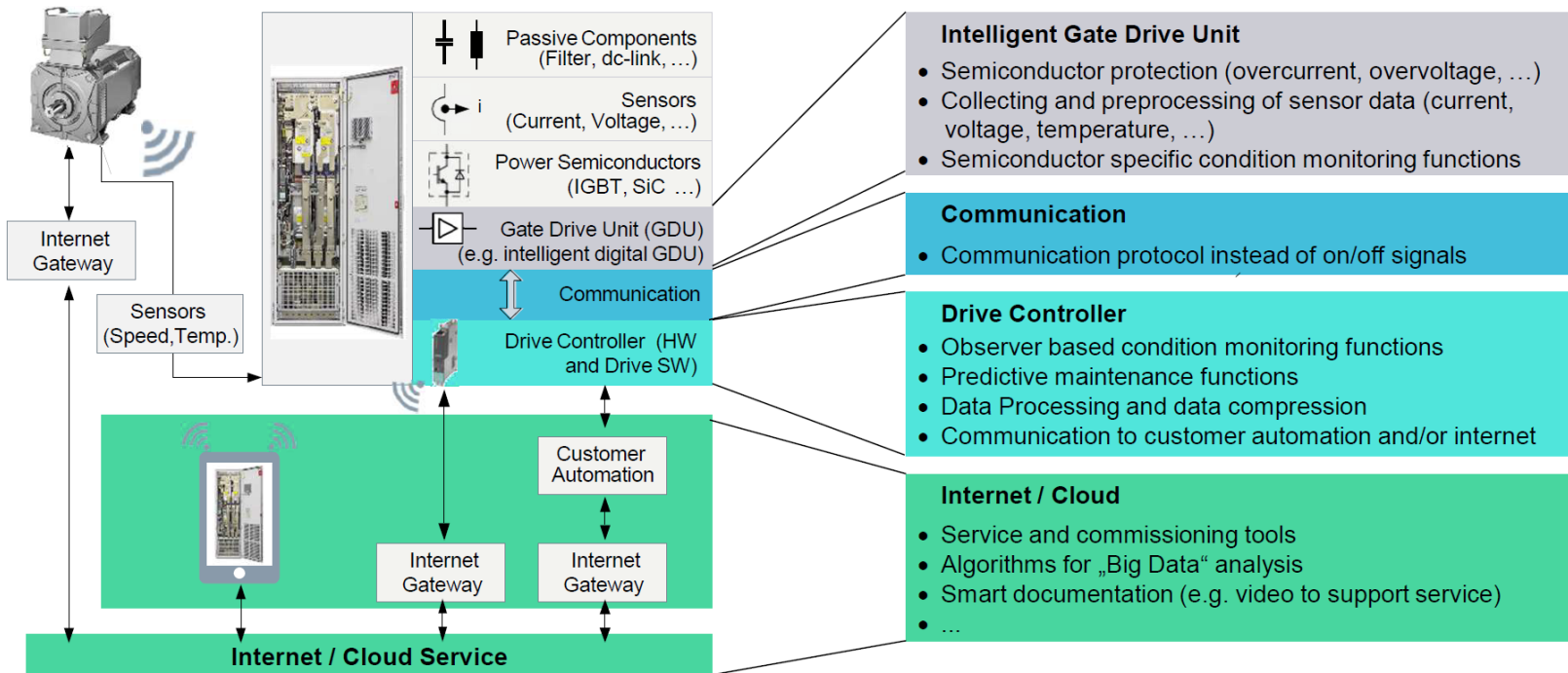

- Sensing & Computing on **Component Level** | **Converter Level** | **System Level** | **Application Level**

Appendix A

*3- Φ / 1- Φ Full-Power Operation
of PFC Rectifier Systems*

3- Φ / 1- Φ Full-Power PFC Rectifier

- 4-Wdg. CM Filter Inductors & Add. Diode Bridge-Leg
- Interleaving of Bridge-Legs in 1- Φ Operation
- Application as EU/USA EV-Charger Front-End




- **22kW / $U_{DC}=750V$ / $U_{AC}=3-\Phi$ 400V OR 1- Φ 240V | 98.4 % Efficiency | 6.8 kW/dm³ Power Density**

Appendix B




*Accurate Measurement of
SiC/GaN Power Semiconductor
On-State & Switching Losses*

On-State Voltage Measurement (1)

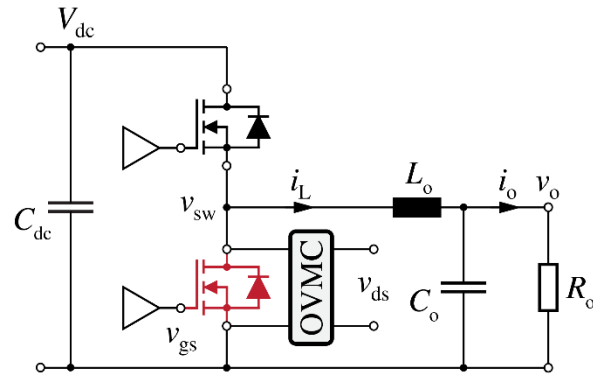- Device / Load Current / Gate Voltage / Junction Temp. → On State-Resistance $R_{DS(on)}$









$$R_{DS(on)} = v_{DS(on)} / i_L$$

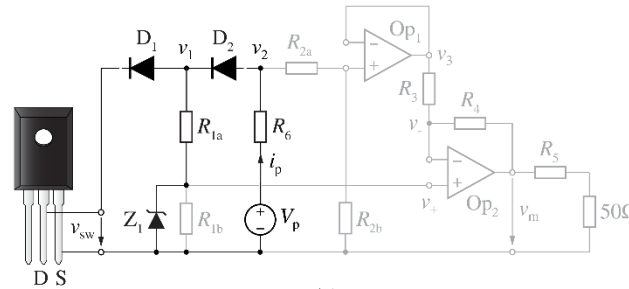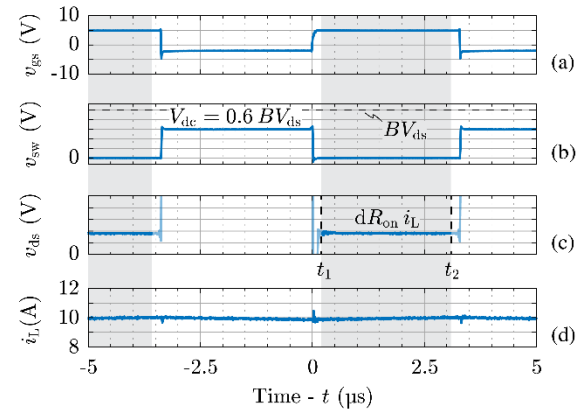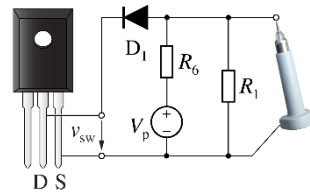

- Decoupling High Blocking Voltage and (Very) Low On-State Voltage ($\approx 1V \ll BV_{DS}$)

On-State Voltage Measurement (2)

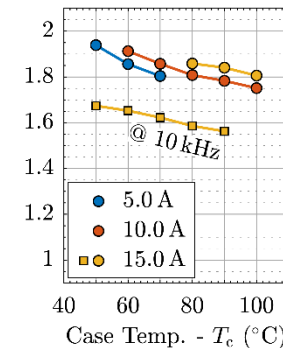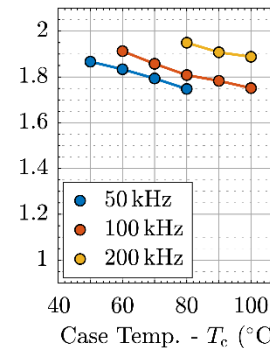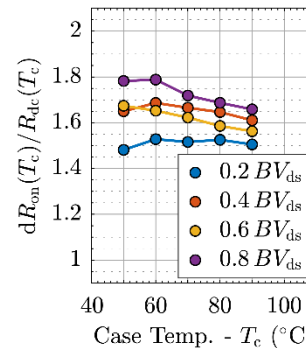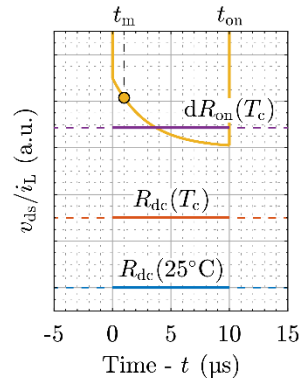
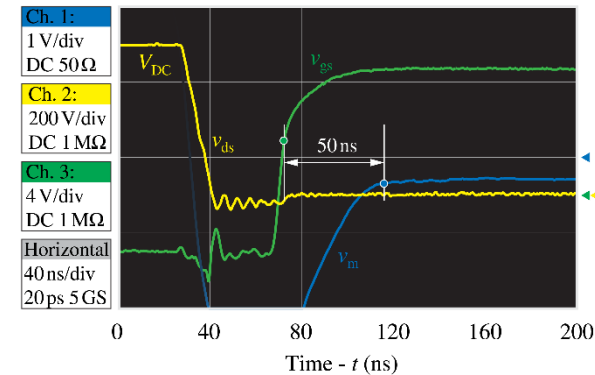
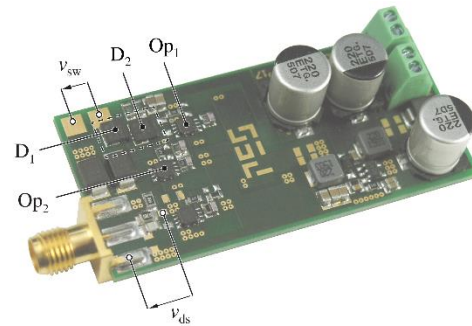
- **High Accuracy** → **Compensation of Decoupling Diode Forward Voltage**
- **Fast Dyn. Response** → **Valid Measurement 50ns After Turn-On**



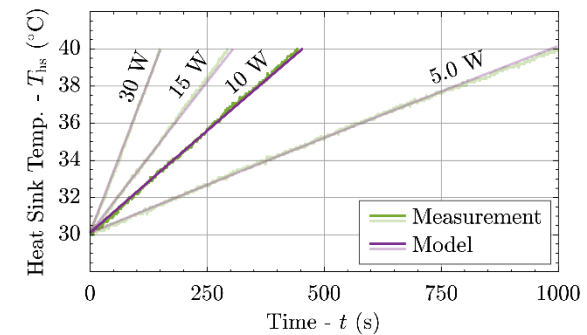
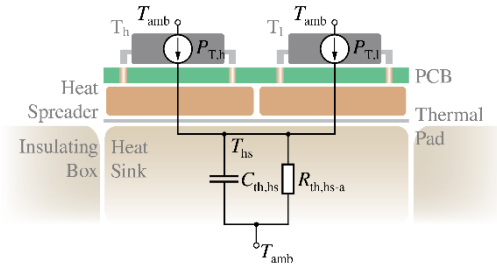
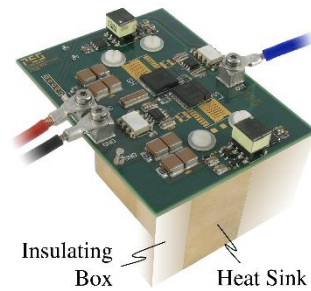
- **Example — Dyn. $R_{DS(on)}$ of GaN HEMTs → 2x $R_{DS(on)}$ @ 100kHz - 0.6BV_{DS}**

Switching Loss Measurement

■ Heat-Sink Temp.-Based Transient Calorim. Method → 15 min / Measurement





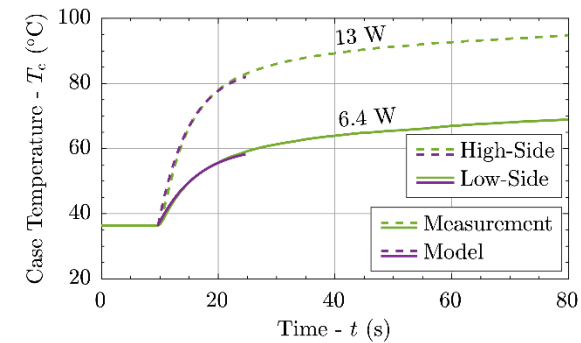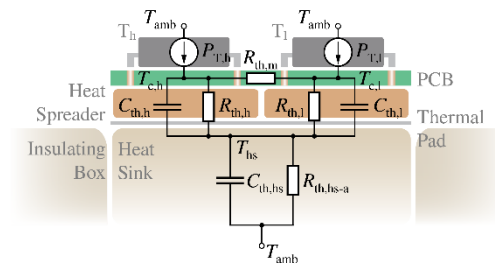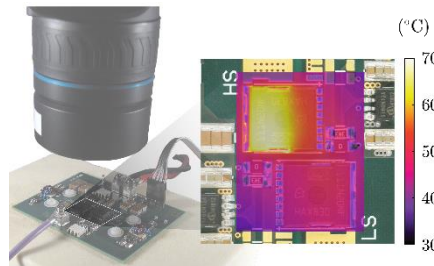■ Case Temp.-Based Ultra-Fast Method → 15 sec / Measurement





Example Measurement Results

650V GaN (ZVS)

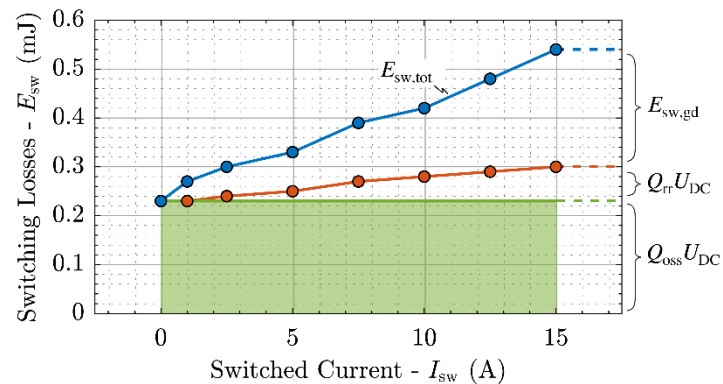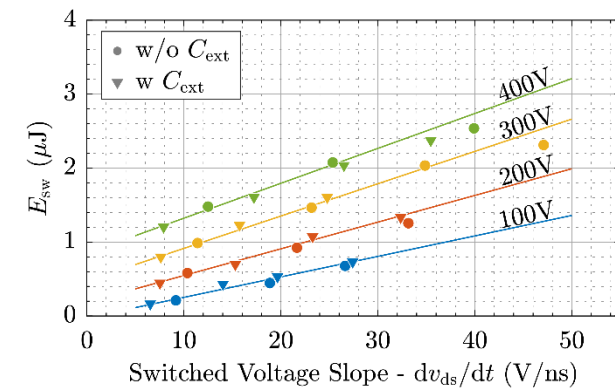

1.2kV SiC (Hard-Sw.)

200V Si vs. GaN (Hard-Sw. & ZVS)



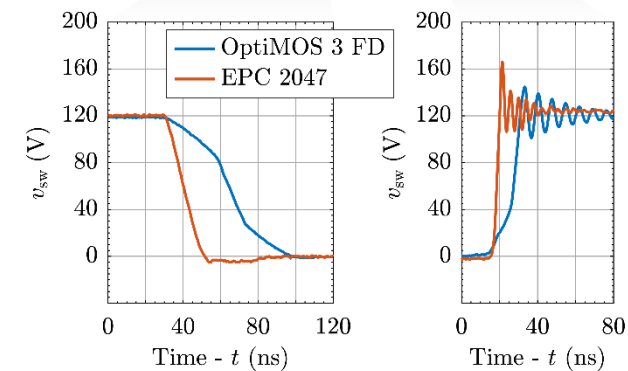
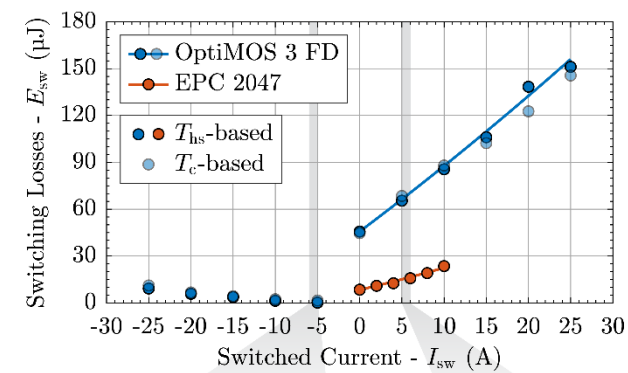


Appendix C

CM/DM EMI Separation

► 3- Φ DM/CM EMI Measurement & Separation

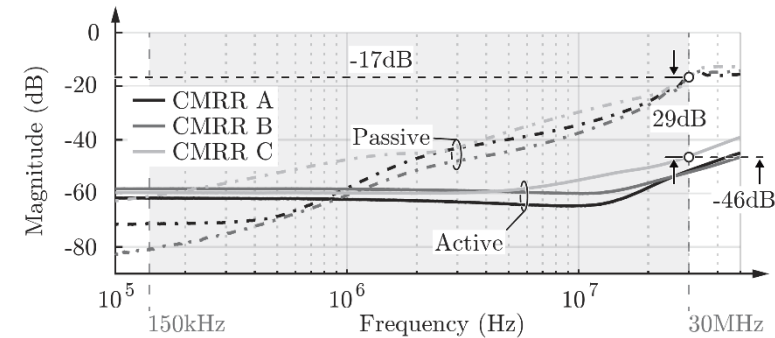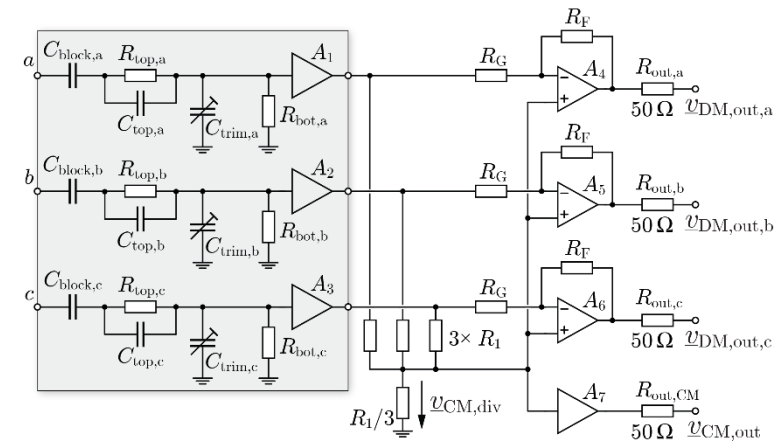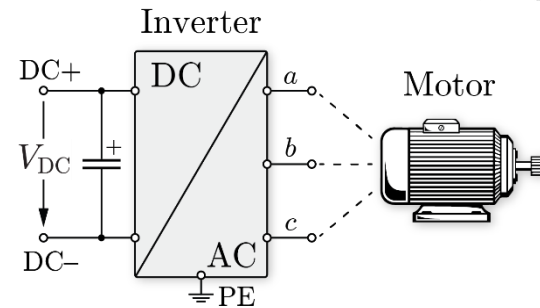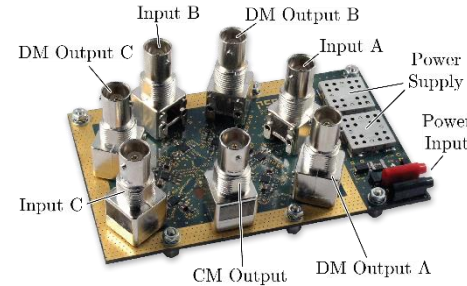- EMI Measurement @ Inverter Output
- DM/CM Splitting for Specific Filter Design



- Cap. Coupled Interface Circuit as Replacement for LISN (Var. Output Freq.)

Power Electronics 4.0

Cognitive Power Electronic Converters

A Few Spotlights




Cognitive Power Electronics: Converter Level

Key Question

- ▶ How to leverage artificial intelligence / **machine learning (ML)** techniques in the context of power electronics?

Converter Level

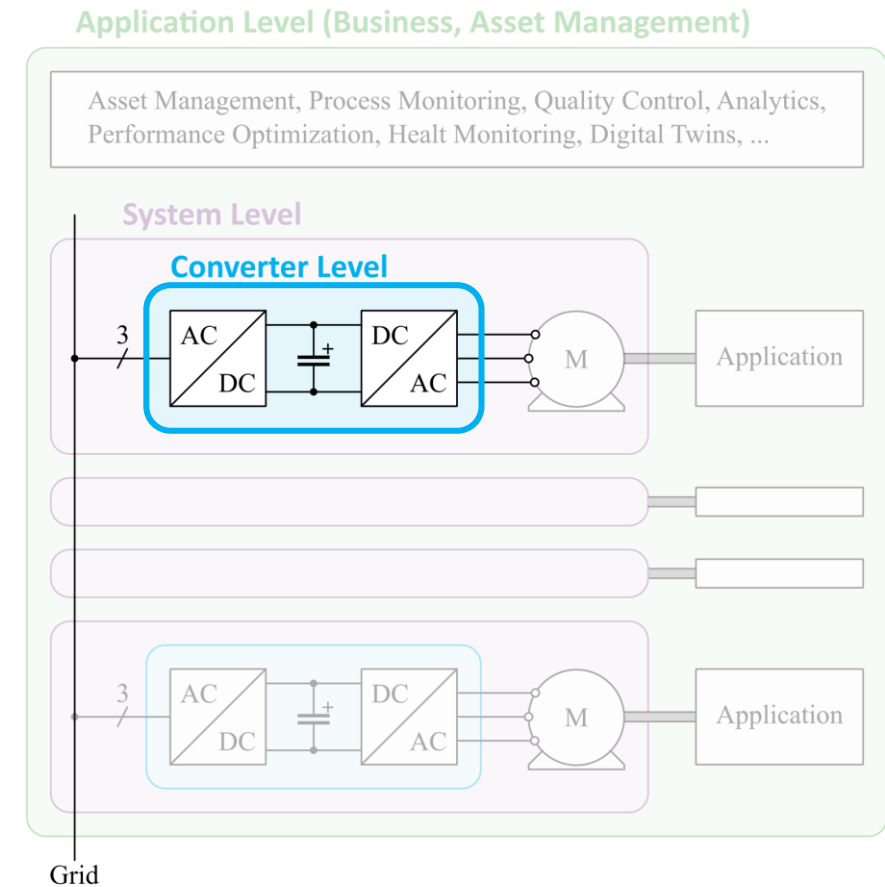- ▶ Design
- ▶ Control / Operation
- ▶ Maintenance




ML Applications in Power Electronics Life Cycle (Examples)



Inductor Modeling

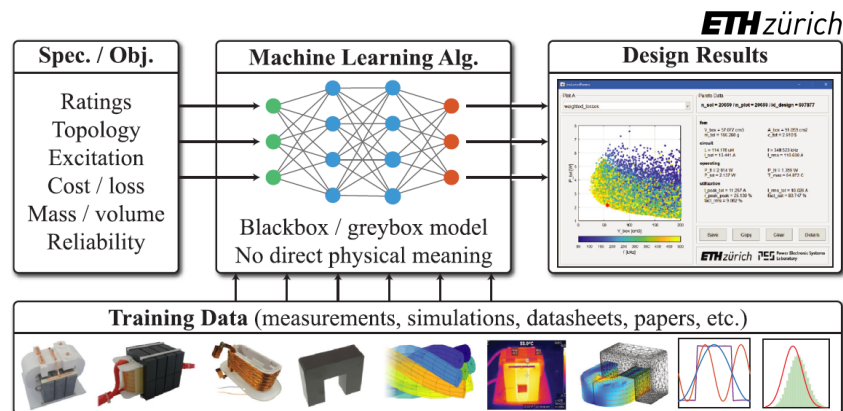
- Design **speedup** (50'000 designs/s) by replacing FEM simulations with trained ML model



<https://ai-mag.github.io/>

Heat Sink Optimization with Genetic Algorithms

- Commercial
- Optimized

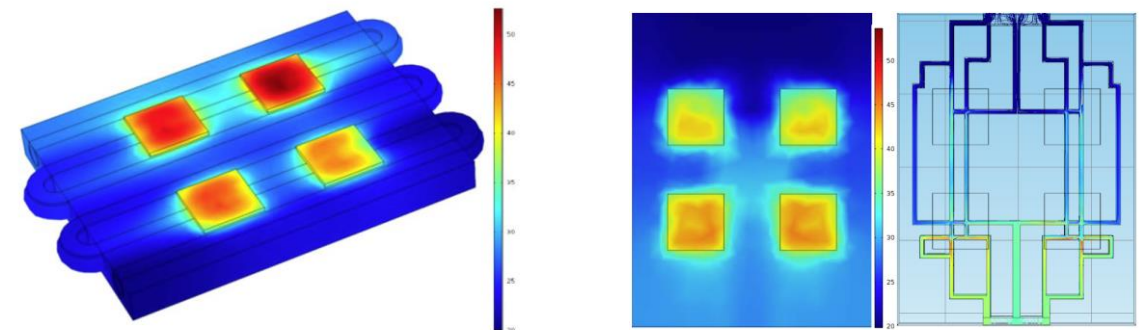

30% lower weight
10 K lower temp. rise
Better temp. homogeneity

ML Applications in Power Electronics Life Cycle (Examples)



Design

Control


Maintenance

Current Control with Neural Network

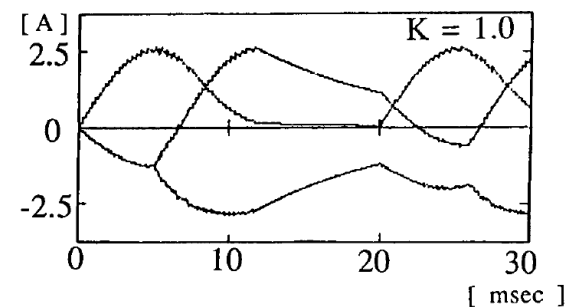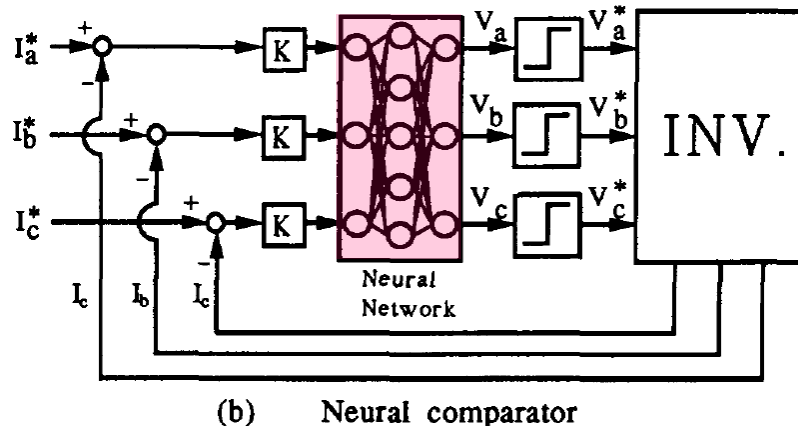- “Neural Comparator” replaces hysteresis comp.



- Hysteresis Comparator

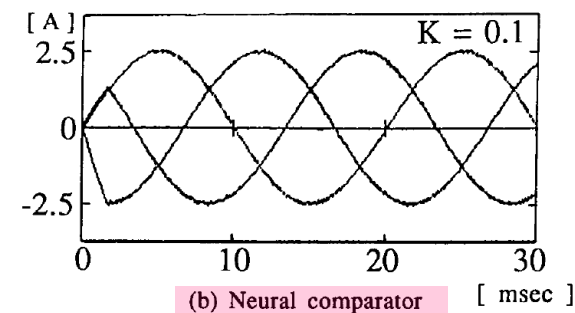

- Neural Comparator
Better fault tolerance
(loss of phase c current meas.)

1989 (!)


ML Applications in Power Electronics Life Cycle (Examples)

Design


Control

Maintenance

Offline

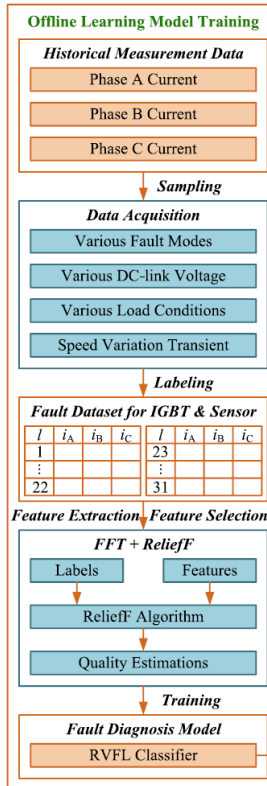


Online

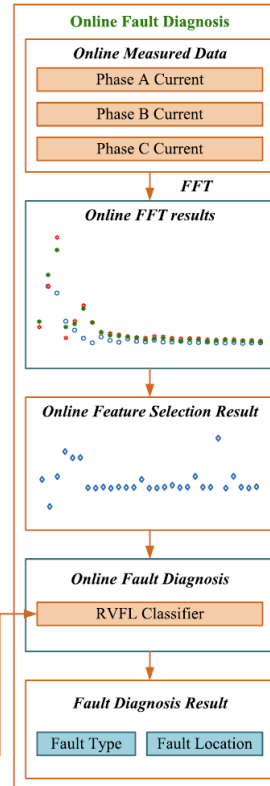


Data-Driven Detection of IGBT and Current Sensor Faults

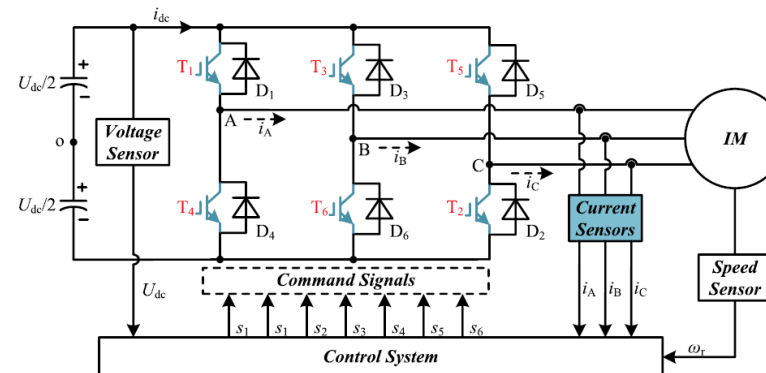
- ▶ Inputs: phase current measurements
- ▶ Output: fault type and location



IGBT open-circuit fault

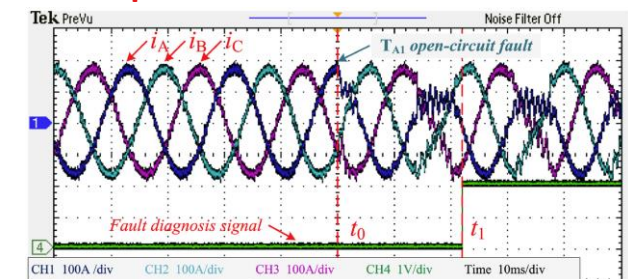

Sensor offset fault

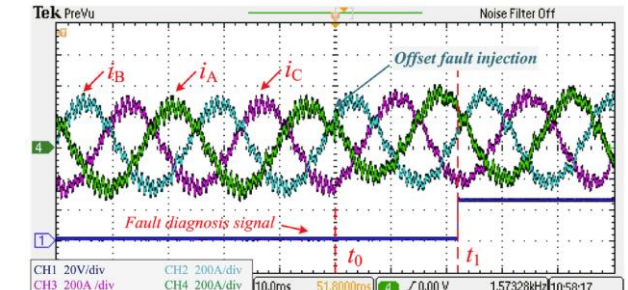

ML Applications in Power Electronics Life Cycle: **There are many!**

Design

Control


Maintenance

► Opportunities

- Mighty **tool** for a wide variety of engineering activities
- High computing power becomes cheap and ubiquitous
- **Use-case-specific** benefits over conventional / deterministic methods must be clarified

► Challenges

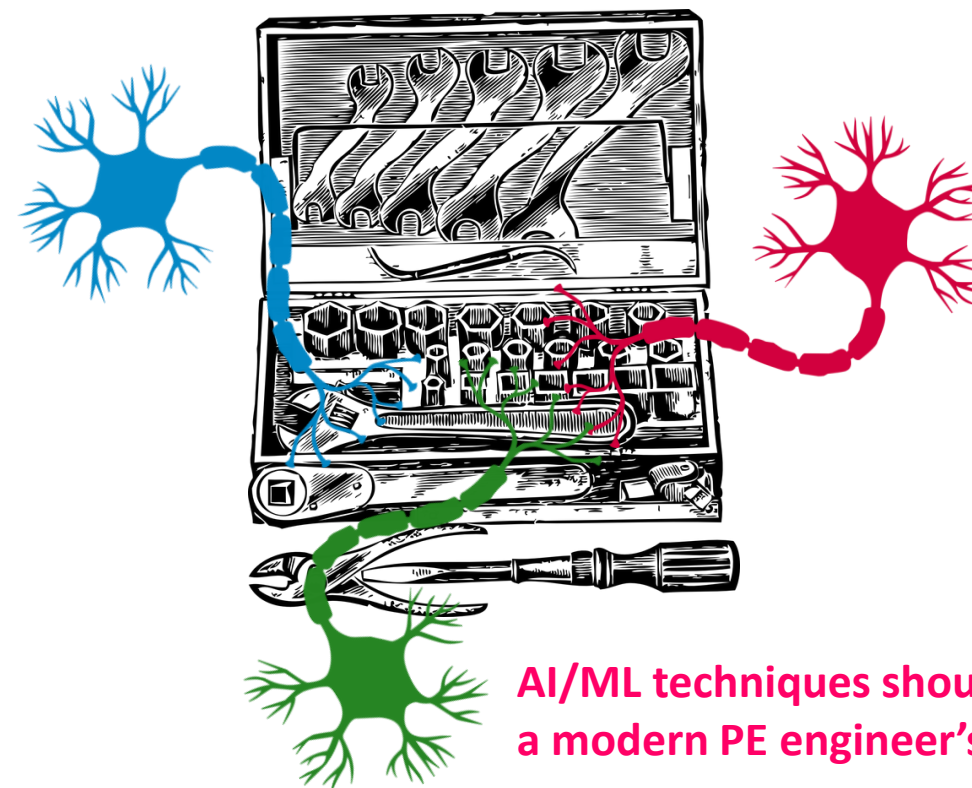- Training data quality and quantity / ability to generalize
- Black-box / statistical nature of ML models
vs. **safety requirements**
- Cybersecurity




AI/ML techniques should be part of a modern PE engineer's toolbox!

Cognitive Power Electronics: Beyond the Converter

Key Question

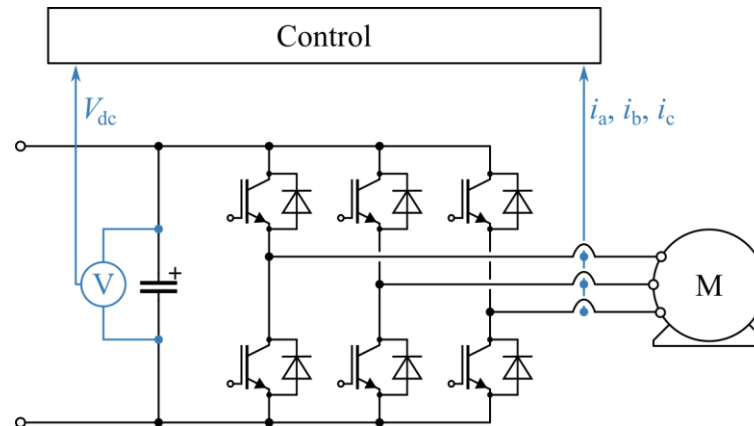- ▶ How to utilize **PE sensing / computing capabilities** for improved interaction with immediate surroundings?
- ▶ Example: VSI with necessary sensors
 - DC Voltage
 - Phase currents




Application Level (Business, Asset Management)

Asset Management, Process Monitoring, Quality Control, Analytics, Performance Optimization, Health Monitoring, Digital Twins, ...


System Level

Converter Level

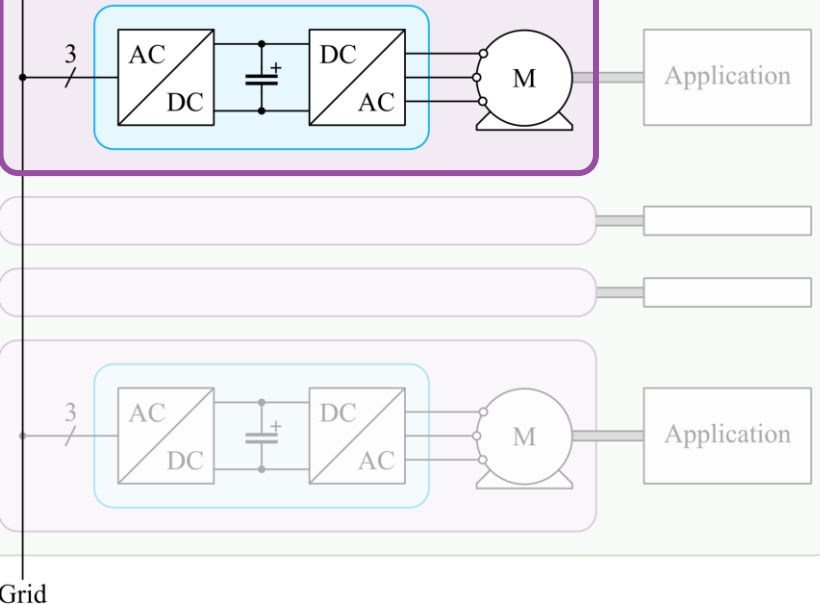

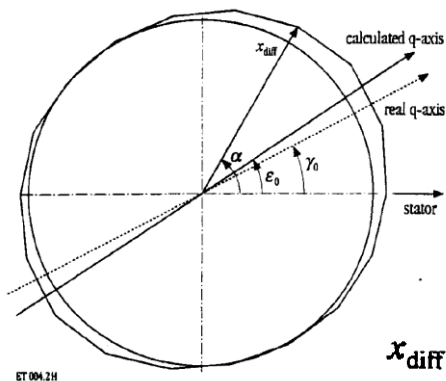Example: INFORM (Indirect Flux detection by On-line Reactance Measurement)

- Proposed in 1988/1991 for PMSM rotor position estimation
- Based on measuring position-dependent differential reactance x_{diff}





$$x_{\text{diff}}(\alpha, \gamma) = \frac{|\underline{u}_s|}{|(\Delta i_s / \Delta \tau)|_{\alpha, \gamma; \omega_m=0}}$$

Switching state
during test sequence

Phase current
measurement

PE 4.0 Concept

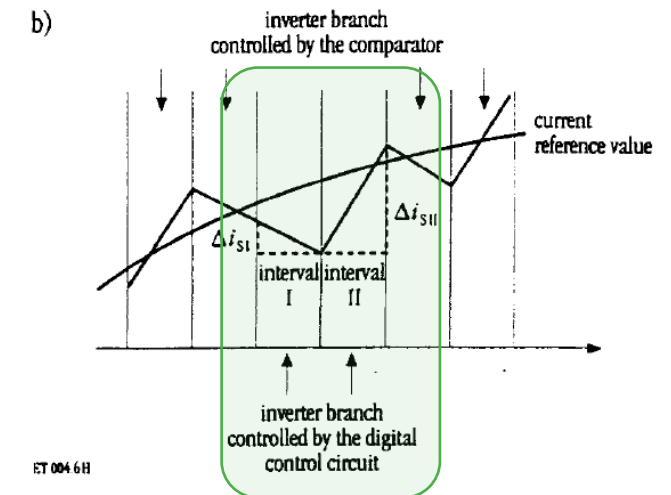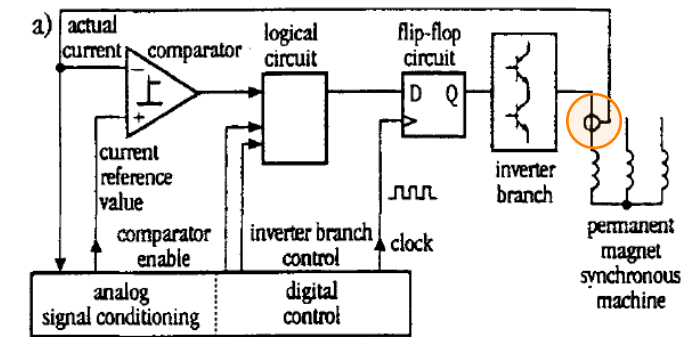- Utilize already available inverter capabilities
 - Current sensors
 - Test signal injection (minor SW modification)






Example: Induction Motor Fault Detection



- ▶ Fault detection based on **stator current monitoring**
- ▶ Research topic since the 1980ies
- ▶ Inverter-as-a-sensor

Today

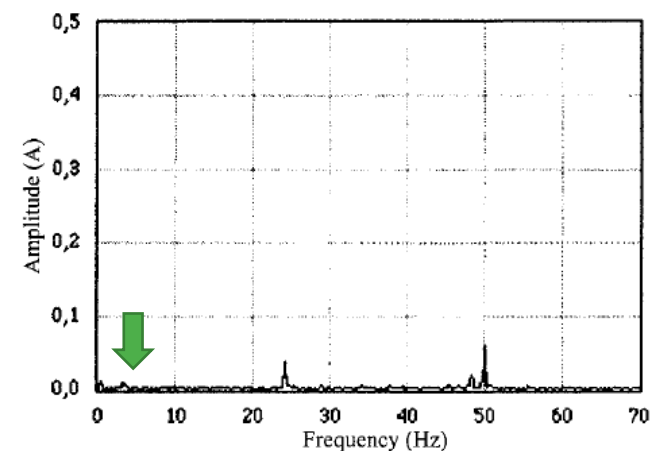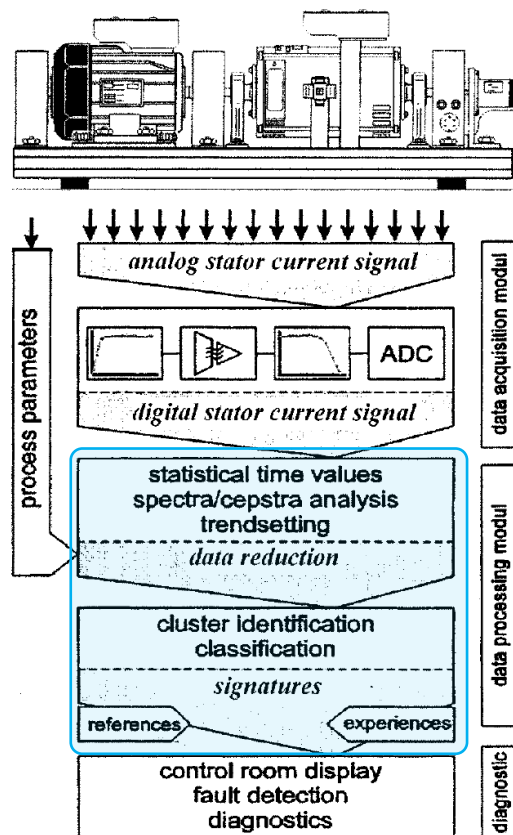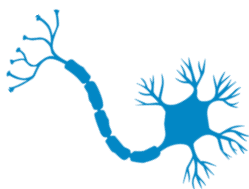
- ▶ Basic workflow unchanged
- ▶ Improvements through
 - Higher computing performance
 - New machine learning algorithms



Healthy

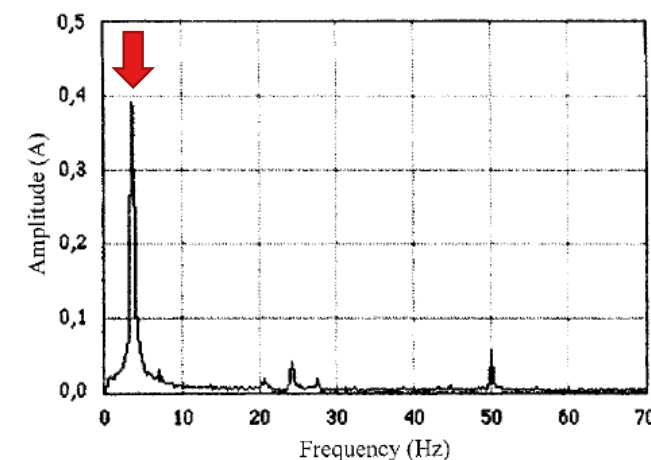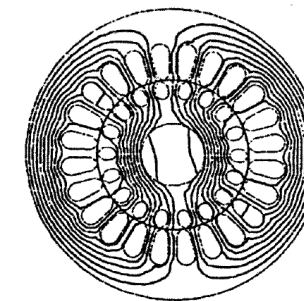

Broken Bars

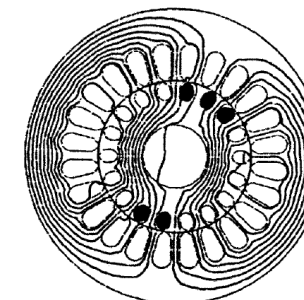


2000 (!)

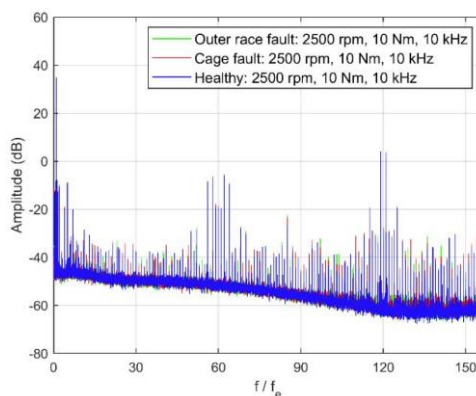Example: Data-Driven Machine Bearing Damage Detection


- Challenge: Quantity + Quality!
- Artificial damage for **training data** set generation




- Current spectra differences dominated by operating point, not by bearing damage



Principal
Component
Analysis
(PCA)

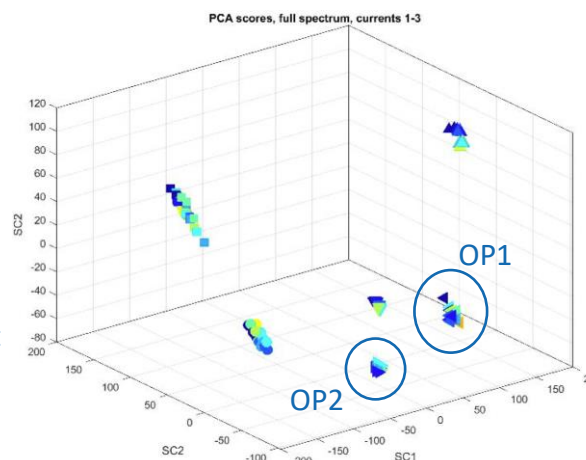


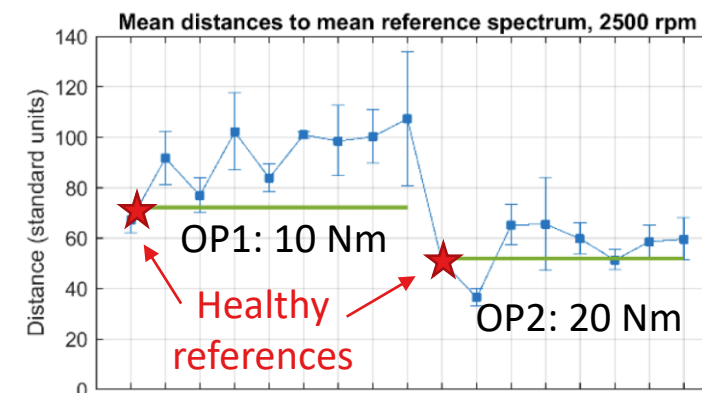
Cognitive Power Electronics for Intelligent Drive Technology




- Fault detection requires **referencing to a healthy case for each operating point!**
- Ongoing research

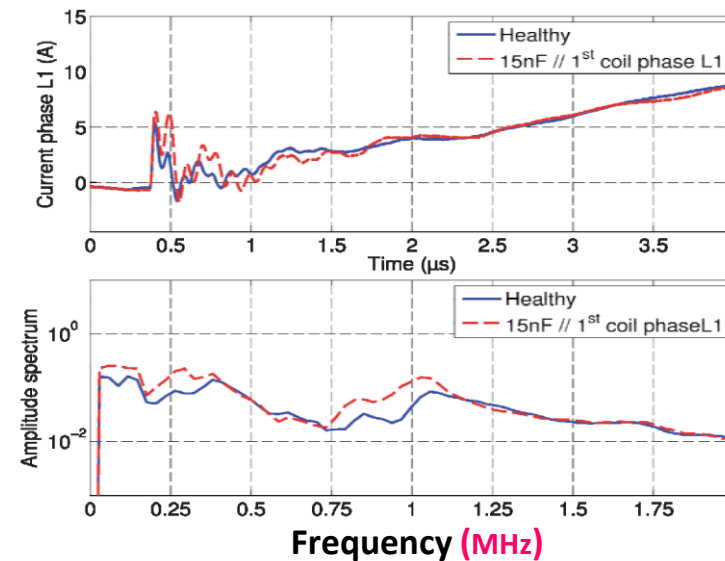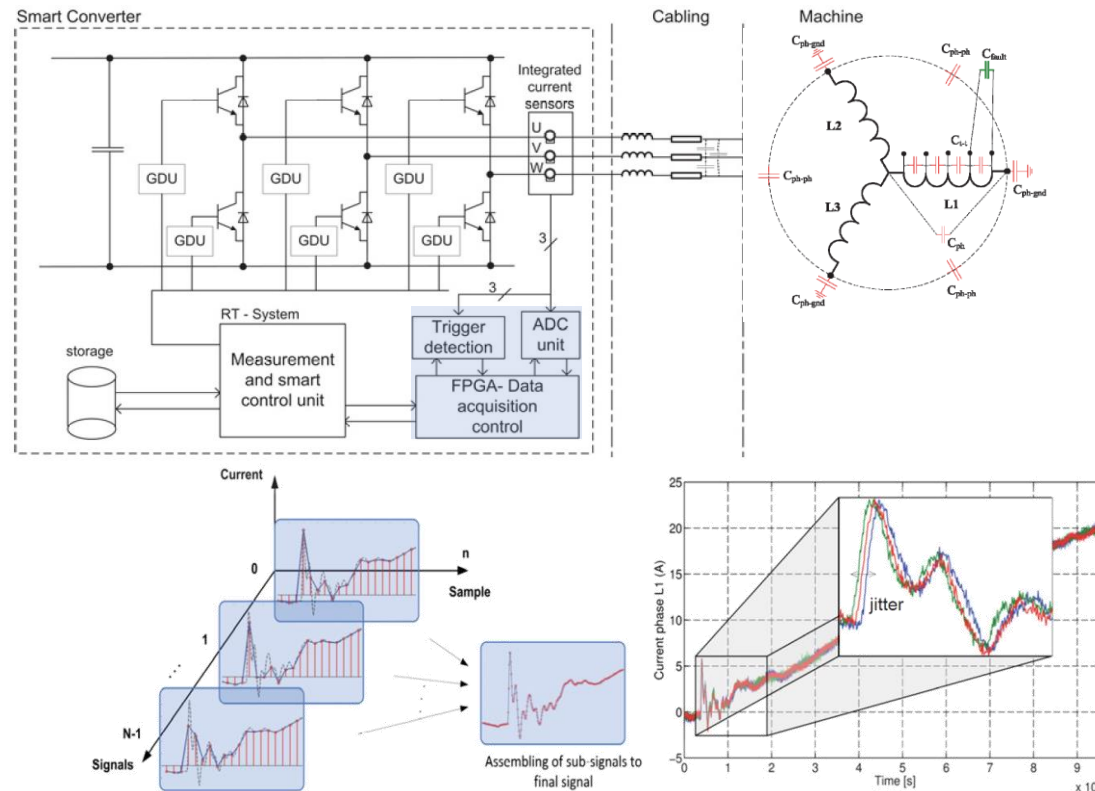Example: Isolation Health Monitoring for MV Traction Motors

- Isolation faults change current response to test voltage pulses (pre-startup)



Fault detection
incl. location

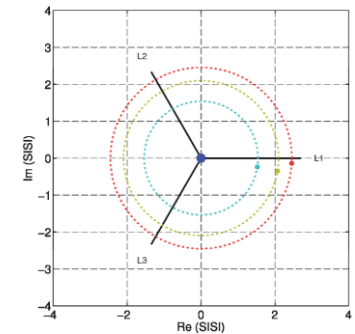

Tricks to achieve required measurement bandwidth:

- 15 MS/s with 1 MS/s ADC
→ Interleaving of multiple measurement seq.
- Jitter can become critical for higher BW



! Remark: Need for Extended Sensing Capabilities?

- ▶ Data (**quality & quantity**) is key for successful ML applications

▶ Improved Sensors

- Higher bandwidth
- Higher sampling rate
- Higher resolution






Memory
Processing power
Uplink bandwidth

▶ Additional Sensors

- ESR of Capacitors
- On-state voltages of semiconductors
- Component / heat sink temperatures
- Vibrations
- ...



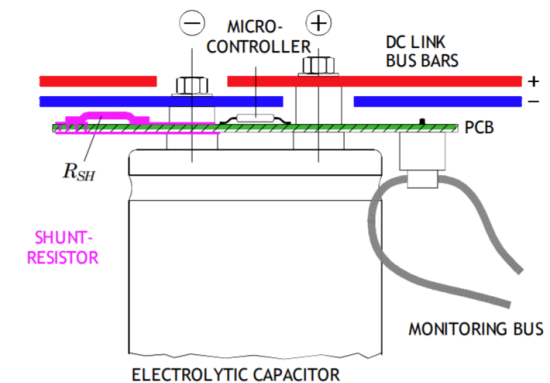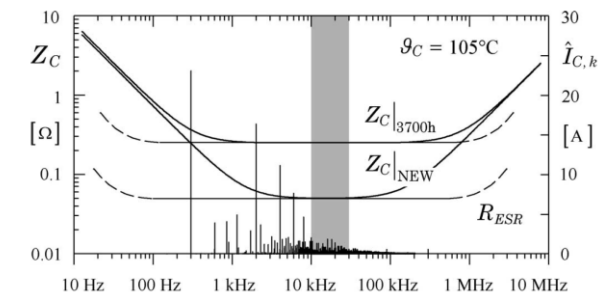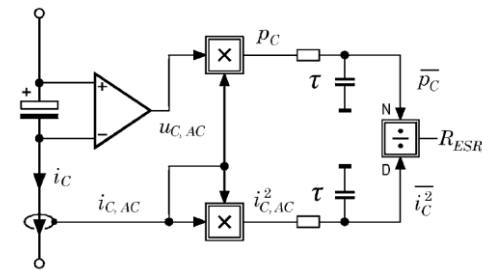Example: Capacitor ESR Meas. for Condition Monitoring




- Measurement of ESR in “frequency window” (temp. comp.)
- Data transfer by opt. fiber or near-field RF link


Remark: Sensing Concepts (1)

On-State Voltage Measurement

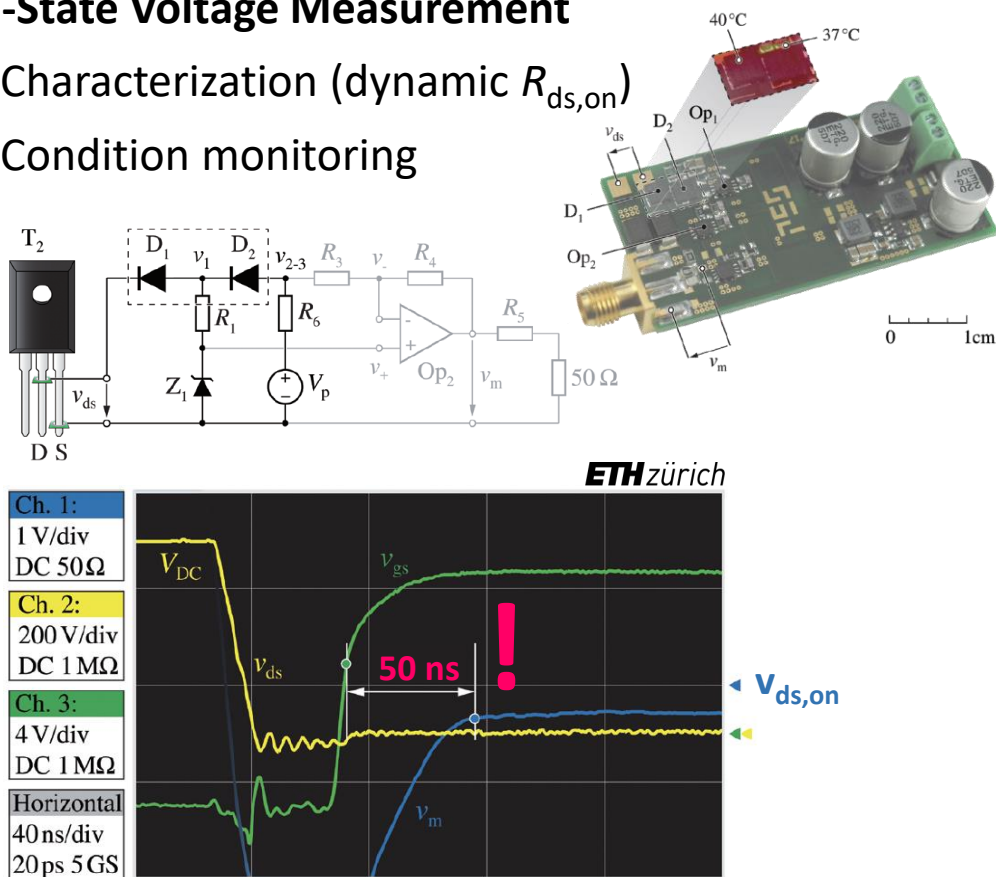
- Characterization (dynamic $R_{ds,on}$)
- Condition monitoring



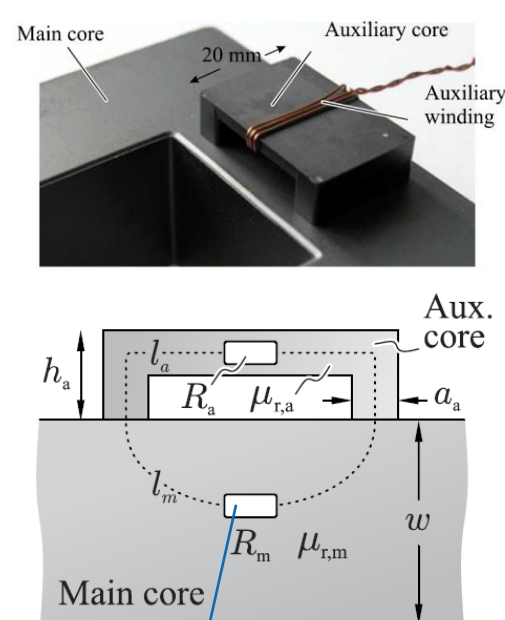Core Flux Density Sensing – The Magnetic Ear



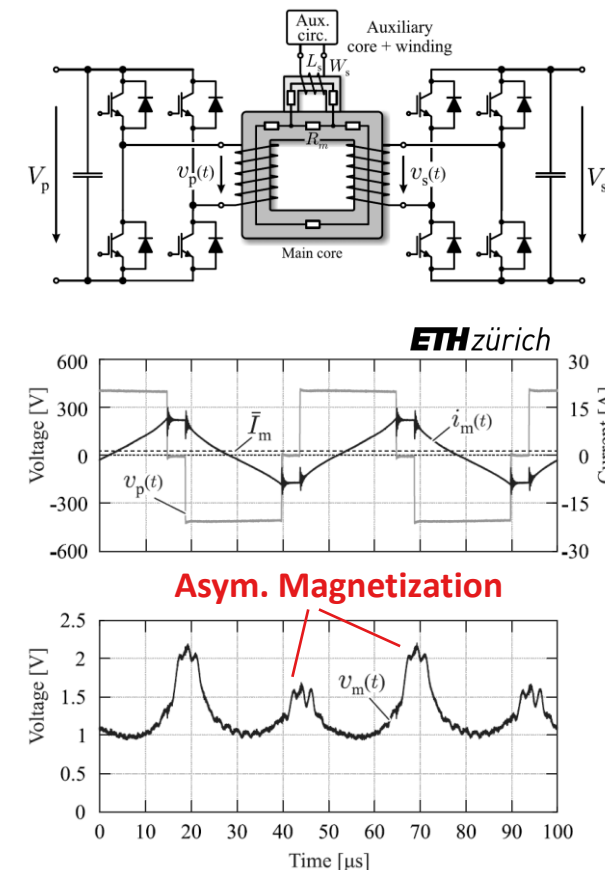
- Shared magnetic path:
 $L_{aux} = f(B_{main})$
- Meas. circuit: $L_{aux} \rightarrow v_m$




Remark: Sensing Concepts (2)

Direct di/dt Sensing

- E.g., INFORM: $x_{\text{diff}}(\alpha, \gamma) = |\underline{u}_s| / |(\Delta i_s / \Delta \tau)|_{\alpha, \gamma; \omega_m=0}$

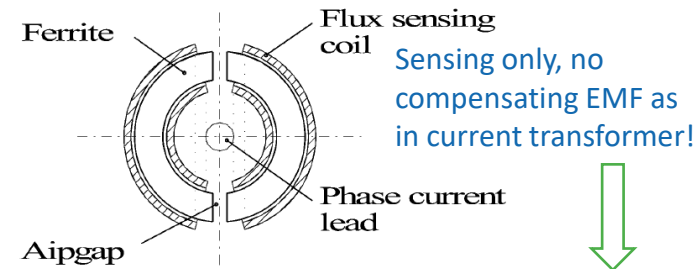



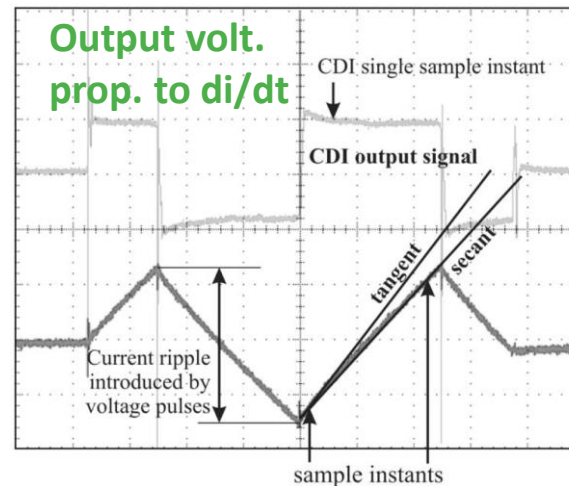
Needed to avoid saturation
(no compensating current)



T. M. Wolbank, J. L. Machl, and H. Hauser, "Closed-loop compensating sensors versus new current derivative sensors for shaft-sensorless control of inverter fed induction machines," *IEEE Trans. Instrum. Meas.*, vol. 53, no. 4, Aug. 2004.


Integrable Current Sensors

- Planar Rogowski Coil

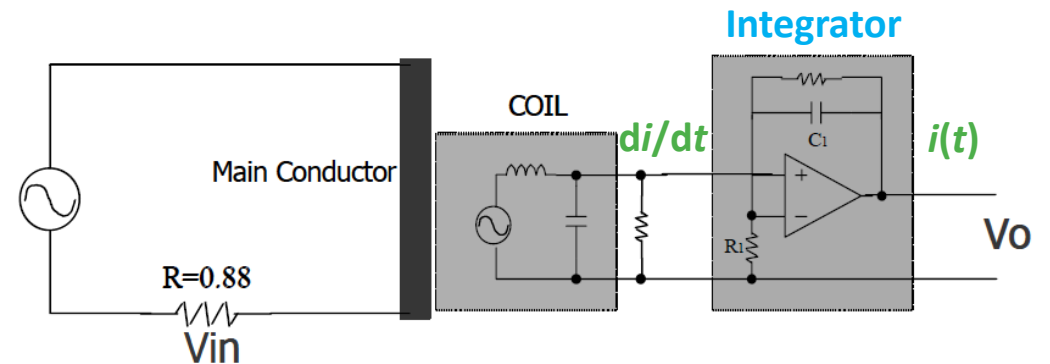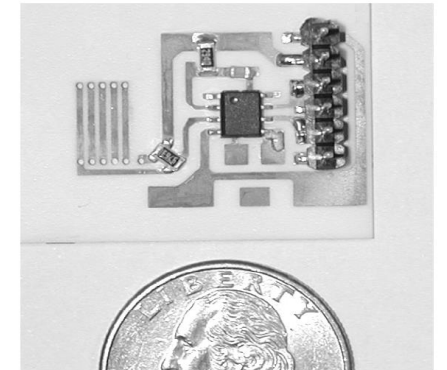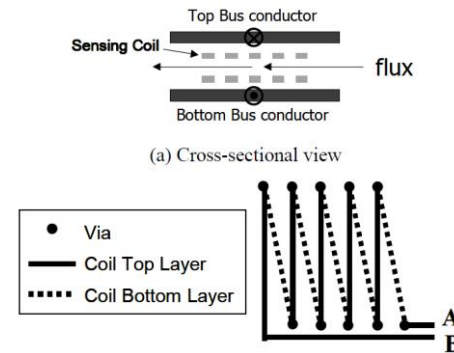

Remark: Sensing Concepts (3) – Utilization of “Parasitic” Physical Effects

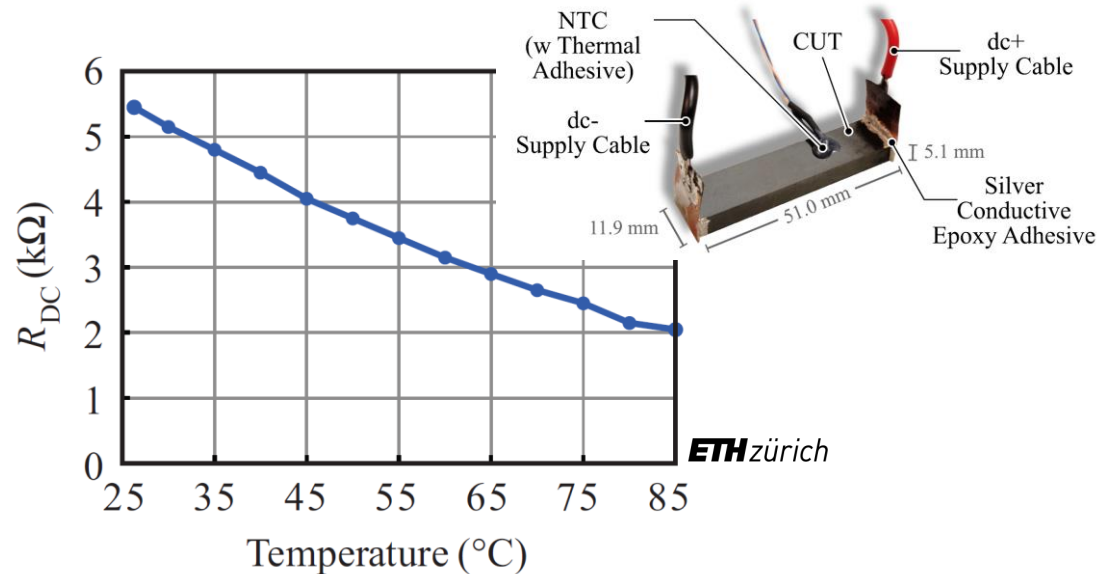Ferrite Core Temperature Sensing via El. Resistance




- Temperature-dependent electrical cond. of ferrites
- Could be utilized for integrated temp. sensing in **Smart Passives**

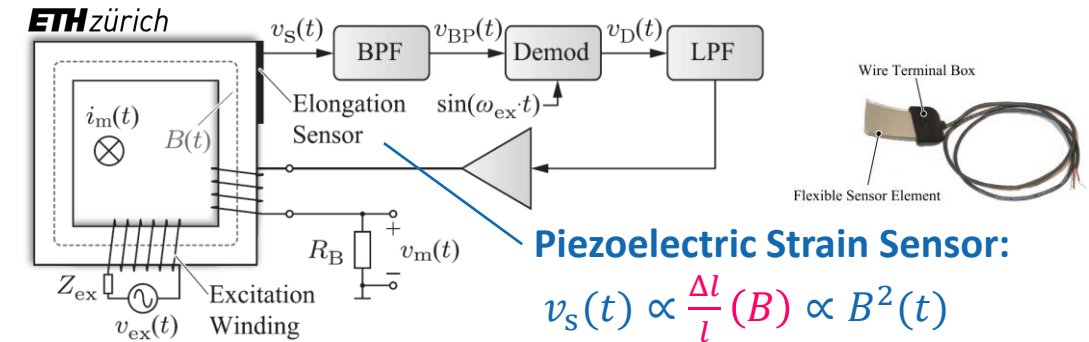
D. Neumayr, D. Bortis, J. W. Kolar, S. Hoffmann, and E. Hoene, “Origin and quantification of increased core loss in MnZn ferrite plates of a multi-gap inductor,” *CPSS Trans. Power Electron. Appl.*, vol. 4, no. 1, Mar. 2019.

P. Papamanolis, T. Guillod, F. Krismer, and J. W. Kolar, “Transient calorimetric measurement of ferrite core losses up to 50 MHz,” *IEEE Trans. Power Electron.*, vol. 36, no. 3, Mar. 2021.

Magnetostriction-Based DC+AC Current Sensor



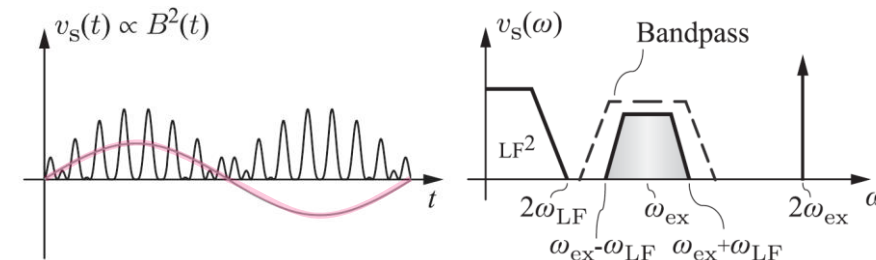- Amplitude modulation/demodulation to measure DC/LF





- Closed-loop performance: **± 20 A, DC...20 MHz**

L. Schrittwieser, M. Mauerer, D. Bortis, G. Ortiz, and J. W. Kolar, “Novel principle for flux sensing in the application of a DC + AC current sensor,” *IEEE Trans. Ind. Appl.*, vol. 51, no. 5, Sep. 2015.

Remark: Sensing Concepts (4) – Utilization of “Parasitic” Physical Effects


Electroluminescence (EL) in Power Semiconductors

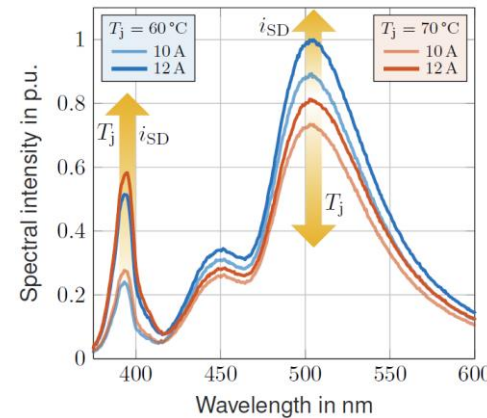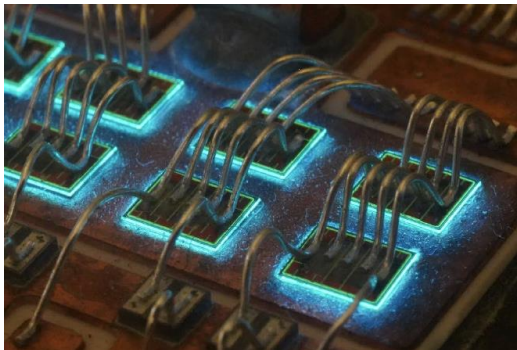- ▶ Every p-n junction can emit light (e.g., LEDs)
 - Si: invisible near IR / SiC: visible (discovered **1907** by H. J. Round)
- ▶ Example: SiC MOSFET Body Diode’s EL Spectrum depends on **temperature** and **current**




ISEA | RWTH AACHEN UNIVERSITY

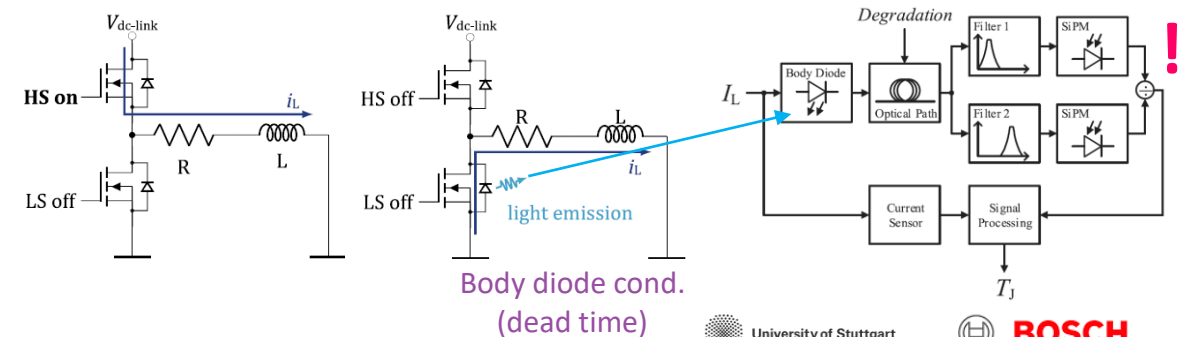L. A. Ruppert, S. Kalker, C. van der Broeck, and R. W. De Doncker, “Analyzing spectral electroluminescence sensitivities of SiC MOSFETs and their impact on power device monitoring,” in *Proc. PCIM Europe Conf.*, 2021.



First Applications (2018)

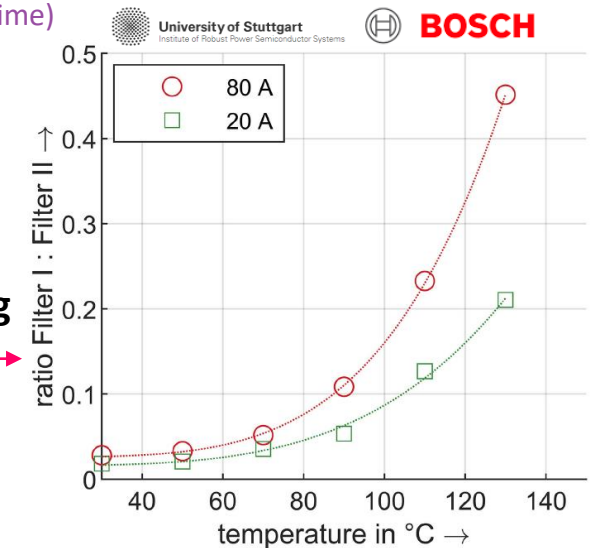- ▶ Current sensing via intensity
- ▶ Junction temperature sensing via **ratio of peak intensities** →
 - Increased robustness against optical path degradation




J. Winkler, J. Homoth, and I. Kallfass, “Utilization of parasitic luminescence from power semiconductor devices for current sensing,” in *Proc. PCIM Europ. Conf.*, Jun. 2018.

J. Winkler, J. Homoth, and I. Kallfass, “Electroluminescence-based junction temperature measurement approach for SiC power MOSFETs,” *IEEE Trans. Power Electron.*, vol. 35, no. 3, 2020.

! Remark: Digital Transformation & Digital Twins

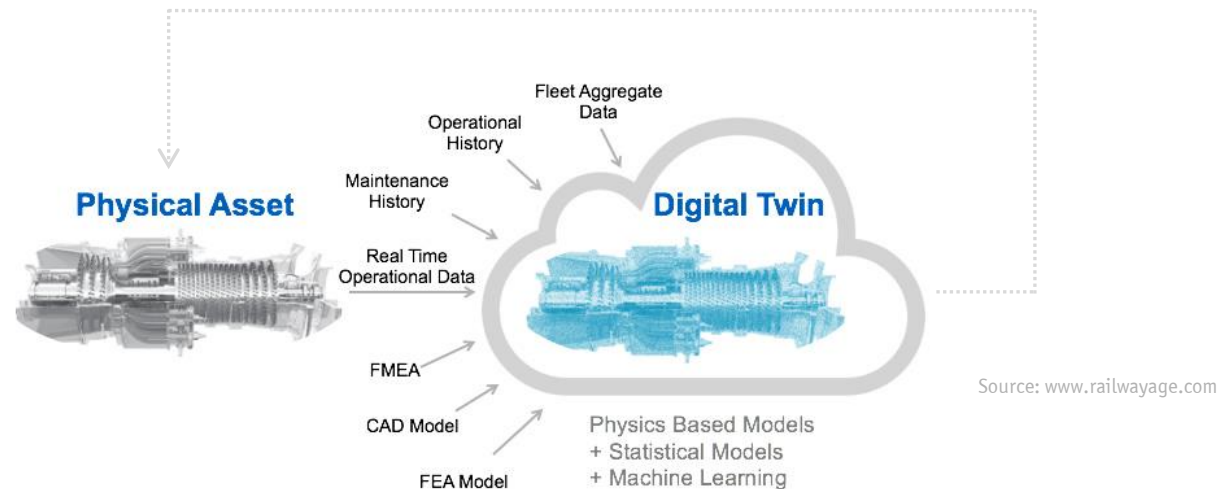- ▶ Digital Thread / **Digital Twin** → “Weaving” real/physical & virtual world together
- ▶ “Digital Birth Certificate” → Keep track of each part/machine through whole lifetime
- ▶ Fully Digital Product Lifecycle → “Digital Tapestry” (Lockheed Martin)




- ▶ **Smart components** with **integrated sensors** connect to Digital Twin
→ Design Improvements / Preventive Maintenance, etc.

Cognitive Power Electronics: Application Level – Power Electronics 4.0

Key Question

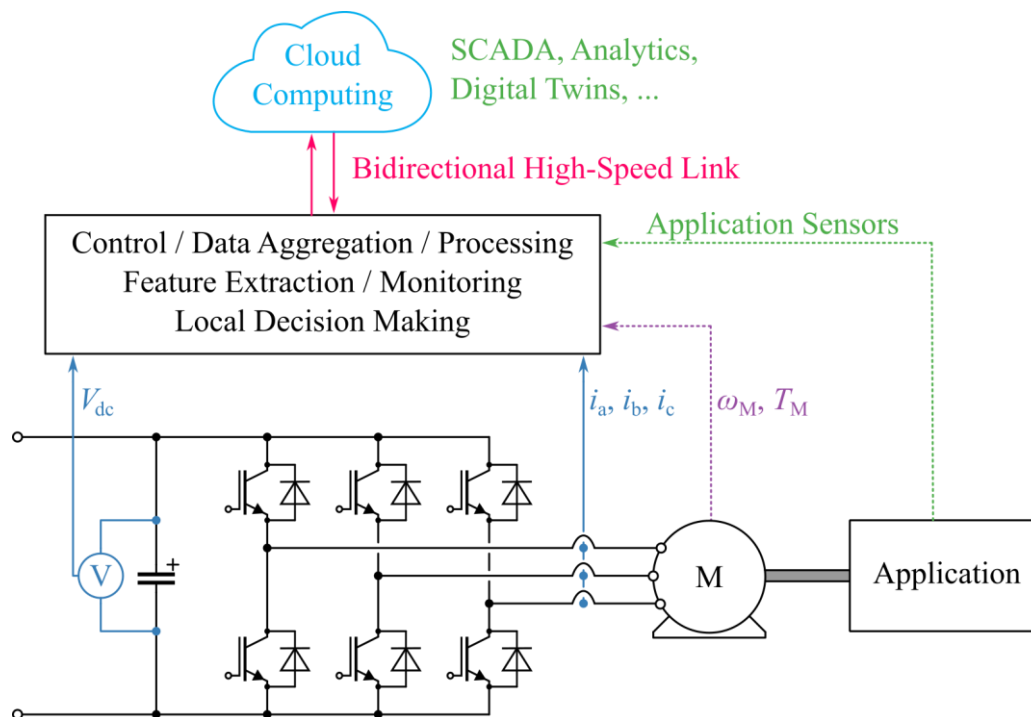- **Future role of power electronic converters** in the application/business context?




Application Level (Business, Asset Management)

Asset Management, Process Monitoring, Quality Control, Analytics, Performance Optimization, Health Monitoring, Digital Twins, ...


System Level

Converter Level

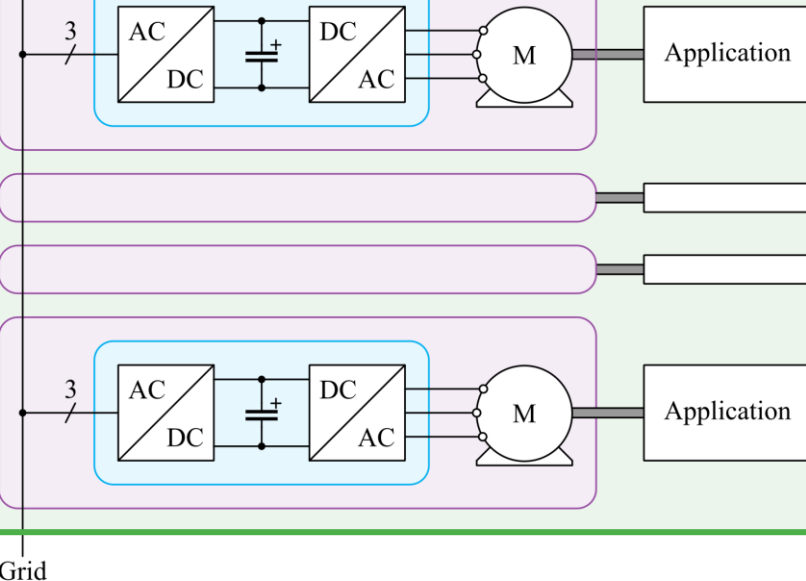

Example: From Gate Drive to Cloud

► **SIEMENS** Smart Inverter Concept

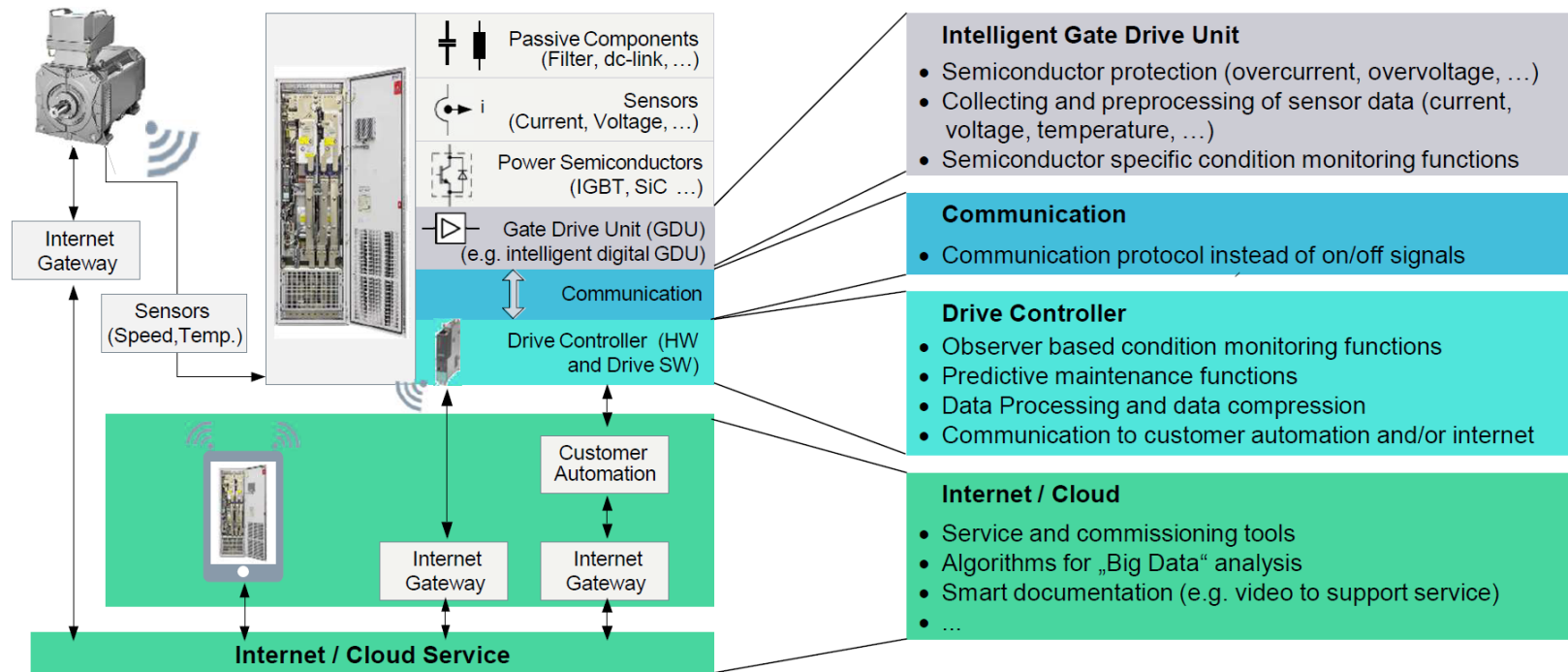

► Utilize high computing power and network effects in the cloud


Example: Wind Park Condition Monitoring

Computing Power

- Scalable computing resources (**cloud**) for resource-intensive tasks



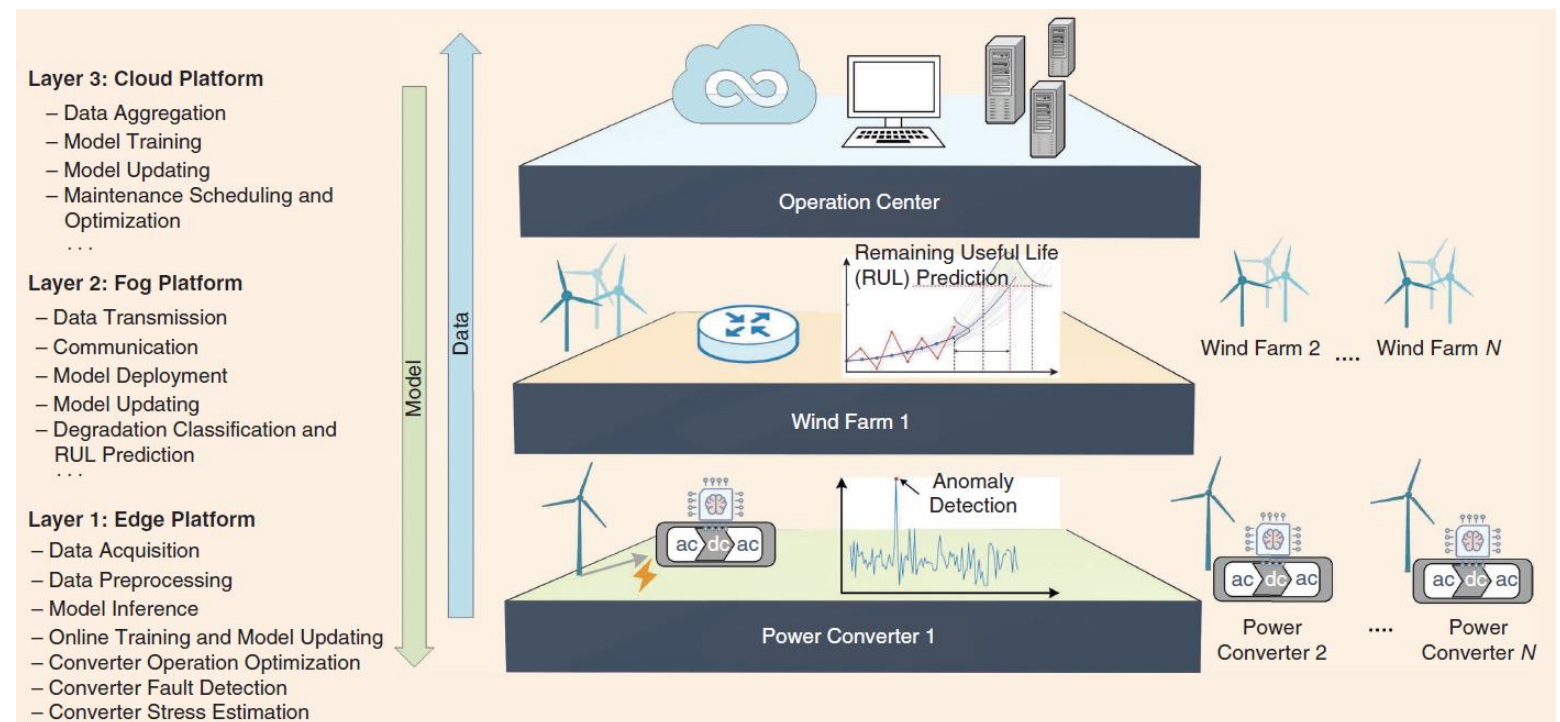- PE controllers as **edge computing** platforms
- PE as piece in a puzzle



S. Zhao and H. Wang, "Enabling data-driven condition monitoring of power electronic systems with artificial intelligence: concepts, tools, and developments," *IEEE Power Electron. Mag.*, vol. 8, no. 1, Mar. 2021.

Example: PE 4.0 as Part of Digital Ecosystems

► **ABB** Ability “Digital Power Train”




► Schneider Electric **EcoStruxure** Innovation At Every Level



Power electronic converters are “pieces in a larger puzzle”

→ **Similar to other IIoT-enabled devices**

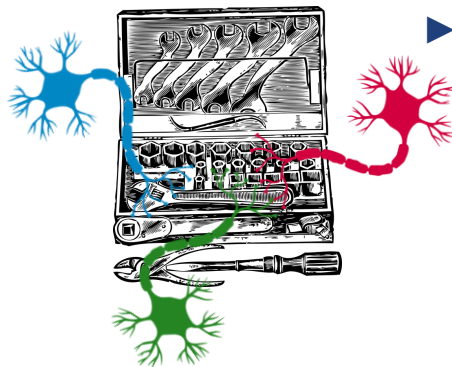Conclusion & Requirements for PE 4.0 Readiness



► AI/ML techniques are one of many means to an end

- Should become **part of an engineer's toolbox**
(as circuit or FEM simulation) → Awareness / training
- Method should follow from the problem to be solved
(not the other way around)
- **Training data** is a key challenge for data-driven methods
(ability to generalize / reliability of predictions)

► Power Electronics 4.0 for Industry 4.0

- **“Just another IIoT-enabled device”**
- Converters act as sensors, sensor hubs, data aggregators, ...
→ Standards for HW/SW integration
- Value generation on the application/business level
(e.g., improved asset management)



► Advanced Sensing Capabilities

- Higher bandwidth/resolution;
memory/CPU/uplink requirements
- Measure additional quantities
(ESR, on-state voltage, ...)
- Utilize “parasitic” physical effects
→ **Smart Components/Passives**




Further Reading

AI/ML Applications in Power Electronics

- ▶ J. O. P. Pinto, B. Ozpineci, and R. Cordero, “**Artificial intelligence applications to power electronics**,” Tutorial at the ECCE USA 2019, Baltimore, MD, USA, Sep. 2019.
- ▶ B. K. Bose, “**Artificial intelligence techniques: How can it solve problems in power electronics?**,” *IEEE Power Electron Mag.*, vol. 7, no. 4, Dec. 2020.
- ▶ S. Zhao, F. Blaabjerg, and H. Wang, “**An overview of artificial intelligence applications for power electronics**,” *IEEE Trans. Power. Electron.*, vol. 36, no. 4, Apr. 2021.

Cognitive Power Electronics

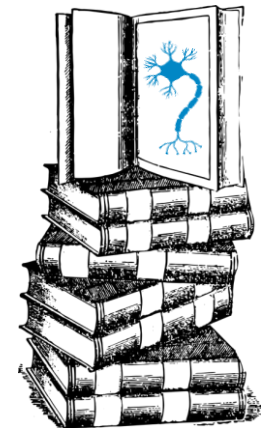- ▶ B. Wunder *et al.*, “**Droop controlled cognitive power electronics for DC microgrids**,” in *Proc. IEEE Int. Telecom. Energy Conf. (INTELEC)*, Broadbeach, Australia, Oct. 2017.
- ▶ G. Roeder, X. Liu, and M. Hofmann, “**Cognitive power electronics for intelligent drive technology**,” in *Proc. Electr. Drives Production Conf. (EDPC)*, Ludwigsburg, Germany, Dec. 2020.



Thank you!

