

Part 4

Experimental Analysis of 1st Gen. 600 V GaN M-BDSs

Jonas Huber, Johann W. Kolar

Power Electronic Systems Laboratory
ETH Zürich

October 10, 2021



Part 4

Experimental Analysis of 1st Gen. 600 V GaN M-BDSs

Jonas Huber, Johann W. Kolar, Neha Nain, Franz Vollmaier


Power Electronic Systems Laboratory
ETH Zürich

October 10, 2021




The Switch: 600 V / 140 mΩ GaN M-BDS 1. Gen. Samples

BDS Realization with Unipolar Devices

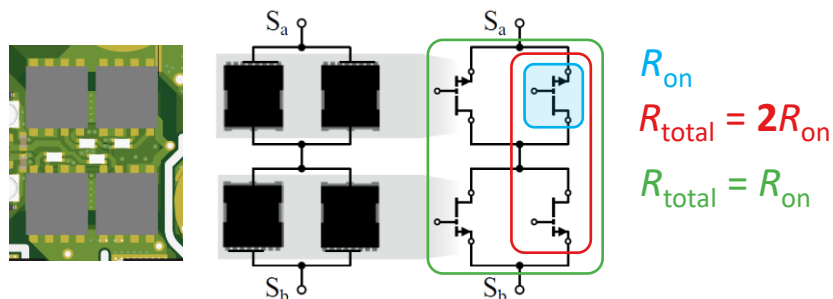

- 4 x Single switch for same R_{on}

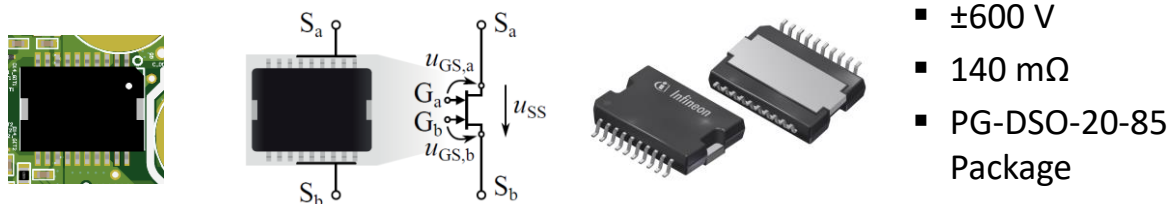
Monolithic Bidirectional Realization (M-BDS)



Package Image Source:
<https://www.infineon.com/cms/en/product/packages/PG-DSO/PG-DSO-20-85/>

GaN M-BDS Internal Structure

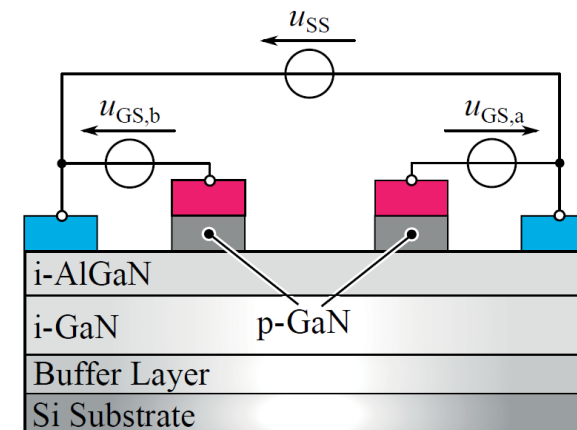- Infineon 600 V CoolGaN™ Technology
Normally-off (Gate Injection Transistor, GIT)
- Two gates (one per blocking direction)
- Internal common-drain configuration






Same chip region used for
blocking both voltage polarities!

The Topologies

GaN/SiC 3-Level T-Type AC-DC PFC Rectifier / DC-AC Inverter


All-GaN AC-AC Current-Source Converter

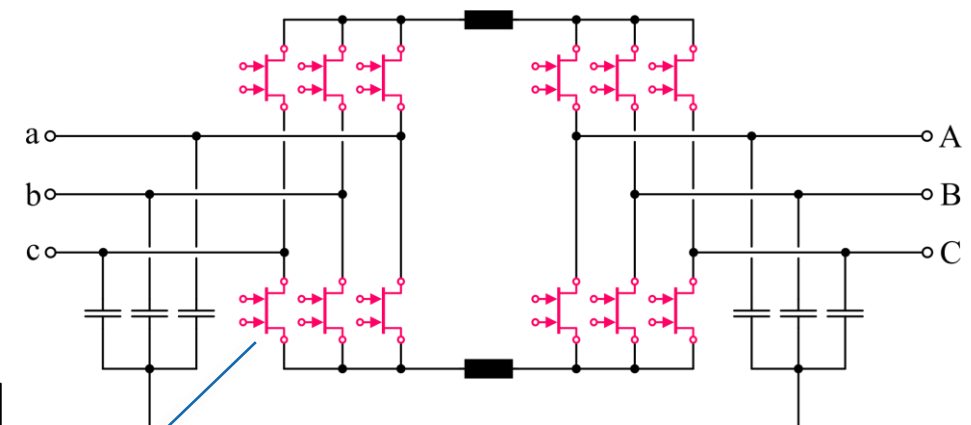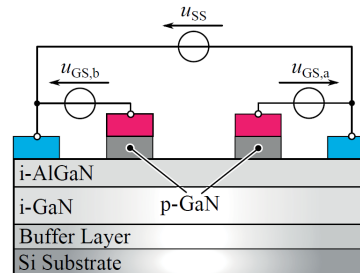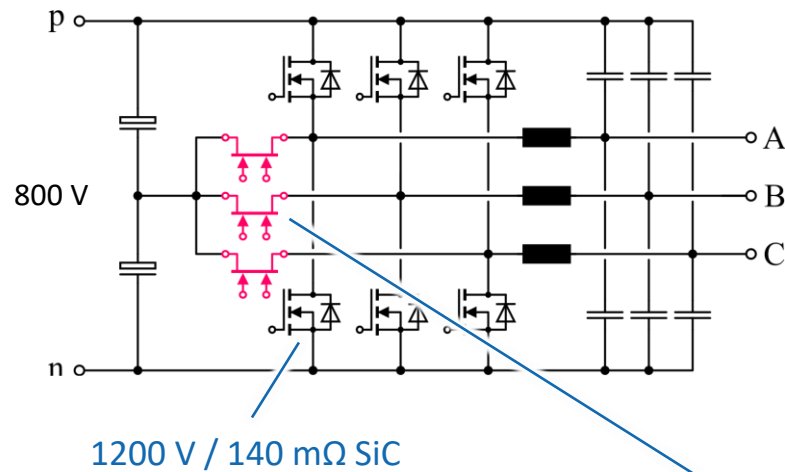

GaN M-BDS Gate Drive Considerations


GaN Gate Injection Transistor (GIT) Gate Behavior

Simplified MOSFET Gate Turn-On

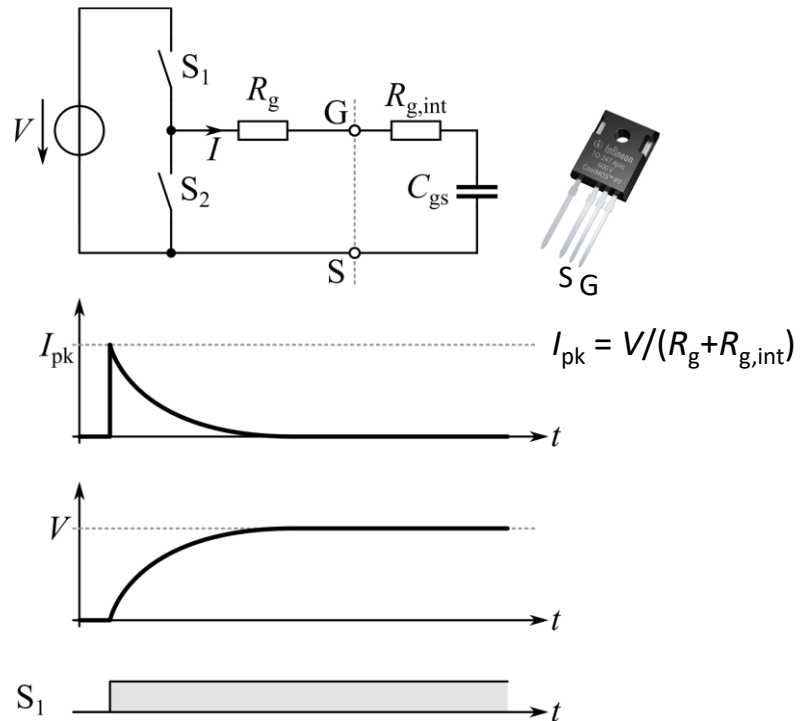

Simplifying assumption: $C_{gs} = \text{const.}$

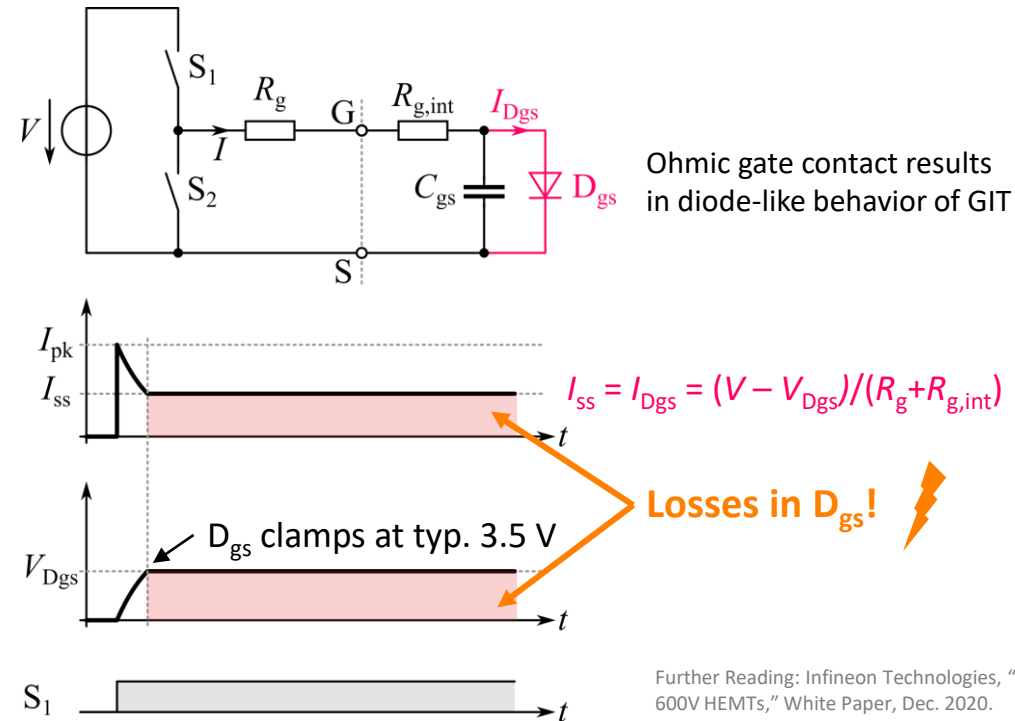Simplified Gate Injection Transistor (GIT) Gate Turn-On




Further Reading: Infineon Technologies, "Gate drive solutions for CoolGaN 600V HEMTs," White Paper, Dec. 2020.

► Requirements for GIT gate drive

- **Small R_g** for fast transients (charging/discharging of C_{gs})
- **Large R_g** during steady-state (small I_{Dgs} of a few 10 mA)

Standard RRC Gate Drive Operating Principle

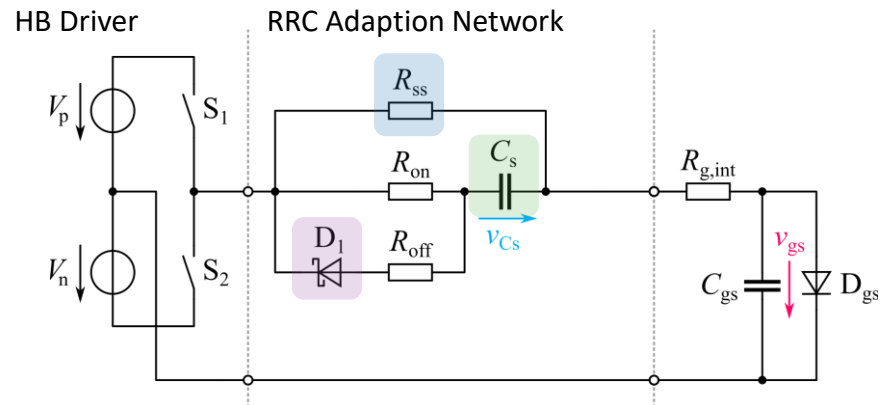
Capacitor to Decouple Transient Low-Impedance Paths



- $C_s \gg C_{gs}$ (typ.): Decoupling of High-Current Paths
- $R_{ss} \gg R_{on}, R_{off}$: Steady-state current (milliamperes)
- D_1 : Separate turn-on/turn-off gate resistors with HB driver

Note: **Dedicated driver ICs** with multiple outputs as alternative

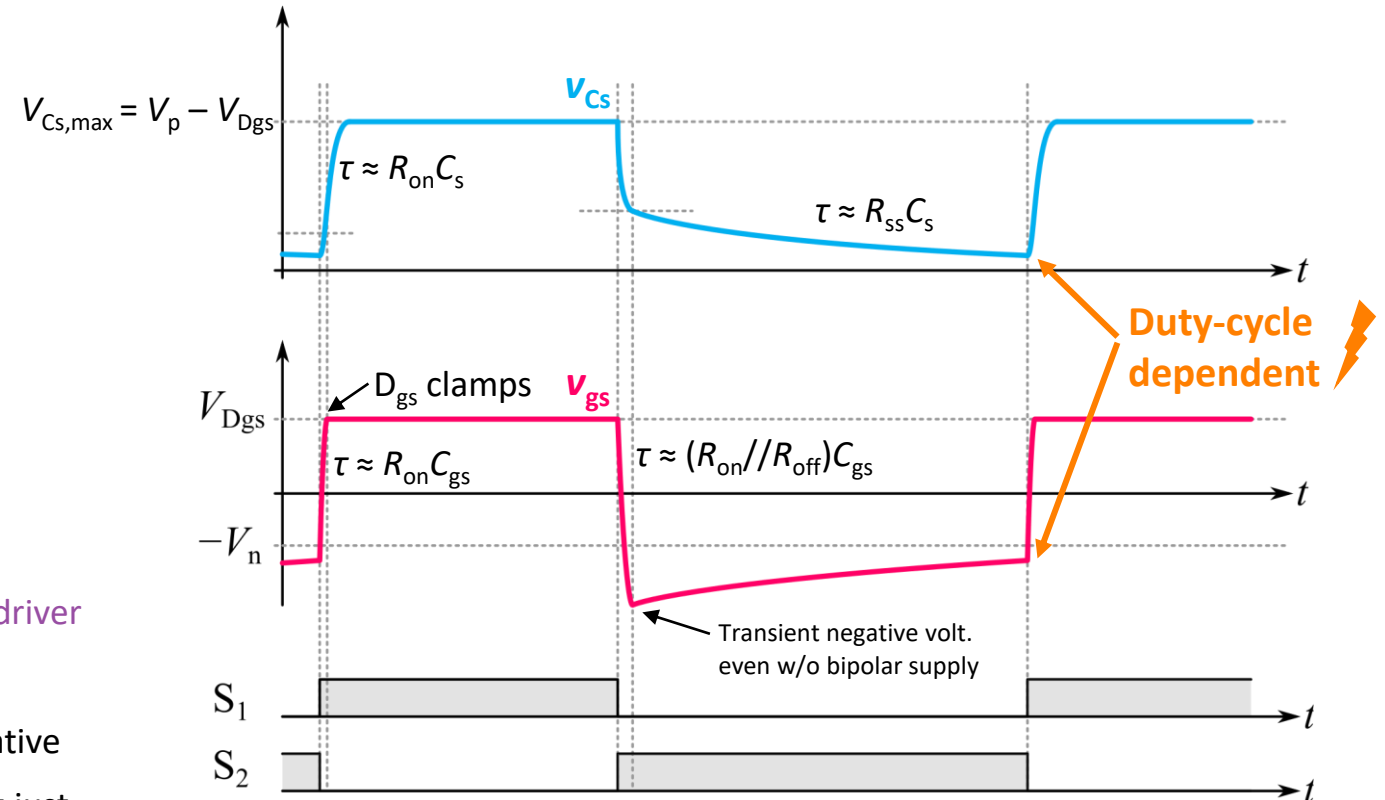Note: **Bipolar supply** to ensure negative v_{gs} at all times (not just transiently; relevant for CSI commutation cells)




Assumptions: $R_{g,int} = 0 \Omega$, $C_s \gg C_{gs}$, simplified gate model ($C_{gs} = const.$)

Note: unipolar supply possible; bipolar supply for better robustness against parasitic turn-on in current-source converter commutation cells (see later).


Advanced RRC Gate Drive Operating Principle

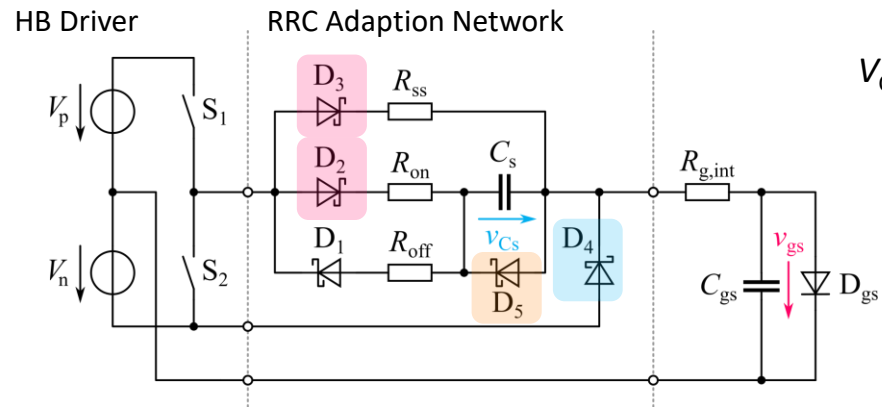Eliminating the Duty-Cycle Dependency of Dynamics



- D_2 : Prevents full discharge of C_s via R_{ss}
- D_3 : Decouple R_{ss} during off-state
- D_4 : Discharge path for C_s during off-state (via R_{off} and D_1) and clamping of gate to negative supply voltage
- D_5 : Prevents negative voltage across C_s (e.g., due to miller current or other distortions; inactive during normal operation)



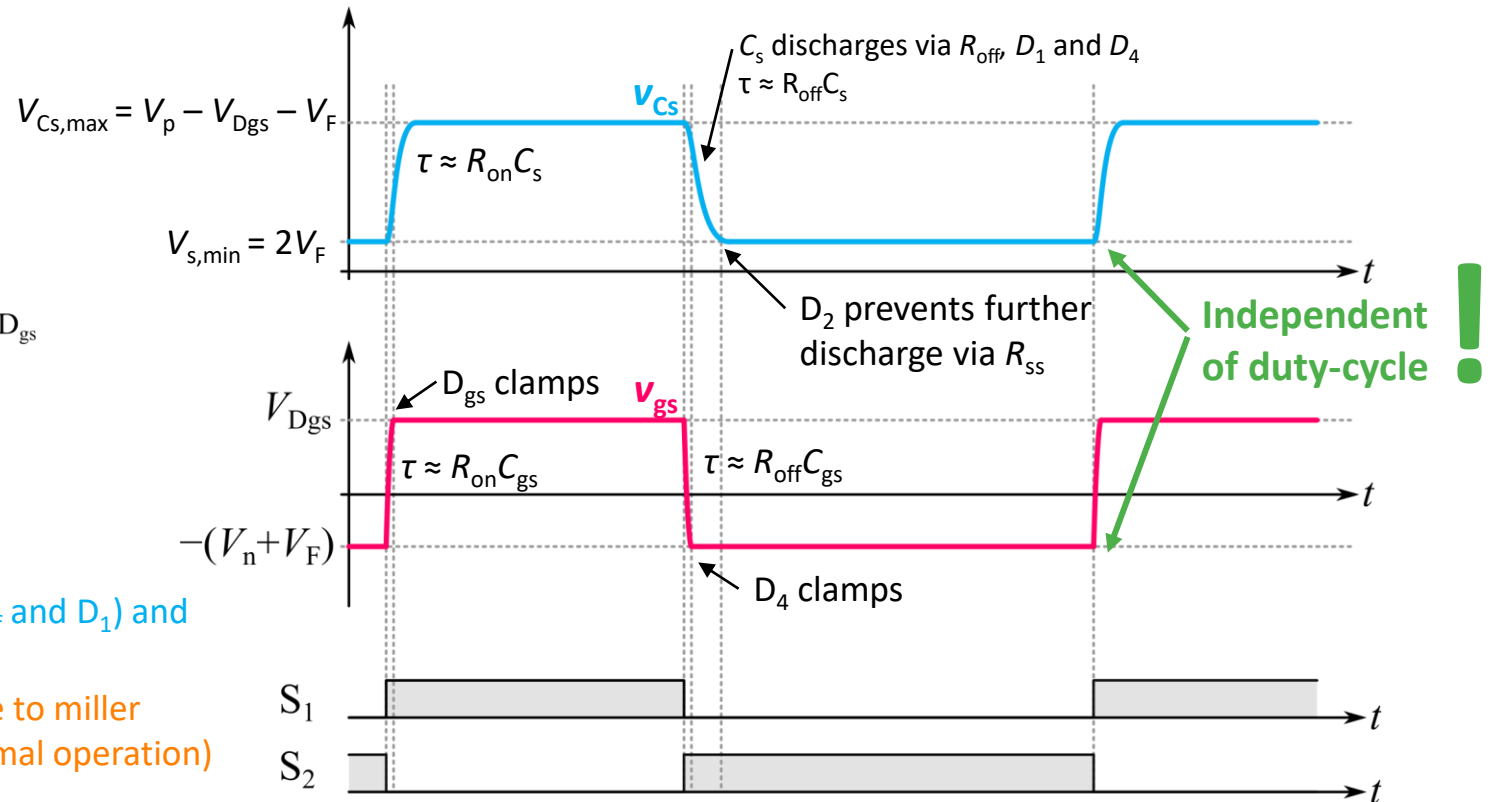
- Straightforward option with standard HB driver IC and a few Schottky diodes



Assumptions: $R_{g,int} = 0 \Omega$, $C_s \gg C_{gs}$, simplified gate model ($C_{gs} = const.$)

Advanced RRC Gate Drive for M-BDS: Realization

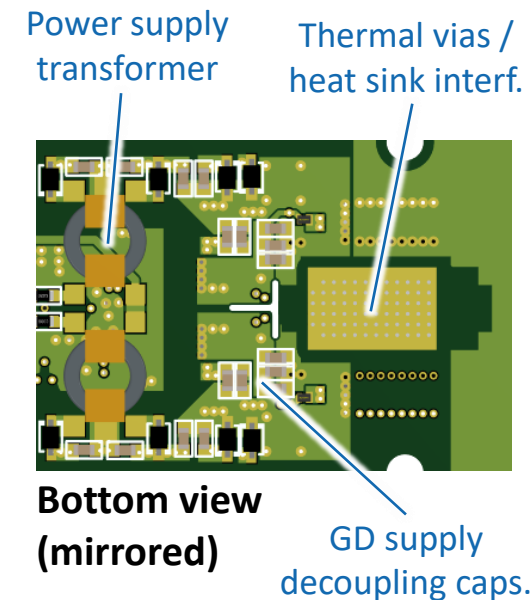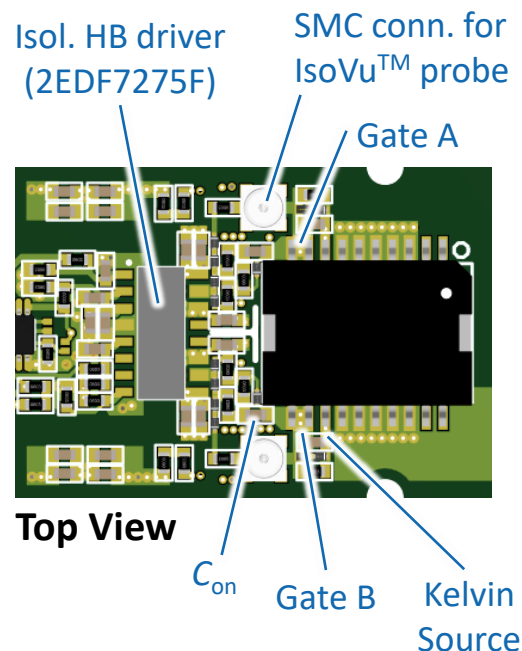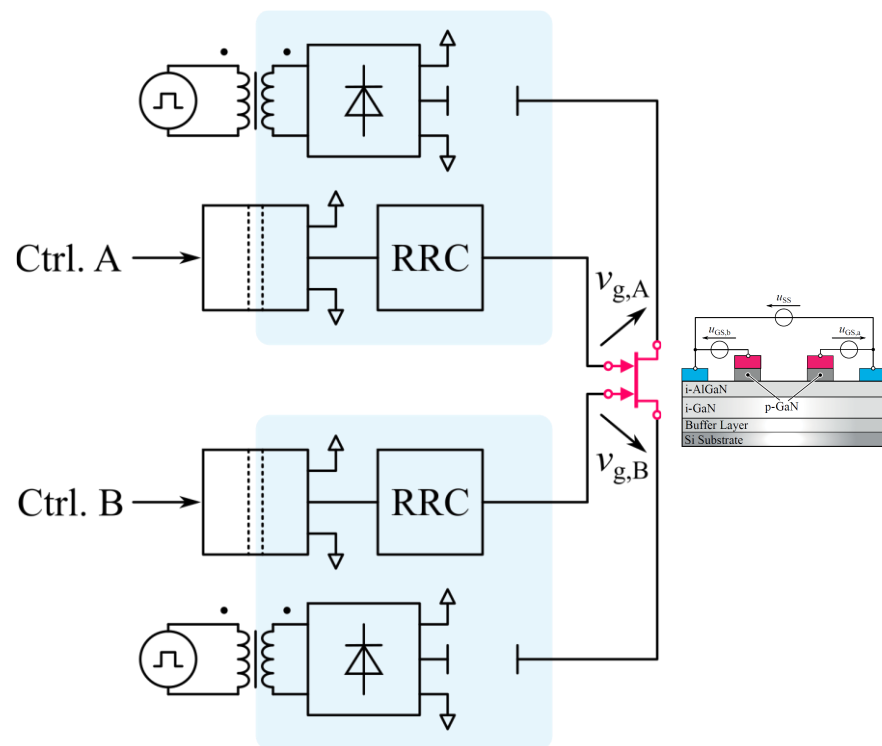- ▶ Two gates per M-BDS / Two isolated power supplies / Two control signals
- ▶ Mostly vertical gate loop (ca. 8...10 nH incl. package) / Adv. RRC network on TOP / HB driver supply decoupling on BOT




Remark: Integration of gate drive → Significant reduction of PCB area!



Advanced RRC Gate Drive for M-BDS: Layout / Measurements

- ▶ Two gates per M-BDS / Two isolated power supplies / Two control signals
- ▶ Mostly vertical gate loop (ca. 8...10 nH incl. package) / Adv. RRC network on TOP / HB driver supply decoupling on BOT

Measured GaN M-BDS v_{gs}

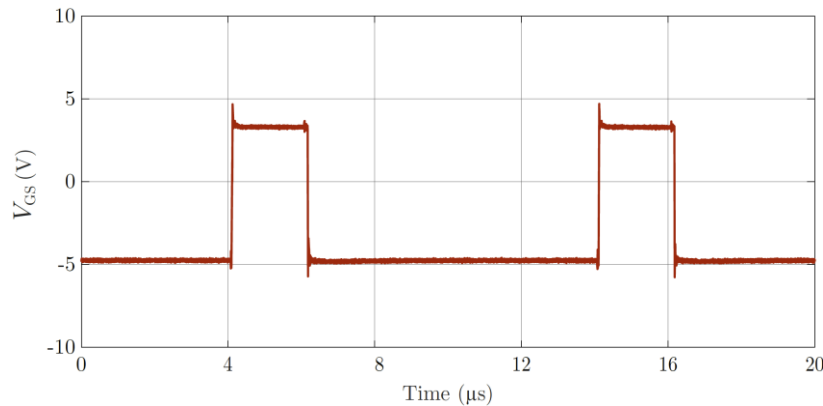

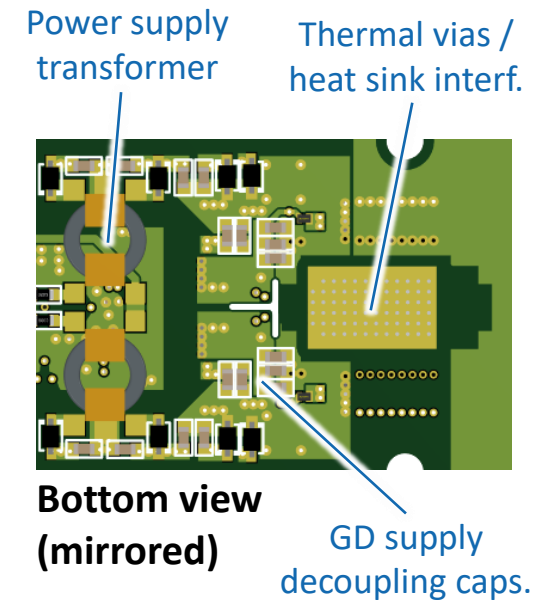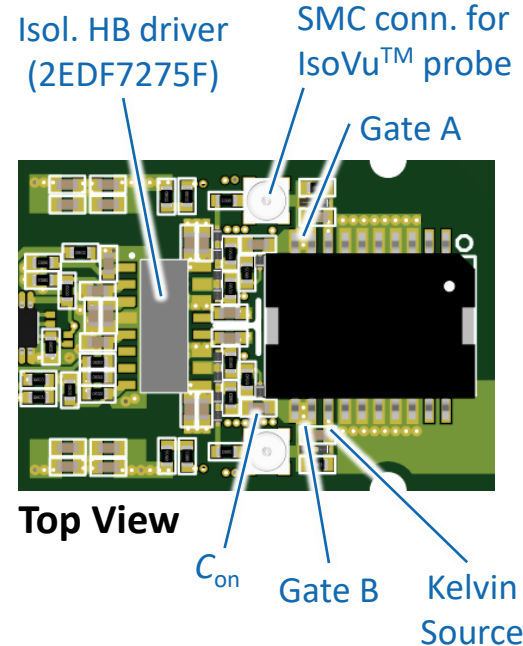$V_p = 8 \text{ V}$, $V_n = 5 \text{ V}$
 $R_{on} = 5 \text{ } \Omega$, $R_{off} = 4.7 \text{ } \Omega$, $C_s = 2.2 \text{ nF}$, $R_{ss} = 680 \text{ } \Omega$




Remark: Integration of gate drive → Significant reduction of PCB area!

3-Level T-Type Inverters/Rectifiers with GaN M-BDSs

- ! Details => Paper @ ECCE USA 2021
- F. Vollmaier, N. Nain, J. Huber, J. W. Kolar, K. K. Leong, and B. Pandya, “Performance evaluation of future T-Type PFC rectifier and inverter systems with monolithic bidirectional 600 V GaN switches.”


3-Level T-Type (TT) Main Converter Stage

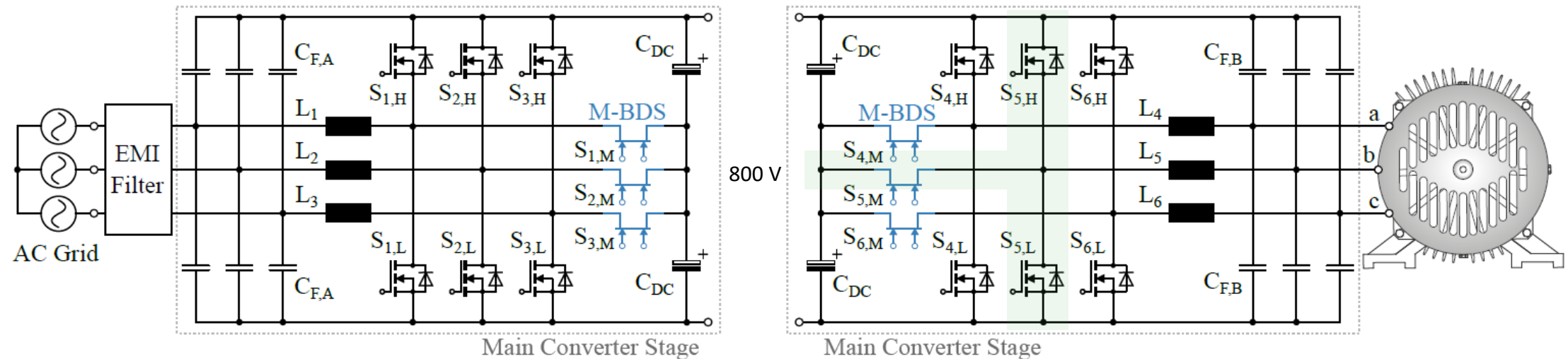- ▶ Bidirectional voltage-source AC-DC or DC-AC conversion / **Basic building block** for PFC rectifiers or motor drive inverters
- ▶ Phase-modular DC-link-referenced first LC-filter stage => DM and CM filtering





- ▶ **Three-level bridge-leg** via connection to DC-link midpoint: **bidirectional conduction & bipolar blocking** => **M-BDS**
- ▶ 800 V DC / $S_{x,H}$, $S_{x,L}$: 1200 V, 140 mΩ SiC MOSFET / $S_{x,M}$: **600 V, 140 mΩ GaN M-BDS**

3-Level TT Bridge-Leg Commutation Cells

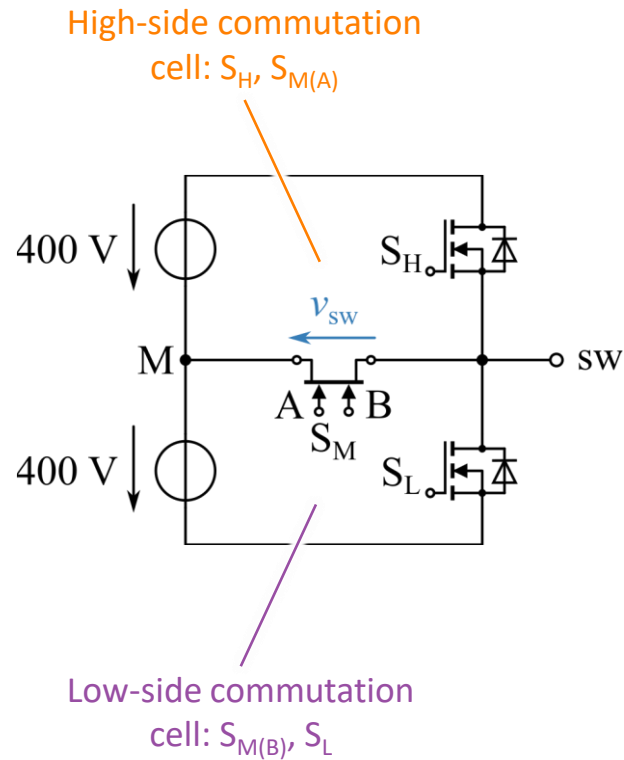



Positive Output Voltage

→ High-side commutation cell active

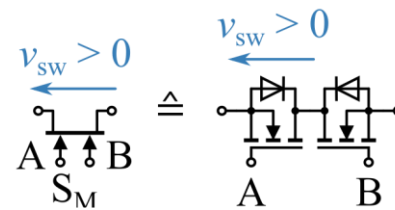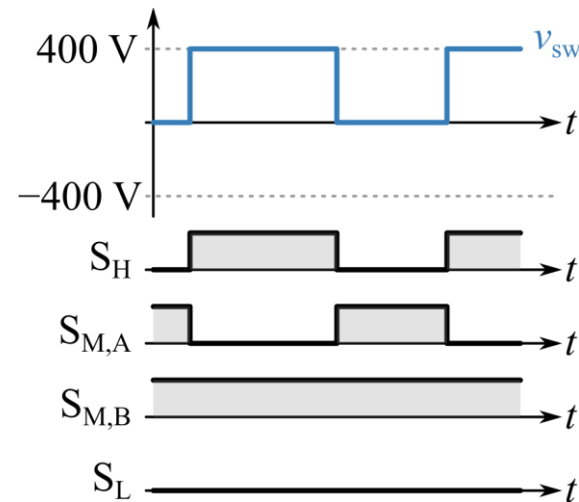



Negative Output Voltage

→ Low-side commutation cell active

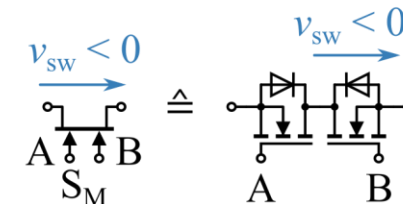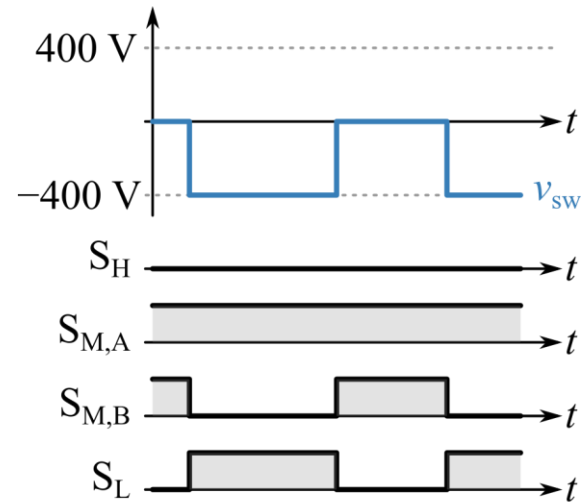


3-Level TT Bridge-Leg Evaluation Board

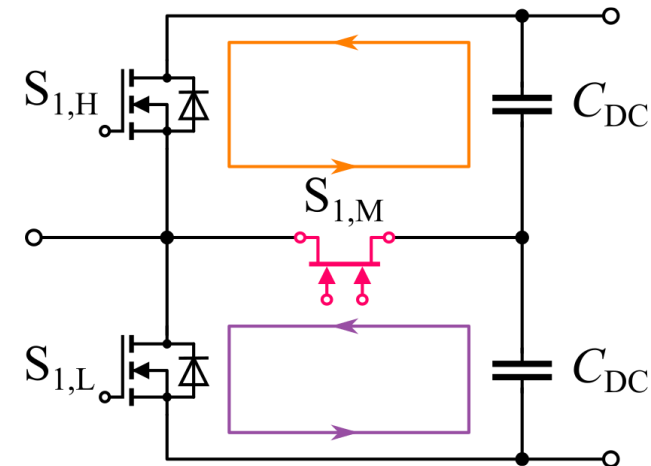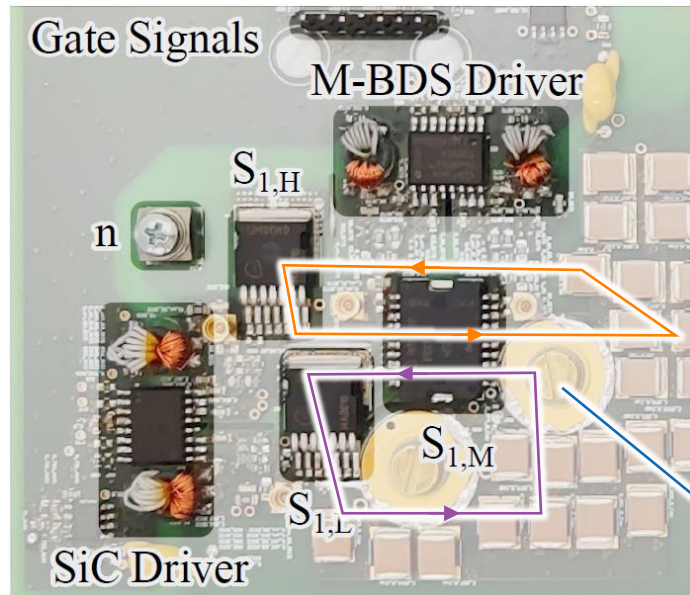- ▶ 800 V DC / $S_{x,H}$, $S_{x,L}$: 1200 V, 140 m Ω SiC MOSFET (IMBG120R140M1H) / $S_{x,M}$: 600 V, 140 m Ω GaN M-BDS
- ▶ Two commutation loops: High-side / Low-side / Commutation inductance ca. 15 nH
- ▶ Advanced RRC gate drive with HB driver (2EDS8265HXUMA1) for M-BDS




- ▶ Cooling through PCB (thermal vias) / Top-side cooled packages would facilitate improved layouts

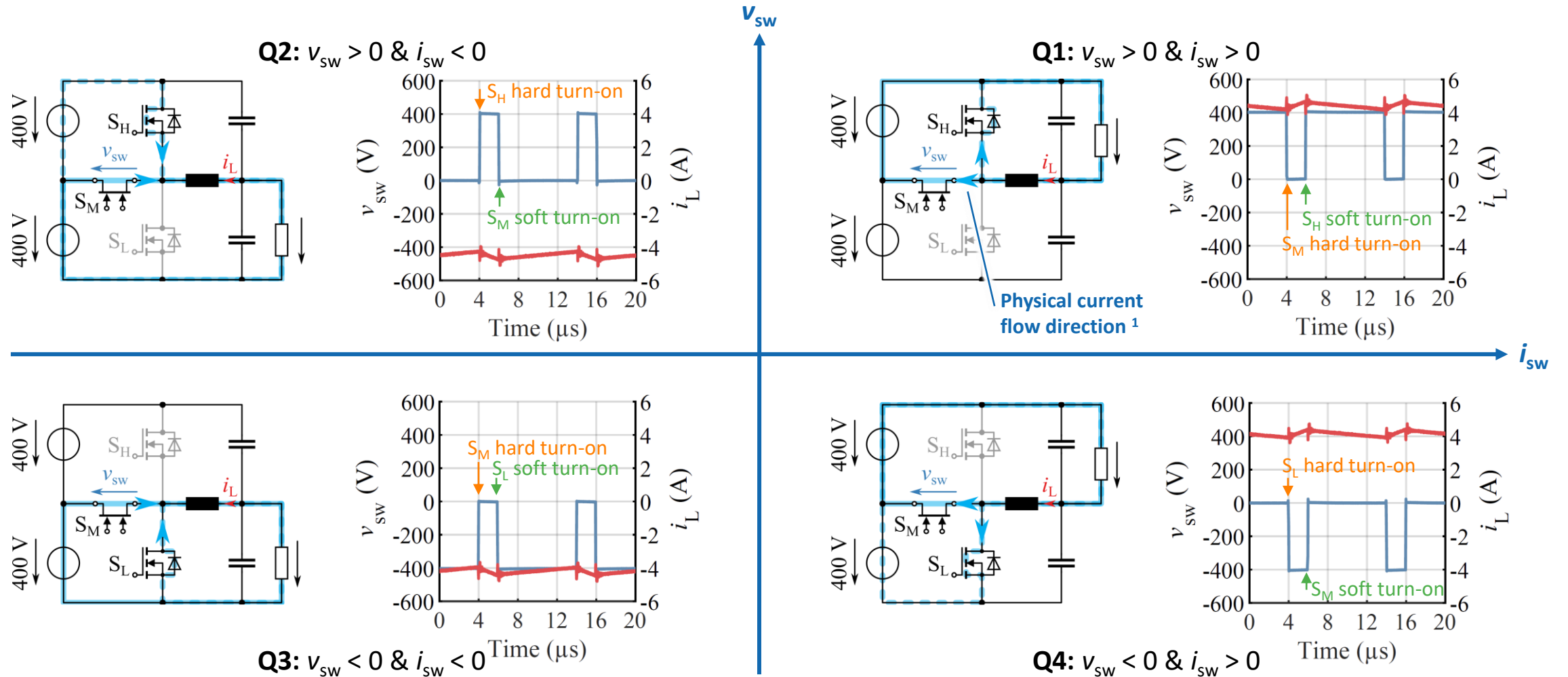Continuous M-BDS Operation at ± 400 V in CCM





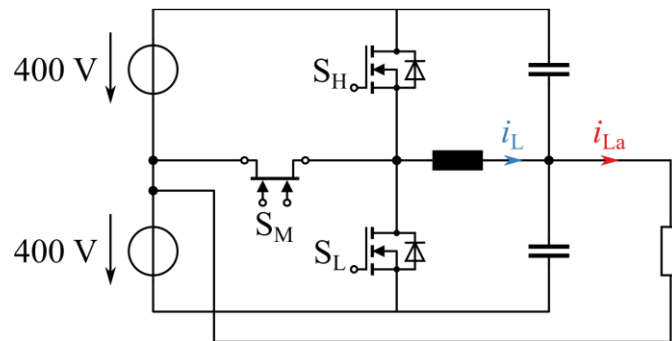Remark: CCM and TCM Operation of TT Bridge-Leg




Exemplary simulations for
800 V DC and 2 kW.


CCM: Continuous Conduction Mode

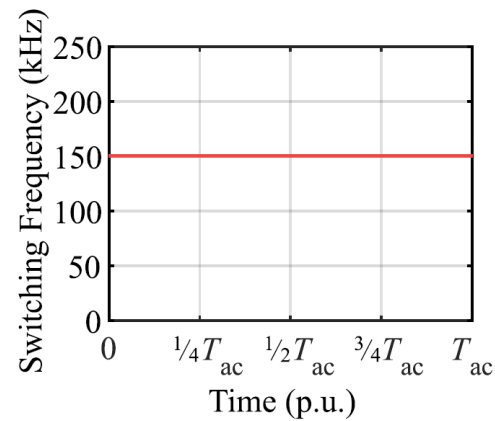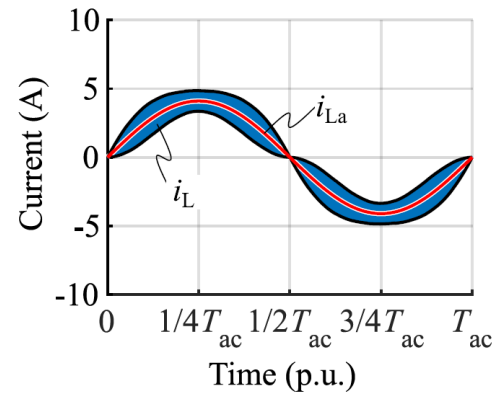

TCM: Triangular Current Modulation

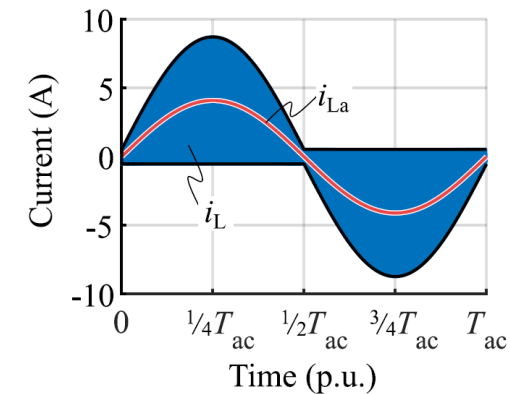


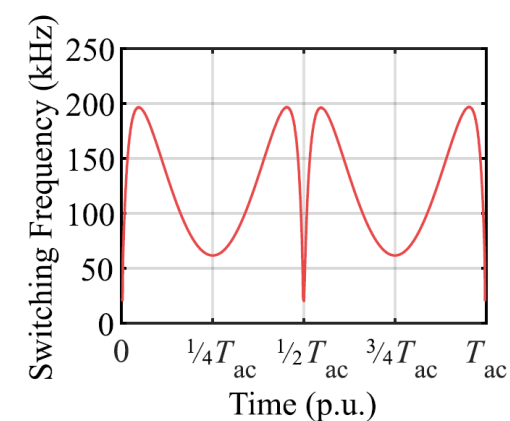Zero-Voltage Switching
(ZVS) for all transitions





Variable sw. frequency

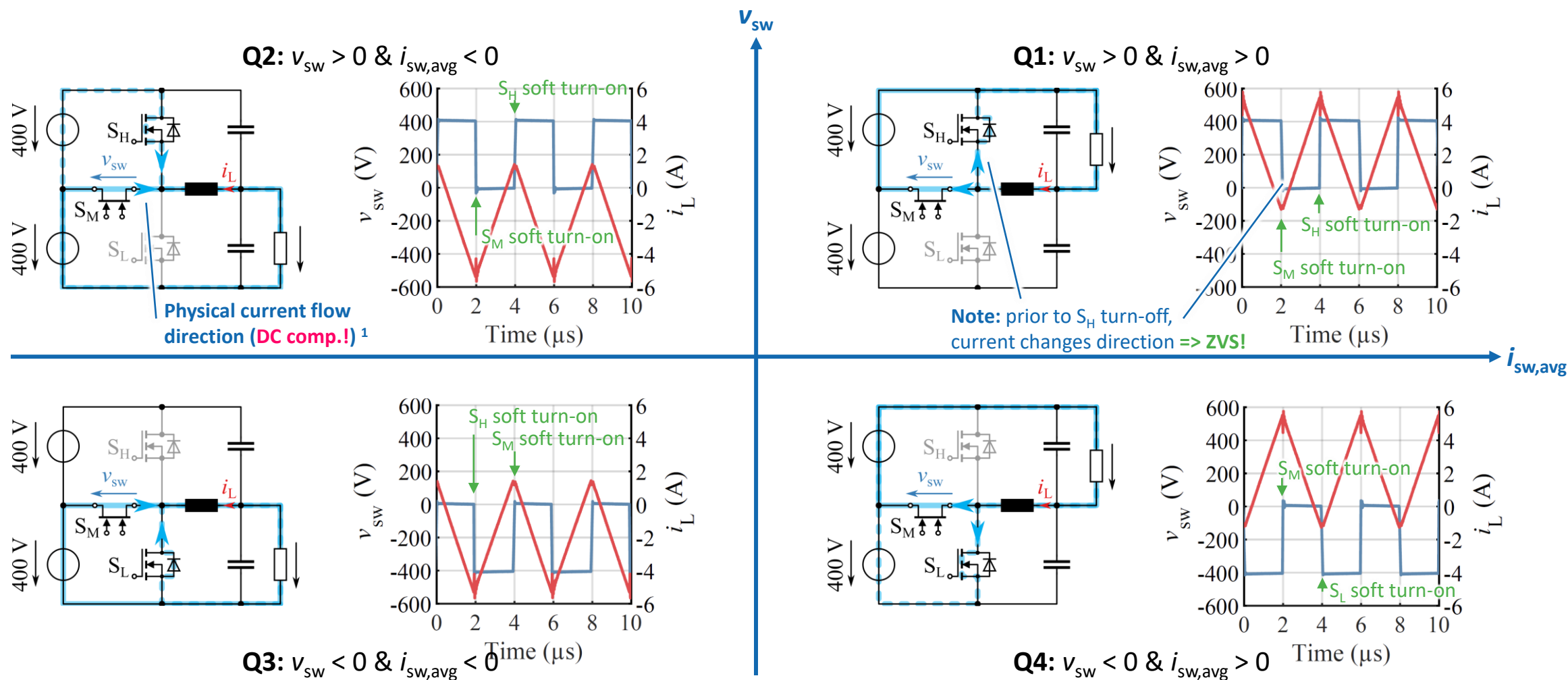Continuous M-BDS Operation at ± 400 V with TCM (Soft-Switching)



Transient Calorimetric Loss Measurement: Principle (1)

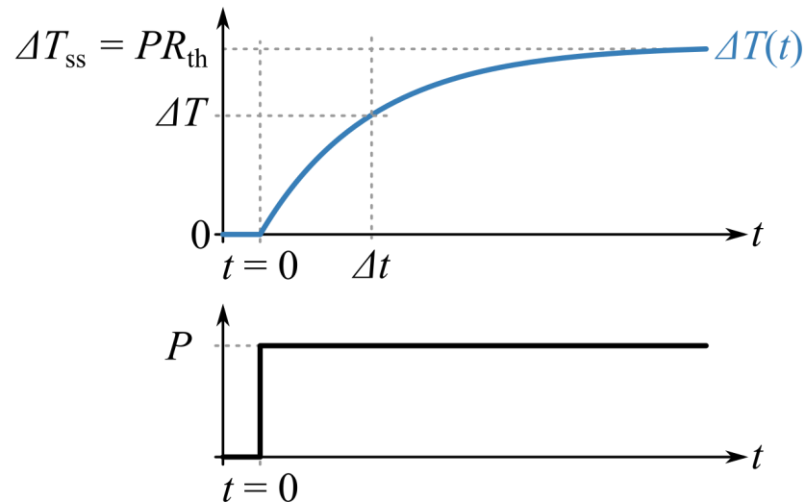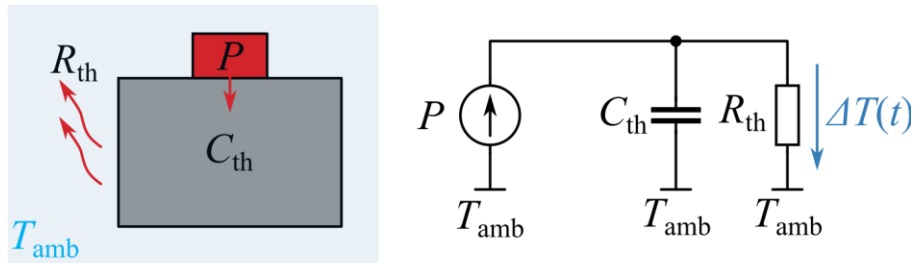- Constant power dissipation into metal block



Step 1: Calibration with Known DC Power Accurate electrical measurement

- Record $\Delta T(\Delta t)$ for several (at least two) known powers
- Fit model and extract model parameters C_{th} and R_{th}

$$\Delta T(\Delta t) = PR_{th} \cdot \left(1 - e^{-\frac{\Delta t}{R_{th}C_{th}}}\right)$$

Step 2: Measurement of Unknown Power Dissipation

- Measure time Δt to reach temperature difference ΔT
- Use calibrated model to calculate power dissipation



$$\Rightarrow P(\Delta T, \Delta t) = \frac{\Delta T}{R_{th} \cdot \left(1 - e^{-\frac{\Delta t}{R_{th}C_{th}}}\right)}$$

Alternative for Step 2

- Record $\Delta T(\Delta t)$ for unknown power dissipation P'
- Fit model with known R_{th} and C_{th} to identify P'

Transient Calorimetric Loss Measurement: Principle (2)

Half-Bridge with Identical Switches

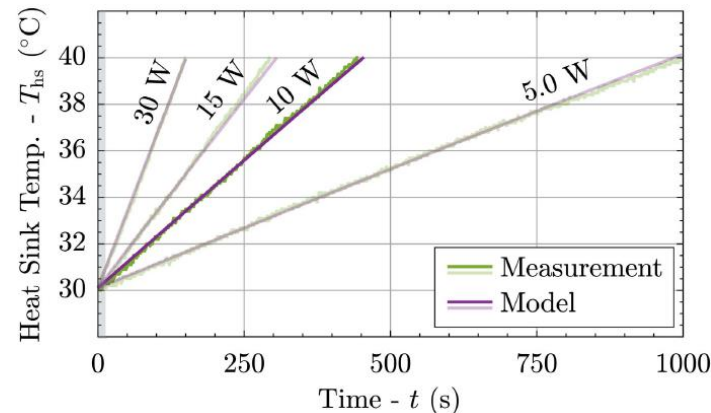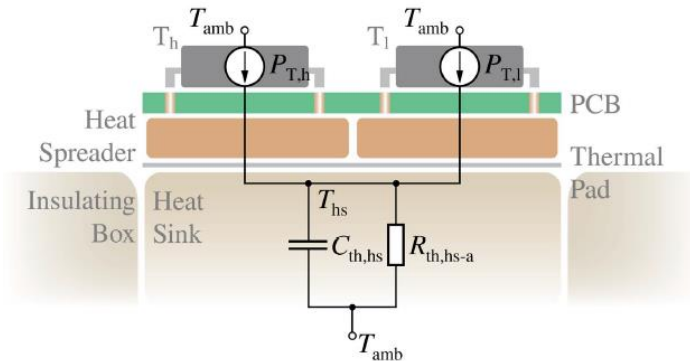

M. Guacci et al., "Experimental characterization of silicon and gallium nitride 200 V power semiconductors for modular multi-level converters using advanced measurement techniques," IEEE J. Emerg. Sel. Topics Power Electron., vol. 8, no. 3, pp. 2238–2254, Sep. 2020.

Note: Heat sink size (C_{th}) follows from desired temperature rise (resolution), measurement time, and power dissipation

Switching Loss Extraction

- Calorimetric loss meas. gives *total* losses
- Conduction losses can be calculated:

$$P_{\text{cond}} = \overbrace{R_{\text{ds(on)}}}^{\text{From calibration}} (\overbrace{P_{\text{total}}}^{\text{Proxy for junction temp.}}) \cdot I_{\text{rms}}^2$$

- Switching energies follow from switching frequency

$$P_{\text{sw}} = P_{\text{total}} - P_{\text{cond}}$$

$$E_{\text{sw}} = E_{\text{on}} + E_{\text{off}} = \frac{P_{\text{sw}}}{f_s} \quad (\text{for CCM})$$


Half-bridge switching energy dissipation per switching period

Soft-Switching Losses

- $E_{\text{sw}} = 2E_{\text{off}}$ for TCM
- Direct & accurate measurement of **residual soft-switching losses!**


TT Bridge-Leg Switching Loss Characterization: Method (1)

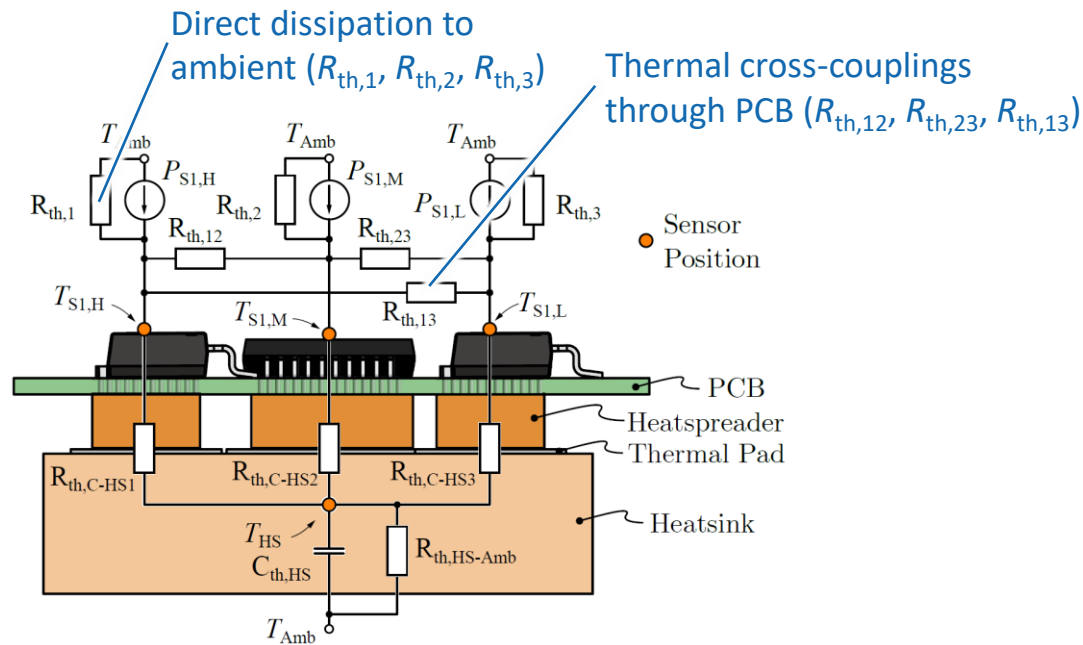- Different device types (SiC, M-BDS) require loss separation: **measure individual case temperatures** ($T_{S1,H}$, $T_{S1,M}$, $T_{S1,L}$) and T_{HS}



- Thermal network with 11 parameters
- Calibration with DC power injection & particle swarm fit (MATLAB)


Calibration Example

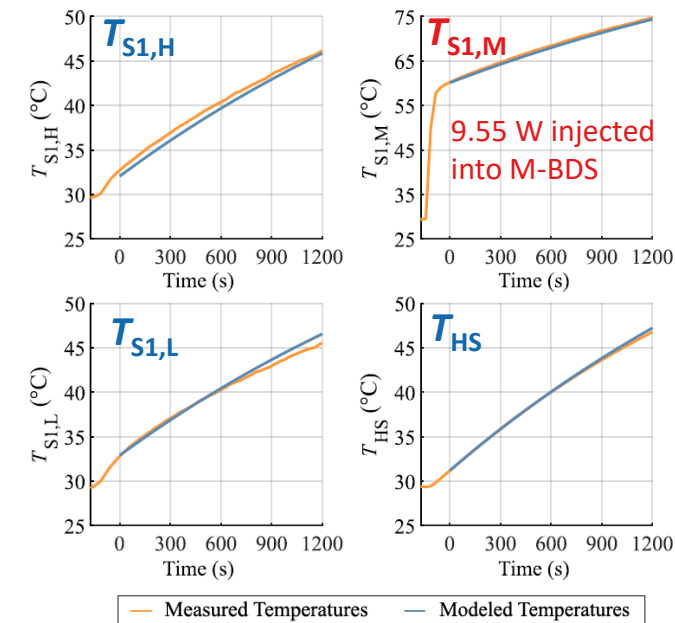


- Note: initial, fast transient ignored (therm. cap. of switches, PCB, heat spreaders, etc.)

TT Bridge-Leg Switching Loss Characterization: Method (2)

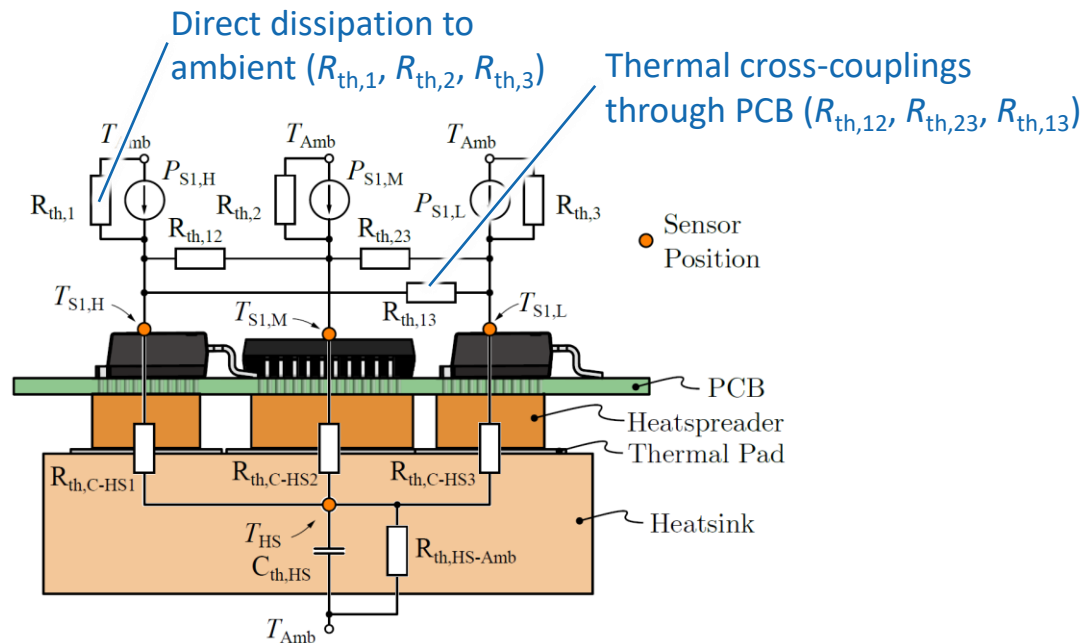- Different device types (SiC, M-BDS) require loss separation: **measure individual case temperatures** ($T_{S1,H}$, $T_{S1,M}$, $T_{S1,L}$) and T_{HS}



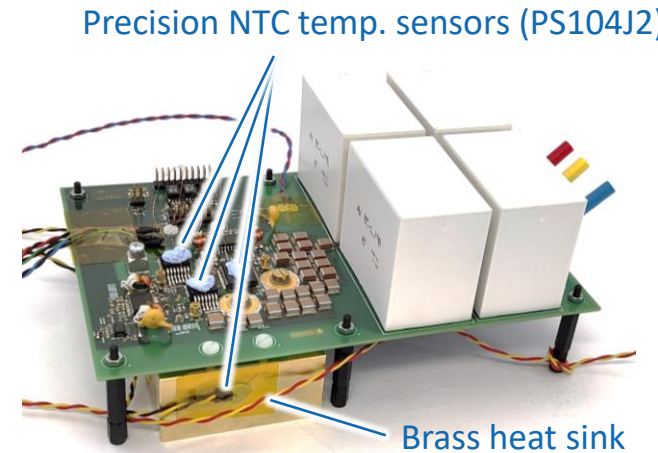- Thermal network with 11 parameters
- Calibration with DC power injection & particle swarm fit (MATLAB)




Loss Extraction with Calibrated Model (Example):

$$P_{S1,H} = \underbrace{\frac{T_{S1,H} - T_{Amb}}{R_{th,1}}}_{\text{Direct to ambient}} + \underbrace{\frac{T_{S1,H} - T_{S2,H}}{R_{th,12}} + \frac{T_{S1,H} - T_{S3,H}}{R_{th,13}}}_{\text{Cross couplings}} + \underbrace{\frac{T_{S1,H} - T_{HS}}{R_{th,C-HS1}}}_{\text{To heat sink}}$$



TT Bridge-Leg Switching Loss Characterization: Results

Calibration Data / Accuracy

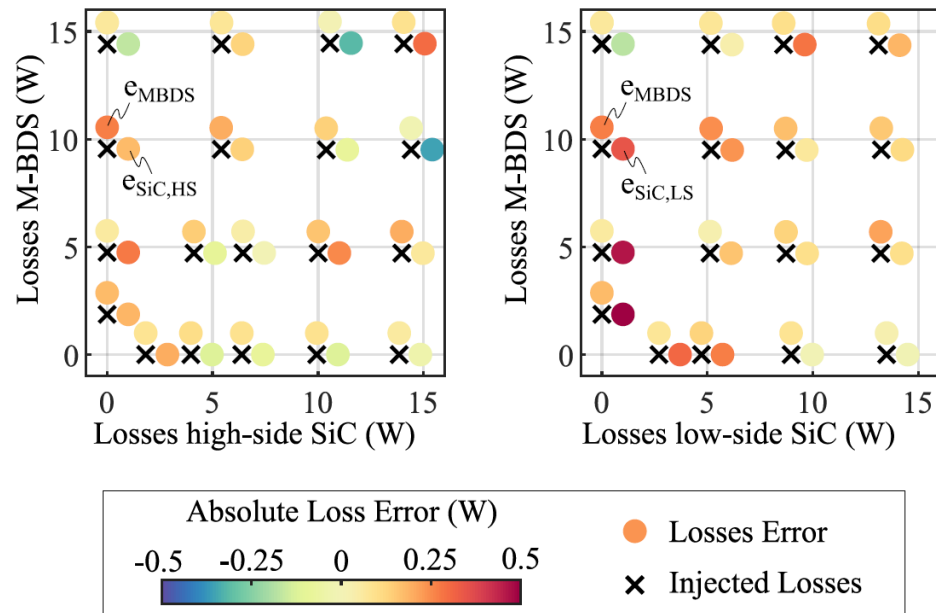- Injected DC power vs. calorimetric measurement




Measured Hard- and Soft-Switching Losses

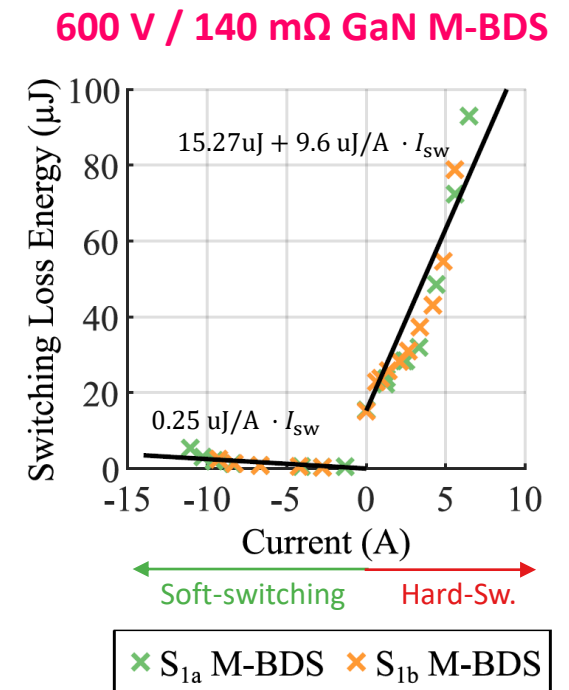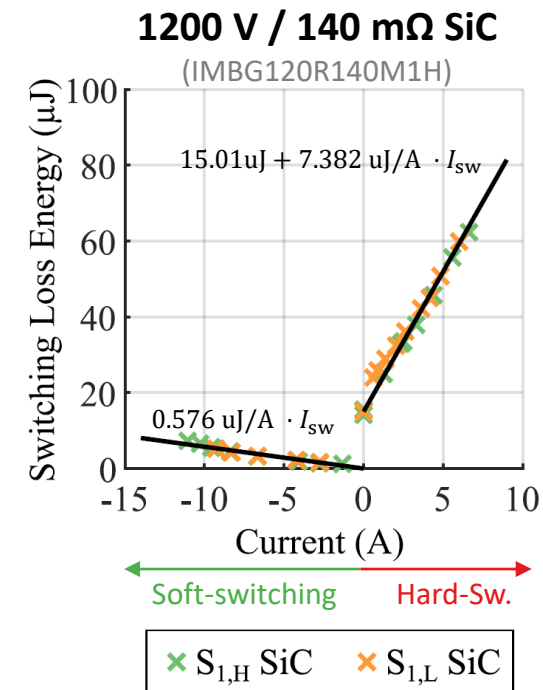

Performance Evaluation of TT Main Converter Stage: CCM Designs


TT Main Converter Stage

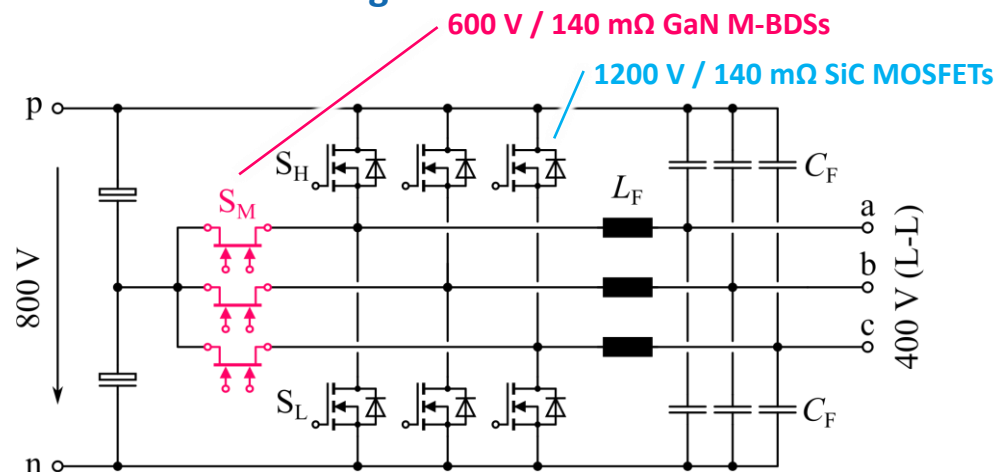


Specifications / Modeling

- $T_j = 125\text{ }^{\circ}\text{C}$, $T_{\text{amb}} = 45\text{ }^{\circ}\text{C}$ / heat sink volume: CSPI = 15 W/(dm³K)
- $\Delta i_{L_F,pp} = 30\%$ (CCM), $\Delta v_{C_F,pp} = 2\%$,
- Pareto-optimal inductor designs (N87 or KoolMu)
- Inverter or rectifier designs with $\cos\phi = \pm 1$

CCM Rectifier Designs

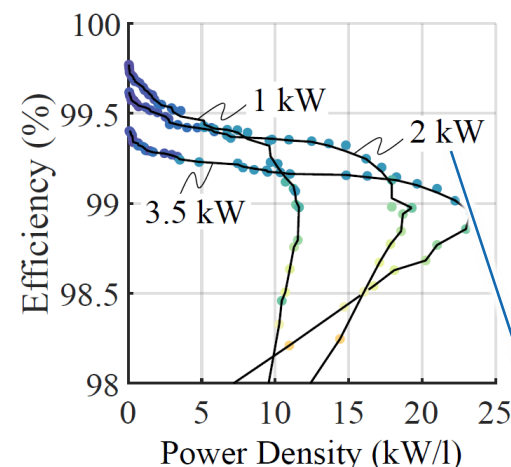


CCM Inverter Designs

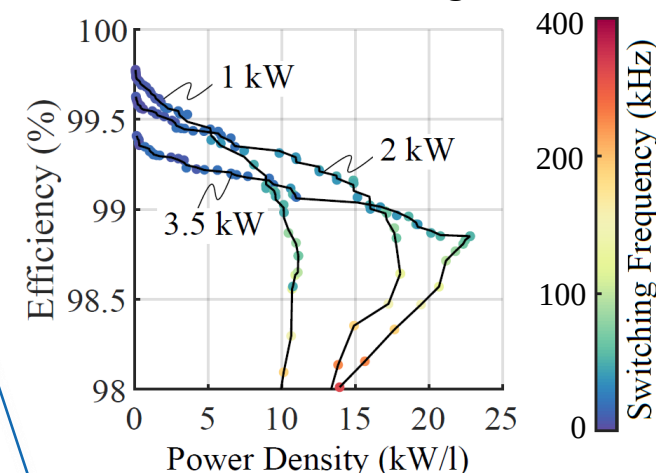

Design Power

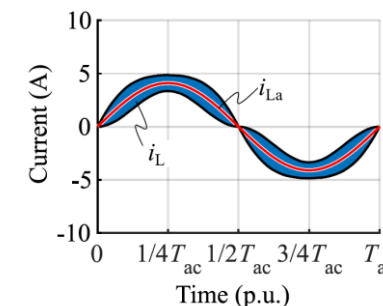- Sweet spot at 2 kW design power:
 $\eta > 99\%$ at $\rho > 15\text{ kW/dm}^3$




Further Details => Paper @ ECCE USA 2021

F. Vollmaier, N. Nain, J. Huber, J. W. Kolar, K. K. Leong, and B. Pandya,
"Performance evaluation of future T-Type PFC rectifier and inverter
systems with monolithic bidirectional 600 V GaN switches."

Performance Evaluation of TT Main Converter Stage: TCM Designs


TT Main Converter Stage

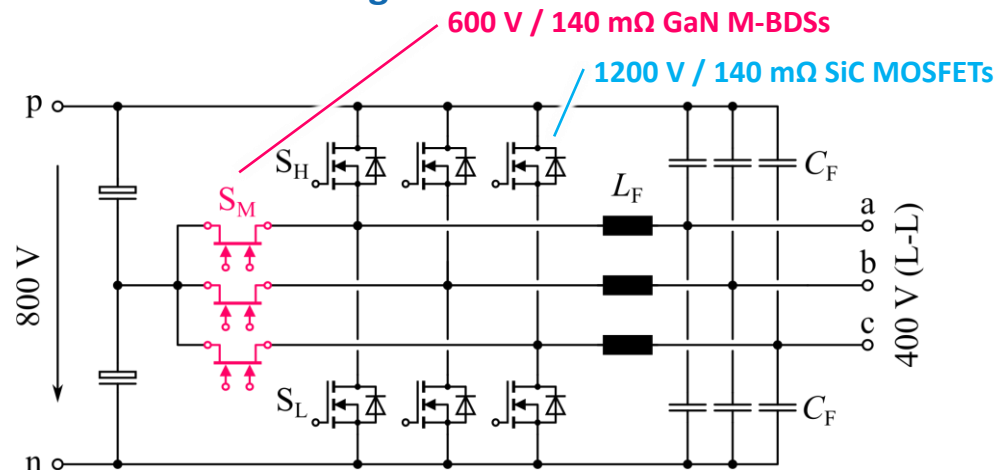


Specifications / Modeling

- $T_j = 125\text{ °C}$, $T_{amb} = 45\text{ °C}$ / heat sink volume: CSPI = 15 W/(dm³K)
- $\Delta i_{LF,pp} = 30\%$ (CCM), $\Delta v_{CF,pp} = 2\%$,
- Pareto-optimal inductor designs (N87 or KoolMu)
- Inverter or rectifier designs with $\cos\phi = \pm 1$


TCM Rectifier Designs

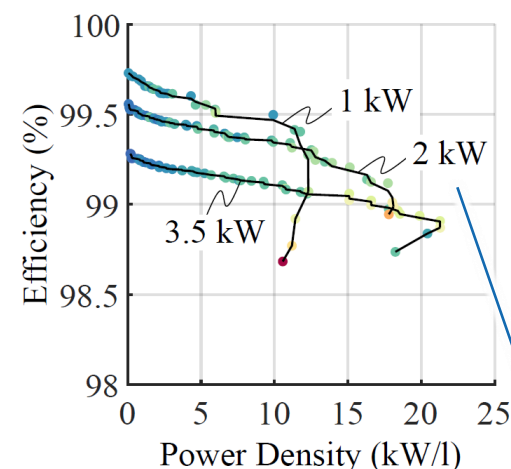

TCM Inverter Designs

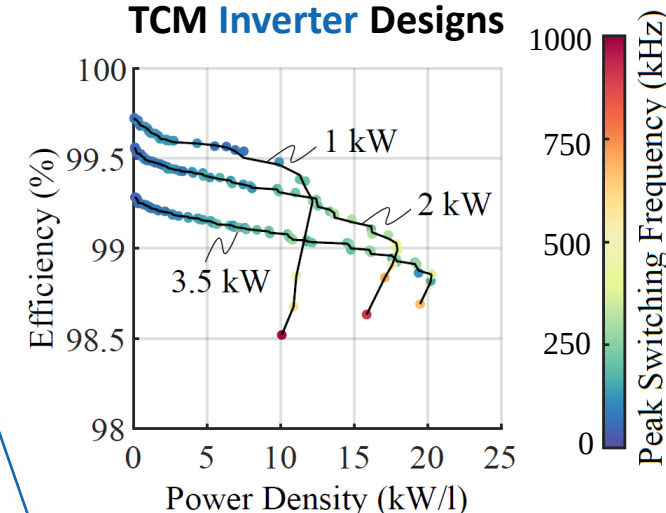

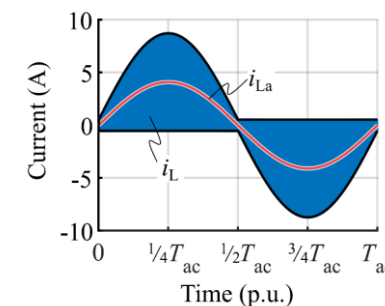- TCM favorable for lower design powers, e.g., 1 kW




Further Details => Paper @ ECCE USA 2021

F. Vollmaier, N. Nain, J. Huber, J. W. Kolar, K. K. Leong, and B. Pandya,
"Performance evaluation of future T-Type PFC rectifier and inverter
systems with monolithic bidirectional 600 V GaN switches."

AC/AC Current-Source Converters with M-BDSs


M-BDS Commutation Cell for AC-AC CSC and DMC

AC-AC Current-Source Converter (CSC)

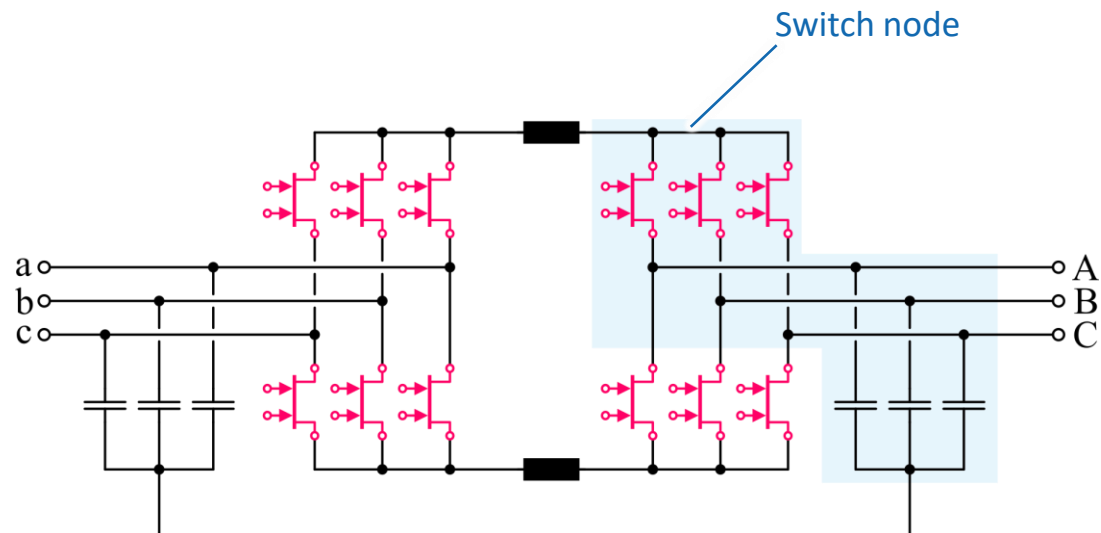

▶ 4 x Basic Commutation Cell







AC-AC Direct Matrix Converter (DMC)

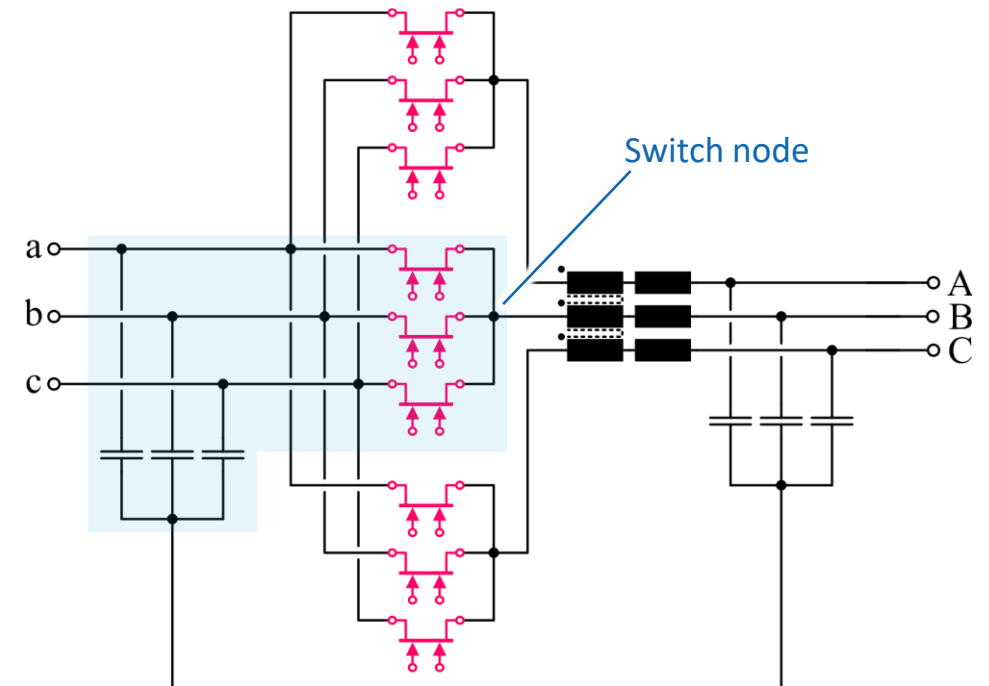

▶ 3 x Basic Commutation Cell

M-BDS Commutation Cell Test PCB: Commutation Loops

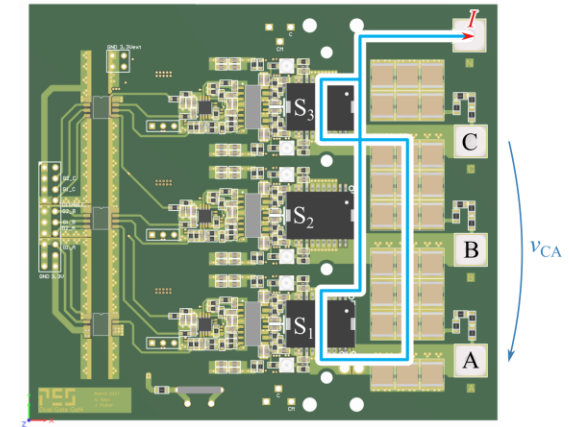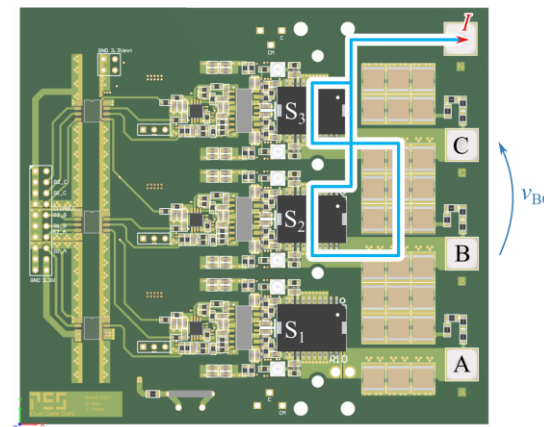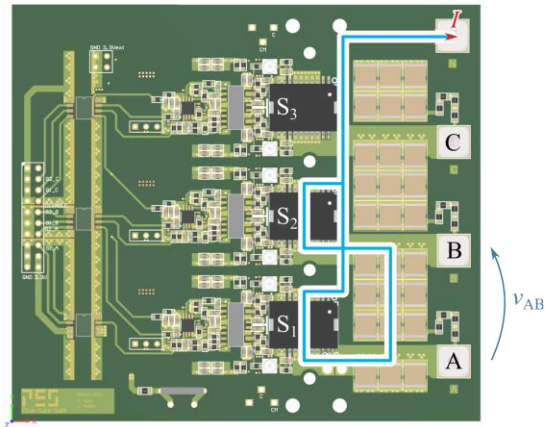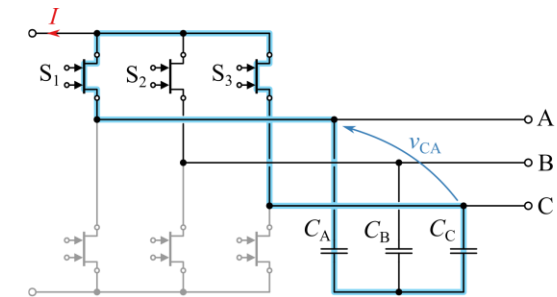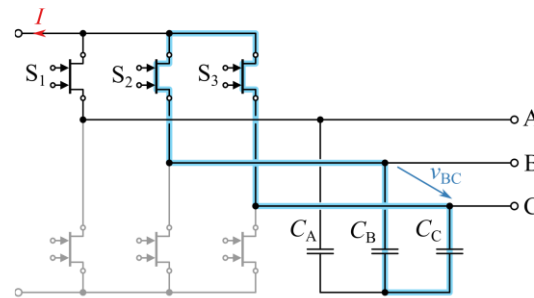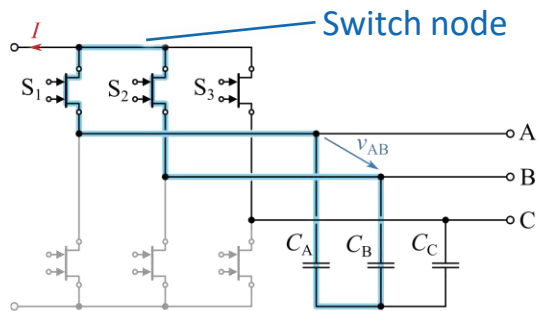
- Commutation voltages: **line-to-line** AC voltages / Commutation capacitors: **two** AC-side filter capacitors



Note: approximate loops only (partly vertical)

Remark: Passive Toggling of Commutation Cell's 3rd Switch

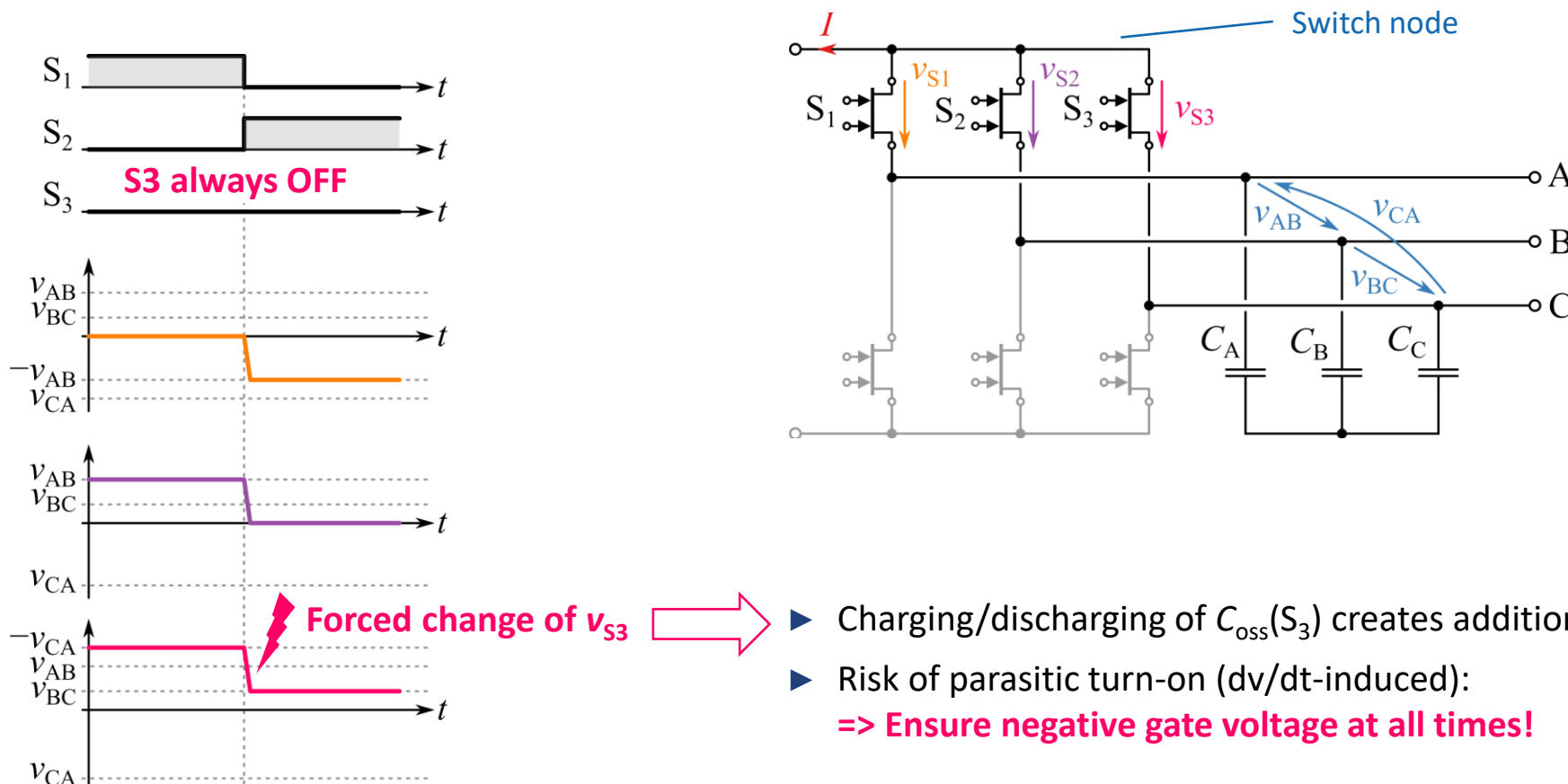
- Three switches connected to common switch node / Example: Commutation from S_1 to S_2




- Charging/discharging of $C_{oss}(S_3)$ creates additional losses¹
- Risk of parasitic turn-on (dv/dt-induced):
=> **Ensure negative gate voltage at all times!**

¹ Note: similar effect also observable in TT bridge-legs

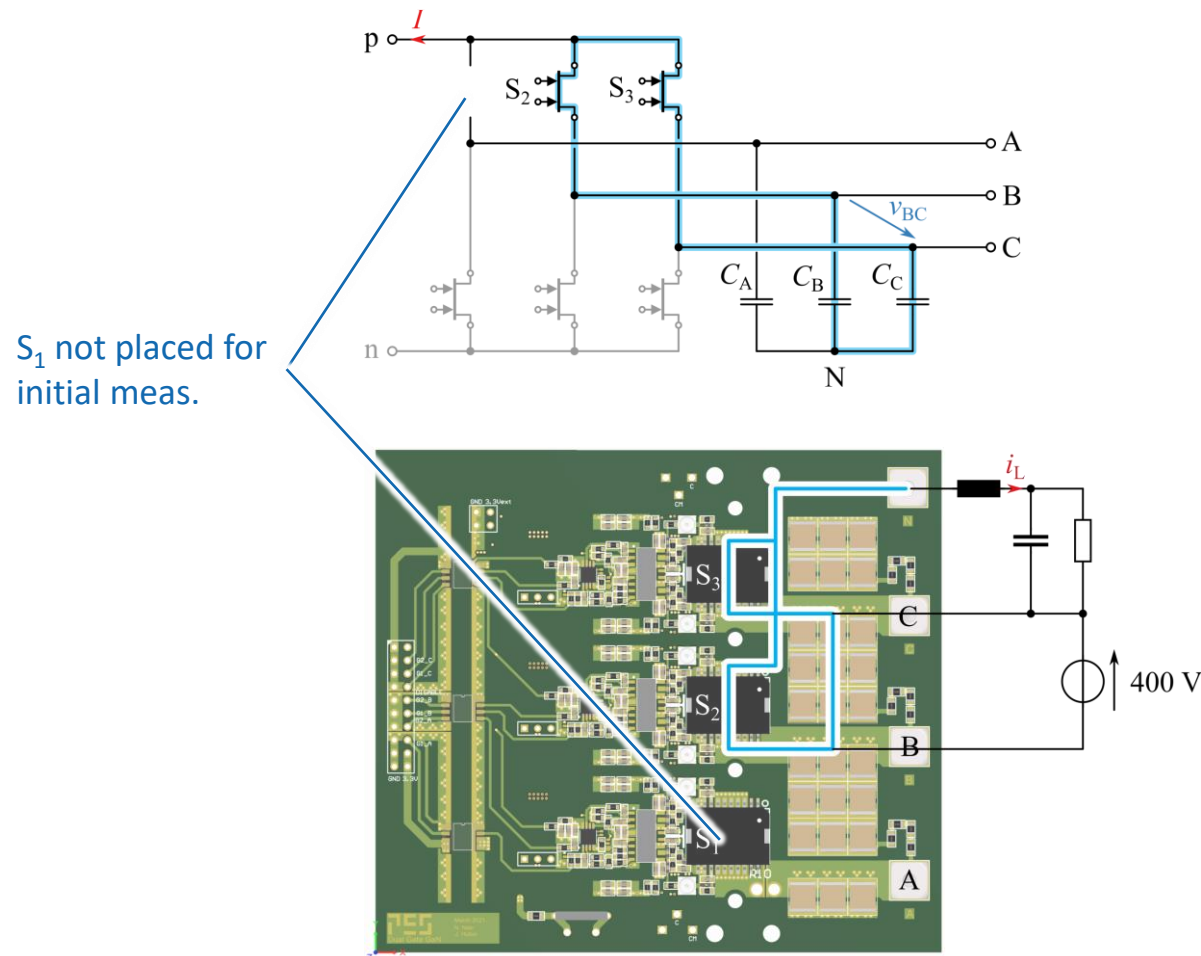M-BDS Commutation Cell Test PCB: Half-Bridge Configuration



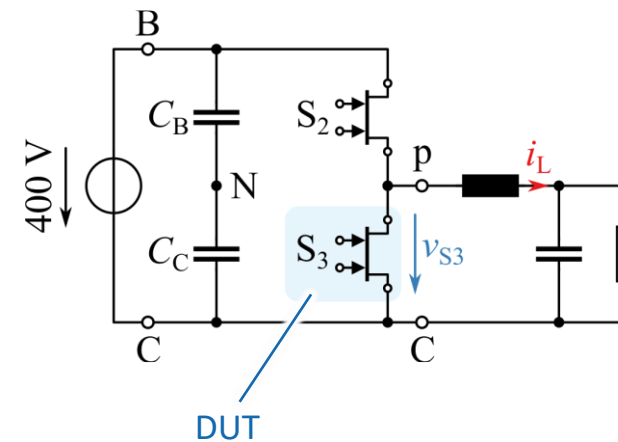
- DUT operation in all **four quadrants** by reconfiguring voltage source / load
 - DC supply between B-C or C-B (± 400 V)
 - Load between p-C or p-B (current direction)



- Impact of S_1 presence to be quantified


Remark: 4-Step Commutation (Positive Current)

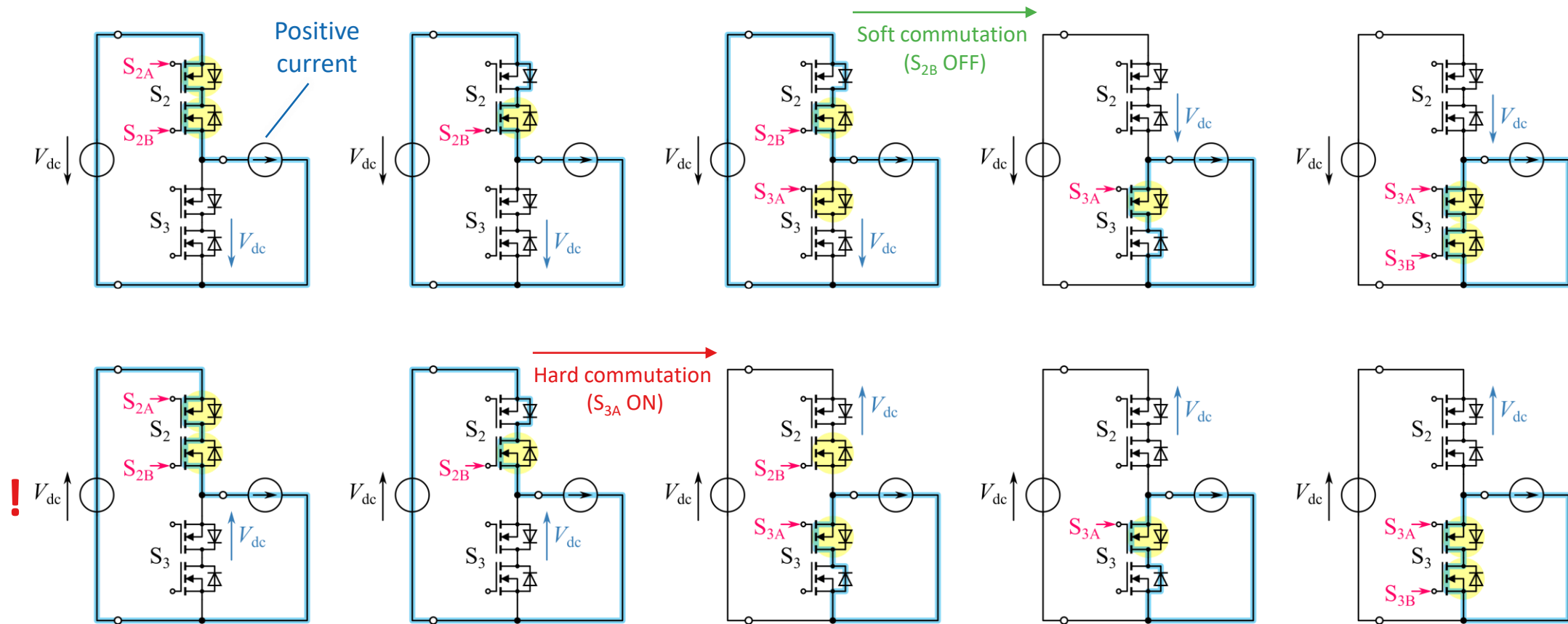- Ensure current path & avoid DC voltage short-circuit / **Current-direction dependent** gating sequence (pos. current shown)




Remark: 4-Step Commutation (Negative Current)

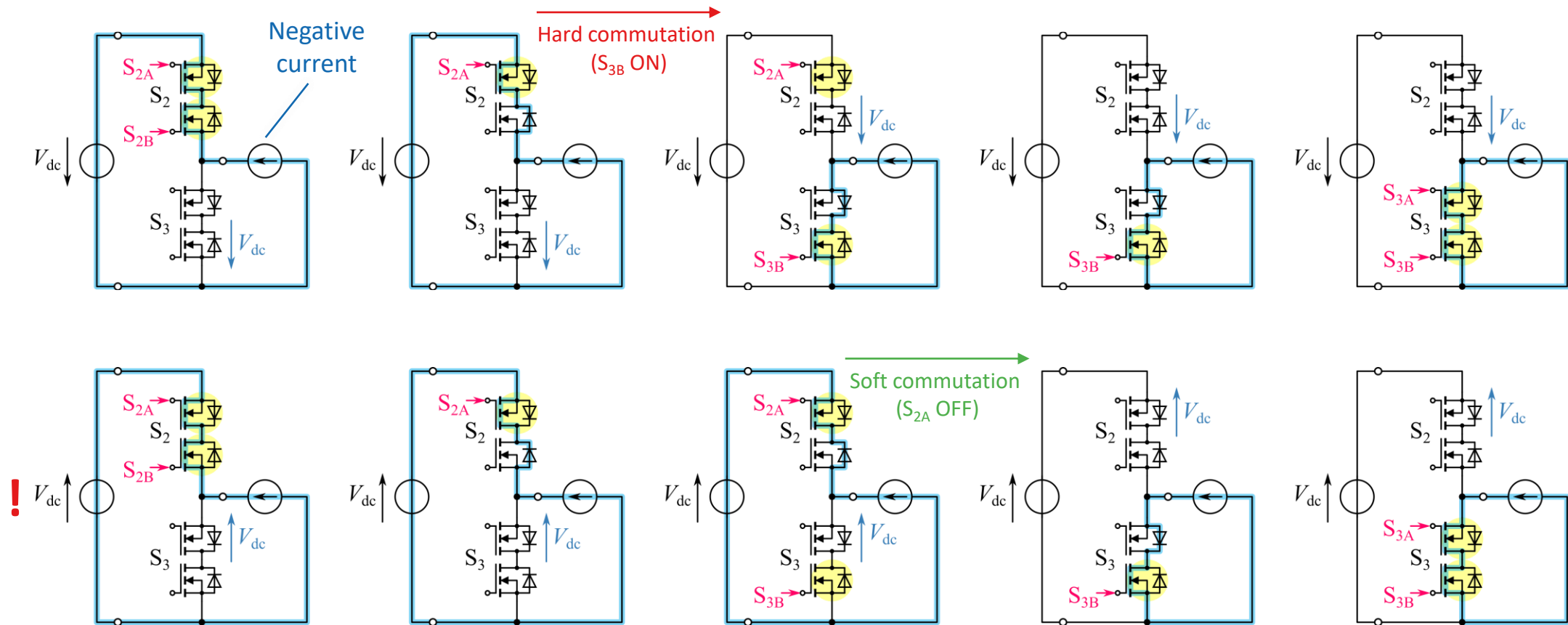- Ensure current path & avoid DC voltage short-circuit / **Current-direction dependent** gating sequence (neg. current shown)



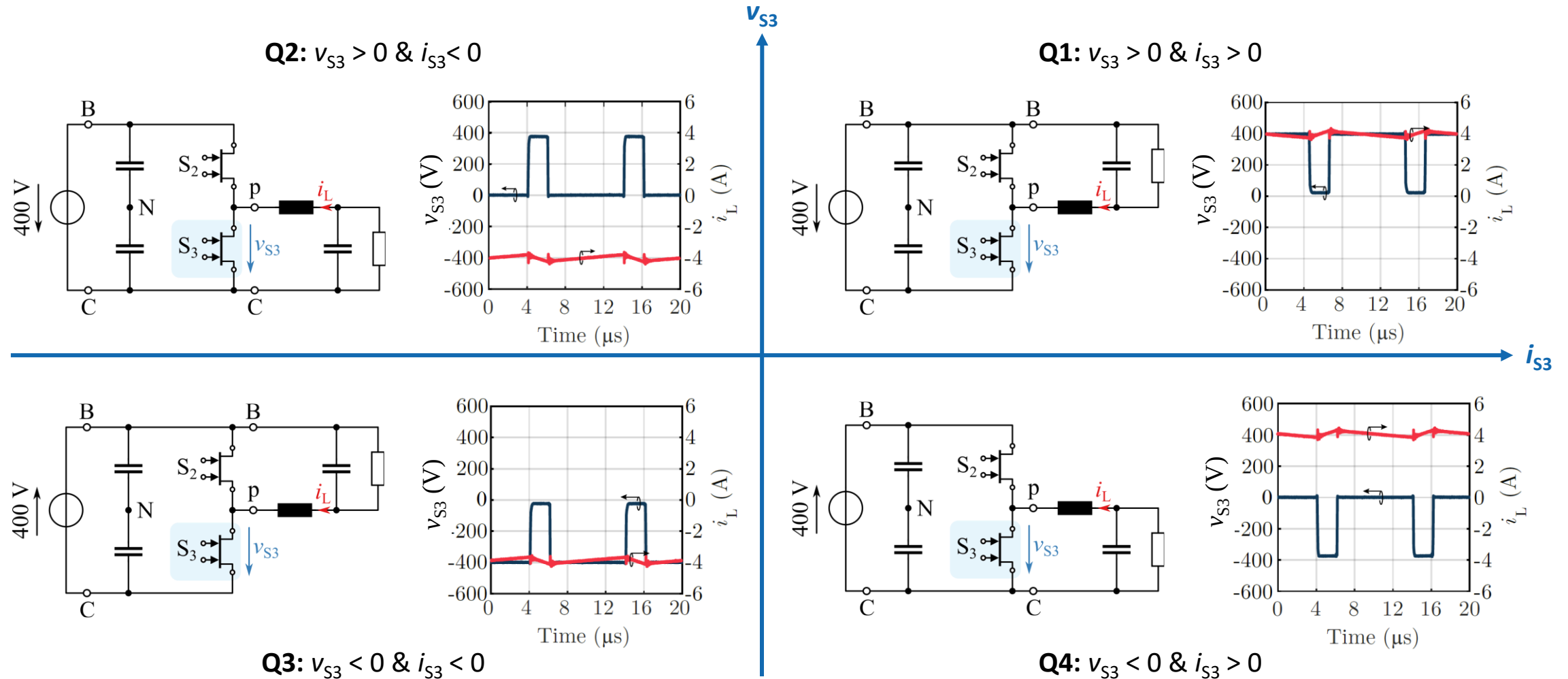
Continuous M-BDS Half-Bridge Operation at ± 400 V




M-BDS Half-Bridge Switching Loss Characterization

- Transient calorimetric method / **4-Step commutation sequence** / All four quadrants / Two voltage levels (CSC)

Test PCB

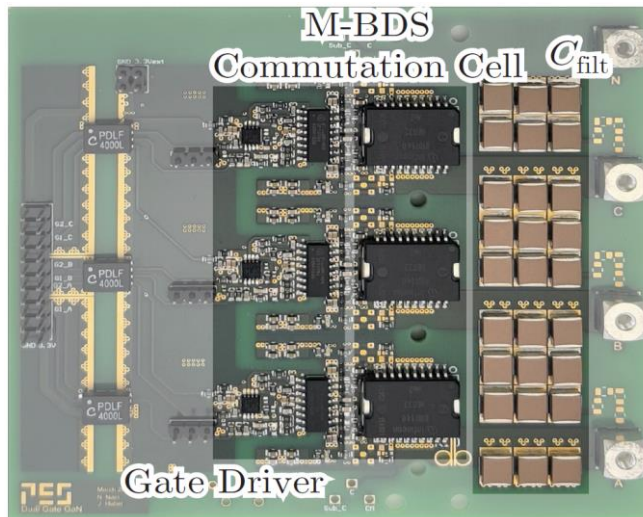

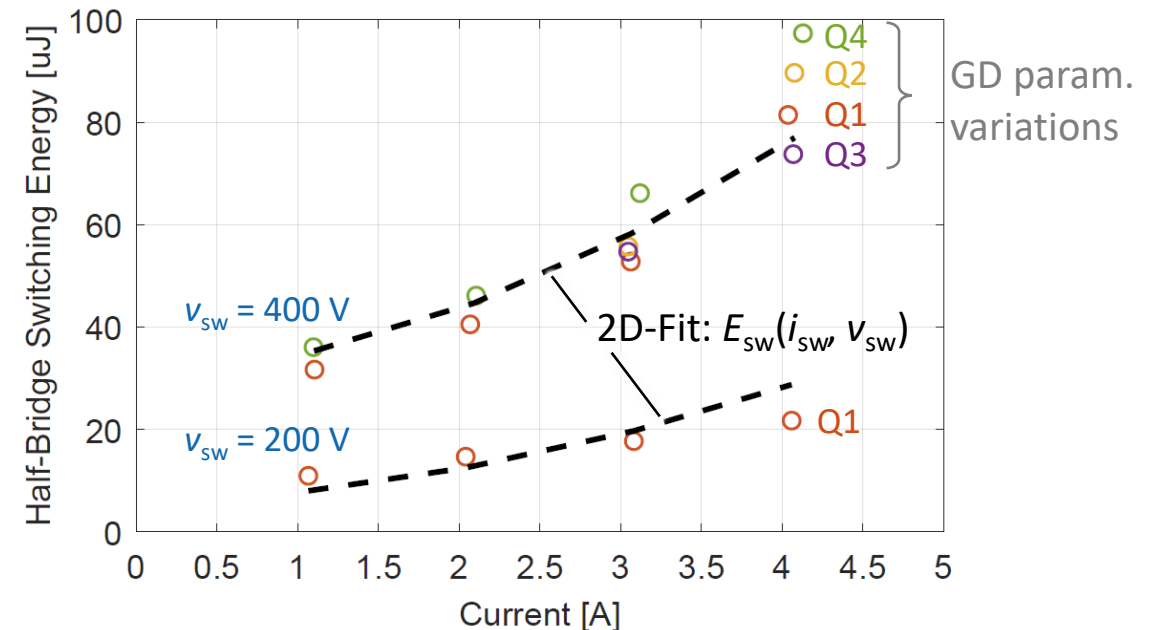
Half-Bridge Hard-Switching Energies ($E_{on} + E_{off}$)



- Note: **Preliminary** results / Gate setup & timings not yet fully optimized => **Lower switching losses achievable**


Performance of AC-AC CSC with 600 V / 140 mΩ GaN M-BDSs

► Motor drives for aircraft applications

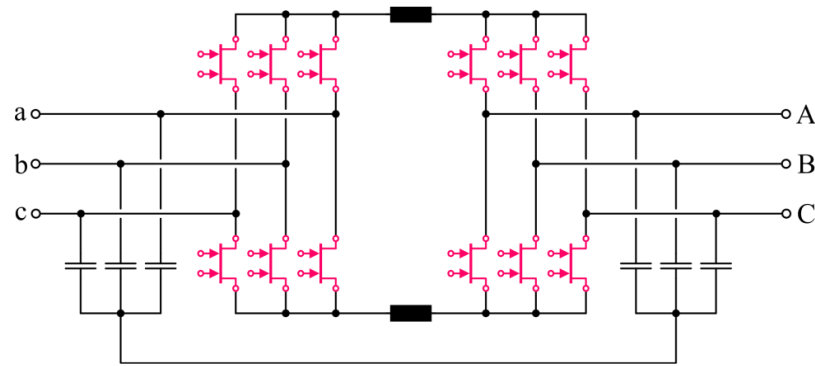


Specifications / Modeling

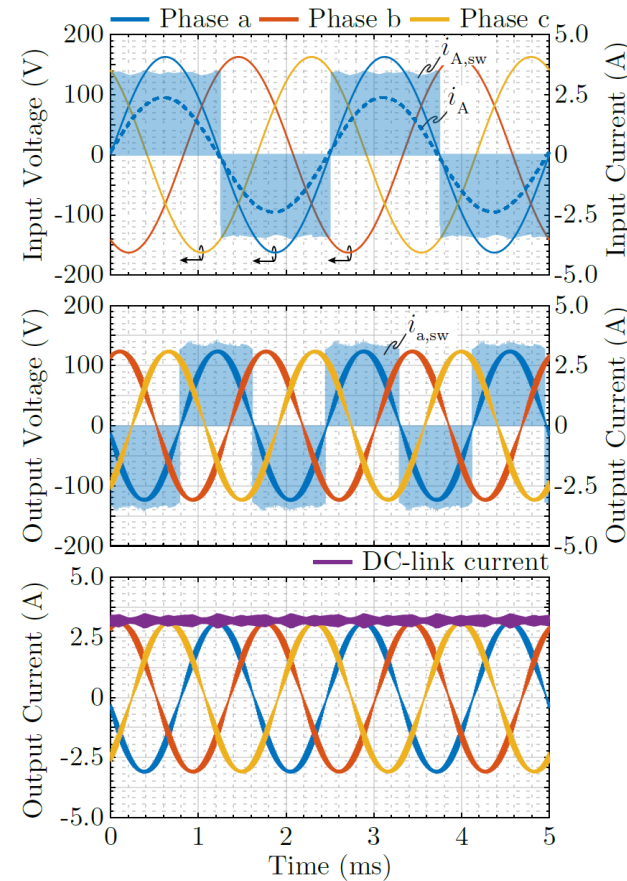- 115 V rms, 400 Hz grid
- 92 V rms, 600 Hz, 1 kW output (design point)
- $T_j = 100\text{ }^{\circ}\text{C}$, $T_{\text{amb}} = 45\text{ }^{\circ}\text{C}$ / heat sink volume: CSPI = 15 W/(dm³K)
- $\Delta i_{\text{Ldc,pp}} = 10\%$ (peak-to-peak), $\Delta Q_{\text{CF}} = 5\%$
- Pareto-optimal inductor designs (N87 or KoolMu)



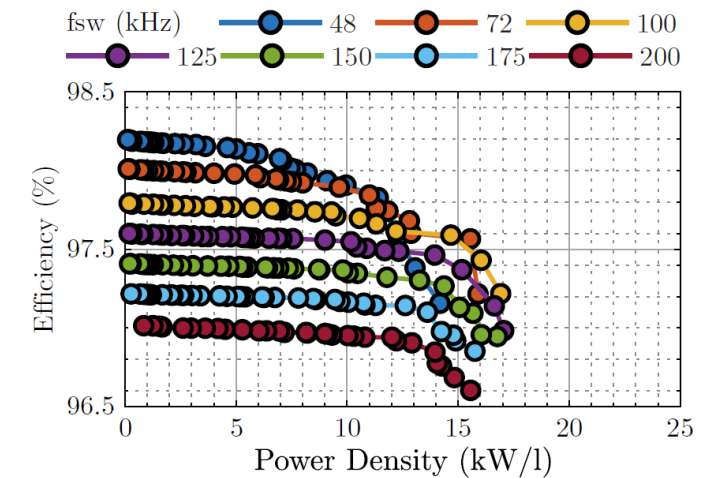► Performance evaluation based on measured M-BDS switching losses



Note: Preliminary results / Work in progress!


Conclusion & Outlook

Conclusion & Outlook


- ▶ 600 V / 140 mΩ  GaN M-BDS continuous operation at ± 400 V
- ▶ Calorimetric switching loss characterization of M-BDS in GaN/SiC TT bridge-leg and **all-GaN CSC commutation cell**



TT DC-AC Converter

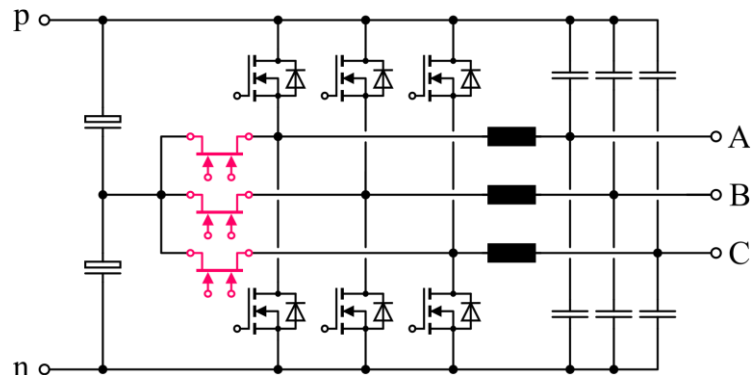

Current-Source AC-AC Converter

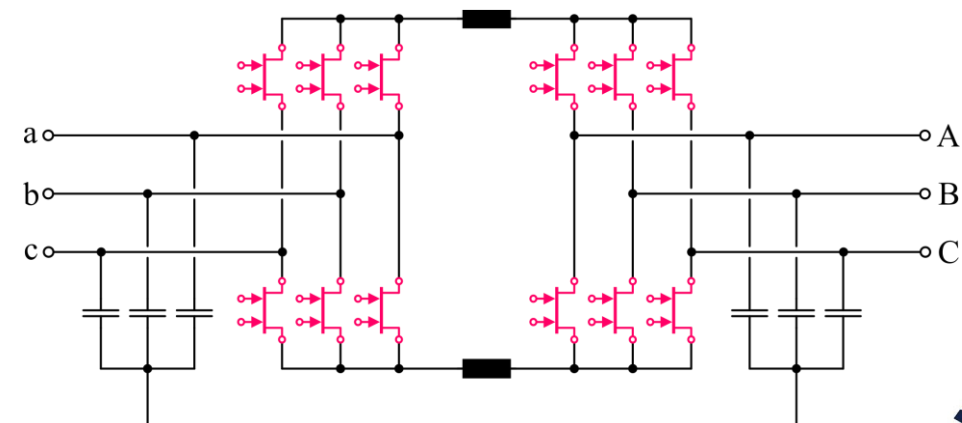

- ▶ **Full prototypes** under development / System-level experimental performance verification
- ▶ GaN M-BDS technology takes flight and promises **straightforward designs** and **superior performance**



Thank You!

