

# **Intelligent Solid State Transformers (SSTs)**

## ***A Key Building Block of Future Smart Grid Systems***

**Johann W. Kolar ...**

Swiss Federal Institute of Technology (ETH) Zurich  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)





Eidgenössische Technische Hochschule Zürich  
Swiss Federal Institute of Technology Zurich


# The MEGA Cube Project

**Johann W. Kolar & Gabriel Ortiz**

Swiss Federal Institute of Technology (ETH) Zurich  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)


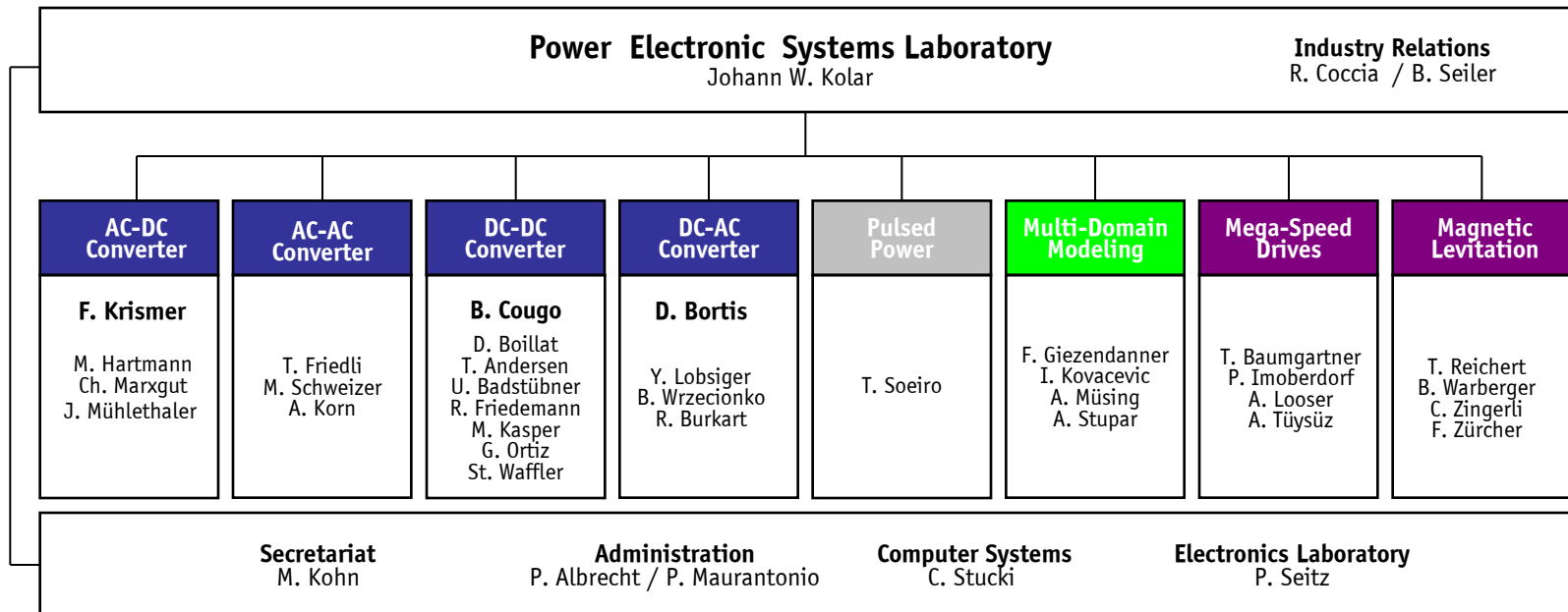
# ETH Zurich - Power Electronic Systems Laboratory




29 Ph.D. Students  
3 Post Docs



Leading Univ.  
in Europe

## PES Research Scope

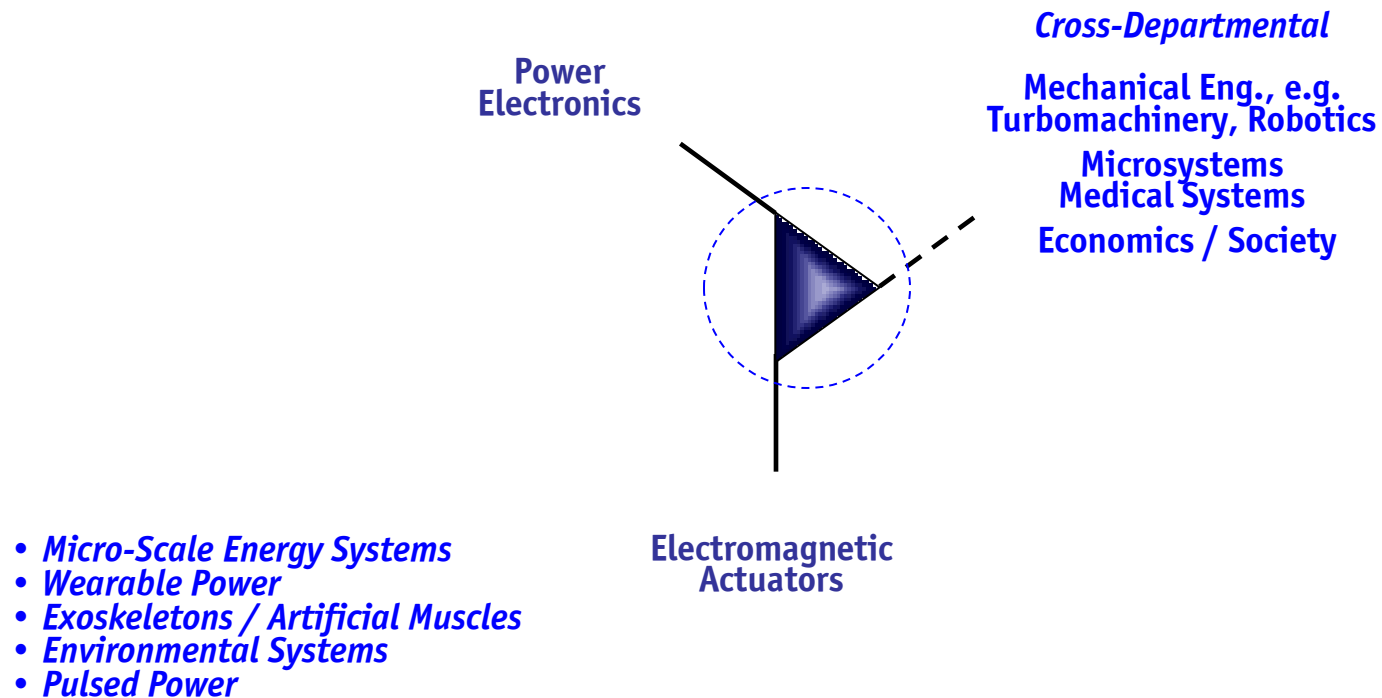


# Industry Collaboration

## ► Core Application Areas

- IT Power Supply
- Renewable Energy
- Industry Automation
- Automotive Systems
- More-Electric Aircraft
- Semiconductor Process Technology
- Medical Systems
- Etc.

## ► 16 International Industry Partners

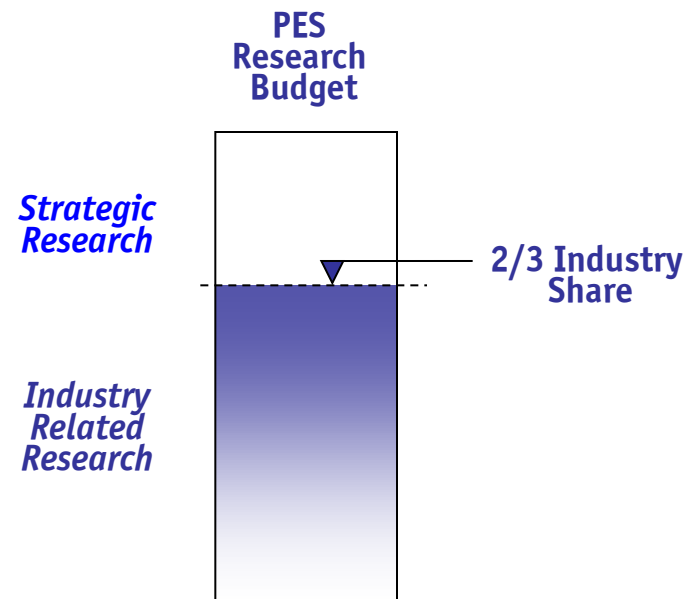

## Examples of Research Results

Ultra-Compact Systems  
Super-Efficient Systems  
MEGA Speed Drives

## 3- $\Phi$ Boost-Type PFC Rectifier


$P_o = 10 \text{ kW}$   
 $U_N = 230V_{AC} \pm 10\%$   
 $f_N = 50\text{Hz or } 360\ldots 800\text{Hz}$   
 $U_o = 800V_{DC}$

$f_p = 250\text{kHz}$

► Si CoolMOS  
 ► SiC Diodes

$\eta = 96.2\% @ P_o$   
 $THD_I = 1.6\% @ P_o$   
 $\gamma = 3\text{kW/kg}$


★ 10kW/dm<sup>3</sup> Power Density

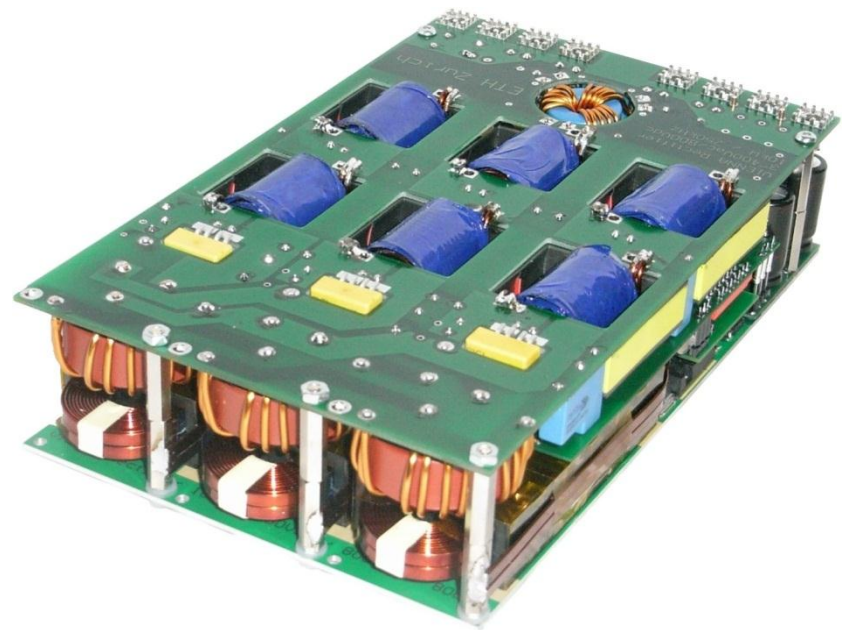

## Mains Behavior @ 400 Hz/800 Hz


$P_o = 10\text{kW}$   
 $U_N = 230\text{V}$   
 $f_N = 400\text{Hz}$   
 $U_o = 800\text{V}$   
 $THD_i = 1.4\%$

10A/Div  
 200V/Div  
 1ms/Div

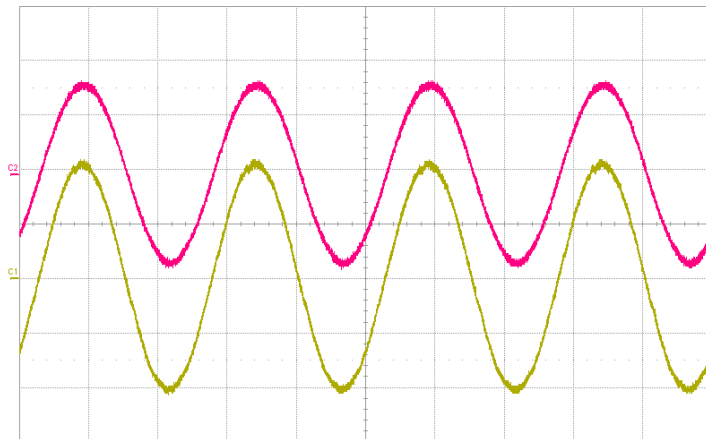

$P_o = 10\text{kW}$   
 $U_N = 230\text{V}$   
 $f_N = 800\text{Hz}$   
 $U_o = 800\text{V}$   
 $THD_i = 1.6\%$


10A/Div  
 200V/Div  
 0.5ms/Div

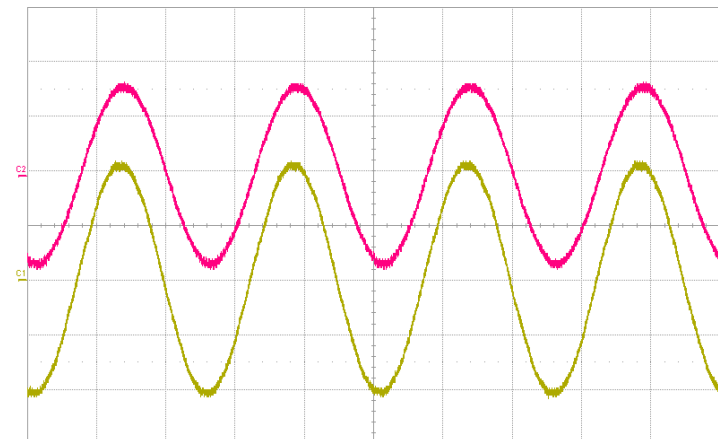
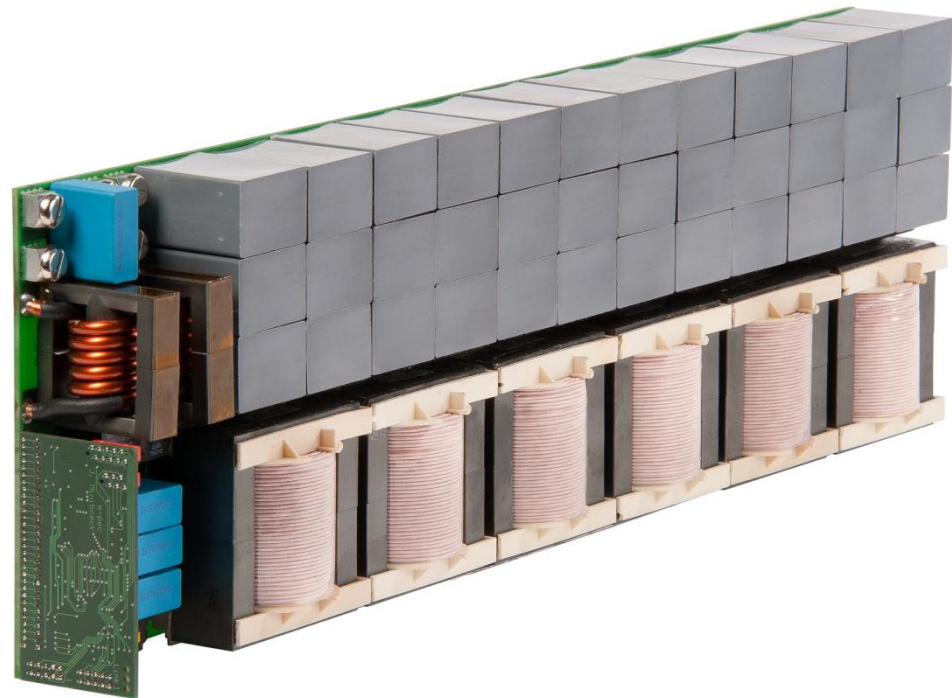
## Bidirectional Super-Efficient 1- $\Phi$ PFC Mains Interface

★ 99.3% @ 1.2kW/dm<sup>3</sup>

*Hardware Testing  
to be finalized in  
November 2011*




► Employs NO SiC Power Semiconductors -- Si SJ MOSFETs only

# Bidirectional Super-Efficient 1- $\Phi$ PFC Mains Interface

★ 99.3% @ 1.2kW/dm<sup>3</sup>

*Hardware Testing  
to be finalized in  
November 2011*

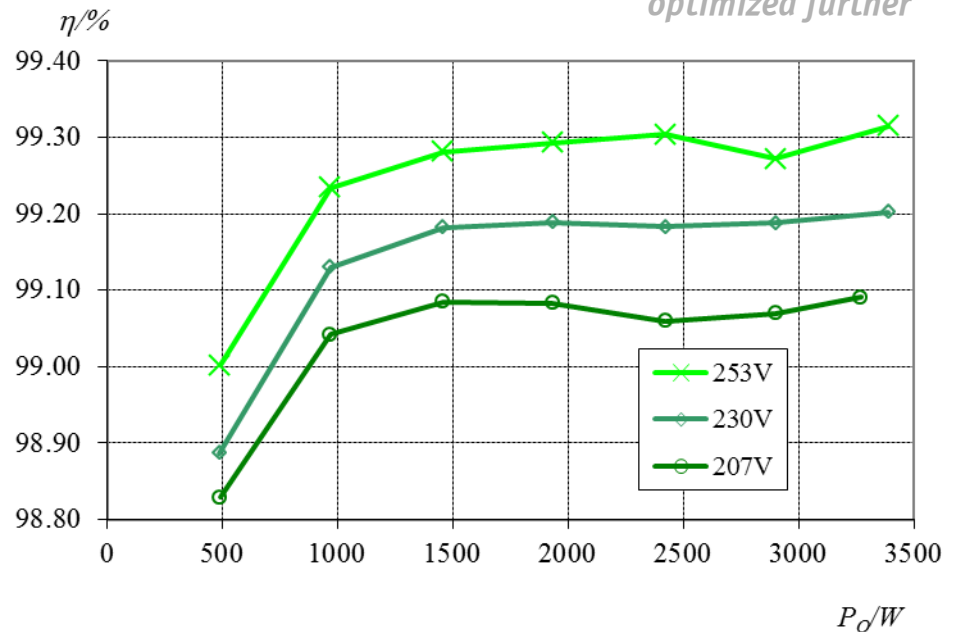*Results of first testing;  
System still to be  
optimized further*




► Employs NO SiC Power Semiconductors -- Si SJ MOSFETs only

## MEGA Speed Drive Systems

***World Record !***

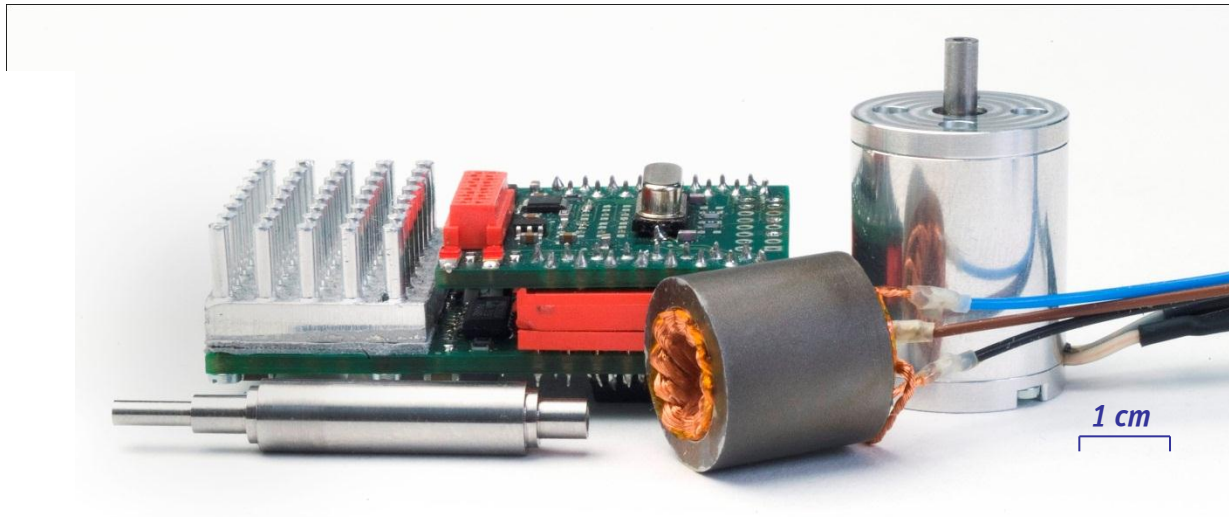**100W @ 1'000'000 rpm**

- $\mu\text{m}$ -Scale PCB Drilling
- Dental Technology
- Laser Measurement Technology
- Turbo-Compressor Systems
- Air-to-Power
- Artificial Muscles
- Mega Gravity Science



# Abstraction of Power Converter Design

Performance Space

Design Space

► Mapping of *Design Space* into *System Performance Space*

Performance Space

- Efficiency
- Power Density
- Costs
- Reliability
- etc.

System


- Phase-Shift DC/DC Conv.
- Resonant DC/DC Conv.
- DC Link AC/AC Conv.
- Matrix AC/AC Conv.
- etc.

Components

- Power Semiconductor
- Interconnections
- Inductors, Transf.
- Capacitors
- Control Circuit
- etc.



Materials

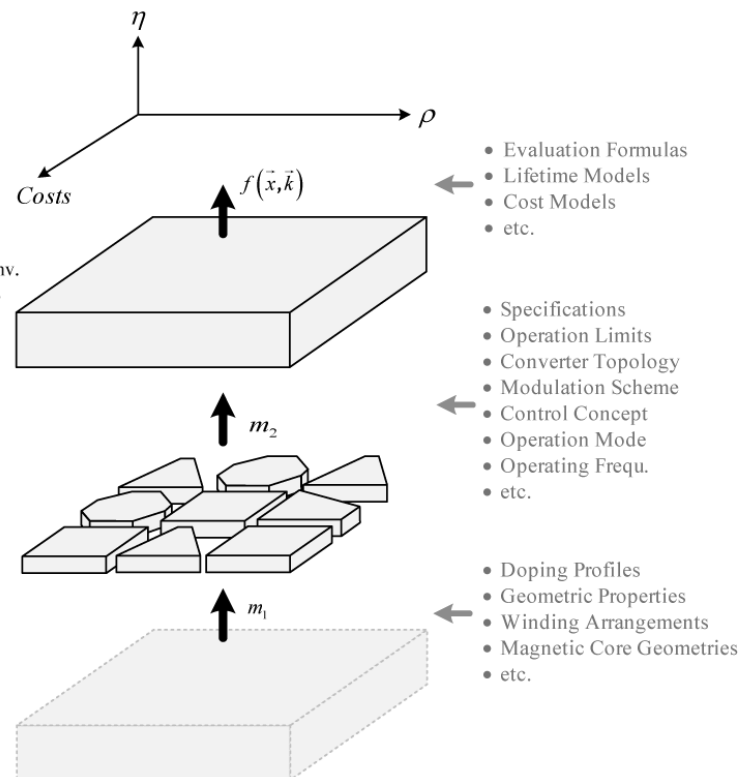- Semiconductor Mat.
- Conductor Mat.
- Magnetic Mat.
- Dielectric Mat.
- etc.


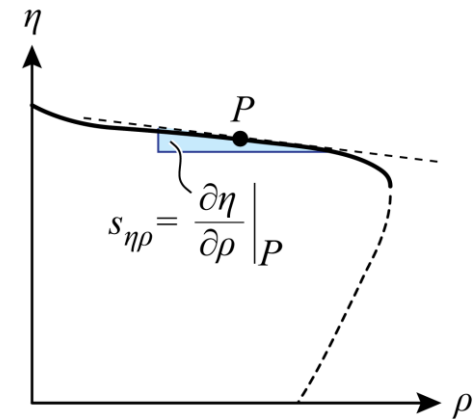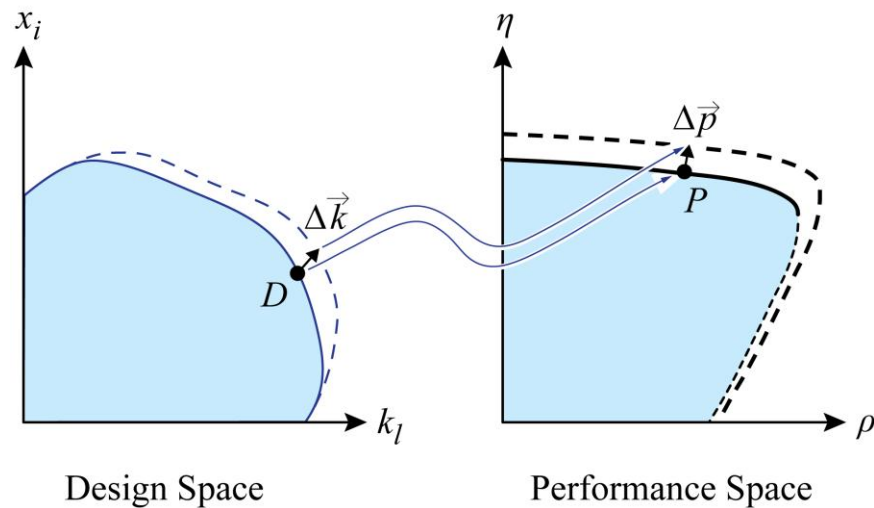
# Technology Sensitivity Analysis Based on $\eta$ - $\rho$ -Pareto Front

- Sensitivity to Technology Advancements
- Trade-off Analysis




# Outline



- ▶ **Introduction to SST Concept**
- ▶ **Applications of SSTs**
- ▶ **Overview of SST Research since 2001**
- ▶ **Details on the MEGA Cube**
- ▶ **Conclusions / Outlook**

# Introduction to Solid State Transformer Concept

## 50/60 Hz Transformer

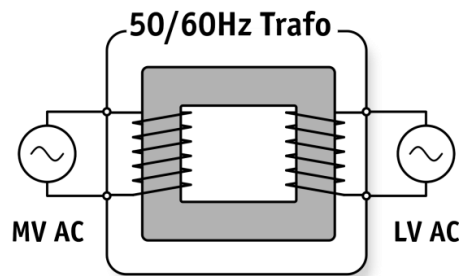

## Solid State Transformer

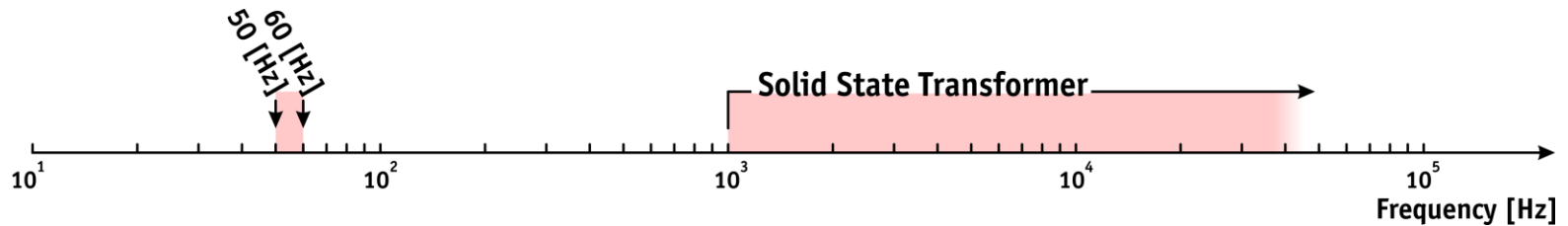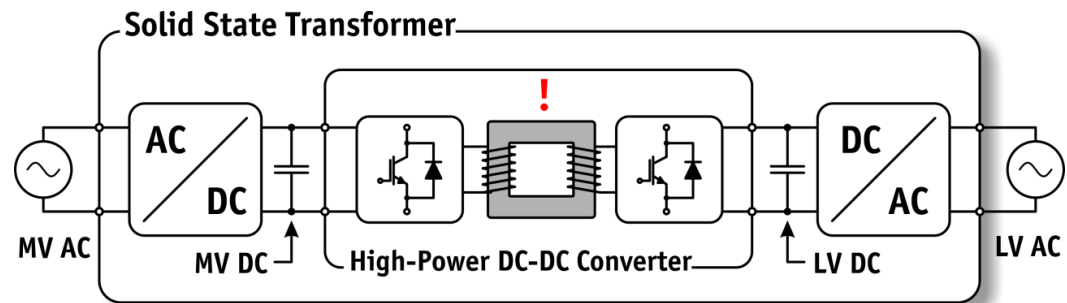


▲ 50/60Hz vs. SST Operating Frequencies in the kHz Range
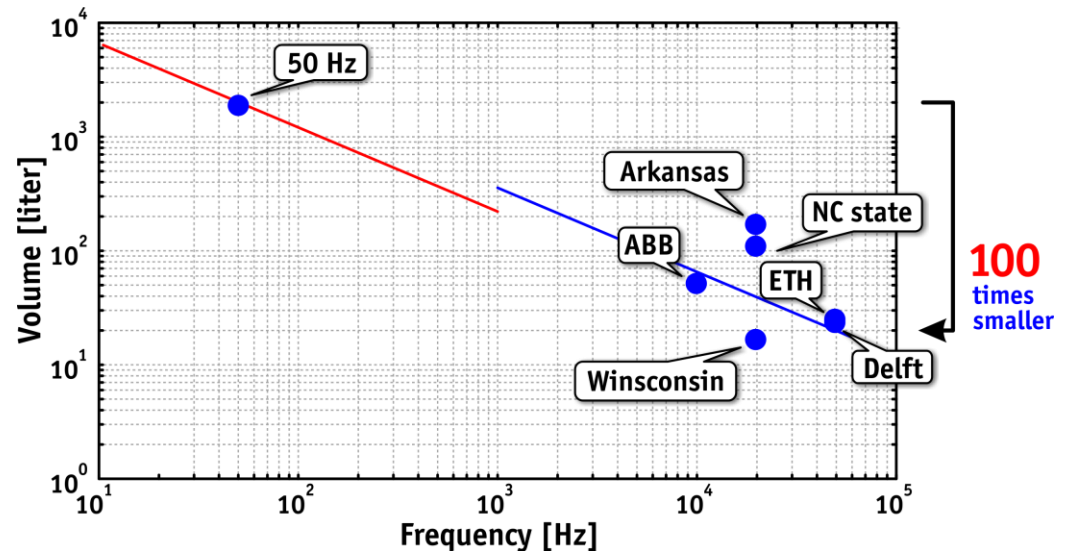
# Size/Weight Reduction

- Higher Operating Frequency Reduces Transformer Size/Weight

$$V_T \propto \frac{1}{\hat{B}} \cdot \frac{1}{f}$$




- ▲ Volume vs. Frequency of Transformers Realized in Previous Research Scaled to 1[MW]

# Reactive Power Control

## ► Power Factor Correction

- VAr Compensation
- Active Filtering

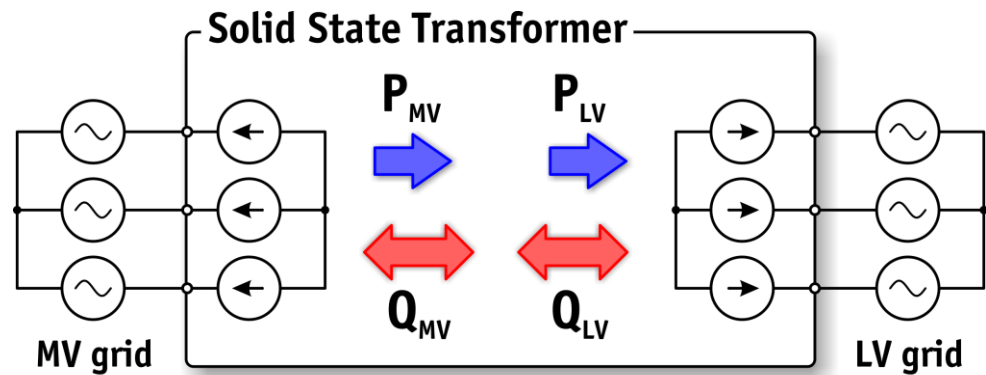


$$\begin{aligned} P_{MV} &= P_{LV} \\ Q_{MV} &= ! \\ Q_{LV} &= ! \end{aligned}$$

▲ SST providing Reactive Power Compensation

# UPS Operation
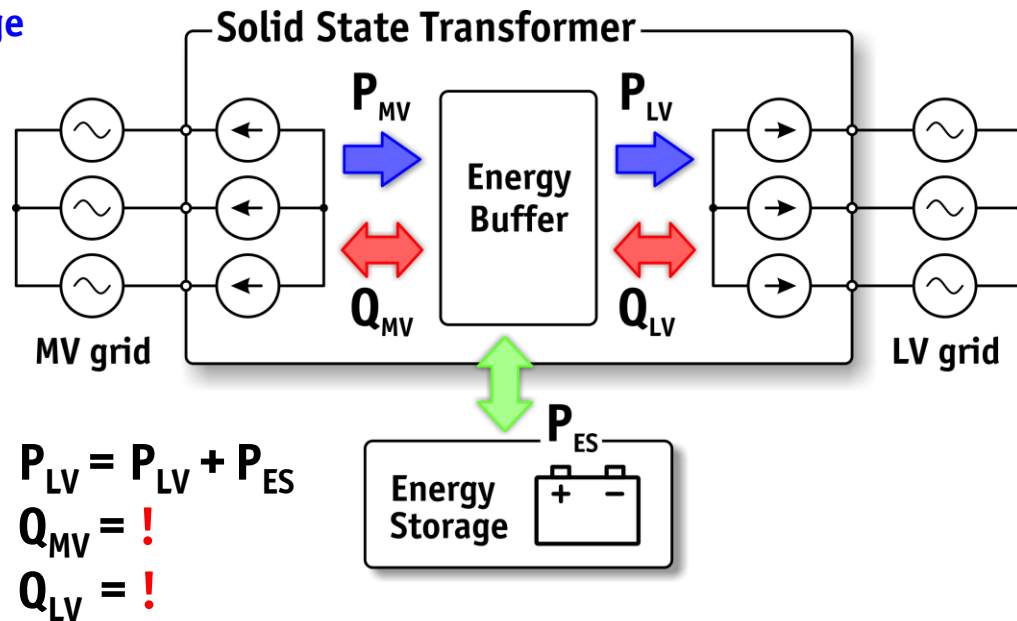
## ► Linked to Energy Storage

- Ability to Source/  
Sink Active Power in  
Both Directions




▲ SST Linked to Energy Storage System - providing UPS

# Applications

## of the Solid State Transformers
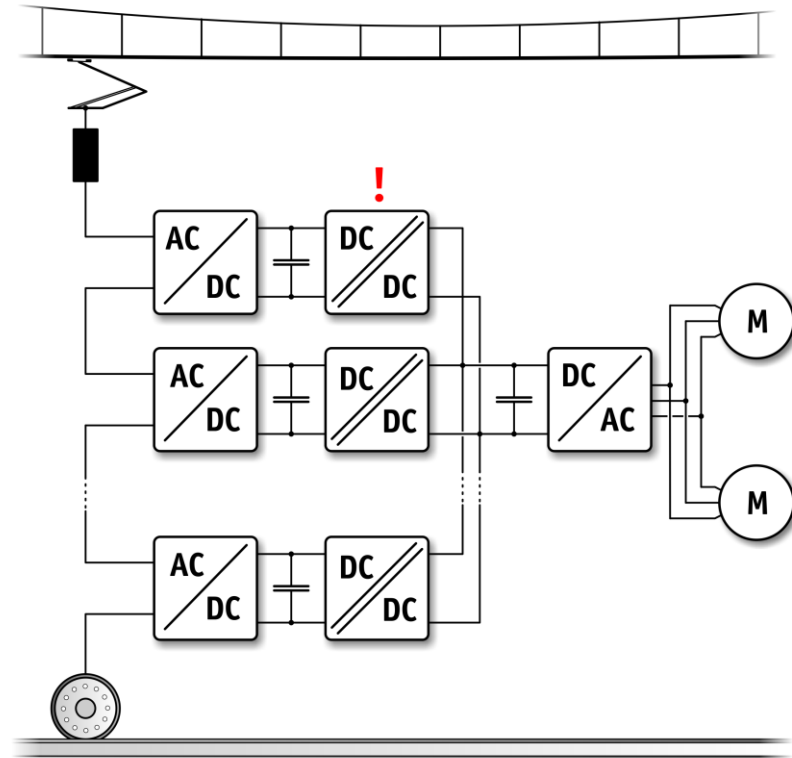
# Traction / Locomotives


- ▶ **Reduced Weight/Size**
- ▶ **Increased Efficiency**
- ▶ **Reduced Line Filtering**



▲ SST Replacing the **Input Transformer** of a Locomotive
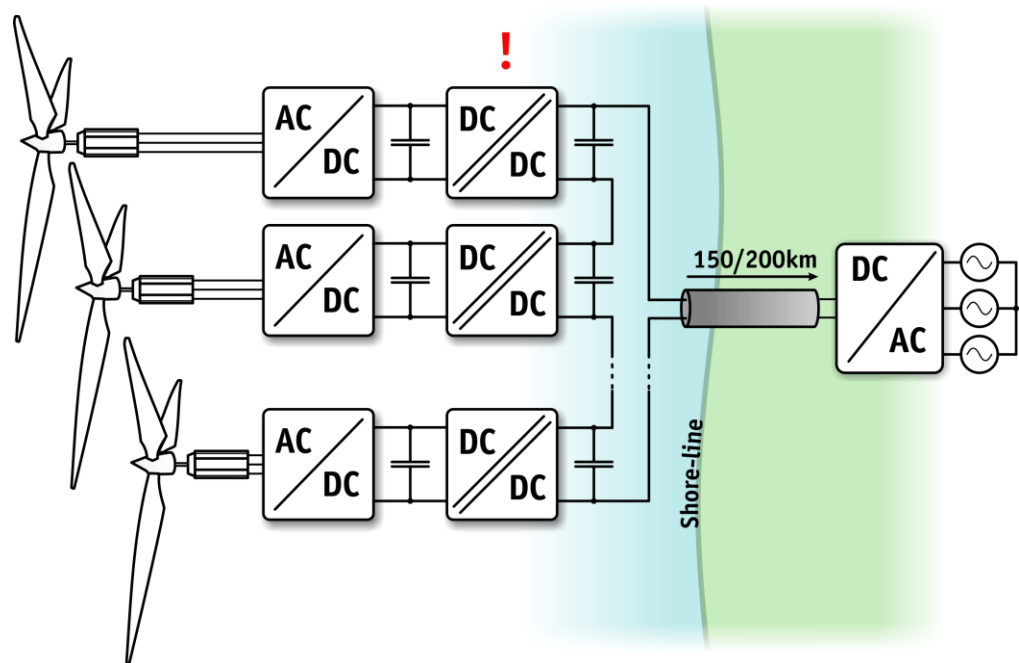
# Wind Power


- ▶ **Reduced Weight/Size**
- ▶ **Increased Efficiency of Power Transmission**



▲ SST in Off-Shore Wind Farms

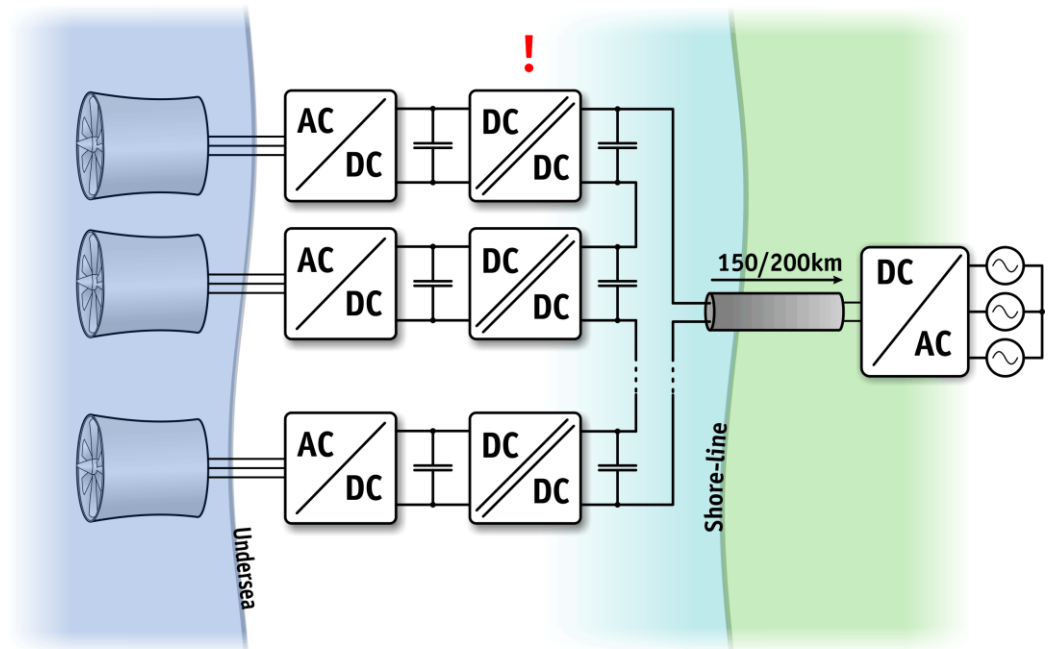
# Tidal Power

- ▶ **Reduced Weight/Size**
- ▶ **Increased Efficiency of Power Transmission**



▲ SST in Tidal Power Plants

# Smart Grid Scheme

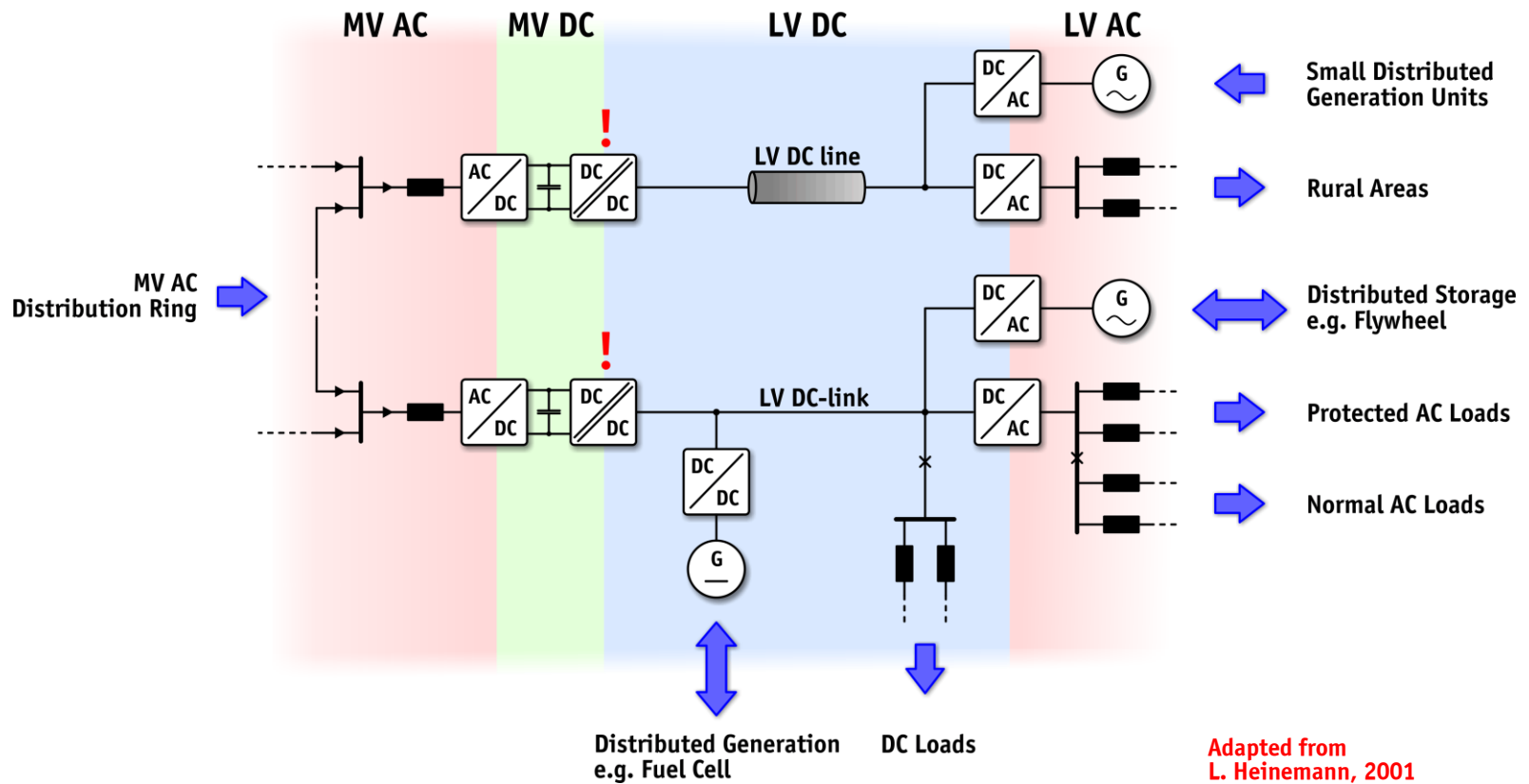

# Overview of SST Research


over the last 10 years

*Introduction to  
The MEGA Cube*

# Traction Applications


- ▶ 2001 ABB (ETH)
- ▶ 2007 Alstom
- ▶ 2007 Bombardier
- ▶ 2009 KTH
- ▶ 2010 Erlangen
- ▶ 2010 West Bohemia

SST Research over the  
Last 10 Years

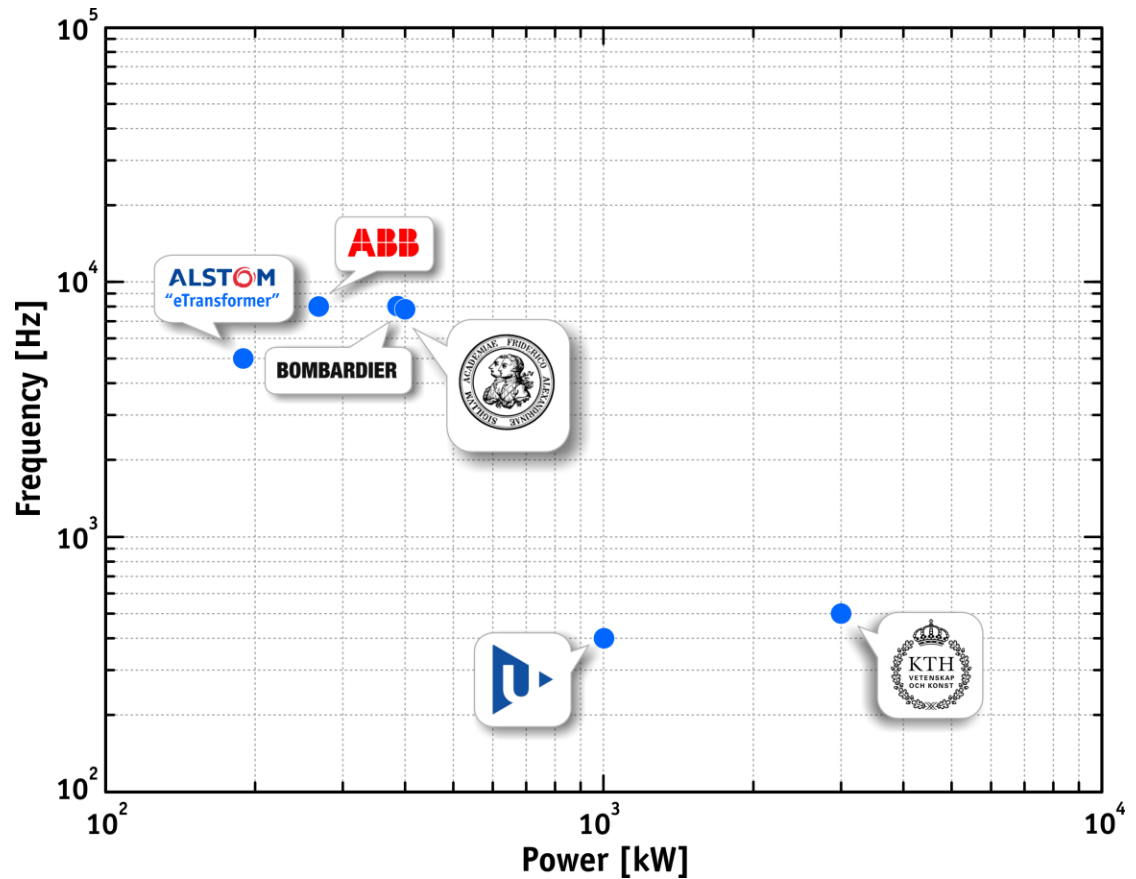
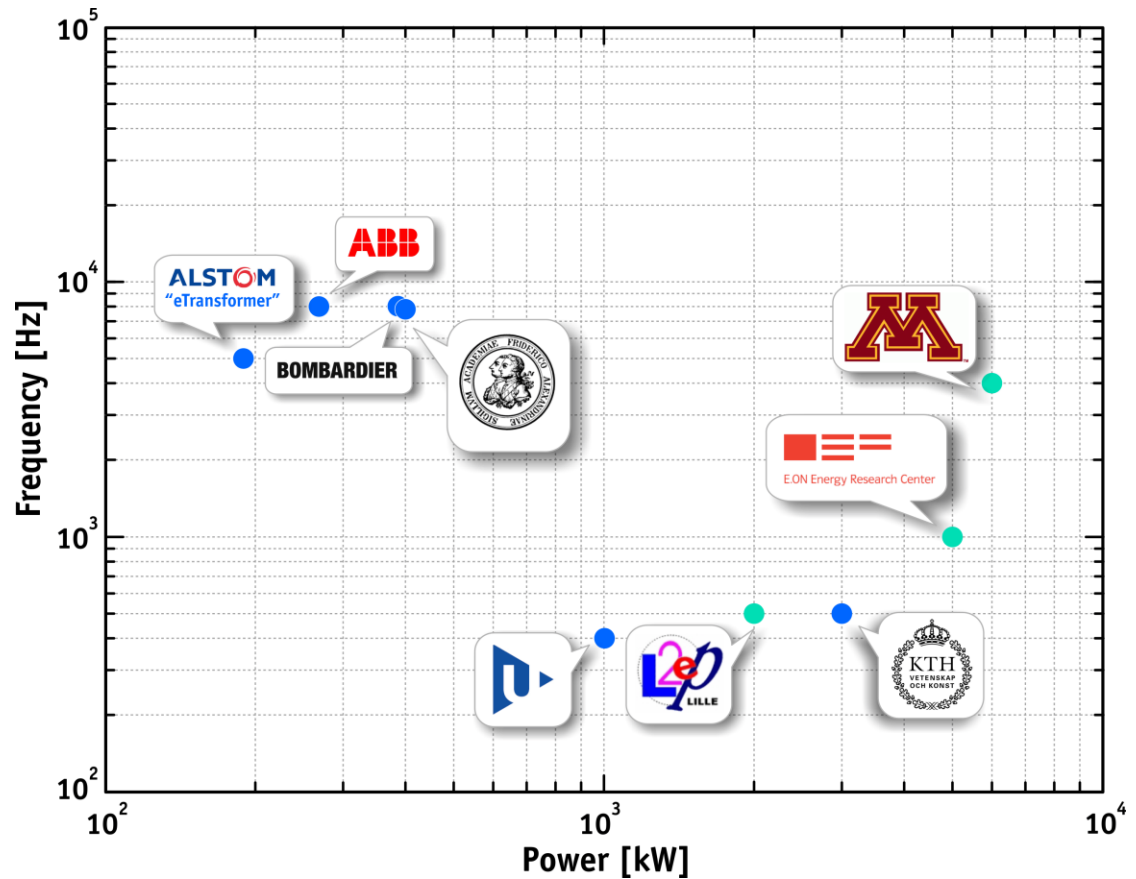
## Wind / Tidal Power


- ▶ 2009 E.ON
- ▶ 2009 Minnesota
- ▶ 2011 L2.E.P.



SST Research over the  
Last 10 Years
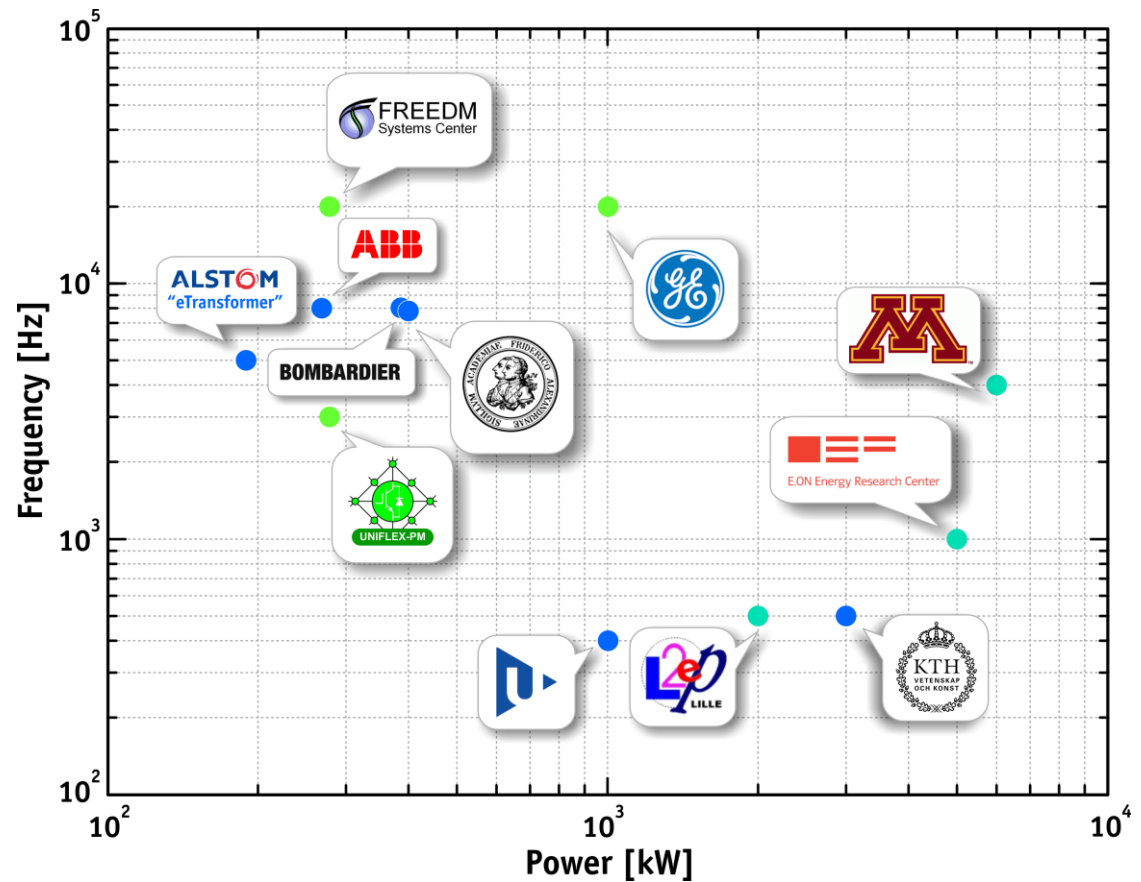
# Smart Grids

- ▶ 2006 UNIFLEX
- ▶ 2007 FREEDM
- ▶ 2011 GE




SST Research over the  
Last 10 Years
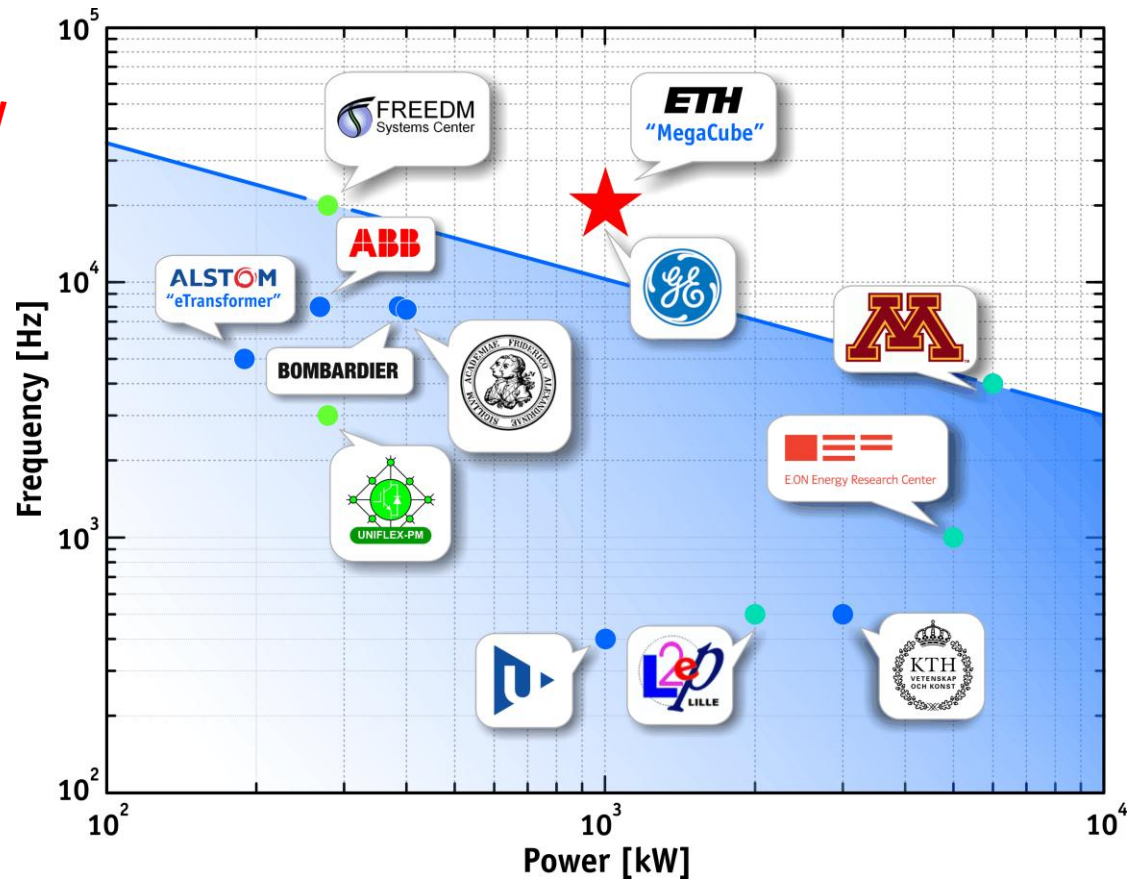
## The MEGA Cube @ ETH Zurich

- ▶ 1MW
- ▶ 20 kHz
- ▶ 12kV MV → 1.2kV LV

SST Research over the  
Last 10 Years... plus  
**MEGA Cube**



## Details on The MEGA Cube


*Medium-Voltage Side*  
*12kV - 20kHz*

# High-Voltage IGBTs

- ▶ Not Designed for Medium-Frequency Operation
- ▶ Zero-Current-Switching Schemes Required



◀ 4.5 kV/150 A  
ABB IGBT Module

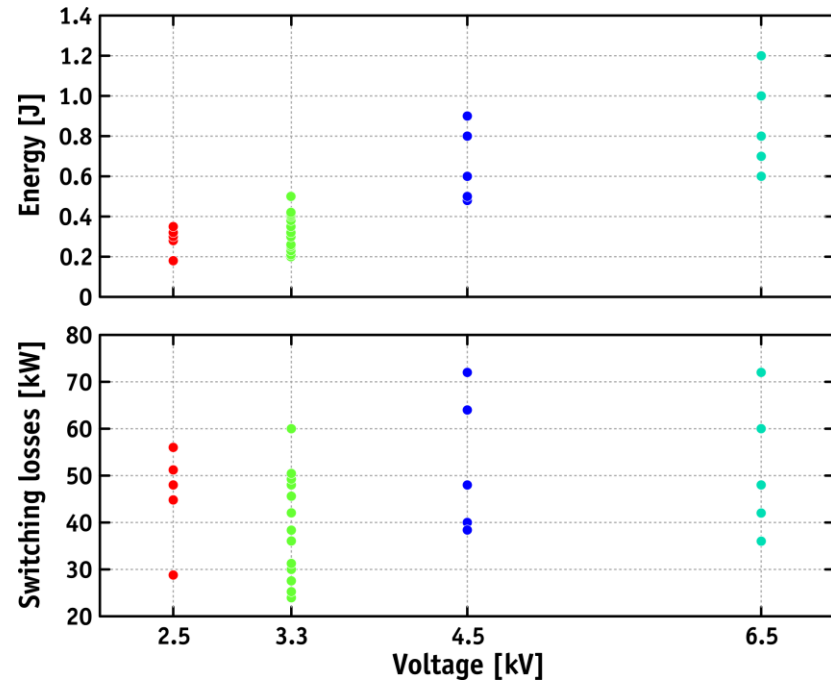


▲ 100 A Turn-Off Energies  
▲ 100 A/20 kHz Switching Losses

# Dual Active Bridge DC/DC Converter

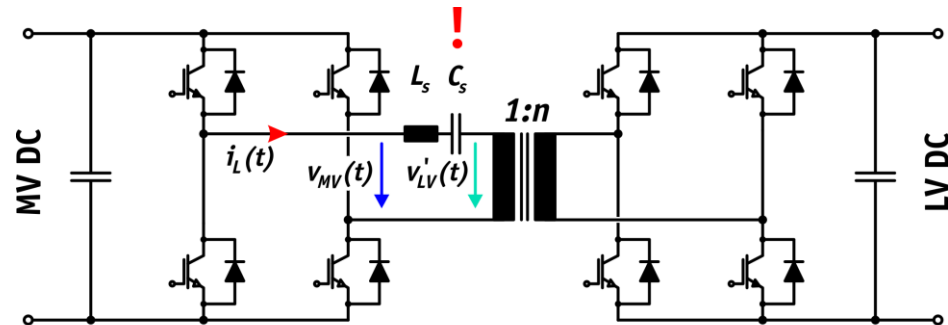
## ► Resonant

- Capacitor and Inductor in Series with Transformer
- Low Switching Losses in MV and LV Bridges


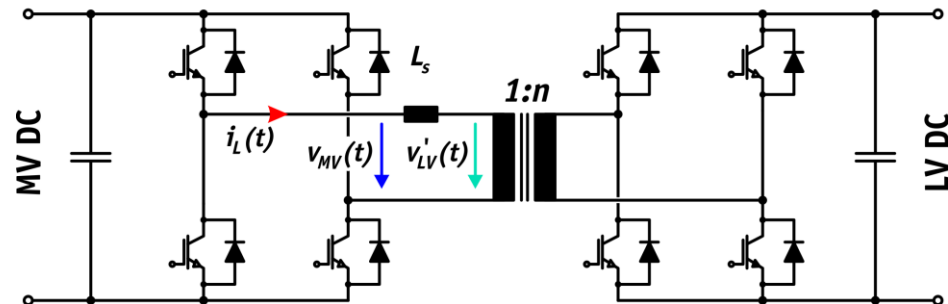
## ► Triangular Current


- Only Inductor in Series with Transformer
- High Switched Currents on LV Side



## Resonant vs. Triangular Current DAB

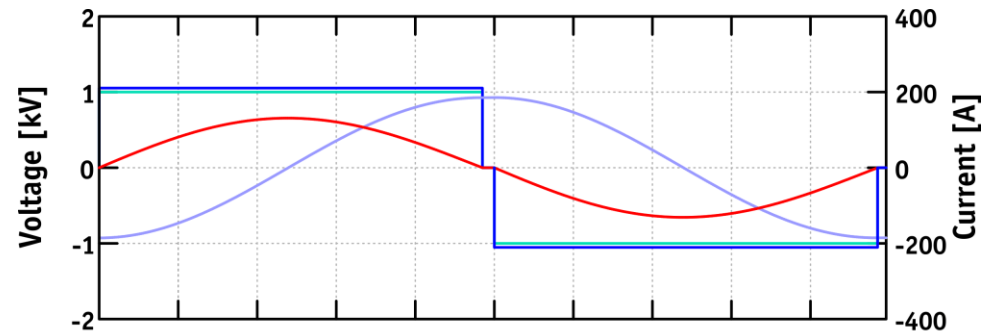
### ► Resonant

- ZCS on LV and MV Sides
- Low Controllability of Transferred Power



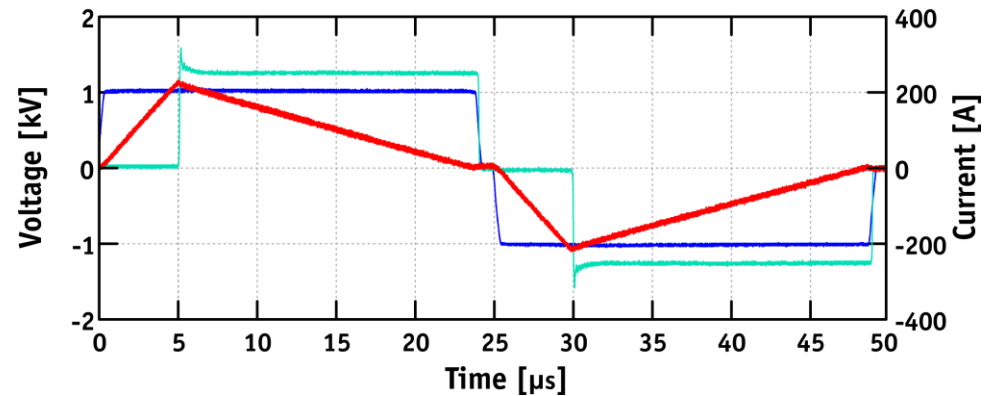
### ► Triangular Current

- ZCS only on MV Side
- Duty Cycle Power Flow Control



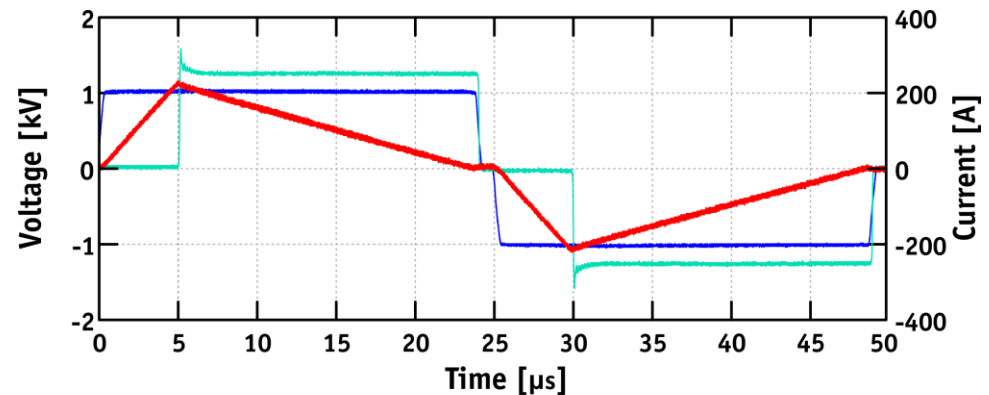
## Triangular Current DAB

- Enables ZCS Only on MV Side
- All Current Turn-Off Events Shifted to LV Side





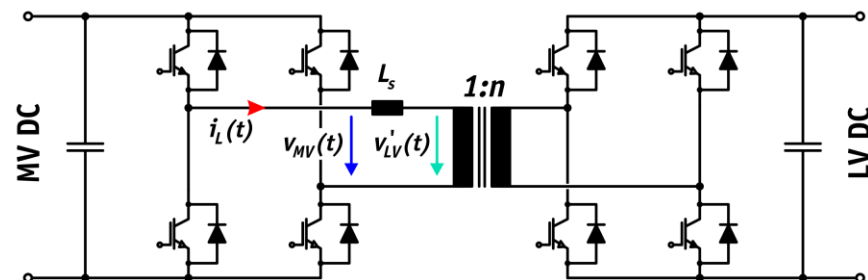Shown for Power  
Transfer from MV to LV Side



## MV Switch Realization - 4.5 kV IGBT

### ► Large Tail Current Despite ZCS

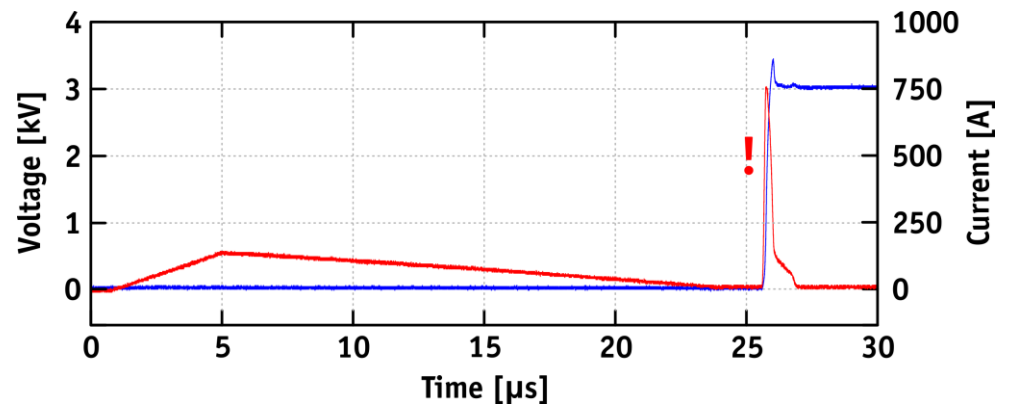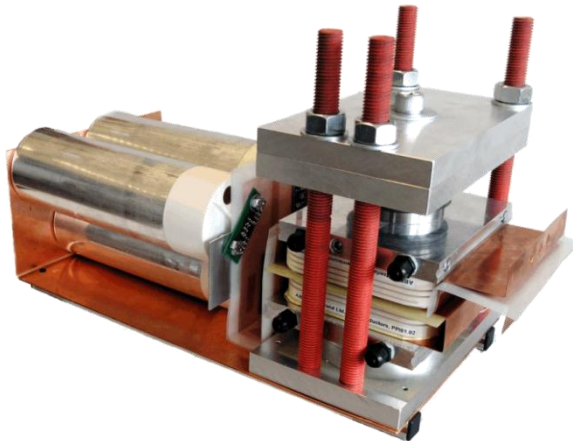


### ▲ 4.5kV Press-Pack IGBT Testbench


### ▲ ZCS Testing @ 3kV DC-Link 150A Peak
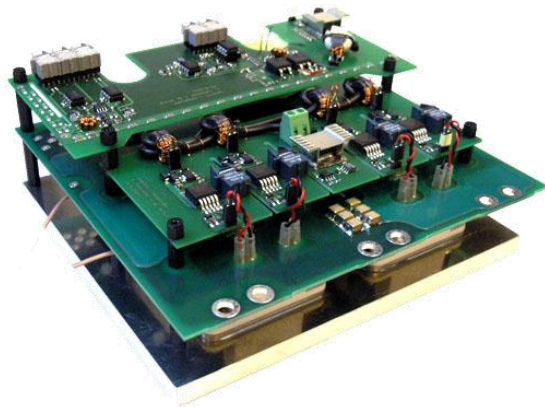
## MV Switch Realization - 1.7 kV IGBT

- ▶ Testbenches for NPT and PT 1.7kV IGBTs
- ▶ Massive ZCS Loss Reduction






▲ 1.7kV PT IGBT NPC Module

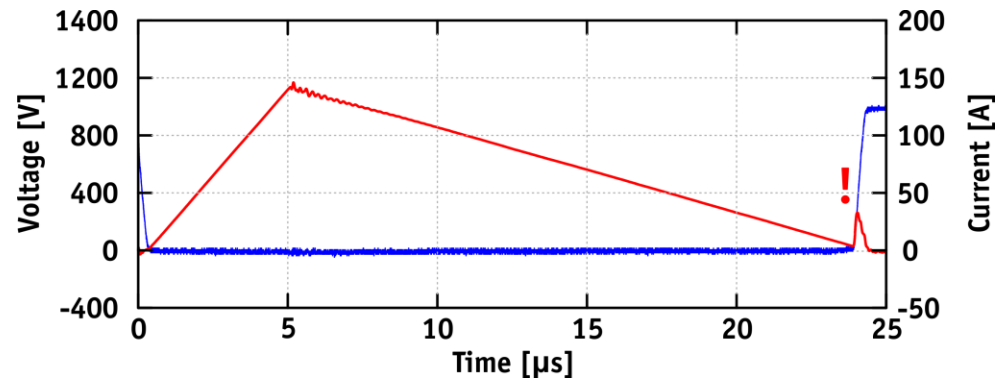

▲ ZCS Testing @ 1kV DC-Link 150A Peak


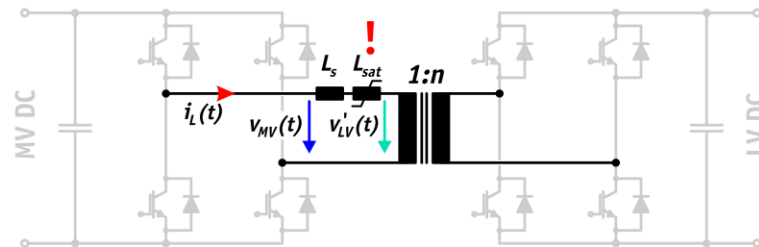
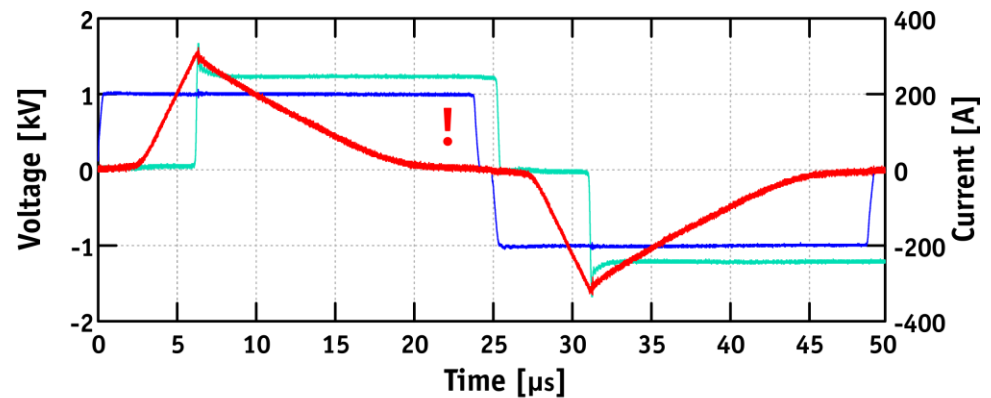
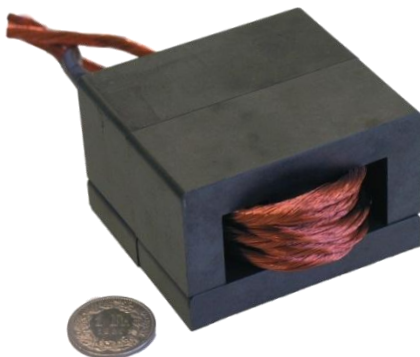
## Enhancement - Saturable Inductor

- Provides Time for Charge Carrier Recombination



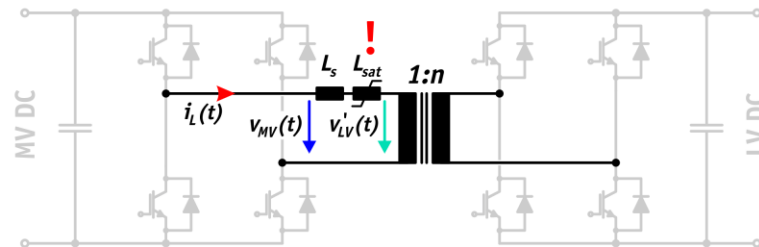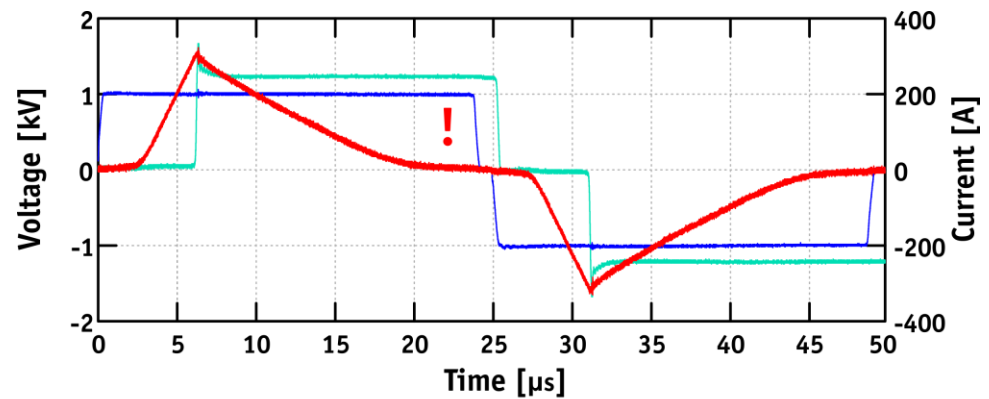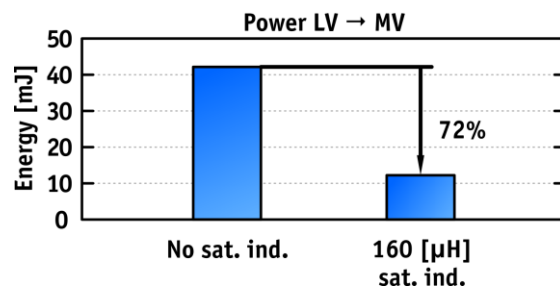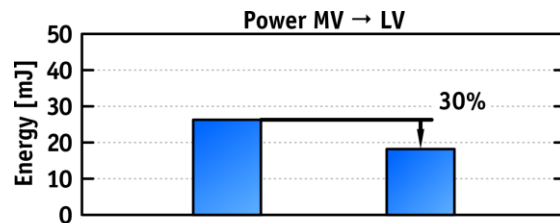
## Enhancement - Saturable Inductor

- Loss Reduction for Both Directions of Power Flow



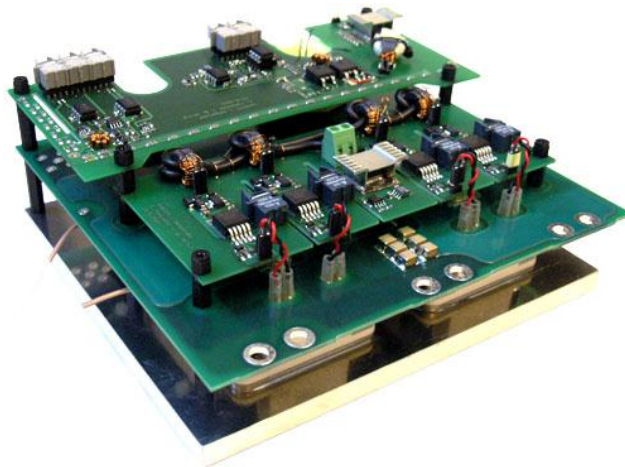
## Modular MV Side

- ▶ **Modular Construction due to MF + MV**
- ▶ **1.7 kV IGBT Used in NPC Structure**



▲ 1.7kV PT IGBT NPC Module

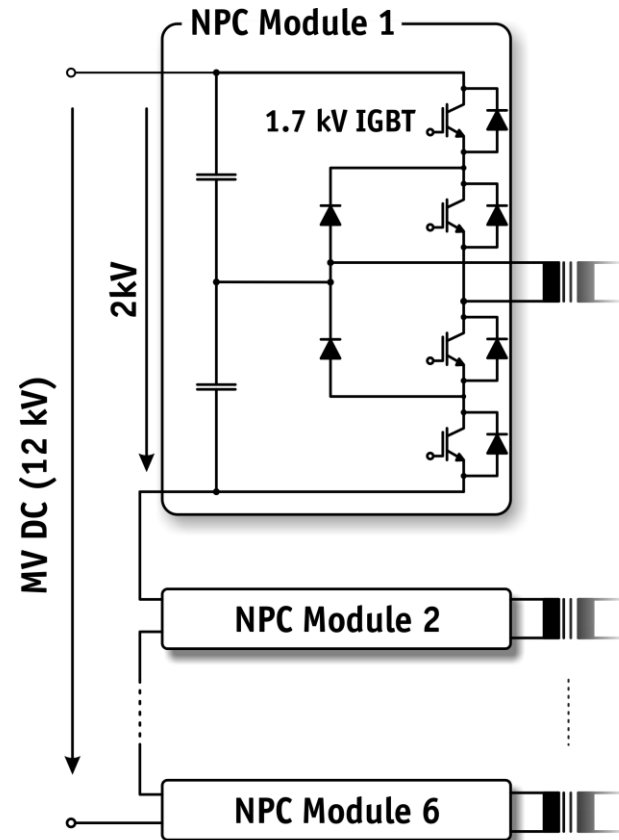



▲ Stacked MV side NPC Modules

## Details on The MEGA Cube

*Low-Voltage Side*  
*1.2kV - 20kHz*
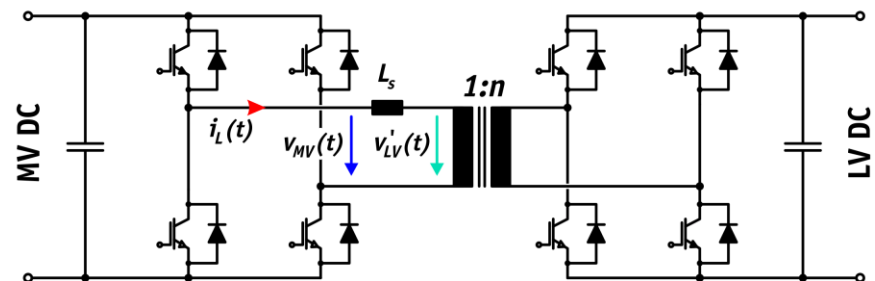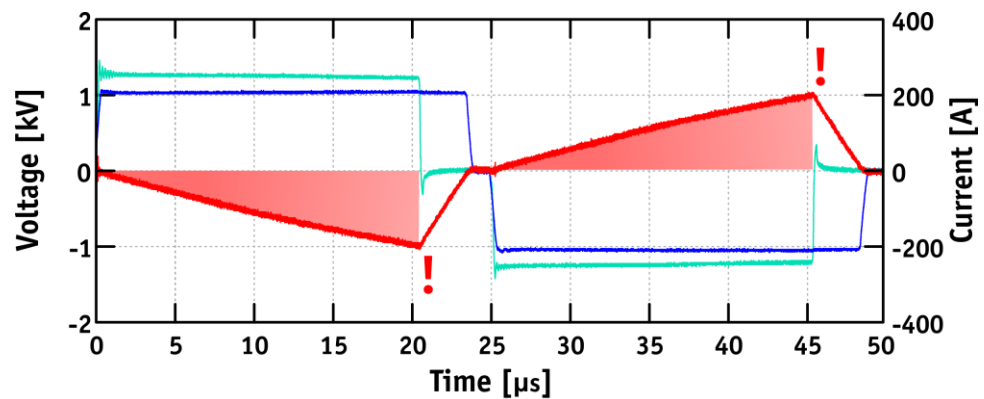
## DAB with Triangular Current



- High Currents Switched / Conducted on LV side
- ZCS on MV Side



Shown for Power  
Transfer from MV to LV Side
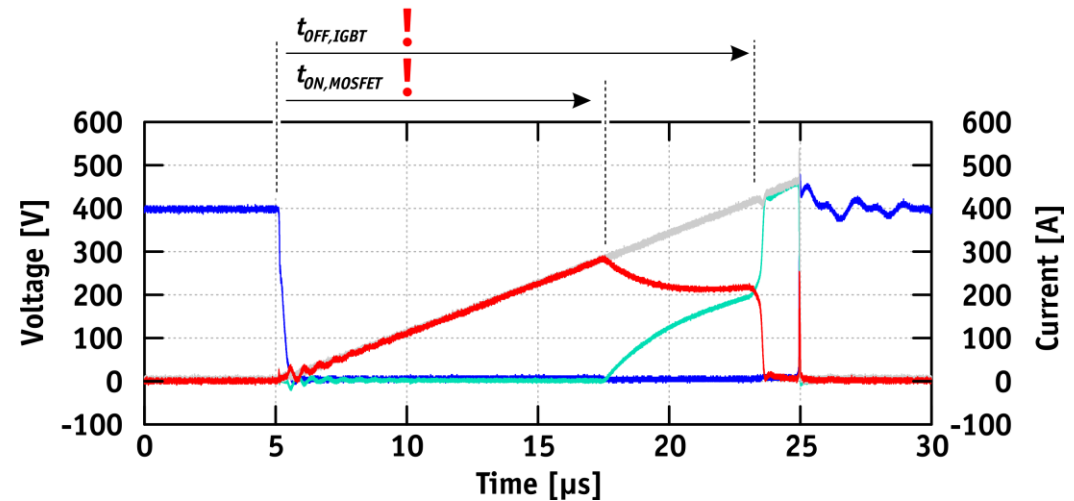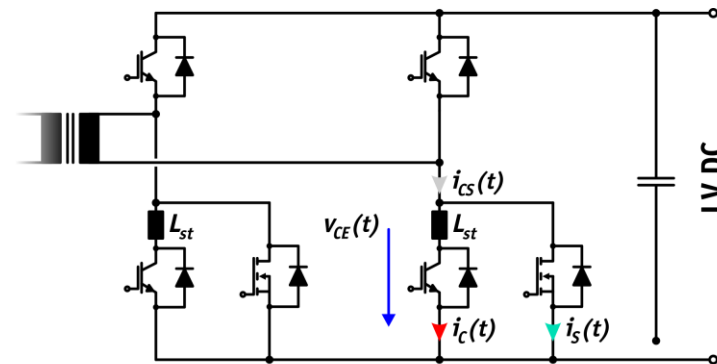
## Hybrid LV Switch


- Low Conduction Losses → IGBT
- Low Switching Losses → MOSFET





Circuit Schematic and  
Waveforms of LV Side  
Hybrid MOSFET/  
IGBT Full-Bridge
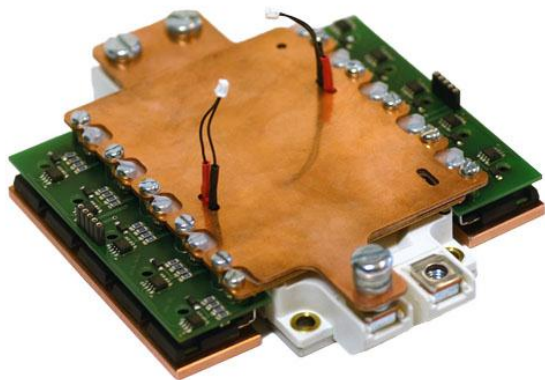
## Module-Based Hybrid Switch

- ▶ IGBT Module: Infineon 600V/600A Econopack
- ▶ MOSFET: Infineon 600V/70A "CoolMOS"



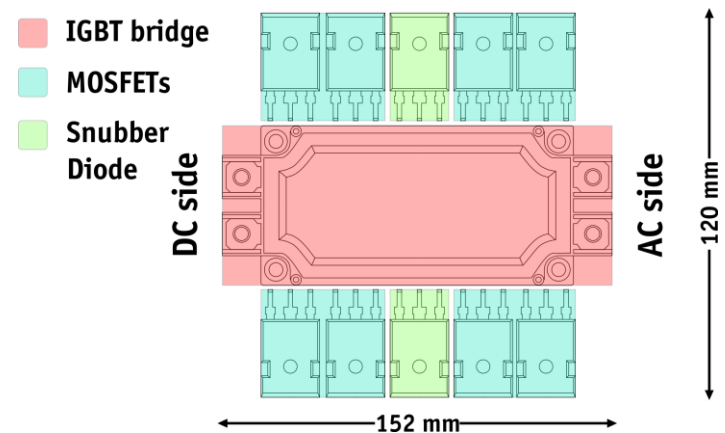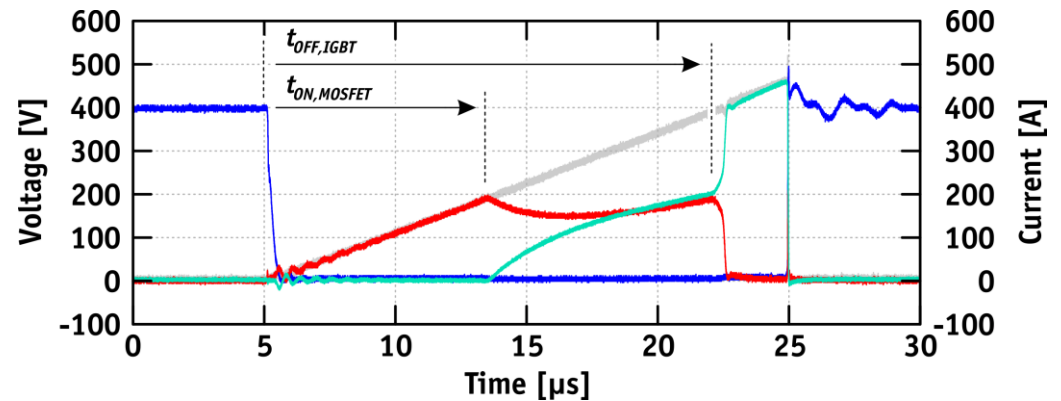
- ▲ Hybrid Switch Based on IGBT Bridge Leg Module





- ▲ Hybrid Switch Layout and Waveforms;  $t_{ON,MOSFET} = 8\mu s$  /  $t_{OFF,IGBT} = 17\mu s$
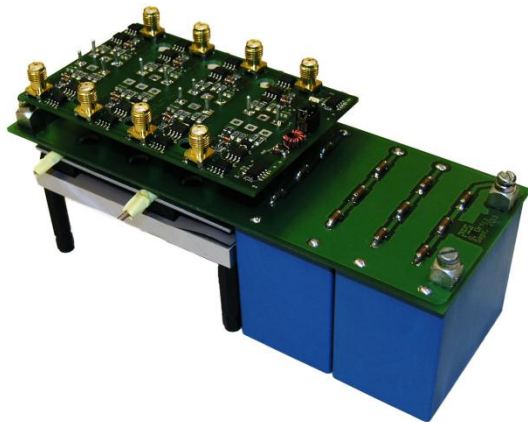
## Interleaved Hybrid Switch

- ▶ IGBT : Infineon 600V/75A Trench Field-Stop
- ▶ MOSFET: Infineon 600V/70A "CoolMOS"



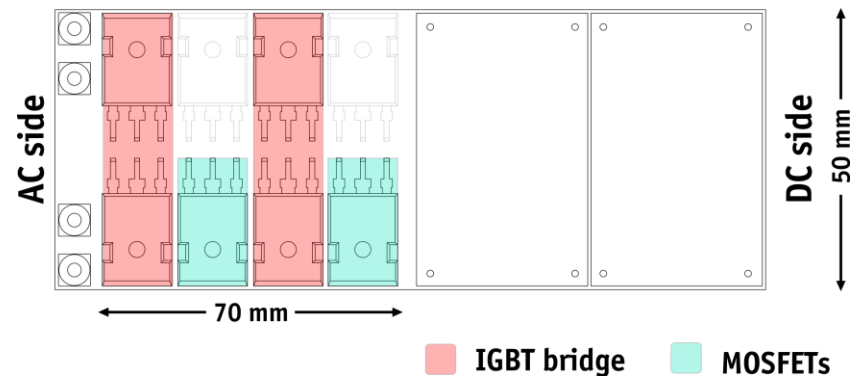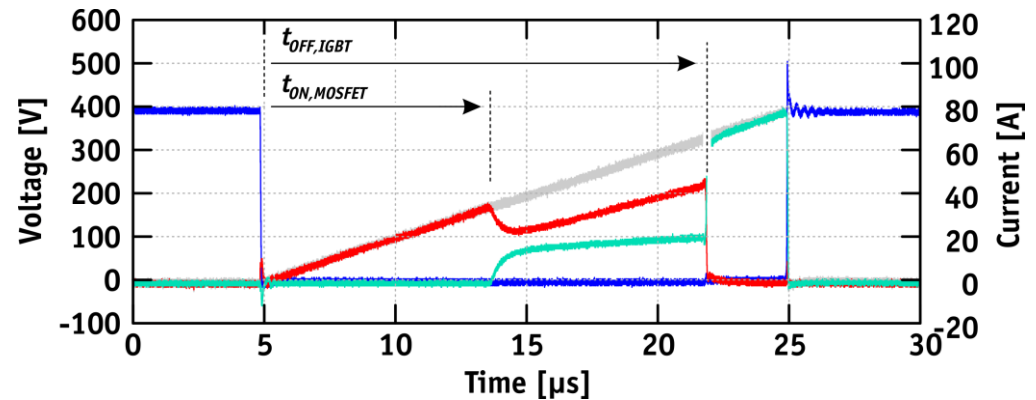
- ▲ Testbench for Interleaved Hybrid Switch




- ▲ Hybrid Switch Layout and Waveforms;  $t_{ON,MOSFET} = 8\mu s$  /  $t_{OFF,IGBT} = 17\mu s$
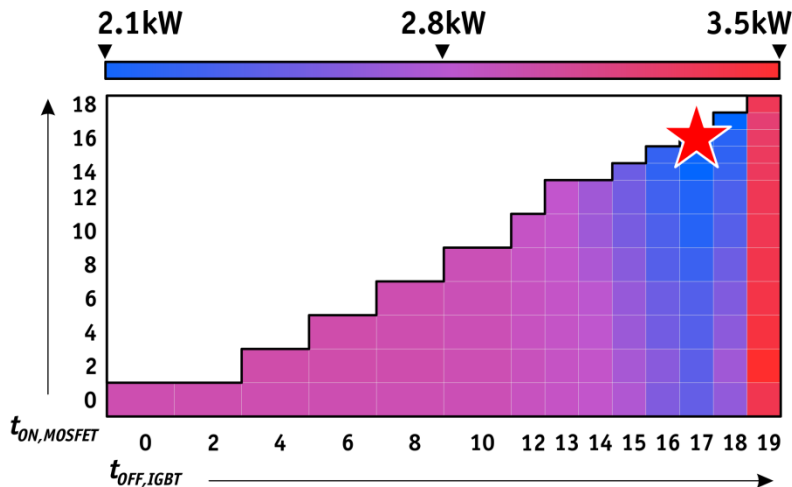
## Module-based vs. Interleaved Hybrid Switch

- Total Losses for a 166 kW Full-Bridge
- Mesh with Different  $t_{ON,MOSFET}$  and  $t_{OFF,IGBT}$  Showing Optimal Selection



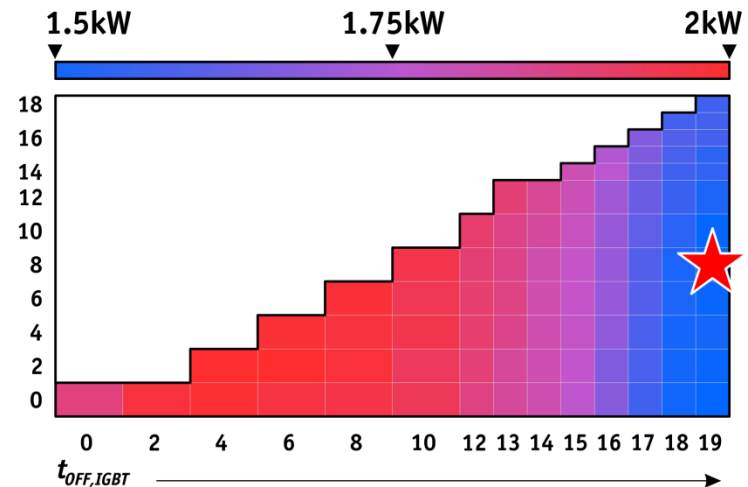▲ Module-Based Full-Bridge Total Losses  
(Conduction and Switching)




▲ Interleaved Full-Bridge Total Losses  
(Conduction and Switching)
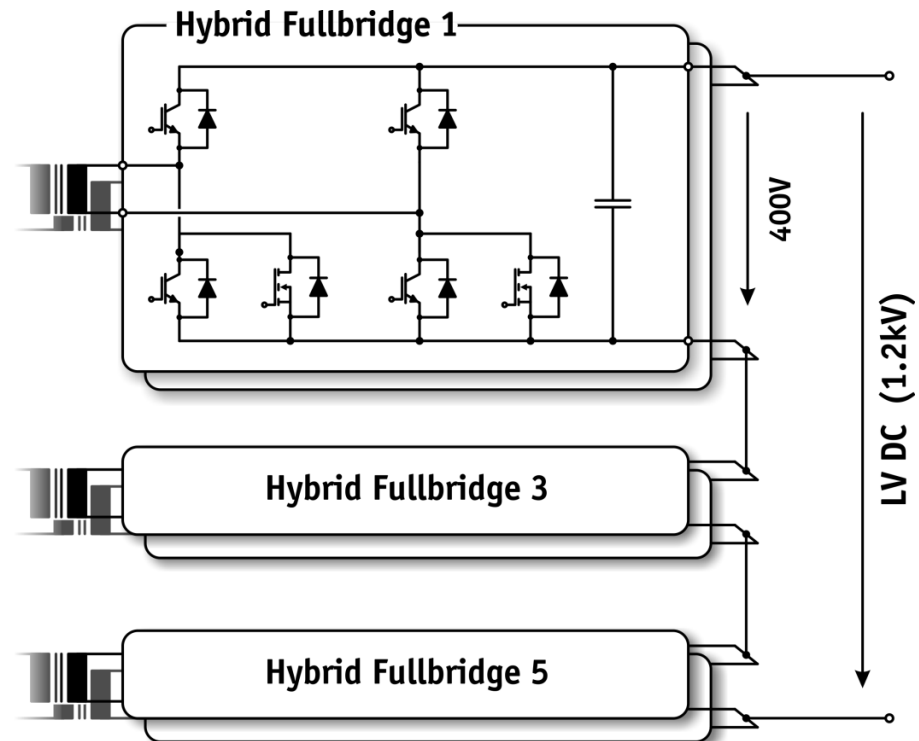
## Modular LV-Side Full-Bridge

- ▶ **6 Modules – 6 x 166 kW**
- ▶ **Hybrid Switch for Low Conduction/Switching Losses**



- ▲ **Testbench for Interleaved Hybrid Switch**



- ▲ **Structure of the Modular LV Side Comprising Hybrid Switch**

# MEGACube The Big Picture

## ► 6 Modules

## ► LV Side

Parallel/Series  
Connection of 400V  
Full Bridges

## ► MV Side

Series Connection  
of NPC Bridges

Module 1


Module 2

Module 3

Module 4

Module 5

Module 6

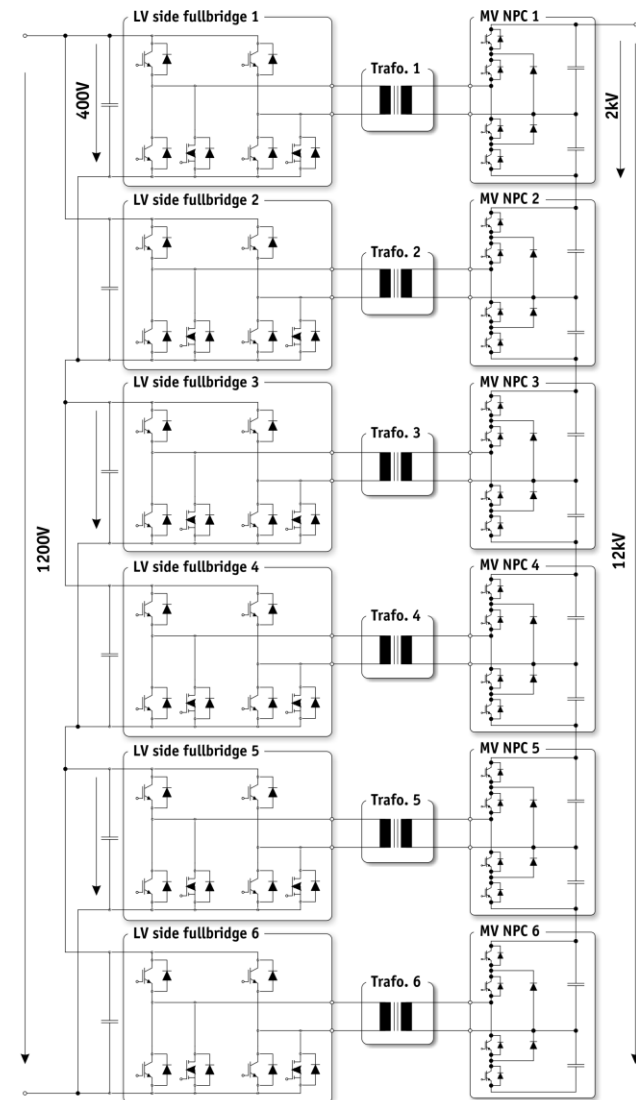


## Details on The MEGA Cube

*Transformer  
20kHz*
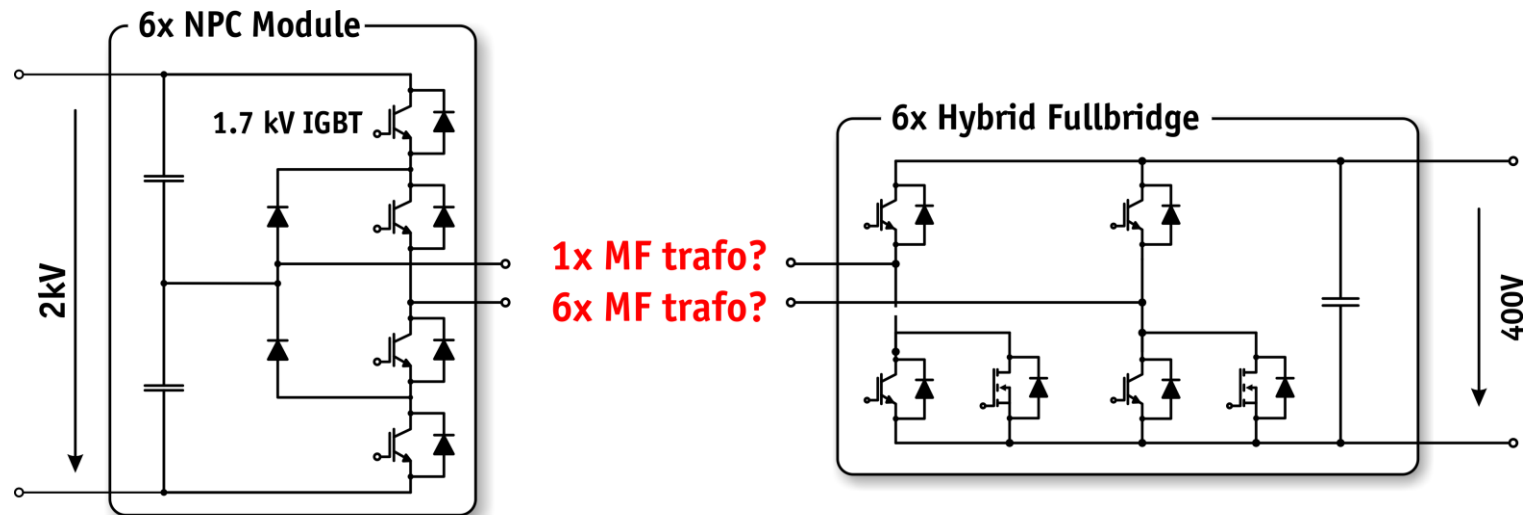
## How Many MF Transformers?

- Six Transformers (One per Module) **OR** One Transformer with 6 LV/MV Windings?



- ▲ MF Transformer - Link of MV NPC Module and LV Hybrid Switch Full-Bridge

## Option 1: Shell-Type



### ► E-Shape Based on Magnetic Core


- Vitroperm 500F / Heatsinks
- HV Litz Cable /
- LV Foil
- Air-Cooled

▲ Shell-Type Transformer with  
HV Cable Winding Designed for 1MW/20kHz
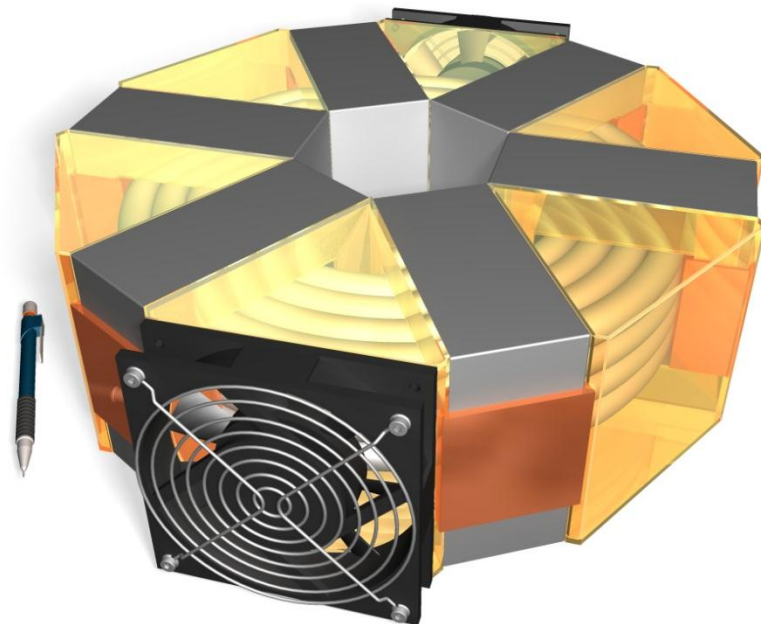
## Option 2: Matrix-Type

- ▶ Several Cores / Each Realizing a Transformer
- ▶ Realization of the Turns Ratio Through Parallel/ Series Connection


- Vitroperm 500F / Heatsinks
- HV Litz Cable /
- LV Foil
- Air-Cooled



▲ Matrix-Type Transformer with  
HV Cable Winding Designed for 1MW/20kHz
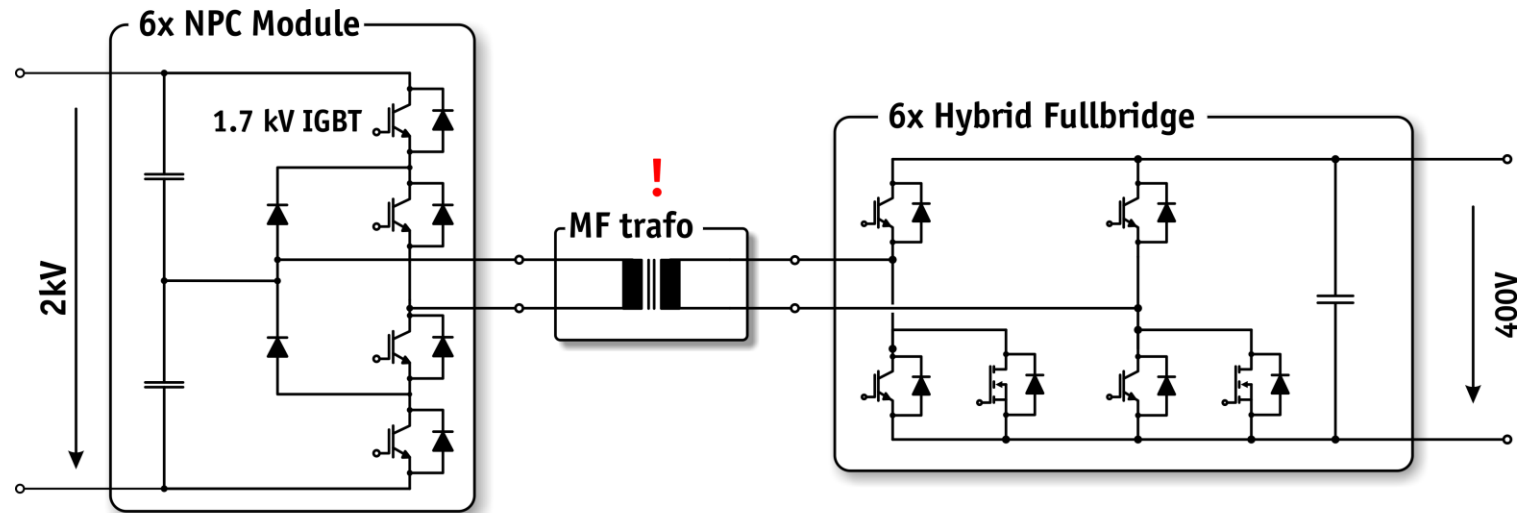
## MF Transformer Split up to 6 Modules

- ▶ Linking MV NPC Module and LV Hybrid-Switch Full-Bridge Modules
- ▶ Isolation + Voltage Adaptation



- ▲ Block Diagram of High-Power DC-DC Converter Utilizing Modular LV and MV Converters


# Transformer Optimization

- ▶ Parameter 1: Core Material
- ▶ Parameter 2: LV Winding  
Number of Turns
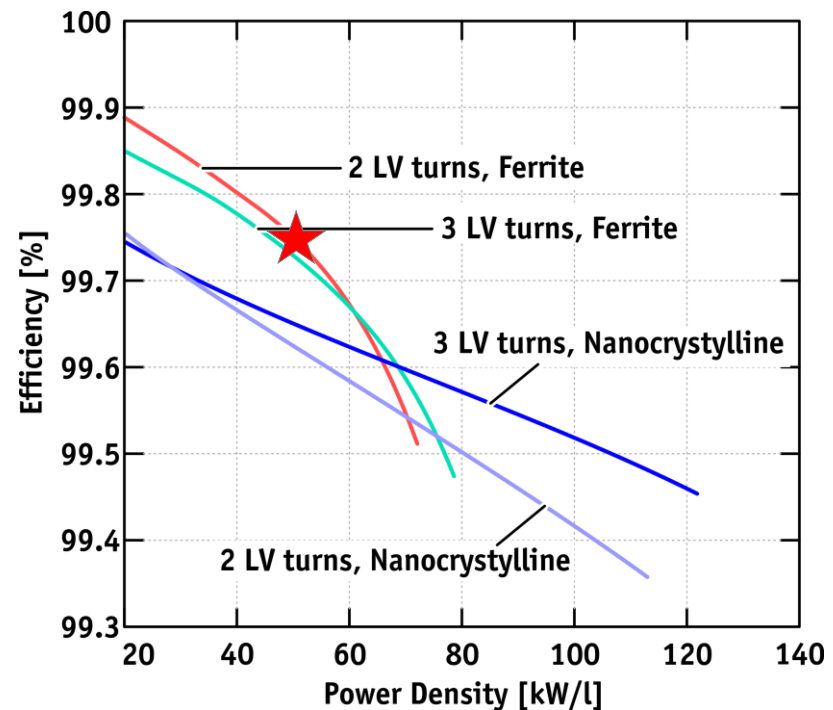
## Selected Design:


- 2 Turns LV Winding
- Stacked Ferrite Cores

Power Density vs. Efficiency Pareto  
Front of the 166kW Transformer


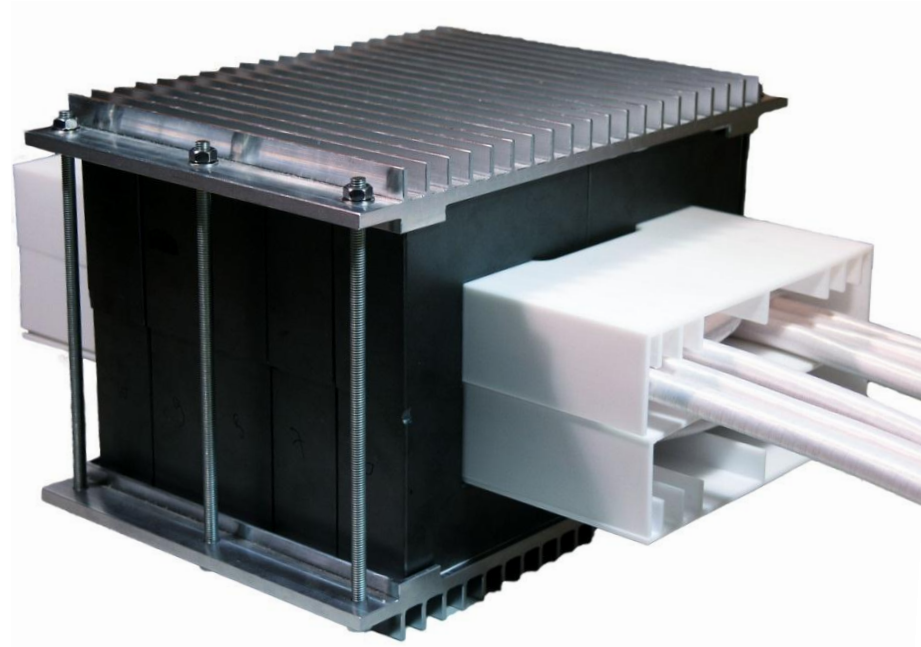
## Assembled Transformer

- ▶ 166kW / 20kHz
- ▶ Ferrite N87
- ▶ 9500 Strands Litz Wire
- ▶ PTFE Isolation Bobbin
- ▶ Forced Air Cooled
- ▶ Efficiency: 99.75%
- ▶ Power Density: 31kW/dm<sup>3</sup>




166kW / 20kHz Transformer

# Preventing Core Saturation

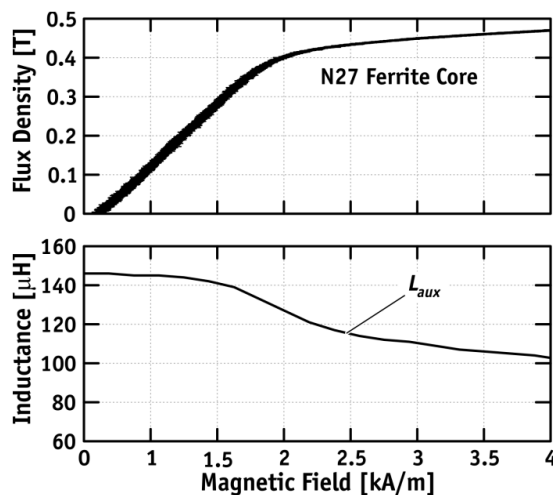
## ► Flux Density Transducer – Magnetic Ear



Shared Magnetic Path between  
Main and Auxiliary core



## ▲ Measured External Core Inductance


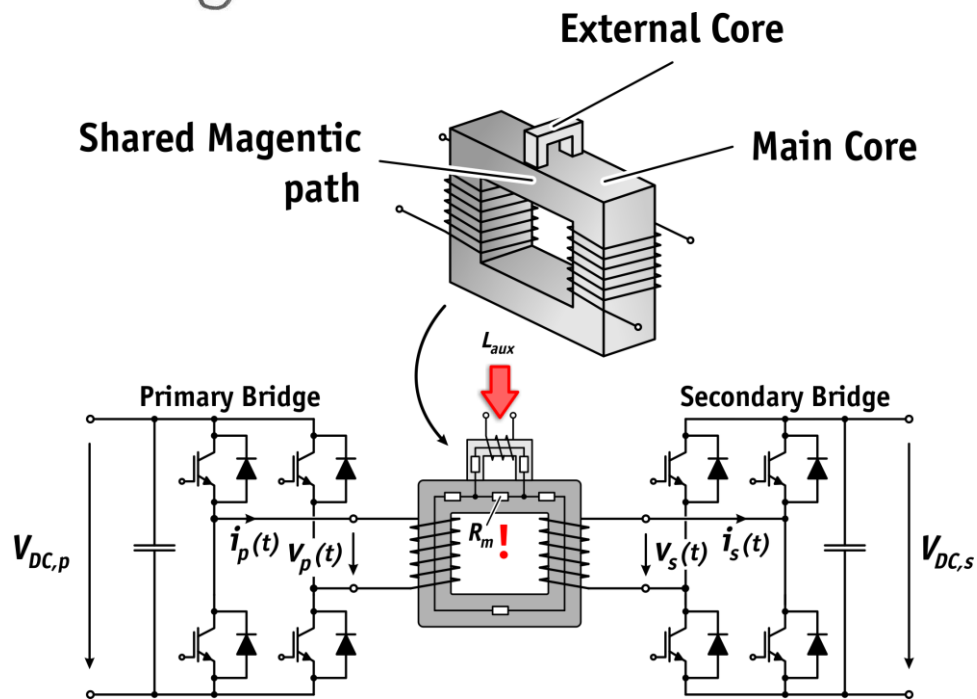


## ▲ Magnetic Ear Concept
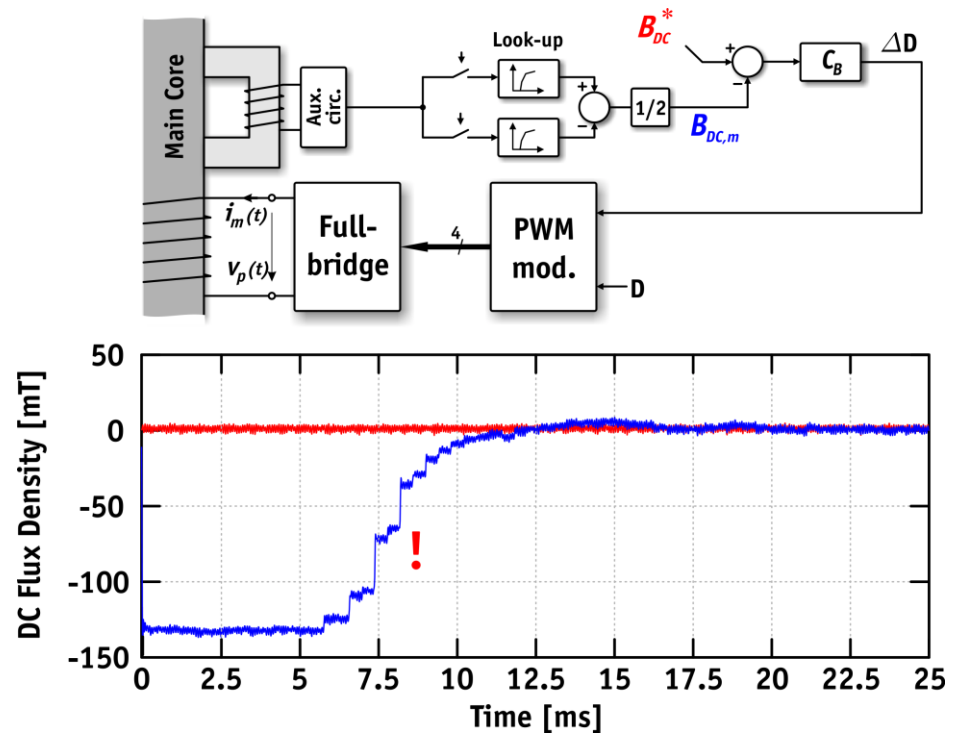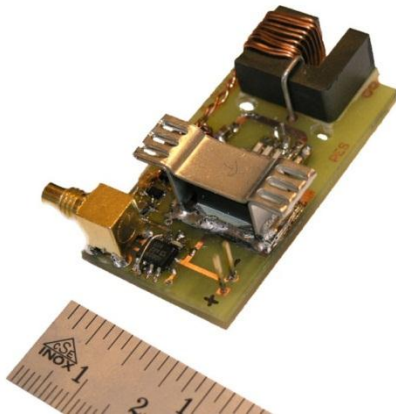
# Magnetic Ear



- Closed-Loop Control of the Flux Density in the Main Core
- Eliminate Problems of DC Magnetization




## — Conclusions / Outlook —

## Conclusions

- ▶ SST Technology Attractive for Traction / Renewable Energy / Smart Grids
- ▶ High-Power MF DC-DC Converters are a Key Component for SSTs
- ▶ 1MW / 20kHz MV to LV MEGA Cube under Construction @ ETH Zurich
- ▶ With Available Semiconductors → ZCS required on MV side
- ▶ Medium Voltage + Medium Frequency → Modular Arrangement
- ▶ Major Opportunities for WBG Power Semiconductors



**Done !**

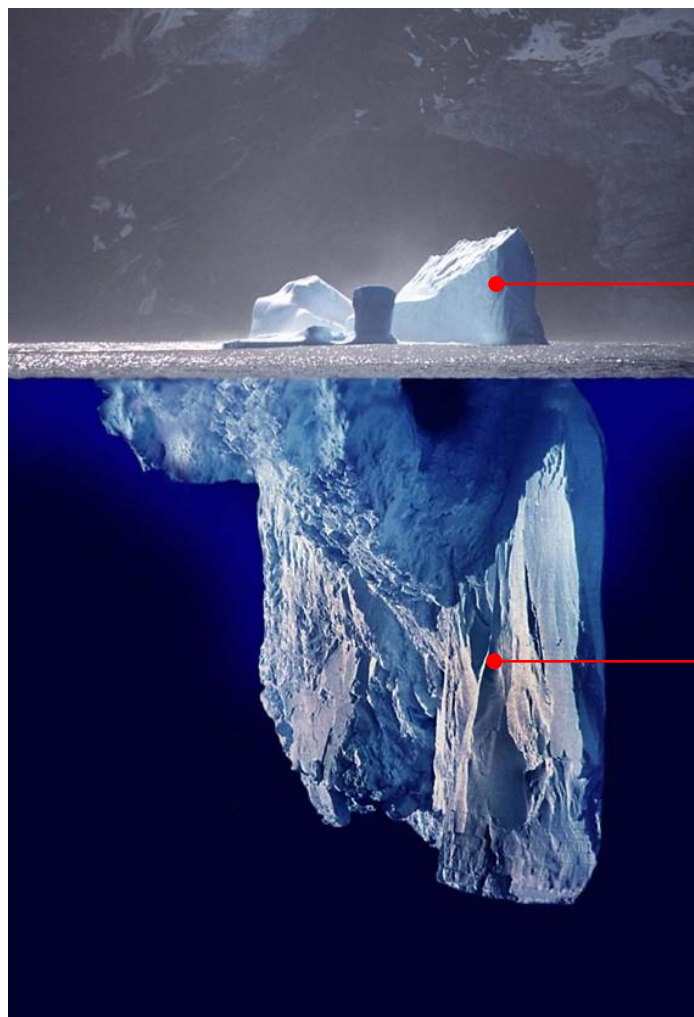

Done !

To be Done...

## Outlook

- ▶ Modeling/Simulation of ZCS Behavior
- ▶ High Performance Cooling Systems
- ▶ Magnetics Thermal Management
- ▶ High RMS Currents of Capacitors
- ▶ Partial Discharge Testing
- ▶ Common Mode Voltages of Stacked MV Modules
- ▶ Alternative Core Materials
- ▶ Winding Resonances
- ▶ High-Current Medium-Frequency Test Setup
- ▶ ...

# Thank You!

# Questions?

