

Google Little Box Reloaded

# ***How to Achieve 200W/in<sup>3</sup> & Beyond? Concepts - Evaluation - Barriers - Future***

**J. W. Kolar, D. Neumayr, D. Bortis**



Swiss Federal Institute of Technology (ETH) Zurich  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)



# Outline

- ▶ The Google Little Box Challenge
- ▶ *Little Box 1.0*
- ▶ *Concepts & Performances of Other Finalists*
- ▶ *Analysis of Advanced Concepts*
- ▶ *Optimization of Little Box 1.0*
- ▶ *Little Box 2.0*
- ▶ *Little Box 3.0 / Conclusions*



E. Hoene / FH IZM  
St. Hoffmann / FH IZM  
F. Zajc / Fraza  
O. Knecht  
F. Krismer  
M. Guacci  
L. Camurca  
M. Kasper

Acknowledgement

# Google Little Box Challenge


Requirements  
The Grand Prize  
Finalists & Finals



# LITTLE BOX CHALLENGE

Google | IEEE

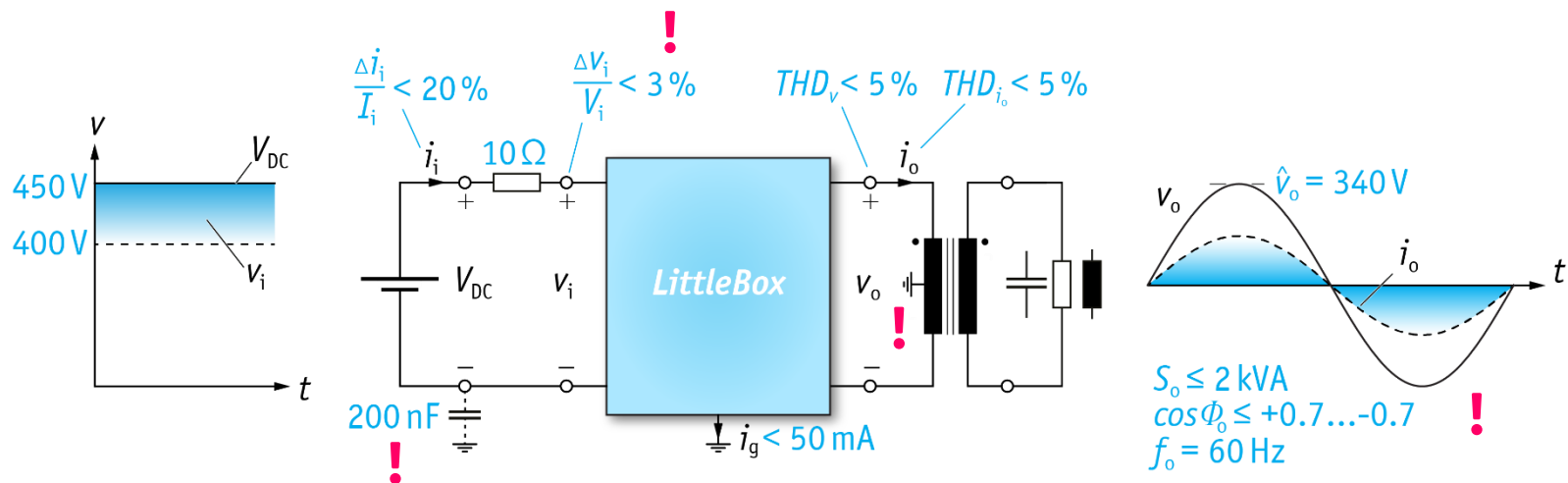- Design / Build the 2kW 1- $\Phi$  Solar Inverter with the Highest Power Density in the World
- Power Density  $> 3\text{ kW/dm}^3$  ( $> 50\text{ W/in}^3$ , multiply  $\text{kW/dm}^3$  by Factor 16)
- Efficiency  $> 95\%$
- Case Temp.  $< 60^\circ\text{C}$
- EMI FCC Part 15 B



■ Push the Forefront of New Technologies in R&D of High Power Density Inverters





## The Grand Prize

- Highest Power Density ( $> 50\text{W}/\text{in}^3$ )
- Highest Level of Innovation



**\$1,000,000**


### ■ Timeline

- Challenge Announced in Summer 2014
- **2000+ Teams Registered Worldwide**
- 100+ Teams Submitted a Technical Description until July 22, 2015
- **18 Finalists (3 No-Shows)**



# LITTLE BOX CHALLENGE Finalists

\* and FH IZM /  
Fraza d.o.o.

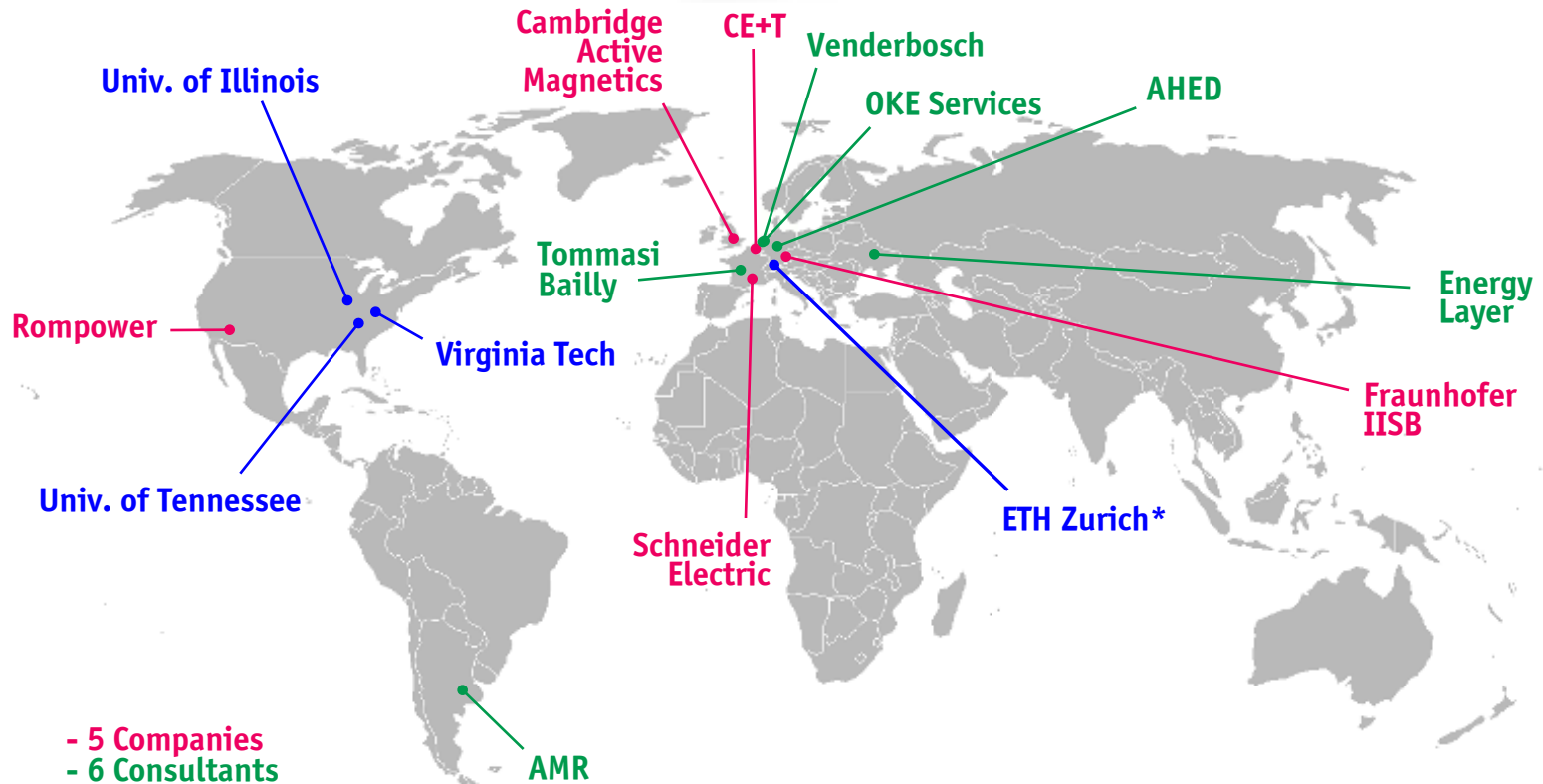


- 5 Companies
- 6 Consultants
- 4 Universities

15 Teams/Participants in the Final @ NREL



## LITTLE BOX CHALLENGE

## Final Presentations

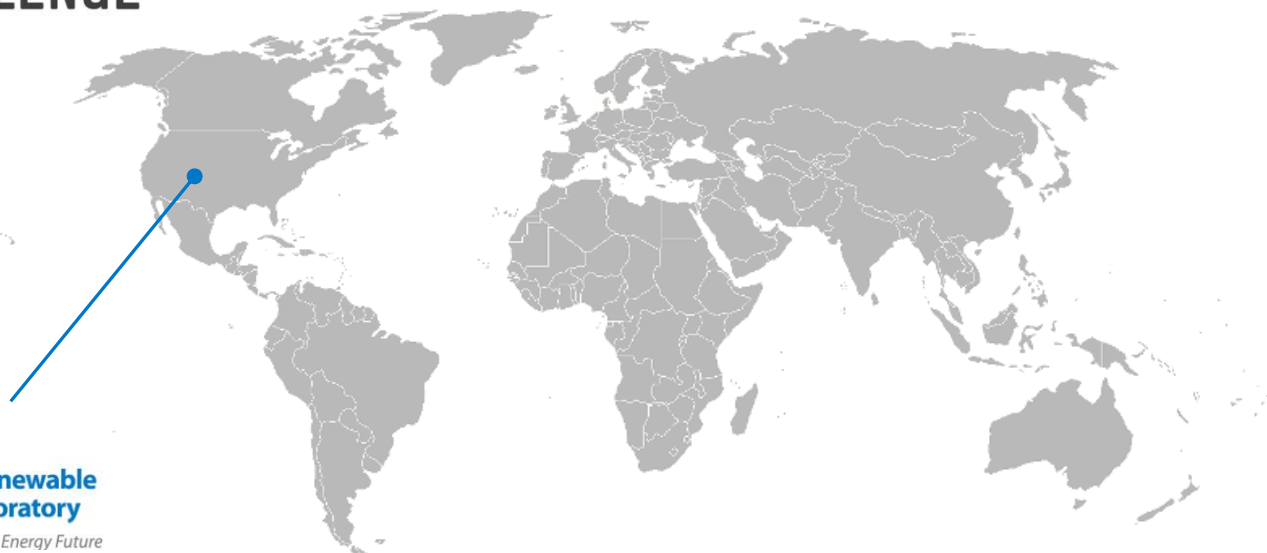

- Finalists Invited to NREL / USA
- **Presentations on Oct. 21, 2015**
- **Subsequent Testing by NREL**




## Little Box 1.0

Converter Topology  
Modulation & Control  
Technologies /Components  
Mechanical Concept  
Exp. Analysis


Acknowledgement



*Derivation of  
Converter Concept*

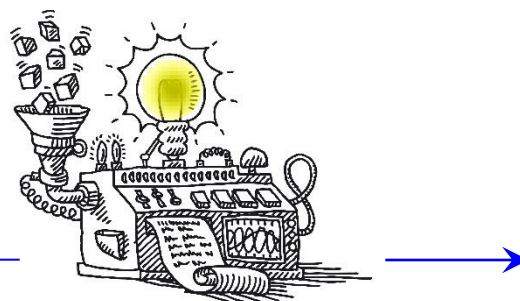


 *1- $\Phi$  Output Power  
Pulsation Buffer*




## Power Pulsation Buffer

### • Parallel Buffer @ DC Input

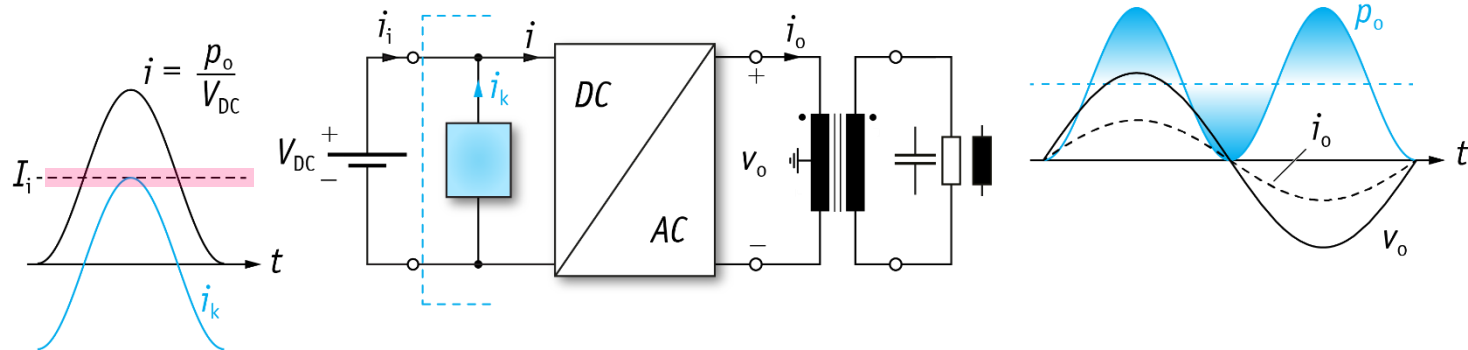

### • Series Buffer @ DC Input

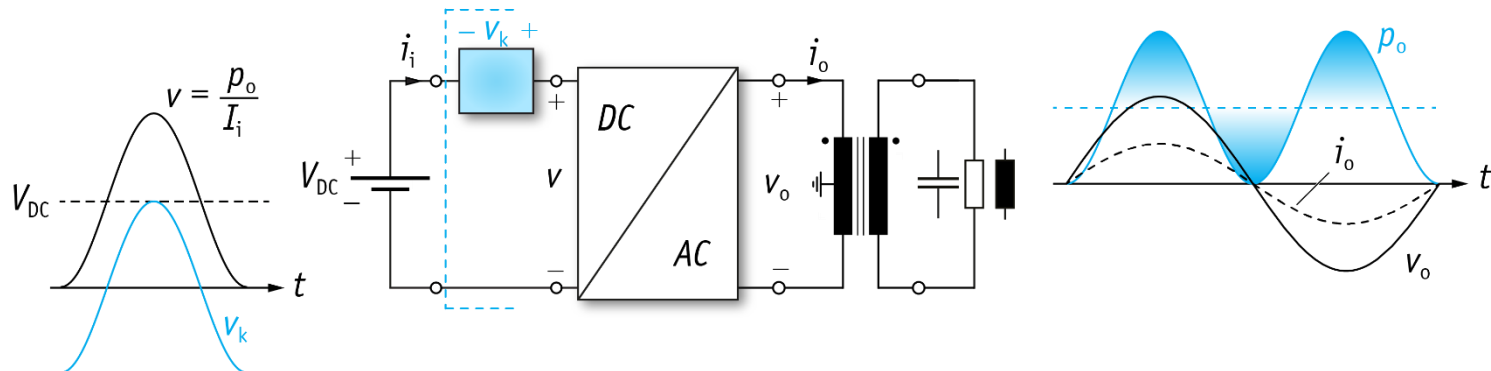


### ■ Parallel Approach for Limiting Voltage Stress on Converter Stage Semiconductors



## Passive Power Pulsation Buffer (1)


- Electrolytic Capacitor

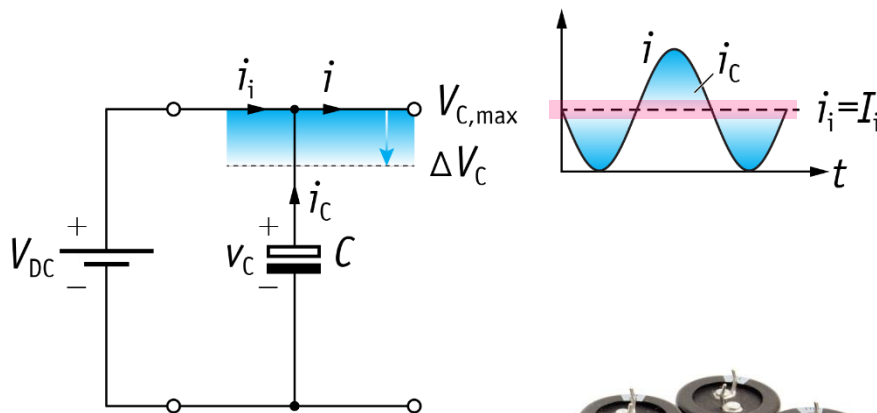

$$\begin{aligned}
 S_0 &= 2.0 \text{ kVA} \\
 \cos \Phi_0 &= 0.7 \\
 V_{C,\max} &= 450 \text{ V} \\
 \Delta V_C / V_{C,\max} &= 3 \%
 \end{aligned}$$



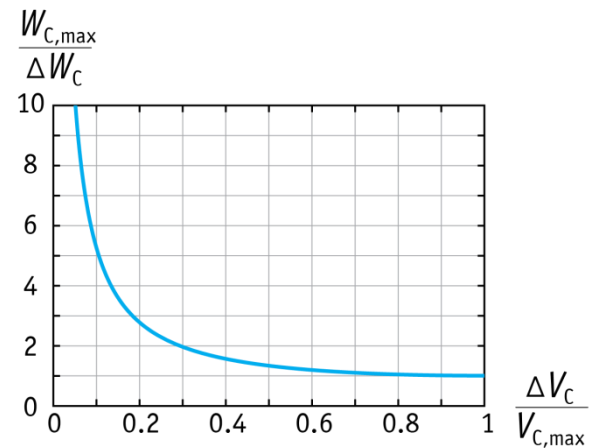
5 x 493µF/450 V
   
 $C = 2.46 \text{ mF}$



 ■  $C > 2.2 \text{ mF} / 166 \text{ cm}^3 \rightarrow$  Consumes 1/4 of Allowed Total Volume !








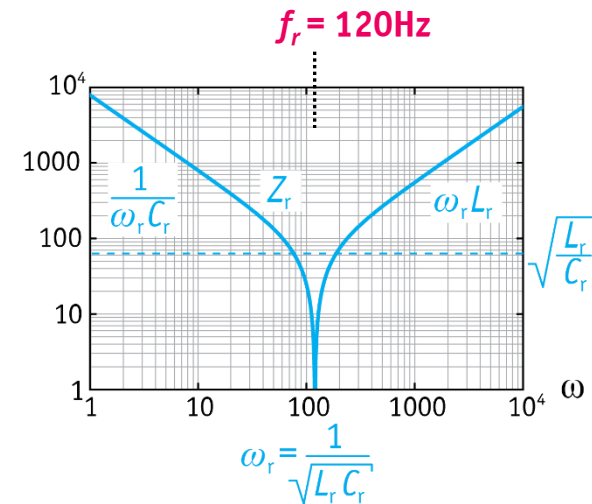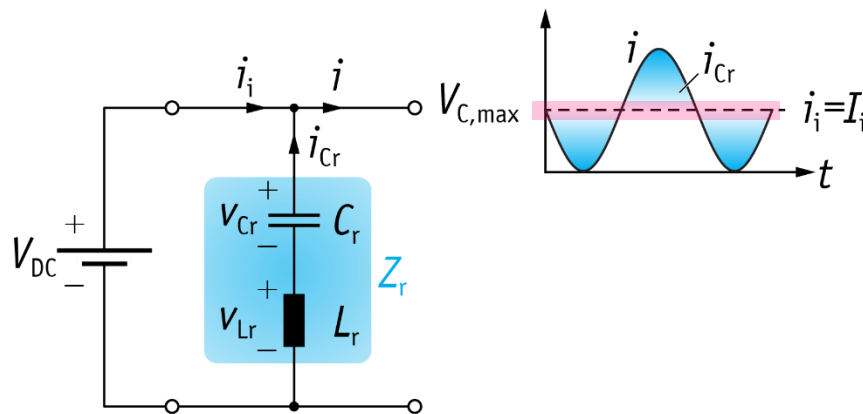
## Passive Power Pulsation Buffer (2)

- Series Resonant Circuit / Used in Rectifier Input Stage of Locomotives




- \*  $C_r = 20 \mu\text{F}$
- \*  $L_r = 127 \text{ mH} @ v_{Lr} = 400 \text{ V}$

■ Unacceptably Large Inductor Volume !




→ Electronic Inductor

 
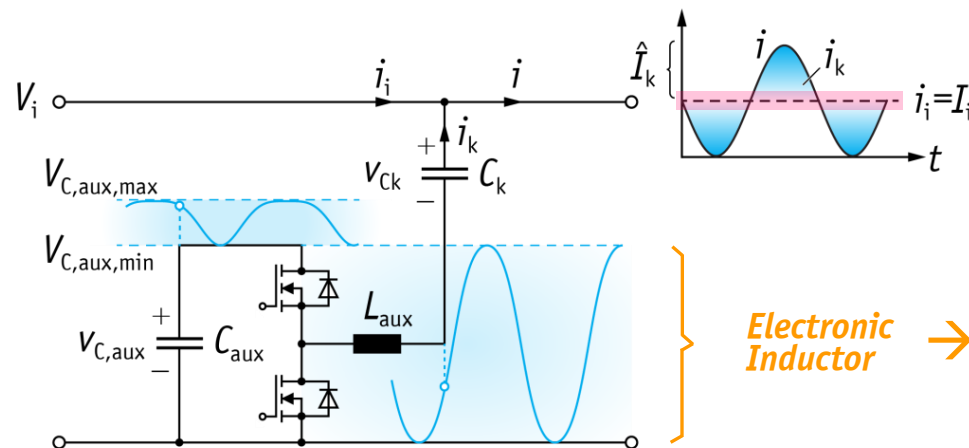
## Partial Active Power Pulsation Buffer

- Coupling Capacitor & “Electronic Inductor” Processing Only *Partial Power*




Electronic Inductor




- \* Ertl (1999)
- \* Enslin (1991)
- \* Pilawa (2015)

 - Low  $U_{C,aux} \rightarrow$  Low Converter Losses
- High Values of  $C_k, C_{aux}$  Required for Low  $U_{C,aux}$
- Full-Bridge Aux. Converter Allows Lower  $U_{C,aux}$




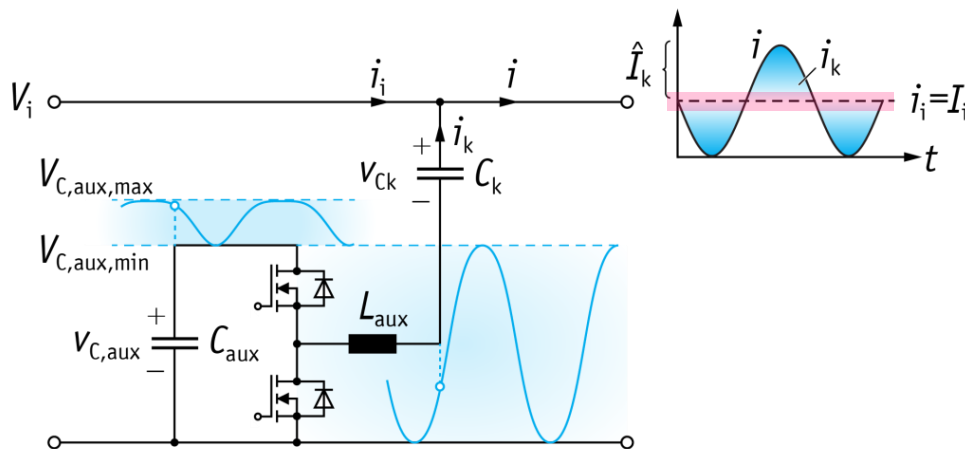
## Partial Active Power Pulsation Buffer


- Coupling Capacitor & “Electronic Inductor”



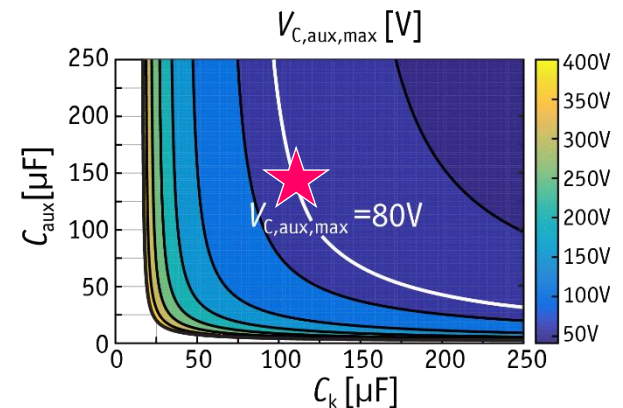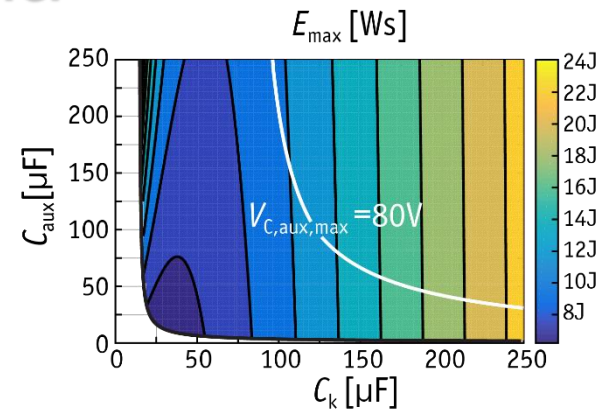- Low  $U_{C,aux} \rightarrow$  Low Converter Losses
- High Values of  $C_k, C_{aux}$  Required for Low  $U_{C,aux}$
- Full-Bridge Aux. Converter Allows Lower  $U_{C,aux}$



Properties of Full-Bridge Aux. Conv.

 

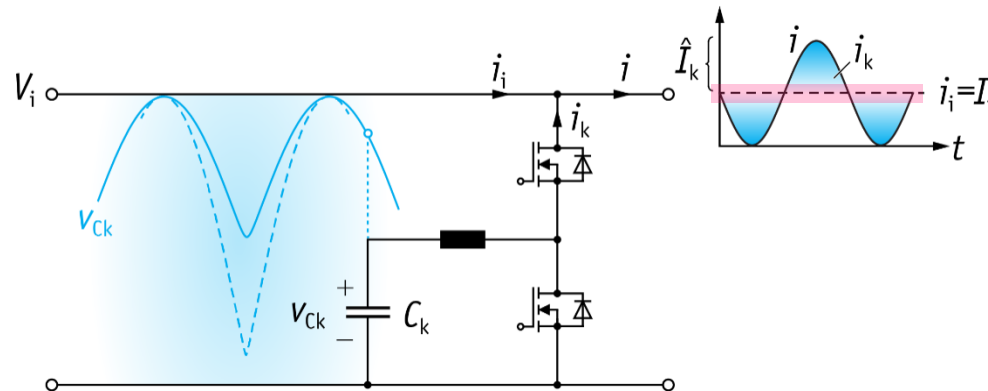
## Full Active Power Pulsation Buffer



\* Kyritsis (2007)

- Large Voltage Fluctuation Foil or Ceramic Capacitor
- Buck- or Boost-Type DC/DC Interface Converter
- Buck-Type allows Utilizing 600V Technology



CeraLink  
TDK




108 x 1.2  $\mu\text{F}$  / 400 V  
 $C_k \approx 140 \mu\text{F}$   
 $V_{Ck} = 23.7 \text{ cm}^3$

- Significantly Lower Overall Volume Compared to Electrolytic Capacitor



*Output Stage*  
*Topology / Modulation*


---

 


## Derivation of Output Stage Topology (1)

- Inversion of Basic 1- $\Phi$  PFC Rectifier Topology

- Boost-Type 1- $\Phi$  PFC Rectifier

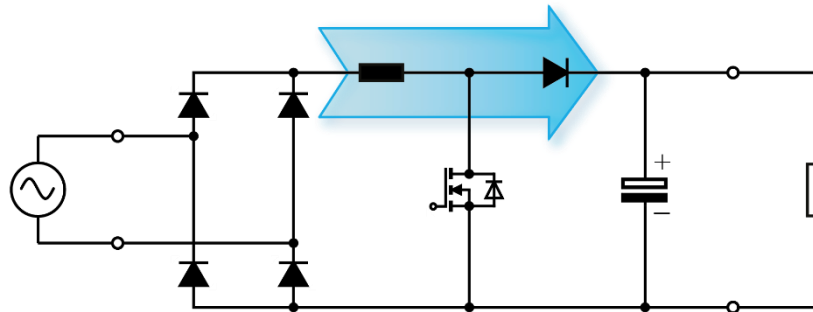



- DC/|AC| Buck Converter & Mains Frequency "Unfolder"

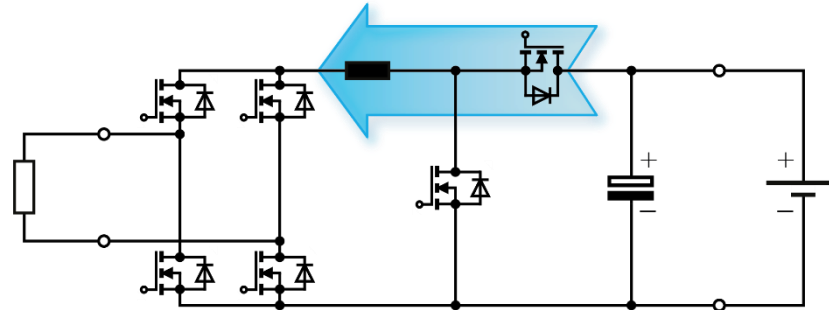


\* Erickson (2009) → Analysis Only for  $\cos \Phi = -1$

## ■ DC/ | AC | -Buck Conv. & Unfolder

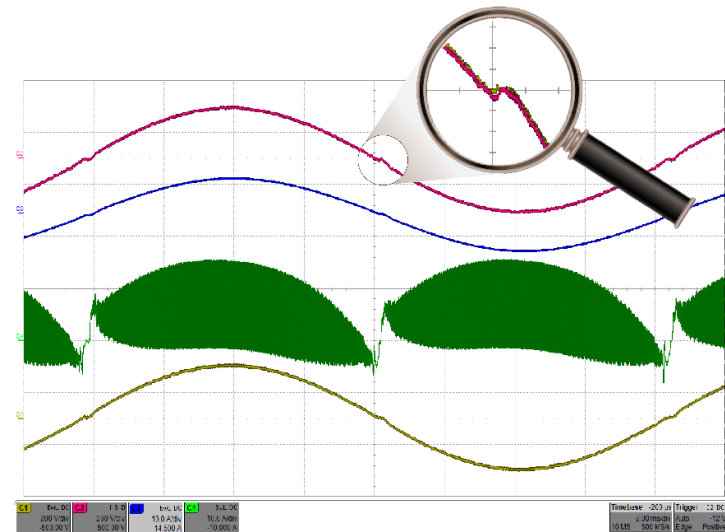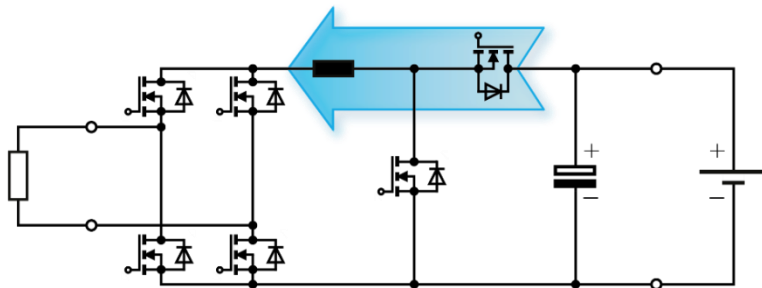- Only Single Bridge Leg for Current Shaping
- Distortion @ Voltage Zero Crossing




- For ZVS TCM Operation of Buck-Stage Bridge Leg | AC | Voltage Cannot be Controlled Down to Zero

 

## Advanced DC/|AC|-Buck Conv. & Unfolder

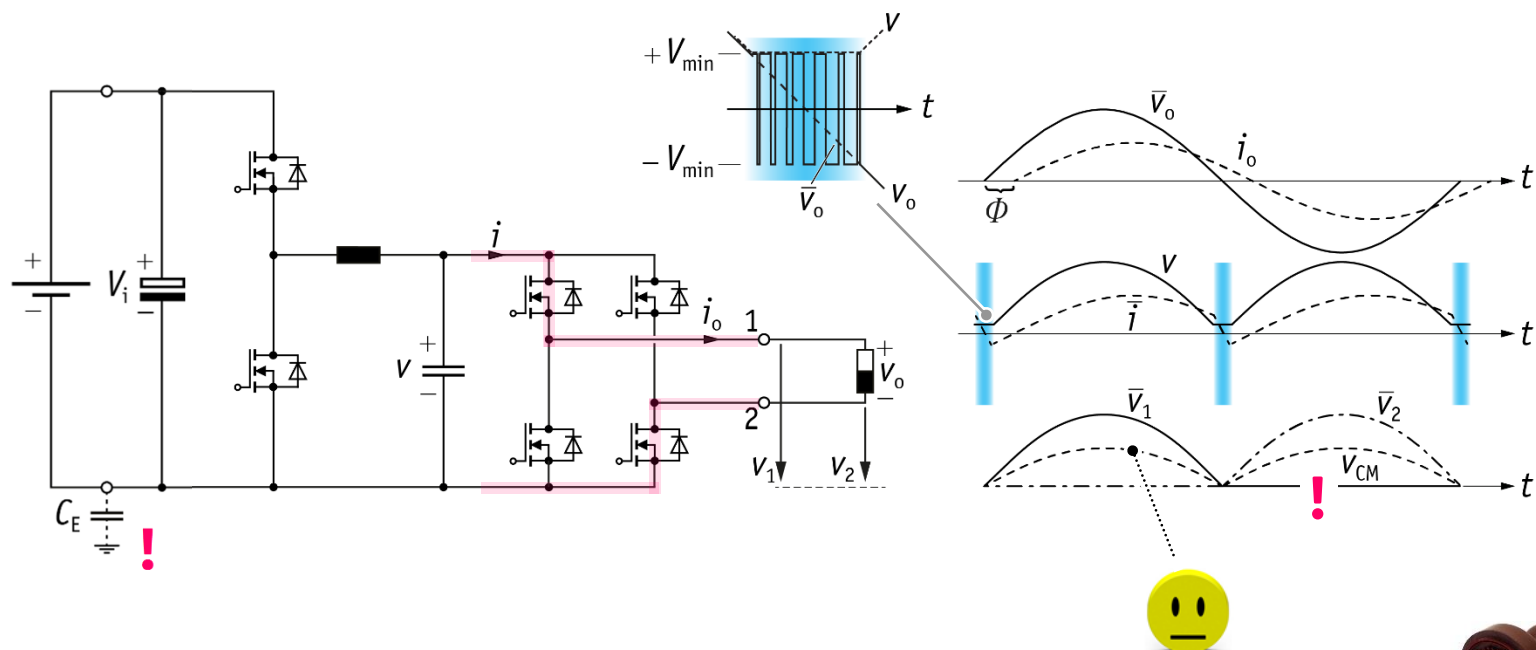
- Temporary PWM Operation of Unfolder @  $U < U_{min}$  to Avoid AC Current Distortion



 - CM Component of Output Voltage  $v_o$
- Larger EMI Filtering Requirement Due to Temporary High-Freq. Switching of Unfolder










# Full-Bridge AC/DC Conv. Topology

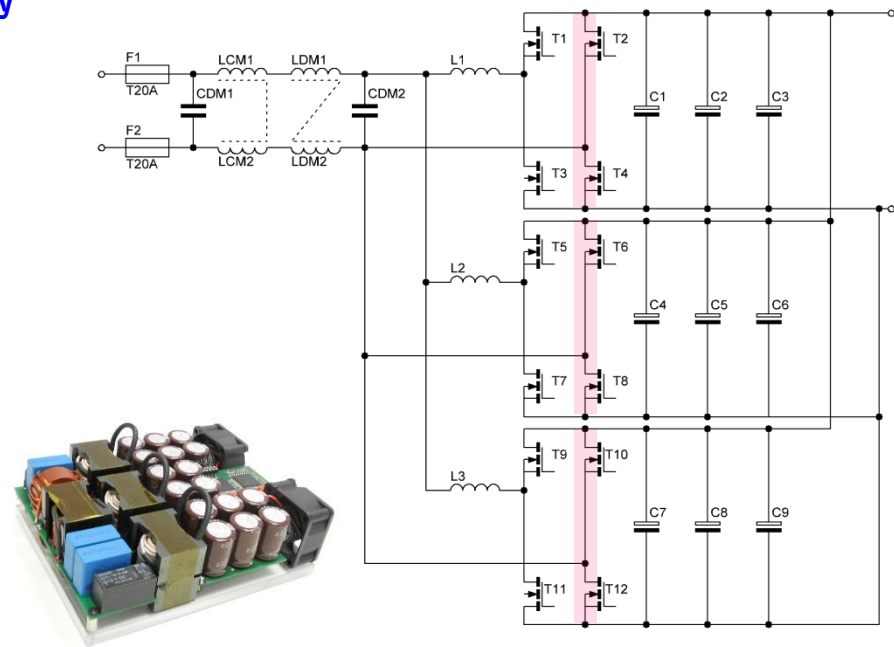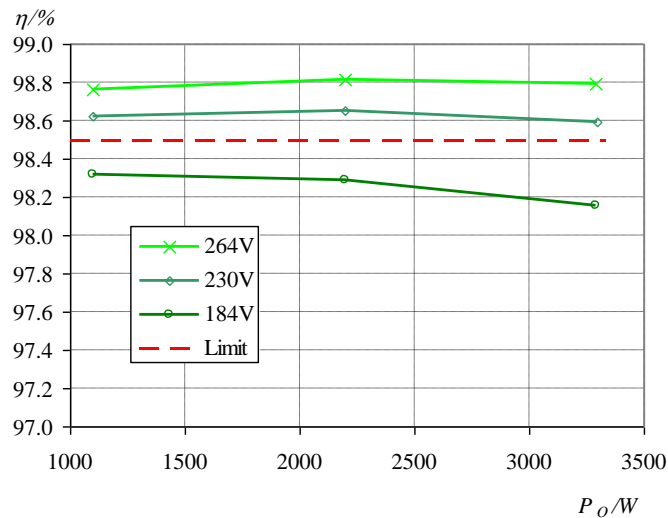- Example of (Bidirectional) 1- $\Phi$  Telecom Boost-Type PFC Rectifier
- Low-Frequency Operation of One Bridge Leg
- Interleaving for High Part Load Efficiency
- Si Superjunction MOSFETs




 ★ 72W/in<sup>3</sup> (4.5kW/dm<sup>3</sup>) incl. Holdup Capacitors @ 98.6%




# Advanced Full-Bridge DC/AC Conv. Topology

- New Control Concept - PWM Operation of Mains Freq. Bridge Leg @  $|u| < u_{0,\min}$

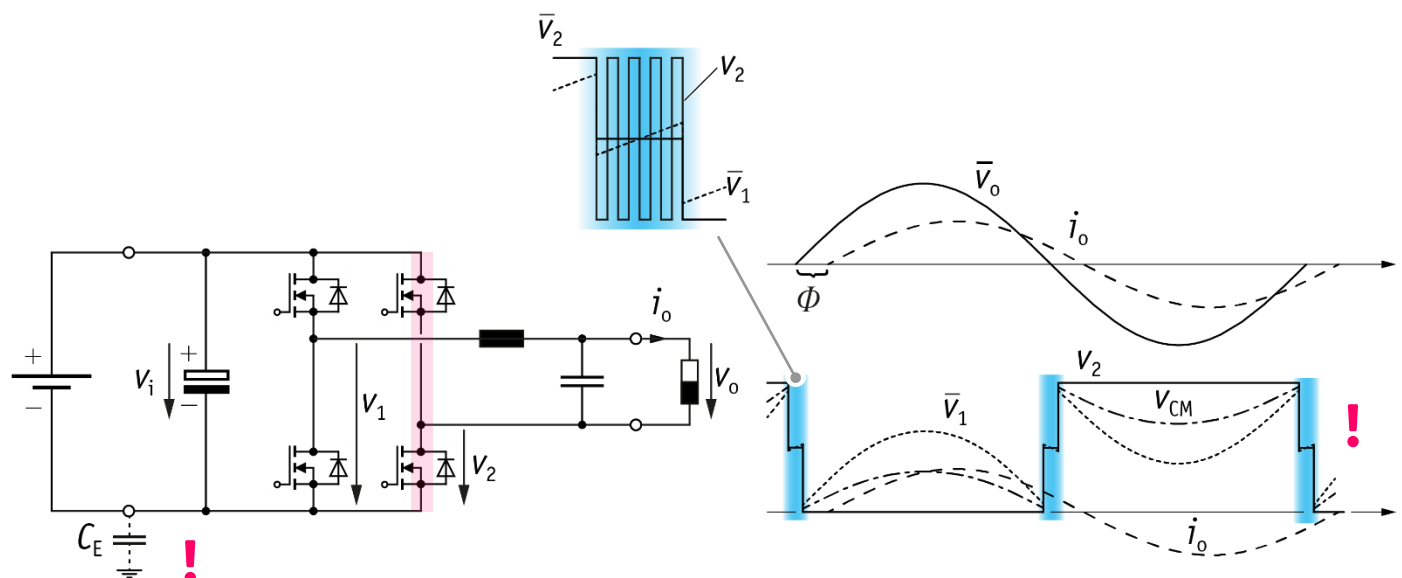


 
- CM Component  $u_{CM}$  of Generated Output Voltage
- Potentially Larger EMI Filtering Requirement





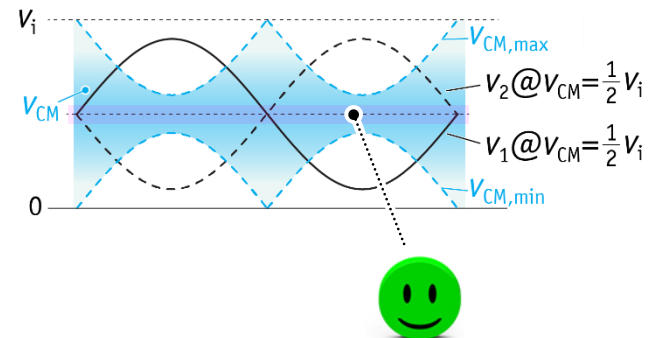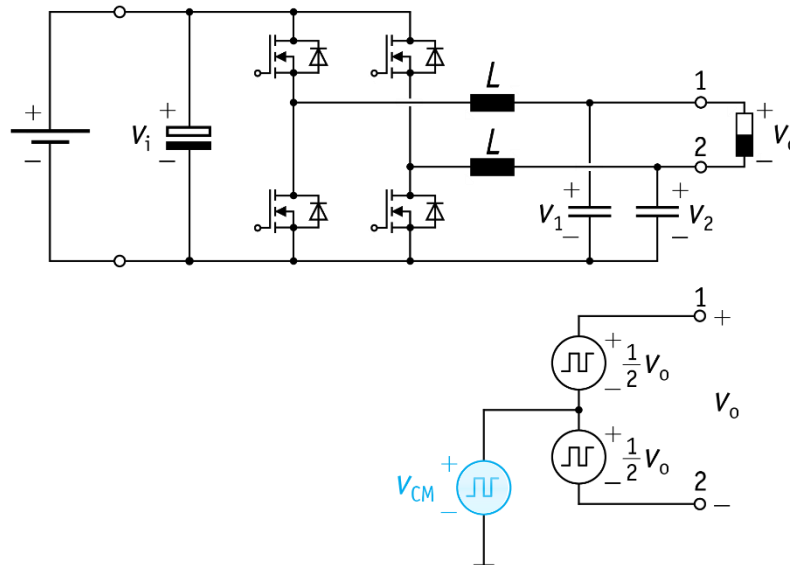
# Symmetric PWM Full-Bridge AC/DC Conv. Topology

- Symmetric PWM Operation of Both Bridge Legs
- No Low-Frequency CM Output Voltage Component







 - DM Component of  $u_1$  and  $u_2$  Defines Output  $u_o$
- CM Component of  $u_1$  and  $u_2$  Represents Degree of Freedom of the Modulation (!)



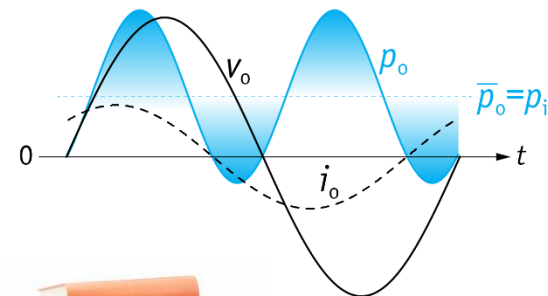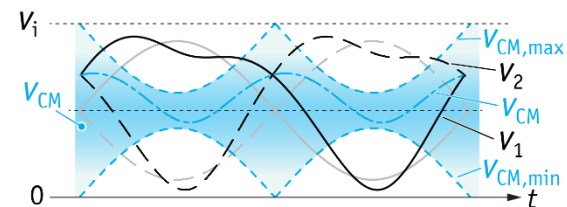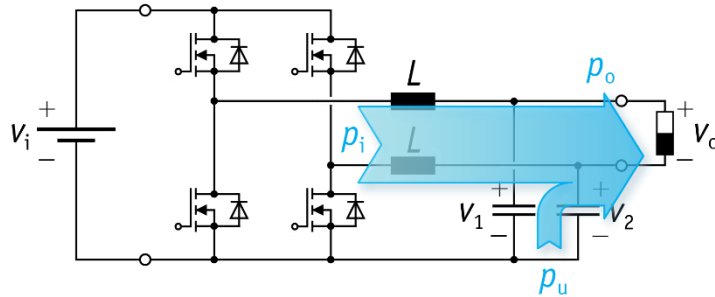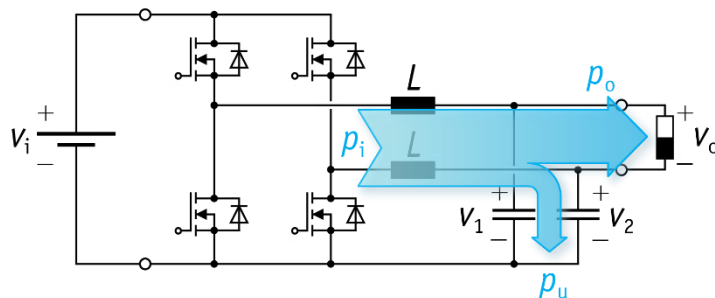
## Remark: AC Side Power Pulsation Buffer

- Full Bridge Output Stage / Full PWM Operation
- CM Reactive Power of Output Filter Capacitors used for Comp. of Load Power Pulsation



\* Serban (2015)

 - CM Reactive Power prop.  $2C$
- DM Reactive Power prop.  $\frac{1}{2}C$






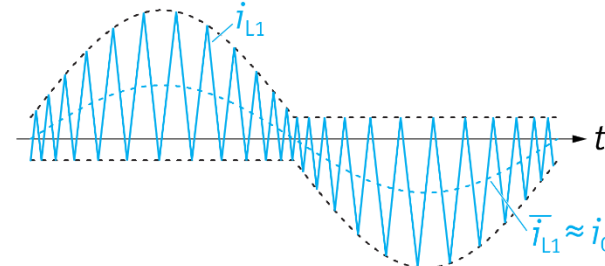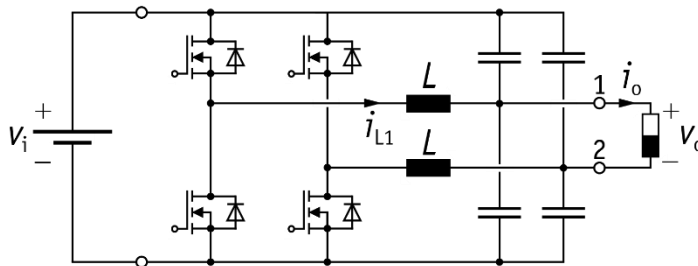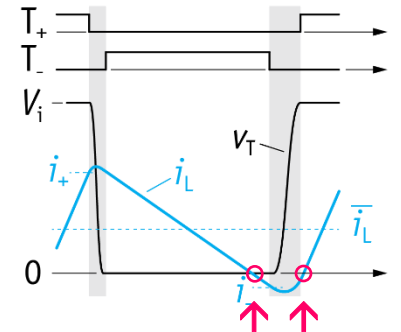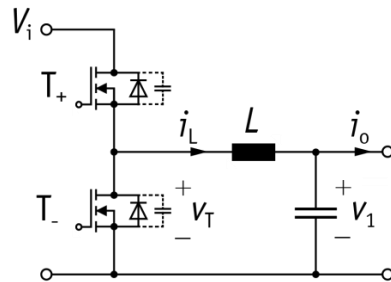
# ZVS of Output Stage / TCM Operation



\* Henze (1988)

- TCM Operation for Resonant Voltage Transition @ Turn-On/Turn-Off






- Requires Only Measurement of Current Zero Crossings,  $i = 0$
- Variable Switching Frequency Lowers EMI


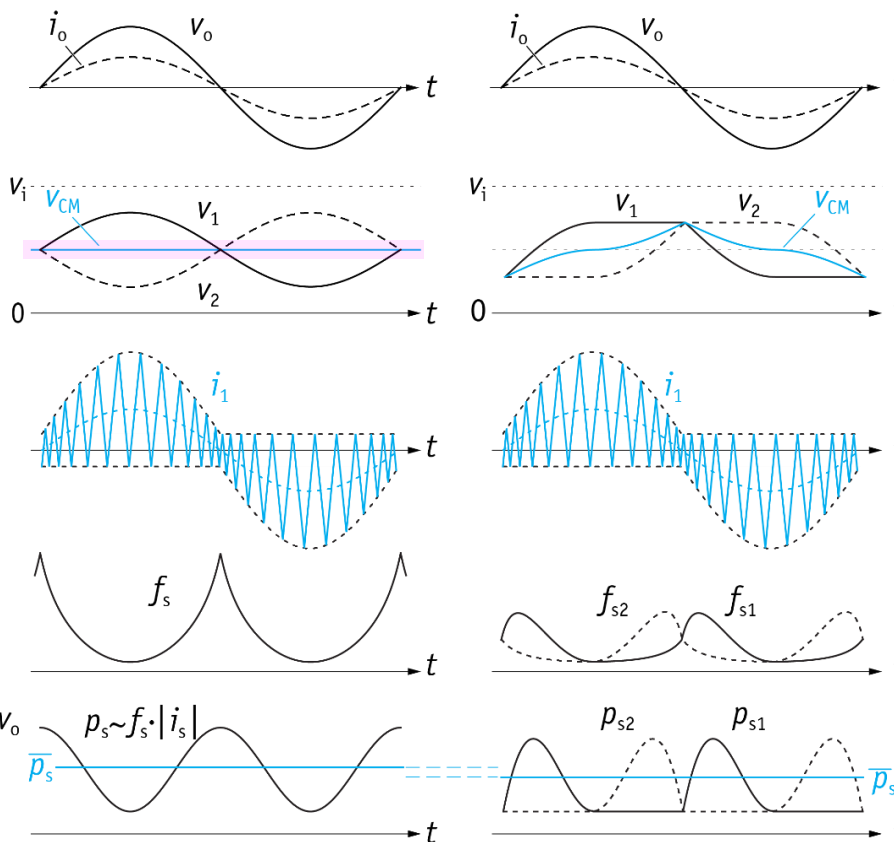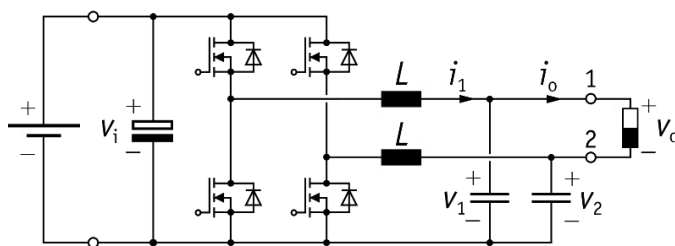
## CM-Enhanced TCM Modulation

- CM Comp. of  $u_1, u_2$  Changes Sw. Frequency
- Limits Sw. Frequency Variation
- Lower Sw. Losses








 
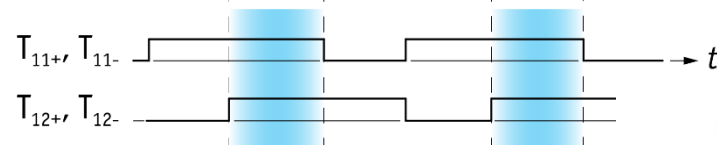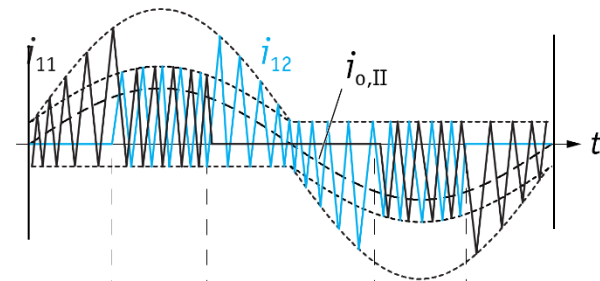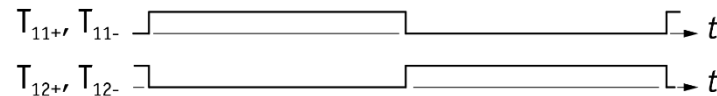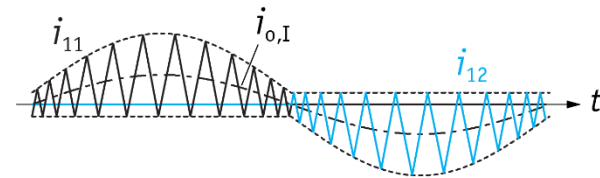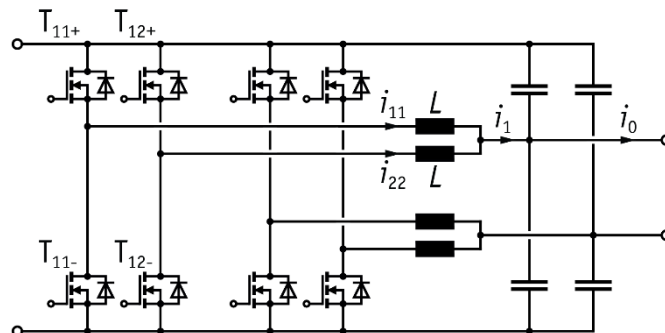
# 4D-Interleaving




- Interleaving of 2 Bridge Legs per Phase - Volume / Filtering / Efficiency Optimum
- Interleaving in Space & Time – Within Output Period
- Alternate Operation of Bridge Legs @ Low Power
- Overlapping Operation @ High Power



 - Opt. Trade-Off of Conduction & Switching Losses / Opt. Distribution of Losses






## Remark: iTCM Inverter Topology


- TCM : Challenging Inductor Design  $\rightarrow$  Superposition of HF & LF Currents
- iTCM: Adding LC-Circuit between Bridge Legs  $\rightarrow$  Separation of LF & HF Currents  $\rightarrow L \gg L_B$

### – TCM

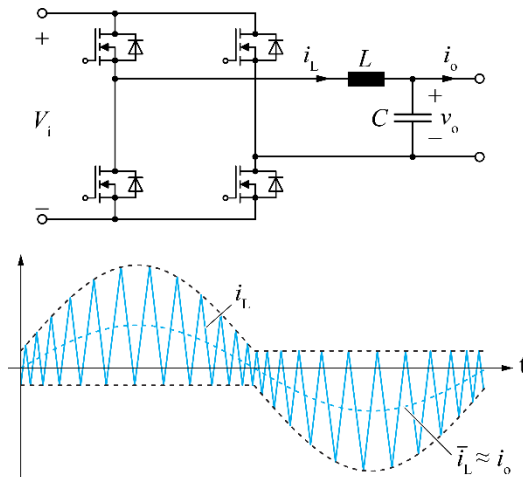

- Low Output Current Ripple
- PWM Modulation Applicable
- Dedicated LF and HF Inductor Designs Possible

### – iTCM

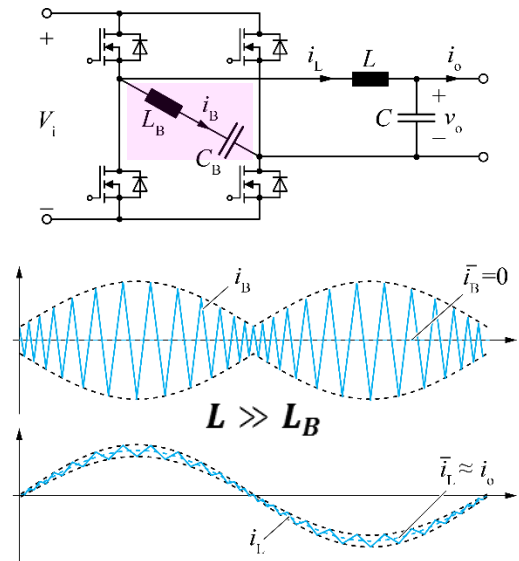


- $\rightarrow$  Reduced Filtering Effort
- $\rightarrow$  Simple Control Strategy
- $\rightarrow$  Improved Converter Efficiency

\* P. Jain (2015)






 

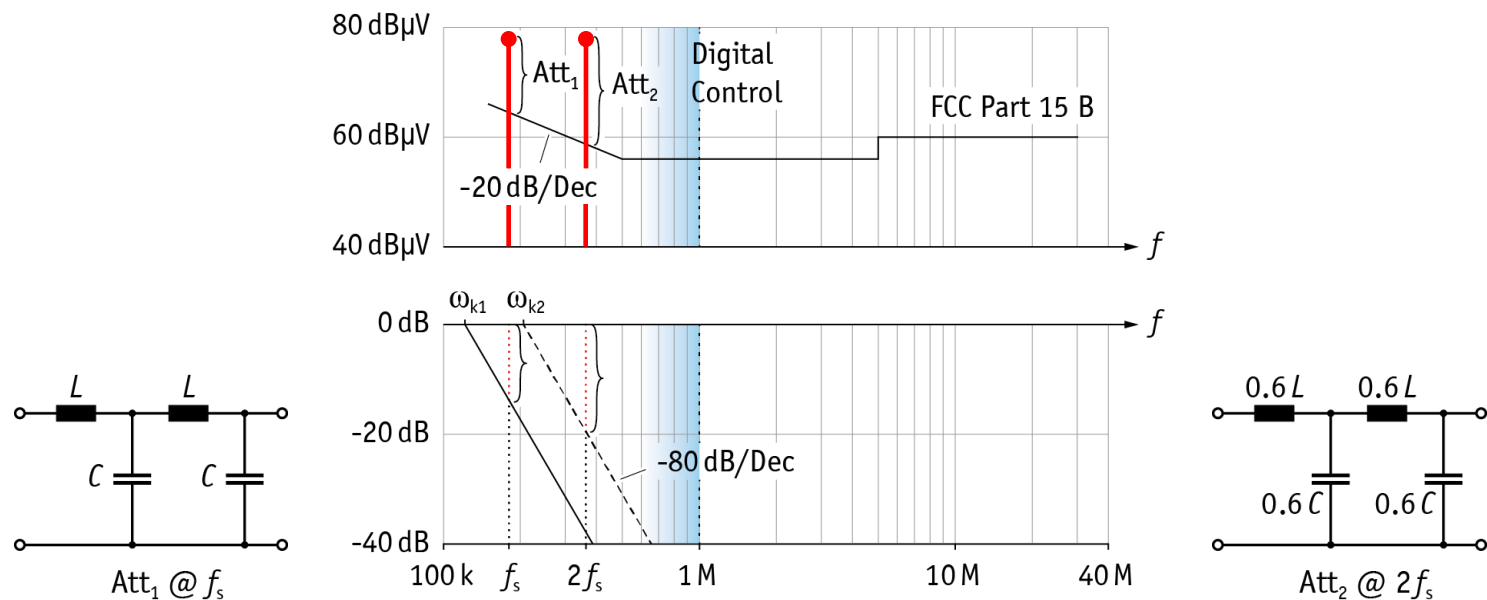
## Selection of Switching Frequency

- Significant Reduction in EMI Filter Volume for Increasing Sw. Frequency



 
- Doubling Sw. Frequ.  $f_s$  Cuts Filter Volume in Half
- Upper Limit due to Digital Signal Processing Delays / Inductor & Sw. Losses – Heatsink Volume


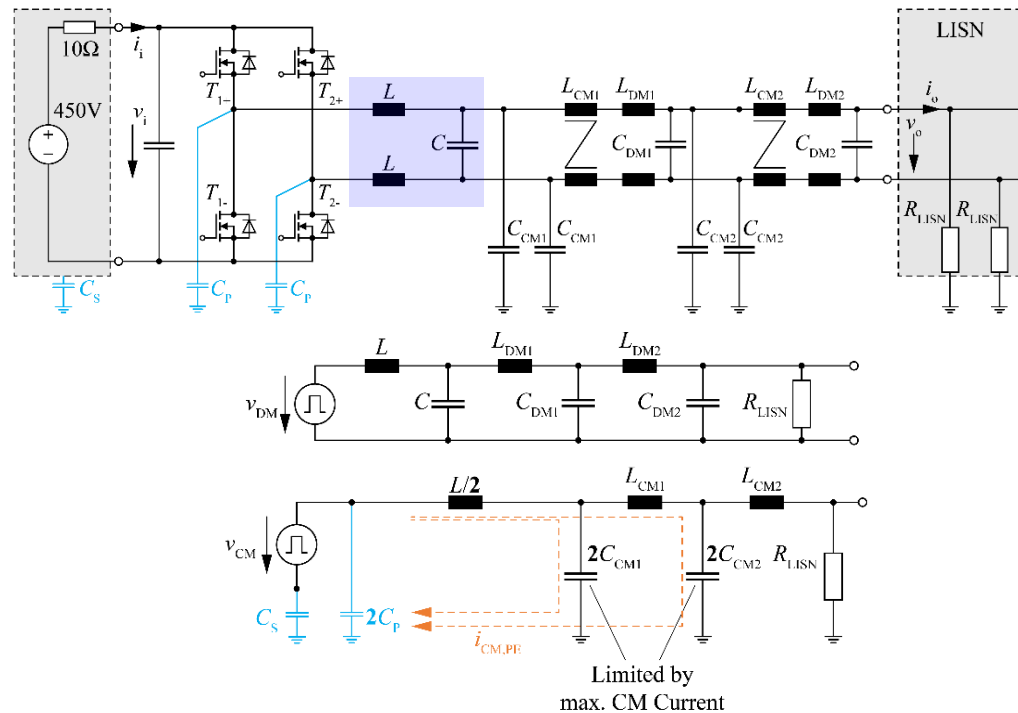
# EMI Filter Topology (1)

- Conventional Filter Structure


- DM Filtering Between the Phases
- CM Filtering Between Phases and PE




- CM Cap. Limited by Earth Current Limit – Typ. 3.5mA for PFC Rectifiers (GLBC: 5mA then 50mA !)
- Large CM Inductor Needed – Filter Volume Mainly Defined by CM Inductors
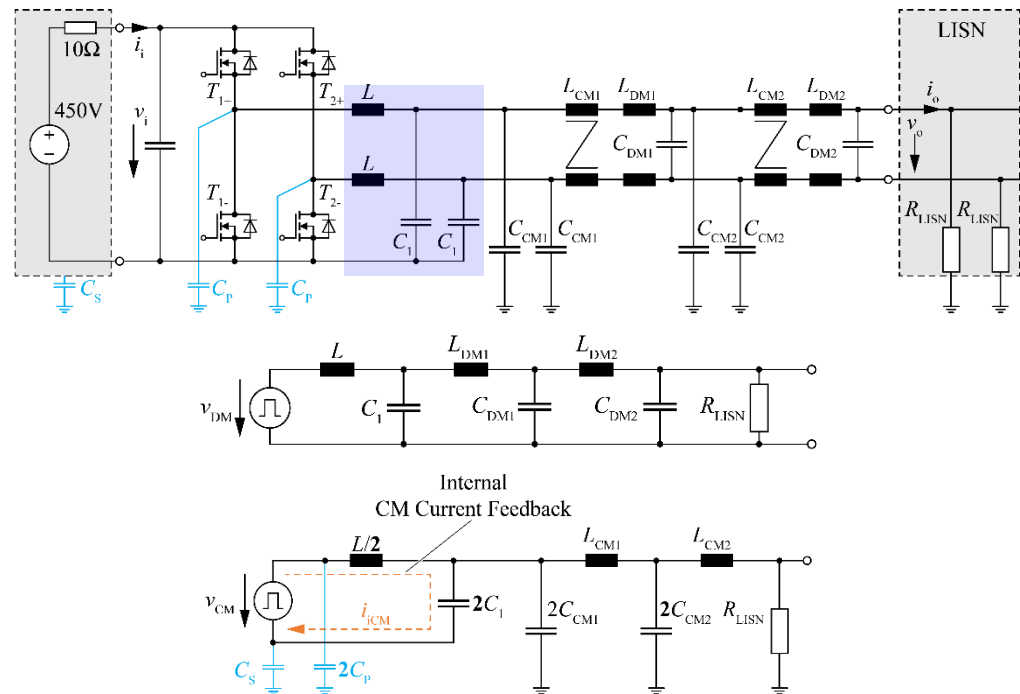
## EMI Filter Topology (2)

- Filter Structure with Internal CM Capacitor Feedback
- Filtering to DC- (and optional to DC+)



 
- No Limitation of CM Capacitor  $C_1$  Due to Earth Current Limit →  $\mu F$  Instead of nF Can be Employed
- Allows Downsizing of CM Inductor and/or Total Filter Volume



## Final Converter Topology

- Interleaving of 2 Bridge Legs per Phase
- Active DC-Side Buck-Type Power Pulsation Buffer
- 2-Stage EMI AC Output Filter

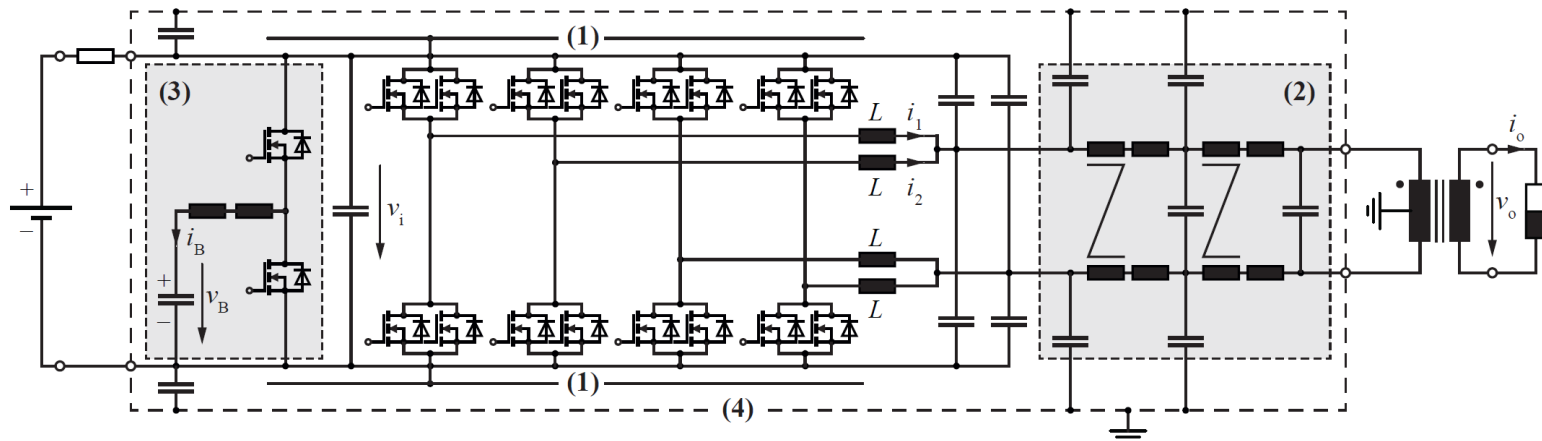- (1) Heat Sink
- (2) EMI Filter
- (3) Power Pulsation Buffer
- (4) Enclosure




- ZVS of All Bridge Legs @ Turn-On/Turn-Off in Whole Operating Range (4D-TCM-Interleaving)
- Heatsinks Connected to DC Bus / Shield to Prevent Cap. Coupling to Grounded Enclosure
 
## *Technologies*





*Power Semiconductors*  
*Cooling*  
*DSP/FPGA*  
*Auxiliary*





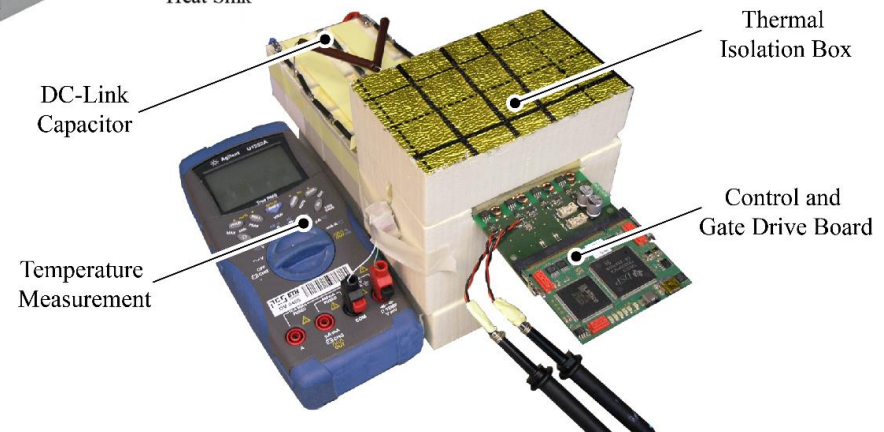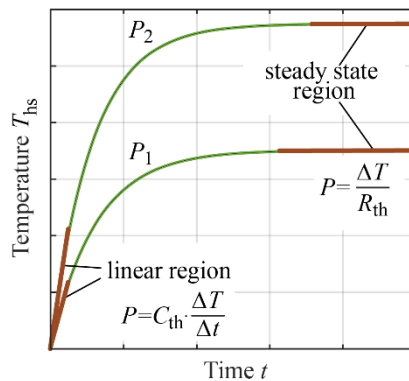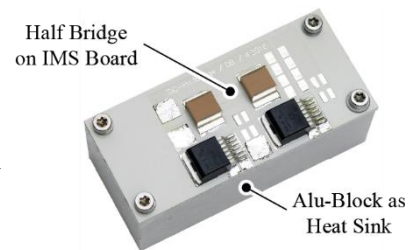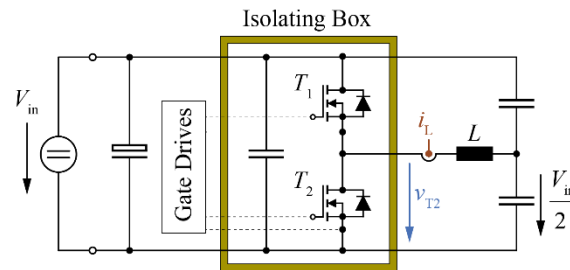
## Evaluation of Power Semiconductors (1)

- Accurate Measurement of ZVS Losses Using Calorimetric Approach
- High Sw. Frequency for Large Ratio of Sw. and Conduction Losses




 - Direct Measurement of the Sum of Sw. and Conduction Losses
- Subtraction of the Conduction Losses Known from Calibration
- Fast Measurement by  $C_{th} \Delta T / \Delta t$  Evaluation



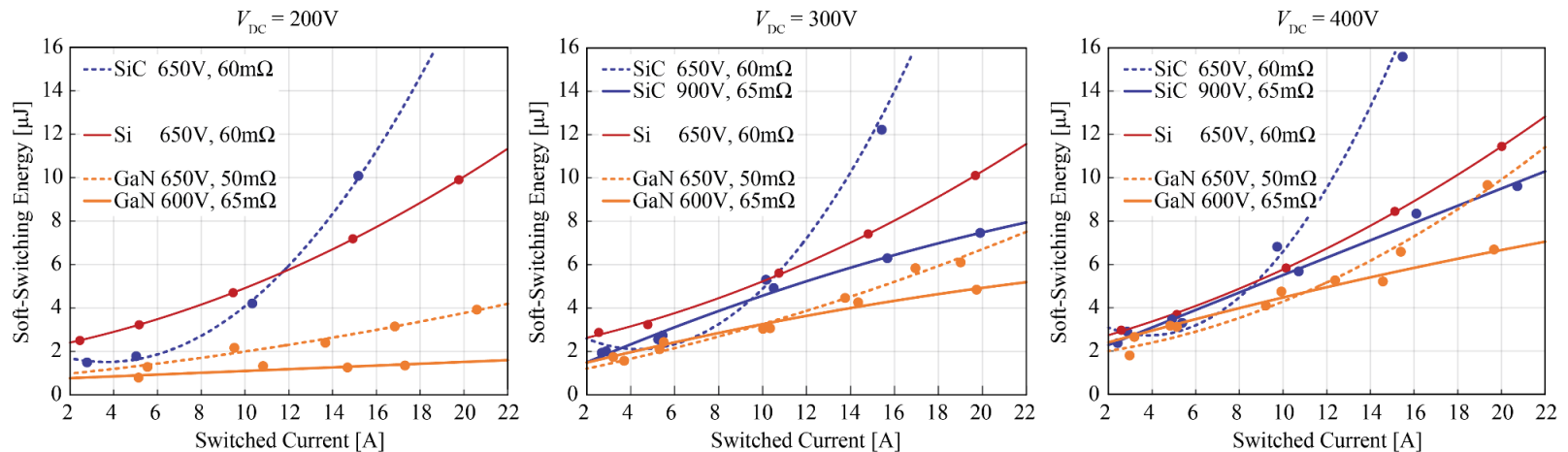
## Evaluation of Power Semiconductors (2)

- Comparison of Soft-Switching Performance of  $\sim 60\text{m}\Omega$ , 600V/650V/900V GaN, SiC, Si MOSFETs
- Measurement of Energy Loss per Switch and Switching Period





 
- GaN MOSFETs Feature Highest Soft-Switching Performance
- Similar Soft-Switching Performance Achieved with Si and SiC
- Almost No Voltage-Dependency of Soft-Switching Losses for Si-MOSFET




## Selected Power Semiconductors

- 600V IFX Normally-Off GaN GIT - ThinPAK8x8
- 2 Parallel Transistors / Switch
- Antiparallel CREE SiC Schottky Diodes

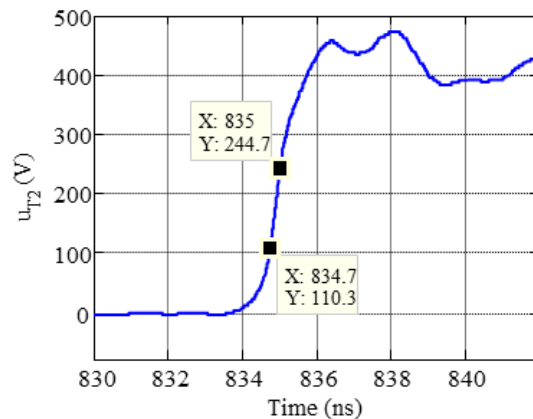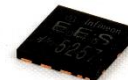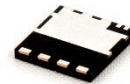- 1.2V typ. Gate Threshold Voltage
- 55 m $\Omega$   $R_{DS(on)}$  @ 25°C, 120m $\Omega$  @ 150°C
- 5 $\Omega$  Internal Gate Resistance




$dv/dt = 500kV/\mu s$

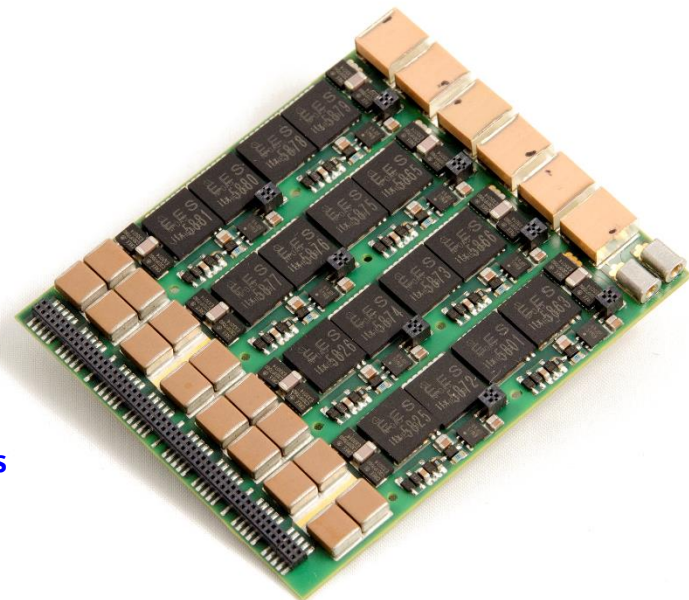

 
- CeraLink Capacitors for DC Voltage Buffering





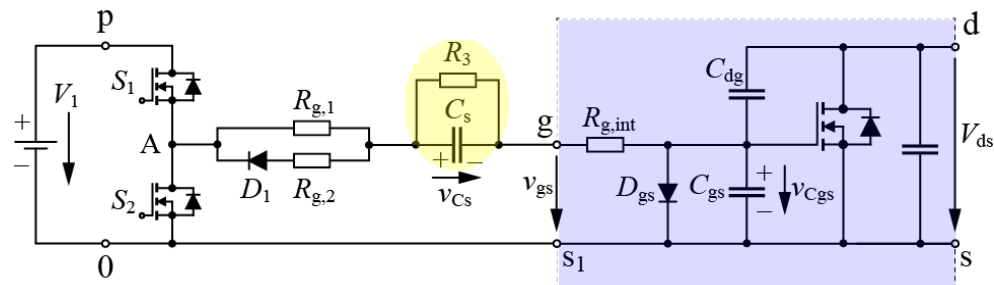
## High $dv/dt$ -Immunity Gate Drive

- Low Threshold-Voltage of GaN GIT Devices → Negative Gate Voltage During Off-State Needed
- Internal Diode Characteristic → Gate Current Limitation During On-State Needed
- State-of-the-Art Gate Drive with Additional RC-Circuit



–  $C_s$  Enables High Gate Current for Fast Turn-On

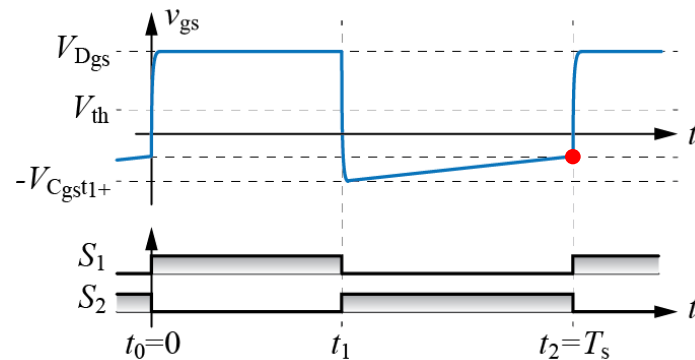–  $R_3$  Discharges  $C_s$  During Off-State




- Duty Cycle and Frequency Dependent Gate Voltage
- Risk of Parasitic Turn-on Due to Switching of Complementary Switch



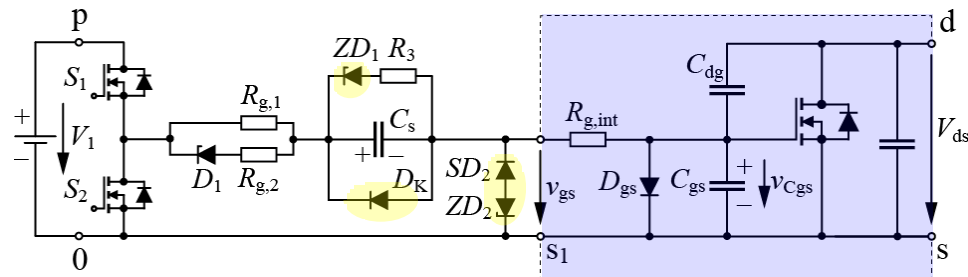
## High dv/dt-Immunity Gate Drive

- Improved Gate Drive Circuit with RC-Circuit and Added Clamping Diodes
- High Current for Fast Turn-On as Conventional Approach



- Diode  $ZD_2$  Quickly Discharges  $C_s$  to  $V_{ZD2}$  @ Turn-Off

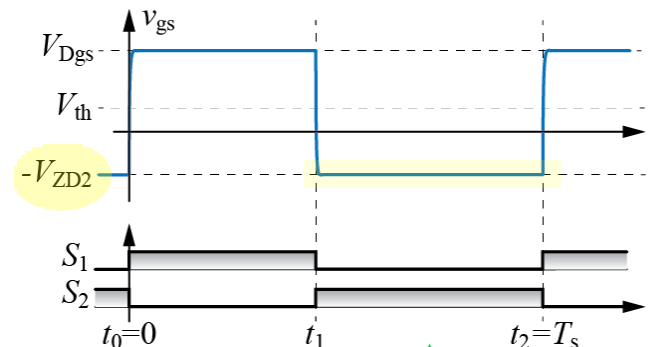- Diode  $ZD_1$  Prevents  $C_s$  from Complete Discharge During Off-State





- **Fixed Neg. Turn-Off Gate Voltage Independent of Duty Cycle and @ Start-Up**


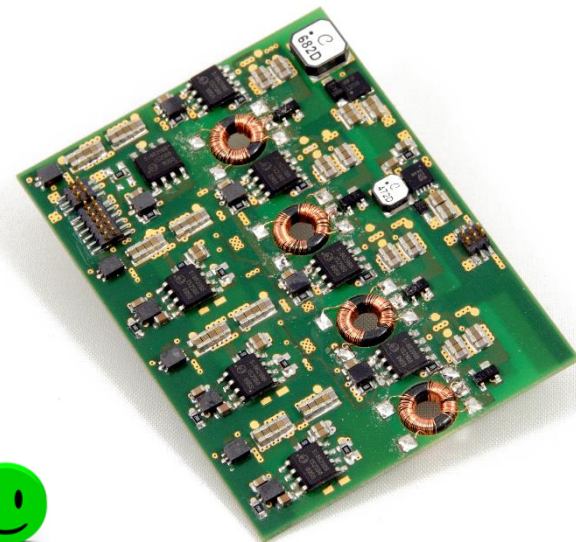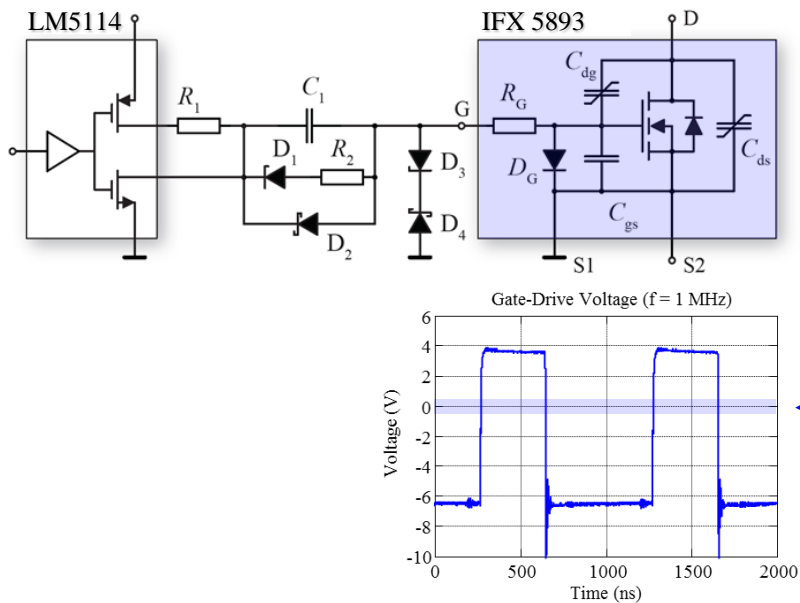
# Final Advanced Gate Drive

- **Fixed Negative Turn-off Gate Voltage** - Independent of Sw. Frequency and Duty Cycle
- **Extreme dv/dt Immunity ( $500\text{ kV}/\mu\text{s}$ )** - Due to CM Choke at Signal Isolator Input



- **Total Prop. Delay  $< 30\text{ ns}$**  incl. Signal Isolator, Gate Drive, and Switch Turn-On Delay


# High Frequency Inductors (1)

- Multi-Airgap Inductor with Multi-Layer Foil Winding Arrangement Minim. Prox. Effect
- Very High Filling Factor / Low High Frequency Losses
- Magnetically Shielded Construction Minimizing EMI
- Intellectual Property of F. Zajc / Fraza

- $L = 10.5 \mu\text{H}$
- 2 x 8 Turns
- 24 x  $80 \mu\text{m}$  Airgaps
- Core Material DMR 51 / Hengdian
- 0.61mm Thick Stacked Plates
- 20  $\mu\text{m}$  Copper Foil / 4 in Parallel
- 7  $\mu\text{m}$  Kapton Layer Isolation
- 20m $\Omega$  Winding Resistance /  $Q \approx 600$
- Terminals in No-Leakage Flux Area




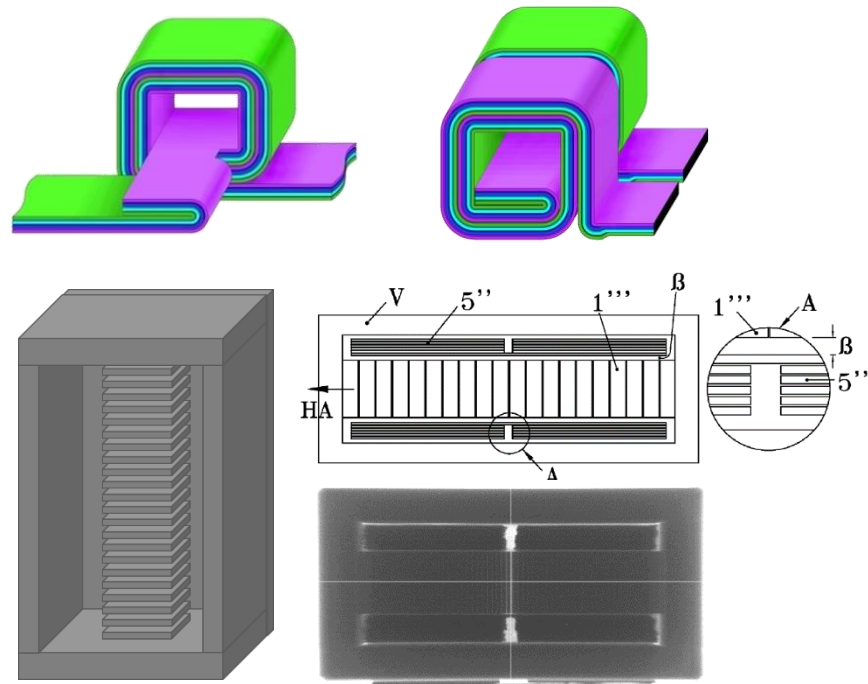■ Dimensions - 14.5 x 14.5 x 22mm<sup>3</sup>



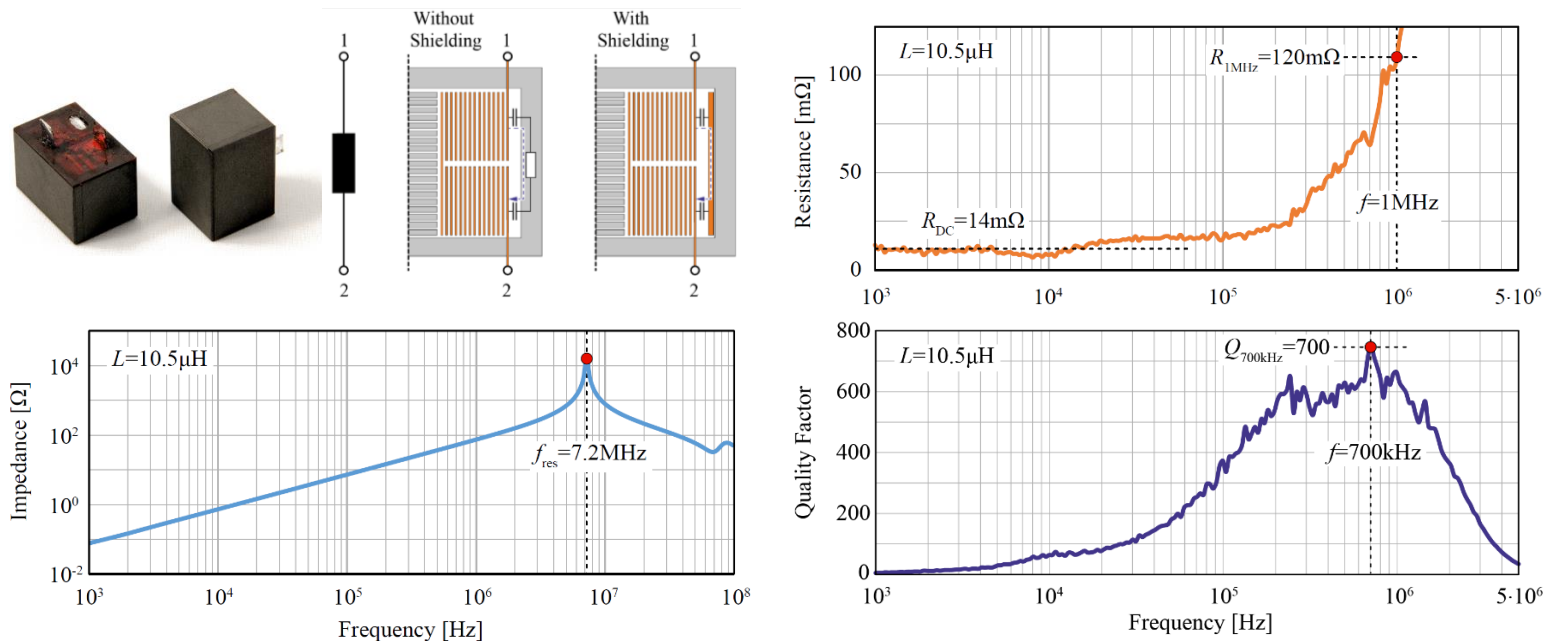
## High Frequency Inductors (2)

- High Resonance Frequency → Inductive Behavior up to High Frequencies
- Extremely Low AC-Resistance → Low Conduction Losses up to High Frequencies
- High Quality Factor



 - Shielding Eliminates HF Current through the Ferrite → Avoids High Core Losses
- Shielding Increases the Parasitic Capacitance




## High Frequency Inductors (3)



\* Knowles (1975!)



- Cutting of Ferrite Introduces Mech. Stress
- Significant Increase of the Loss Factor
- Reduction by Polishing / Etching (5  $\mu\text{m}$ )

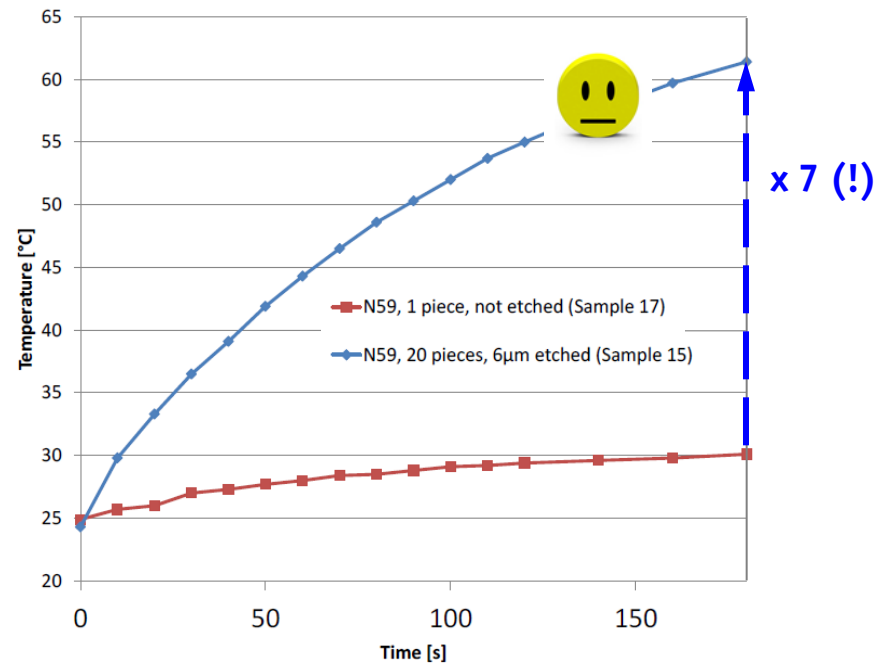■ Comparison of Temp. Increase of a Bulk and a Sliced Sample @ 70mT / 800kHz


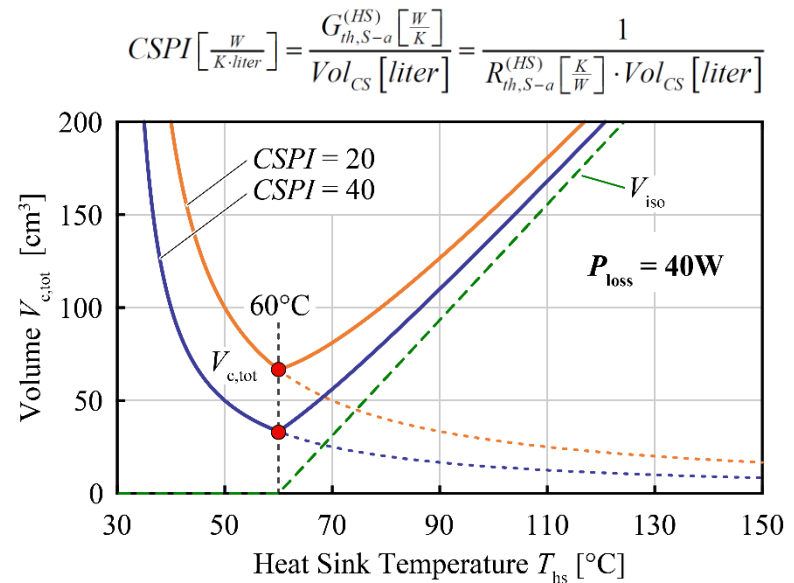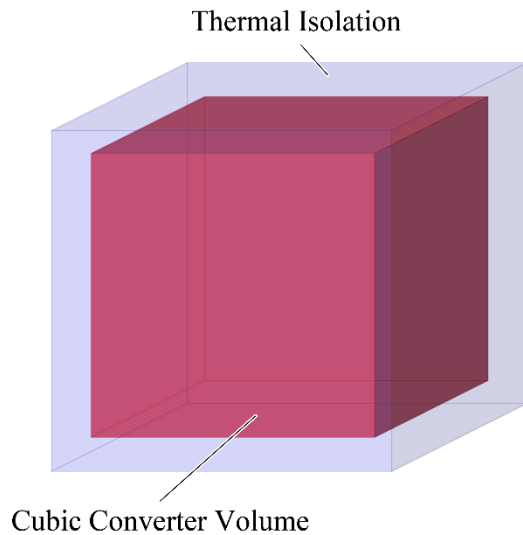
# Thermal Management

- 30°C max. Ambient Temperature
- 60°C max. Allowed Surface and Air Outlet Temperature
- Evaluation of Optimum Heatsink Temperature for Thermal Isolation of Converter




- Minimum Volume Achieved w/o Thermal Isolation with Heatsink @ max. Allowed Surface Temp.



## Thermal Management

- **Overall Cooling Performance Defined by Selected Fan Type and Heatsink**


- **Radial Blower**

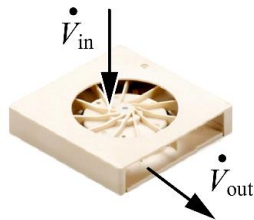



- Axial Fan

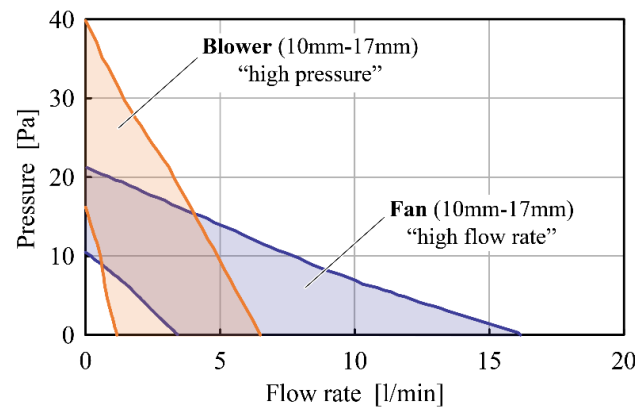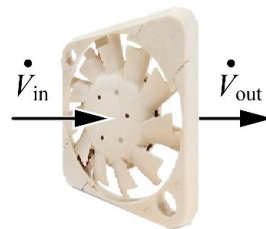

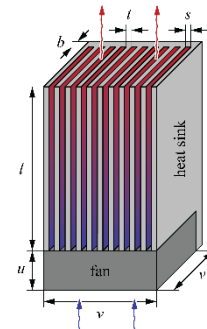- Square Cross Section of Heatsink for Using a Fan




- Flat and Wide Heatsink for Blower

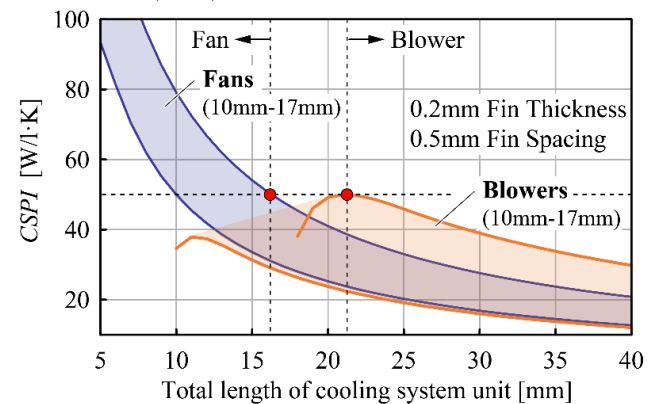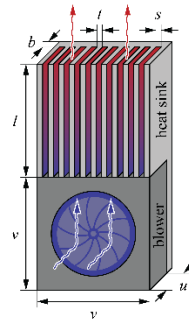

 - Optimal Fan and Heat Sink Configuration Defined by Total Cooling System Length
- Cooling Concept with Blower Selected → Higher *CSPI* for Larger Mounting Surface







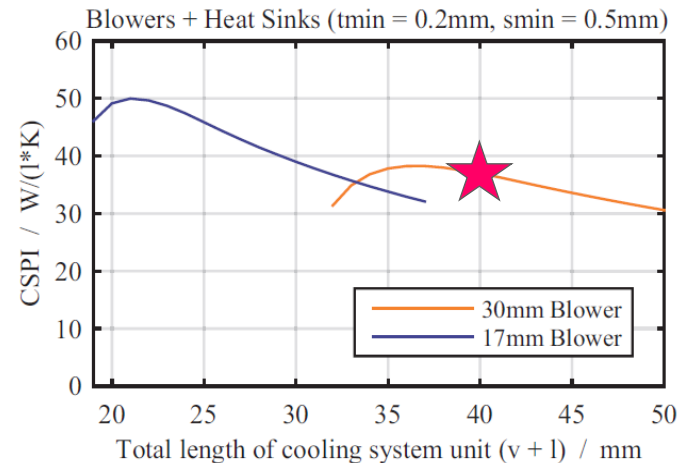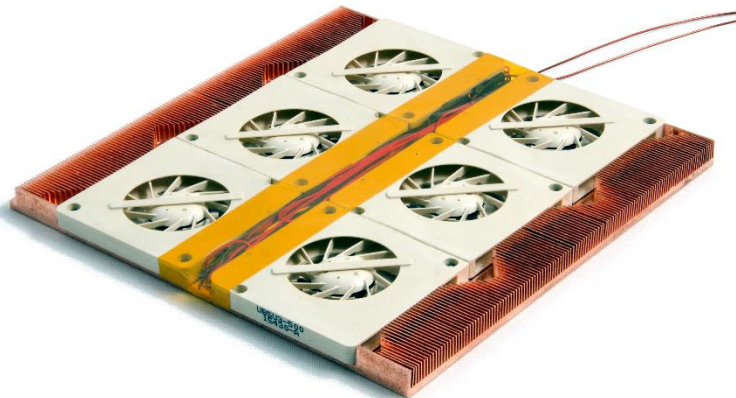
## Final Thermal Management Concept (1)

- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters

- 200um Fin Thickness
- 500um Fin Spacing
- 3mm Fin Height
- 10mm Fin Length
- $CSPI = 37 \text{ W}/(\text{dm}^3 \cdot \text{K})$
- 1.5mm Baseplate




 - $CSPI_{eff} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$  Considering Heat Distribution Elements
- Two-Side Cooling  $\rightarrow$  Heatsink Temperature =  $52^\circ\text{C}$  @ 80W (8W by Natural Convection)


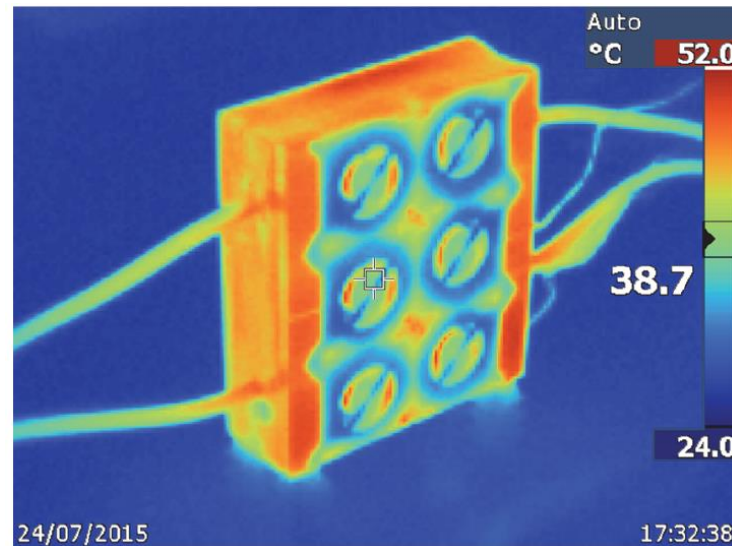
## Final Thermal Management Concept (2)

- $CSPI = 37 \text{ W}/(\text{dm}^3 \cdot \text{K})$
- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters
- $CSPI_{\text{eff}} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$  incl. Heat Cond. Layers



- $CSPI_{\text{eff}} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$  Considering Heat Distribution Elements
- Two-Side Cooling → Heatsink Temperature =  $52^\circ\text{C}$  @ 80W (8W by Natural Convection)





## $i=0$ Detection

- Analyzed Methods
  - Shunt Current Measurement
  - Measurement of the  $R_{ds,on}$
  - Two Antiparallel Diodes
  - Giant Magneto-Resistive Sensor
  - Hall Element

### Various Drawbacks

Losses, No Galvanic Isolation, Low Signal-to-Noise Ratio (SNR), Size, Bandwidth, Realization Effort


- Saturable Inductor

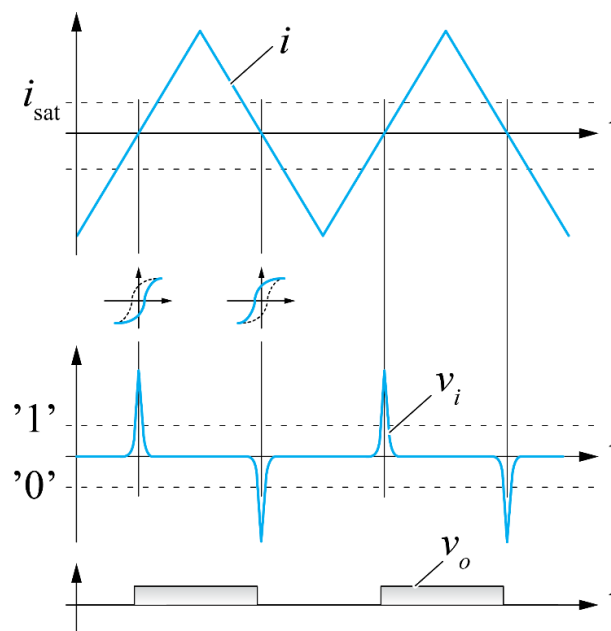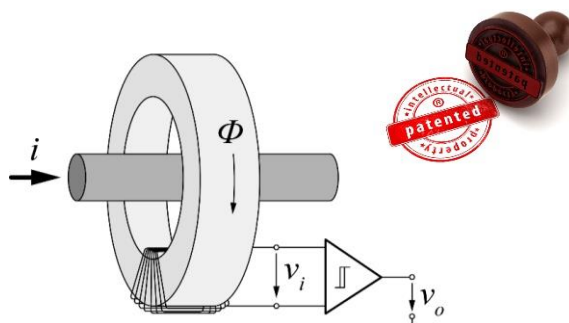


- Galvanic Isolation, High SNR, Small Size, High Bandwidth, Simple Design
- Min. Core Volume/Cross Section for Min. Core Losses
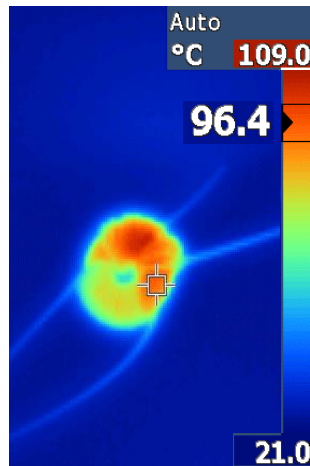
## $i=0$ Detection


- Saturable Inductor
  - Toroidal Core R4 x 2.4 x 1.6, EPCOS (4mm Diameter)
  - Core Material N30, EPCOS



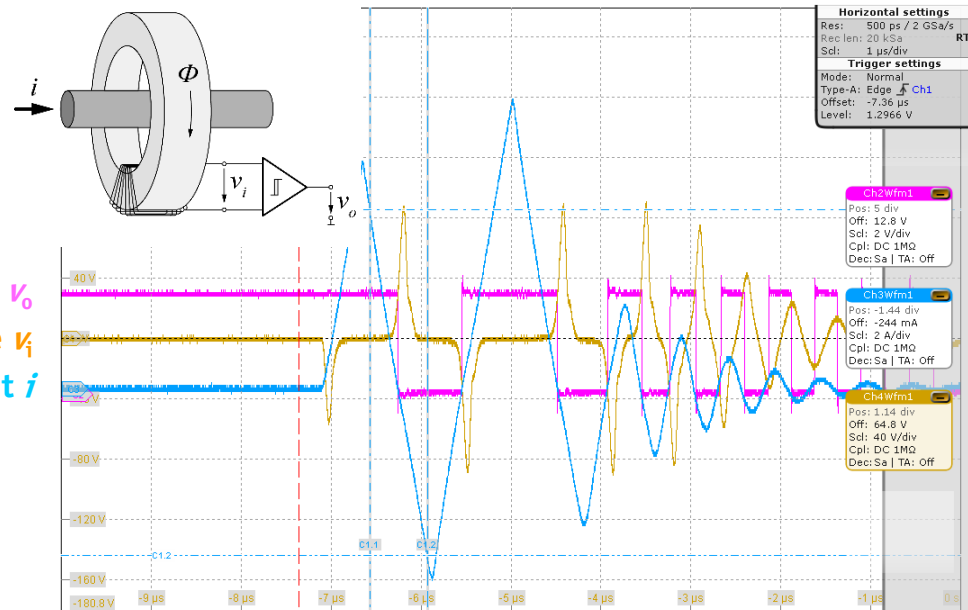Digital Signal  $v_o$   
Induced Voltage  $v_i$   
Current  $i$




 
- Operation Tested up to 2.5MHz Switching Frequency



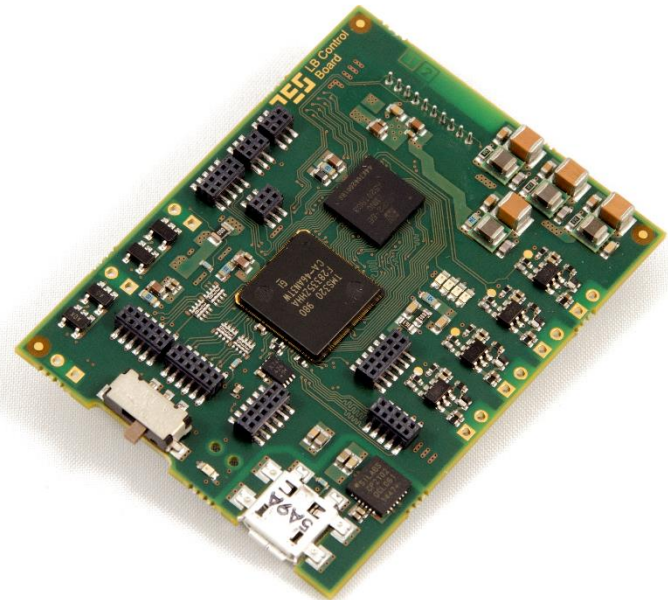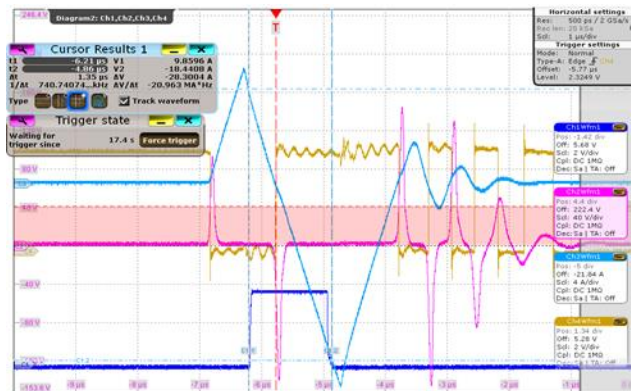
## Control Board & $i=0$ Detection

- Fully Digital Control - Overall Control Sampling Frequency of 25kHz
- TI DSC TMS320F28335 / 150MHz / 179-pin BGA / 12mm x 12mm
- Lattice FPGA LFXP2-5E / 200MHz / 86-pin BGA / 8mm x 8mm

- TCM Current / Induced Voltage / Comparator Output





 - $i=0$  Detection of TCM Currents Using R4/N30 Saturable Inductors
- Galv. Isolated / Operates up to 2.5MHz Switching Frequency / <10ns Delay



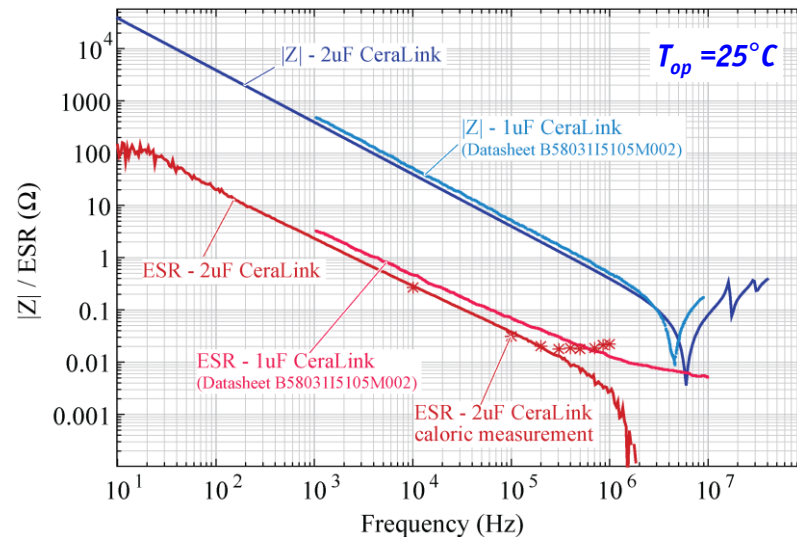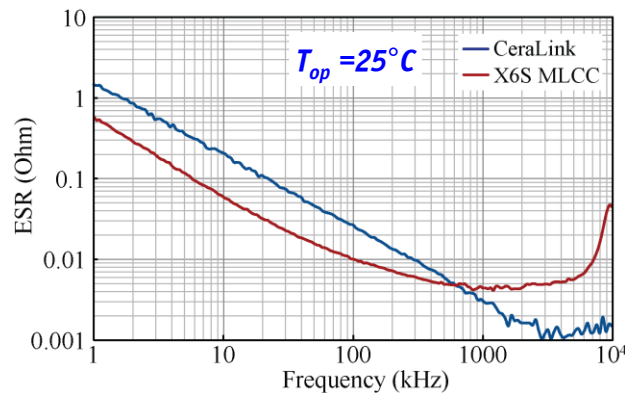
## Active Power Pulsation Buffer Capacitor (1)

- **Electrolytic Capacitors** – Limited by Lifetime-Relevant Current Limit
- **2.2 $\mu$ F, 450 V Class II X6S MLCC** – Highest Energy Density but Cap. Decreases with DC Bias
- **Novel 1  $\mu$ F / 2  $\mu$ F, 650 V CeraLink™ Cap. (PLZT Ceramic) Features High Cap. @ High DC Bias**
- **Allows 125°C Operating Temp. & Shows Very Low ESR @ High Frequencies**






 - **CeraLink Resonance Frequency at Several MHz**
- **Small-Signal ESR of CeraLink in MHz Frequ. Range Sign. Lower Comp. to X6S MLCC**



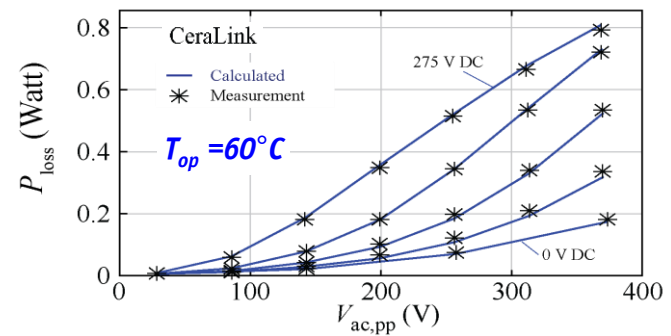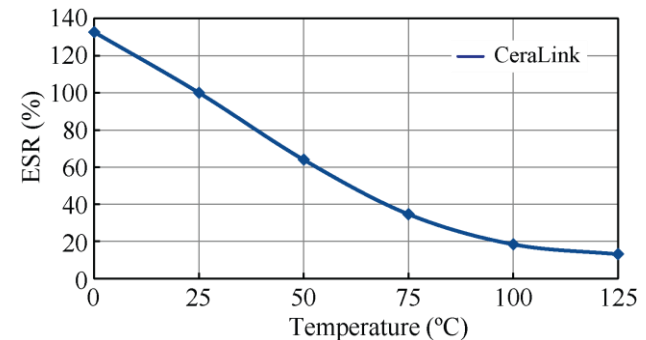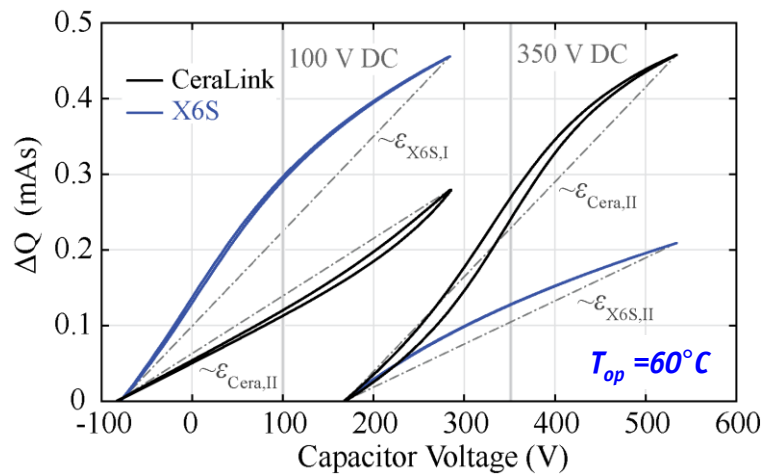
## Active Power Pulsation Buffer Capacitor (2)

- CeraLink**
  - Large-Signal Excitation with 2xLine-Frequ. Reveals Large Hysteresis
  - Significantly Higher Losses @ 2xLine-Frequ. Comp. to X6S MLCC
  - ESR Drops Significantly @ Higher Temperatures
  - 36 $\mu$ F (27 $\mu$ F) Blocks of Prepackaged Single Chips
  - Reliable Mech. Construction
- X6S MMLC**
  - Only Available as Single Chips
  - Complicated Packaging







 
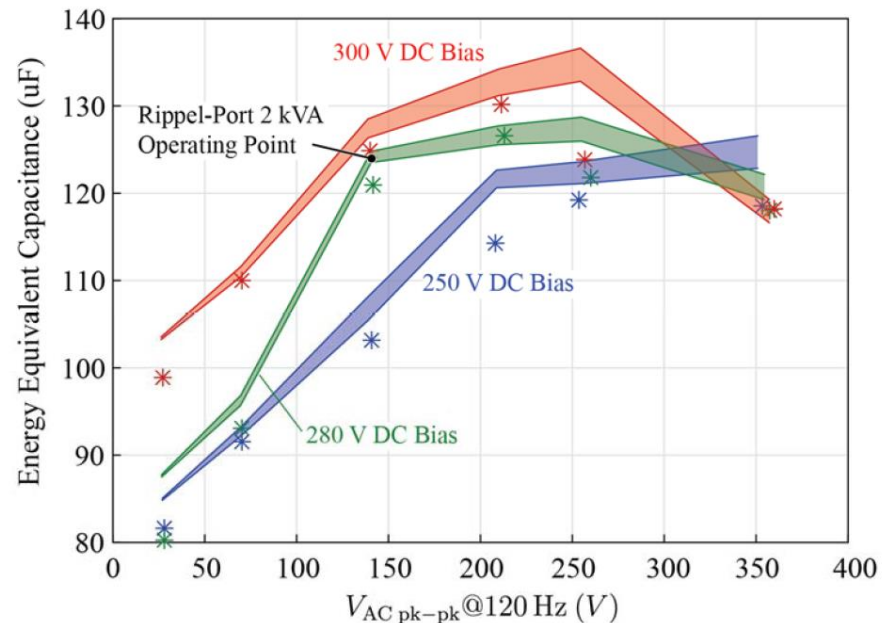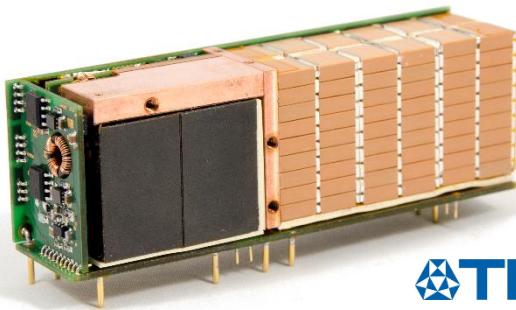
## Final Active Power Pulsation Buffer

- High Energy Density 2<sup>nd</sup> Gen. 400VDC CeraLink Capacitors Utilized as Energy Storage
- Highly Non-Linear Behavior → Optimal DC Bias Voltage of 280VDC
- Losses of 6W @ 2kVA Output Power

- 108 x 1.2 $\mu$ F / 400 V
- 23.7cm<sup>3</sup> Capacitor Volume




- Effective Large Signal Capacitance of  $C \approx 160\mu F$






# Active Power Pulsation Buffer Control (1)

- New Cascaded Control Structure

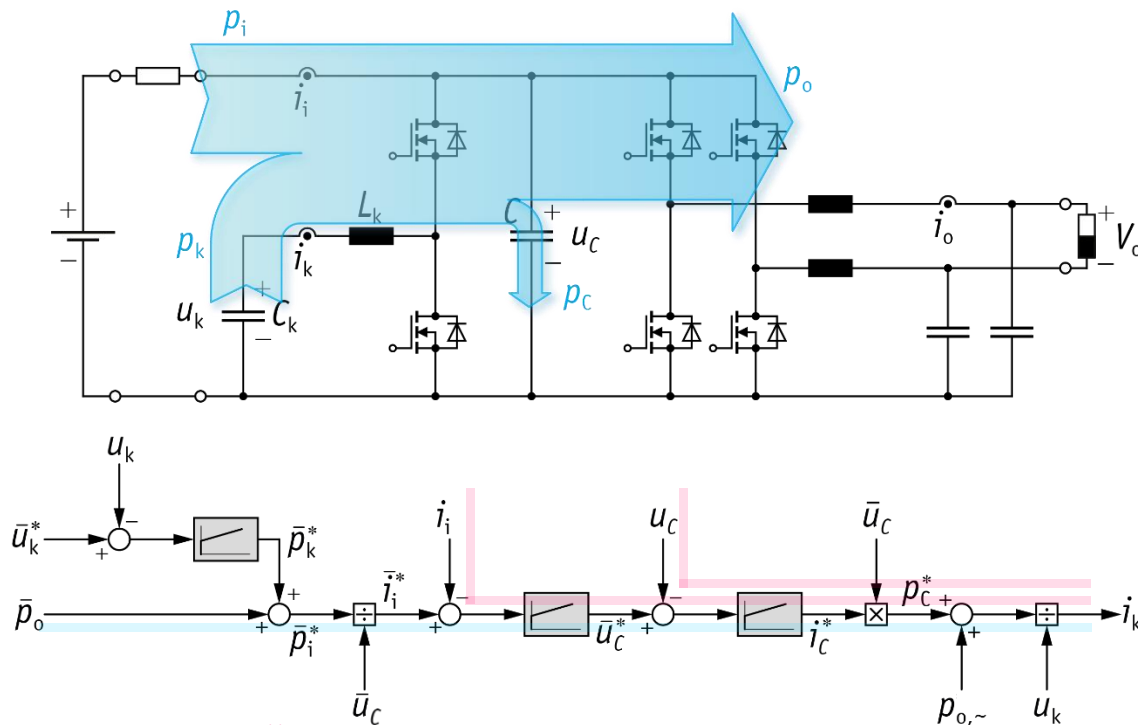

 
- P-Type Resonant Controller
- Feedforward of Output Power Fluctuation
- Underlying Input Current ( $i_i$ ) / DC Link Voltage ( $u_c$ ) Control





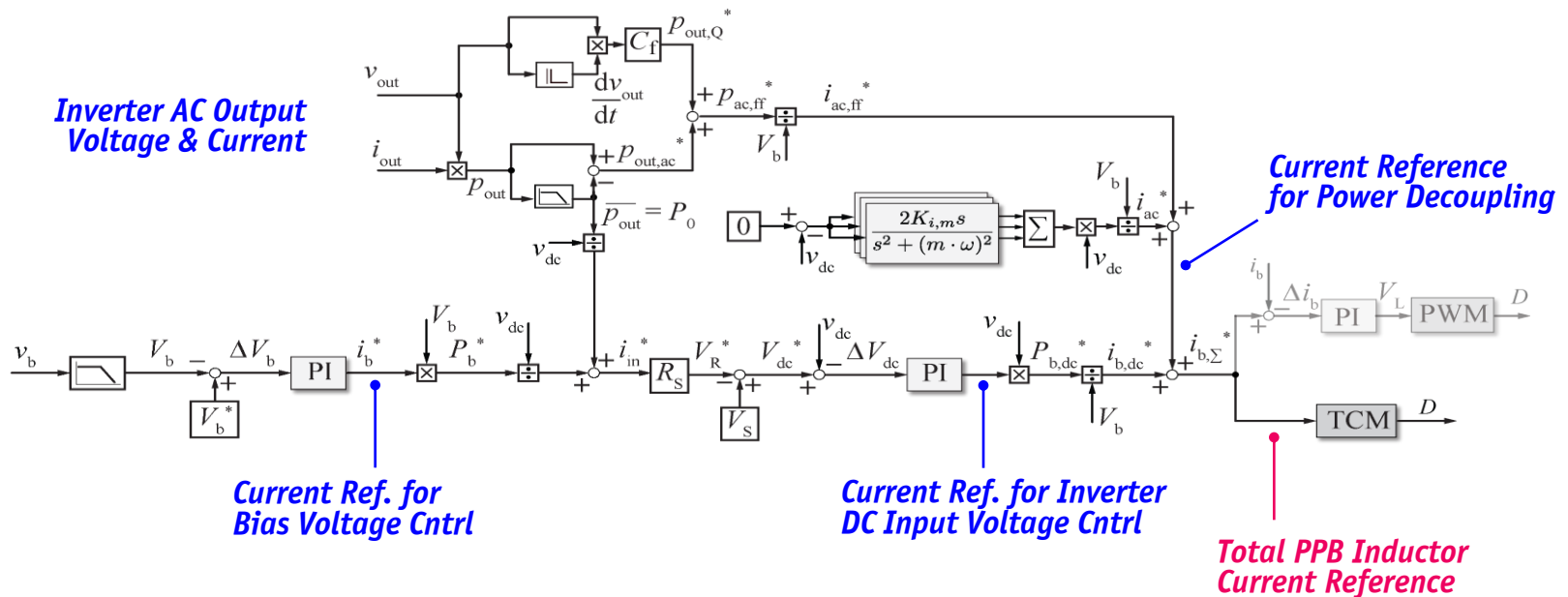
## Active Power Pulsation Buffer Control (2)

- Multiple Controller Outputs Combined in a Single Current Reference







 - Regulation of Mean Buffer Voltage (Bias Voltage)
- Tight Control of Inverter DC Link Voltage also During Transients
- Active Power Decoupling – Rejection of 2xLine-Frequ. Ripple in Inverter DC Input Voltage



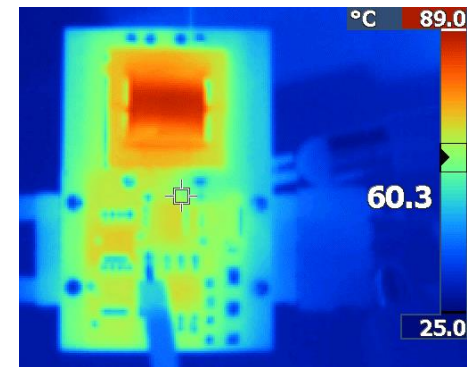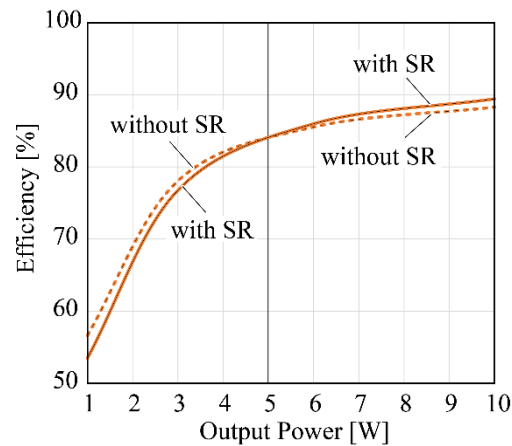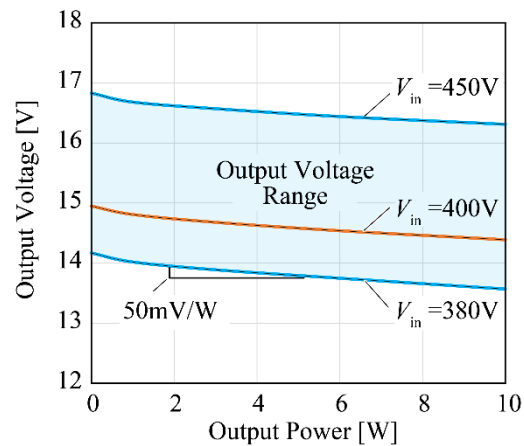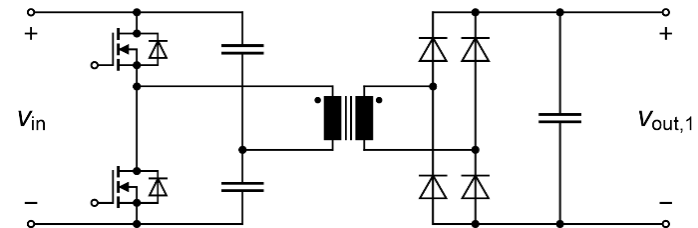
## Auxiliary Supply

- Constant 50% Duty Cycle Half Bridge w. Diode Rect. or Synchr. Rectification (SR)
- ZVS → Compact / Efficient / Low EMI





@  $V_{in} = 380V$ ,  $P_{out} = 10W$

 - Only Marginal Eff. Gain with Synchr. Rectification for Output Power Levels > 5W



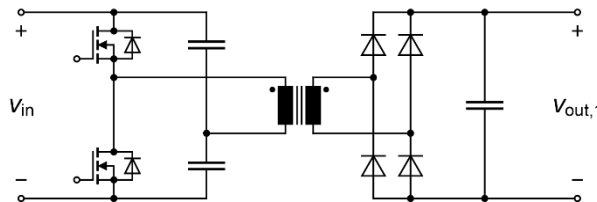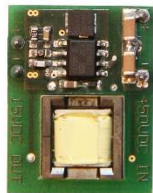
## Auxiliary Supply & Measurement Circuits


- Constant 50% Duty Cycle Half Bridge with Synchr. Rectification
- ZVS → Compact / Efficient / Low EMI ( $f_s=465$  kHz)
- 10W Max. Output Power
- 390V...450V Input Operating Range
- 13.8V...16.8V DC Output in Full Inp. Voltage / Output Power Range
- 90% Efficiency @  $P_{max}$



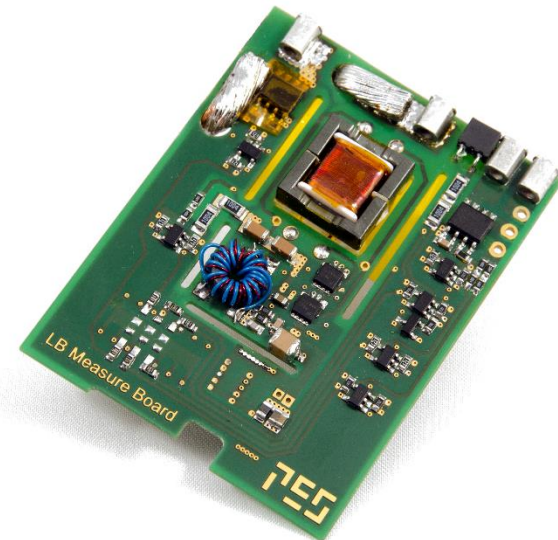■ 19mm x 24mm x 4.5mm (2cm<sup>3</sup> Volume )




*3D-CAD Construction* →

 

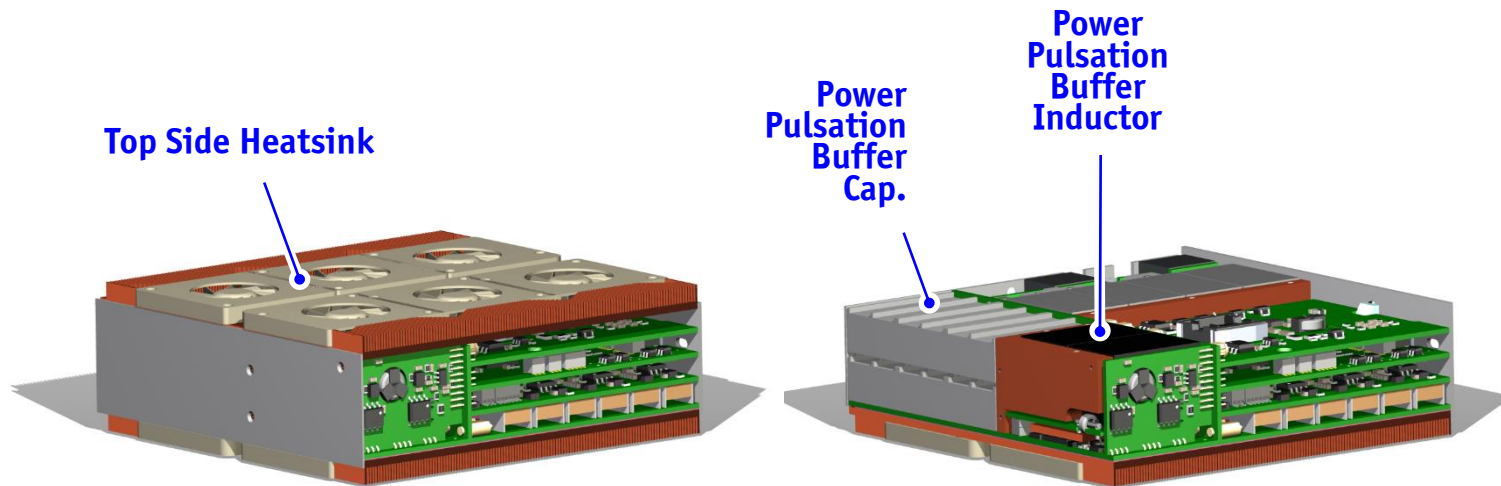
## Mechanical Construction (1)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




 ■  $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$  ( $14.8\text{in}^3$ )  $\rightarrow 8.2\text{ kW/dm}^3$



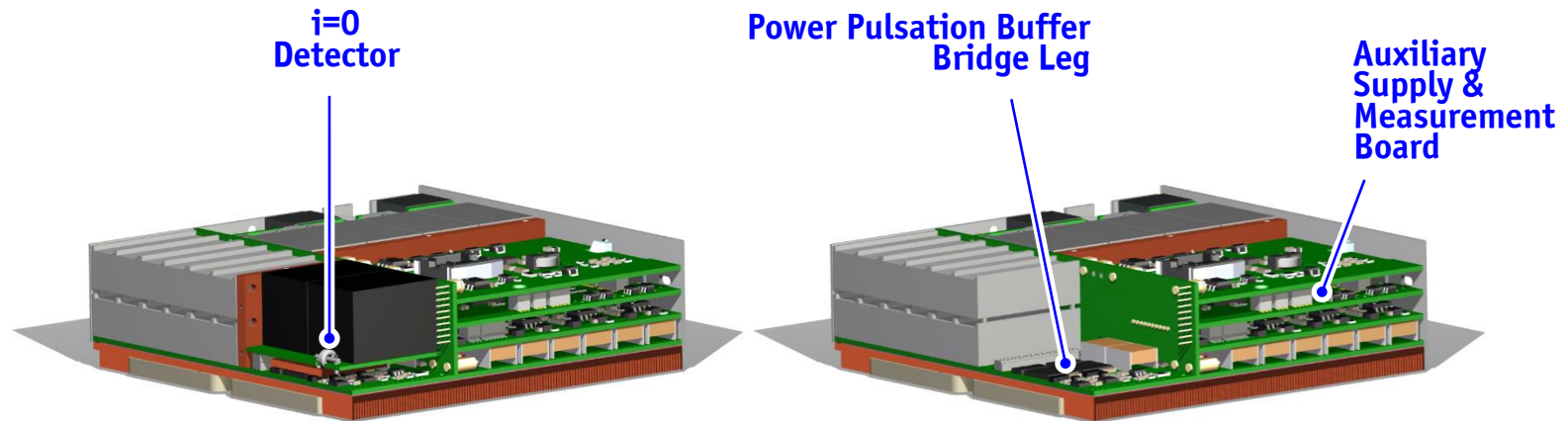
## Mechanical Construction (2)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$




 ■  $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$  ( $14.8\text{in}^3$ )  $\rightarrow 8.2\text{ kW/dm}^3$



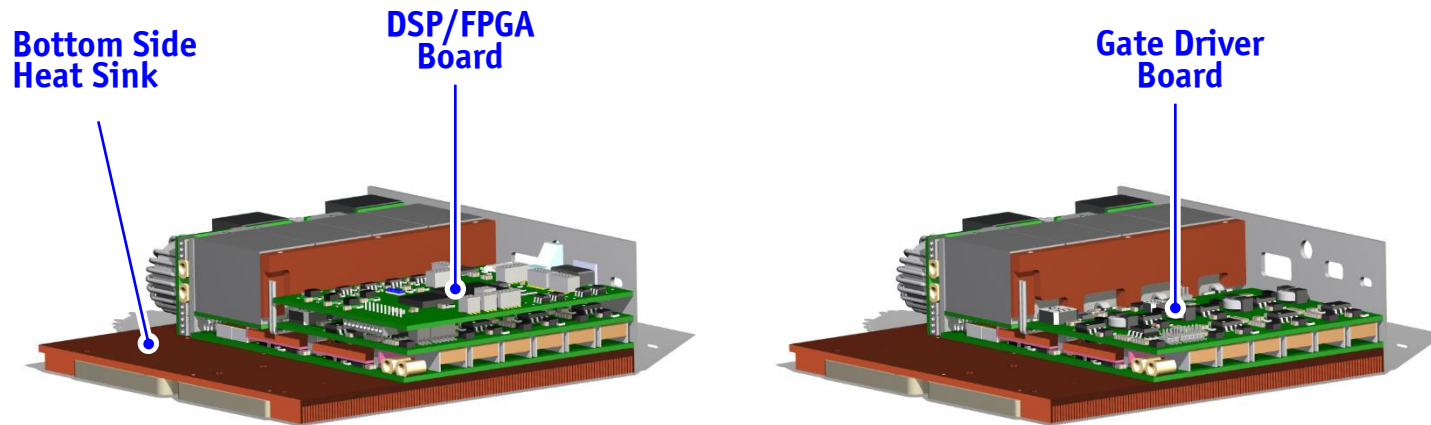
## Mechanical Construction (3)

- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$



 
■  $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$  ( $14.8\text{in}^3$ )  $\rightarrow 8.2\text{ kW/dm}^3$





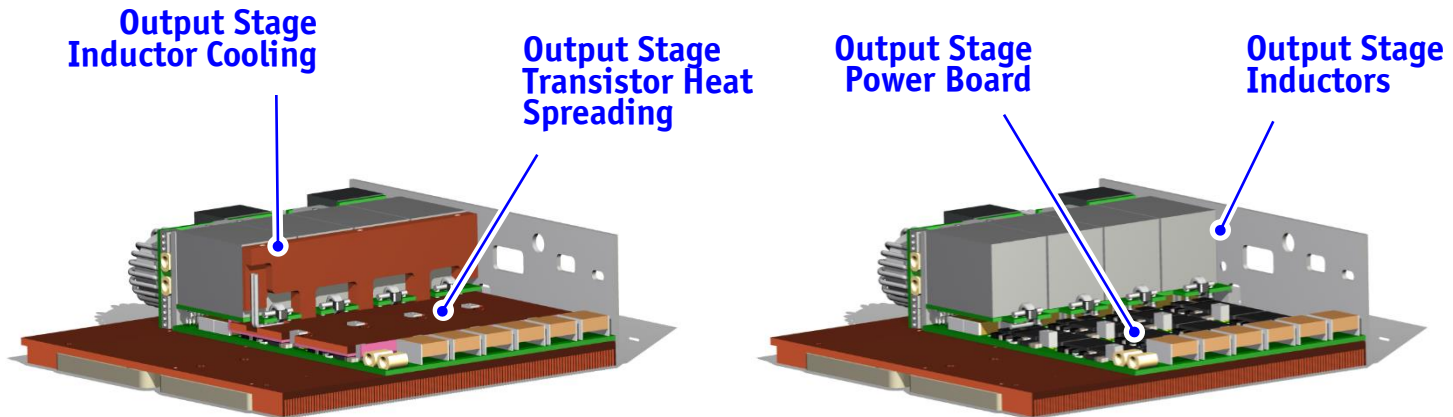
## Mechanical Construction (4)


- Built to the Power Density Limit @  $\eta = 95\%$  /  $T_c < 60^\circ\text{C}$



 ■  $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$  ( $14.8\text{in}^3$ )  $\rightarrow 8.2\text{ kW/dm}^3$




## Mechanical Construction (5)

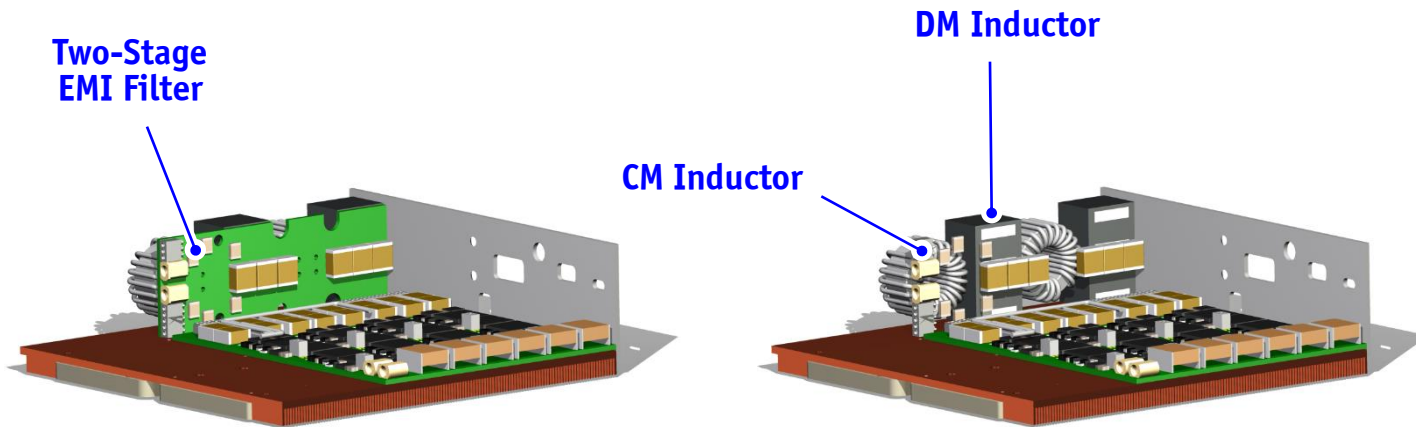

■  $88.7\text{mm} \times 88.4\text{mm} \times 31\text{mm} = 243\text{cm}^3$  ( $14.8\text{in}^3$ )  $\rightarrow 8.2\text{ kW/dm}^3$
 
## *Experimental Results*

*Hardware*  
*Output Voltage/Input Current Quality*  
*Thermal Behavior*  
*Efficiency*  
*EMI* →



## Little Box 1.0 - Prototype I


- System Employing Electrolytic Capacitors as 1- $\Phi$  Power Pulsation Buffer


273 cm<sup>3</sup>  
7.3 kW/dm<sup>3</sup>  
97,5% Efficiency @ 2kW  
 $T_c = 58^\circ\text{C}$  @ 2kW

$\Delta u_{DC} = 2.85\%$   
 $\Delta i_{DC} = 15.4\%$   
 $THD+N_U = 2.6\%$   
 $THD+N_I = 1.9\%$

97mm x 90.8 mm x 31mm ( 16.6in<sup>3</sup> )


- Compliant to All Specifications

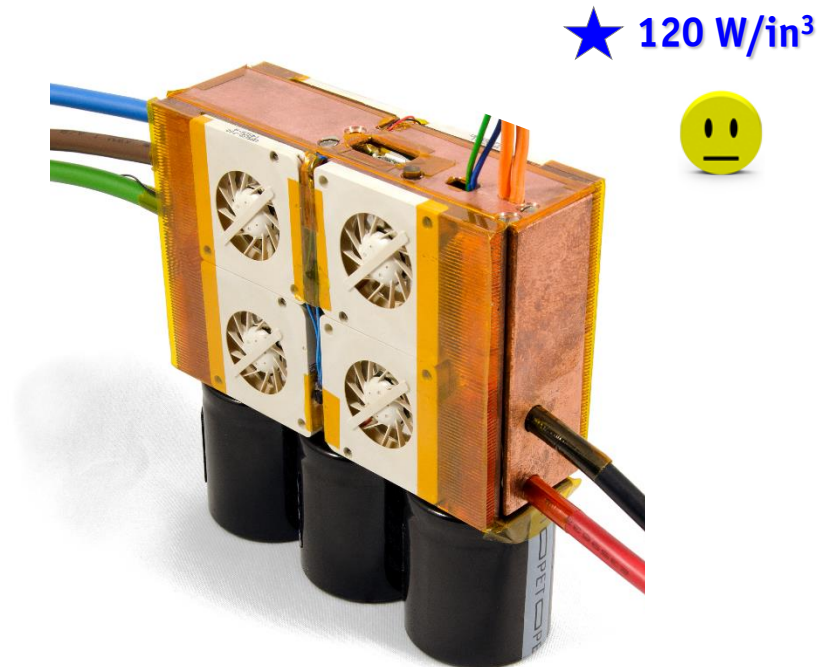

 
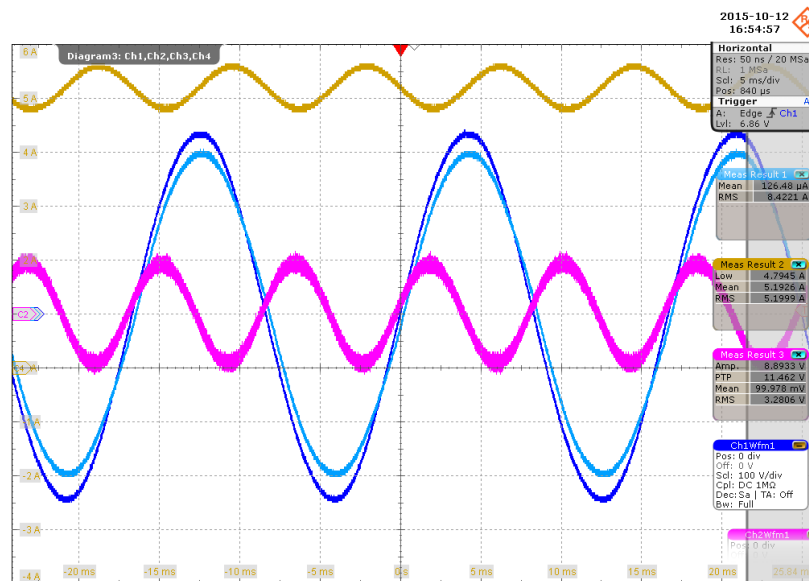
## Little Box 1.0-I Measurement Results (1)

- System Employing Electrolytic Capacitors as 1- $\Phi$  Power Pulsation Buffer





Ohmic Load / 2kW

DC Input Current  
DC Voltage Ripple  
Output Voltage  
Output Current


- Compliant to All Specifications
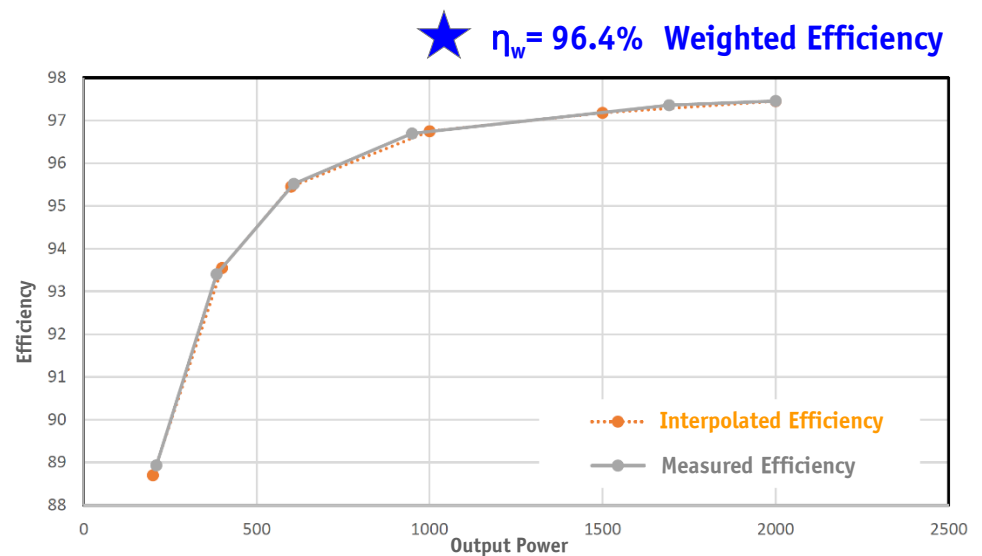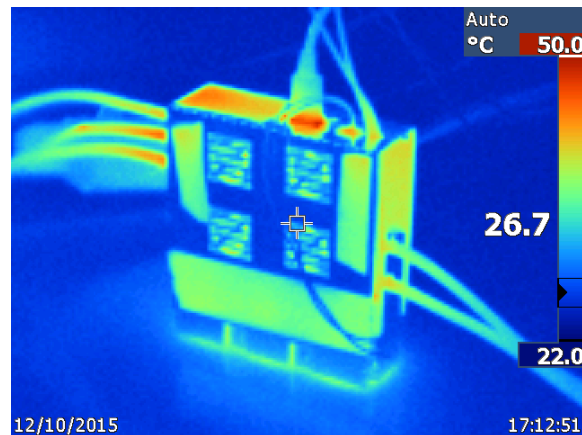
## Little Box 1.0-I Measurement Results (2)

- System Employing Electrolytic Capacitors as 1- $\Phi$  Power Pulsation Buffer





 - Heating of System Lower than Specified Limit ( $T_{C,max} = 60^\circ\text{C}$  @  $T_{amb} = 30^\circ\text{C}$ )



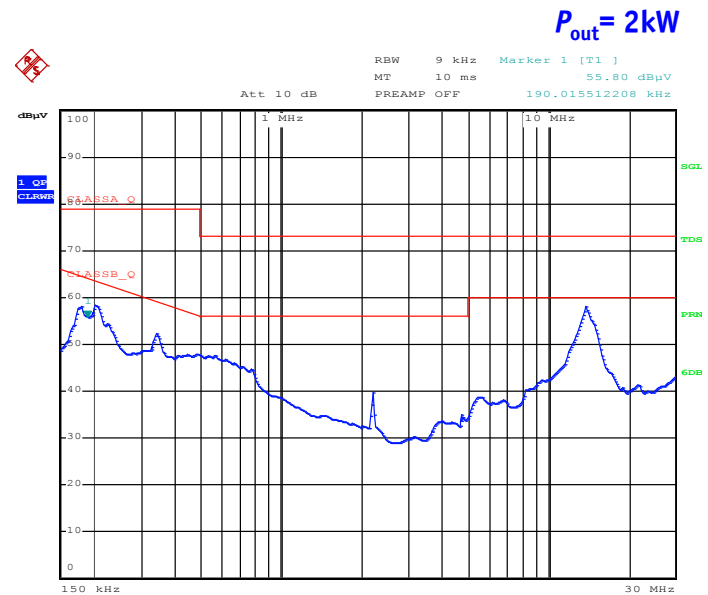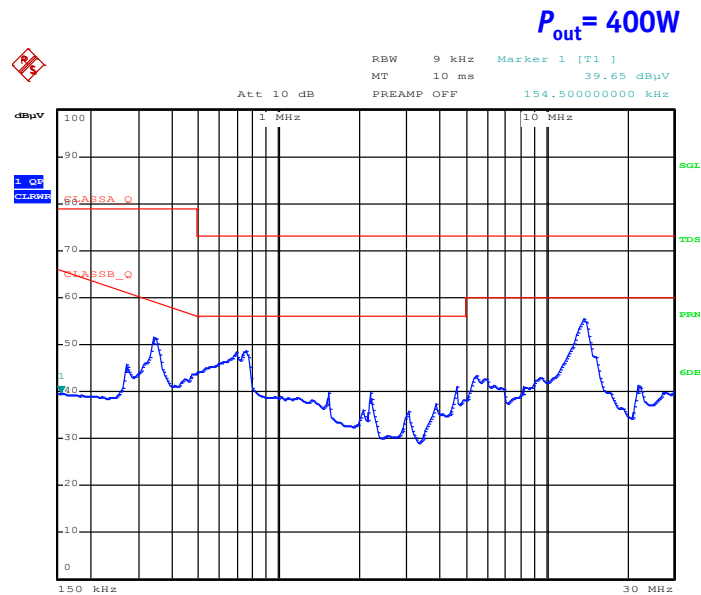
## Little Box 1.0-I Measurement Results (3)

- System Employing Electrolytic Capacitors as 1- $\Phi$  Power Pulsation Buffer



- Compliant to All Specifications

 

## Little Box 1.0 - Prototype II (Final)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer

- 8.2 kW/dm<sup>3</sup>
- 8.9cm x 8.8cm x 3.1cm
- 96,3% Efficiency @ 2kW
- $T_c=58^\circ\text{C}$  @ 2kW


- $\Delta u_{DC} = 1.1\%$
- $\Delta i_{DC} = 2.8\%$
- $THD+N_U = 2.6\%$
- $THD+N_I = 1.9\%$

- Compliant to All *Original* Specifications (!)


- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



★ 135 W/in<sup>3</sup>

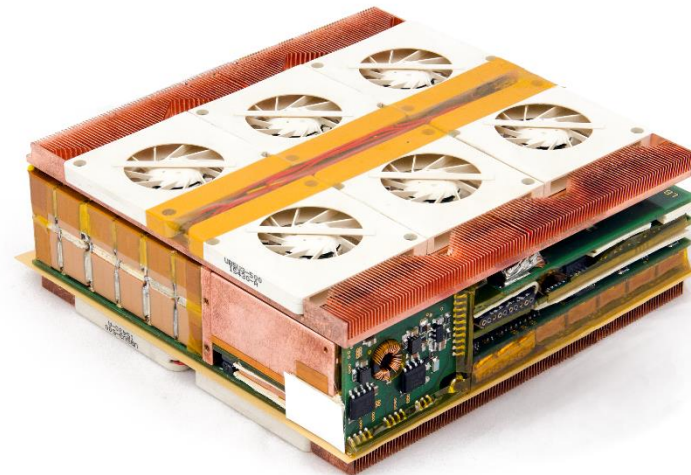



 

## Little Box 1.0 - Prototype II (Final)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer

- 8.2 kW/dm<sup>3</sup>
- 8.9cm x 8.8cm x 3.1cm
- 96,3% Efficiency @ 2kW
- $T_c=58^\circ\text{C}$  @ 2kW


- $\Delta u_{DC} = 1.1\%$
- $\Delta i_{DC} = 2.8\%$
- $THD+N_U = 2.6\%$
- $THD+N_I = 1.9\%$


- Compliant to All *Original* Specifications (!)

- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



★ 135 W/in<sup>3</sup>

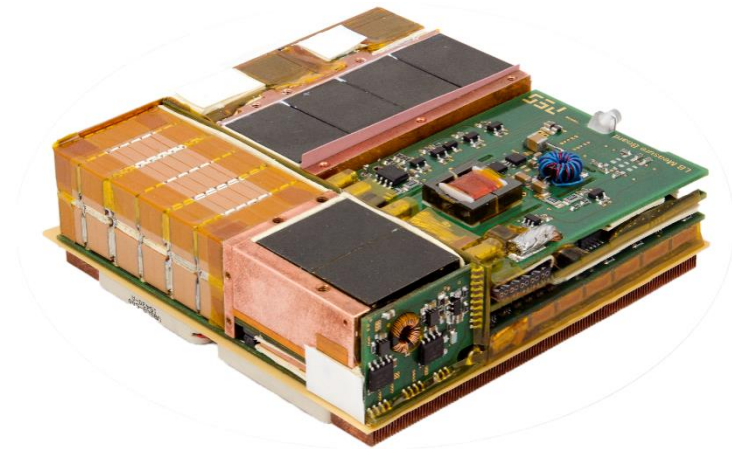


 

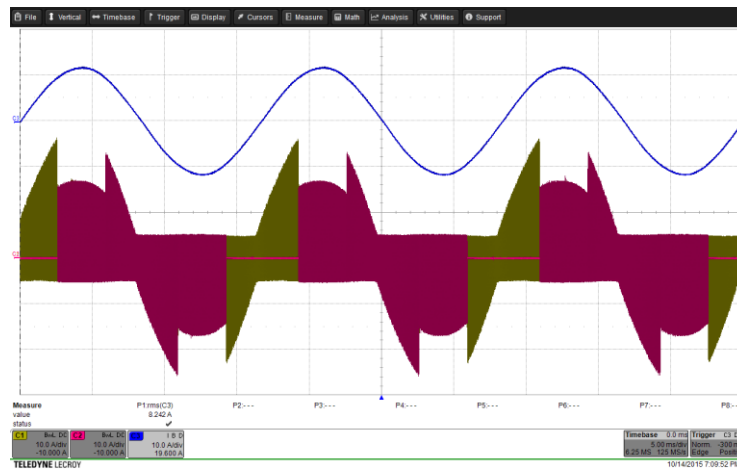
## Little Box 1.0-II Measurement Results (1)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer


Output Current  
Inductor Current Bridge Leg 1-1  
- Ohmic Load / 2kW  
Inductor Current Bridge Leg 1-2



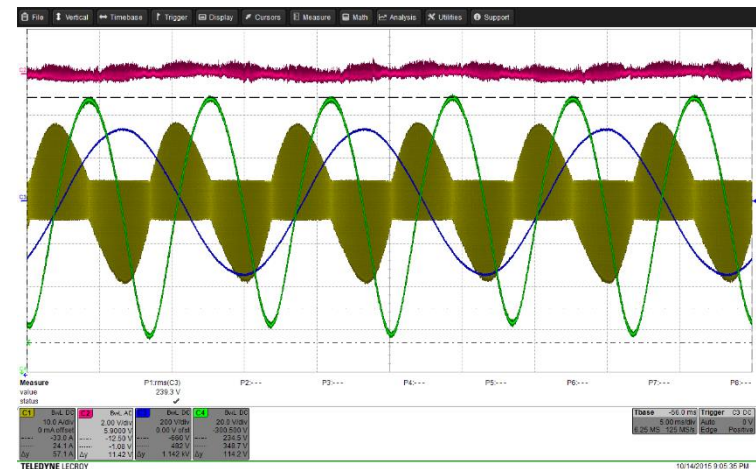DC Link Voltage (AC-Coupl.)  
Buffer Cap. Voltage  
Buffer Cap. Current  
Output Voltage




- Compliant to All Specifications

 
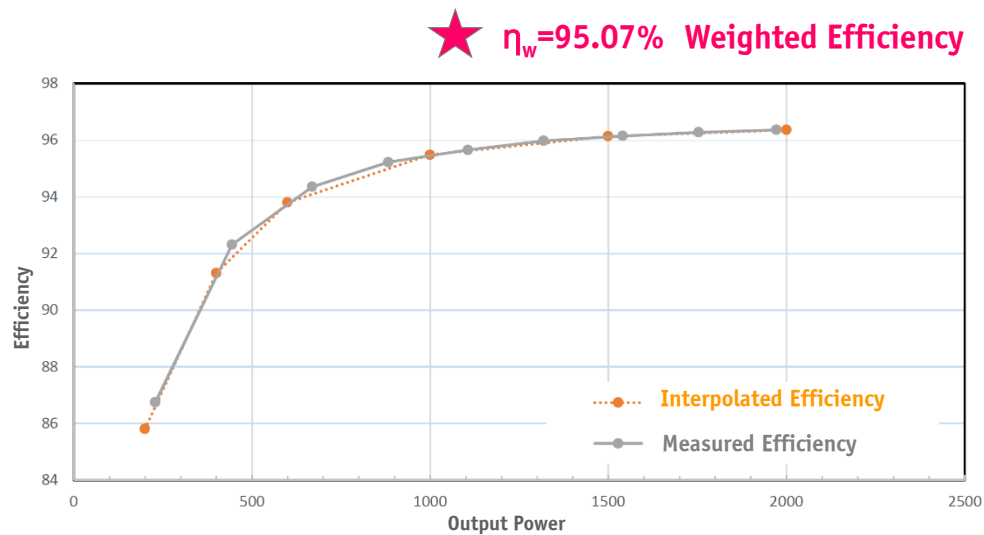
## Little Box 1.0-II Measurement Results (2)


- System Employing Active 1- $\Phi$  Power Pulsation Buffer




- Compliant to All Specifications
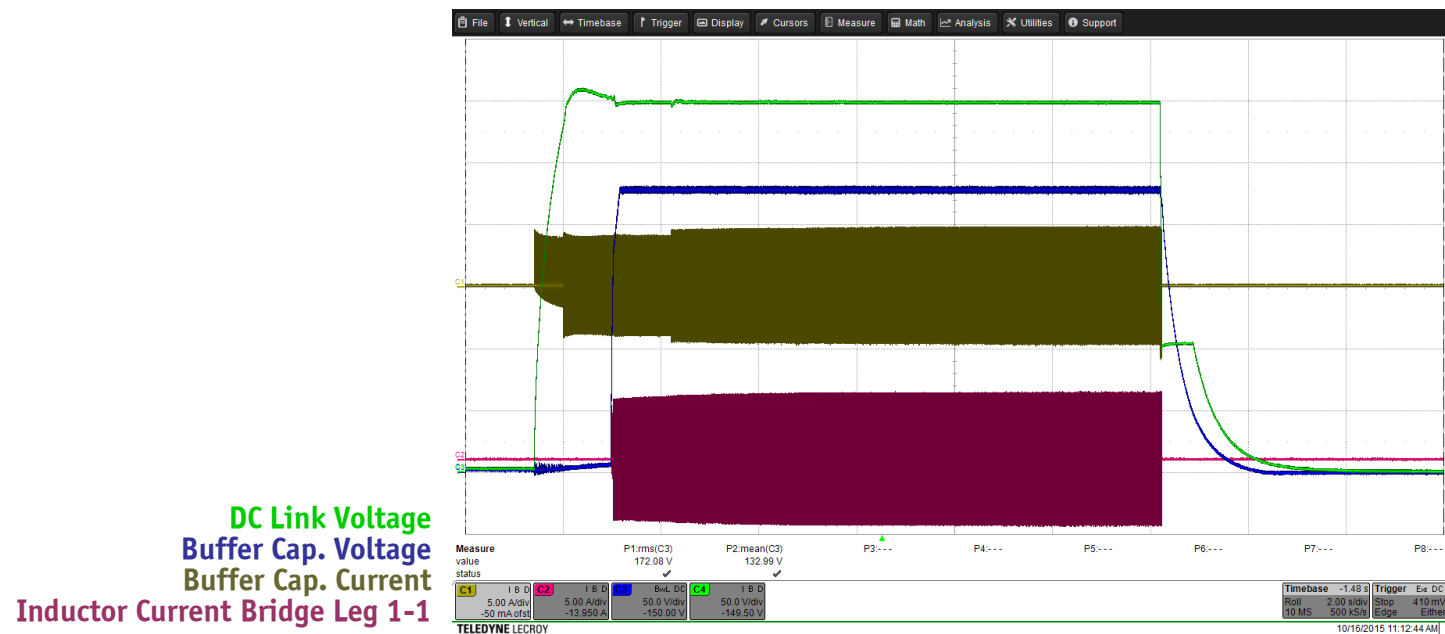
## Little Box 1.0-II Measurement Results (3)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer



 
- Start-up and Shut-Down (No Load Operation)



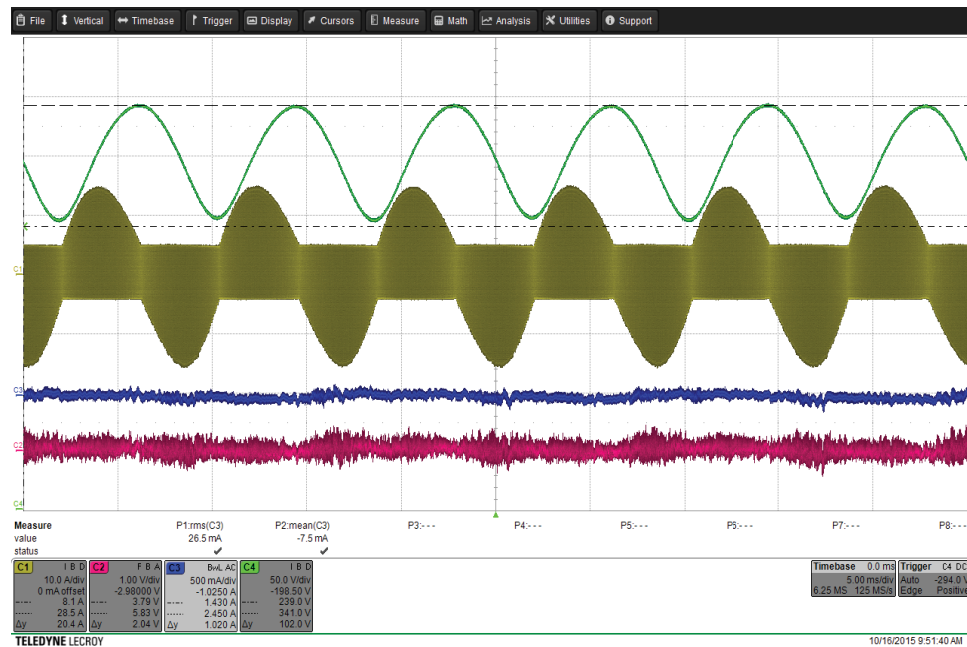
## Little Box 1.0-II Measurement Results (4)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer

Buffer Cap. Voltage  
 Buffer Cap. Current  
 Converter Input Current (AC Coupled)  
 DC Link Voltage (AC Coupled)




 - Stationary Operation @ 2kW Output Power



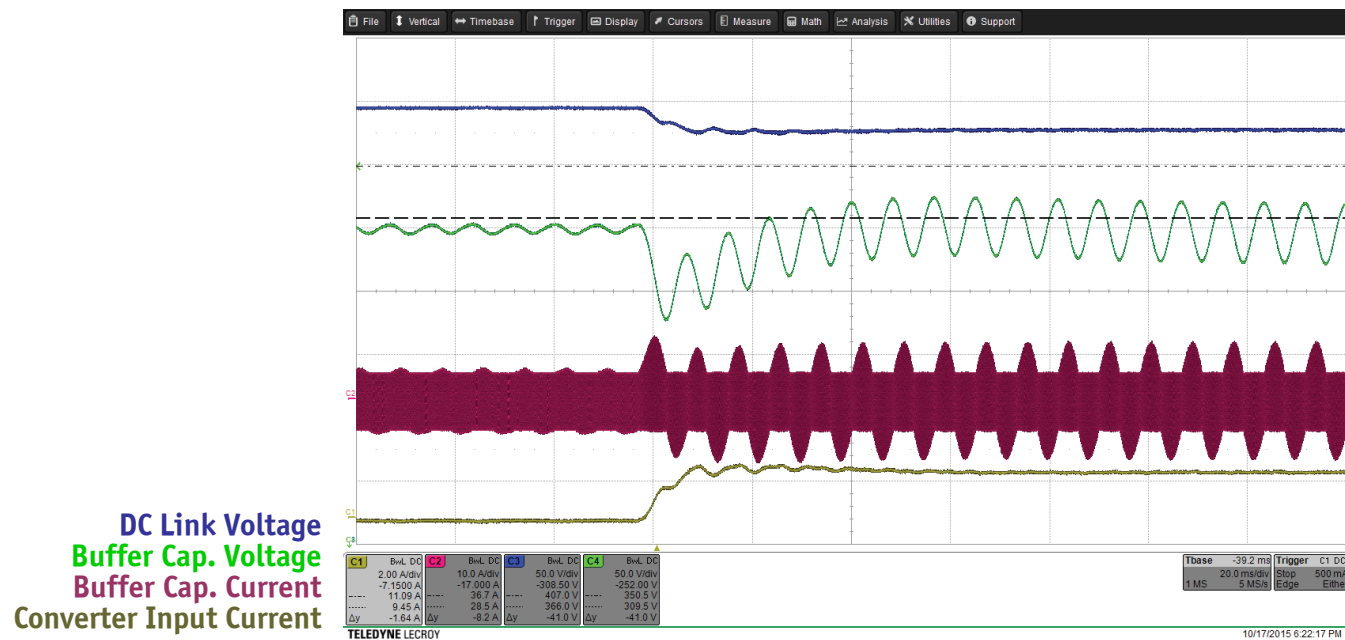
## Little Box 1.0-II Measurement Results (5)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer




 - Transient Response for Load-Step of 0 Watt  $\rightarrow$  700 Watt



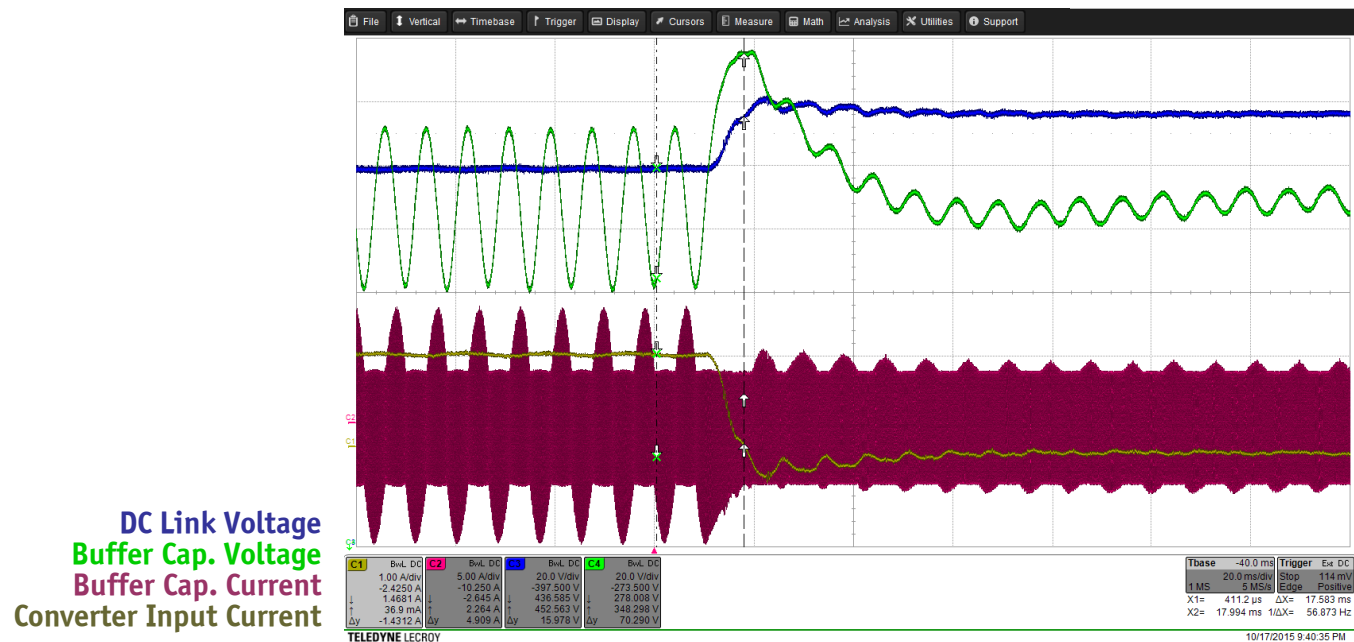
## Little Box 1.0-II Measurement Results (6)

- System Employing Active 1- $\Phi$  Power Pulsation Buffer




 - Transient Response for Load-Step of 700 Watt  $\rightarrow$  0 Watt




## Little Box 1.0-II Volume and Loss Distribution
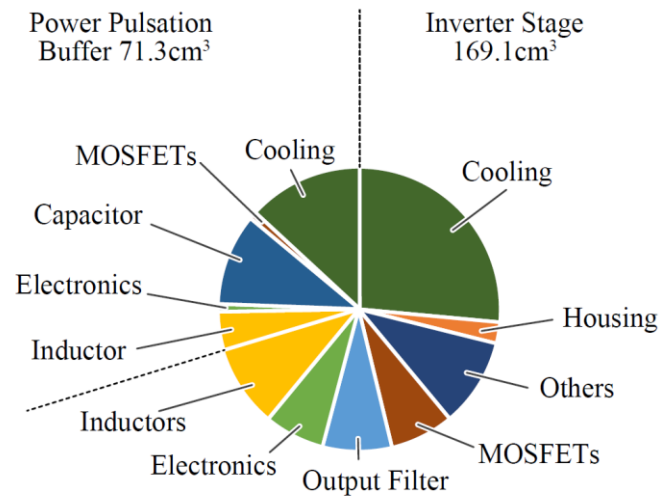
### Volume Distribution (240cm<sup>3</sup>)



### Loss Distribution (75W)

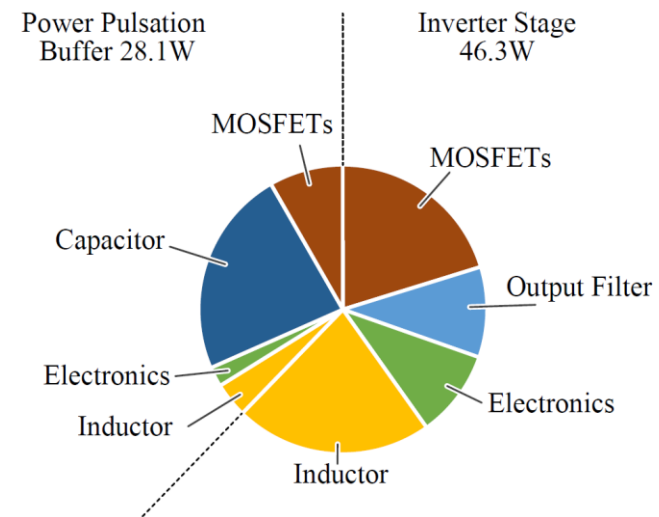

- Large Heatsink (incl. Heat Conduction Layers)
- Large Losses in Power Fluctuation Buffer Capacitor (!)
- TCM Causes Relatively High Conduction & Switching Losses @ Low Power
- Relatively Low Switching Frequency @ High Power – Determines EMI Filter Volume



## ■ *Other Finalists*



*Topologies*  
*Switching Frequencies*  
*Power Density / Efficiency Comparison* →

Detailed Descriptions:  
[www.LittleBoxChallenge.com](http://www.LittleBoxChallenge.com)


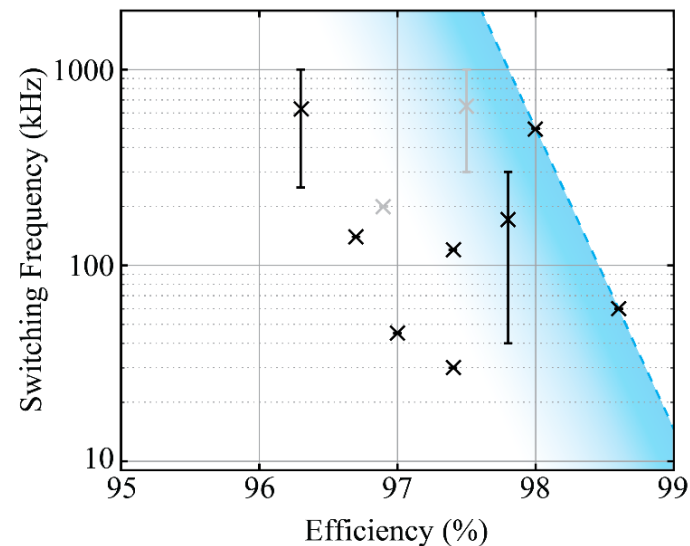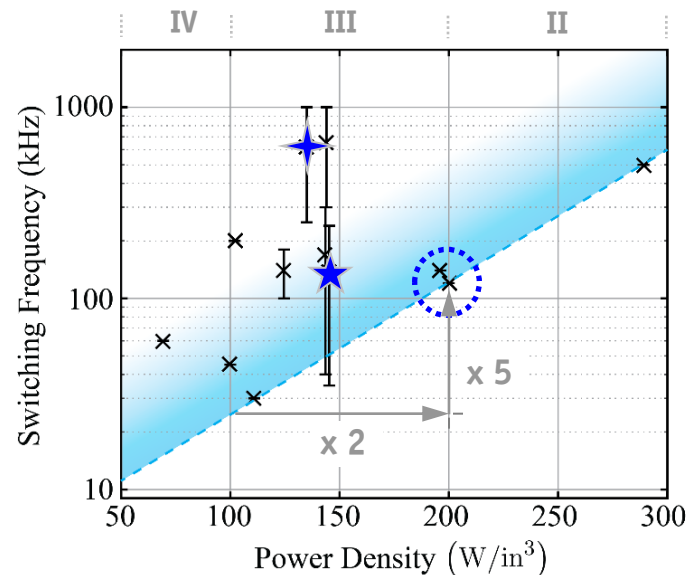
## Finalists - Performance Overview

- **18 Finalists (3 No-Shows)**
- 7 Groups of Consultants / 7 Companies / 4 Universities




- **70...300  $\text{W/in}^3$**
- **35 kHz...500kHz...1 MHz** (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps or Electrolytic Caps)
- **GaN (11 Teams)** / SiC (2 Teams) / Si (2 Teams)


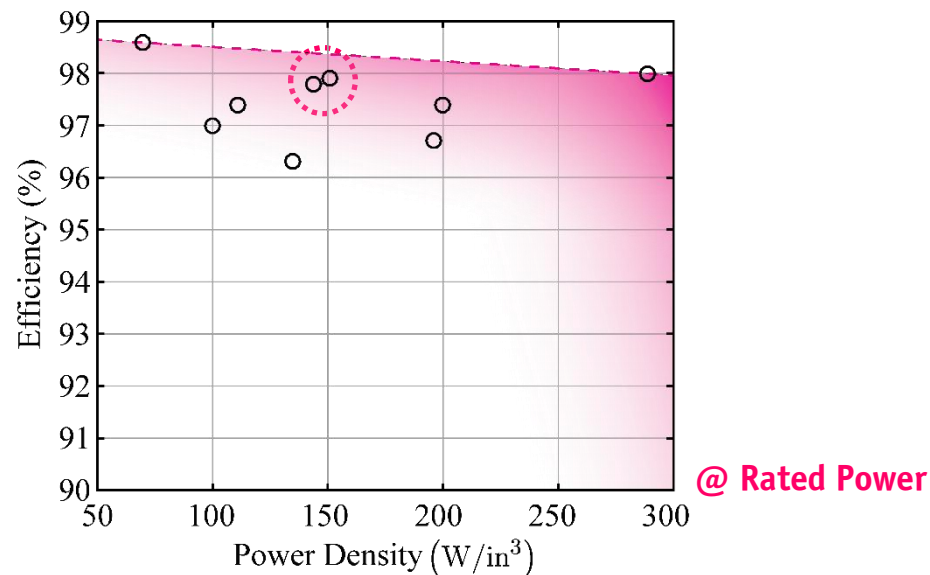
## Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities




- 70...300  $\text{W}/\text{in}^3$
- 35 kHz...500kHz...1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps or Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)


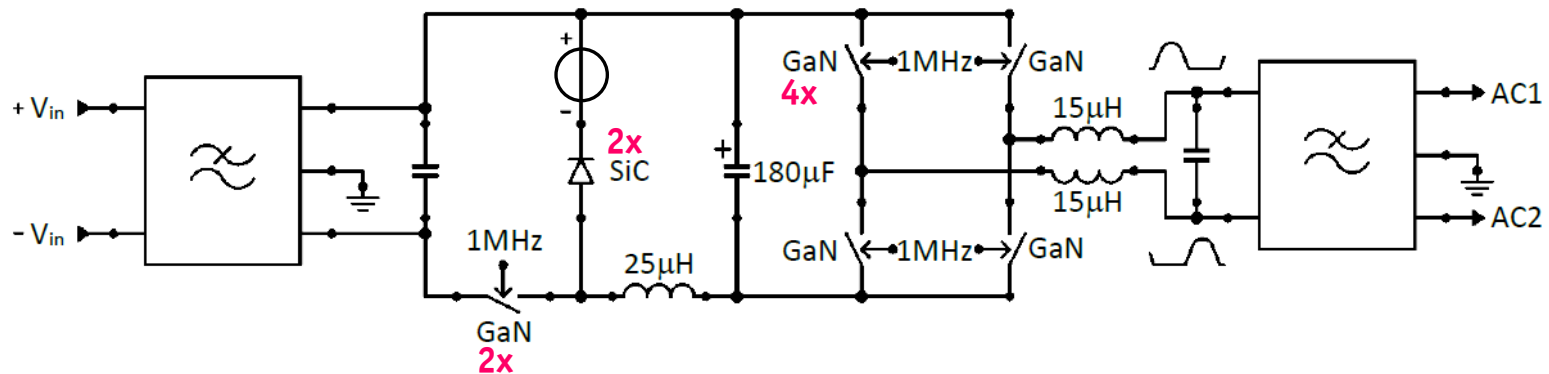
## Category I: 300 – 400 W/in<sup>3</sup> (1 Team)

- “Over the Edge”
- Hand-Wound Overstressed & Too Small Electrolytic Capacitors (210uF/400V)
- No Voltage Margin of Power Semiconductors (450V GaN, Hard Switching)
- 50V Voltage Source for Semicond. Voltage Stress Reduction
- Low-Frequ. CM AC Output Component




- Alternate Switching of Full-Bridge Legs
- Input Cap. of Full-Bridge Used for Power Pulsation Buffering
- 256 W/in<sup>3</sup> (400 W/in<sup>3</sup> Claimed) / 1MHz
- Multi-Airgap Toroidal Inductors (3F46,  $C_p \approx 1.5\text{pF}$ )
- Bare Dies Directly Attached to Pin-Fin Heatsink
- High Speed Fan (Mini Drone Motor & Propeller)


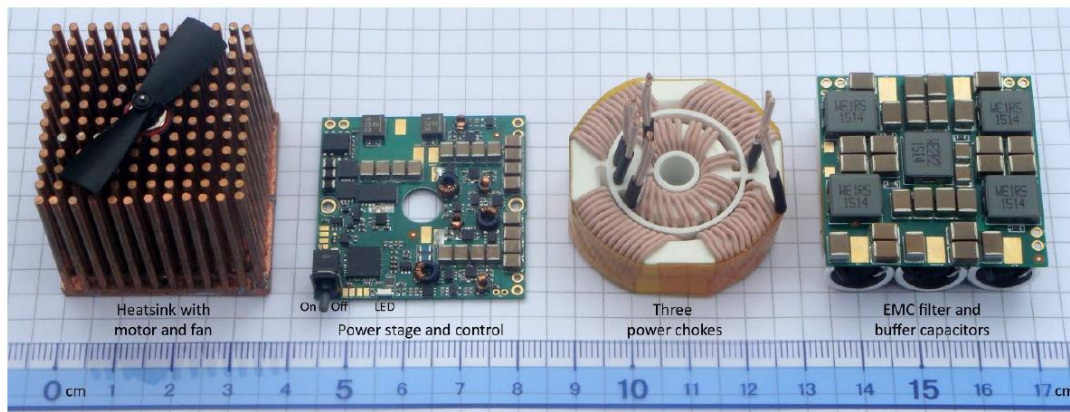
## Category I: 300 – 400 W/in<sup>3</sup> (1 Team)

- “Over the Edge”
- Hand-Wound Overstressed Electrolytic Capacitors (210uF (?)/400V)
- No Voltage Margin of Power Semiconductors (450V GaN, Hard Switching)
- 50V Voltage Source for Semicond. Voltage Stress Reduction





- Alternate Switching of Full-Bridge Legs
- Input Cap. of Full-Bridge Used for Power Pulsation Buffering
- 256 W/in<sup>3</sup> (400 W/in<sup>3</sup> Claimed) / 1MHz
- Multi-Airgap Toroidal Inductors (3F46,  $C_p \approx 1.5\text{pF}$ )
- Bare Dies Directly Attached to Pin-Fin Heatsink
- High Speed Fan (Mini Drone Motor & Propeller)



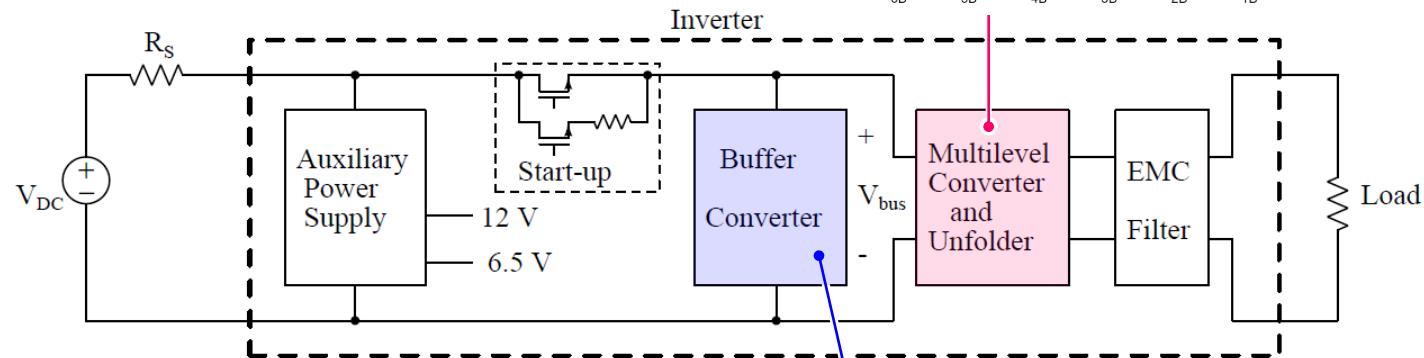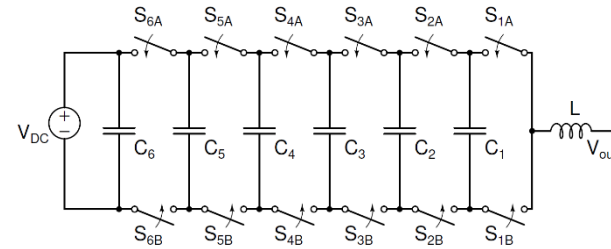
## Category II: 200 – 300 W/in<sup>3</sup> (4 Teams) – Example #1

- “At the Edge”
- High Complexity
- 7-Level Flying Capacitor Converter
- Series-Stacked Active Power Buffer



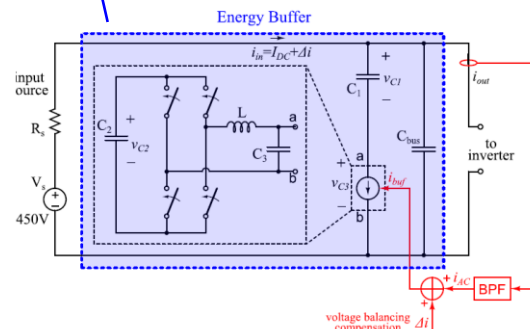
- 216 W/in<sup>3</sup>
- 100V GaN
- Integrated Switching Cell
- 720kHz Eff. Sw. Frequ. (7 x 120kHz)




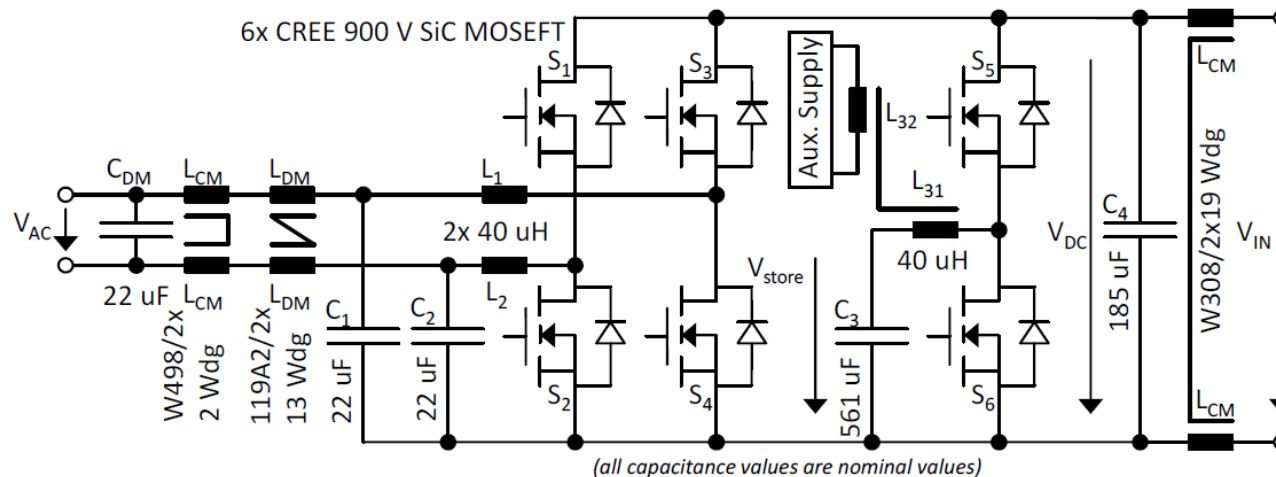
## Category II: 200 – 300 W/in<sup>3</sup> (4 Teams) – Example #2

- “At the Edge”
- Very Well Engineered Assembly (e.g. 3D-Printed Heatsink w. Integr. Fans, 1 PCB Board, etc.)
- No Low-Frequ. Common-Mode AC Output Component




- 201W / in<sup>3</sup>
- Multi-Airgap (8 Gaps) Inductors
- 900V SiC @ 140kHz (PWM, Soft & Hard Switching)
- Buck-Type Active DC-Side Power Pulsation Filter / Ceramic Capacitors (X6S)


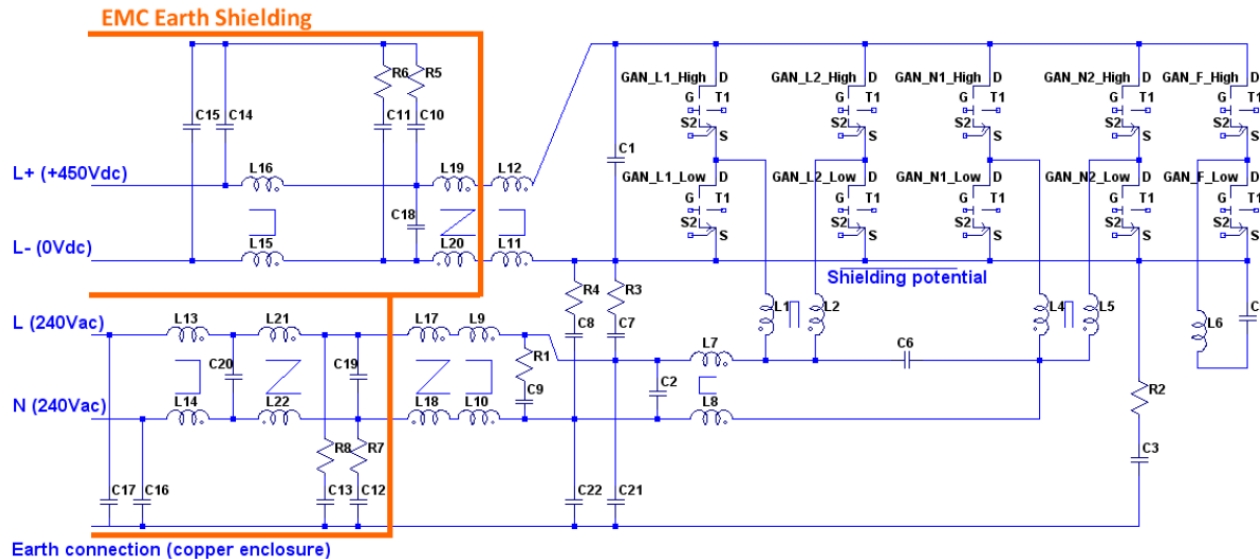
## Category III: 100 – 200 W/in<sup>3</sup> (8 Teams) – Example

- “Advanced Industrial”
- Sophisticated 3D Sandwich Assembly incl. Cu Honeycomb Heatsink
- Shielded Multi-Stage EMI Filter @ DC Input and AC Output
- No Low-Frequ. Common-Mode AC Output Component



- 143 W/in<sup>3</sup>
- GaN @ ZVS (35kHz...240kHz)
- 2 x Interleaving for Full-Bridge Legs
- Buck-Type DC-Side Active Power Pulsation Filter (<150μF)







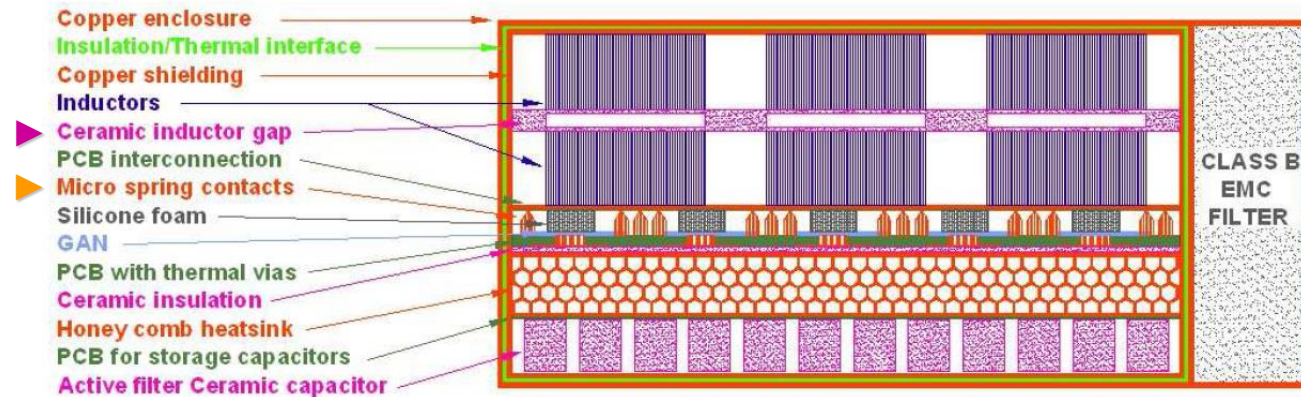
## Category III: 100 – 200 W/in<sup>3</sup> (8 Teams) – Example

- “Advanced Industrial”
- **Sophisticated 3D Sandwich Assembly** incl. Cu Honeycomb Heatsink
- Shielded Multi-Stage EMI Filter @ DC Input and AC Output
- No Low-Frequ. Common-Mode AC Output Component




- 143 W/in<sup>3</sup>
- GaN @ ZVS (35kHz...240kHz)
- 2 x Interleaving for Full-Bridge Legs
- Buck-Type DC-Side Active Power Pulsation Filter (<150μF)





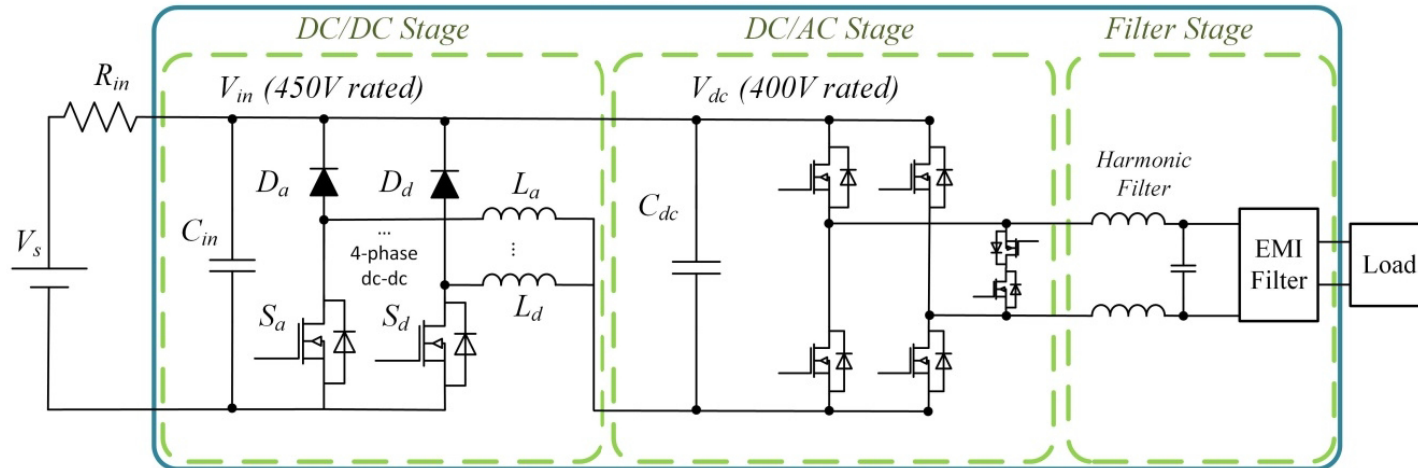
## Category IV: 50 – 100 W/in<sup>3</sup> (1 Team)

- “Industrial”
- 400V<sub>max</sub> Full-Bridge Input Voltage
- DC-Link Cap. Used as Power Pulsation Buffer (470uF)
- GaN Transistors / SiC Diodes (400kHz DC/DC, 60kHz DC/AC)
- Multi-Stage EMI Filter @ AC Output and L<sub>CM</sub> + Feed-Trough C<sub>CM</sub> @ DC Inp. (Not Shown)



- $\approx 70 \text{ W/in}^3$
- 98% CEC Efficiency
- 4.4% DC Input Current Ripple
- 54°C Surface Temp. / Cooling with 10 Mirco-Fans

 ■ **Competition  
Conclusions**  
*Key Technologies  
Power Density Limit* →



# Google Little Box Challenge Summary

## ■ Overall

- Engineering “Jewels”
- No (Fundamentally) New Approach / Topology
- Passives & 3D-Packaging are Finally Defining the Power Density
- Careful Heat Management (Adv. Heat Sink, Heat Distrib., 2-Side Integr. Cooling, etc.)
- Careful Mechanical Design (3D-CAD, Single PCB, Avoid Connectors, etc.)
- Clear Power Density / Efficiency Trade-Off

## ■ 200W/in<sup>3</sup> (12kW/dm<sup>3</sup>) System


- $f_s < 150\text{kHz}$  (Constant)
- SiC (Not GaN)
- ZVS (Partial)
- Full-Bridge Output Stage
- Active Power Pulsation Buffer (Buck-Type, X6S Cap.)
- Conv. EMI Filter Structure
- Multi-Airgap Litz Wire Inductors
- DSP Only (No FPGA)

100+ Teams  
3 Members / Team, 1 Year  
300 Man-Years  
3300 USD / Man-Year



 
## Analysis of Advanced Concepts & Technologies

X6S Capacitors  
Series Power Pulsation Buffer  
Optimal Frequency Modulation  
Flying Cap. Converter Topology  
Autotrafo-Based Inverter


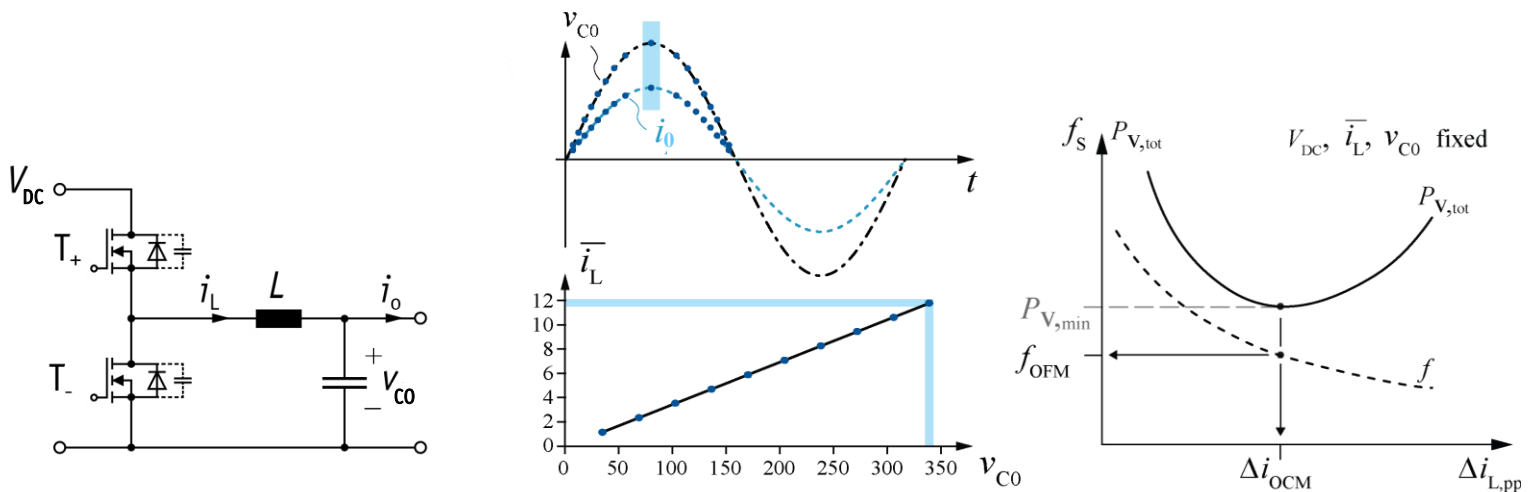
## Eff. Optimal Frequ. / Current-Ampl. Modulation (1)


- **TCM** -- Enables ZVS but Suffers From Large Current Ripple & Wide Frequency Variation
- **PWM** -- Const. Sw. Frequency but Hard Switching Around AC Current Maximum
- **Optimal Combination of TCM and PWM** → Optim. Frequ. / Curr. Ripple Variation Over Mains Period
- Experimental Determination of **Loss-Opt. Sw. Frequency  $f_{OFM}$**  Considering DC/DC Conv. Stage
- DC/AC Properties Calculated Assuming Corresponding Local DC/DC Operation




- **Loss-Optimal Local Sw. Frequ.  $f_{OFM}$**  for Given  $V_{DC}$  & Local Avg. Value of  $i_L$  & Local Outp. Cap. Voltage  $v_{C0}$
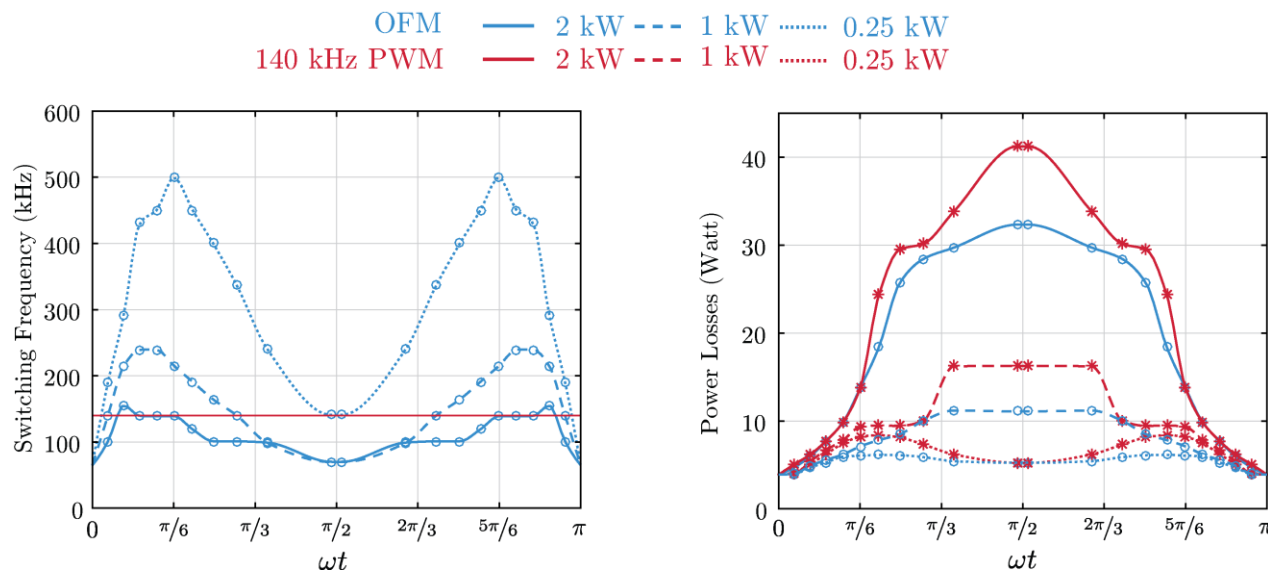
## Eff. Optimal Frequ. / Current-Ampl. Modulation (2)

- Calculated Optimal Sw. Frequ. & Power Loss as Function of the Position in a Mains Half Cycle
- Comparison with 140 kHz Const. Frequency PWM




 - Higher Average Switching Frequency @ Light Loads
- Reduction of  $f_{sw}$  Around Peak of Mains Voltage (for Ohmic Load) in Order to Sustain ZVS


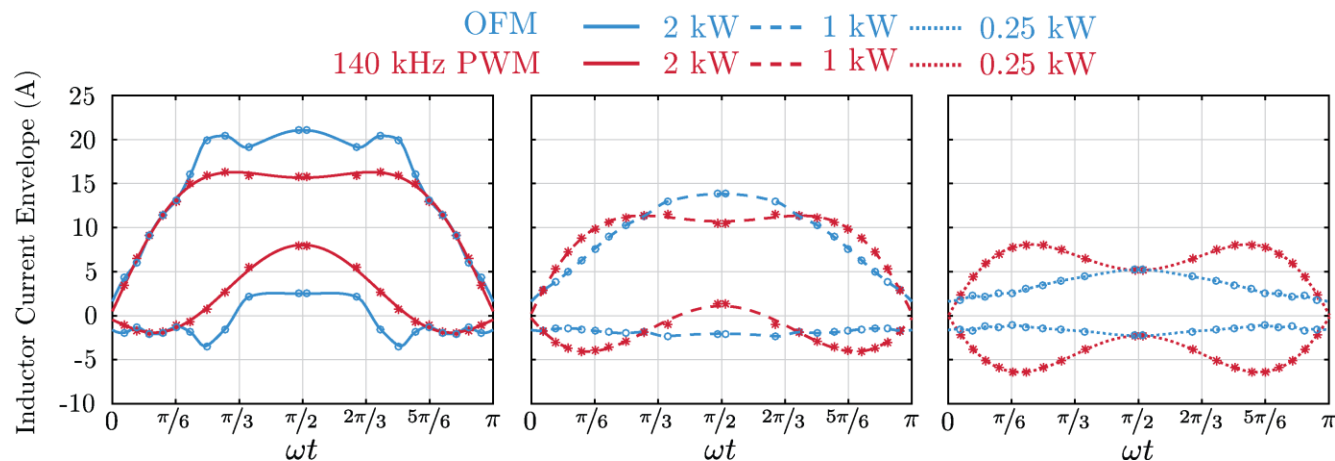
## Eff. Optimal Frequ. / Current-Ampl. Modulation (3)

- Resulting Inductor Current Envelope for Different Output Power Levels






- Higher Average Switching Frequency @ Light Loads
- Reduction of  $f_{sw}$  Around Peak of Mains Voltage (for Ohmic Load) in Order to Sustain ZVS




## CeraLink / X6S Large-Signal Analysis (1)

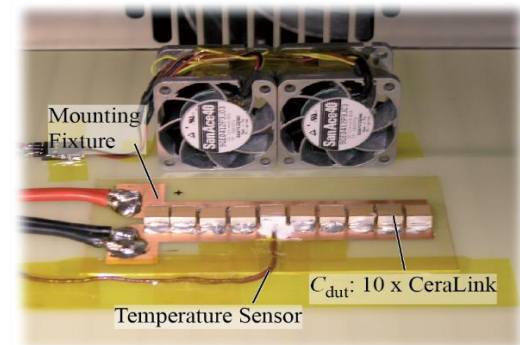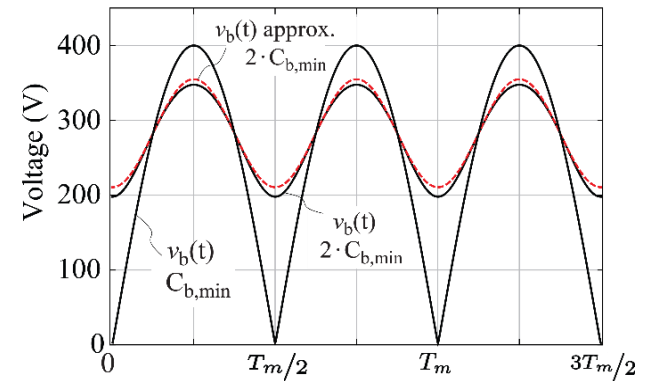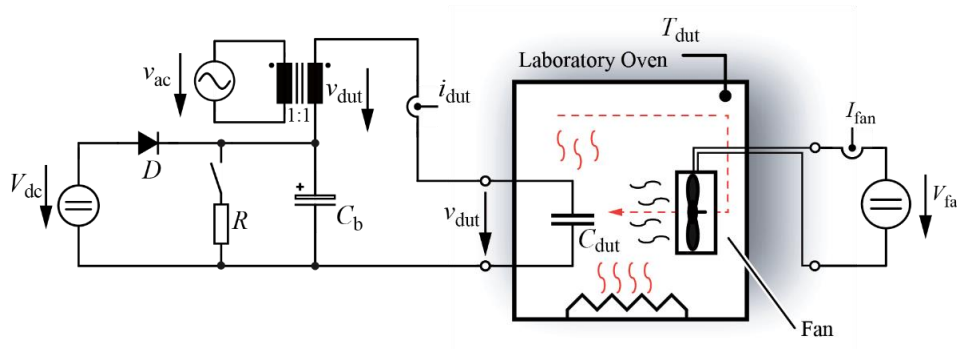- **2.2  $\mu$ F/450V Class II X6S MLCC (TDKs) Features Highest Energy Density**
- **Performance Comparison with Novel CeraLink Capacitor**

- **Experimental Setup for Generation of DC Bias & Superimposed AC Voltage**



 - **PPB Design Optimiz.** Requires **Large-Signal Capacitance** and **Power Loss Data** in All Operating Points





## CeraLink / X6S Large-Signal Analysis (2)



- Variation of DC Bias and Superimposed AC Voltage @ 60°C Operating Temp.

✗ Designed Op. Point


EPCOS/TKD  
CeraLink 2μF, 600V ▶

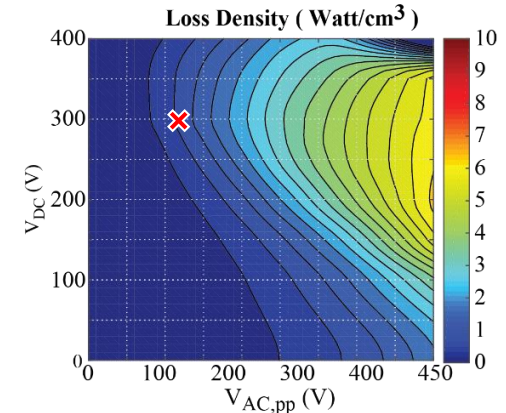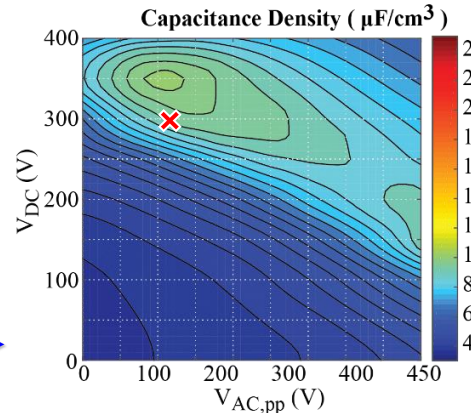

TDK Class II  
X6S MLCC 2.2μF, 450V ▶

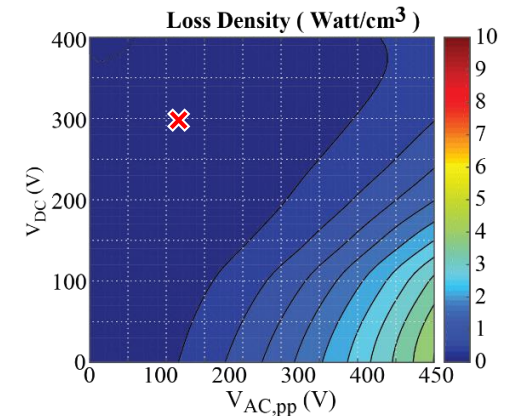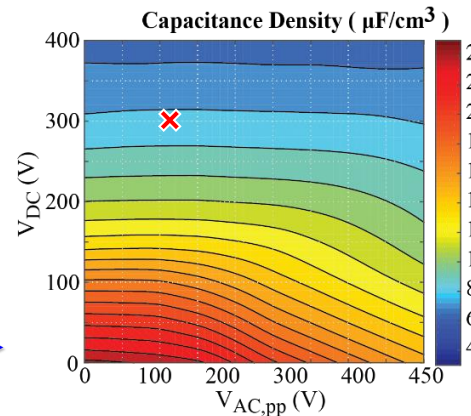


 
- PPB Design Optimiz. Requires Large-Signal Capacitance and Power Loss Data in All Operating Points



# Power Pulsation Buffer – Partial-Power Approach (1)


- Performance Comparison of Full-Power and Partial-Power Power Pulsation Buffer (PPB) Concepts
- Hybrid Approach (IV) Employs Red. Size Electrolytic DC-Link Cap. and Series-Conn. Partial-Power PPB
- Capacitor Volumes are Incl. Heatsink Vol. for Loss Dissipation ( $CSPI_{eff} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$ )

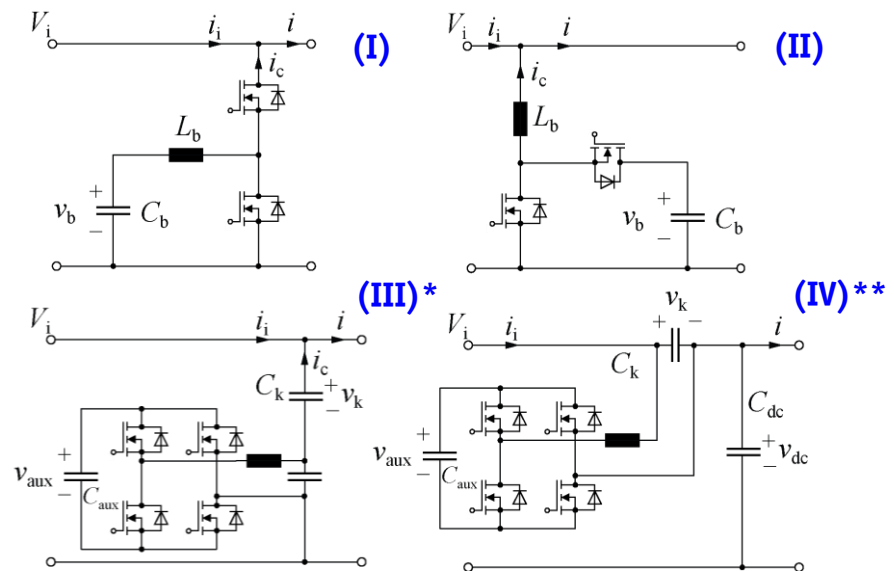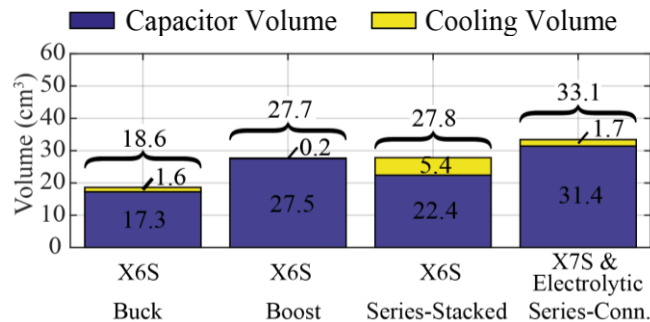- (I) Buck-Type  
(II) Boost-Type  
(III) Partial-Power Series-Stacked  
(IV) Partial-Power Series-Connected




■ Buck-Type PPB Realized with  $2.2\mu\text{F}/450 \text{ V}$  X6S MLCC Features Smallest Cap. Volume

\*Pilawa  
\*\* Schneider  
Electric

 

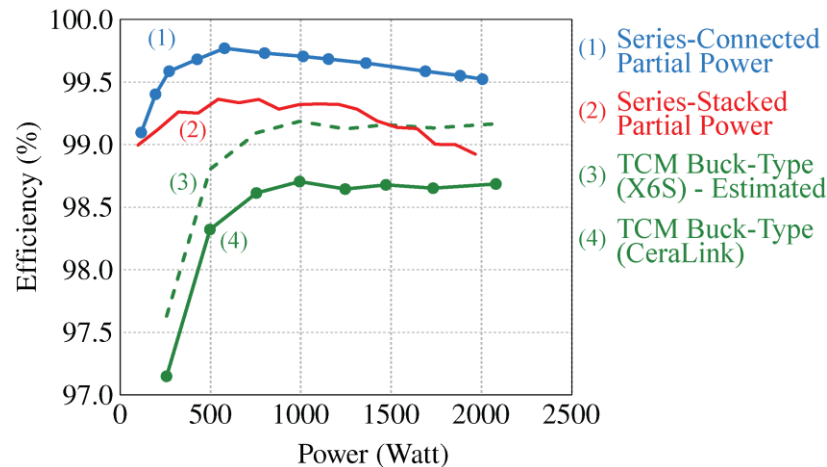
## Power Pulsation Buffer – Partial-Power Approach (2)

- Performance Comparison of Full-Power and Partial-Power Power Pulsation Buffer (PPB) Concepts
- Partial-Power Concepts Feature Higher Efficiency Especially @ Light Load



- Peak Efficiency of 99.75% Reached with Series-Connected PPB @ 600 Watt
- Part-Load Efficiency of Buck-Type PPB Expected to be Higher with PWM

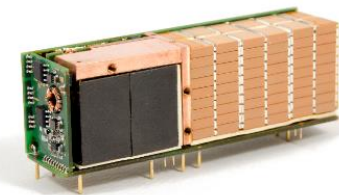
**Buck-Type with CeraLink**  
Vol. = 76.6 cm<sup>3</sup>  
η = 98.7 %




**Series-Conn. Partial-Power**  
Vol. = 57.31 cm<sup>3</sup>  
η = 99.5 %



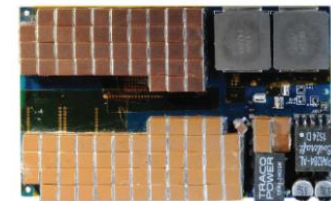**Series-Stacked Partial-Power\***  
Vol. = 80 cm<sup>3</sup>  
η = 98.9 %




\*Pilawa

 


# Performance of Series-Type Partial-Power PPB (1)
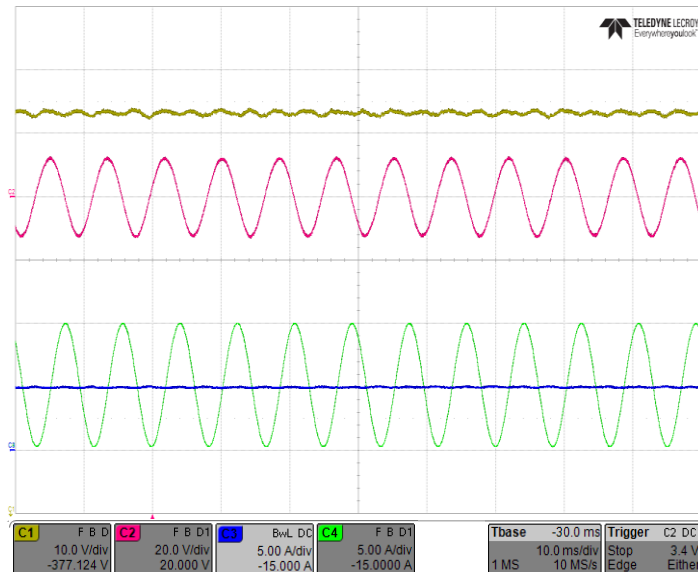
## Stationary Operation @ Rated Power of 2 kW

Input Voltage,  $v_i$   
 Filter Voltage,  $v_f$   
 Input Current,  $i_i$   
 Pulsating Current,  $i_o$




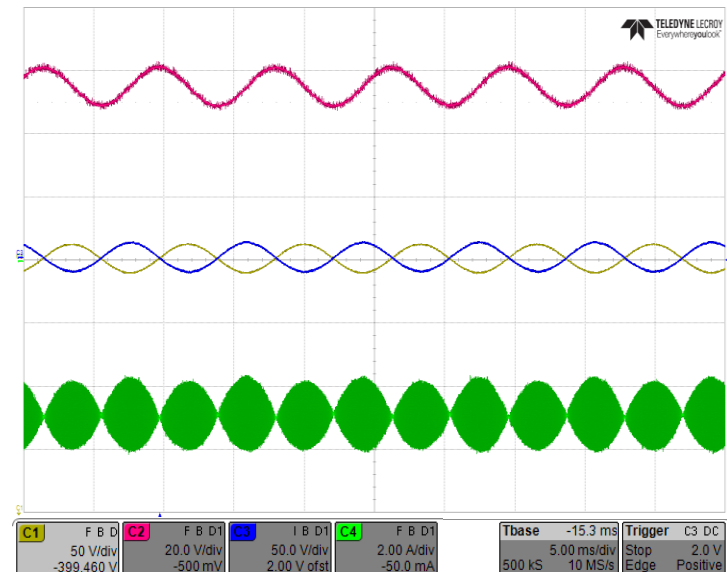Buffer Voltage,  $v_{buf}$   
 DC-Link Voltage,  $v_{dc}$   
 Filter Voltage,  $v_f$   
 Filter Current,  $i_f$



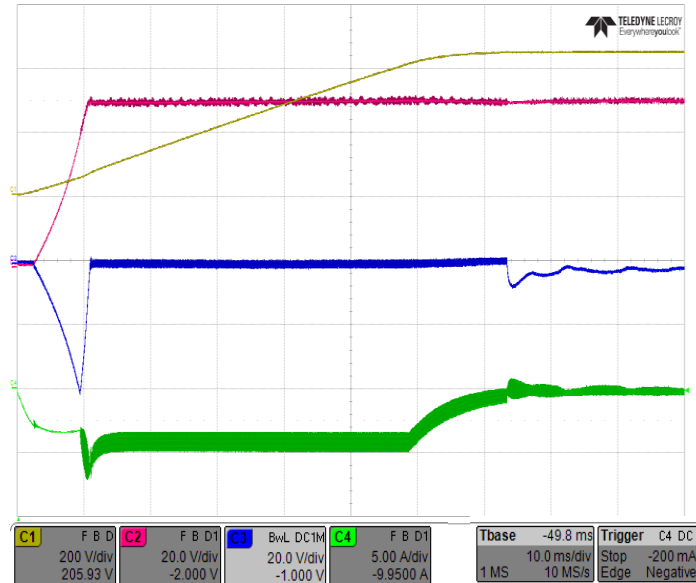
## Performance of Series-Type Partial-Power PPB (2)

Buffer Voltage,  $V_{buf}$   
 DC-Link Voltage,  $V_{dc}$   
 Filter Voltage,  $V_f$   
 Filter Current,  $i_f$



■ Startup of the Converter

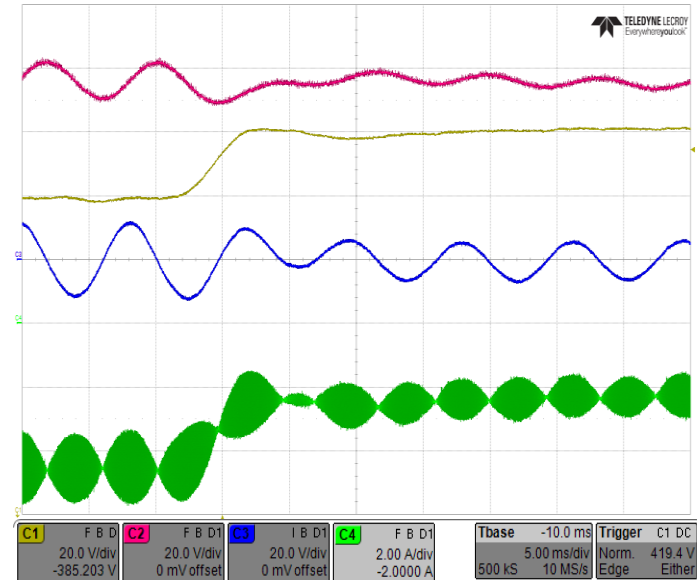Buffer Voltage,  $V_{buf}$   
 Input Voltage,  $V_i$   
 Filter Voltage,  $V_f$   
 Filter Current,  $i_f$






■ Load Step 2kW → 1kW


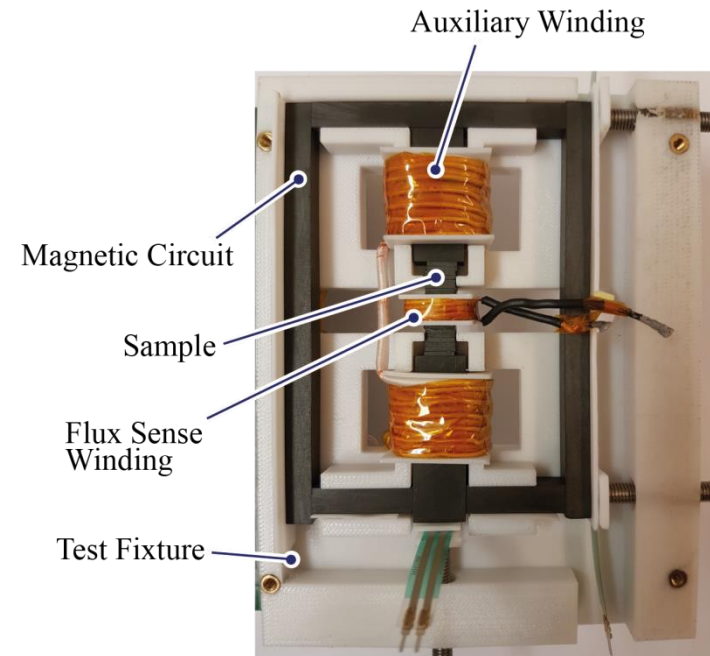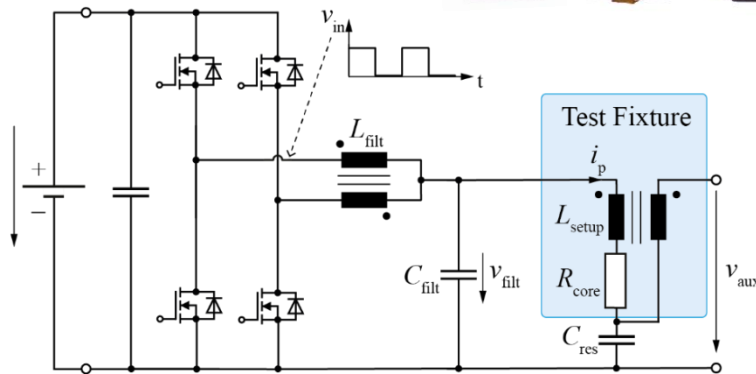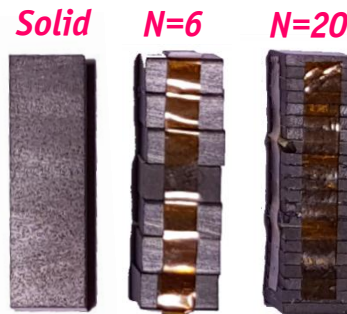
# Multi-Airgap Inductor Core Loss Measurements (1)

- Investigated Materials - DMR51, N87, N59
- 30  $\mu\text{m}$  PET Foil with Double Sided Adhesive Between the Plates
- Varying Number  $N$  of Air Gaps Assembled from Thin Ferrite Plates
- Number of Air Gaps:



- Sinusoidal Excitation with Frequencies in the Range of 250 kHz ...1MHz



# Multi-Airgap Inductor Core Loss Measurements (2)

- High-Q Low-Pass Filtering of 50% Duty Cycle Volt. Ensures Sinus. Excitation
- Operation @ Resonance for High Measurement Accuracy
- No Phase Displacement of Sensed Voltage and Current
- Flux Density Adjusted by Input Voltage Level




\* Mu (2015)

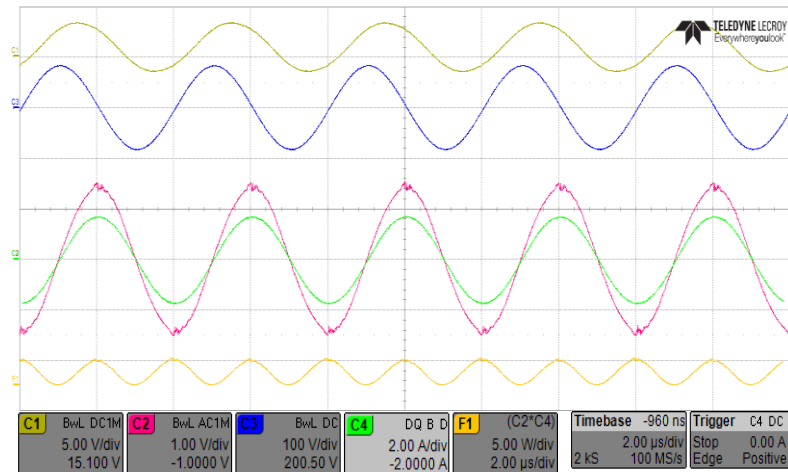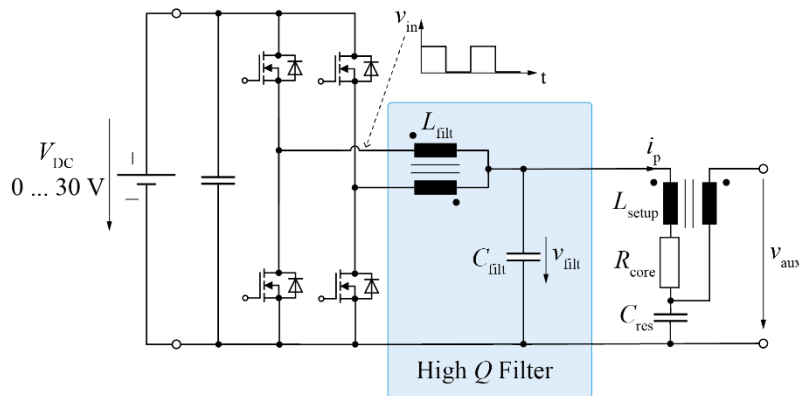Filter Cap. Voltage  $v_{\text{filt}}$   
Flux Sense Voltage  
Auxiliary Voltage  $v_{\text{aux}}$   
Primary Current  $i_p$   
Core Losses  $p_{\text{loss}}$






 

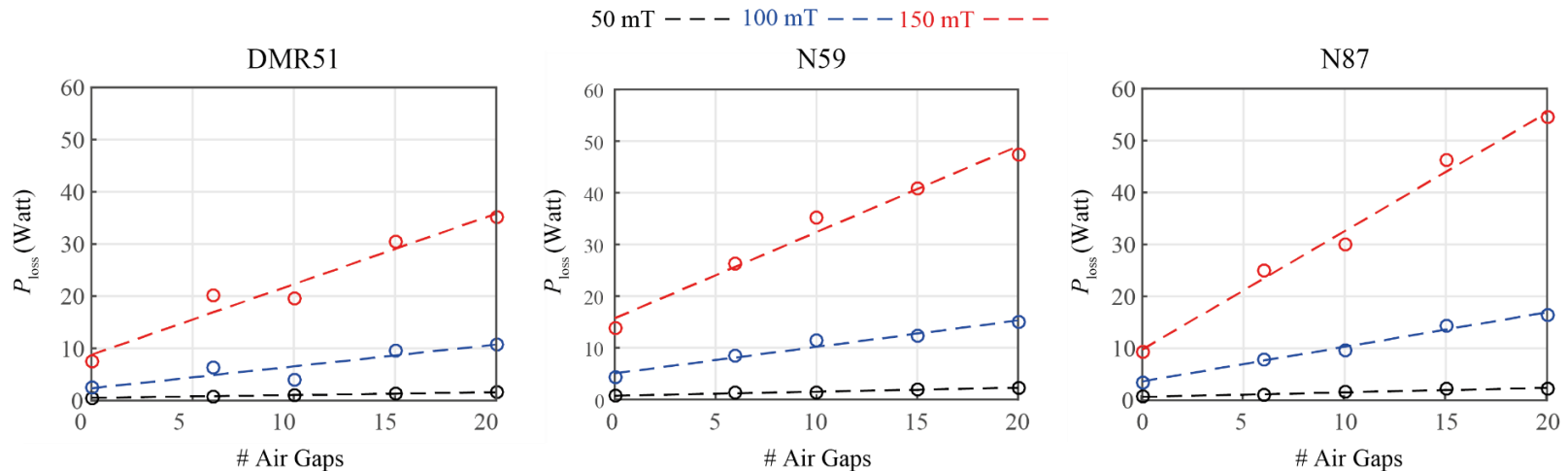
## Multi-Airgap Inductor Core Loss Measurements (3)

- Total Core Loss in Sample with Varying Air Gaps and Test Fixture
- Excitation @ 500 kHz





 - Losses Increase Linearly with the Number of Introduced Air Gaps
- Conclusion -- Surface Layers Deteriorated by Machining of Ferrite



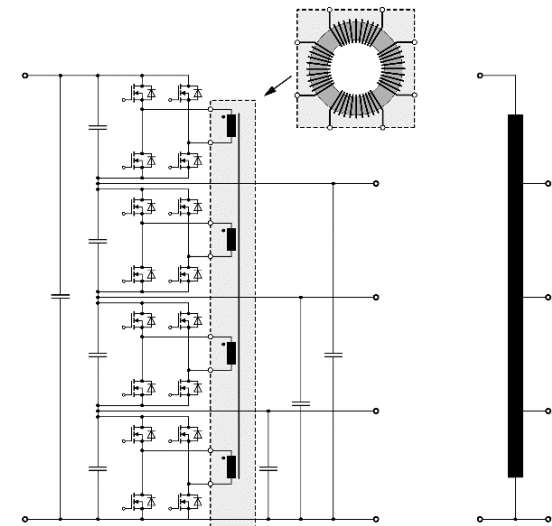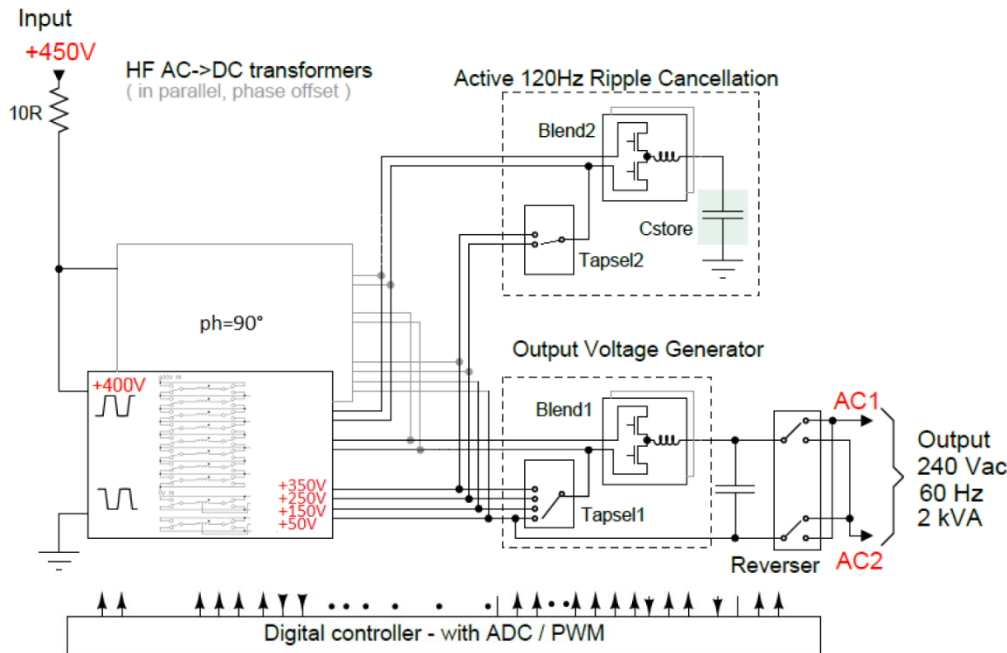
# Sw. Frequ. Auto-Transformer Approach

- Multi-Tap Switching Frequ. Multi-Air-Gap Autotransformer Realizing a Multi-Tap Voltage Divider
- Tap Switch & Series Active Filter for Gen. of Sinus. Output Voltage from Multi-Step Waveform
- Low-Voltage Power Semiconductors




 - Concept Presented by "Cambridge Active Magnetics" @ Final
- Power Density Unclear (Presentation @ Final: 159W/in<sup>3</sup>, 290W/in<sup>3</sup> Shown as Target in Report)
- Efficiency Unclear (10W of Losses @ 2kW in Documentation, Equal to Only  $R = 150\text{m}\Omega$  in Total?)




## Multi-Tapped Sw. Frequ. Auto-Transformer (1)

- Multi-Stage Multi-Level Inverter

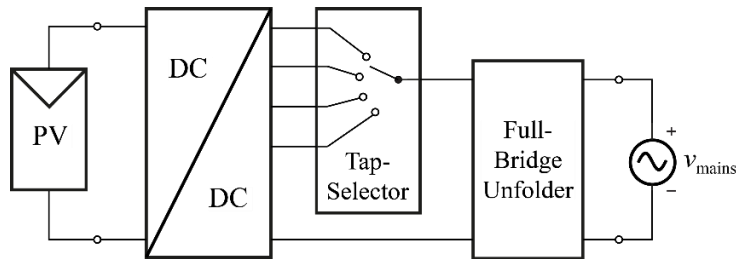


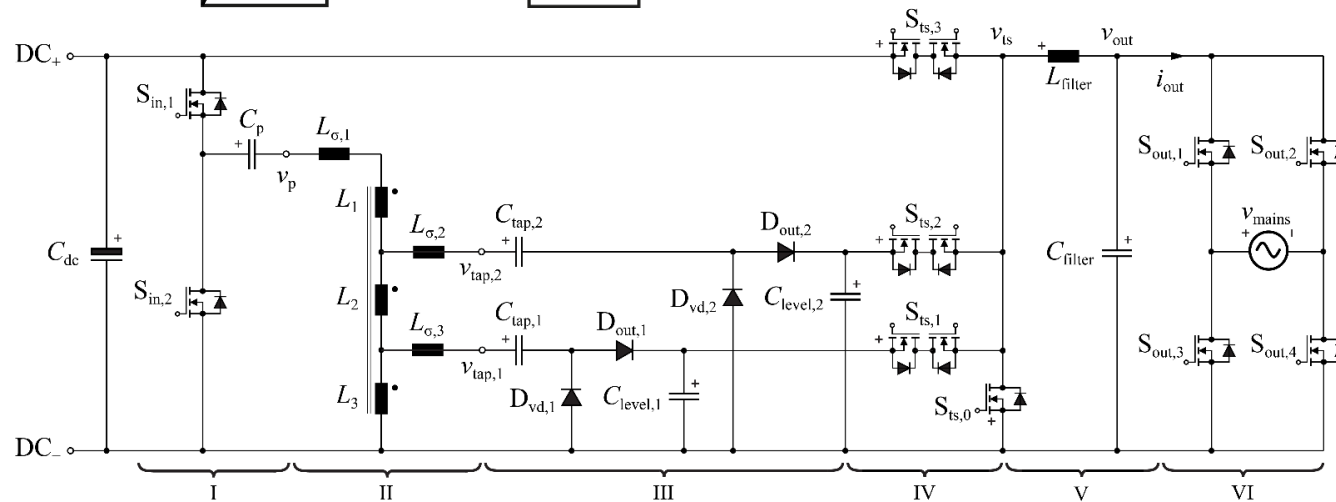- DC-AC-DC (I) Resonant ZVS Half-Bridge  
(II) Multi-Tapped Auto-Transf.  
(III) Voltage-Doubler Rectifier
- DC-AC (IV) PWM Tap-Selector  
(V) Output Filter  
(VI) Full-Bridge Unfolder




 
■ Topology & Operation Different to Approach Presented by "Cambridge Active Magnetics"






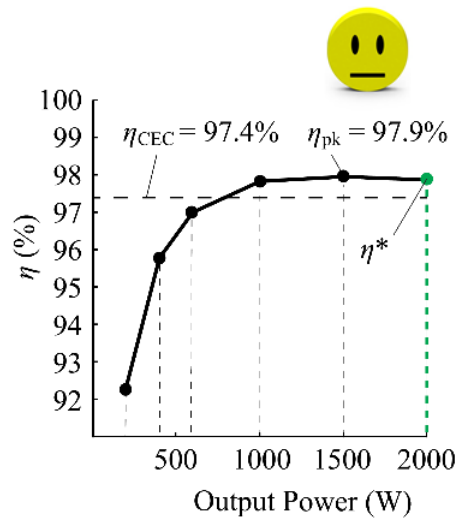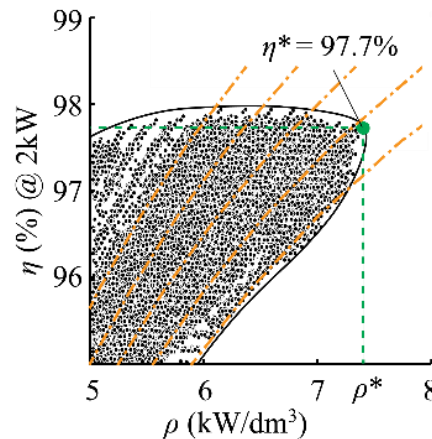
## Multi-Tapped Sw. Frequ. Auto-Transformer (2)

- $\eta\rho$ -Pareto Optimization of the Converter System
- Efficiency **97.7% @ 2kW (97.4% CEC)**
- Power Density **120W/in<sup>3</sup> (7.4kW/dm<sup>3</sup>)**



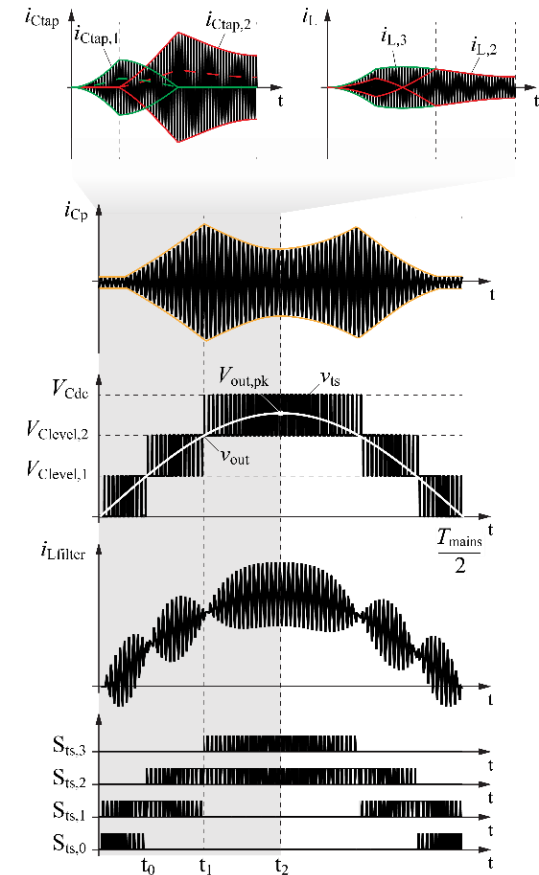- Efficiency of Resonant Multi-Level DC/DC Stage **> 99%**



 

# Multi-Level Converter Approach

- Multi-Level PWM Output Voltage - Minimizes Ind. Volume
- Flying Cap. Conv. – No Splitting of DC Inp. Voltage Required
- Low-Voltage GaN or Si Power Semiconductors



(11) EP 2 779 410 A2

(12) EUROPEAN PATENT APPLICATION

→ (43) Date of publication: 17.09.2014 Bulletin 2014/38

(51) Int. Cl.: H02M 7/483 (2007.01)

(21) Application number: 14159869.8

(22) Date of filing: 14.03.2014

(84) Designated Contracting States:  
AL AT BE BG CH CY CZ DE DK EE ES FI FR GB  
GR HR HU IE IT LI LT LU LV MC MK MT NL NO  
PL PT RO RS SE SI SK SM TR  
Designated Extension States:  
BA ME

(71) Applicant: Solaredge Technologies Ltd. ←

(72) Inventor: Yoscovitch, Ilan  
45240 Hod Hasharon (IL)


(74) Representative: Jansen, Cornelis Marinus et al  
V.O.  
Johan de Wittlaan 7  
2517 JR Den Haag (NL)

(30) Priority: 14.03.2013 US 201313826556

(54) Multi-level inverter


■ Basic Patent on FCC Converter – Th. Meynard (1991) !


FIG. 1

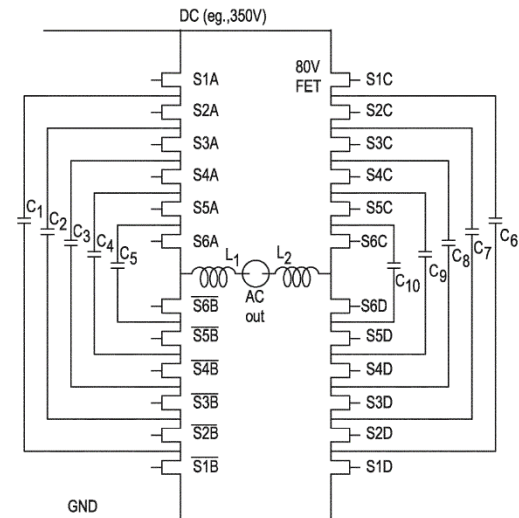

Full-Bridge  
Topology or  
DC/AC Buck-Type  
+ Unfolder




FIG. 4

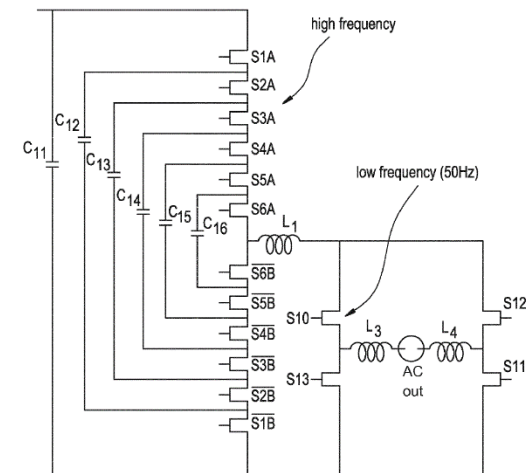

 

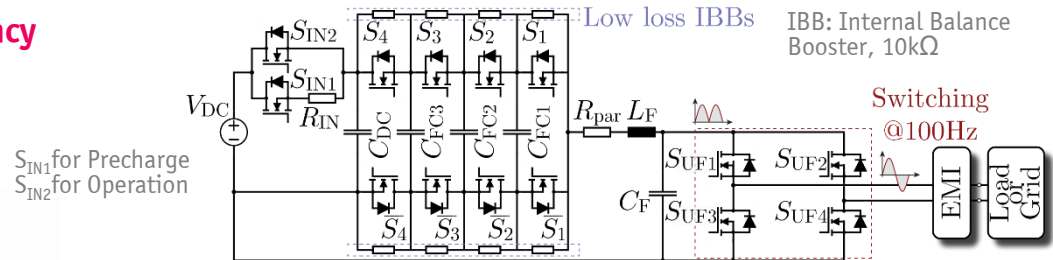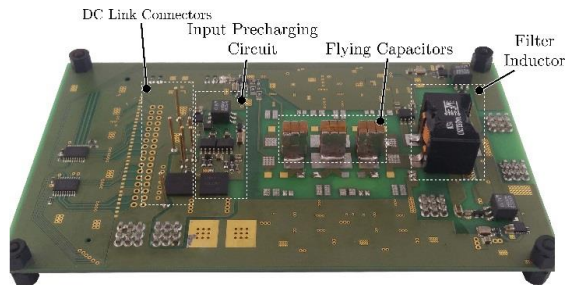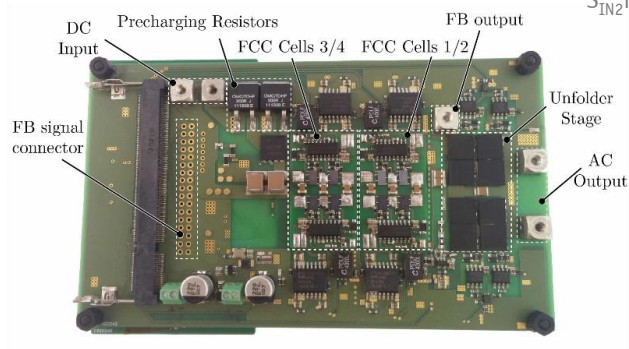
## Multi-Level Conv. Approach – Flying Cap. Conv. (1)


- 5 Voltage Levels
- 320 kHz Single-Cell Sw. Frequency
- 12 $\mu$ F Flying Capacitors
- Improved Phase-Shift PWM




Output Voltage before the output filter

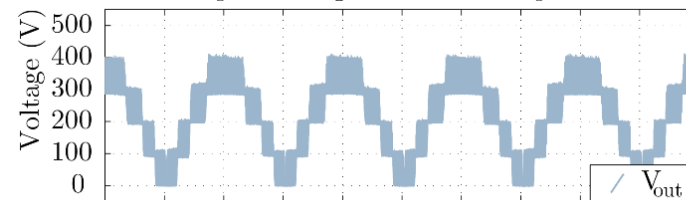

Output Voltage - Output Current

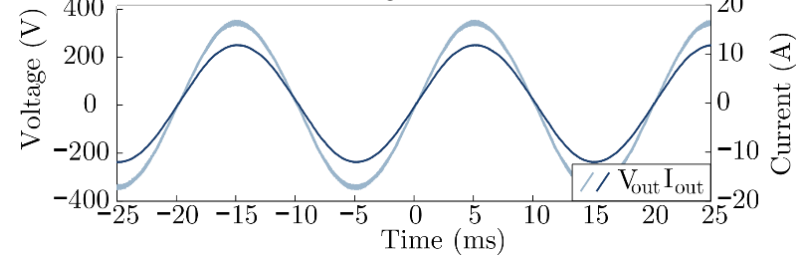

 


## Multi-Level Conv. Approach – Flying Cap. Conv. (2)

- Analysis of Symmetry of FC Voltages During Start-Up, Shut-Down, Stand-By, Output S.C. Missing
- Inverter & Rectifier Operation



**(I) Rectifier Operation – No Load, PWM Disabled**  
**@  $t=0$ , FCs Discharging over Balance Resistors,**  
**Voltage Symmetry Maintained, PWM Re-Enabled**  
**@  $t=150\text{ms}$ ,  $U_{\text{out}}$  Control @  $t=300\text{ms}$**

**(II) Rectifier Operation Under Load, Loss of Mains**  
**or PWM Disabled (Load Still Present), FCs**  
**Discharging over Diodes – Voltage Unbalance,**  
**Bridge Leg Re-Enabled @  $t=150\text{ms}$ , Dedicated**  
**Control Procedure Requ. for Regaining FC Volt.**  
**Symmetry**

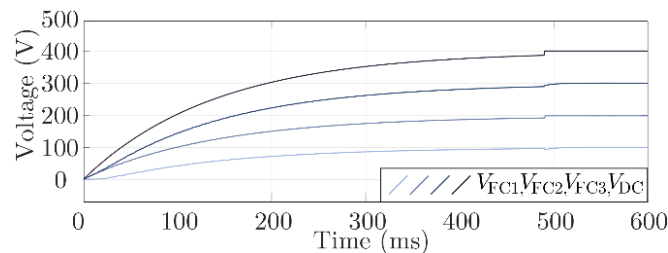**(III) Inverter Operation – Start-Up from DC-Side,**  
**Pre-Charge Resistors Bridged @  $t=500\text{ms}$**



**(III)**

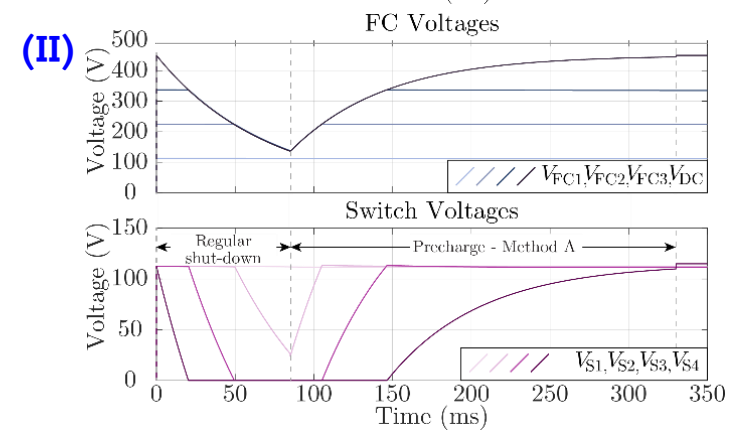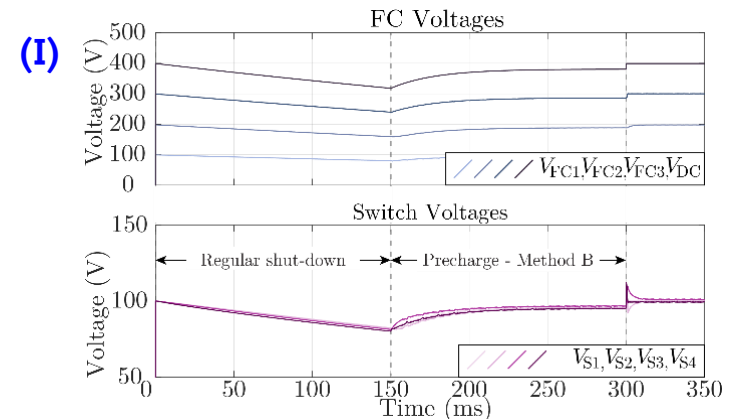


**(II)**
 
## Optimization of Little-Box 1.0


$\eta$ -Pareto Front  
TCM vs. Large Ripple PWM  
The Ideal Switch is Not Enough (!)  
Design Space Diversity





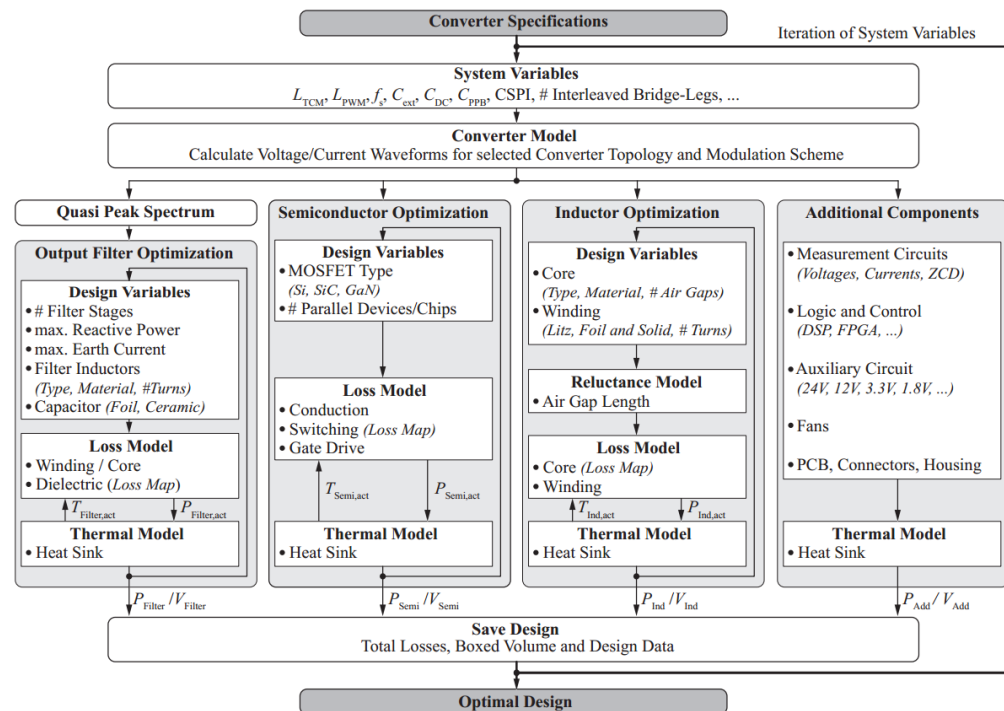
# Multi-Objective Optimization

- Detailed System Models - Power Buffer/Output Stage/EMI Filter
- Detailed Multi-Domain Component Models (incl. GaN & SiC)
- Consideration of Very Large # of Degrees of Freedom




 ■ Pareto Optimization Shows Trade-Off Between Power Density and Efficiency


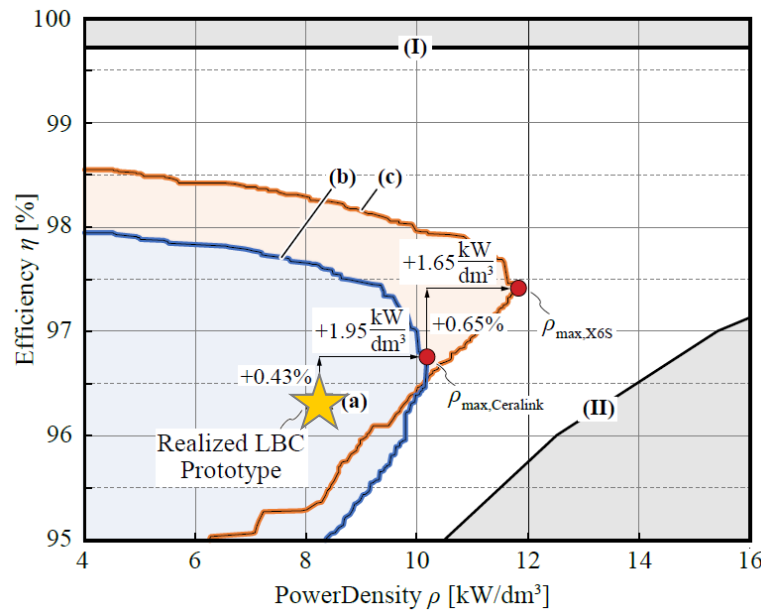
## Little Box 1.0 $\eta$ -Performance Limits


- Multi-Objective Optimization of Little-Box 1.0 (incl. CeraLink  $\rightarrow$  X6S)
- Absolute Performance Limits (I) - DSP/FPGA Power Consumption  
(II) - Heatsink Volume @  $(1-\eta)$



(a) ★ Realized Prototype


 
(b) CeraLink Power Pulsation Buffer  
(c) X6S Power Pulsation Buffer

- Further Performance Improvement for Triangular Current Mode (TCM)  $\rightarrow$  PWM



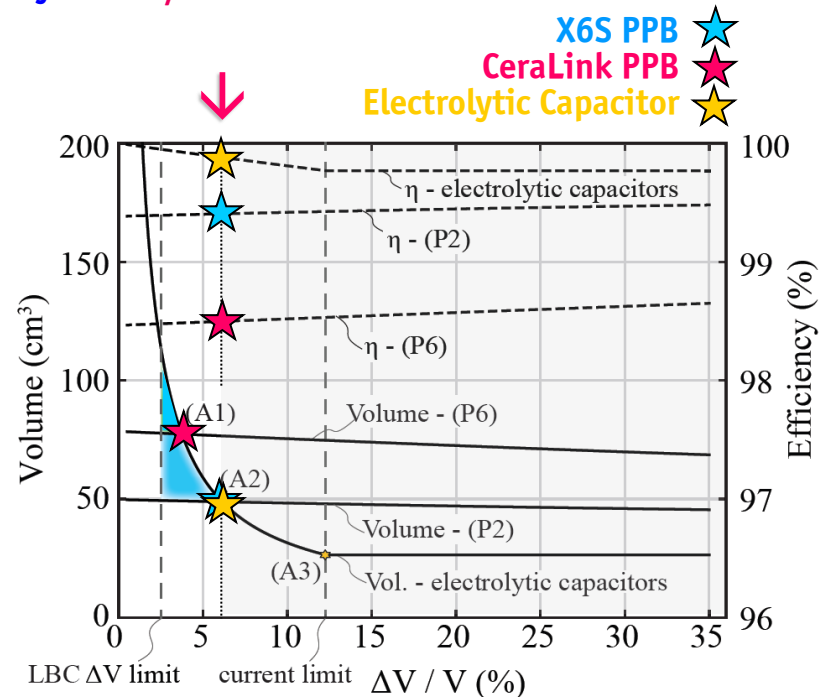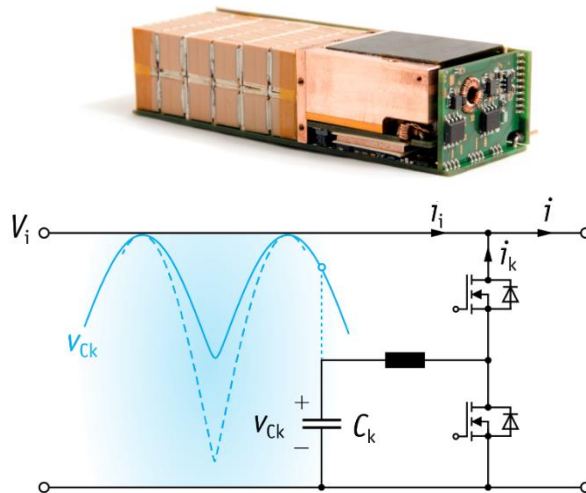
## Power Pulsation Buffer (PPB) vs. Electrolytic Capacitor (1)

- Lower Volume Comp. to Electrolytic Caps only for  $\Delta V/V < 6\%$
- No Efficiency Benefit of PPB (!)




 - Electrolytics Favorable for High Efficiency @ Moderate Power Density
- Electrolytics Show Lower Vol. & Lower Losses if Large  $\Delta V/V$  is Acceptable (e.g. for PFC Rectifiers)



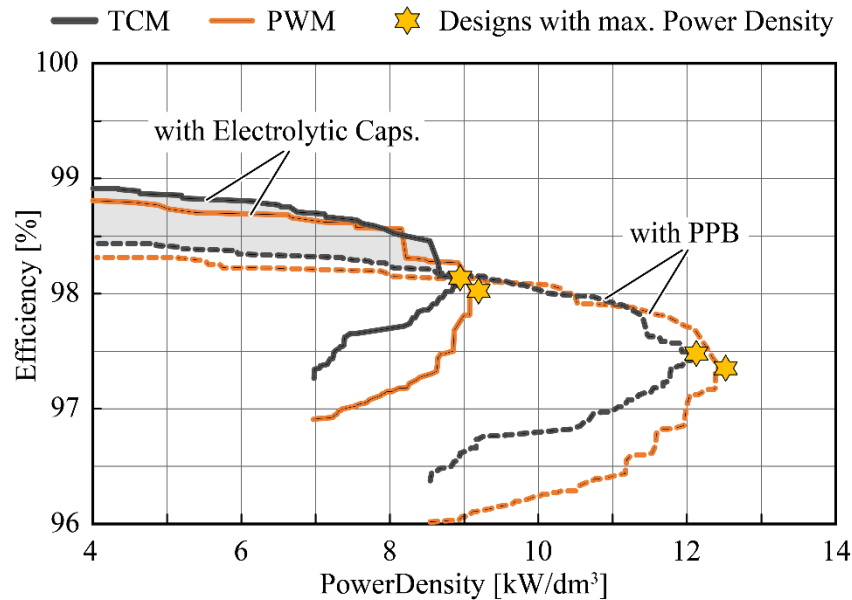
## Power Pulsation Buffer (PPB) vs. Electrolytic Capacitor (2)

- Analysis for Google Little Box Challenge Specification  $\Delta V/V < 3\%$
- Efficiency Benefit of PPB only for  $\rho > 9 \text{ kW/dm}^3$




 - Electrolytics Favorable for High Efficiency @ Moderate Power Density ( $\Delta\eta = +0.5\%$ )
- Electrolytics Show Lower Vol. & Lower Losses if Large  $\Delta V/V$  is Acceptable (e.g. for PFC Rectifiers)



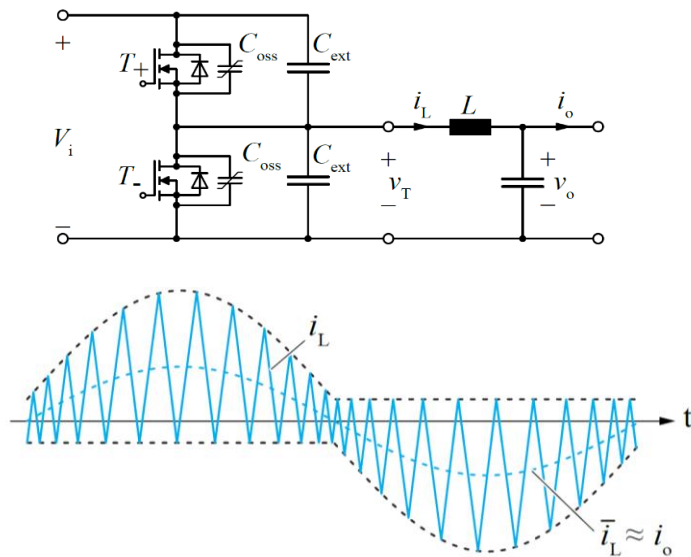
## Little Box 1.0 -- TCM $\rightarrow$ PWM

- Very High Sw. Frequency  $f_s$  of TCM Around Current Zero Crossings
- Efficiency Reduction due to Remaining TCM Sw. Losses & Gate Drive Losses Reduction
- Wide  $f_s$ -Variation Represents Adv. & Disadvantage for EMI Filter Design



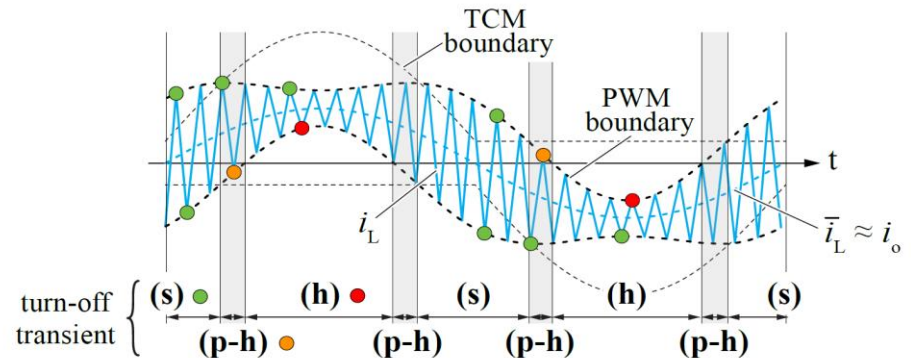(s) Soft-Switching (ZVS)  
(p-h) Partial Hard Switching  
(h) Hard-Switching






- PWM -- Const. Sw. Frequency & Lower Conduction Losses
- PWM @ Large Current Rippel -- ZVS in Wide Intervals



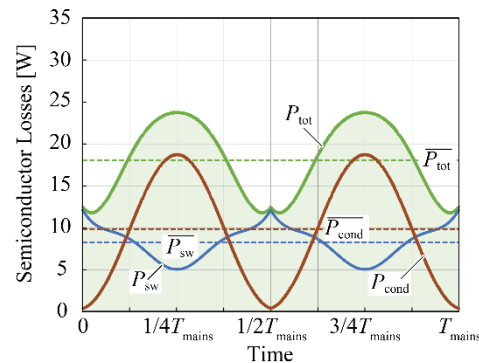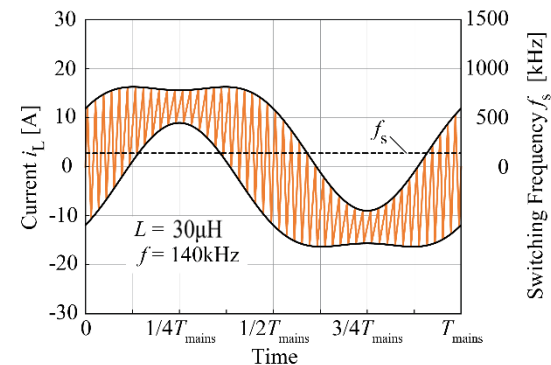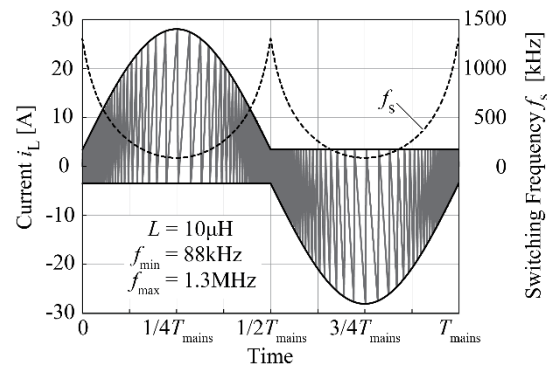
## Little Box 1.0 -- TCM $\rightarrow$ PWM

- Optimization for GaN GIT & No Interleaving
- Resulting Opt. Inductance of Output Inductor  $L=10\mu\text{H}$  (TCM),  $L=30\mu\text{H}$  (PWM)



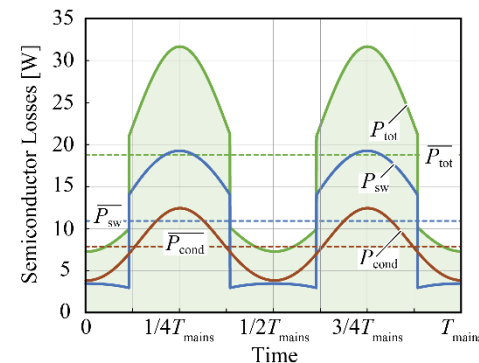
$\rho = 11.9\text{kW}/\text{dm}^3$   
 $\eta = 97.4\%$



$\rho = 12.5\text{kW}/\text{dm}^3$   
 $\eta = 97.4\%$



■ PWM vs. TCM -- Slightly Higher Max. Power Density @ Same Efficiency

The Ideal Switch is  
Not Enough (!) →

 
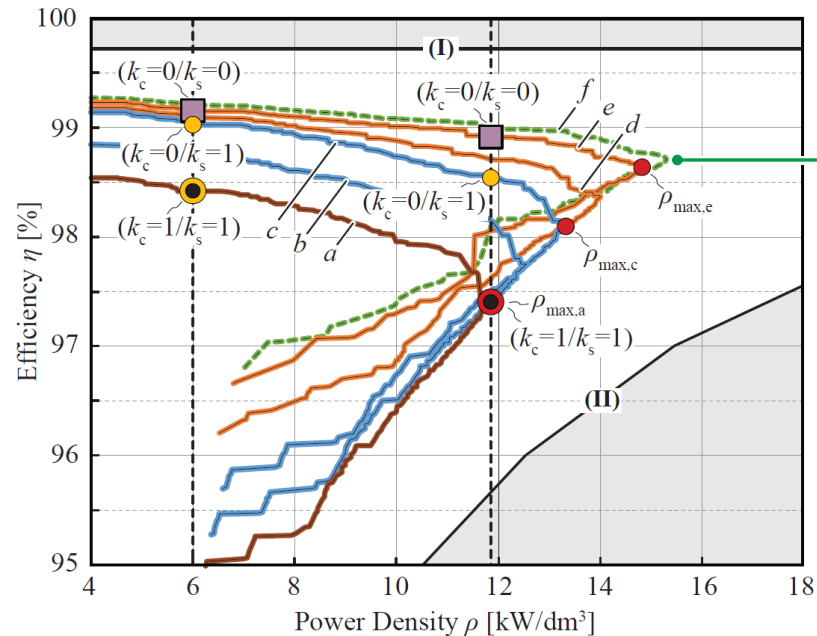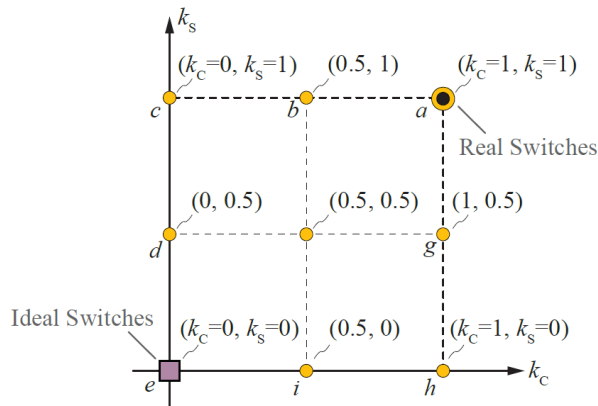
## Little Box 1.0 @ Ideal Switches


- Multi-Objective Optimization of Little-Box 1.0 (X6S Power Pulsation Buffer)
- Step-by-Step Idealization of the Power Transistors
- Ideal Switches:  $k_c = 0$  (Zero Cond. Losses);  $k_s = 0$  (Zero Sw. Losses)



Zero Output Cap.  
and Zero Gate  
Drive Losses



 
- Analysis of Improvement of Efficiency @ Given Power Density & Maximum Power Density





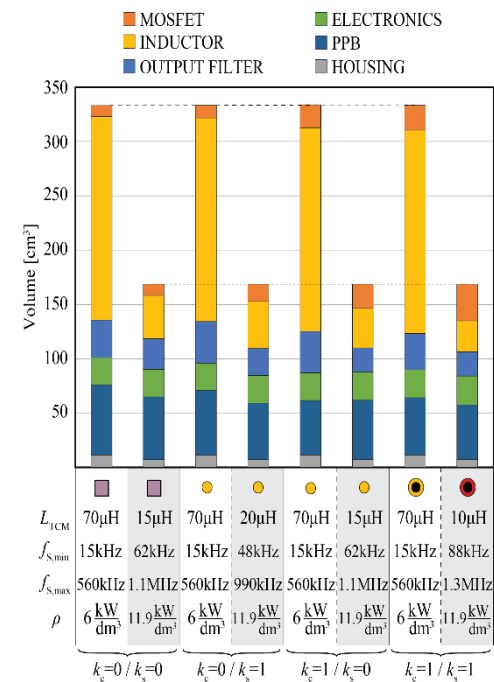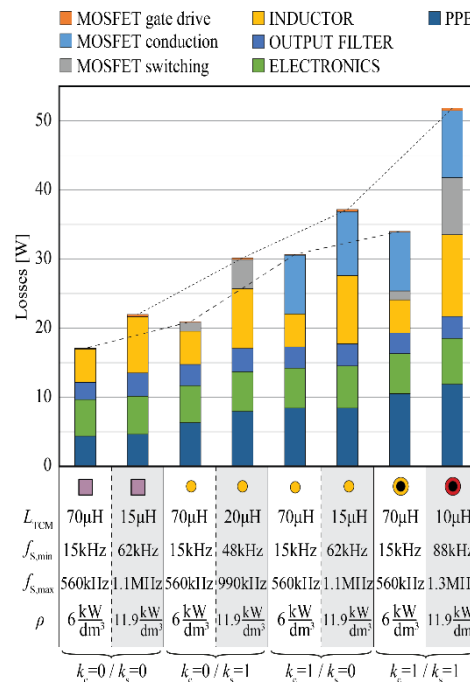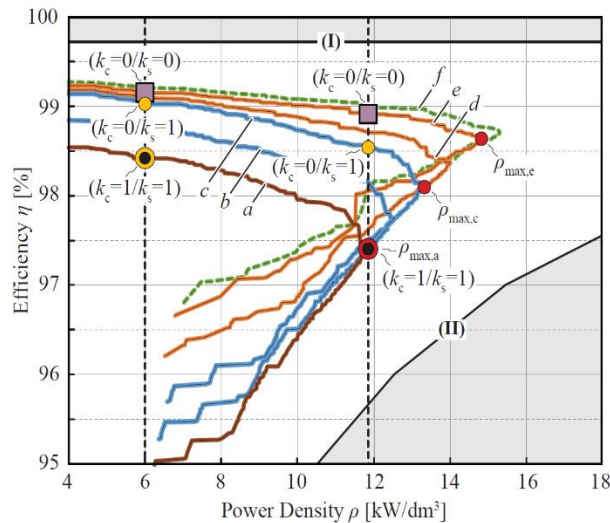
## Little Box 1.0 @ Ideal Switches -- TCM

- $\Delta\eta = +0.5\%$  @  $\rho = 6\text{kW/dm}^3$  - Main Benefit from Zero Conduction Losses ( $k_c=0$ )
- $\Delta\eta = +1.5\%$  @  $\rho = 12\text{kW/dm}^3$  - Add. Benefit from Zero Sw. Losses ( $k_s=k_c=0$ )






 - Minor Improvement of Max. Power Density -  $\rho = 12\text{kW/dm}^3 \rightarrow 15\text{kW/dm}^3$  (PPB Cap. & Inductors)
- Finite Remaining Volume & Losses  $\rightarrow$  The Ideal Switch is Not Enough (!)


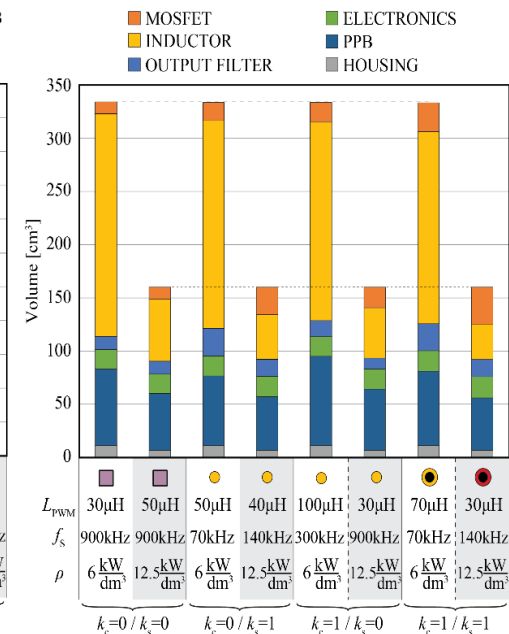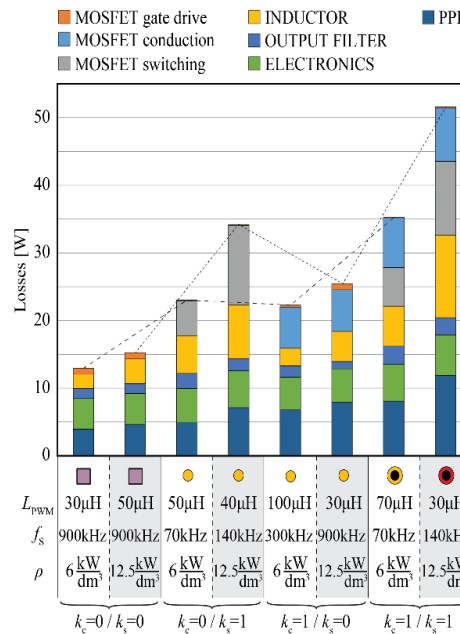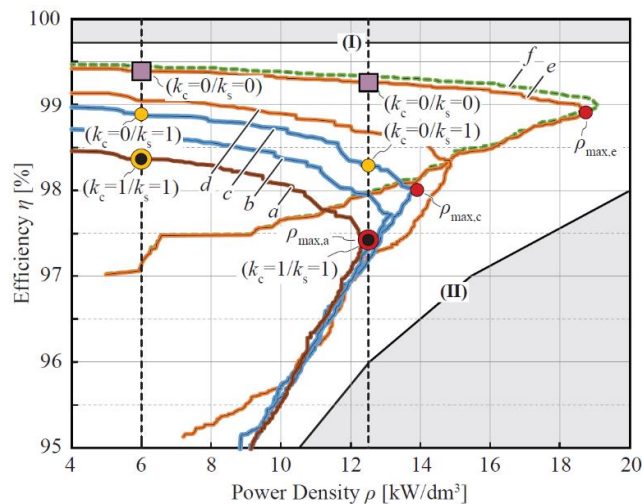
## Little Box 1.0 @ Ideal Switches -- PWM





- $\Delta\eta = +1.0\%$  @  $\rho = 6\text{ kW/dm}^3$  - Benefit from Zero Cond. & Zero Sw. Losses ( $k_s = k_c = 0$ )
- $\Delta\eta = +1.75\%$  @  $\rho = 12\text{ kW/dm}^3$  - Benefit from Zero Cond. & Zero Sw. Losses ( $k_s = k_c = 0$ )



- 50% Improvement of Max. Power Density -  $\rho = 12\text{ kW/dm}^3 \rightarrow 19\text{ kW/dm}^3$  (PPB & Inductors)
- Finite Remaining Volume & Losses  $\rightarrow$  The Ideal Switch is Not Enough (!)



# Little Box 1.0 @ Ideal Switches -- PWM

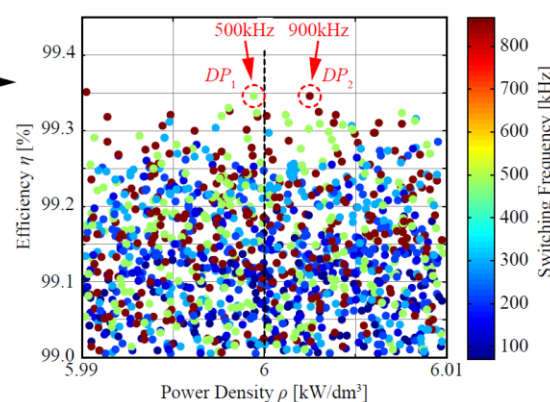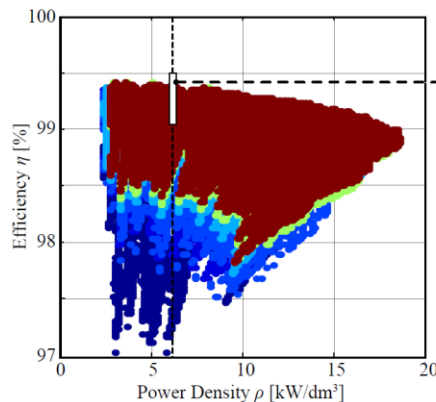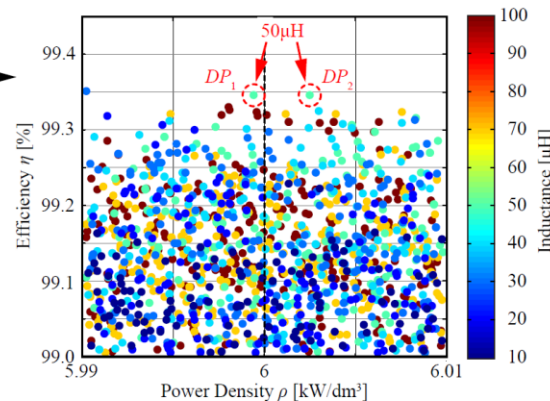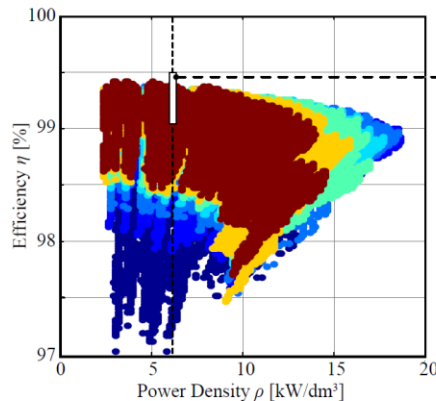

$\rho = 6 \text{ kW/dm}^3$   
 $\eta \approx 99.35\%$

$L = 50 \mu\text{H}$   
 $f_s = 500 \text{ kHz or } 900 \text{ kHz}$

- $L$  &  $f_s$  are Independent Variables (Dependent for TCM)
- Large Design Space Diversity (Mutual Compensation of HF and LF Loss Contributions)


## Little Box 2.0

DC/ | AC | Converter + Unfolder  
PWM vs. TCM incl. Interleaving  
 $\eta$ -Pareto Limits for Non-Ideal Switches



## Little Box 2.0 – New Converter Topology

- **Alternative Converter Topology** - DC/ | AC | - Buck Converter + Unfolder
- **60Hz-Unfolder** (Temporary PWM for Ensuring Continuous Current Control)
- **TCM** or PWM of DC/ | AC | - Buck-Converter

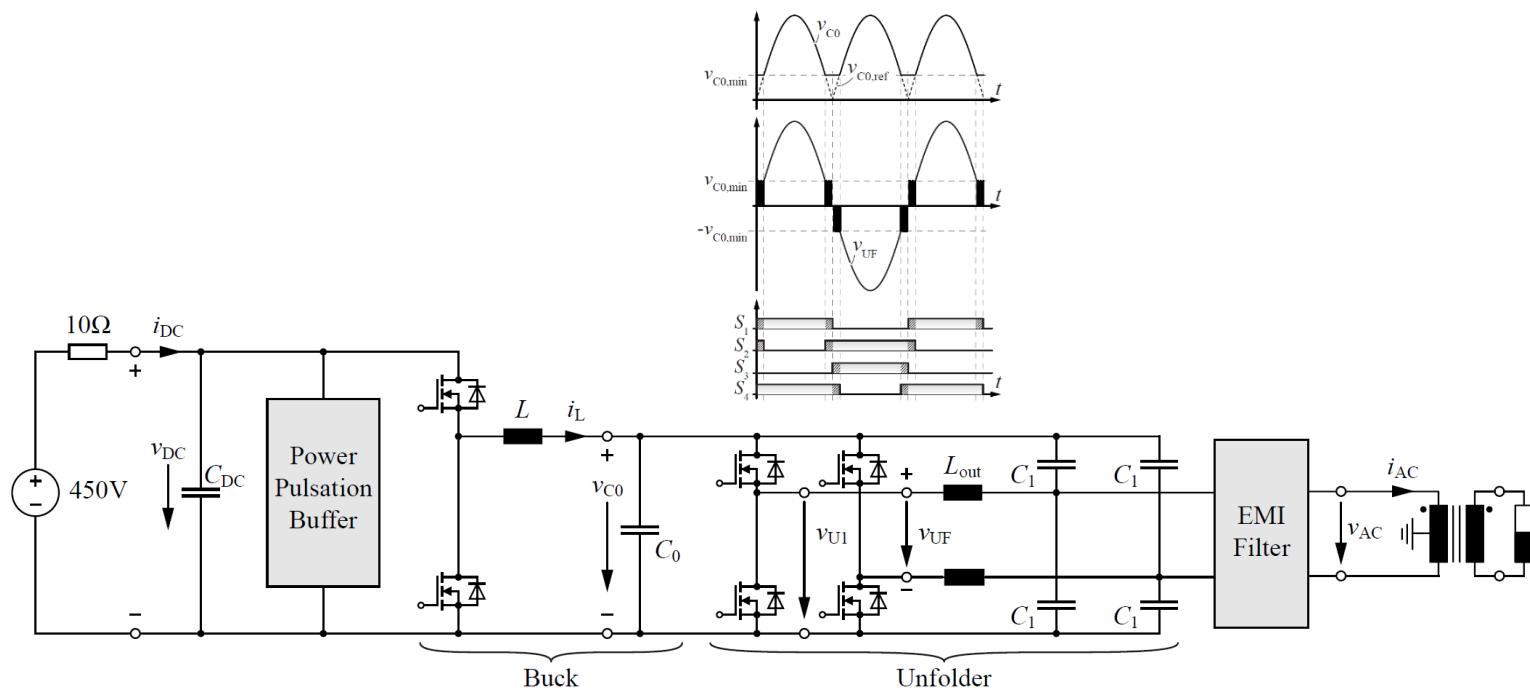


- **Full Optimization** of All Converter Options for **Real Switches** / X6S Power Pulsation Buffer



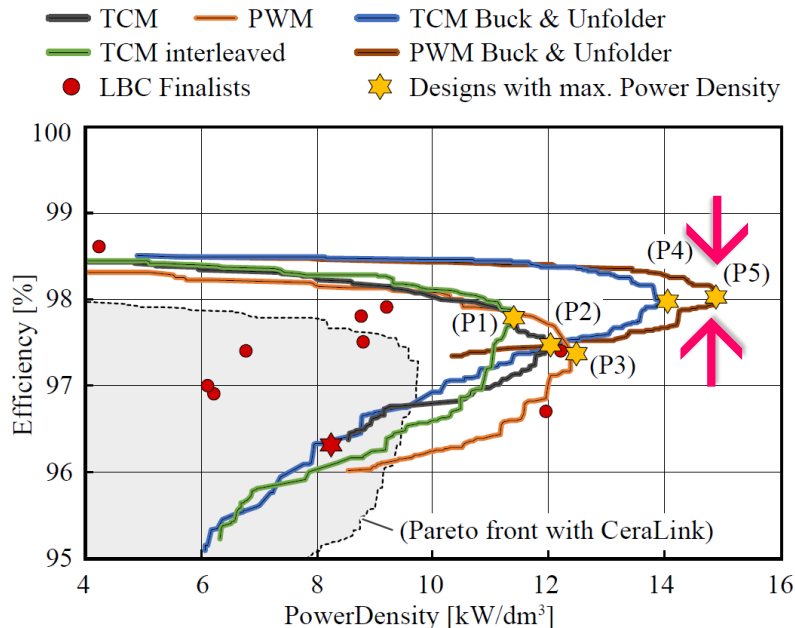
## Little Box 2.0 – Multi-Objective Optimization

- **DC/AC - Buck Converter + Unfolder & PWM Shows Best Performance**
- **Full-Bridge Employs 2 Switching Bridge Legs - Larger Volume & Losses**
- **Interleaving Not Advantageous – Lower Heatsink Vol. but Larger Total Vol. of Switches and Inductors**



-- 4D-Interleaving Considered for TCM


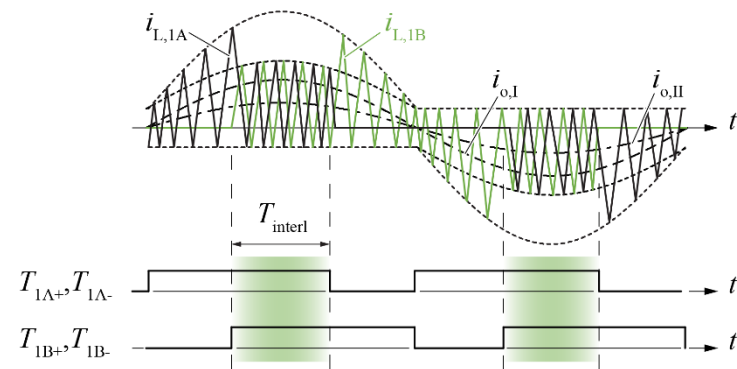


■  $\rho = 250\text{W/in}^3$  (15kW/dm<sup>3</sup>) @  $\eta = 98\%$  Efficiency Achievable for Full Optimization


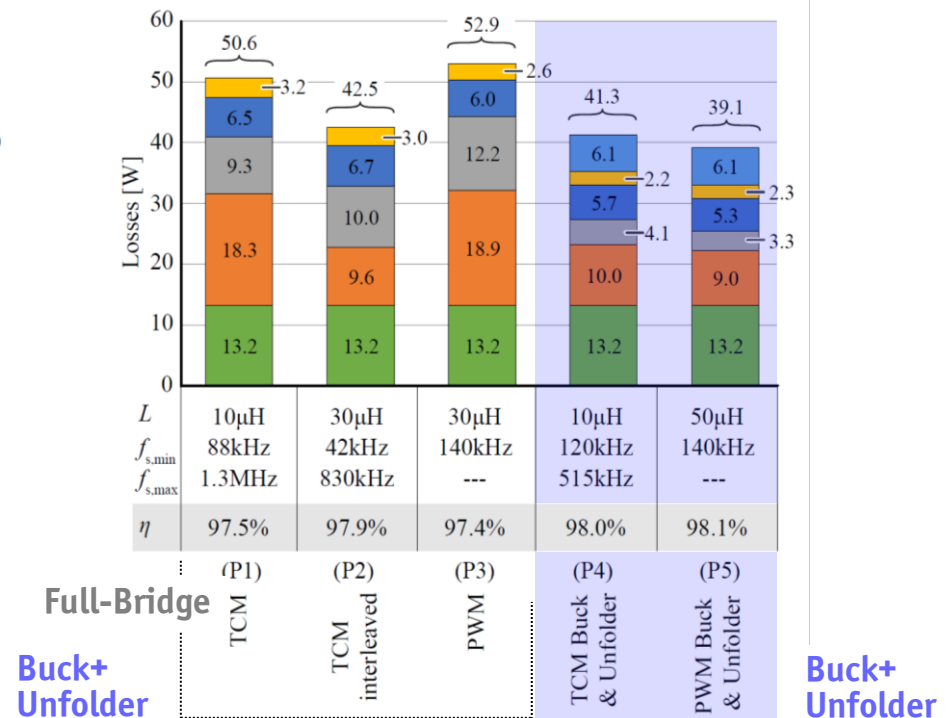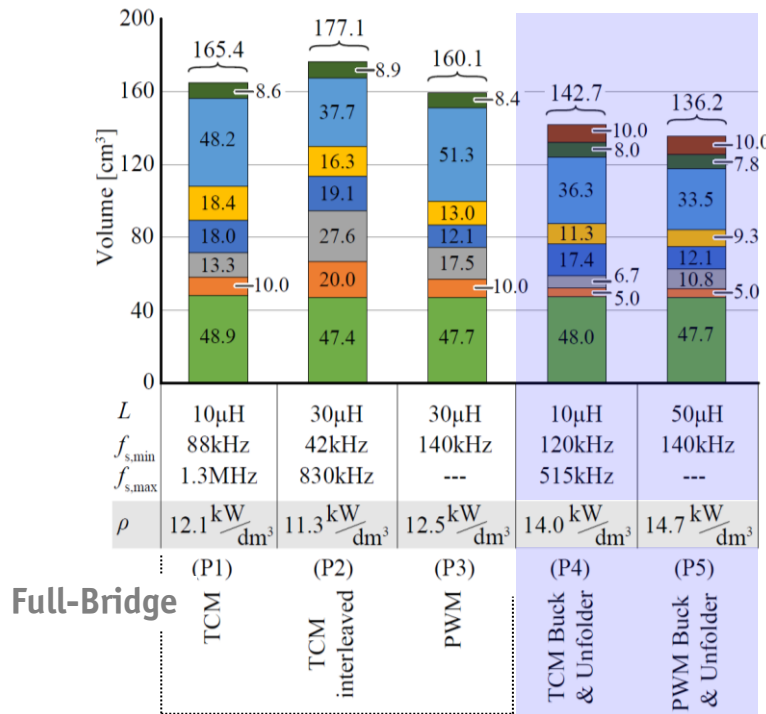
# Little Box 2.0 – Volume & Loss Distribution @ (P1...5)

■ Unfolder   
 ■ Housing   
 ■ Cooling   
 ■ Output filter   
 ■ Electronics   
 ■ Inductor   
 ■ MOSFETs   
 ■ PPB



- Volume Dominated by Heatsink & PPB (Power Pulsation Buffer)
- Losses for Buck+Unfolder Dominated by Switches & PPB

## ***Experimental Results***


*Control Block Diagram  
Output Voltage/Input Current Quality  
Efficiency*







## Little Box 2.0 – Control Structure


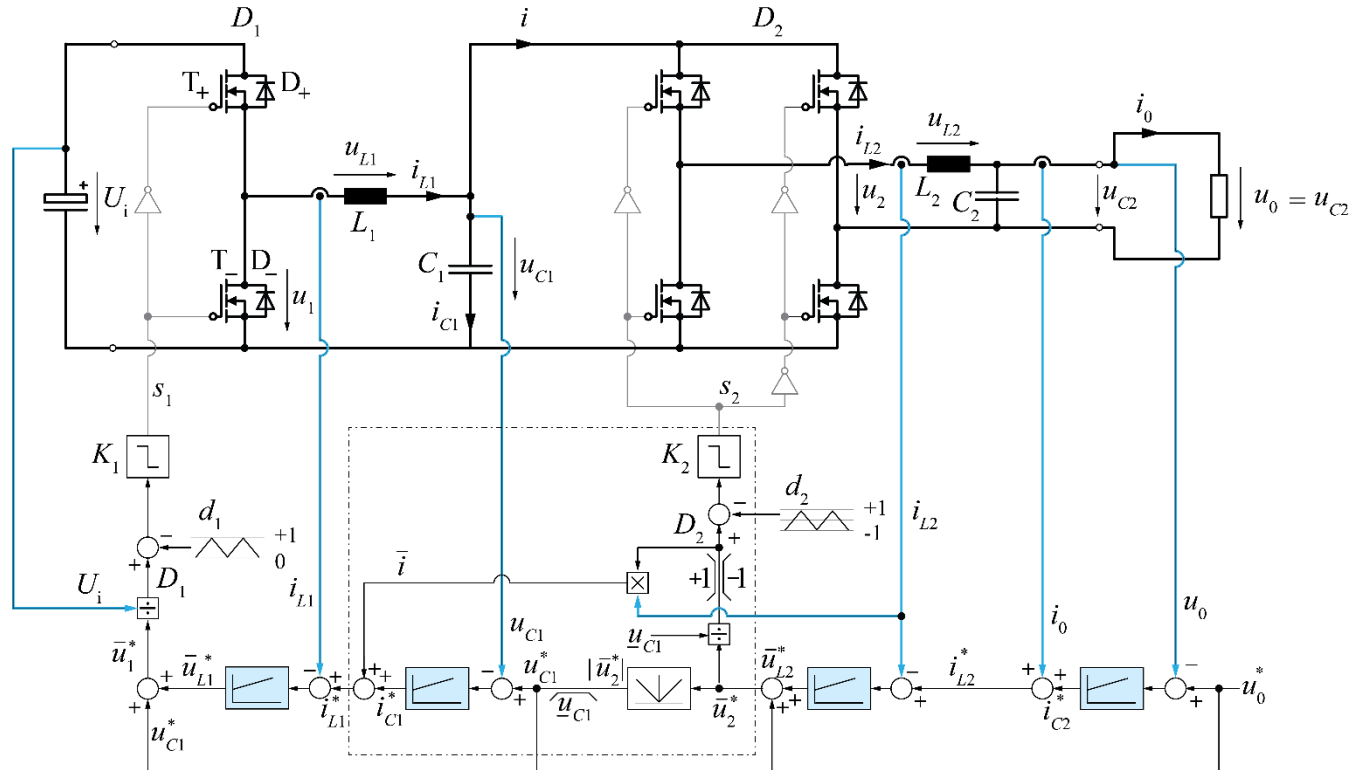


- Each Stage (Buck & Unfolder) Controlled with Cascaded Current and Voltage Loop
- Without Switching of Unfolder Control Like for Conventional Boost PFC Rectifier



# Analysis of DC/ | AC | -Buck Converter & Unfolder

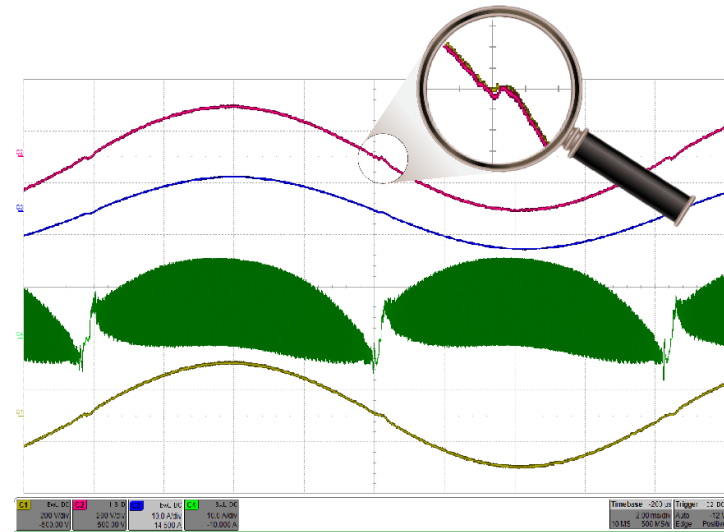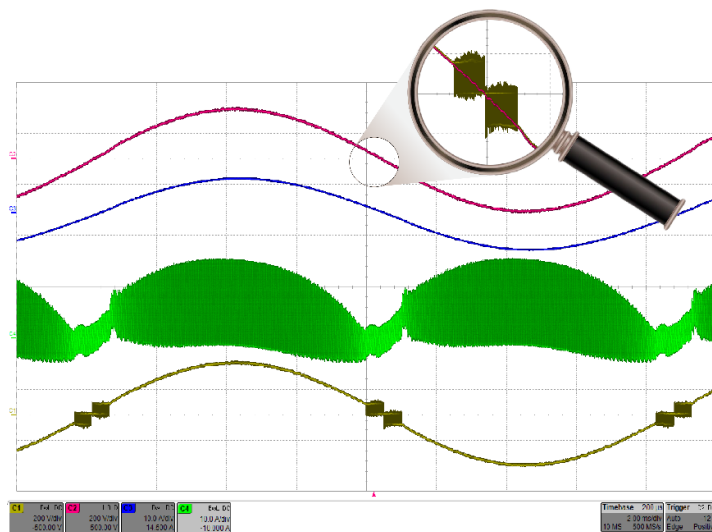- Voltage Zero Crossing Behavior With & Without Switching of Unfolder









- Output Voltage & Current Fully Controlled Around Voltage Zero Crossings
- Slope of Buck Conv. Outp. Current can be Decreased – Adv. for React. Loads (Step-Change of DC Current)



## Little Box 2.0 – Measured Waveforms

### • DC/|AC| Buck-Stage Output Voltage & Inductor Current

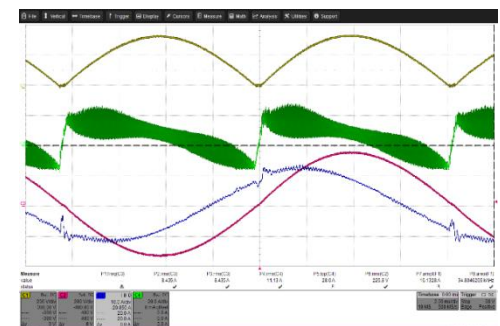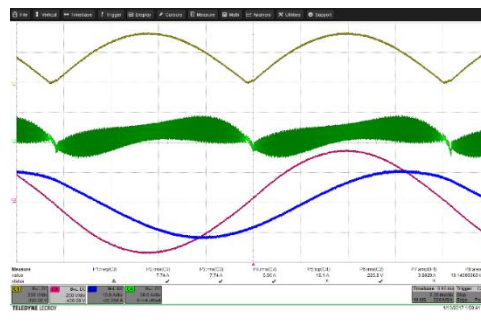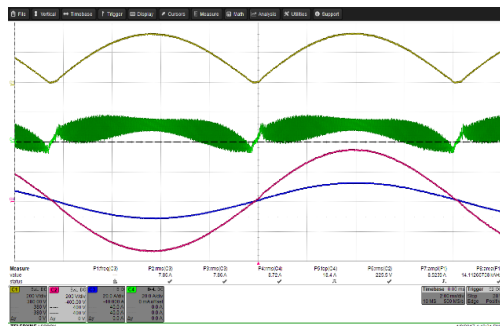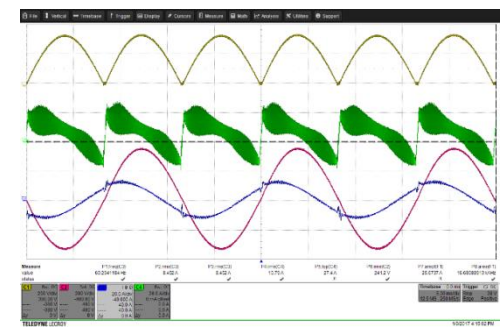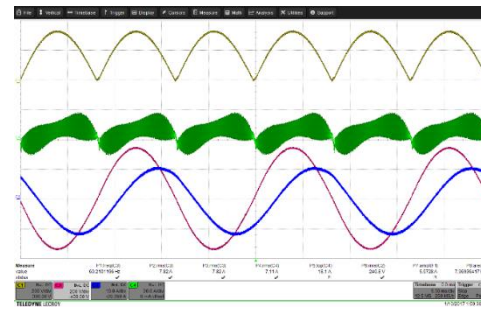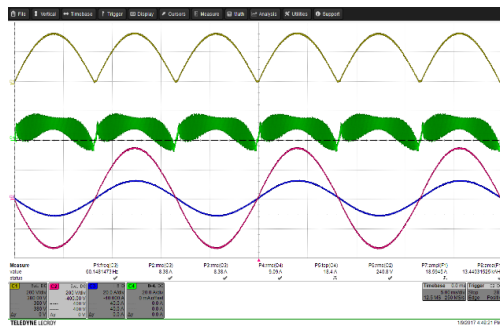

■ Resistive Load


■ Inductive Load

■ Capacitive Load



## Little Box 2.0 – Preliminary Efficiency Measurements

- Performance of First DC/ | AC | - Buck Converter + Unfolder Prototype
- PWM Operation
- Without Power Pulsation Buffer

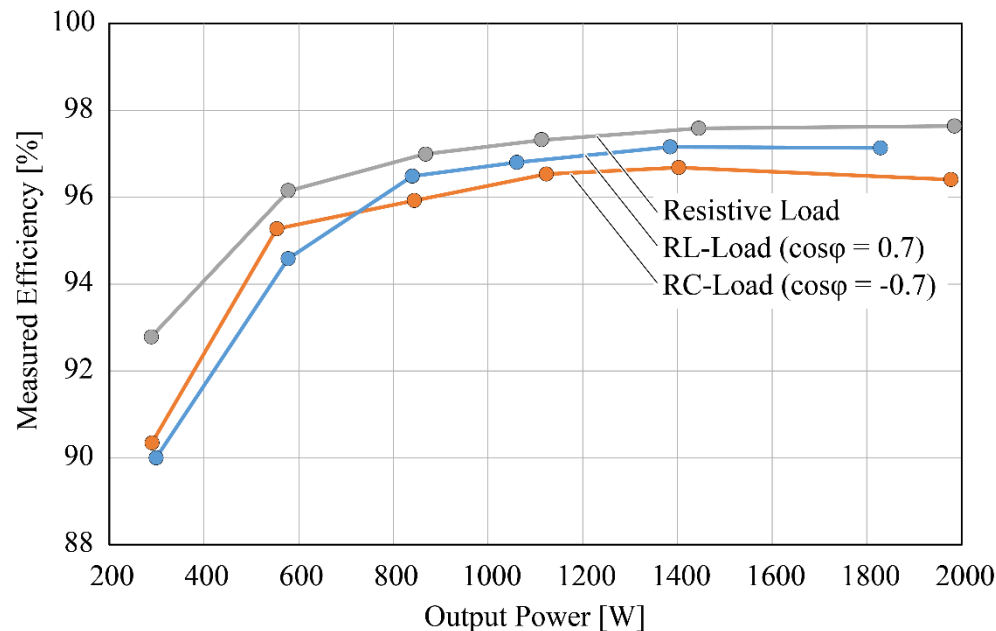

- 98% for Res. Load Achievable for Red. of Cond. Losses of PCB (Copper Cross Sect.) & Unfolder ( $R_{ds,on}$ )

## Little Box 3.0

5...10MHz Switching Frequency  
Performance of Low- $\mu$  HF Magnetic Materials  
Electrolytic Caps vs. Power Pulsation Buffer





## ► Magnetics Operation Frequency Limit (1)

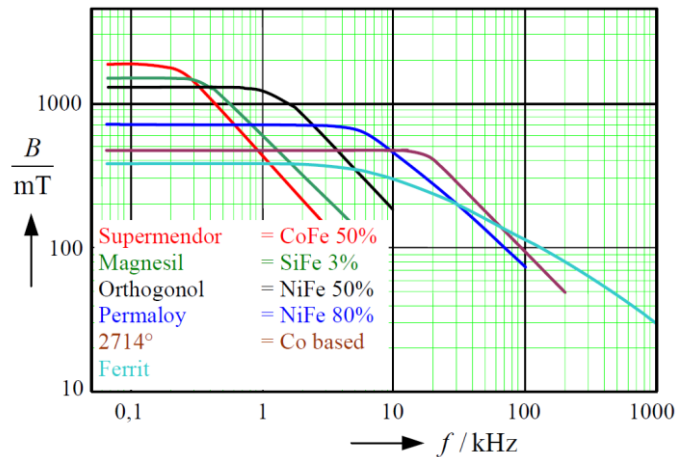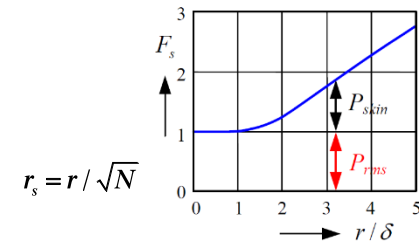
### • Serious Limitation of Operating Frequency by HF Losses

Source: Prof. Albach, 2011

- Core Losses (incr. @ High Frequ. & High Operating Temp.)
- Temp. Dependent Lifetime of the Core
- Skin-Effect Losses
- Proximity Effect Losses





■ Adm. Flux Density for given Loss Density

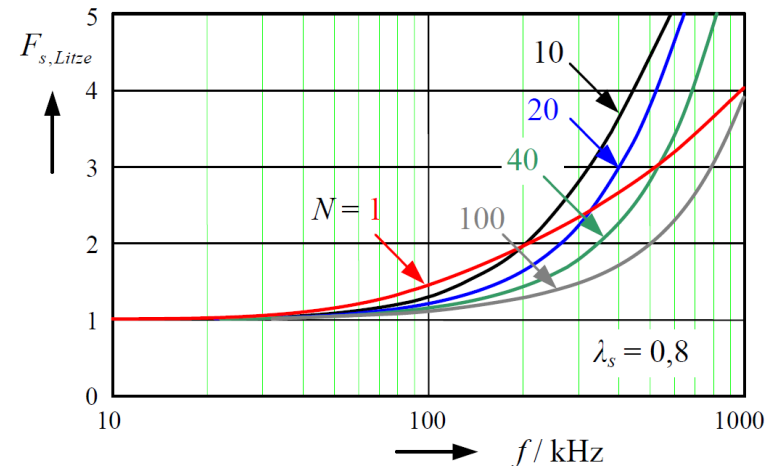
■ Skin-Factor  $F_s$  for Litz Wires with  $N$  Strands

## ► Magnetics Operating Frequency Limit (2)

- (Modified) “Core Material Perform. Factor”  $F_{0.75} = B_{pk} \cdot f^{0.75}$  Defined for Def. Core Loss
- Performance Factor prop. to VA Handling Capability – Min. Vol. @ Max. of  $F_{0.75}$
- Little Benefit of Increased  $f_s$  for Conv. Ferrites in 200kHz...2MHz
- Peak Performance of Low- $\mu$  HF Core Materials @ 5-10 MHz

Source:  
Hanson et al.  
ECCE 2015

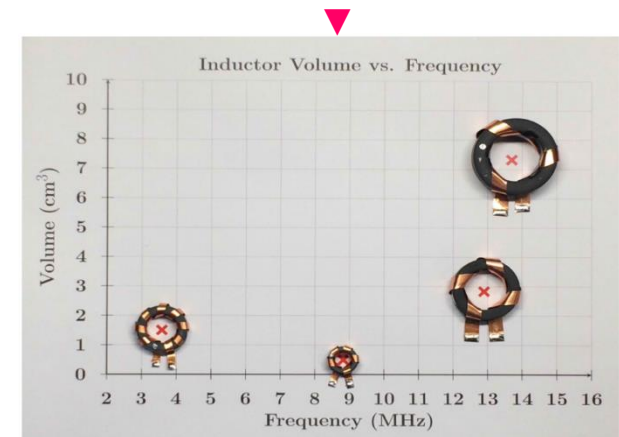
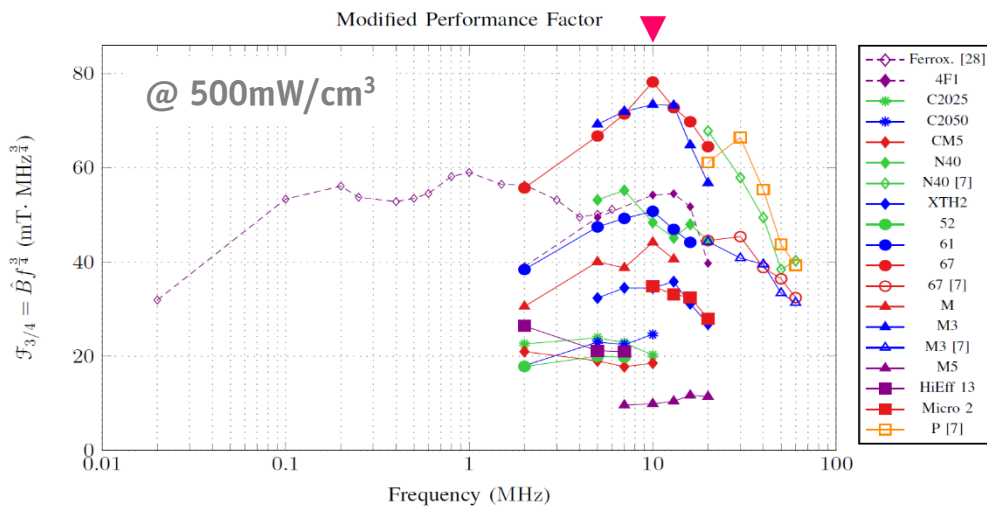


Fair-Rite 67 ( $\mu_r=40$ )  
All Inductors w.  $Q=200$

- $f_s$  in the MHz-Range Results in Very Low EMI Filter Volume

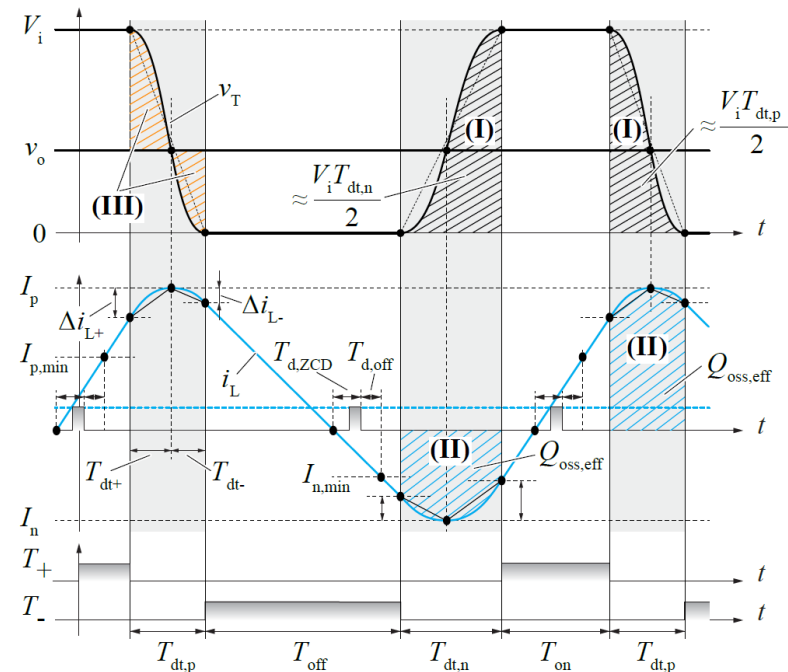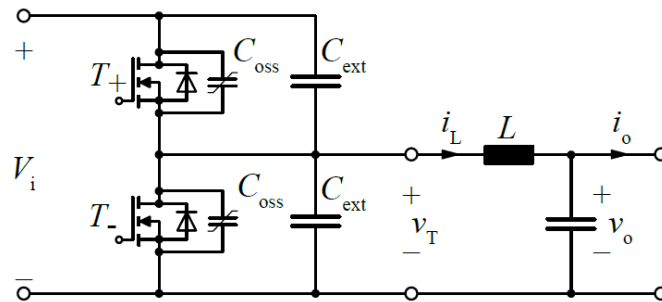
## ► TCM Digital Control / Timing Challenges @ $f_s > 1\text{MHz}$

- Dead Times Required for Res. Transition (ZVS)
- $i = 0$  Detection Time Delay
- Signal Isolator & Gate Drive Time Delays
- Rel. Large Cond. Losses @ Low Output Current



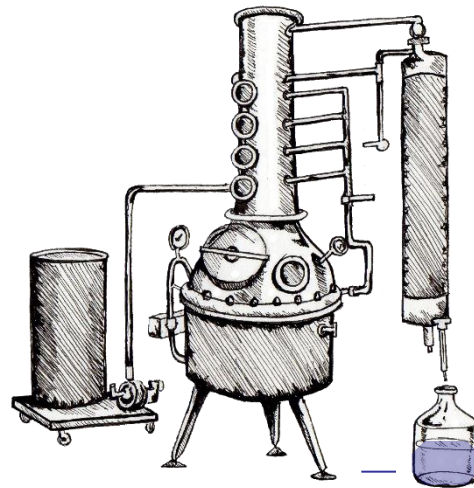- New High Speed / Low-Volume / Low-Loss  $i = 0$  Detection Concepts Required
- Integrated Gate Drive w. (Hysteresis) Current Control Functionality Required





Source: whiskeybehavior.info

## Overall Summary



## Performance Limits / Future Requirements

- 220...250W/in<sup>3</sup> for Two-Level Bridge Leg + Unfolder
- 250...300W/in<sup>3</sup> for Highly Integrated Multi-Level Approach
- Isol. Distance Requirements Difficult to Fulfill
- Fulfilling Ind. Overvoltage Requirements would Signific. Reduce Power Density
- Low Frequency (20kHz...120kHz) SiC vs. HF (200kHz...1.2MHz) GaN
- Multi-Cell Concepts for LV Si (GaN) vs. Two-Level SiC (GaN)
- New Integr. Control Circuits and  $i=0$  Detection for Sw. Frequency >1MHz
- Integrated Gate Drivers & Switching Cells
- High Frequency Low Loss Magnetic Materials
- High Bandwidth Low-Volume Current Sensors
- Low Loss Ceramic Capacitors Tolerating Large AC Ripple
- Passives w. Integr. Heat Management and Sensors
- 3D Packaging
- New U-I-Probes Required for Ultra-Compact Conv. R&D
- Spec. Testing Devices Equipped with Integr. Measurement Functions
- Convergence of Sim. & Measur. Tools → Next Gen. Oscilloscope
- New Multi-Obj. Multi-Domain Simulation/Optim. Tools

## References

ETH Zurich  
Other Finalists  
Non-Finalists  
General

## ► Publications of ETH Zurich

**D. Neumayr, D. Bortis, E. Hatipoglu, J. W. Kolar, G. Deboy**, *New Efficiency Optimal Frequency Modulation (OFM) for High Power Density DC/AC Converter Systems*, to be published in Proc. of the International Future Energy Electronics Conference (IFEEC-ECCE Asia), Kaohsiung, Taiwan, June 3-7, 2017.

**D. Neumayr, M. Guacci, D. Bortis, J. W. Kolar**, *Novel Temperature-Gradient based Calorimetric Measurement Principle to Obtain Soft-Switching Benchmark of GaN and SiC Power Devices*, Proceedings of the 29<sup>th</sup> IEEE International Symposium on Power Semiconductor Devices and ICs (ISPSD), Sapporo, Japan, May 28 - June 1, 2017.

**D. Rothmund, D. Bortis, J. Huber, D. Biadene, J. W. Kolar**, *10kV SiC-Based Bidirectional Soft-Switching Single-Phase AC/DC Converter for Medium-Voltage Solid-State Transformer Applications*, Proceedings of the 8<sup>th</sup> International Symposium on Power Electronics for Distributed Generation Systems (PEDG), Florianopolis, Brazil, April 17-20, 2017.

**M. Guacci, D. Neumayr, D. Bortis, J. W. Kolar, G. Deboy**, *Analysis and Design of a Multi-Tapped High-Frequency Auto-Transformer Based Inverter System*, Proceedings of the 17<sup>th</sup> IEEE Workshop on Control and Modeling for Power Electronics (COMPEL), Trondheim, Norway, June 27-30, 2016.

**D. Neumayr, D. Bortis, J. W. Kolar**, *Comprehensive Large-Signal Performance Analysis of Ceramic Capacitors for Power Pulsation Buffers*, Proceedings of the 17<sup>th</sup> IEEE Workshop on Control and Modeling for Power Electronics (COMPEL), Trondheim, Norway, June 27-30, 2016.

**D. Bortis, D. Neumayr, J. W. Kolar**,  *$\eta$ -Pareto Optimization and Comparative Evaluation of Inverter Concepts considered for the GOOGLE Little Box Challenge*, Proceedings of the 17<sup>th</sup> IEEE Workshop on Control and Modeling for Power Electronics (COMPEL), Trondheim, Norway, June 27-30, 2016.

**J. W. Kolar, D. Bortis, D. Neumayr**, *The Ideal Switch is Not Enough*, Proceedings of the 28<sup>th</sup> IEEE International Symposium on Power Semiconductor Devices and ICs (ISPSD), Prague, Czech Republic, June 12-16, 2016.

**D. Bortis, O. Knecht, D. Neumayr, J. W. Kolar**, *Comprehensive Evaluation of GaN GIT in Low- and High-Frequency Bridge Leg Applications*, Proceedings of the 8<sup>th</sup> International Power Electronics and Motion Control Conference (IPEMC-ECCE Asia), Hefei, China, May 22-25, 2016.

**D. Neumayr, D. Bortis, J. W. Kolar**, *Ultra-Compact Power Pulsation Buffer for Single-Phase DC/AC Converter Systems*, Proceedings of the 8<sup>th</sup> International Power Electronics and Motion Control Conference (IPEMC-ECCE Asia), Hefei, China, May 22-25, 2016.

## ► Publications of Other Finalists

**F. Frebel, O. Bomboir, P. Bleus, D. Rixhon**, *Transformer-less 2kW Non-Isolated 400VDC/230VAC Single-Stage Micro-Inverter*, Proc. of the IEEE Intern. Telecommunications Energy Conference (INTELEC), 2016.

**R. Ghosh, M. Srikanth, D. Klikic, M. Wang, R. Mitova**, *Novel Active Ripple Filtering Schemes used in the Little Box Inverter*, to be published in Proc. of the Intern. Conf. on Power Conv. and Intelligent Motion (PCIM Europe), 2017.

**l. Zhang, R. Born, X. Zhao, J.S. Lai**, *A High Efficiency Inverter Design for Google Little Box Challenge*, Proc. of the IEEE Workshop on Wide Bandgap Power Devices and Applications (WiPDA), 2015.

**C. Zhao, B. Trento, L. Jiang, E. A. Jones, B. Liu, Z. Zhang, D. Costinett, F. Wang, L. M. Tolbert, J. F. Jansen, R. Kress, R. Langley**, *Design and Implementation of GaN-Based 100-kHz 102-W/in<sup>3</sup> Single-Phase Inverter*, IEEE Journal of Emerging and Selected Topics in Power Electronics, vol. 4, no. 3, pp. 824–840.

**S. Qin, Y. Lei, C. Barth, W. C. Liu, R. C. N. Pilawa-Podgurski**, *A High Power Density Series-Stacked Energy Buffer for Power Pulsation Decoupling in Single-Phase Converters*, to be published in the IEEE Transactions on Power Electronics.

**T. Menrath, S. Matlok, S. Endres, S. Zelter, B. Eckardt**, *Mechatronic Design of 2kW SiC DC/AC Converter with 200W/in<sup>3</sup>*, to be published in Proc. of the Intern. Conf. on Power Conv. and Intelligent Motion (PCIM Europe), 2017.

## ► General Publications

**Solaredge Technologies Ltd.**, *Multi-level Inverter*, European Patent Application EP 2779410A2 (Inventor: I. Yoscovitch), filed March 14, 2014, published Sept. 17, 2014.

**C. P. Henze, H. C. Martin, D. W. Parsley**, *Zero-voltage Switching in High Frequency Power Converters using Pulse Width Modulation*, Proc. of the IEEE Applied Power Electronics Conference (APEC), 1988, pp. 33-40.

**R. W. Erickson, A. P. Rogers**, *A Microinverter for Building-Integrated Photovoltaics*, Proc. of the IEEE Applied Power Electronics Conference (APEC), 2009, pp. 911-917.

**M. Pahlevaninezhad, P. Jain**, *Zero Voltage Switching interleaved Boost AC/DC Converter*, US Patent US 8723487B2 (May 13, 2014), filed March 9, 2012.

**J. E. Knowles**, *The Origin of Increase in Magnetic Losses Induced by Machining Ferrites*, IEEE Trans. on Magnetics, vol. 11, pp. 1–5, 1975.

## Biographies of the Authors

kolar@lem.ee.ethz.ch  
neumayr@lem.ee.ethz.ch  
bortis@lem.ee.ethz.ch



**Johann W. Kolar** (F'10) received his Ph.D. degree (summa cum laude) from the Vienna University of Technology, Austria. He is currently a Full Professor and the Head of the Power Electronic Systems Laboratory at the Swiss Federal Institute of Technology (ETH) Zurich. He has proposed numerous novel PWM converter topologies, and modulation and control concepts and has supervised over 60 Ph.D. students. He has published over 750 scientific papers in international journals and conference proceedings, 3 book chapters, and has filed more than 140 patents. He has presented over 20 educational seminars at leading international conferences, has served as IEEE PELS Distinguished Lecturer from 2012 through 2016, and has received 25 IEEE Transactions and Conference Prize Paper Awards, the 2014 IEEE Power Electronics Society R. David Middlebrook Achievement Award, the 2016 IEEE William E. Newell Power Electronics Award, the 2016 IEEE PEMC Council Award, and the ETH Zurich Golden Owl Award for excellence in teaching. He has initiated and/or is the founder of 4 ETH Spin-off companies. The focus of his current research is on ultra-compact and ultra-efficient SiC and GaN converter systems, wireless power transfer, Solid-State Transformers, Power Supplies on Chip, as well as ultra-high speed and ultra-light weight drives, bearingless motors, and energy harvesting.



**Dominik Neumayr** (SM10) started his academic education at the University of Applied Sciences (FH) for Automation Engineering in Wels and received the Dipl.-Ing. (FH) degree in 2008. He was with the Center for Advanced Power Systems (CAPS) in Tallahassee/Florida working on Power/Controller Hardware-in-the-Loop simulations and control systems design for AC/DC/AC PEBB based converter systems from ABB. He continued his academic education at the Swiss Federal Institute of Technology in Zurich (ETH Zurich) and received the M.Sc. degrees in electrical engineering and information technology in 2015. Since spring 2015 he is a PhD student at the Power Electronic Systems (PES) Laboratory, ETH Zurich. His current research focuses on ultra-high power density converter systems.



**Dominik Bortis** (M'08) received the M.Sc. degree in electrical engineering and the Ph.D. degree from the Swiss Federal Institute of Technology (ETH) Zurich, Switzerland, in 2005 and 2008, respectively. In May 2005, he joined the Power Electronic Systems Laboratory (PES), ETH Zurich, as a Ph.D. student. From 2008 to 2011, he has been a Postdoctoral Fellow and from 2011 to 2016 a Research Associate with PES, co-supervising Ph.D. students and leading industry research projects. Since January 2016 Dr. Bortis is heading the newly established research group Advanced Mechatronic Systems at PES.

**Thank You !**

