



4.8 MHz GaN Class-D Power Amplifier and Measurement Systems for Next Generation Power Electronics

Pascal Niklaus and Johann W. Kolar

Postdoctoral Researcher

Power Electronic Systems Laboratory

ETH Zurich

niklaus@lem.ee.ethz.ch

Infineon TechTalk

03.03.2023

Next Generation Power Electronics (NGPE)

- Transition to a **Net Zero Emissions Society** relies on highly efficient power conversion/processing technologies
- Lower **functional volume** and **faster dynamics** required

▼ High-Speed Drive



▼ PV/Wind Inverter



▼ SST



▼ EV Drivetrain



▼ EV Charger



→ Realized with **increased switching frequencies**

Outline


- Challenges resulting from increased switching frequencies up to the multi-MHz range



- ▶ Converter Design and Testing



 - ▶ Measurement Technology
 - ▶ I-Measurement
 - ▶ Isolated V-Measurement




100 kHz Large-Signal Bandwidth GaN-Based 10 kVA Class-D Power Amplifier

Very High Power Density Converter Systems with Multi-MHz Switching Frequencies

UHBWPA: Applications + Specifications



 - P-HIL → Three-phase Ultra-High Bandwidth Power Amplifier (UHBWPA)
- Focus on single-phase module of DC/AC stage



▼ UHBWPA Specifications



Parameter		Value
Peak Output Voltage per Phase	$V_{out,pk}$	0 ... 350 V
Output Frequency	f_{out}	dc ... 100 kHz
Output Power per Phase	S_{out}	0 ... 10 kVA
DC Link Voltage	V_{dc}	800 V
Effective Switching Frequency	$f_{sw,eff}$	4.8 MHz
System Efficiency (Nom. Op. Pt.)	η	95 %

→ Fast dynamics (100kHz) and high efficiency (95%) at nominal power of 10kW per phase



UHBWPA: Linear vs. Switch-Mode



▼ Linear UHBWPA

  


▼ Switch-Mode UHBWPA

  



- **Switch-mode** for higher efficiency → 100kHz BW needs **≈5MHz sw. frequency** (1-stage filter)
- Advanced topology to **increase f_{sw}** with **minimal losses** and to **reduce ripple** with **minimal volume**

Advanced Circuit Topology


 
- Series & Parallel interleaving
- Multi-level switch-node voltage + very high effective switching frequency



$$\Delta v_{sw} = \frac{V_{dc}}{M-1}$$

  

$$\Delta v_{sw,eff} = \frac{V_{dc}}{N}$$

  

$$\Delta v_{sw,eff} = V_{dc} / ((M-1) \cdot N)$$

$$f_{sw,eff} = (M-1) \cdot N \cdot f_{sw}$$

→ Find best combination of series (M) and parallel (N) interleaving

Output Filter Design


- Nominal operating point
 - 230 V_{rms}, 10 kW, 100 kHz
- Fixed $f_{sw,eff} = 4.8 \text{ MHz}$
- Filter design space
 - Max. BW $\rightarrow$ min. f_c
 - 1% max. output volt. ripple
 - 15% max. ind. volt. drop
 - 30% max. cap. current

★ $L_{filt} = 1.26 \mu\text{H}$, $C_{filt} = 99 \text{ nF}$



- $\rightarrow L_{br} = N \cdot L_{filt} = 3.8 \mu\text{H}$

▽ $L_{filt} = 0.6 \mu\text{H}$, $C_{filt} = 99 \text{ nF}$

- Volume minimal filter

 






$$f_{sw,eff} = 4.8 \text{ MHz}$$

  

$\rightarrow$ Find **best combination** of series (M) and parallel (N) interleaving with **given output filter** and $f_{sw,eff}$

Optimal Design Selection

     
- Filter design space
 - $L_{\text{filt}} = 1.26 \mu\text{H}$, $C_{\text{filt}} = 99 \text{ nF}$
- Nominal operating point
 - $230 V_{\text{rms}}$, 10 kW , 100 kHz
- 70 m Ω / 600 V GaN HEMT (IGOT60R070D1)




→ Selection of $M=3 / N=3$ considering efficiency / filter volume / design complexity trade-off

Hardware Demonstrator – CAD

 
- $M=3 / N=3$ hardware single-phase 10kW demonstrator
- $f_{\text{sw,eff}} = 4.8\text{MHz}$ (800kHz per device)
- Modular layout of $N=3$ branches



Power PCB

 

Measurement PCB

 


Control PCB

→ Three vertically stacked PCBs to maximize power density and signal integrity

Power PCB – Power Commutation Loop

 
- Top-side cooled power semiconductors placed on bottom-side
- Minimum power commutation loop → Coplanar arrangement on two adjacent layers
→ Exemplary shown for T_{8H3} and T_{8L3}



→ Power loop inductance $< 2.2 \text{ nH}$ (outer sw. cell) / $< 1.5 \text{ nH}$ (inner sw. cell) (device: $L_{DS,int} \approx 3.5 \text{ nH}$)

Power PCB – Gate Commutation Loop

 - Gate-Drivers placed on **top-side** (adjacent to each switch)
- Minimum turn-on/off commutation loop → **Coplanar** arrangement on two adjacent layers
→ Exemplary shown for T_{4L3}




→ Gate loop inductance $\approx 3\text{nH}$ (on-path) / $\approx 4\text{nH}$ (off-path) (device: $L_{GS,int} \approx 7\text{nH}$ (!))


→ No parasitic turn-on

Hardware Demonstrator – CAD

 
- $M=3 / N=3$ hardware single-phase 10kW demonstrator
- $f_{\text{sw,eff}} = 4.8\text{MHz}$ (800kHz per device)
- Modular layout of $N=3$ branches



Power PCB

 

Measurement PCB

 


Control PCB

→ Three vertically stacked PCBs to maximize power density and signal integrity


Measurement PCB – Isolated GD Supplies

 - Individual isolated GD supply for each switch



Series resonance
 $f_{res} = \text{ca. } 400 \text{ kHz}$

 
Ultra-low coupling-C
 $C_{ps} = \text{ca. } 1 \text{ pF}$




→ No overlap between primary and secondary + Low-C transformer → High dv/dt immunity

Hardware Demonstrator – CAD

 
- $M=3 / N=3$ hardware single-phase 10kW demonstrator
- $f_{\text{sw,eff}} = 4.8\text{MHz}$ (800kHz per device)
- Modular layout of $N=3$ branches



Power PCB

 

Measurement PCB



 


Control PCB

→ Three vertically stacked PCBs to maximize power density and signal integrity

Hardware Demonstrator

  
 
- $M=3 / N=3$ hardware single-phase 10kW demonstrator



→ 25kW/dm³ (410W/in³) power density

Hardware Demonstrator – Volume Breakdown

 
 
- $M=3 / N=3$ hardware single-phase 10kW demonstrator



→ Almost 40% of volume occupied by mechanical parts

Hardware Demonstrator – Inductor

  - $M=3 / N=3$ hardware single-phase 10kW demonstrator



Weighted Losses:

Arr. 1: ca. 31.3W



Arr. 2: ca. 7.7W

	R_{dc} m Ω	$R_{ac,100k}$ m Ω	$R_{ac,1.6M}$ Ω
Arr. 1	3.40	9.14	1.47
Arr. 2	3.20	4.53	0.33
L_{br1}	3.15	4.41	0.28
L_{br2}	3.46	5.84	0.30
L_{br3}	3.25	4.83	0.33

→ Pot core branch inductor → No ext. fringing field → No eddy-current losses in metallic enclosure

Experimental Verification

  - Operation with sinusoidal reference at **100 kHz** and **10 kW** (full-load) output power (230 V_{rms}, 43.5 A_{rms})
- Open-loop** operation
- 24 ns interlocking time




→ ≈ 40 dB attenuation of 3rd and 5th harmonic

Experimental Verification

- Operation with sinusoidal reference at 100kHz and 10kW (full-load) output power



 i_{L1} 6 A/div
 i_{L2} 6 A/div
 i_{L3} 6 A/div
 i_{sum} 18 A/div




→ Adequate current balancing without active symmetry control

Experimental Verification: Efficiency

- $M=3 / N=3$ hardware demonstrator $\rightarrow f_{\text{sw,eff}} = 4.8 \text{ MHz}$
- Open-loop operation with $V_{\text{out}} = 230 \text{ V}_{\text{rms}}$
- 24 ns interlocking time



Low-inductive
load resistor (2 kW)


 


$\rightarrow \eta = 95.8\% @ 100 \text{ kHz}, 10 \text{ kW}$ (nom. op. point)


$\rightarrow$ Losses dominated by (hard-) switching losses

Experimental Verification: Efficiency

  - Impact of output frequency and input capacitor connection @ $P_{out} = 3.3\text{ kW}$



 Low-inductive connection of external DC-link capacitors (< 30 nH)




- Significant drop at 70 kHz (-1%) → ca. 80 App oscillation between 3L3 and Film-C DC-link bank
- Low-inductive connection to mitigate resonance

Thermal Management


 
- 4.5 mm thin Al coldplate
- Direct cooling of power semiconductors + inductors

- 12V / 14W Pump
- Volume Flow ≈ 2 l/min
- 10l H₂O Tank $\rightarrow$ "open-circuit" (No Heat Exchanger)
- 15 mm x 2 mm Channel




TG6050 TIM
6 W/(m·K), 1 mm

- $\rightarrow$ Loss estimation: $P_{\text{loss,est}} = c_{P,H2O} \cdot \rho_{H2O} \cdot \dot{V} \cdot \Delta\vartheta_{H2O}$
- $\rightarrow P_{\text{loss,est}} = 150\text{W}$ for $\Delta\vartheta_{H2O} = \vartheta_{H2O,out} - \vartheta_{H2O,in} = 1\text{K}$, $\dot{V} = 2\text{l/min}$
- $\rightarrow \vartheta_{\text{Case,Switch}} < 65^\circ\text{C} \rightarrow \vartheta_{J,\text{Switch}} < 100^\circ\text{C}$ (estimated with $R_{\text{th,j-c}} = 1\text{K/W}$, $P_{\text{switch}} = 34\text{W}$)
- $\rightarrow$ Room for improvement with better TIM + alternative package (?)

  


Outline: Output Voltage Control

 
- Cascaded current and voltage control
- v_{ref} , i_{load} and inductor voltage feedforward



 - $>300\text{kHz}$ closed-loop control BW possible
- Minimal loop delay crucial for ultra-fast control



 F. Krismer, et al., "Optimized Cascaded Controller Design for a 10 kW / 100 kHz Large Signal Bandwidth AC Power Source," IEEE Energy Conversion Congress and Exposition (ECCE USA), Detroit, MI, USA, Oct. 11-15, 2020.





High-Frequency DC-Coupled Current Measurement Sensors

Bandwidth Extension of Commercial Hall-Effect Current Sensors to $>10\text{MHz}$

LF + HF Sensor Combination



 
 
- Minimal error in the transition / combiner region
- Active combiner circuit



→ 4 decades overlap required → Possible with lower sensor response overlap range?

LF + HF Sensor Combination

    - Inherent well-defined high-pass response of HF sensor
- Manual matching of crossover frequency




→ Only 2 decades overlap required → Find suitable HF sensors

Investigated HF Sensors

- Max. BW and minimal volume


Isolated Inductive Voltage Sensing

 

→ No add. volume!


$$v = i_1 \cdot \frac{sM}{1 + sRC}$$

Current Transformer

 


→ Higher BW
 
$$v = i_1 \cdot R \cdot \frac{sM/(R + R_2)}{1 + sL_2/(R + R_2)}$$



Pickup Coils

→ Highest BW + linear

 


→ Which sensor offers best performance?




Experimental Verification – Frequency Response

- All sensors **tested in-circuit**

▼ Setup Frequency Response

 

▼ Frequency Domain


 


- 10MHz BW fulfilled with all sensors
- PUC C with highest BW and smallest form factor




Experimental Verification – Time Domain Behavior

- All sensors tested in-circuit

  


Hall sensor only

▼ Time Domain – Sensors after L

 

 - Accurate tracking of triangular current
- PUC C with highest BW and smallest form factor




High-Bandwidth Isolated Voltage Measurements with Very High Common Mode Rejection Ratio

Accurate Measurements during Fast Voltage Transients


Modeling of Required CMRR

 - Spectral envelope of trapezoidal CM voltage
- Rectangular error voltage




$$f_{c1} = \frac{1}{\pi \cdot t_p} = \frac{f_{sw}}{\pi \cdot D}$$
 
$$f_{c2} = \frac{1}{\pi \cdot t_s} = \frac{dv/dt}{\pi \cdot V_{dc}}$$






→ Only V_{dc} + dv/dt determine CMRR requirement and NOT switching frequency

For $\Delta V_{e,pp} = 1 \text{ V}$

 

Isolated Voltage Measurement System

   - Small and decoupled C_{earth} → Low CM current i_{CM}
- Several measures to limit/redirect i_{CM}







Parameter	Value
Input Voltage Range	$\pm 1 \dots \pm 75 \text{ V}$
Bandwidth	130 MHz
Sampling Rate	400 MSPS
Vertical Resolution	8 Bit
CMRR @ 100 MHz	>108 dB

→ Fully independent of other equipment (no oscilloscope etc. required)


Isolated Voltage Measurement System

    - Battery operation (ca. 2h for power cons. of 2W)
- Low-C isolated power supply
- Wide input voltage range (5 – 50V), 5W output power



- Coupling capacitance < 2 pF, isolation > 1 kV (tested)
- Unlimited operating time

Experimental Verification

 


◀ Freq.
Dom.

◀ 100 dB


◀ 100 MHz

→ **>100dB CMRR @ 100MHz, 130MHz BW**

▼ Time Domain

 

 → Accurate tracking of $v_{GS,HS}$, **no CM distortion**



Conclusions / Summary


■ Test and verification of Next Generation Power Electronics

▼ 3L3 UHBPA



- Part of P-HIL test env.
- Topological evaluation
- Hardware demonstrator with 25kW/dm³ power density
- 95.8% efficiency @ 230V_{rms}, 10kW, 100kHz

▼ I-Sensor

 

- Hall sensor BW extension to >50MHz
- Diff. HF sensors compared
- Superior CMRR
- Compact design

▼ V-Sensor



- Isolated V-measurement
- Fluctuating ref. potential
- Isolated measurement system realized
- 130MHz BW + 100dB CMRR @ 100MHz

→ Several challenges related to very high switching frequency converters addressed

Thank you!



► Slides

Further Reading:

- P. S. Niklaus, J. W. Kolar, and D. Bortis, “100 kHz Large-Signal Bandwidth GaN-Based 10 kVA Class-D Power Amplifier with 4.8 MHz Switching Frequency,” *IEEE Transactions on Power Electronics*, Vol. 38, No. 2, pp. 2307-2326, February 2023.
DOI: <https://doi.org/10.1109/TPEL.2022.3213930>
- F. Krismer, V. Behrunani, P. S. Niklaus, and J. W. Kolar, “Optimized Cascaded Controller Design for a 10 kW / 100 kHz Large Signal Bandwidth AC Power Source,” in *Proc. of the IEEE Energy Conversion Congress and Exposition (ECCE USA)*, Detroit, MI, USA, October 11-15, 2020
DOI: <https://doi.org/10.1109/ECCE44975.2020.9236149>
- P. S. Niklaus, D. Bortis, and J. W. Kolar, “Beyond 50 MHz Bandwidth Extension of Commercial DC-Current Measurement Sensors with Ultra-Compact PCB Integrated Pickup Coils,” *IEEE Transactions on Industry Applications*, Vol. 58, No. 4, pp. 5026-5041, August 2022.
DOI: <https://doi.org/10.1109/TIA.2022.3164865>
- P. S. Niklaus, R. Bonetti, C. Stäger, J. W. Kolar, and D. Bortis, “High-Bandwidth Isolated Voltage Measurements with Very High Common Mode Rejection Ratio for WBG Power Converters,” *IEEE Open Journal of Power Electronics*, Vol. 3, pp. 651-664, September 2022.

