

Synergetically Controlled Three-Phase Boost-Buck Ultra-Wide Output Voltage Range Isolated EV Battery Charger

Yunni Li, Johann W. Kolar

Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch

In collaboration with:



Acknowledgements: J. Azurza, J. Schäfer



Introduction

► Motivation

- Growing sales of EVs
- High power density and high efficiency of the charging system





► Future Fast EV Charger Specifications

- Extremely wide input-output voltage range
- Buck-boost capability

► Two-Stage EV Charging System

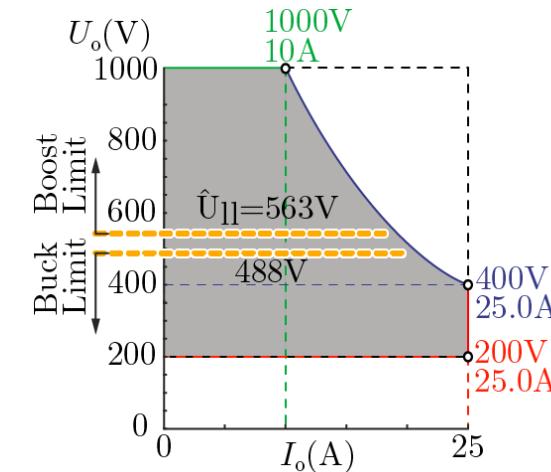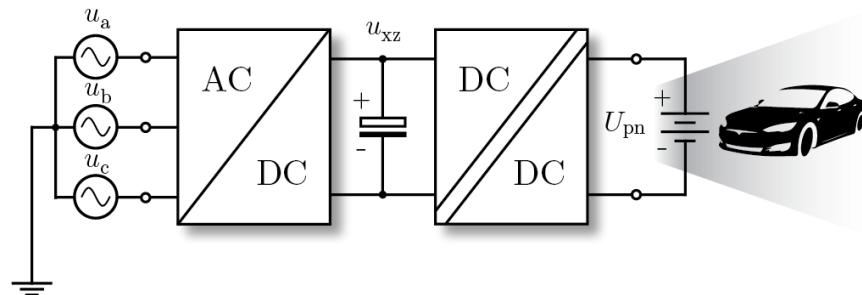- AC/DC front-end + isolated DC/DC converter



Introduction

► Motivation



- Growing sales of EVs
- High power density and high efficiency of the charging system

► Future Fast EV Charger Specifications

- Extremely wide input-output voltage range
- Buck-boost capability

► Two-Stage EV Charging System

- Vienna Rectifier front-end (VR)

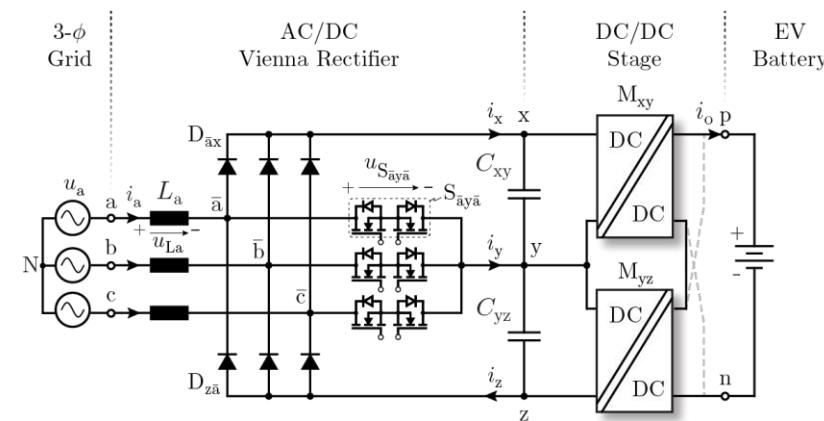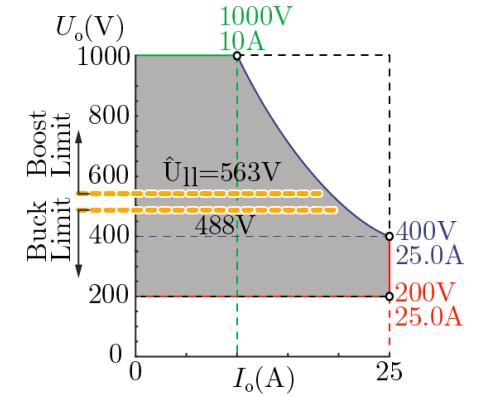

Introduction

► Motivation


- Growing sales of EVs
- High power density and high efficiency of the charging system

► Future Fast EV Charger Specifications




- Extremely wide input-output voltage range
- Buck-boost capability

► Two-Stage EV Charging System

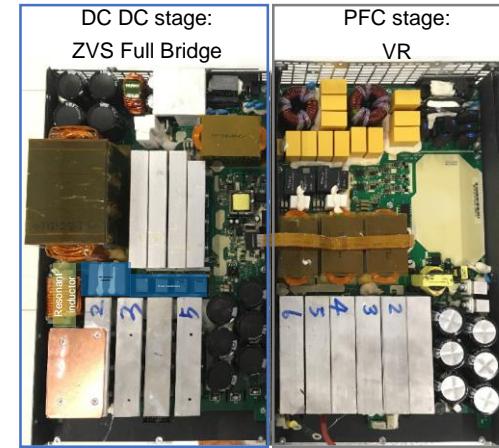- Vienna Rectifier front-end (VR)
- Isolated DC/DC converters
 - Phase-shifted converters
 - ZVS full bridge, DAB etc.



Source: INFY 20kW EV Charger Module

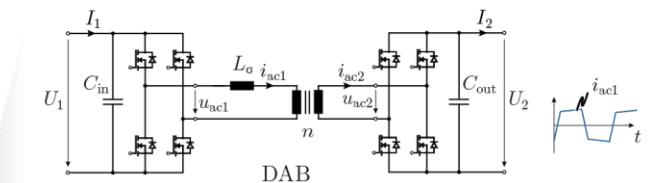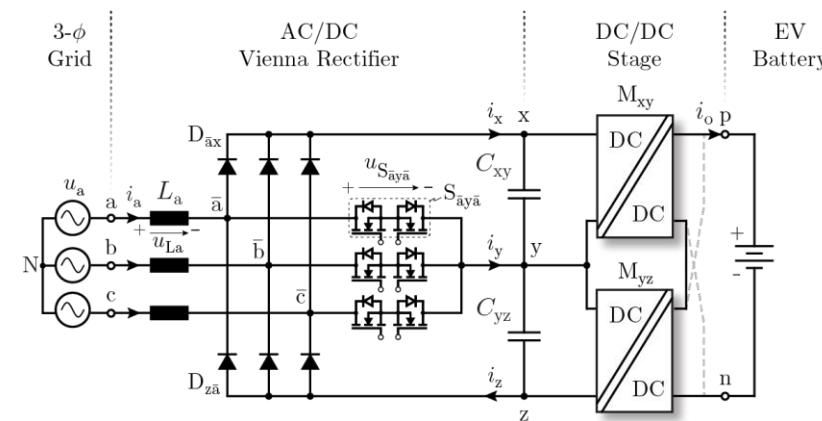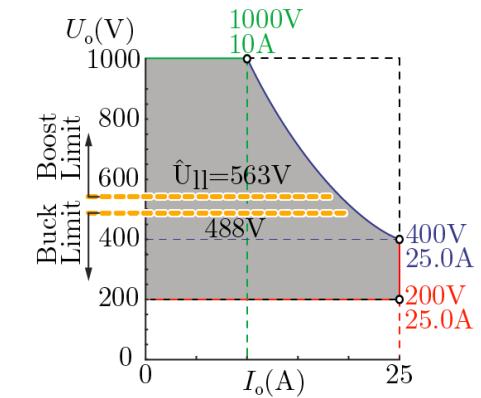

Introduction

► Motivation


- Growing sales of EVs
- High power density and high efficiency of the charging system

► Future Fast EV Charger Specifications




- Extremely wide input-output voltage range
- Buck-boost capability

► Two-Stage EV Charging System

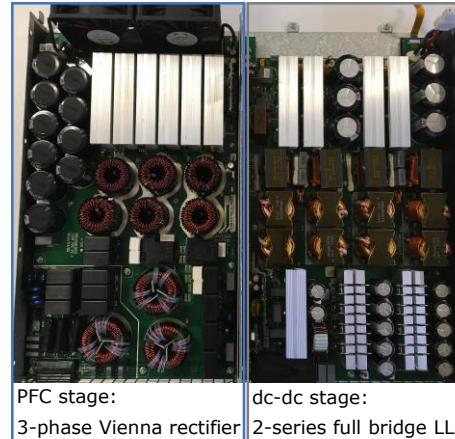- Vienna Rectifier front-end (VR)
- Isolated DC/DC converters
 - Phase-shifted converters
 - Resonant converters
 - LLC



Source: UU Green 15kW EV Charger Module

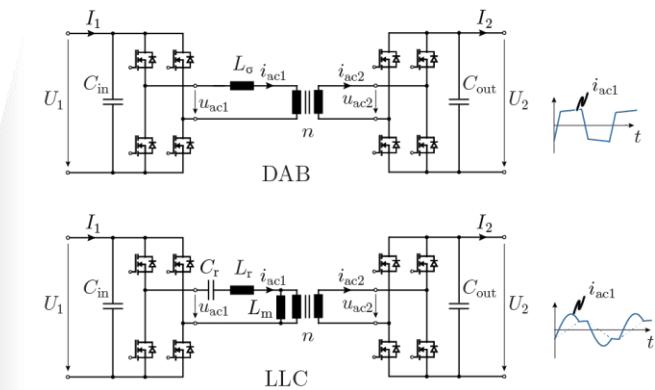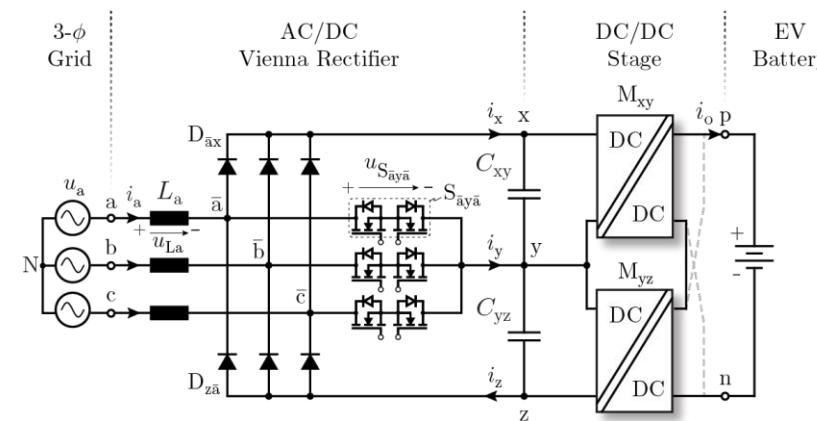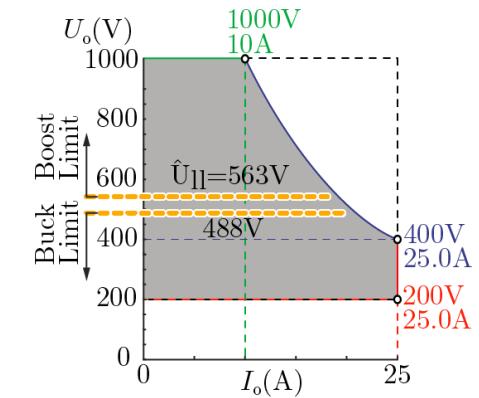

Introduction

► Motivation

- Growing sales of EVs
- High power density and high efficiency of the charging system






► Future Fast EV Charger Specifications

- Extremely wide input-output voltage range
- Buck-boost capability

► Two-Stage EV Charging System: Challenges

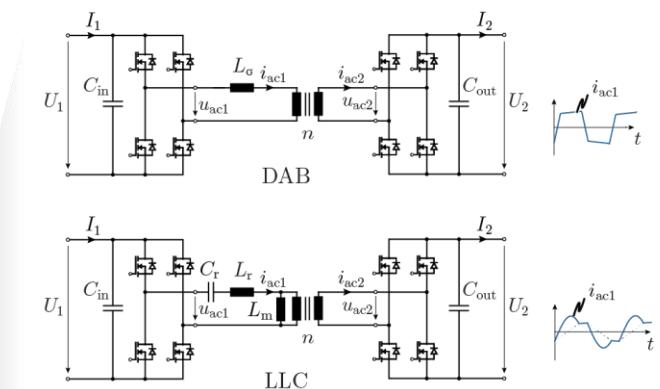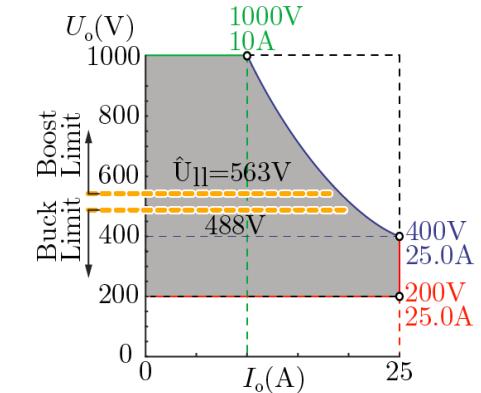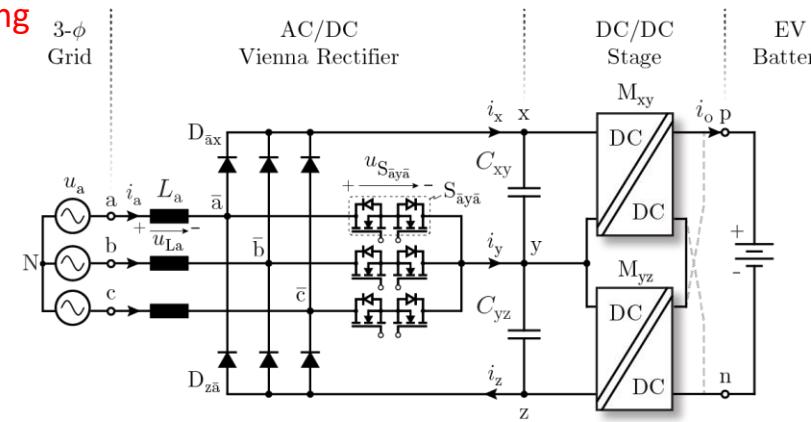- Vienna Rectifier front-end (VR)
- Isolated DC/DC converters
 - Phase-shifted converters
 - Reactive power / RMS current, soft-switching
 - Resonant converters
 - High f_{sw} , losses of magnetic components



Introduction

► Motivation

- Growing sales of EVs
- High power density and high efficiency of the charging system






► Future Fast EV Charger Specifications

- Extremely wide input-output voltage range
- Buck-boost capability

► Two-Stage EV Charging System: Solutions

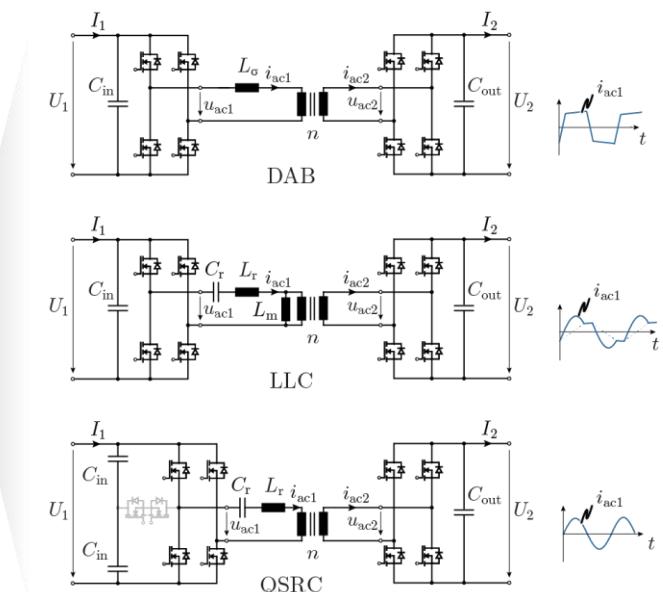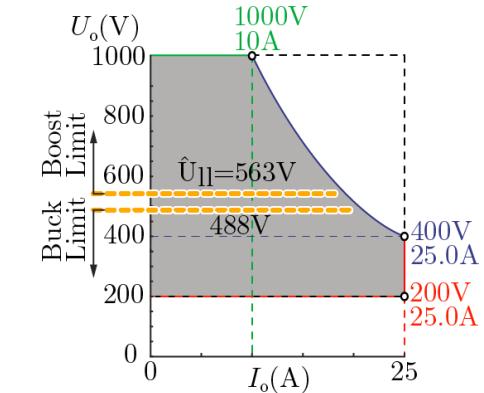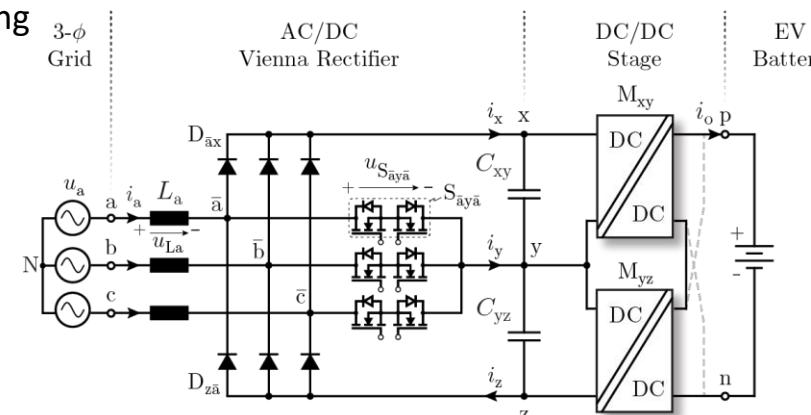- Vienna Rectifier front-end (VR)
- Isolated DC/DC converters
 - Phase-shifted converters
 - Reactive power / RMS current, soft-switching
 - Resonant converters
 - High f_{sw} , losses of magnetic components
 - QSRC (Quantum Series Resonant Converter)
 - Constant f_{sw} , sinusoidal currents
 - Buck-boost capability
 - Currently in investigation



Introduction

► Motivation

- Growing sales of EVs
- High power density and high efficiency of the charging system






► Future Fast EV Charger Specifications

- Extremely wide input-output voltage range
- Buck-boost capability

► Two-Stage EV Charging System: Solutions

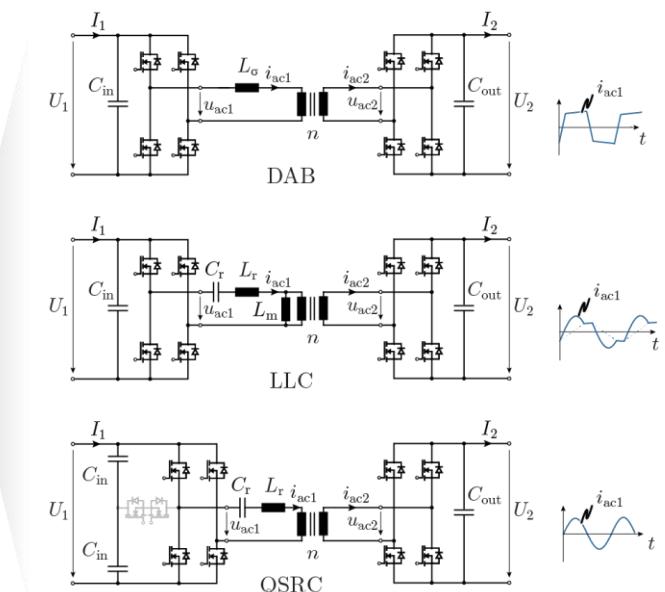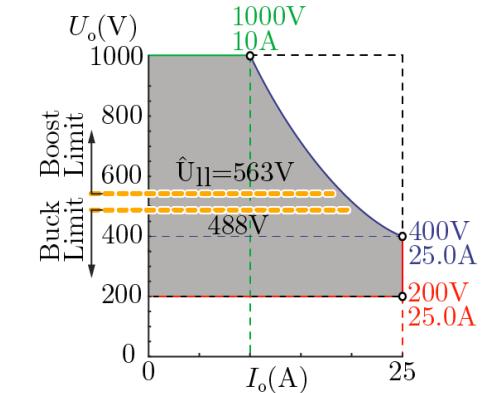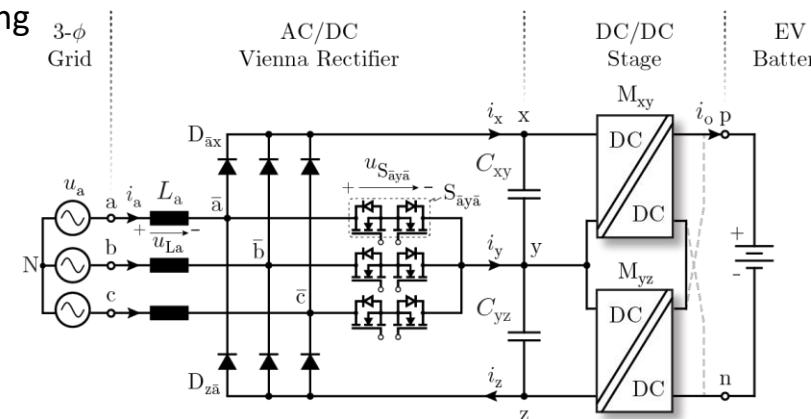- Vienna Rectifier front-end (VR)
- Isolated DC/DC converters
 - Phase-shifted converters
 - Reactive power / RMS current, soft-switching
 - Resonant converters
 - High f_{sw} , losses of magnetic components
 - QSRC
 - Decoupled control? Synergetic control!



Introduction

► Motivation

- Growing sales of EVs
- High power density and high efficiency of the charging system

► Future Fast EV Charger Specifications

- Extremely wide input-output voltage range
- Buck-boost capability


► Two-Stage EV Charging System

► 10kW Demonstrator System


- Vienna Rectifier front-end
- 4DAB: 2 in parallel, 2 in series both input/output

► Semiconductors

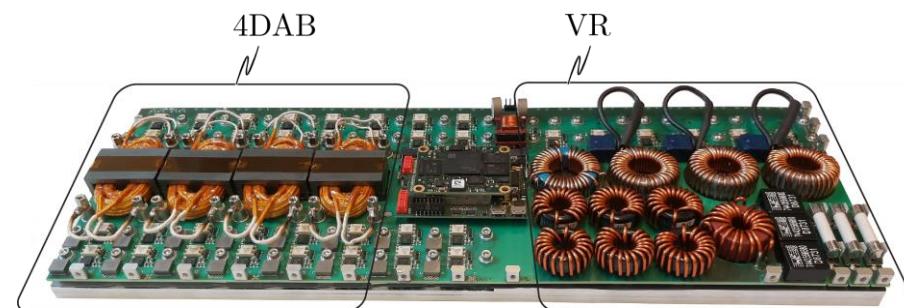- 600V GaN Switches (Infineon, IGOT60R070D1)
- 1200V SiC Schottky Diodes (Infineon, IDM10G120C5)



Parameters	Value
Rated Power	10 kW
Input Voltage Range	320-530 V _{rms}
Output Voltage Range	250-1000 V _{dc}
Power Density	10 kW/dm ³ (2x 20 kW/dm ³)
Size	400 x 140 x 18 mm ³
Efficiency (Target)	95 %
Switching Frequency	560kHz (VR) 140kHz – 400kHz (DAB)

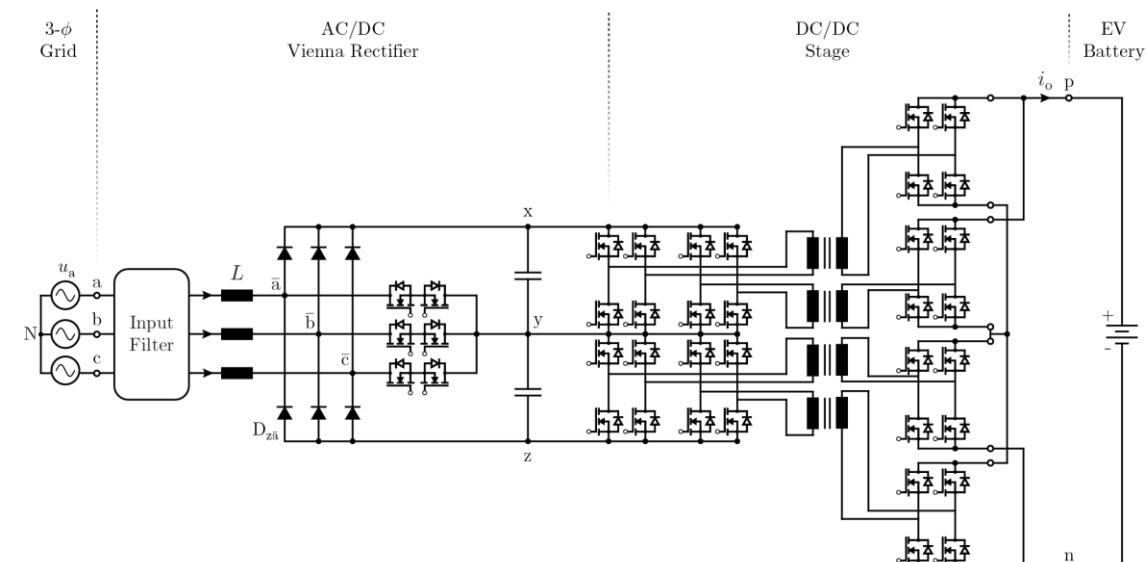

External Hw. Design: J. Miniböck



Outline

- Introduction
- Operating Principle of the Two-Stage Charger System
- Firmware Structure
- Measurements of DAB Test System
- Measurements of the 10kW VR + DAB Demonstrator System
- Conclusions

Operating Principle of the Two-Stage Charger System : Vienna Rectifier

► Conventional modulation (3/3 - PWM)

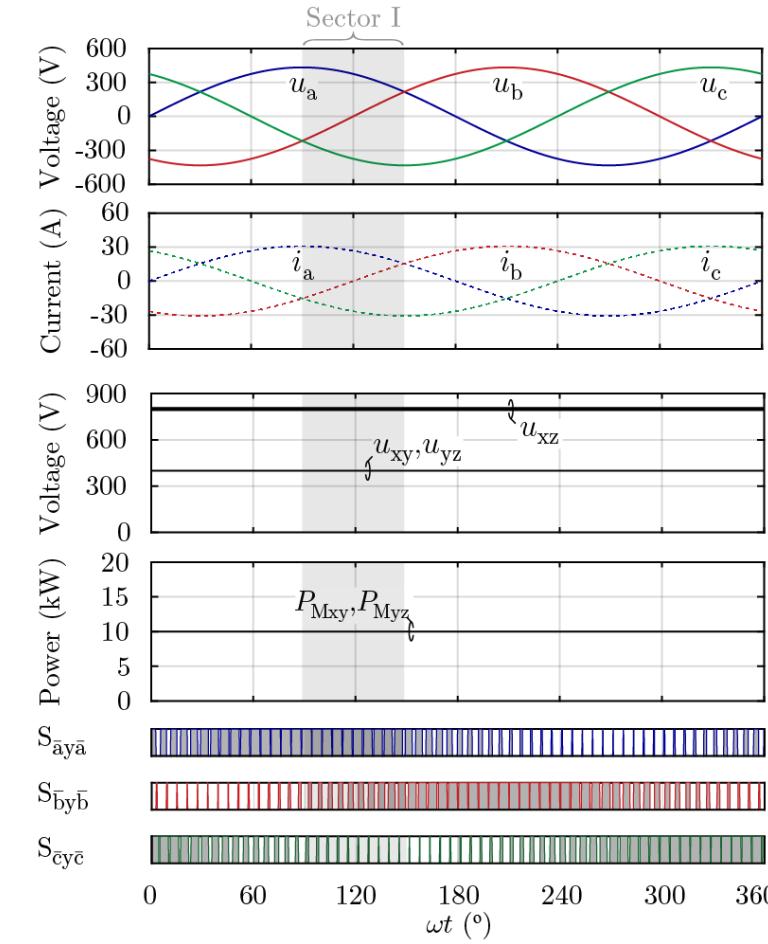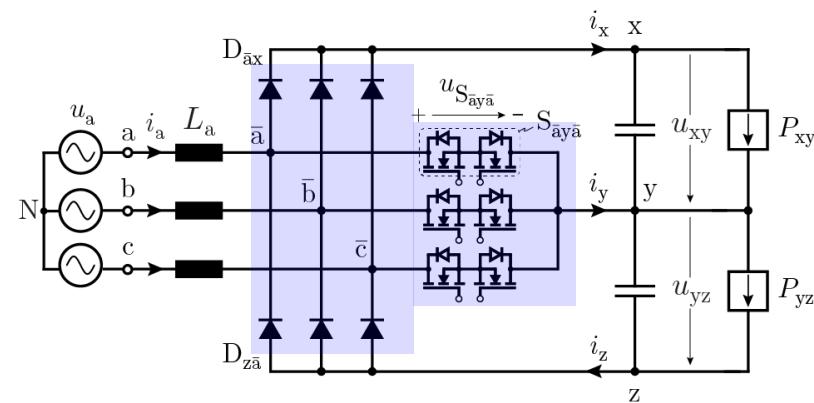- **3/3 Phases** pulse width modulated
- **Constant DC voltage** (equal splitting)
- **Decoupled AC/DC and DC/DC**





Operating Principle of the Two-Stage Charger System : Vienna Rectifier

► Conventional modulation (3/3 - PWM)

- 3/3 phases are pulse width modulated
- Constant DC voltage (equal splitting)
- Decoupled AC/DC and DC/DC

► 1/3 Modulation


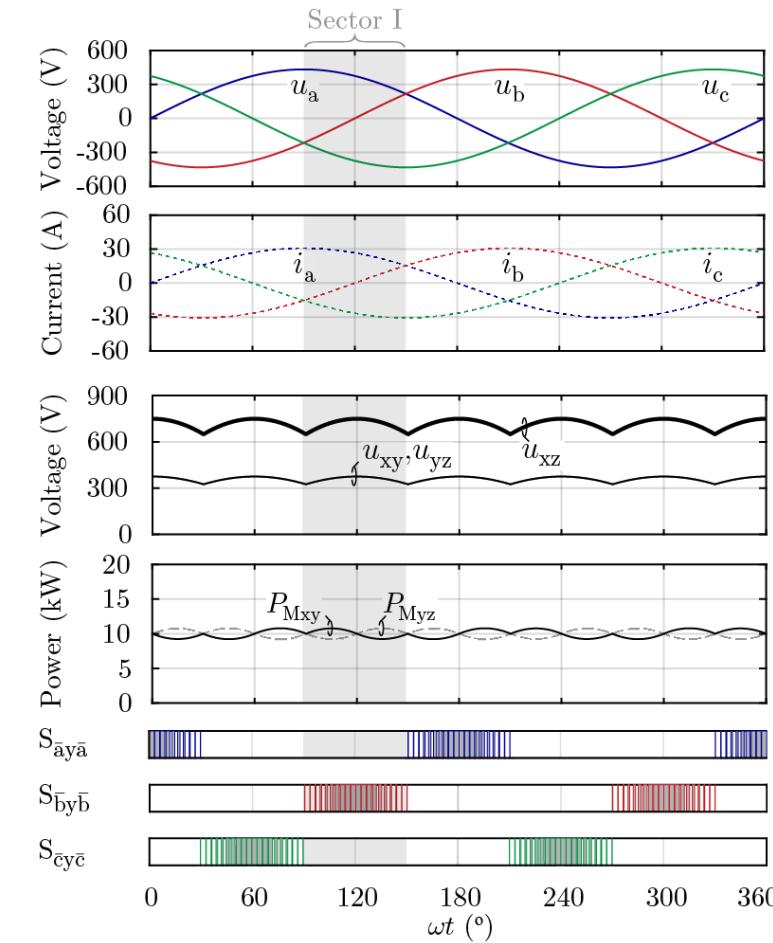
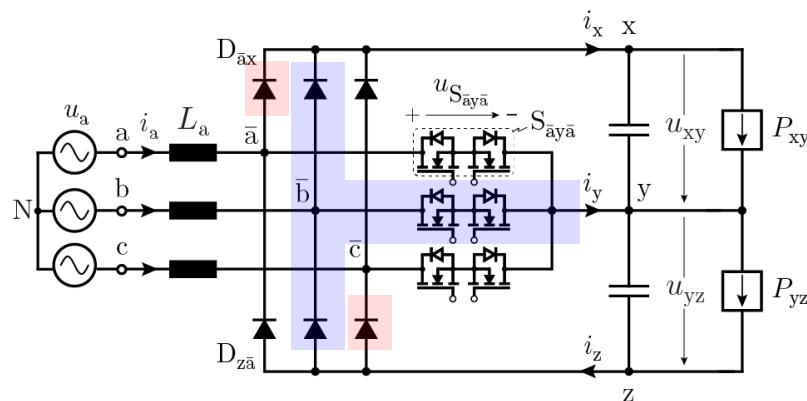
- Only the phase with lowest current is switched
- Sinusoidal PFC currents
- Achieved by **Synergetic Control** scheme
- Significant switching **loss saving**
 - Performance improvement: efficiency/power density
 - Cost reduction: cheaper switches



Operating Principle of the Two-Stage Charger System : Vienna Rectifier

► Diode Rectifier

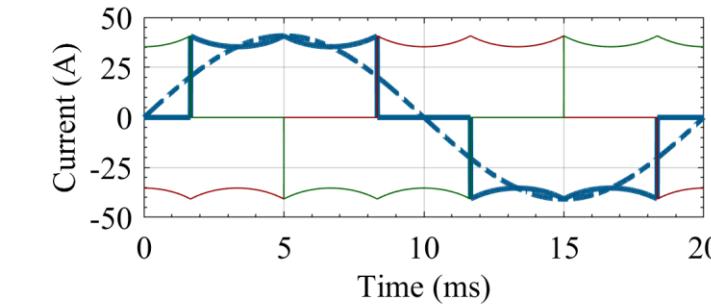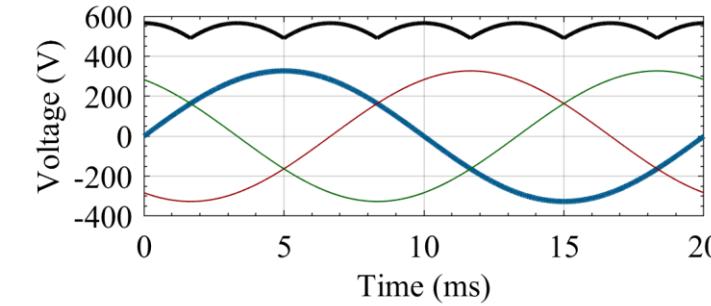
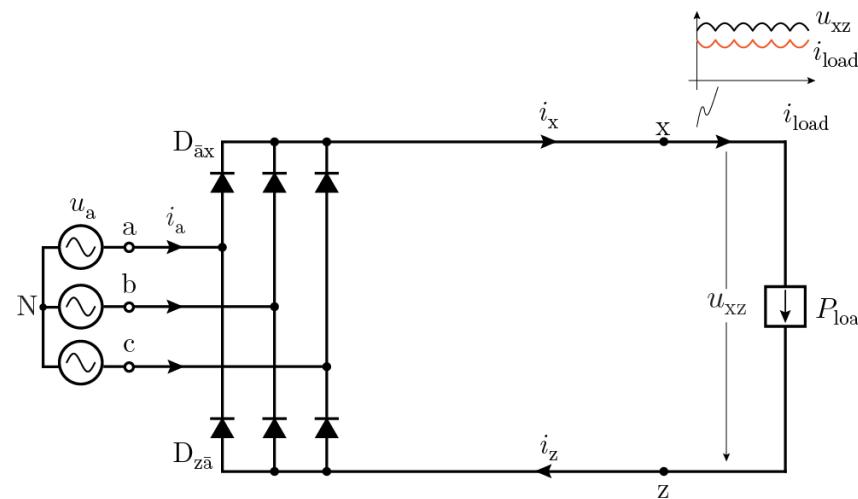
- Constant power load
- Simple realization
- Minimum DC-link voltage – six-pulse shape
- Block-shaped input currents: **low freq. harmonics**



Operating Principle of the Two-Stage Charger System : Vienna Rectifier

► Integrated Active Filter (IAF)

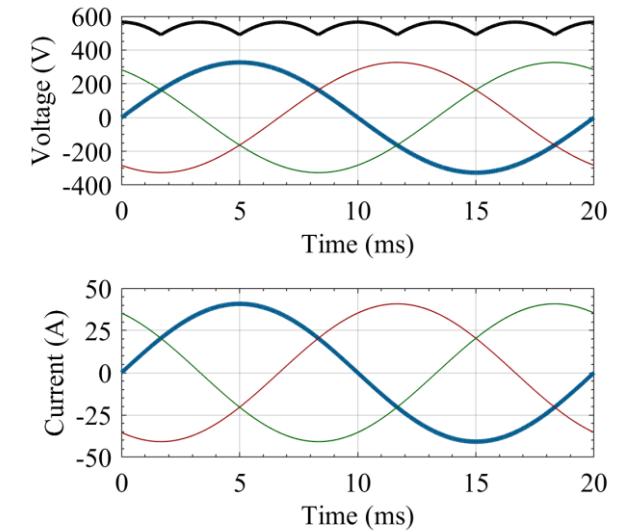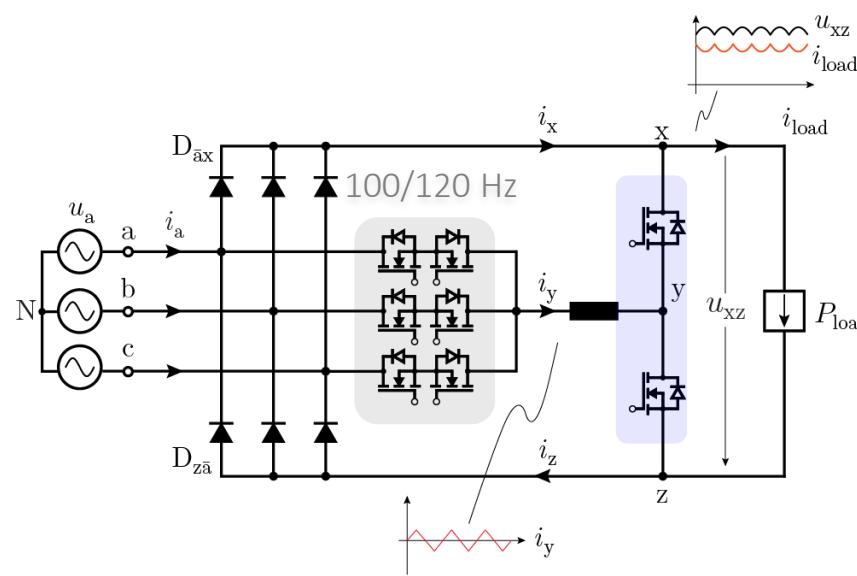- Only 1 bridge leg PWM
- Insert a current prop. to smallest voltage in the “middle phase”
- “Phase-selector” 100/120 Hz switches
- Achieve sinusoidal input currents
- No boost capability





Operating Principle of the Two-Stage Charger System : Vienna Rectifier

► Integrated Active Filter (IAF)

- Only 1 bridge leg PWM
- Insert a current prop. to smallest voltage in the “middle phase”
- “Phase-selector” 100/120 Hz switches
- Achieve sinusoidal input currents
- No boost capability

► IAF vs. VIENNA – Similar Structures

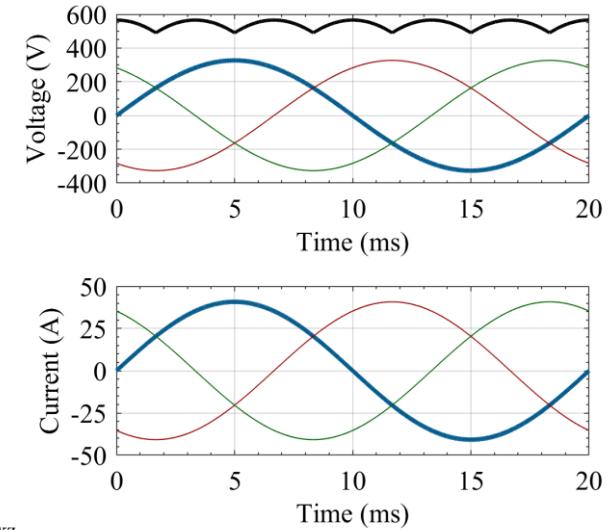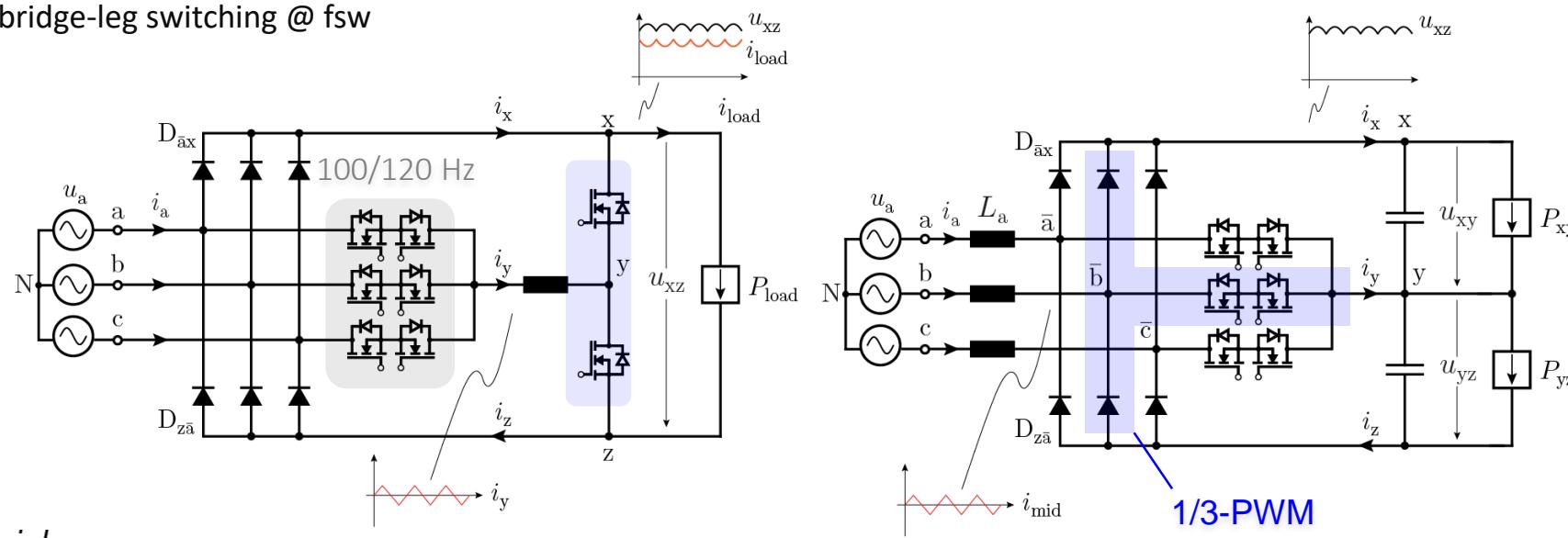- 1x inductor in IAF -> 3x inductors in VIENNA
- Less semiconductors
- **VIENNA can boost**
- 1/3 bridge-leg switching @ fsw



Operating Principle of the Two-Stage Charger System : Vienna Rectifier

► 3/3 PWM vs 1/3 PWM



- Reduced switching transitions

► Coupled Control of AC/DC and DC/DC

- Implementation effort: one-time

► DC link Capacitance Reduction

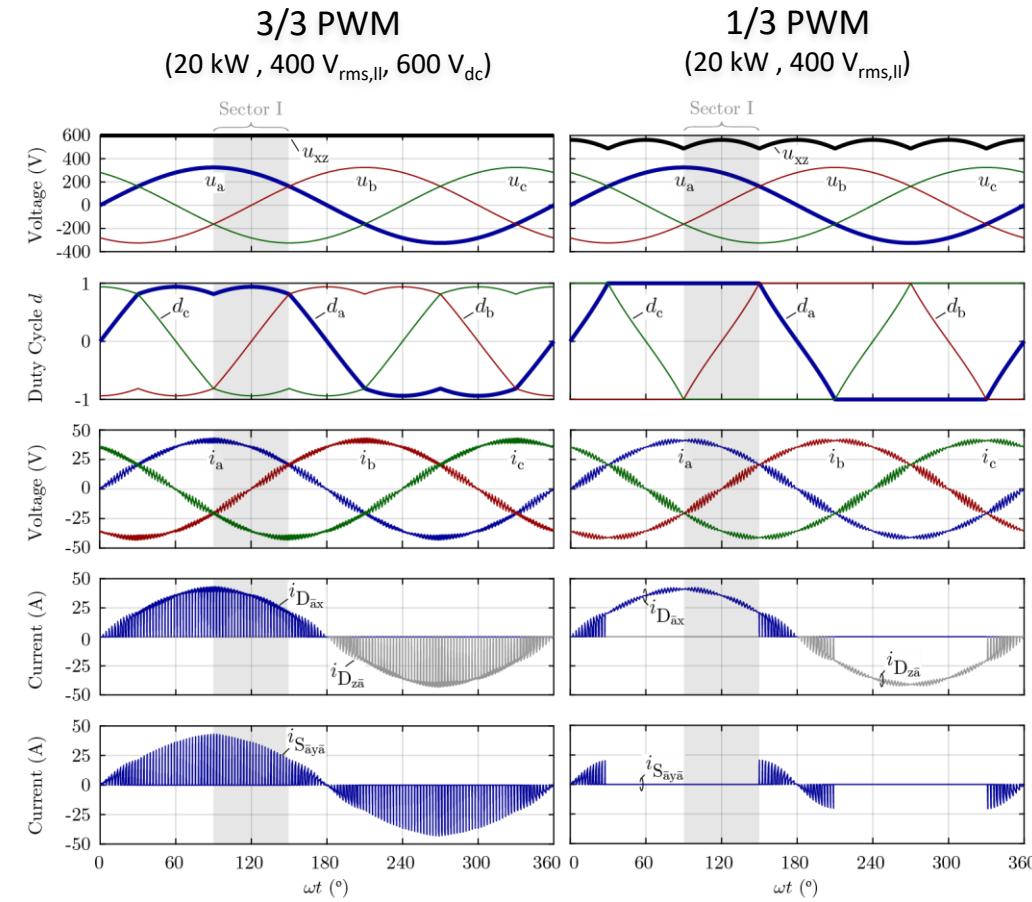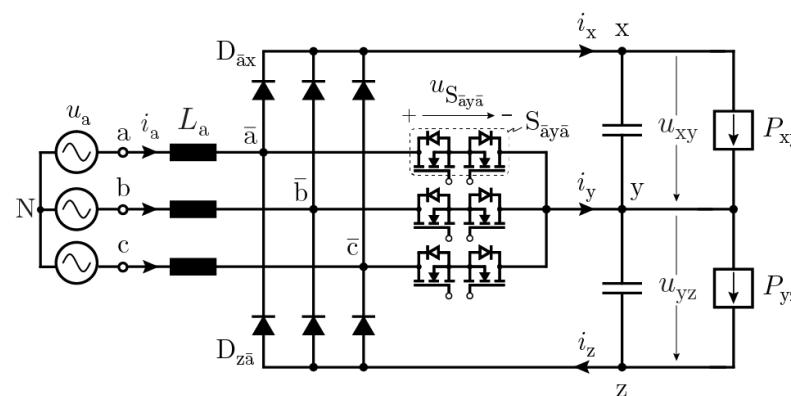
- Space saving
- Potential surge protection devices



Operating Principle of the Two-Stage Charger System : Vienna Rectifier



► Synergetic Control Structure

- Synergetic cascaded control structure

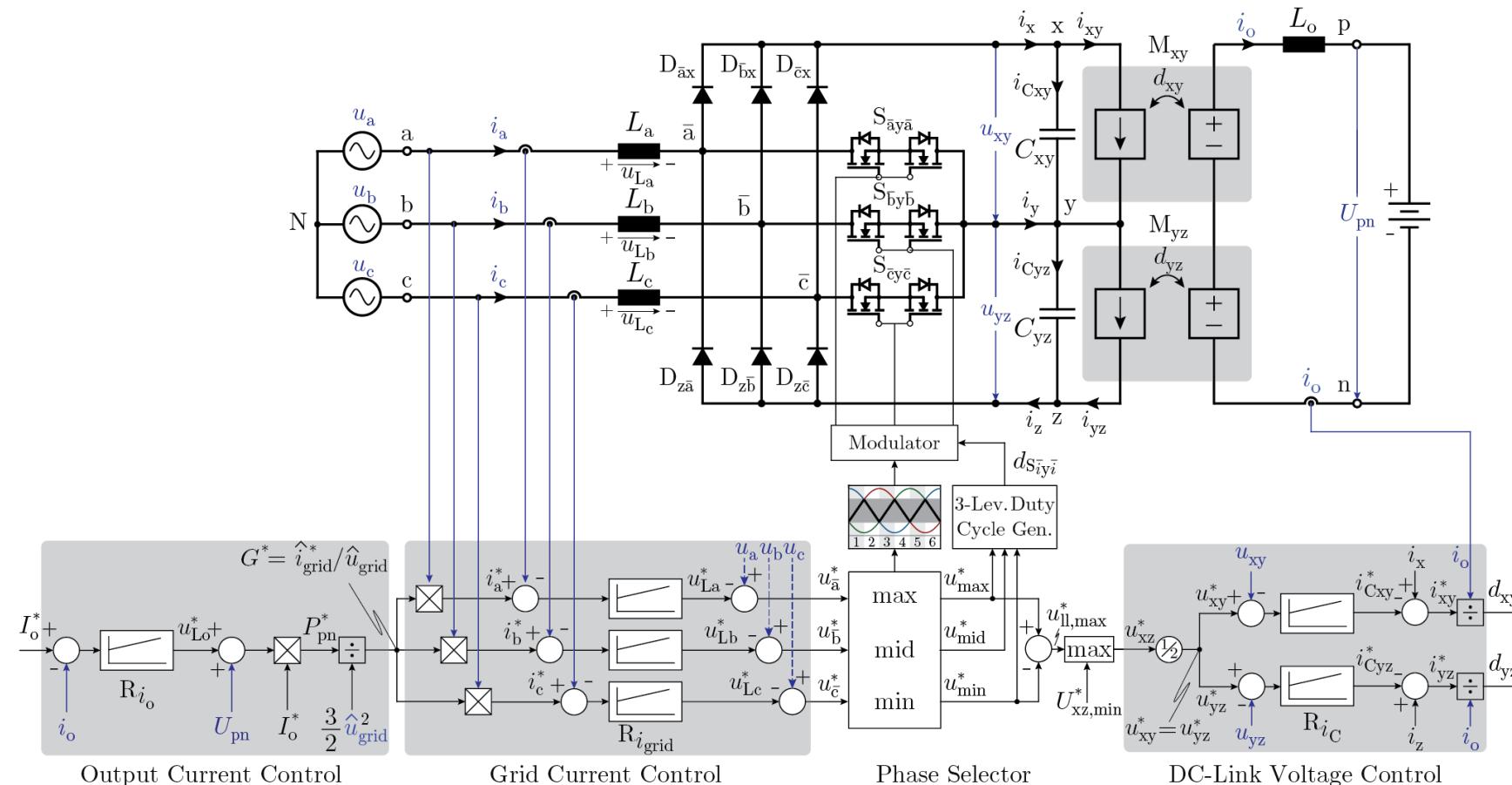

Operating Principle of the Two-Stage Charger System : Vienna Rectifier

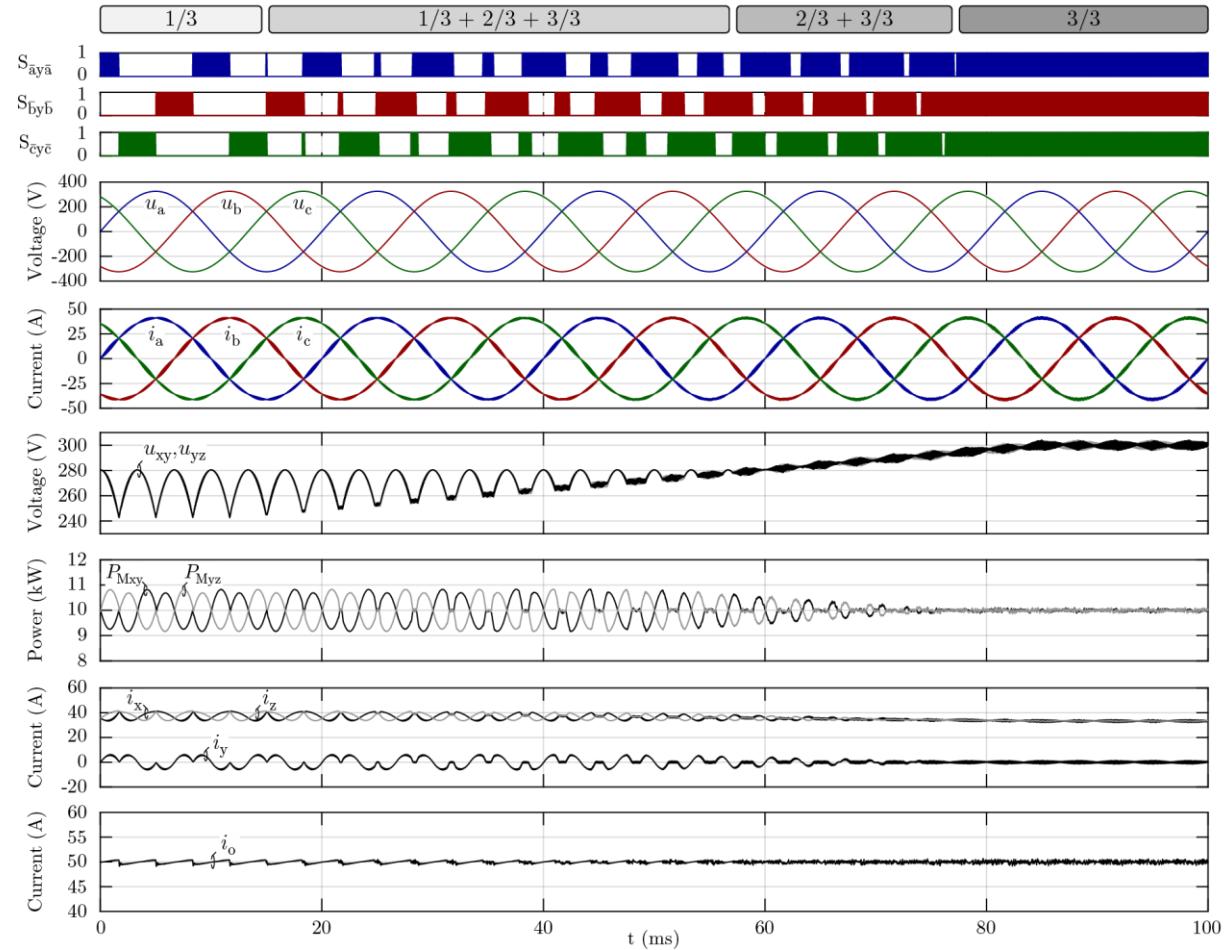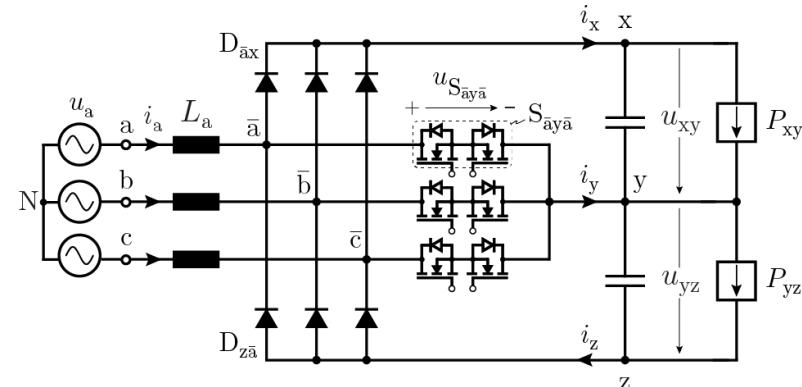► Simulation Results : DC-Link Voltage Transition



Operating Principle of the Two-Stage Charger System : Vienna Rectifier

► Semiconductor Loss Savings



- Switching Losses $E_{sw} = \text{Constant Term} + \text{Current Dep. (Linear) Term}$

$$\text{3/3-PWM: } P_{sw,3/3} = (E_{sw,0} + E_{sw,1} \cdot I_{avg}) f_{sw}$$

$$\text{1/3-PWM: } P_{sw,1/3} = \left(\underbrace{\frac{E_{sw,0}}{3}}_{-66\%} + \underbrace{\left(1 - \frac{\sqrt{3}}{2}\right) E_{sw,1} \cdot I_{avg}}_{-86\%} \right) f_{sw}$$

- Conduction losses






		3/3-PWM	1/3-PWM	Diff.
Switches	RMS	10.2 A	3.7 A	- 63.4 %
Diodes	RMS	19.3 A	20.4 A	+ 5.5 %
	AVG	11.1 A	12.44 A	+ 12.3 %

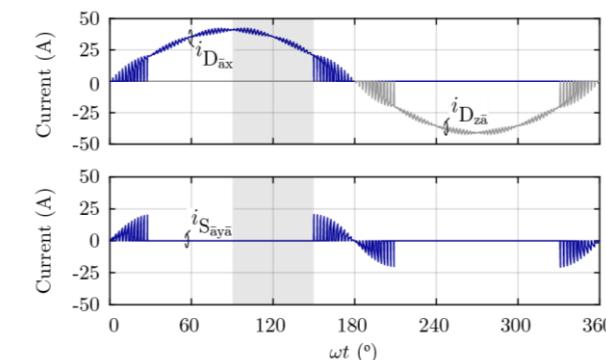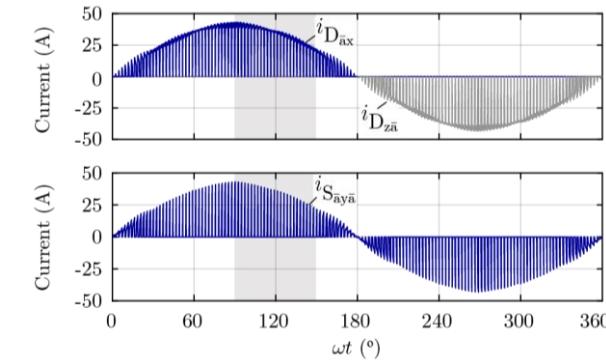



Operating Principle of the Two-Stage Charger System : DC/DC Stage

► Isolated DC/DC Converters

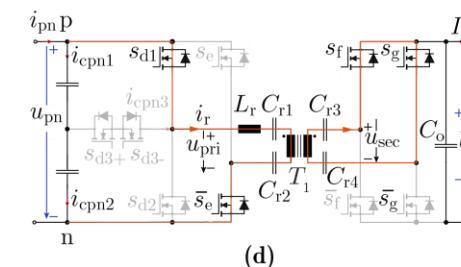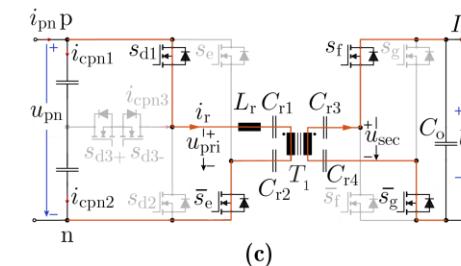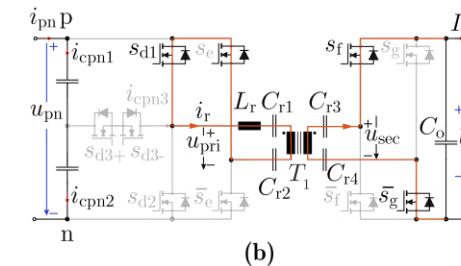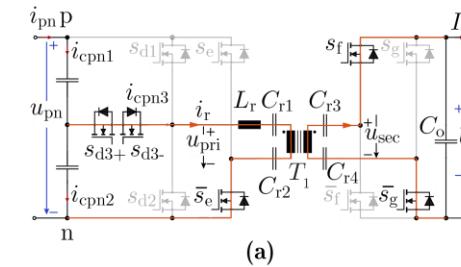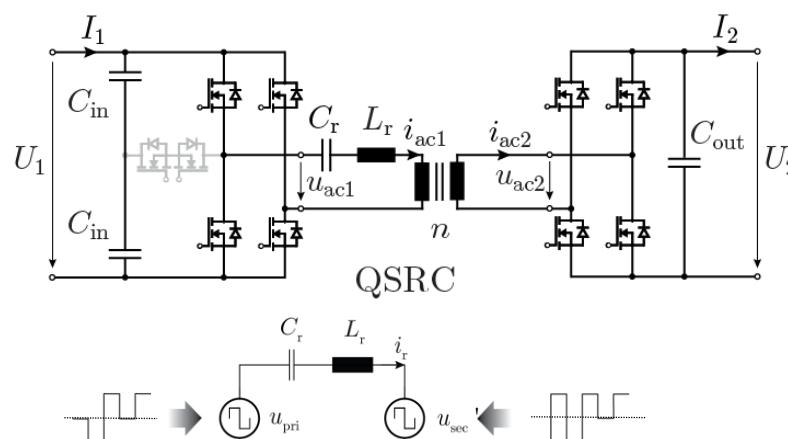
- Phase-shifted converters
 - DAB
 - Complexity
 - Reactive power (high RMS current)
 - Trapezoidal currents: EMI unfriendly
 - Active switches on the secondary side
- Resonant converters
 - LLC
 - High f_{sw} , losses of magnetic components
 - QSRC (Quantum Series Resonant Converter)**
 - Constant f_{sw} , sinusoidal currents
 - Buck-boost capability



Buck-Mode With the T-Type Bridge-Leg

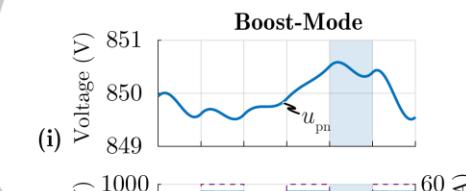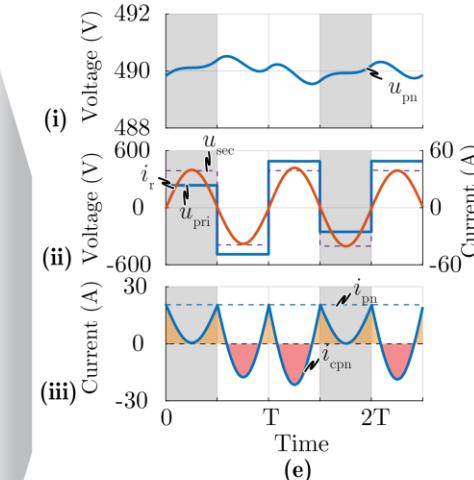




Boost-Mode

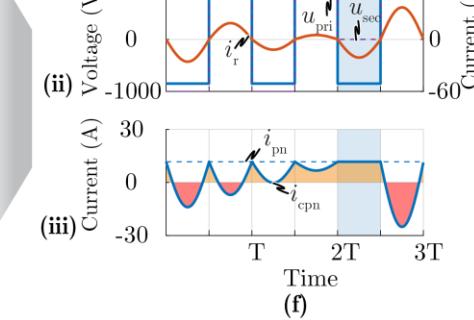

Operating Principle of the Two-Stage Charger System : Dual-Active-Bridge Converter

► Phase-Shift Modulation (PSM)

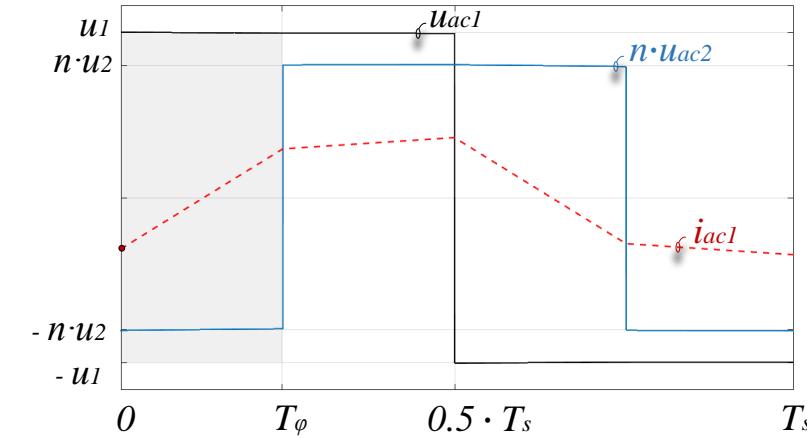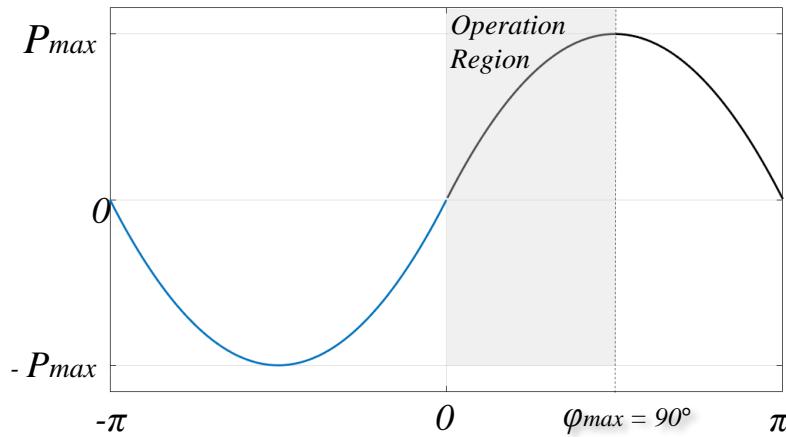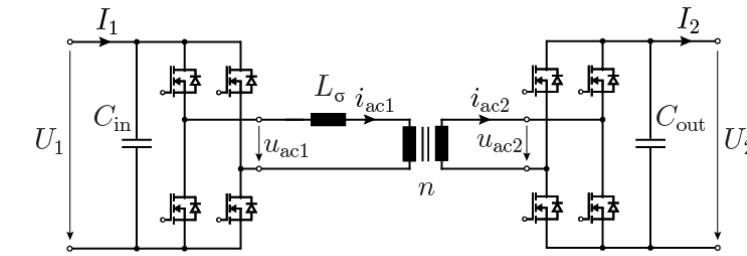- Phase-shift between the primary & secondary side full bridge
- Buck & Boost capability
- Bidirectional (on-board chargers)





Operating Principle of the Two-Stage Charger System : Dual-Active-Bridge Converter

► Phase-Shift Modulation (PSM)

- Phase-shift between the primary & secondary side full bridge
- Buck & Boost capability
- Bidirectional

► Advanced Modulation

- More degrees of freedom
 - d_1, d_2, f_{sw}
- Simple & straightforward implementation
- Different operating regions
 - **Buck** ($U_1 > nU_2$)
 - $d_1 = nU_2/U_1, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - **Transition** ($U_1 = nU_2$): PSM
 - $d_1 = 0.5, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - **Boost** ($U_1 < nU_2$)
 - $d_1 = nU_2/U_1, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - High switching losses due to high voltage and f_{sw}

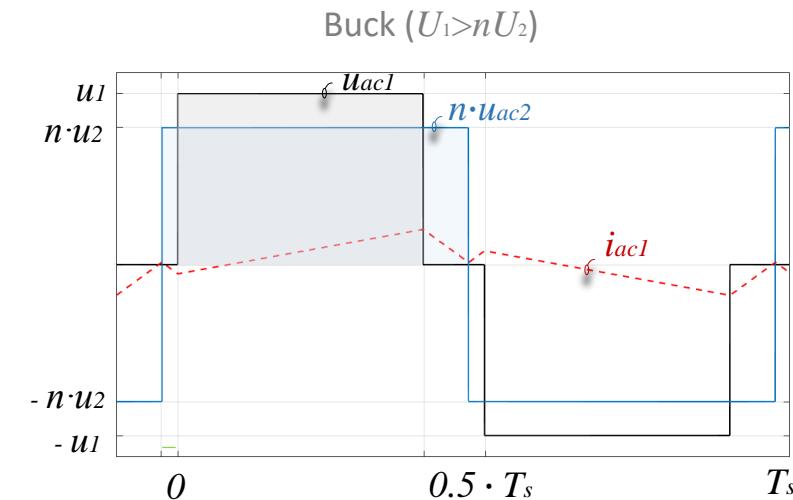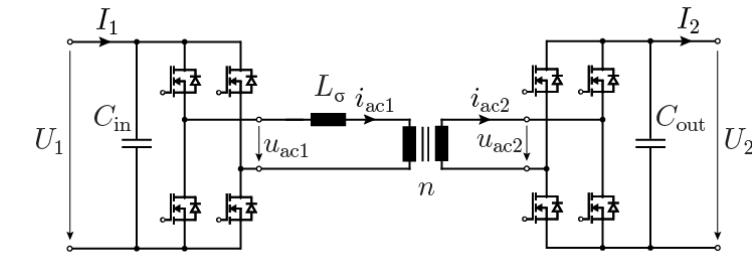



Operating Principle of the Two-Stage Charger System : Dual-Active-Bridge Converter

► Phase-Shift Modulation (PSM)

- Phase-shift between the primary & secondary side full bridge
- Buck & Boost capability
- Bidirectional

► Advanced Modulation

- More degrees of freedom
 - d_1, d_2, f_{sw}
- Simple & straightforward implementation
- Different operating regions
 - Buck ($U_1 > nU_2$)
 - $d_1 = nU_2/U_1, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - Transition ($U_1 = nU_2$): PSM
 - $d_1 = 0.5, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - Boost ($U_1 < nU_2$)
 - $d_1 = nU_2/U_1, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - High switching losses due to high voltage and f_{sw}
 - $d_1 = 0.5, d_2, f_{sw}$ optimized to ensure soft switching

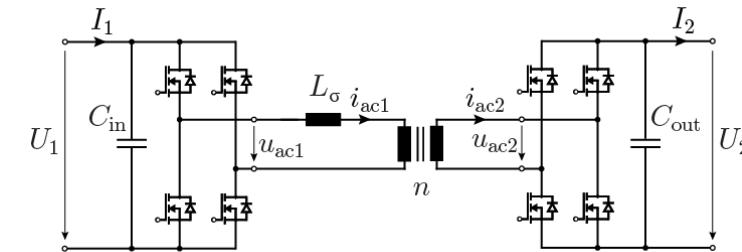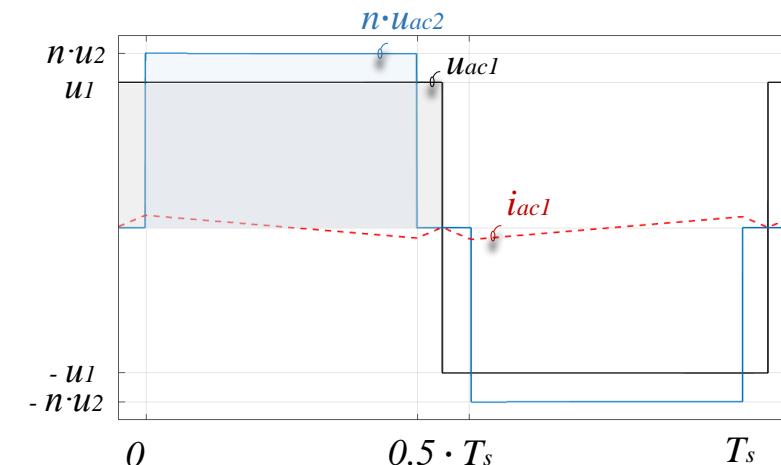Boost ($U_1 < nU_2$)


Operating Principle of the Two-Stage Charger System : Dual-Active-Bridge Converter

► Basic Modulation


- Phase-shift between the primary & secondary side full bridge
- Buck & Boost capability
- Bidirectional

► Advanced Modulation

- More degrees of freedom
 - d_1, d_2, f_{sw}
- Simple & straightforward implementation
- Different operating regions
 - Buck ($U_1 > nU_2$)
 - $d_1 = nU_2/U_1, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - Transition ($U_1 = nU_2$): PSM
 - $d_1 = 0.5, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - Boost ($U_1 < nU_2$)
 - $d_1 = nU_2/U_1, d_2 = 0.5, f_{sw}$ increases with U_1 to keep the same V·s
 - High switching losses due to high voltage and f_{sw}
 - d_1, f_{sw} optimized, $d_2 = 0.5$, to ensure soft switching
- Possible improvements
 - Minimum I_{rms}
 - Soft switching
 - Refer to Dr. Florian Krismeyer's PhD Thesis

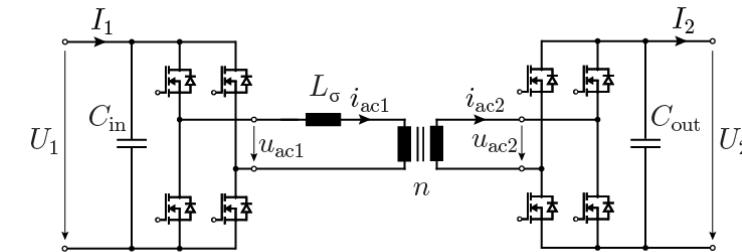



Boost ($U_1 < nU_2$)

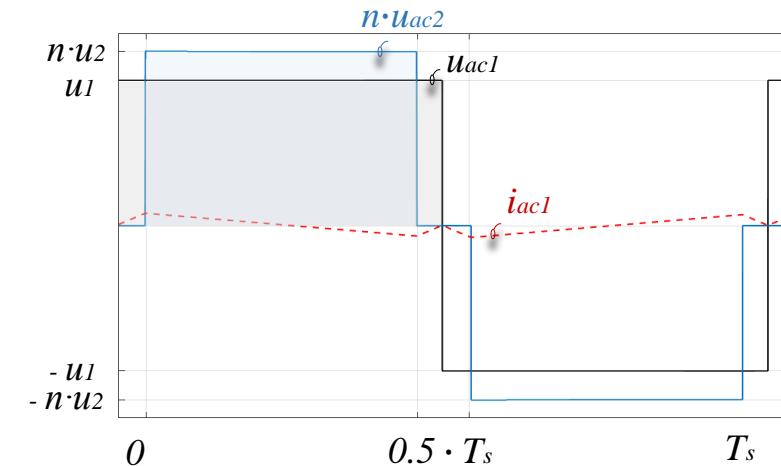

Operating Principle of the Two-Stage Charger System

► Simulation Results : DC-Link Voltage Transition

- VR + 4DABs

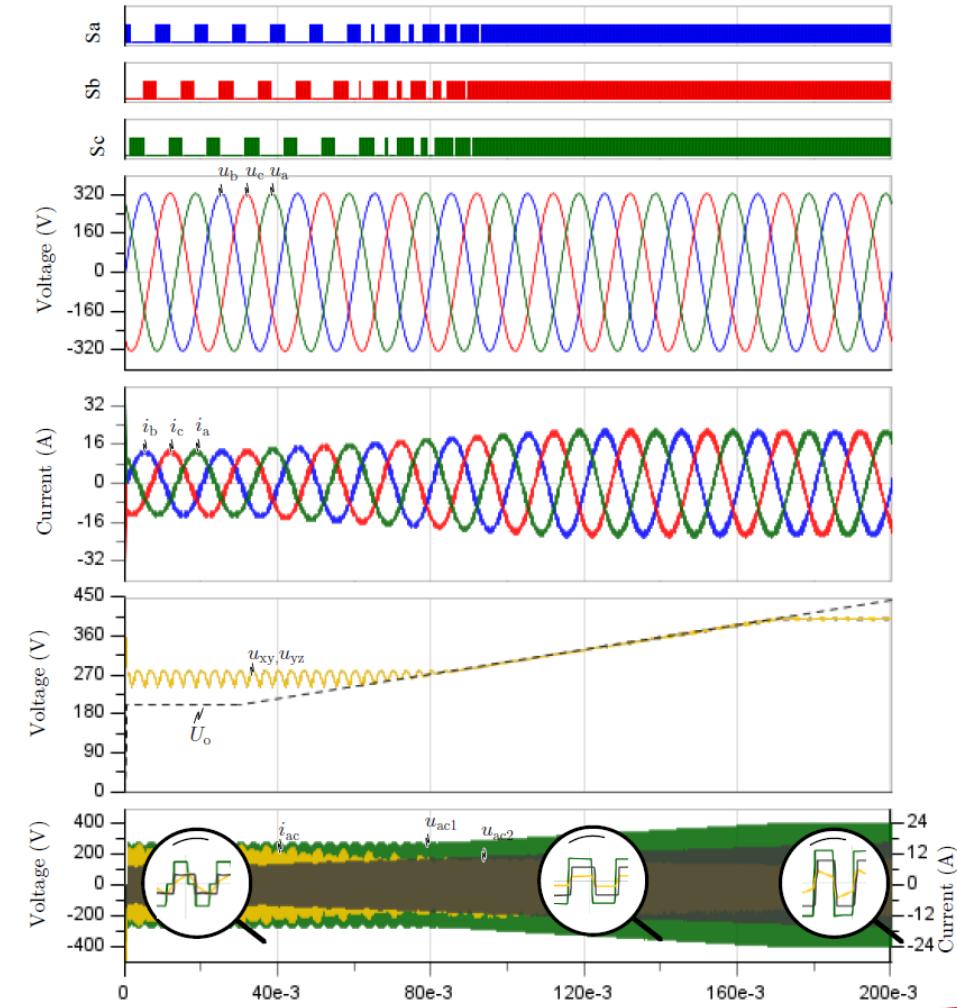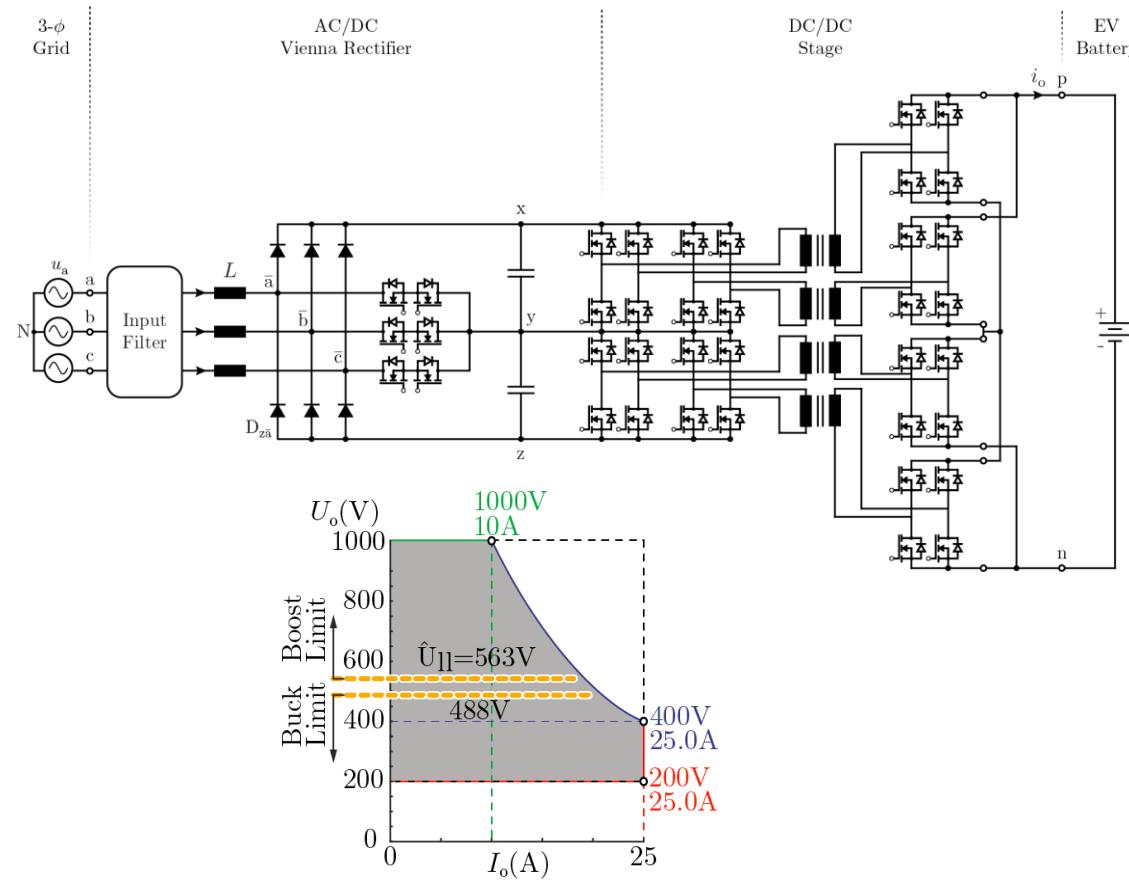

Firmware Structure

► Controller


- **Zynq®-7000 from Xilinx**
 - An FPGA + A dual core ARM® processor with peripherals
- SoC Module XC7Z020 from Trenz Electronic
- Custom designed development board
 - 16x external ADCs (AD7274 – 12 bits – 3MSPS)
 - Isolated UART communication
 - Debug interface



Trenz Electronic
SoC Module




Ad-hoc Custom
Control Board

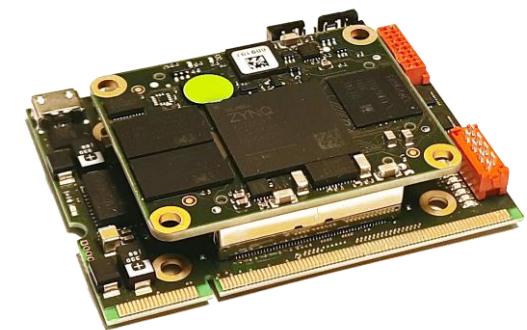

► Development Environment

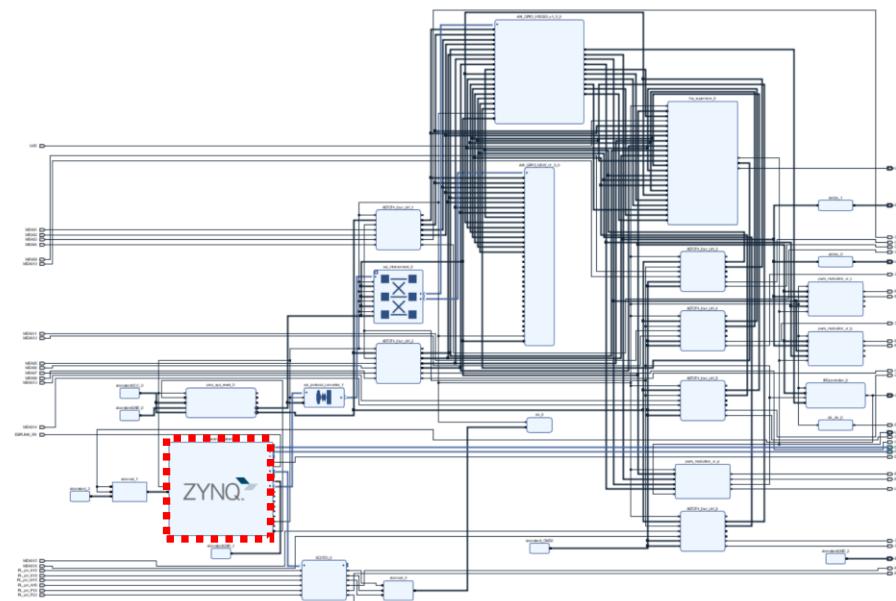
- **Vivado® Design Suite / IP Integrator**
 - Design environment for configuration of Processing system (DSP)
 - Hardware design for programmable logic (FPGA)
- **Software Development Kit (SDK)**
 - Software application / debugging



Firmware Structure

► Decoupled Control of VR & DAB

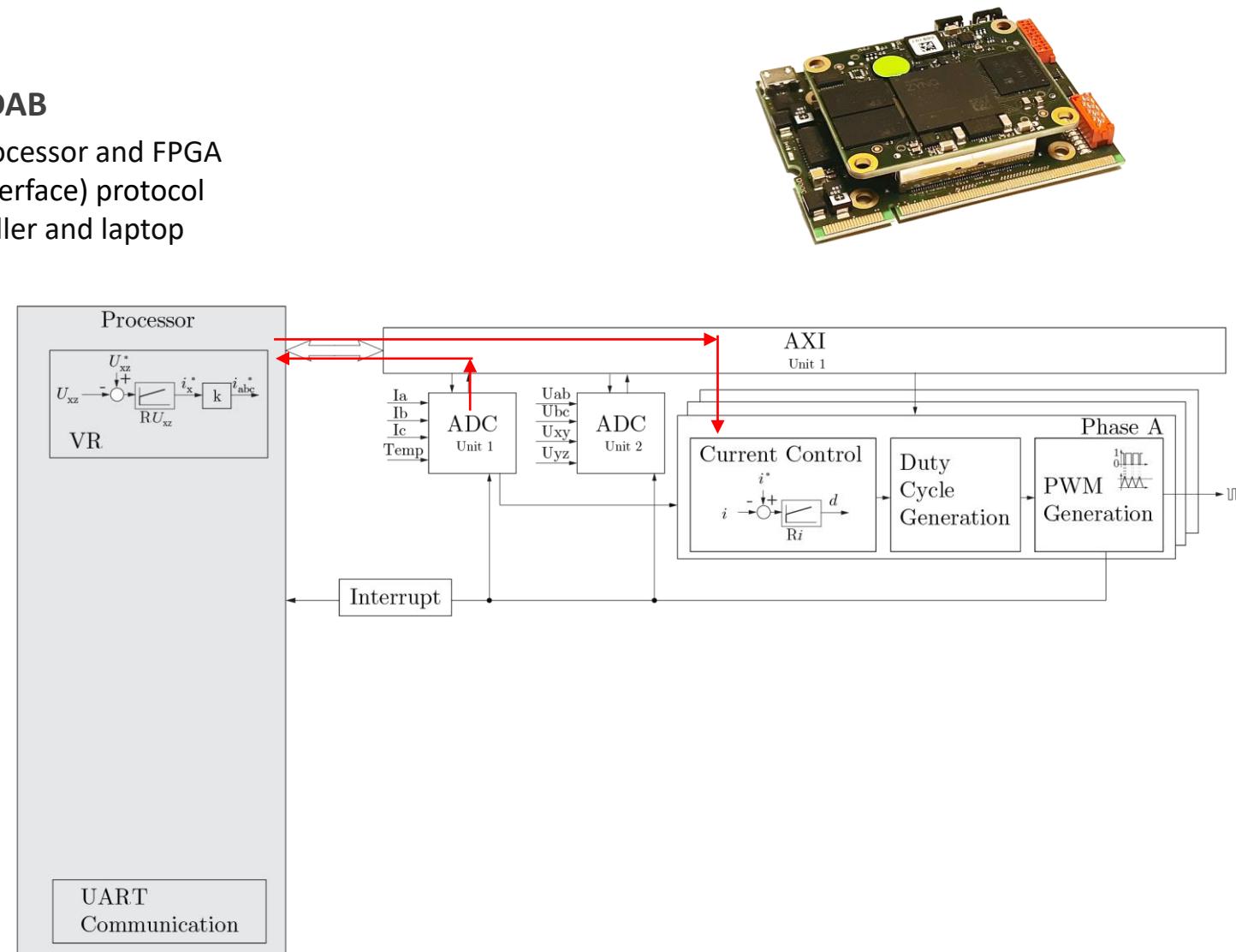
- Communication between the processor and FPGA
 - AXI (Advanced eXtensible Interface) protocol
- Communication between controller and laptop
 - UART
- VR
 - Output voltage control
 - 30kHz,
 - implemented in C
 - Input current Control
 - 560kHz
 - implemented in VHDL



Firmware Structure

► Decoupled Control of VR & DAB

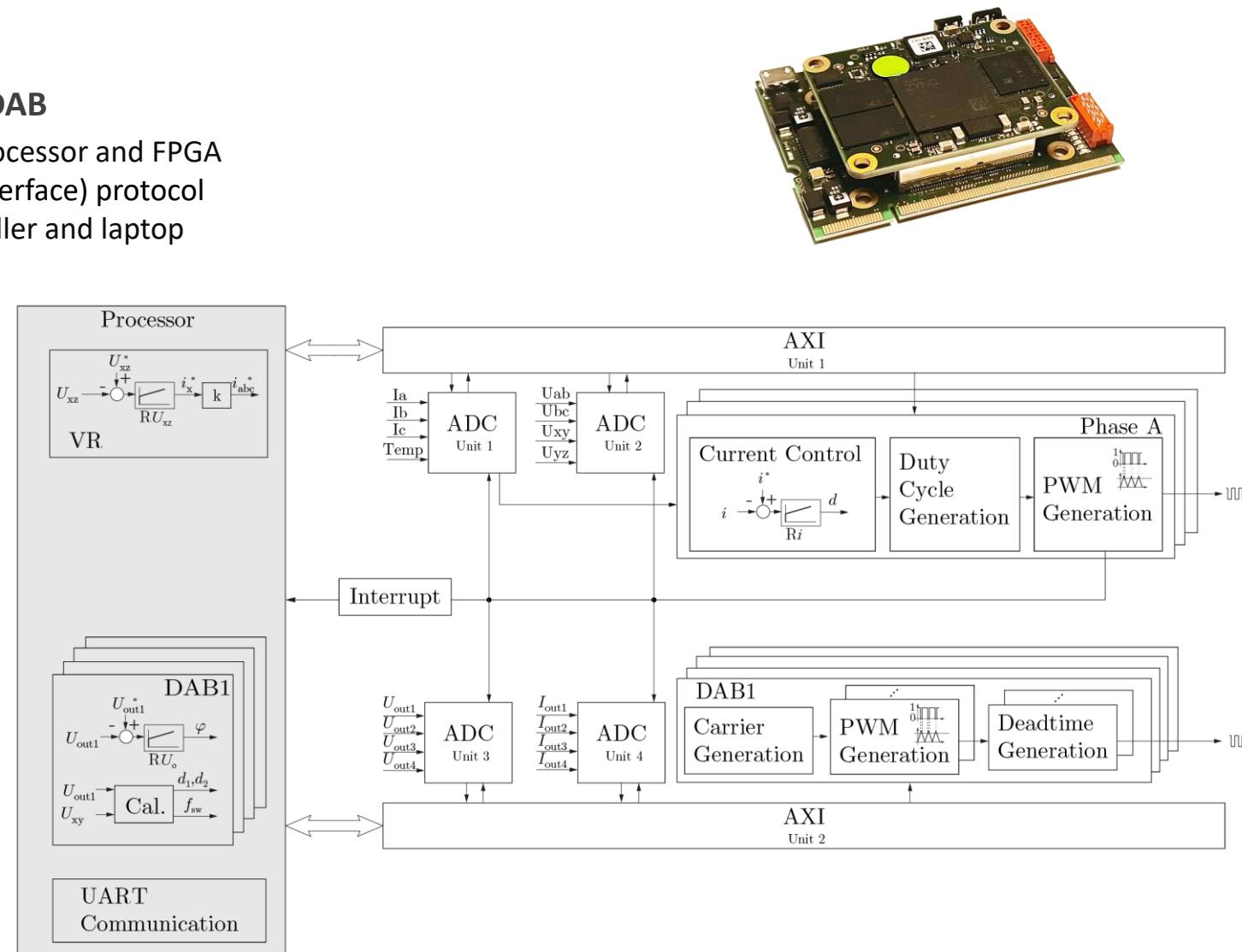
- Communication between the processor and FPGA
 - AXI (Advanced eXtensible Interface) protocol
- Communication between controller and laptop
 - UART
- VR
 - Output voltage control
 - 30kHz
 - implemented in C
 - Input current Control
 - 560kHz
 - implemented in VHDL
- DAB
 - Output voltage control
 - 30kHz
 - implemented in C



Firmware Structure


► Decoupled Control of VR & DAB

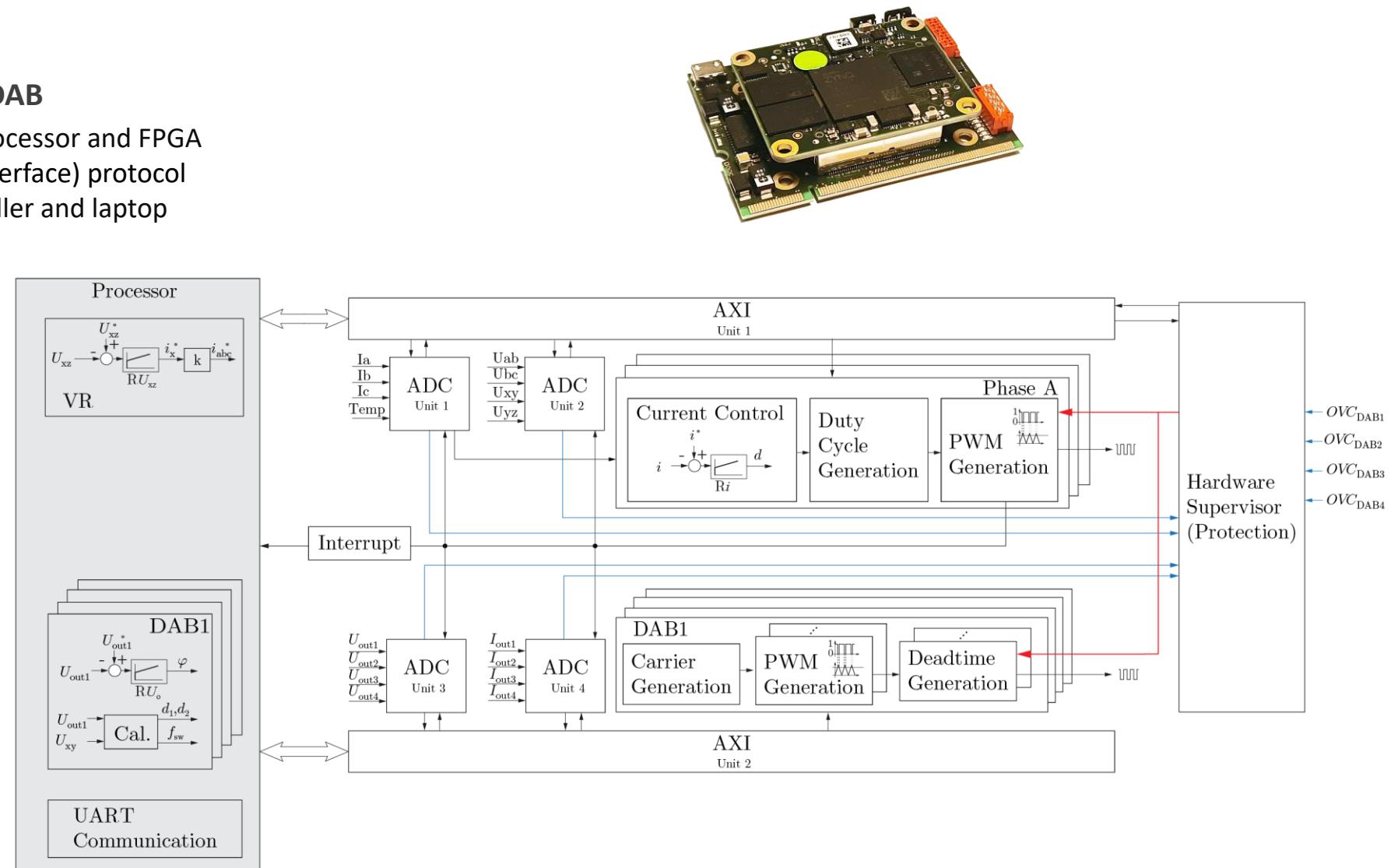- Communication between the processor and FPGA
 - AXI (Advanced eXtensible Interface) protocol
- Communication between controller and laptop
 - UART
- VR
 - Output voltage control
 - 30kHz
 - implemented in C
 - Input current Control
 - 560kHz
 - implemented in VHDL
- DAB
 - Output voltage control
 - 30kHz
 - implemented in C
- **Hardware Supervisor**
 - Protection




Measurements of the DAB Test System

► Topology & Specifications

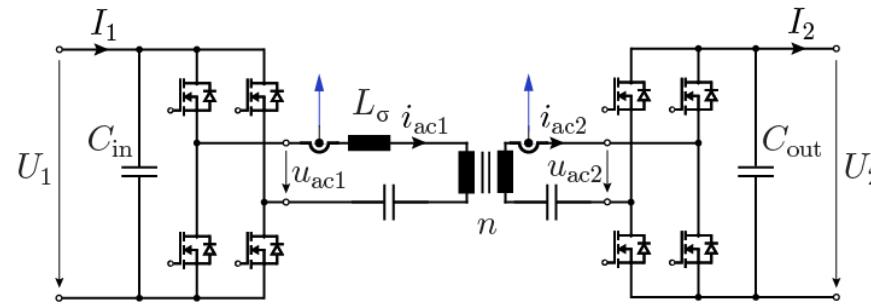

Parameters	Value
Rated Power	2.5 kW
Input Voltage Range	280-400 V _{dc}
Output Voltage Range	125-500 V _{dc}
Turns Ratio	16:10
Leakage Inductance	12uH
Switching Frequency	140kHz – 400kHz

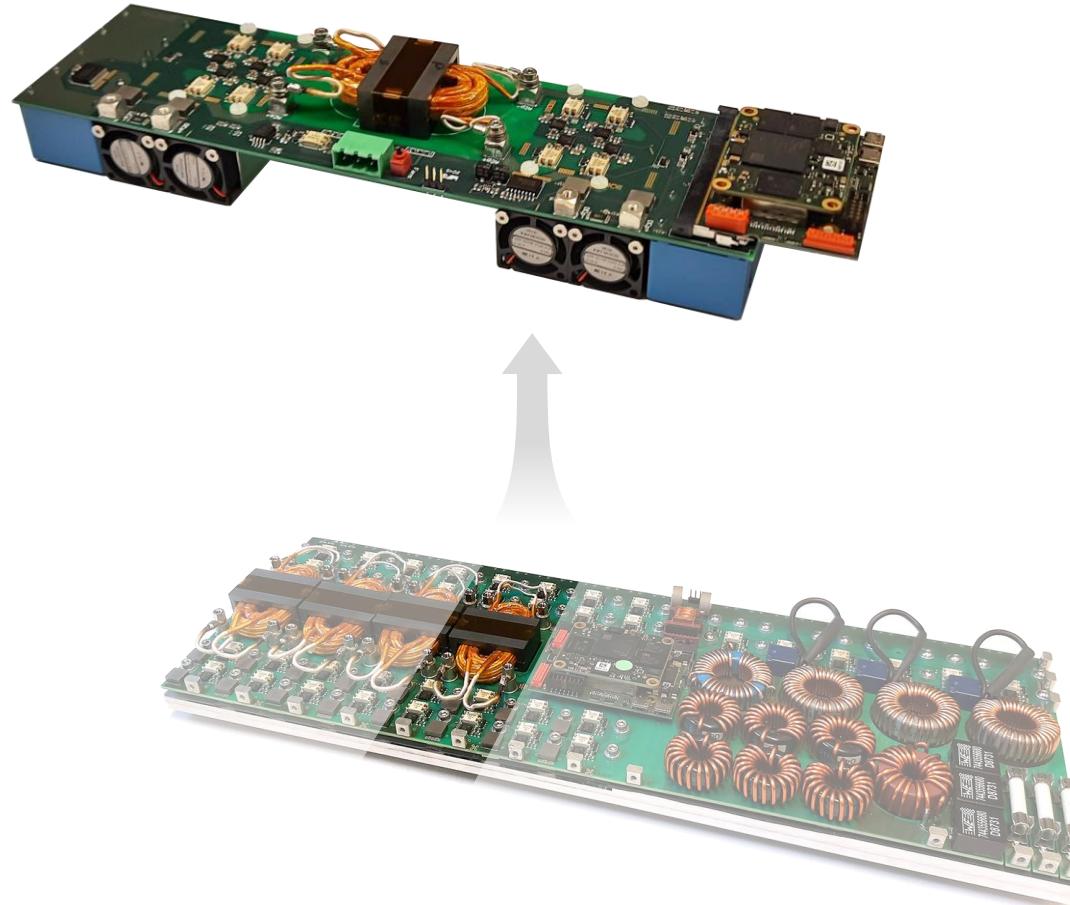

► Commissioning and Measurements



- Same components

Measurements of the DAB Test System

► Topology & Specifications

► Commissioning and Measurements

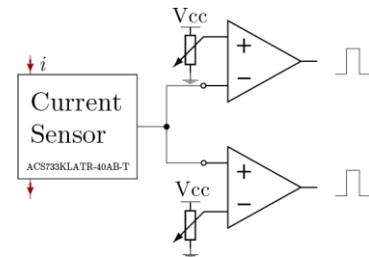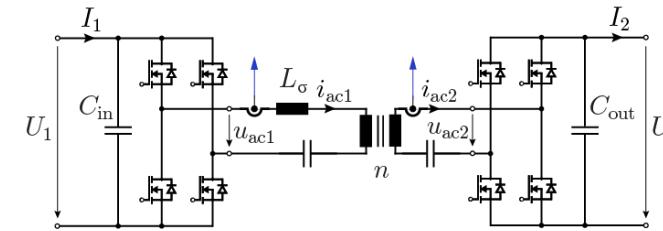- Protection Circuits
 - Current sensors + comparators -> digital signals to FPGA
 - Delay around 100-200ns: fast reaction





Measurements of the DAB Test System

► Topology & Specifications

► Commissioning and Measurements

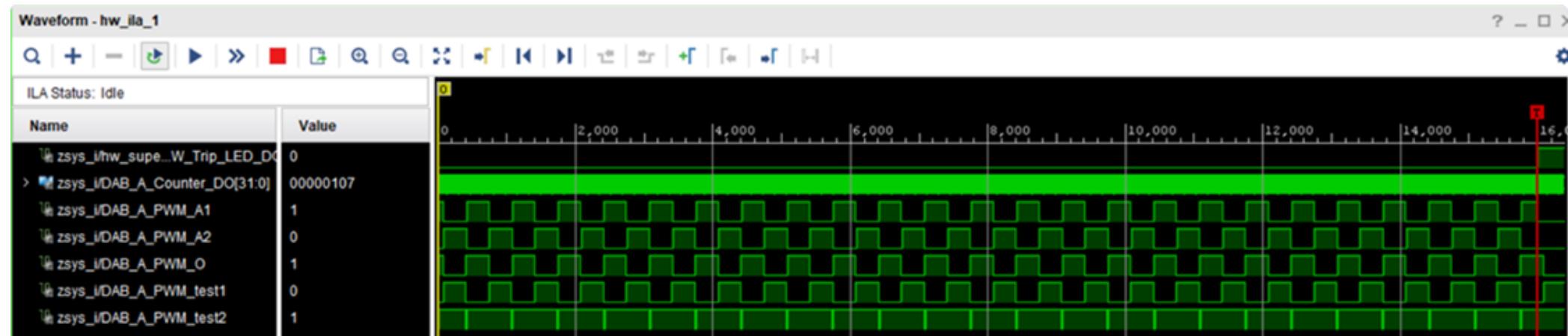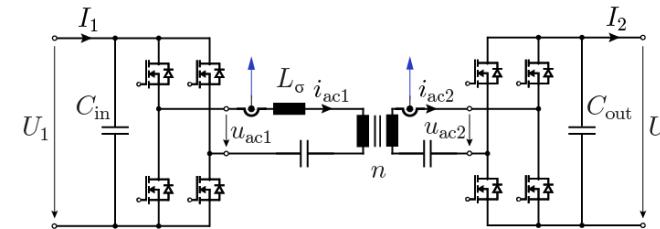- Protection Circuits
- Integrated Logic Analyzer(ILA Core) of the Zynq platform
 - Up 64 probes per block
 - Up to 4096 bits per probe





Measurements of the DAB Test System

► Topology & Specifications

► Commissioning and Measurements

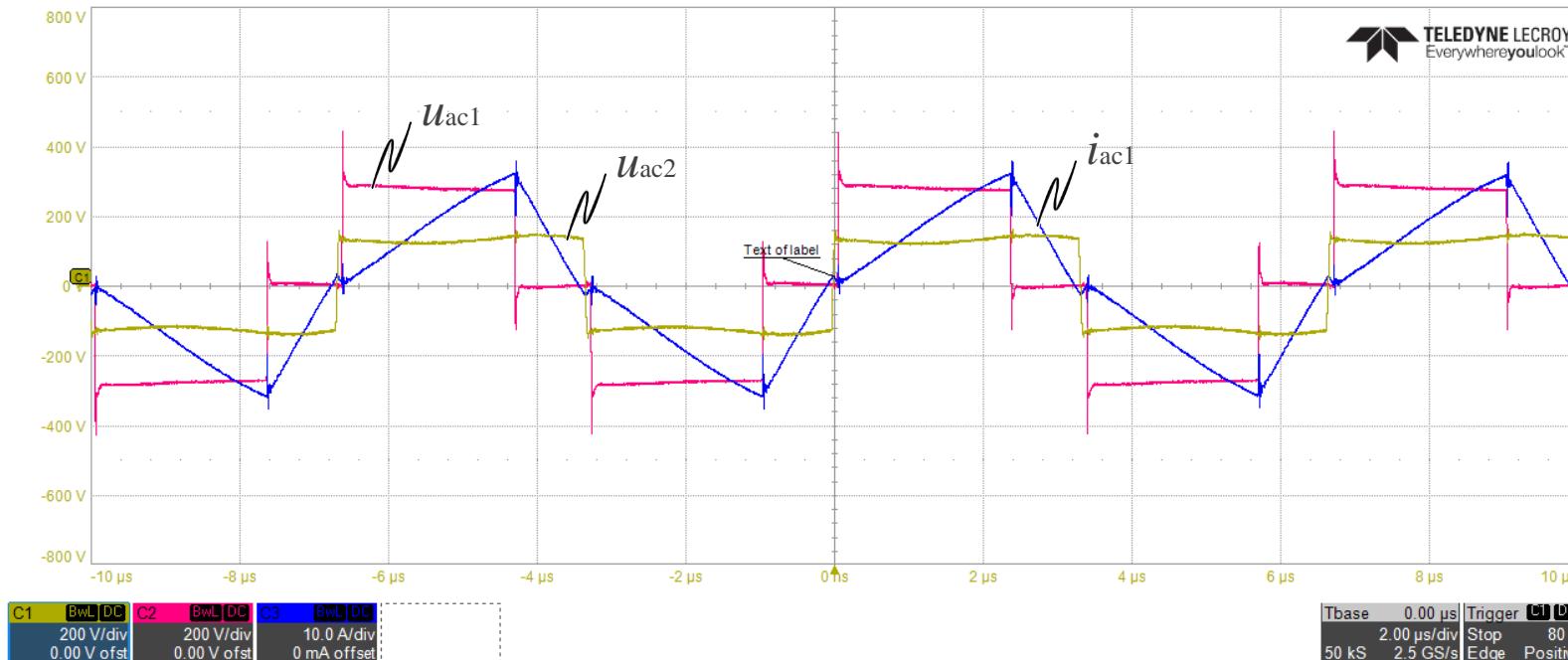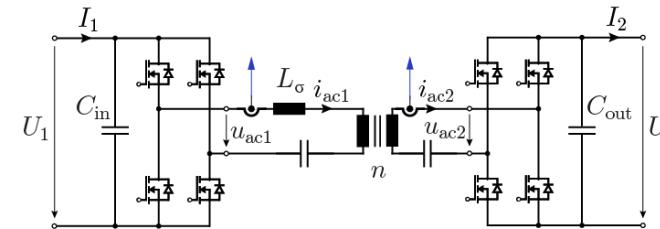- Protection Circuits
- Integrated Logic Analyzer(ILA Core) of the Zynq platform
- Waveforms
 - 125V out (280V in)
 - Soft switching of 3 half-bridges, hard-switching of 1 half-bridge





Measurements of the DAB Test System

► Topology & Specifications

► Commissioning and Measurements

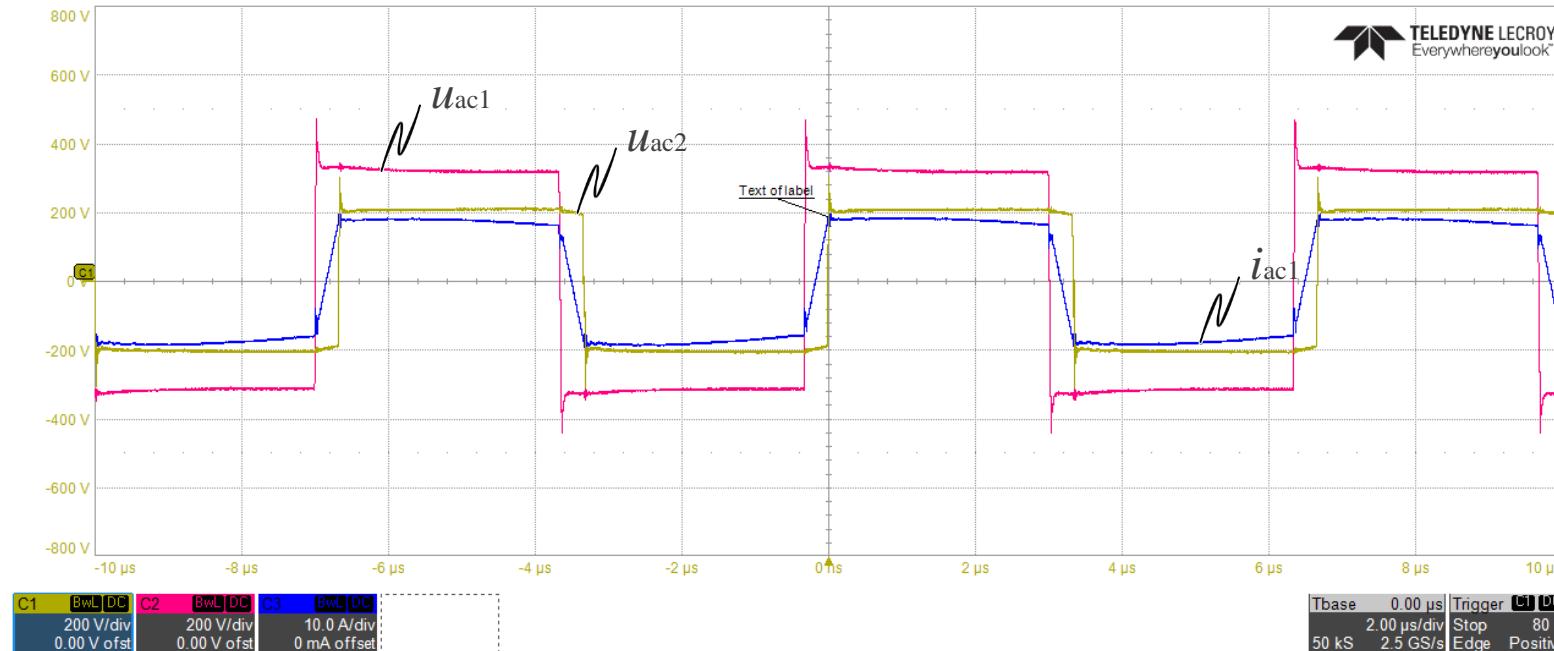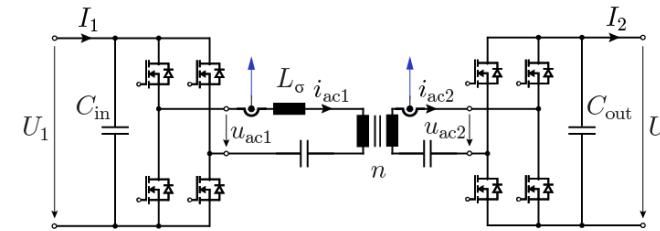- Protection Circuits
- Integrated Logic Analyzer(ILA Core) of the Zynq platform
- Waveforms
 - 125V out
 - 200V out(320V in)
 - Soft switching for all half-bridges





Measurements of the DAB Test System

► Topology & Specifications

► Commissioning and Measurements

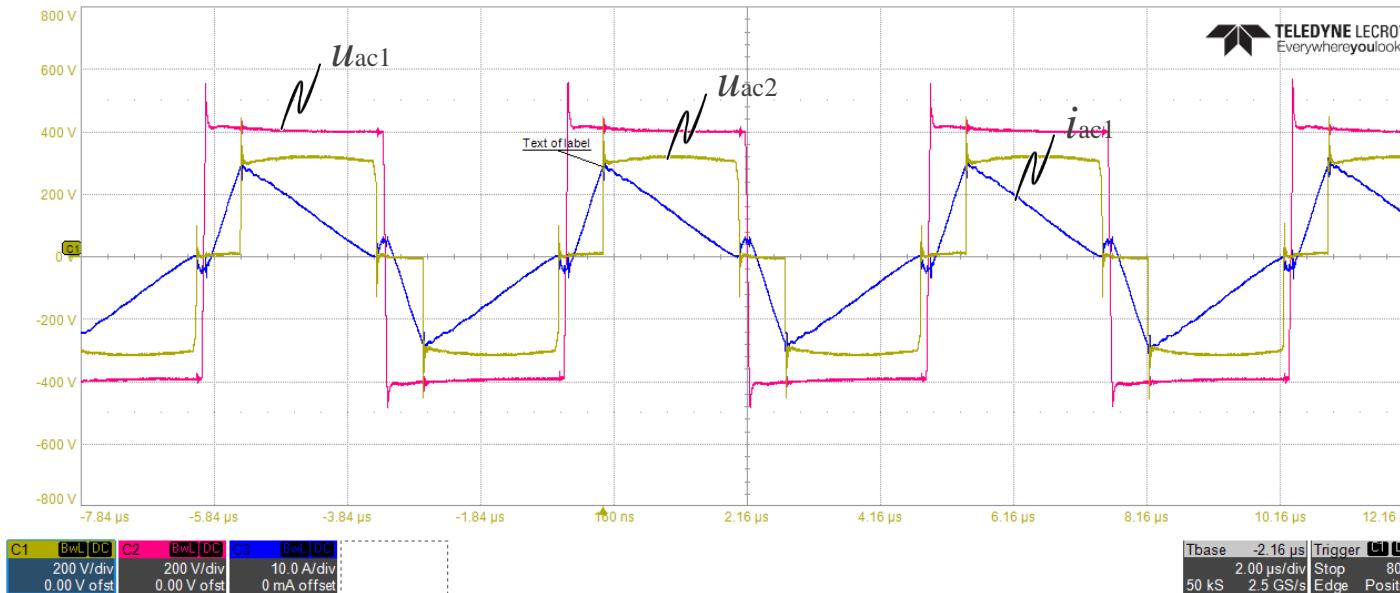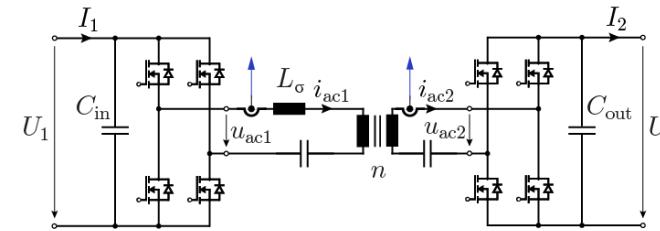- Protection Circuits
- Integrated Logic Analyzer(ILA Core) of the Zynq platform
- Waveforms
 - 125V out
 - 200V out
 - 300V out (400V in)
 - Soft switching of 3 half-bridges, hard-switching of 1 half-bridge





Measurements of the DAB Test System

► Topology & Specifications

► Commissioning and Measurements

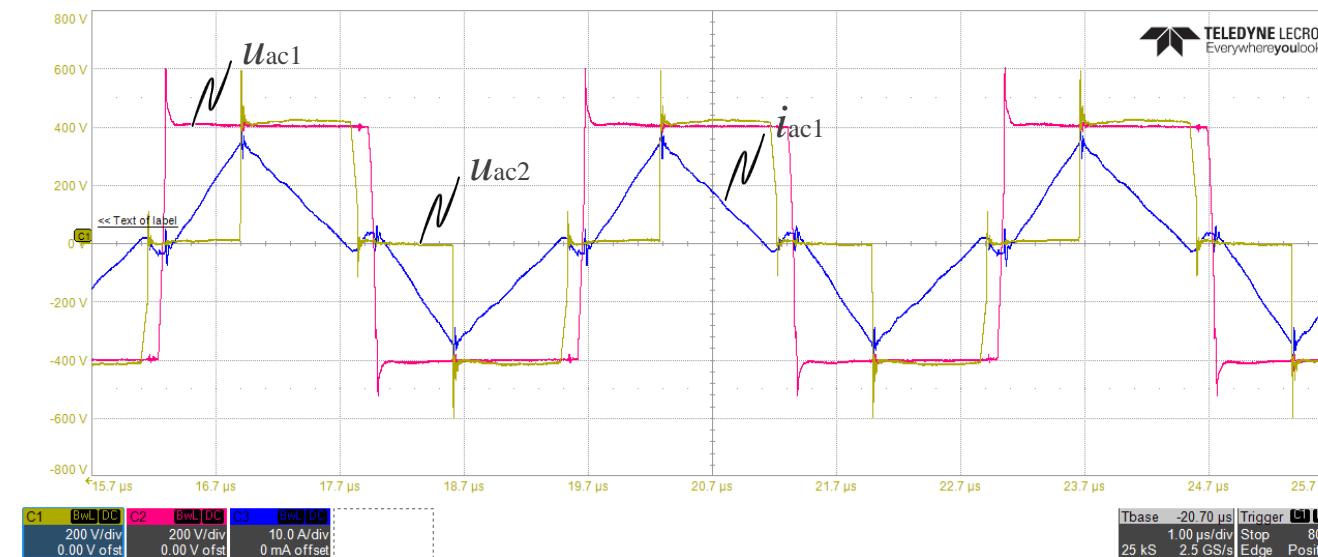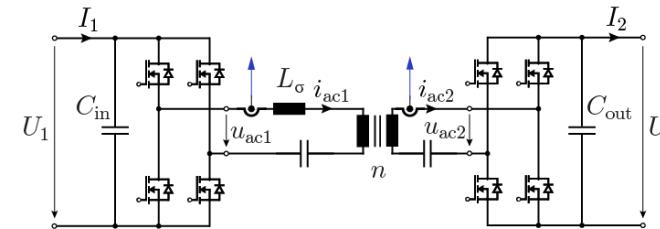- Protection Circuits
- Integrated Logic Analyzer(ILA Core) of the Zynq platform
- Waveforms
 - 125V out
 - 200V out
 - 300V out
 - 400V out (400V in)
 - Partial-soft switching of 3 half-bridges(considering RMS current), soft-switching of 1 half-bridge








Measurements of the DAB Test System

► Topology

► Specifications

► Commissioning and Measurements

- Protection Circuits
- Integrated Logic Analyzer(ILA Core) of Zynq platform
- Waveforms
- Transformer Design
 - **Litz wire**
 - Much higher R_{ac} due to integrated leakage inductance
 - **Foil windings**
 - In Parallel with the vertical magnetic field → lower losses
 - Easy cooling
 - **Non-idealities**
 - Wrinkles in the foils: eddy currents (vertically penetrating field)
 - Air gaps in the custom-made core.
 - Terminals
 - Extra air gaps to cancel the field: difficult to fix the windings in lab environment

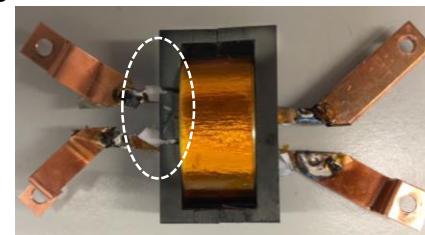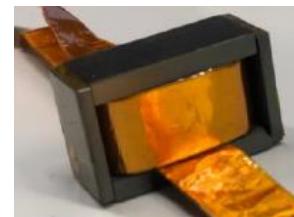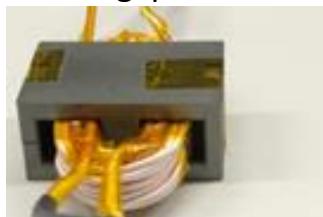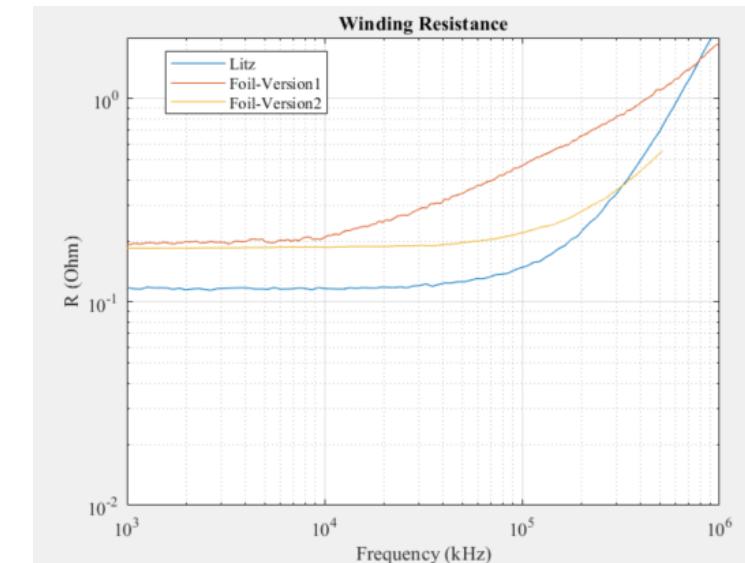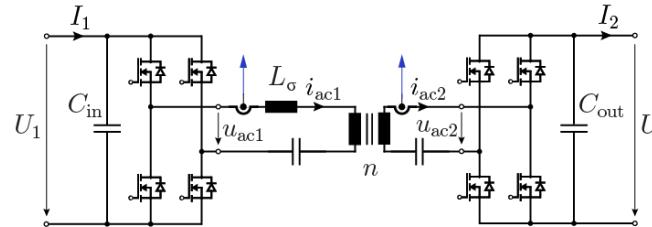





Measurements of the DAB Test System

► Topology

► Specifications

► Commissioning and Measurements

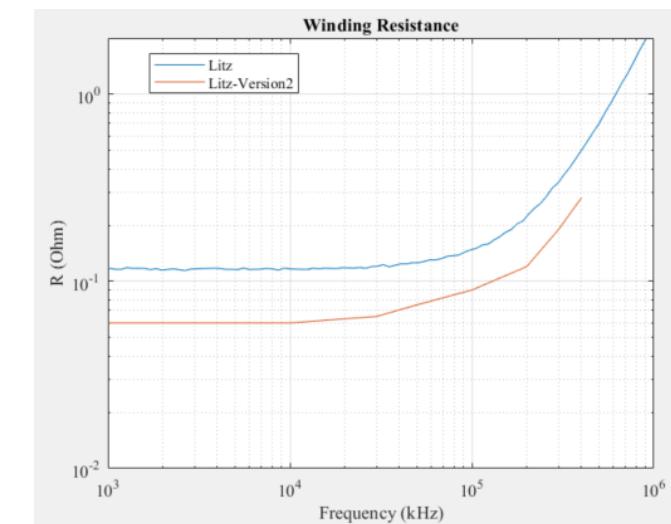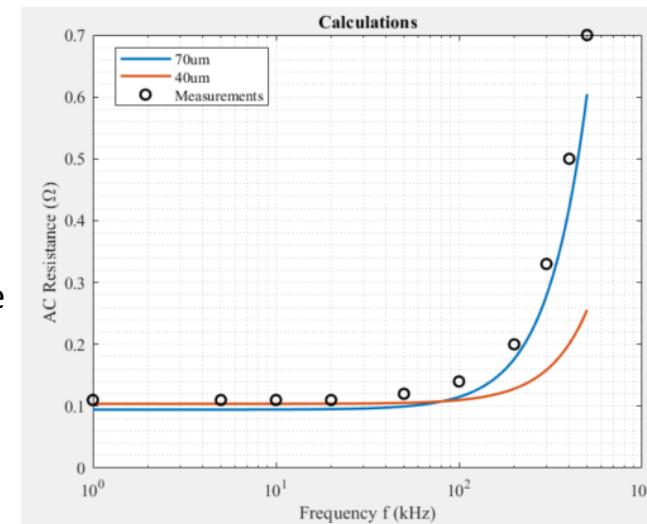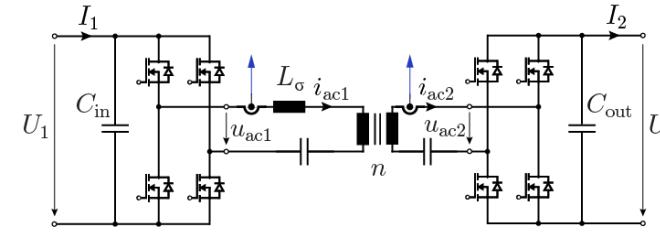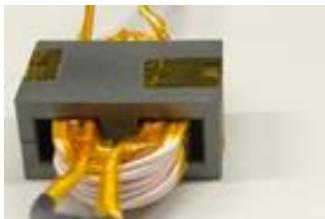- Protection Circuits
- Integrated Logic Analyzer(ILA Core) of Zynq platform
- Waveforms
- Transformer Design
 - Litz wire loss modeling: **70um Vs. 40um**, R_{ac} decrease
 - Fully utilized winding window → lower R_{dc}
 - Parallel windings
 - Further improvements with custom-made litz wire of the appropriate number of strands





Measurements of the DAB Test System

► Topology

► Specifications

► Commissioning and Measurements

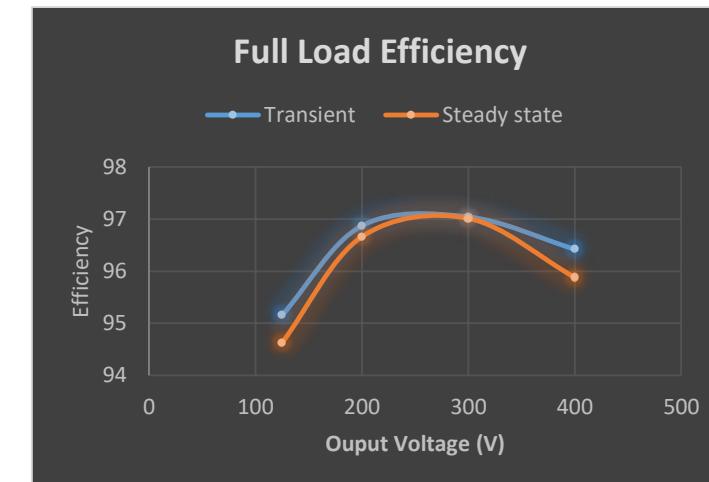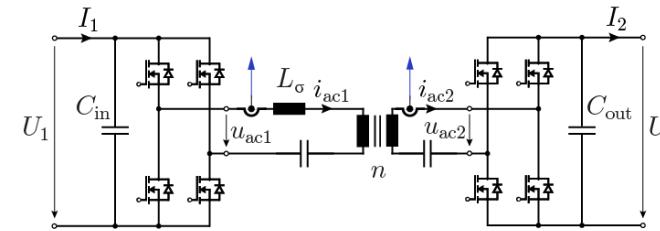- Protection Circuits
- Integrated Logic Analyzer(ILA Core) of Zynq platform
- Waveforms
- Transformer Design
- Efficiency measurements
 - Peak efficiency 97%
- Temperature measurements (NTCs)
 - Core Temperature $\leq 100^{\circ}\text{C}$, winding Temperature $\leq 80^{\circ}\text{C}$



Measurements of the 10kW Demonstrator System

► Topology


- Vienna Rectifier Front-end
- 4DAB: 2 in parallel, 2 in series both input/output

► Specifications

Parameters	Value
Rated Power	10 kW
Input Voltage Range	320-530 V _{rms}
Output Voltage Range	250-1000 V _{dc}
Power Density	10 kW/dm ³ (2x 20 kW/dm ³)
Size	400 x 140 x 18 mm ³
Efficiency (Target)	95 %
Switching Frequency	560kHz (VR) 140kHz – 400kHz (DAB)

► Semiconductors

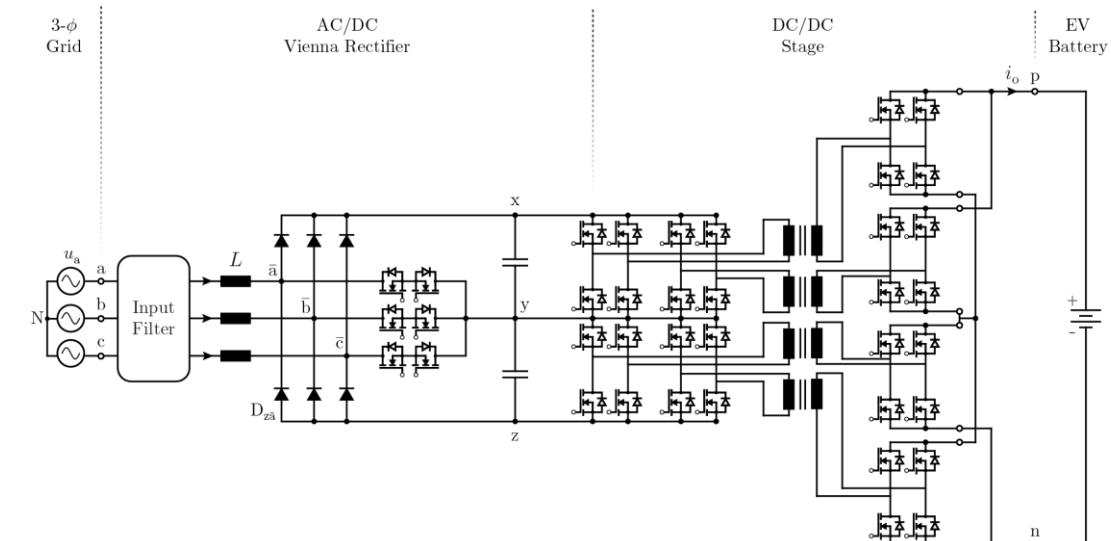- 600V GaN Switches (Infineon, IGOT60R070D1)
- 1200V SiC Schottky Diodes (Infineon, IDM10G120C5)



Measurements of the 10kW VR + DAB Demonstrator System

► Topology



- Vienna Rectifier Front-end
- 4DAB: 2 in parallel & series, both input/output

► Specifications

► Measurements of the VR

► Measurements of the DABs

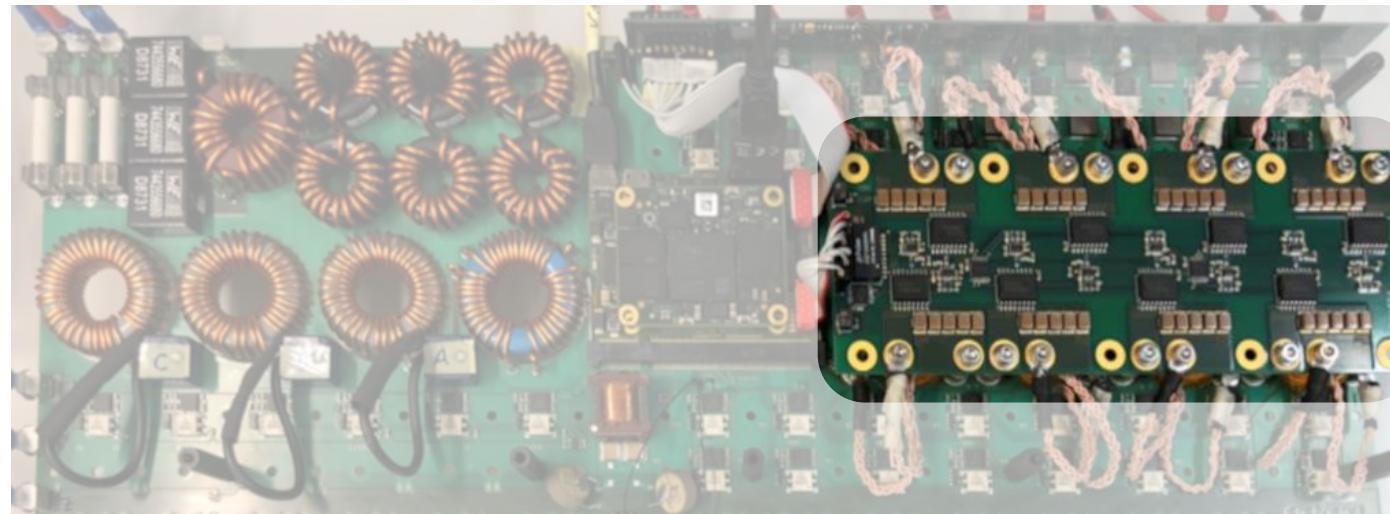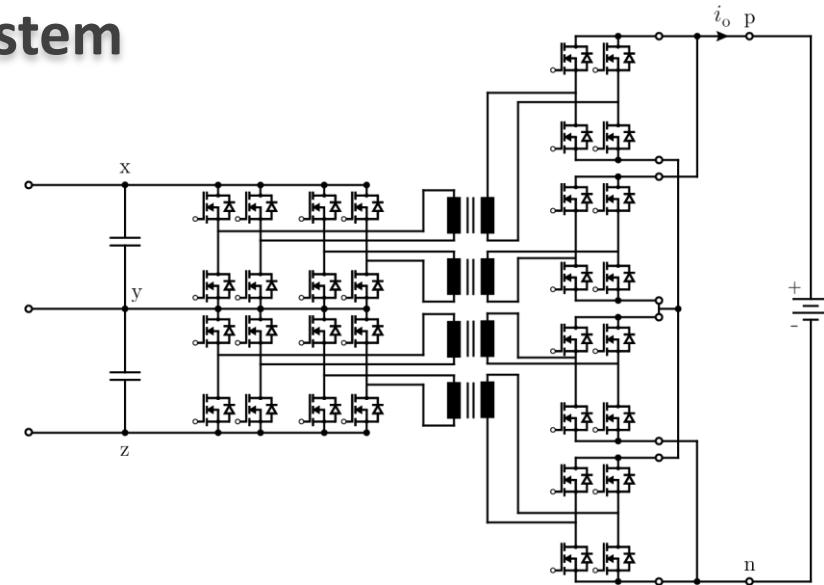- Protection board
 - 4 channels for each DAB, both primary & secondary sides



Measurements of the 10kW VR + DAB Demonstrator System

► Topology

- Vienna Rectifier Front-end
- 4DAB: 2 in parallel & series, both input/output




► Specifications

► Measurements of the VR

► Measurements of the DABs

- Protection board
- Efficiency measurements of 4 individual modules
 - Transformer terminals close to PCB traces → magnetic field & eddy currents
 - Layout

Full Load Efficiency

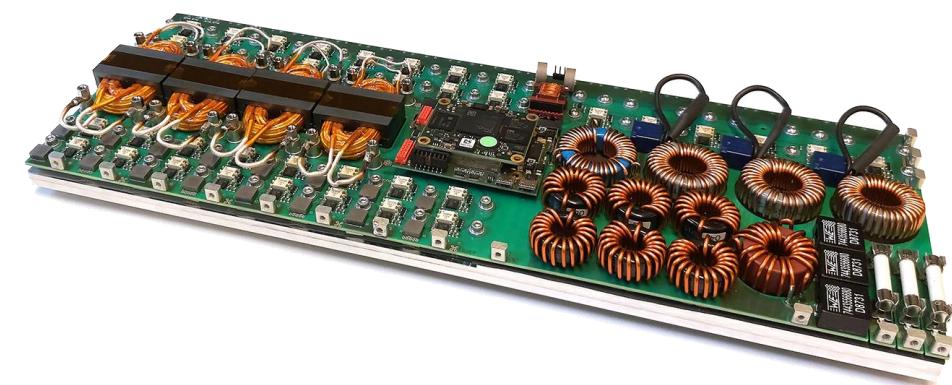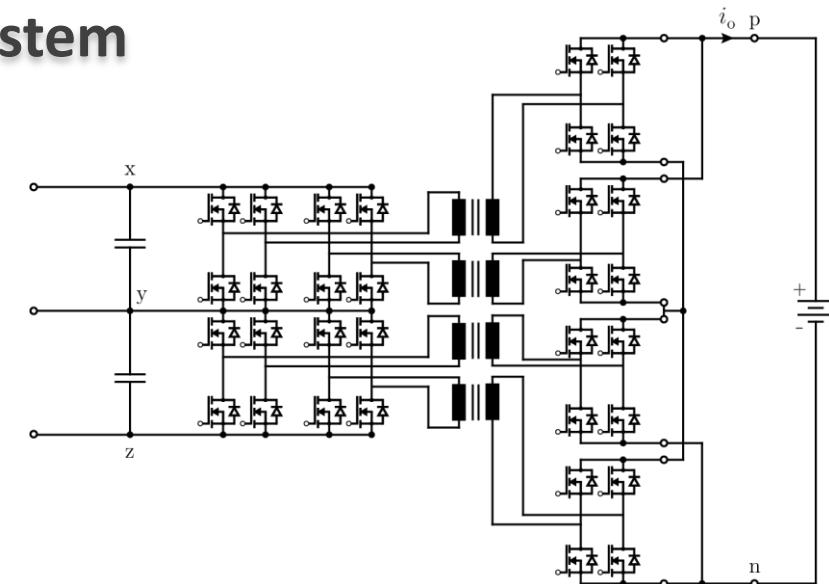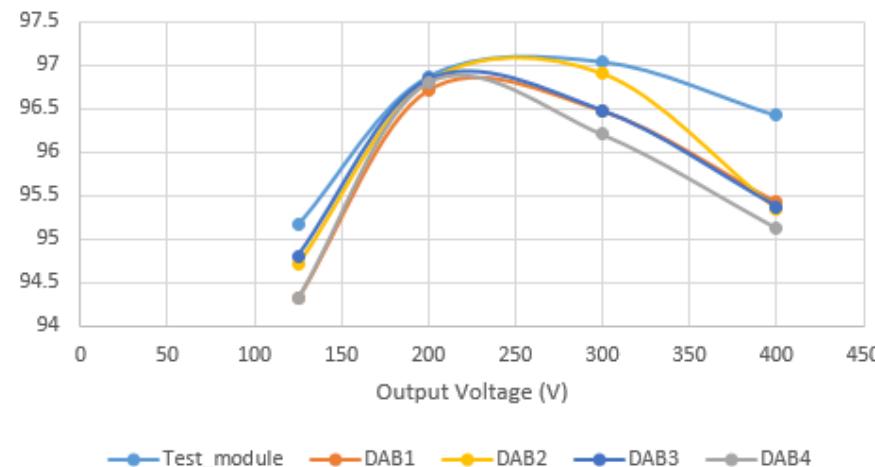

Measurements of the 10kW VR + DAB Demonstrator System

► Topology



- Vienna Rectifier Front-end
- 4DABs: 2 in parallel & series, both input/output

► Specifications

► Measurements of the VR

► Measurements of the DABs

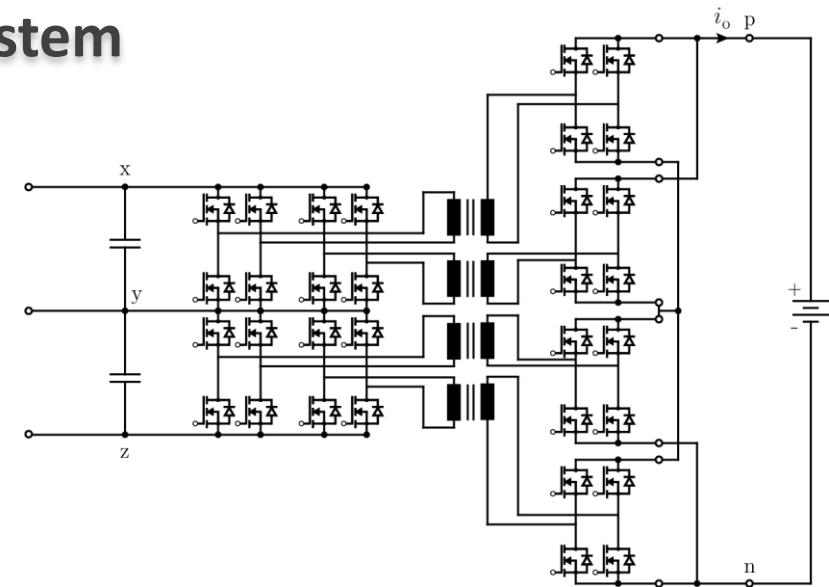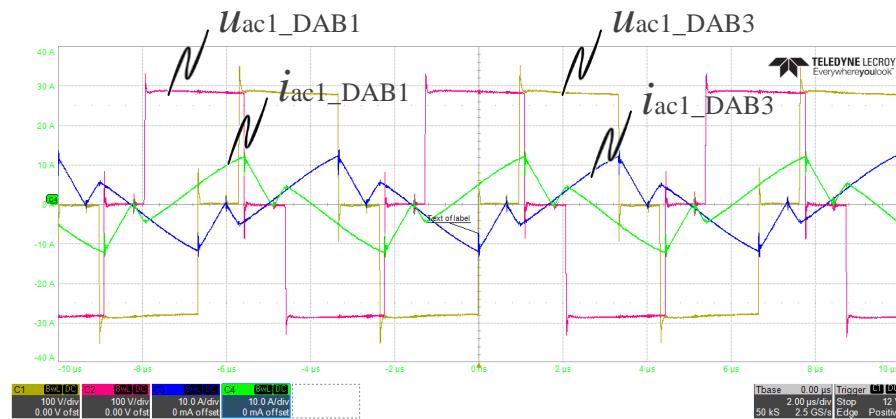- Protection board
- Efficiency measurements of 4 individual modules
- Operation of 2 modules (125V out)
 - Input in series, output in parallel
 - Balanced currents
 - Random phase-shift: possible to be synchronized to minimize output voltage ripples



Measurements of the 10kW VR + DAB Demonstrator System




► Topology

- Vienna Rectifier Front-end
- 4DABs: 2 in parallel, 2 in series both input/output

► Specifications

► Measurements of the VR

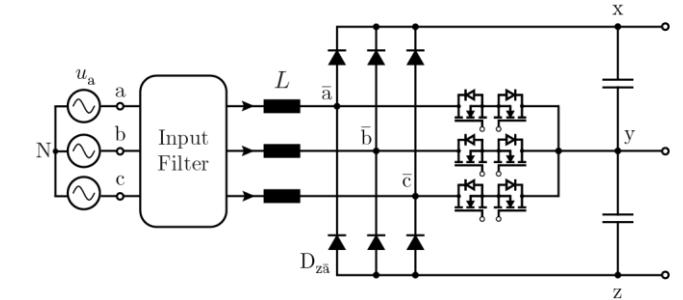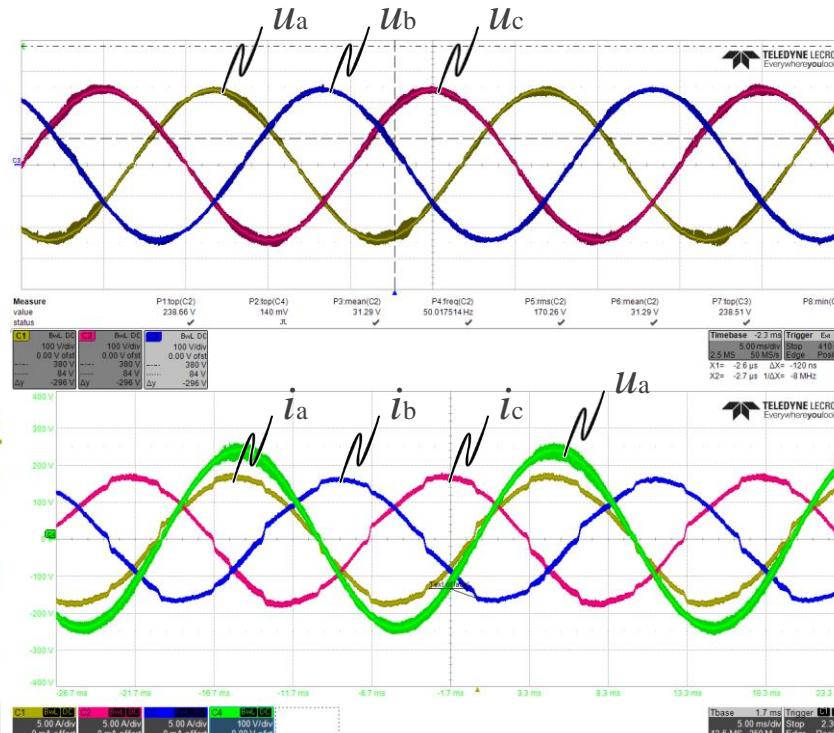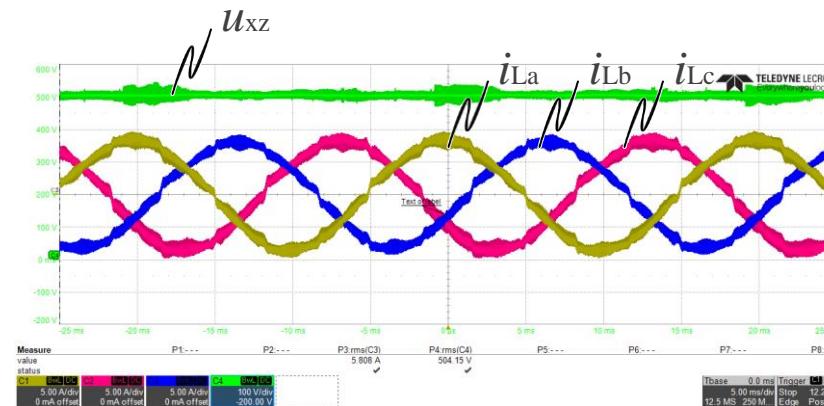- 500V DC link voltage, 3kW
- Three-phase sinusoidal input currents Vs. voltages
- THD: 5.37%
- Currents in the boost inductors



Measurements of the 10kW VR + DAB Demonstrator System




► Topology

- Vienna Rectifier Front-end
- 4DABs: 2 in parallel & series, both input/output

► Specifications

► Measurements of the VR

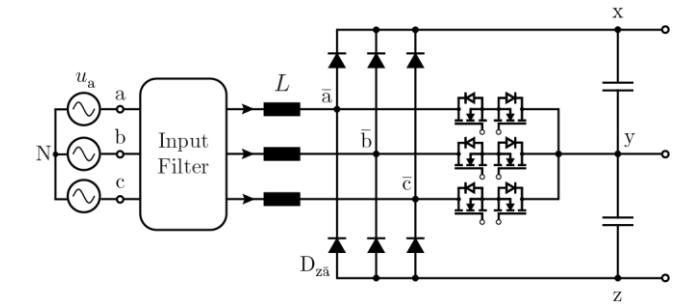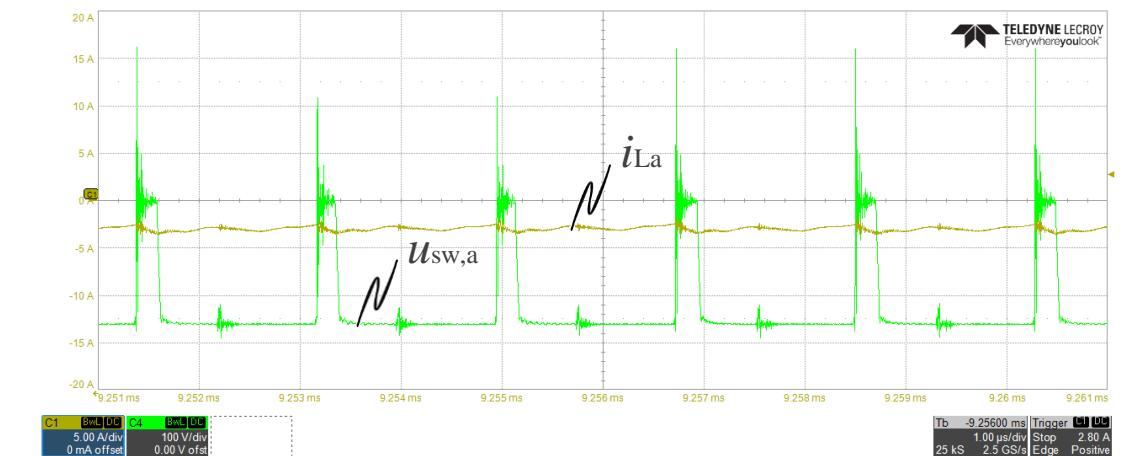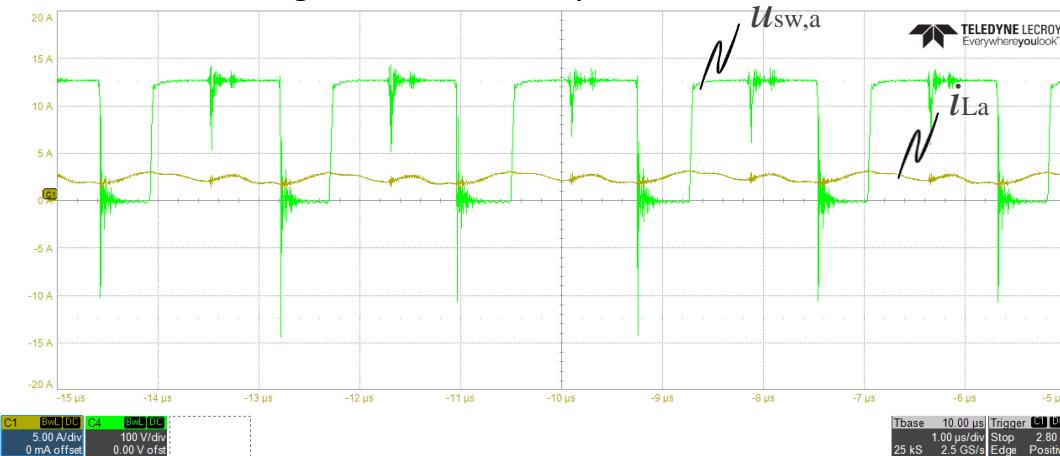- 500V DC link voltage, 3kW
- Three-phase sinusoidal input currents Vs. voltages
- THD: 5.37%
- Currents in the boost inductors
- Switching node voltages
 - Positive & negative half mains cycle



Measurements of the 10kW VR + DAB Demonstrator System



► Topology

- Vienna Rectifier Front-end
- 4DABs: 2 in parallel & series, both input/output

► Specifications

► Measurements of the VR

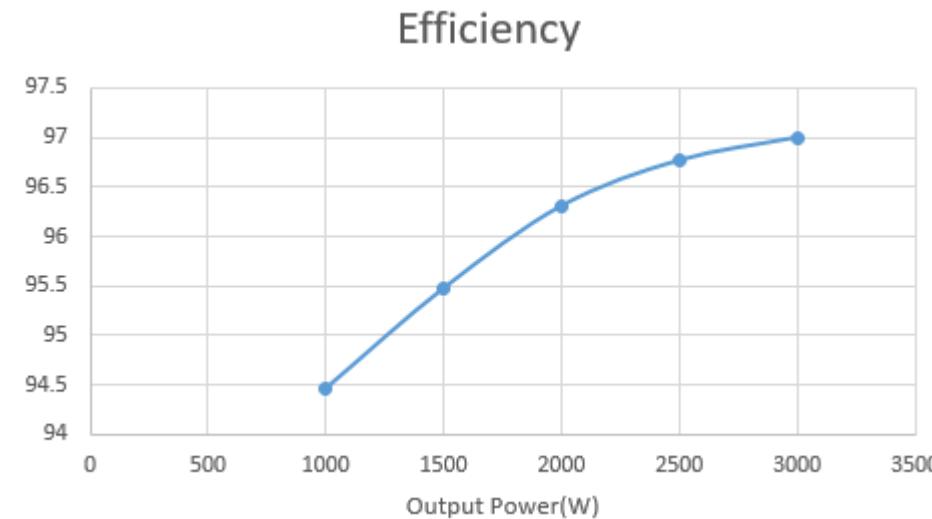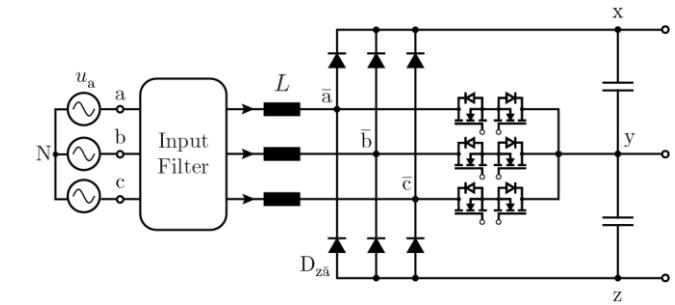- 500V DC link voltage, 3kW
- Three-phase sinusoidal input currents Vs. voltages
- THD: 5.37%
- Currents in the boost inductors
- Efficiency measurements (Yokogawa 3000WT, 500V)
- 700V, 5kW, 97%
- Higher Efficiencies expected for full-load
- Further improvement with 1/3 modulation



Measurements of the 10kW VR + DAB Demonstrator System

► Topology




- Vienna Rectifier Front-end
- 4DABs: 2 in parallel & series, both input/output

► Specifications

► Measurements of the VR

► Measurements of the DABs

► Measurements of the VR + 2xDABs

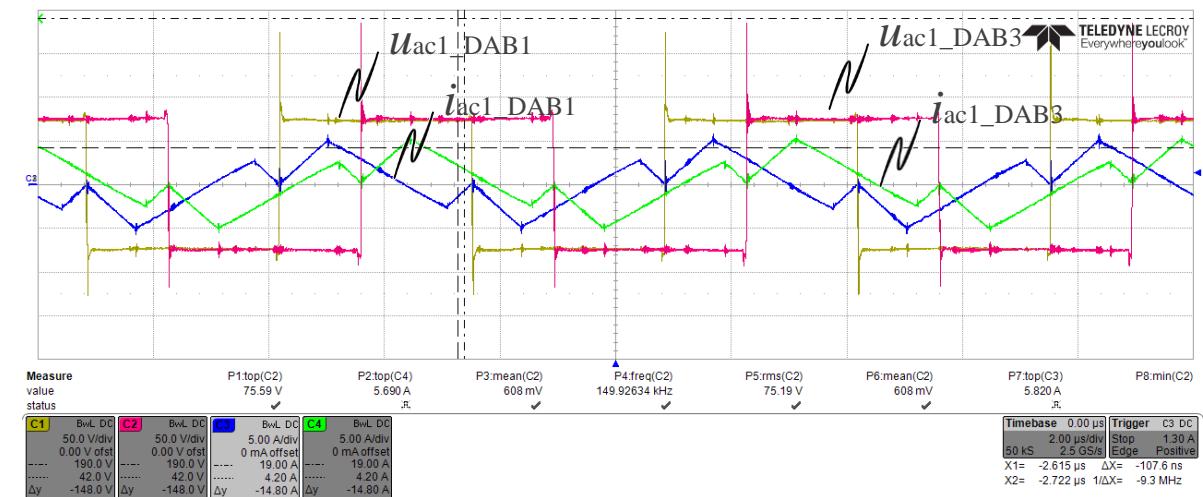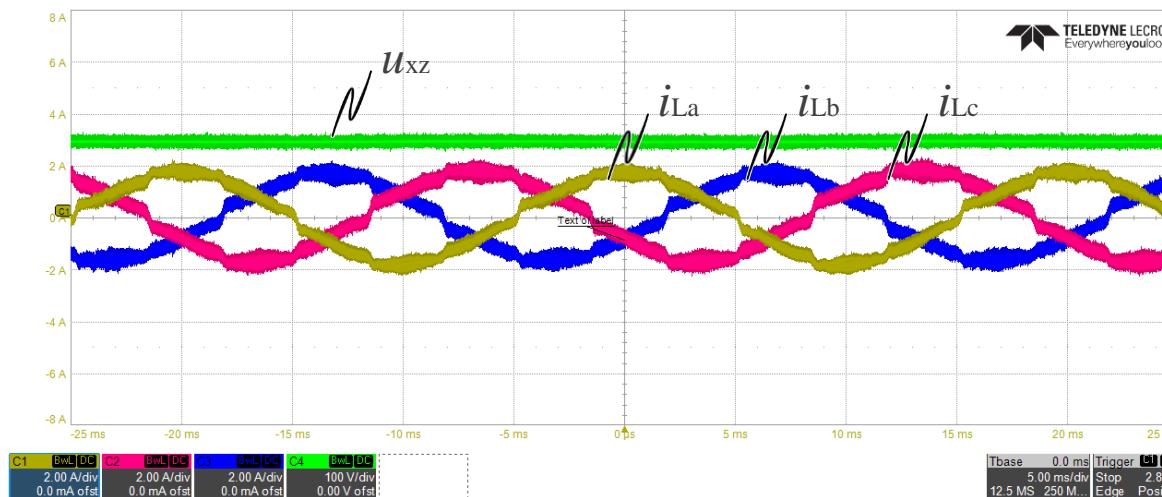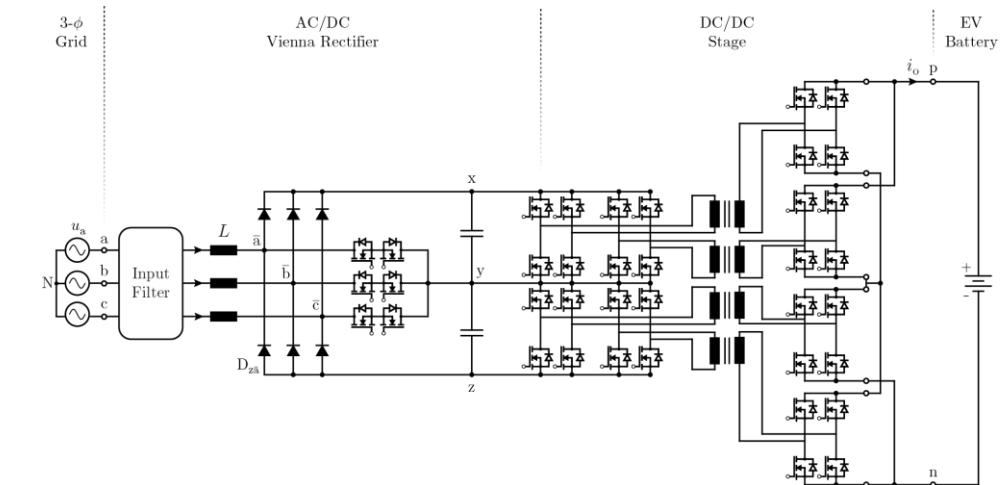

Measurements of the 10kW VR + DAB Demonstrator System

► Topology

- Vienna Rectifier Front-end
- 4DABs: 2 in parallel & series, both input/output

► Specifications

► Measurements of the VR


► Measurements of the DABs

► Measurements of the VR + 2xDABs

- Missing Pulses at higher voltages

► Next Steps

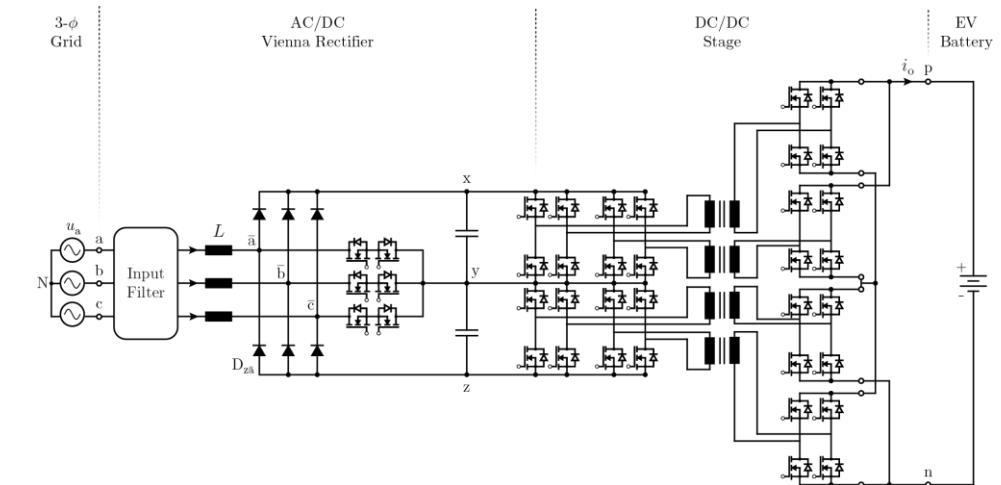- Test VR at higher voltages & power
- Looking into the missing-pulse problem
- Possible redesign of the system



Conclusions and Takeaways

- ▶ Proposed Solutions for EV Charger: 1/3 VIENNA Rectifier + Isolated DC/DC Converter
- ▶ Principle Verification
- ▶ Firmware Implementation
- ▶ Protection Circuits for Complex Systems
- ▶ Transformer Design
- ▶ Commissioning of the Isolated DC/DC Stage: Test System
- ▶ Commissioning of the Isolated DC/DC Stage: 4 Individual Modules
- ▶ Commissioning of the VR
- ▶ Combination Operation of Both Stages: in Progress
- ▶ Noise Suppression in Layout Design



Thank You !

