

# Google Little-Box Reloaded

Advances In Ultra-Compact GaN  
Based Single-Phase DC/AC Power Conversion



**Dominik Neumayr**



Swiss Federal Institute of Technology (ETH) Zurich  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)



# Google Little-Box Reloaded

Advances In Ultra-Compact GaN  
Based Single-Phase DC/AC Power Conversion



**D. Neumayr, D. Bortis, M. Guacci, J. Azurza, J. W. Kolar**



Swiss Federal Institute of Technology (ETH) Zurich  
Power Electronic Systems Laboratory  
[www.pes.ee.ethz.ch](http://www.pes.ee.ethz.ch)



# Outline

- ▶ **Google Little Box Challenge**
  - ▶ *Requirements*
  - ▶ *Little Box 1.0*
- ▶ **Further Analysis & New Approach**
  - ▶ *New Circuit Topology*
  - ▶ *Adv. Measurement Techniques*
  - ▶ *Little Box 2.0*
- ▶ **Conclusions**




Acknowledgement

M. Kasper  
O. Knecht  
F. Krismer
 
# Google Little Box Challenge

Requirements  
Little Box 1.0  
Other Finalists







# LITTLE BOX CHALLENGE

Google | IEEE

 - Design / Build the 2kW 1- $\Phi$  Solar Inverter with the Highest Power Density in the World
- Power Density  $> 3\text{ kW/dm}^3$  ( $50\text{ W/in}^3$ )
- Efficiency  $> 95\%$
- Case Temp.  $< 60^\circ\text{C}$
- EMI FCC Part 15 B



 ■ Push the Forefront of New Technologies in R&D of High Power Density Inverters



## The Grand Prize

- Highest Power Density ( $> 50\text{W}/\text{in}^3$ )
- Highest Level of Innovation



**\$1,000,000**



### ■ Timeline

- Challenge Announced in Summer 2014
- **2000+ Teams Registered** Worldwide
- 100+ Teams Submitted a Technical Description until July 22, 2015
- **18 Finalists (3 No-Shows)**



 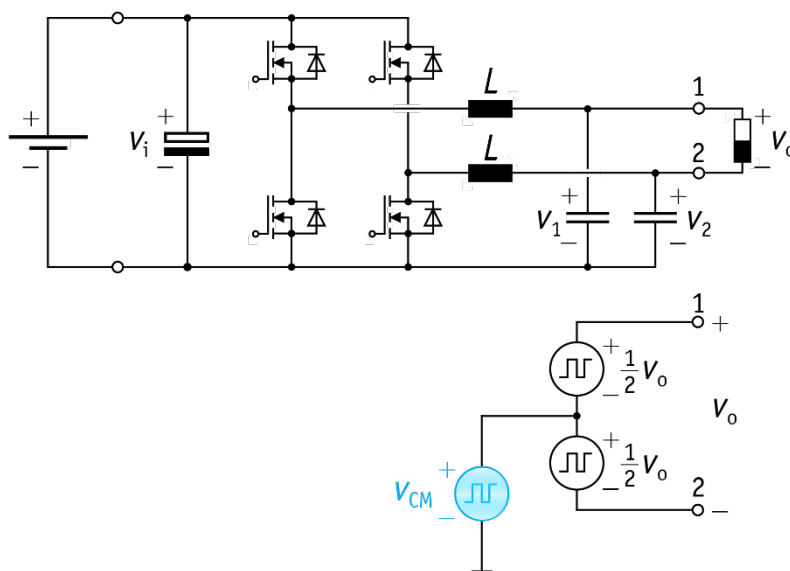
## Selected Converter Topology

- Full-Bridge Output Stage
- Modulation of Both Bridge Legs





 - DM Component of  $u_1$  and  $u_2$  Defines Output Voltage  $u_o$
- No Low-Frequency CM Component of  $u_1$  and  $u_2$  (Different to e.g. 1- $\Phi$  PFC Rectifier Systems !)


 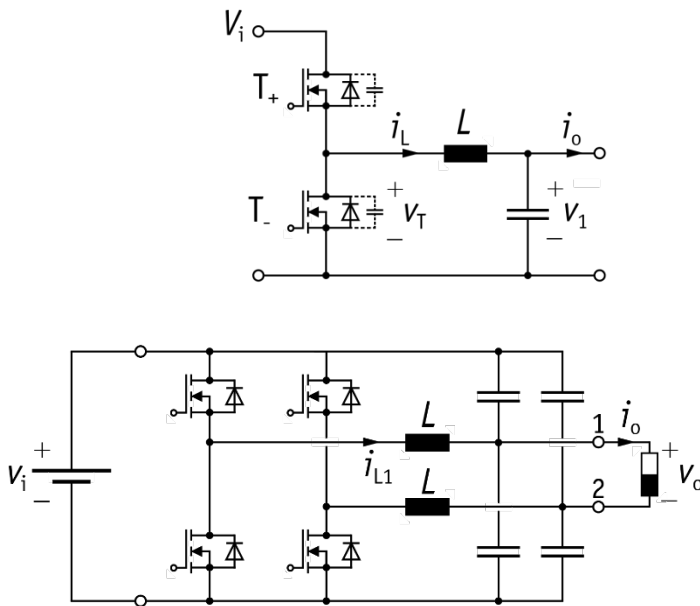
# Triangular Current Mode (TCM) ZVS Operation

- TCM Operation for Resonant Voltage Transition @ Turn-On/Turn-Off






- Requires Only Measurement of **Current Zero Crossings,  $i = 0$**
- High  $f_s$  Around  $i = 0$  Challenging for Digital Control
- Variable Sw. Freq.  $f_s$  Lowers EMI



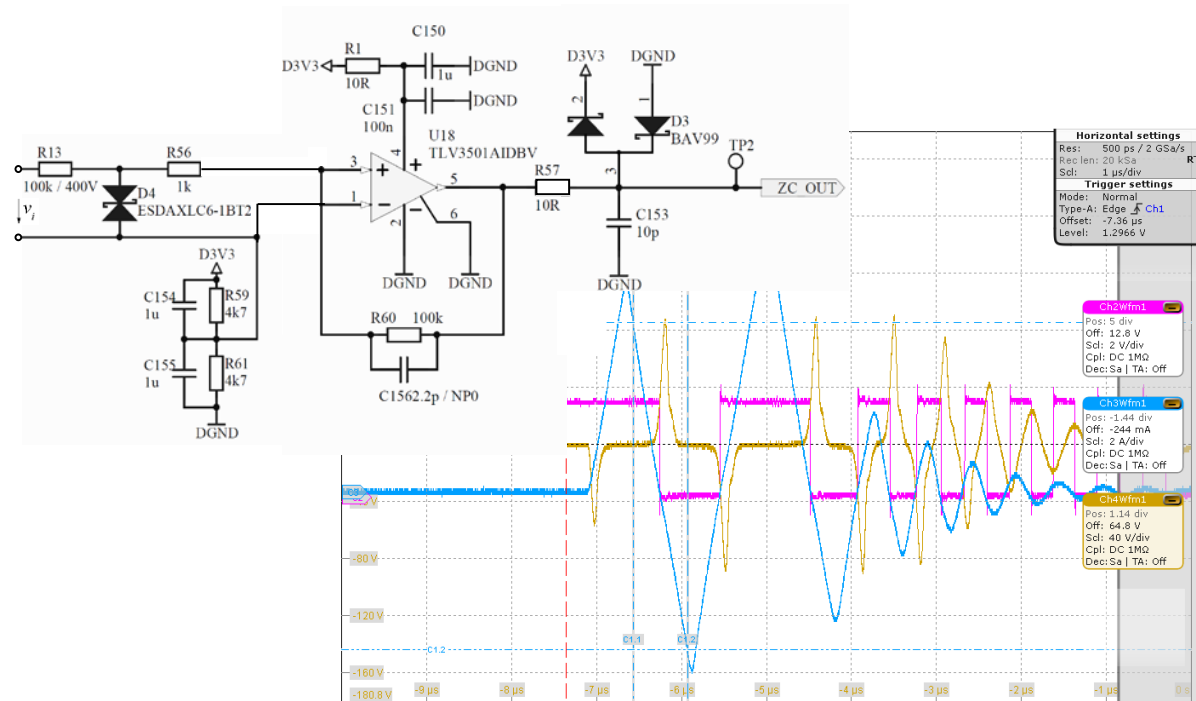  
# *i=0* Detection

- Saturable Inductor – Toroidal Core R4 x 2.4 x 1.6, EPCOS (4mm Diameter)
- Core Material N30, EPCOS







 
- Operation Tested up to 2.5MHz Switching Frequency



  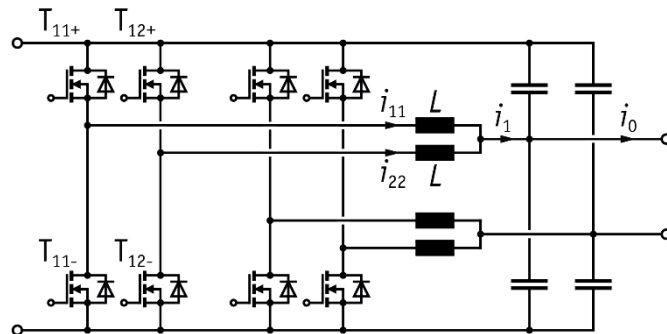  
## 4D-Interleaving



- Interleaving of 2 Bridge Legs per Phase - Volume / Filtering / Efficiency Optimum
- Interleaving in Space & Time – Within Output Period
- Alternate Operation of Bridge Legs @ Low Power
- Overlapping Operation @ High Power




 - Opt. Trade-Off of Conduction & Switching Losses / Opt. Distribution of Losses




## DC-Side Passive Power Pulsation Buffer

- Electrolytic Capacitor

 

 
$$\begin{aligned} S_0 &= 2.0 \text{ kVA} \\ \cos \Phi_0 &= 0.7 \\ V_{C,max} &= 450 \text{ V} \\ \Delta V_C / V_{C,max} &= 3 \% \end{aligned}$$



 
■  $C > 2.2\text{mF} / 166 \text{ cm}^3 \rightarrow$  Consumes 1/4 of Allowed Total Allowed Volume !




 
## DC-Side Active Power Pulsation Buffer

- Large Voltage Fluctuation **Foil or Ceramic Capacitor**
- Buck-Type (Lower Voltage Levels) or Boost-Type DC/DC Interface Converter



CeraLink  
TDK




108 x 1.2  $\mu$ F / 400 V  
 $C_k \approx 140 \mu$ F  
 $V_{Ck} = 23.7 \text{ cm}^3$

 ■ Significantly Lower Overall Volume Compared to Electrolytic Capacitor









## DC-Side Active Power Pulsation Buffer

- Cascaded Control Structure

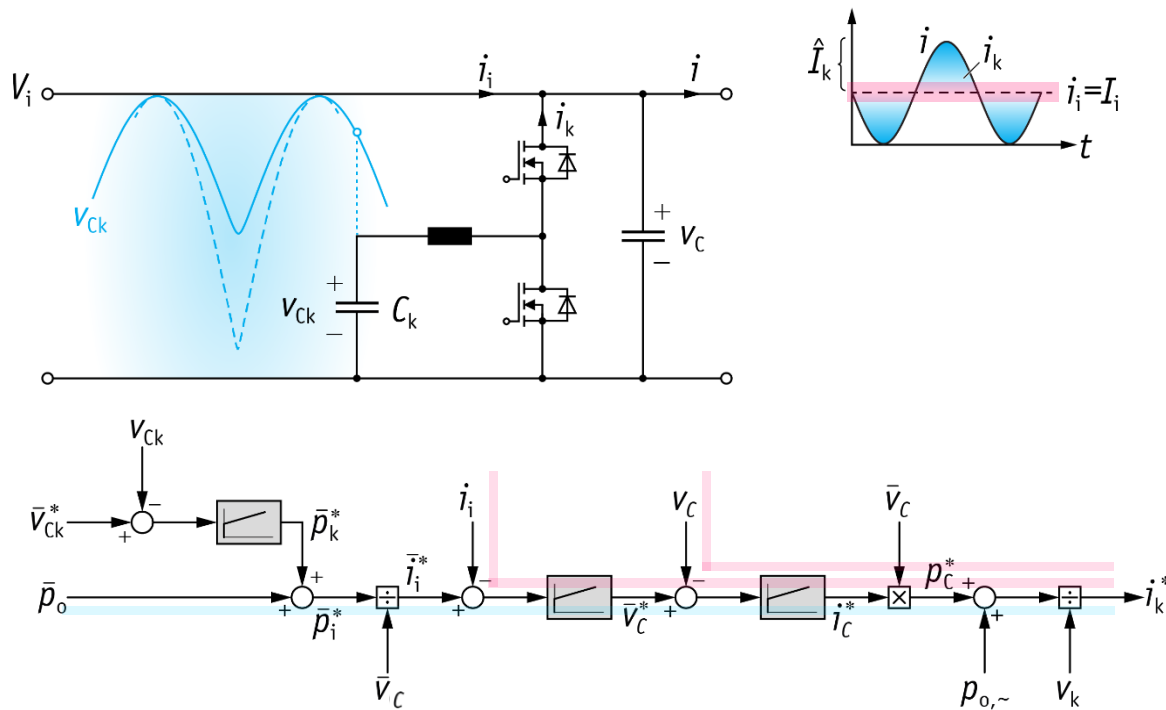

 
- P-Type Resonant Controller
- Feedforward of Output Power Fluctuation
- Underlying Input Current ( $i_i$ ) / DC Link Voltage ( $u_c$ ) Control



 
# Selected Power Semiconductors



- 600V IFX Normally-Off GaN GIT - ThinPAK8x8
- State-of-the-Art Gate Drive



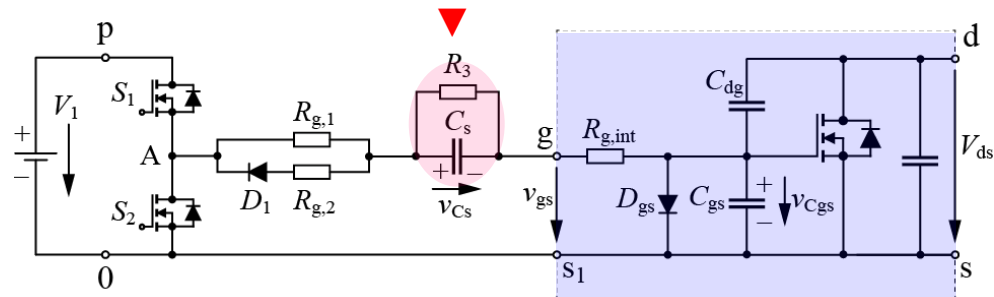
$$\begin{aligned} V_{gs,th} &= 1.2V \\ R_{ds,on} &= 55 \text{ m}\Omega @ 25^\circ\text{C} \\ R_{g,int} &= 5\Omega \end{aligned}$$




–  $C_s$  Enables High Gate Current for Fast Turn-On

 –  $R_3$  Discharges  $C_s$  During Off-State



 
- Duty Cycle and Frequency Dependent Gate Voltage





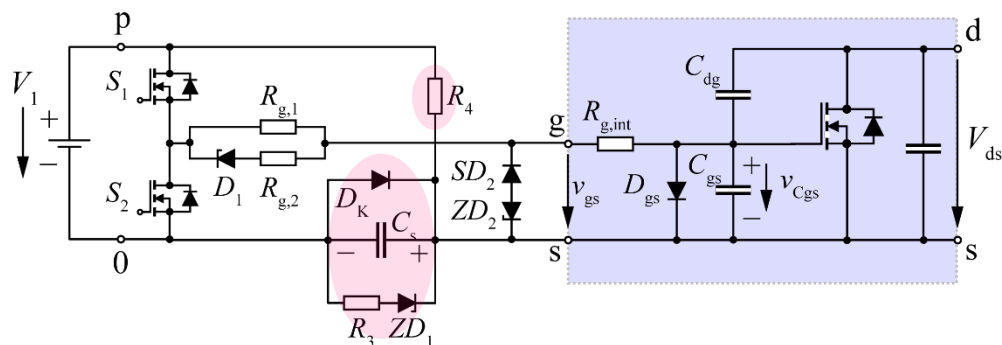
## High $dv/dt$ -Immunity Gate Drive

- Fixed Negative Turn-Off Gate Voltage - Independent of Sw. Frequency and Duty Cycle
- Extreme  $dv/dt$ -Immunity ( $500\text{ kV}/\mu\text{s}$ ) - Due to CM Choke at Signal Isolator Input
- $< 30\text{ ns}$  Overall Prop. Delay



- Diode  $ZD_2$  Quickly Discharges  $C_s$  to  $V_{ZD2}$  @ Turn-Off

 - Diode  $ZD_1$  Prevents Complete Discharge of  $C_s$  During Off-State




- $R_4$  Ensures Precharge of  $C_s \rightarrow$  Neg. Gate Voltage @ Start-Up



# EMI Filter Topology (1)
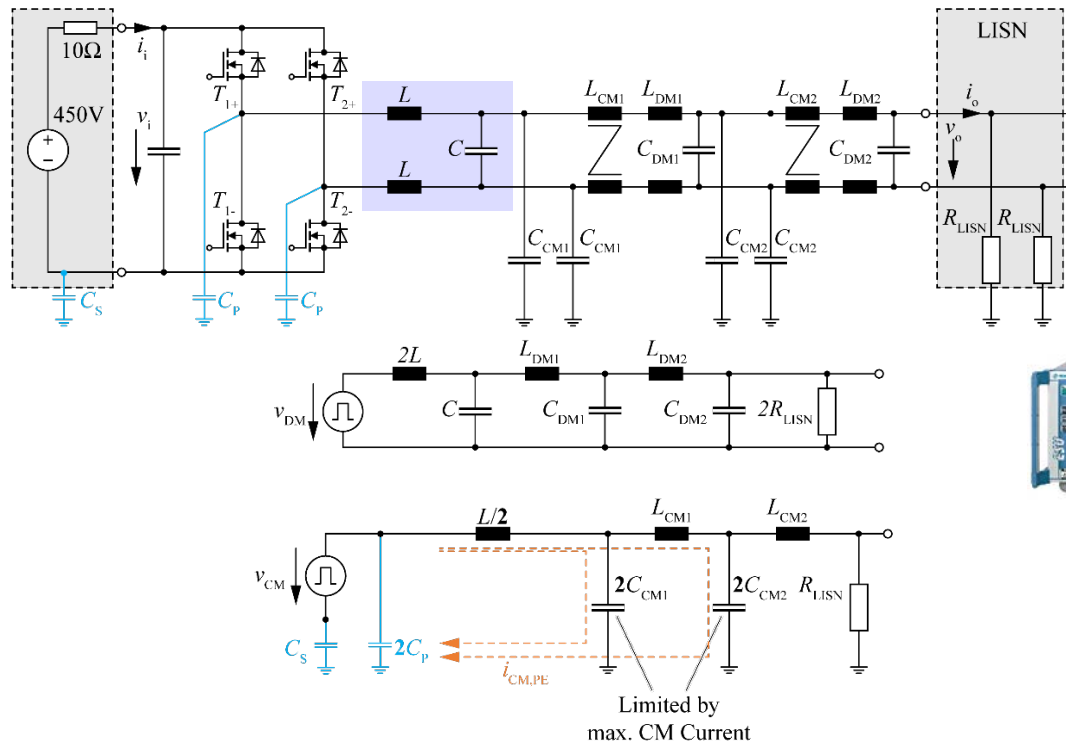
## Conventional Filter Structure

- DM Filtering Between the Phases
- CM Filtering Between Phases and PE




- CM Cap. Limited by Earth Current Limit – Typ. 3.5mA for PFC Rectifiers (GLBC: 5mA, later 50mA !)
- Large CM Inductor Needed – Filter Volume Mainly Defined by CM Inductors



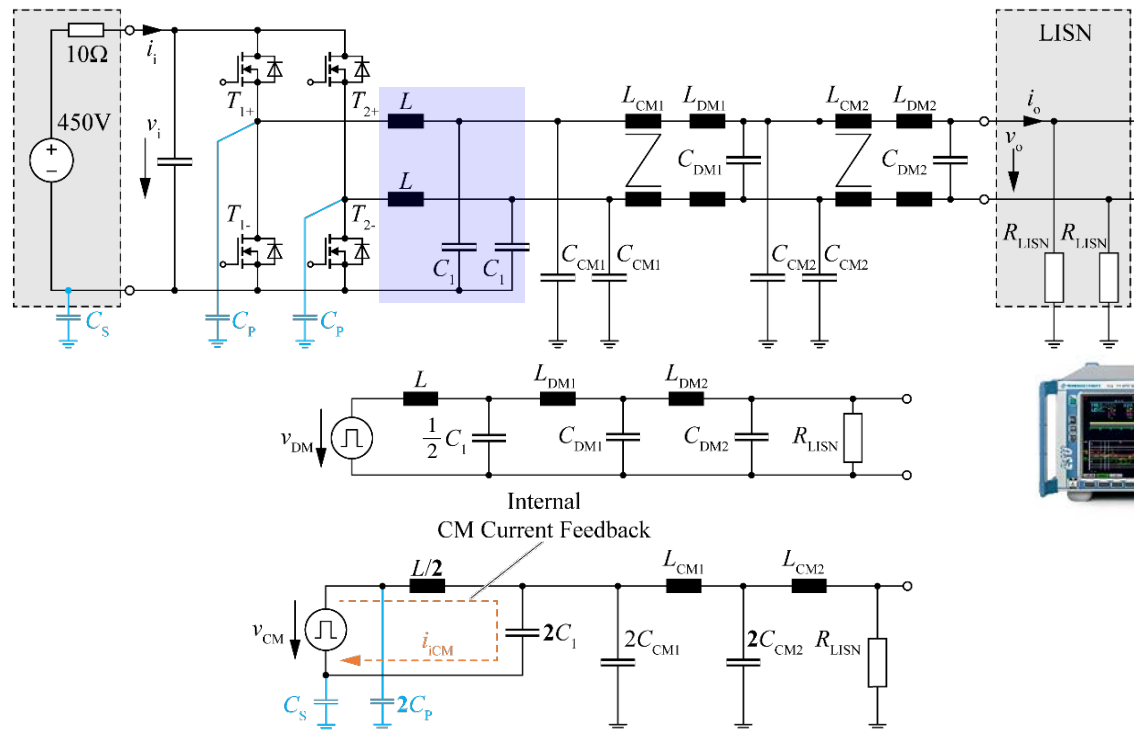
## EMI Filter Topology (2)

- Filter Structure with Internal CM Capacitor Feedback
- Filtering to DC- (and Optional to DC+)



 
- No Limitation of CM Capacitor  $C_1$  Due to Earth Current Limit  $\rightarrow \mu\text{F}$  Instead of nF Can be Employed
- Allows Downsizing of CM Inductor and/or Total Filter Volume



## Final Converter Topology

- Interleaving of 2 Bridge Legs per Phase
- Active DC-Side Buck-Type Power Pulsation Buffer
- First Stage AC Filter Caps Connected to DC-
- 2-Stage EMI AC Output Filter

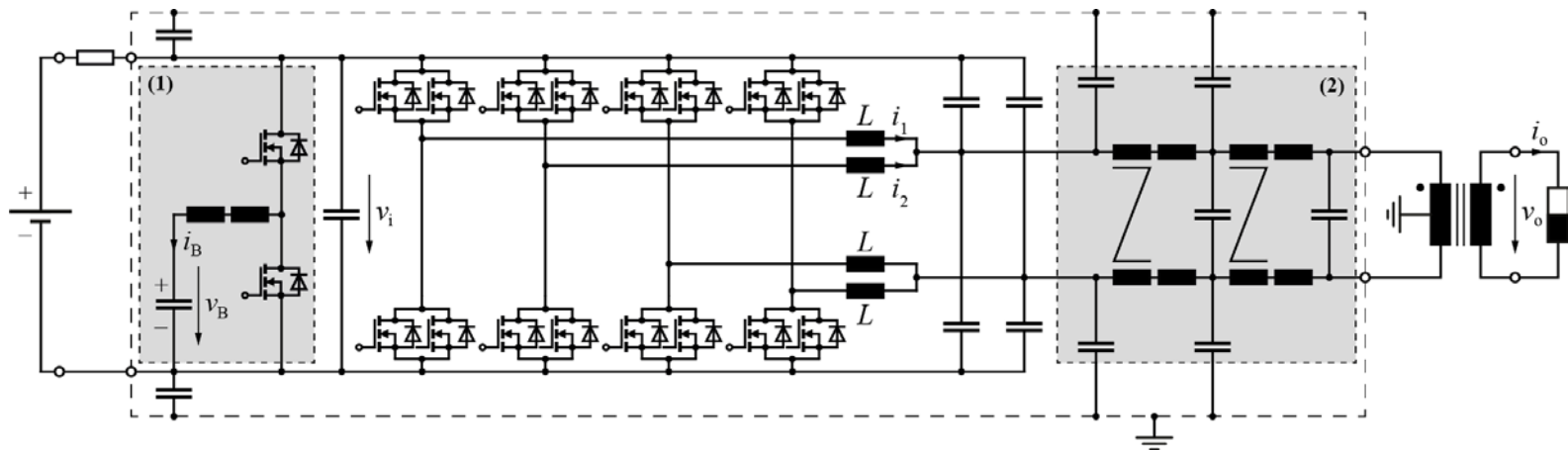(1) Power Pulsation Buffer  
(2) EMI Output




- ZVS of All Bridge Legs @ Turn-On/Turn-Off in Whole Operating Range (4D-TCM-Interleaving)
- Heatsinks Connected to DC Bus / Shield to Prevent Cap. Coupling to Grounded Enclosure
 
# High Frequency Inductors (1)





- Multi-Airgap Inductor with Multi-Layer Foil Winding Arrangement Minim. Prox. Effect
- Very High Filling Factor / Low High Frequency Losses
- Magnetically Shielded Construction Minimizing EMI
- Intellectual Property of F. Zajc / Fraza

- $L = 10.5 \mu\text{H}$
- 2 x 8 Turns
- 24 x 80  $\mu\text{m}$  Airgaps
- Core Material DMR 51 / Hengdian
- 0.61mm Thick Stacked Plates
- 20  $\mu\text{m}$  Copper Foil / 4 in Parallel
- 7  $\mu\text{m}$  Kapton Layer Isolation
- 20m $\Omega$  Winding Resistance /  $Q \approx 600$
- Terminals in No-Leakage Flux Area



 ■ Dimensions - 14.5 x 14.5 x 22mm<sup>3</sup>





 
 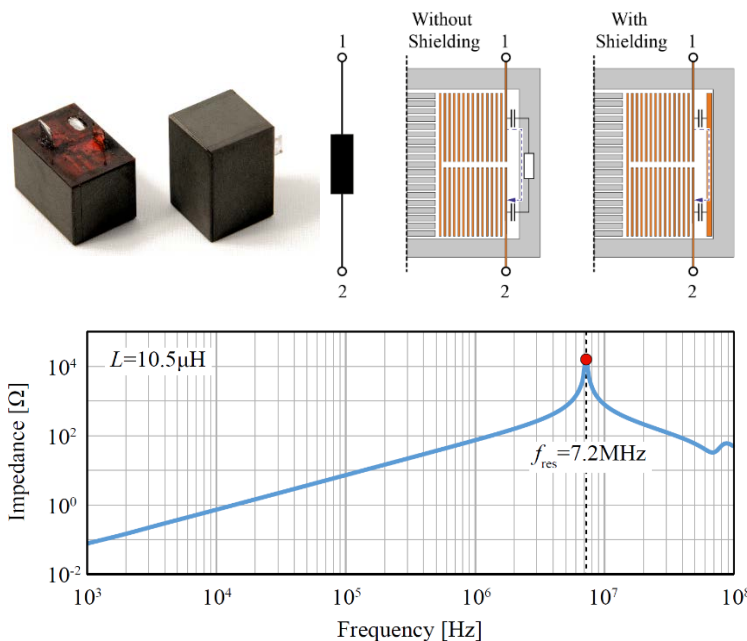
## High Frequency Inductors (2)



- High Resonance Frequency → Inductive Behavior up to High Frequencies
- Extremely Low AC-Resistance → Low Conduction Losses up to High Frequencies
- High Quality Factor



- Shielding Eliminates HF Current through the Ferrite → Avoids High Core Losses
- Shielding Increases the Parasitic Capacitance


## High Frequency Inductors (3)



\* Knowles (1975!)



- Cutting of Ferrite Introduces Mech. Stress
- Significant Increase of the Loss Factor
- Reduction by Polishing / Etching (5  $\mu\text{m}$ )

 ■ Comparison of Temp. Increase of a Bulk and a Sliced Sample @ 70mT / 800kHz


  
# Thermal Management (1)

- 30°C max. Ambient Temperature
- 60°C max. Allowed Surface and Air Outlet Temperature
- Evaluation of Optimum Heatsink Temp. for Thermal Isolation of Converter




- Minimum Volume Achieved w/o Thermal Isolation with Heatsink @ max. Allowed Surface Temp.



## Thermal Management (2)

- Overall Cooling Performance Defined by Selected Fan Type and Heatsink


– Radial Blower

 



– Axial Fan

  

 – Square Cross Section of Heatsink for Using a Fan



– Flat and Wide Heatsink for Blower

 
 


- Optimal Fan and Heat Sink Configuration Defined by Total Cooling System Length
- Cooling Concept with Blower Selected → Higher CSPI for Larger Mounting Surface
  
## Thermal Management (3)

- 30mm Blowers with Axial Air Intake / Radial Outlet
- Full Optimization of the Heatsink Parameters

- 200um Fin Thickness
- 500um Fin Spacing
- 3mm Fin Height
- 10mm Fin Length
- $CSPI = 37 \text{ W}/(\text{dm}^3 \cdot \text{K})$
- 1.5mm Baseplate



- $CSPI_{eff} = 25 \text{ W}/(\text{dm}^3 \cdot \text{K})$  Considering Heat Distribution Elements
- Two-Side Cooling  $\rightarrow$  Heatsink Temperature =  $52^\circ\text{C}$  @ 80W (8W by Natural Convection)





## Little Box 1.0

★ 135 W/in<sup>3</sup>


- System Employing Active CeraLink™ 1- $\Phi$  Power Pulsation Buffer


- 8.2 kW/dm<sup>3</sup>
- 8.9cm x 8.8cm x 3.1cm
- $f_s = 250\text{kHz} \dots 1\text{MHz}$
- 96,3% Efficiency @ 2kW
- $T_c = 58^\circ\text{C}$  @ 2kW

- $\Delta u_{\text{DC}} = 1.1\%$
- $\Delta i_{\text{DC}} = 2.8\%$
- $\text{THD} + N_U = 2.6\%$
- $\text{THD} + N_I = 1.9\%$

- Compliant to All “Original” Specifications (!)

 - $i_{\text{gnd}} < 5\text{mA}$  (!)
- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents



 

## Little Box 1.0

★ 135 W/in<sup>3</sup>


- System Employing Active CeraLink™ 1- $\Phi$  Power Pulsation Buffer


- 8.2 kW/dm<sup>3</sup>
- 8.9cm x 8.8cm x 3.1cm
- $f_s = 250\text{kHz} \dots 1\text{MHz}$
- 96,3% Efficiency @ 2kW
- $T_c = 58^\circ\text{C}$  @ 2kW

- $\Delta u_{\text{DC}} = 1.1\%$
- $\Delta i_{\text{DC}} = 2.8\%$
- $\text{THD} + N_U = 2.6\%$
- $\text{THD} + N_I = 1.9\%$

- Compliant to All "Original" Specifications (!)

 - $i_{\text{gnd}} < 5\text{mA}$  (!)
- No Low-Frequ. CM Output Voltage Component
- No Overstressing of Components
- All Own IP / Patents





 


## Measurement Results (1)

- System Employing Active CeraLink™ 1- $\Phi$  Power Pulsation Buffer

- Ohmic Load / 2kW

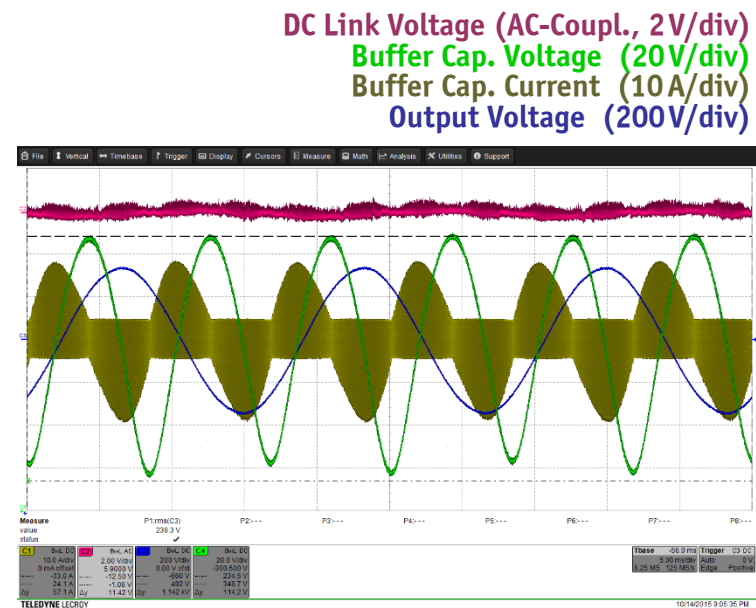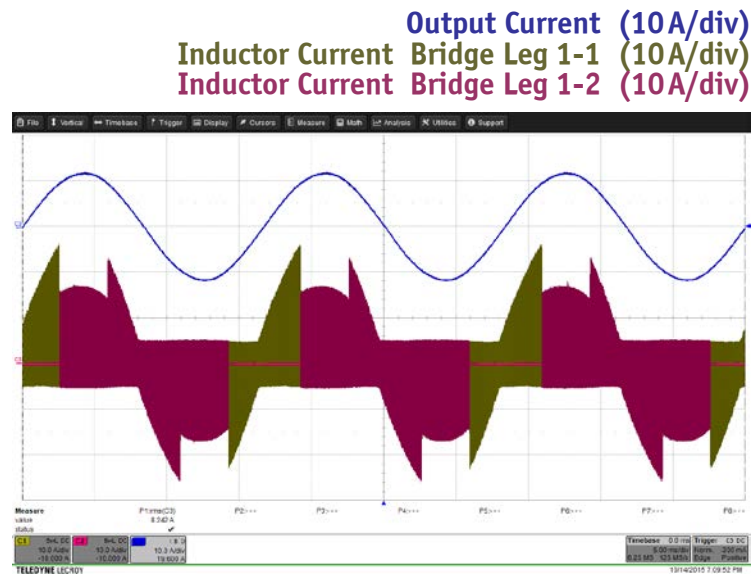


- Compliant to All Specifications

 
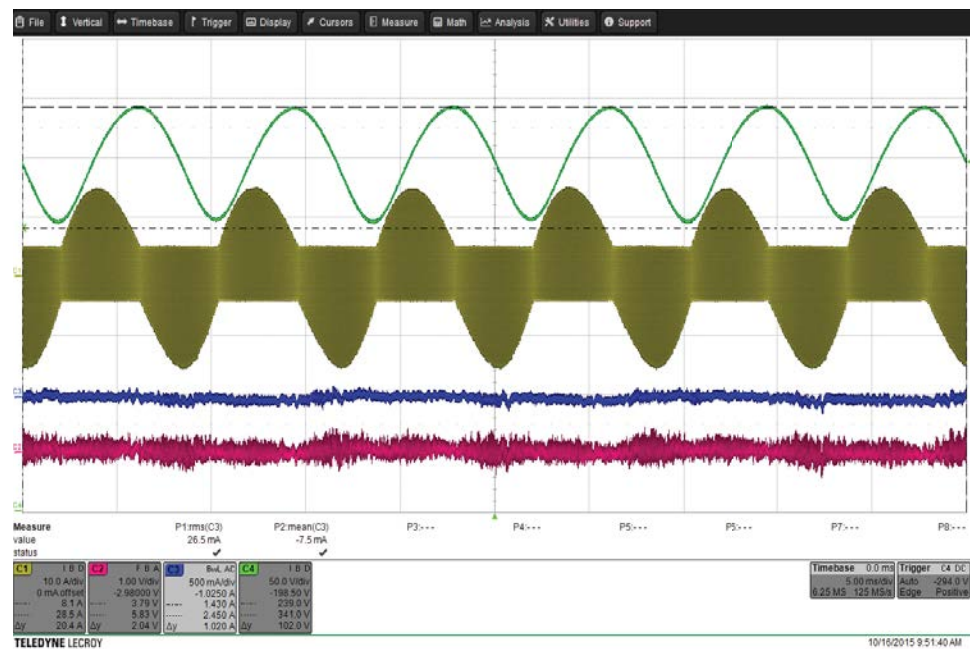
## Measurement Results (2)

- System Employing Active CeraLink™ 1- $\Phi$  Power Pulsation Buffer

Buffer Cap. Voltage (50V/div)  
 Buffer Cap. Current (10A/div)  
 Conv. Inp. Curr. (AC Coupl. 500mA/div)  
 DC Link Voltage (AC Coupl. 1V/div)




- Stationary Operation @ 2kW Output Power



 
## Measurement Results (3)

- System Employing Active CeraLink™ 1- $\Phi$  Power Pulsation Buffer

★  $\eta_w = 95.07\%$  Weighted Efficiency




- Compliant to All Specifications

 


## Volume & Loss Distribution
 
### Volume Distribution (240cm<sup>3</sup>)



### Loss Distribution (75W)

 


- Large Heatsink (incl. Heat Conduction Layers)
- Large Losses in Power Fluctuation Buffer Capacitor (!)
- TCM Causes Relatively High Conduction & Switching Losses @ Low Power
- Relatively Low Switching Frequency @ High Power – Determines EMI Filter Volume


 
## Finalists - Performance Overview

- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

**Note:** Numbering of Teams is Arbitrary



- (1) Virginia Tech
- (2) Schneider Electric
- (3) EPRI (Univ. of Tennessee)
- (4) Venderbosch
- (5) Energy Layer
- (6) ETH Zurich
- (7) Rompower
- (8) Tommasi-Bailly
- (9) Red Electric Devils
- (10) AHED
- (11) FH IISB
- (12) Univ. of Illinois
- (13) AMR

- 70...300  $\text{W}/\text{in}^3$
- 35 kHz... 500kHz... 1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic instead of Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)

Google  
Little Box Challenge  
Grand Prize Winner



Dr. Paul Bleus  
Directeur R&D



*Red Electric Devils*


Olivier Bomboir, Paul Bleus, Fabrice  
Frebel, Thierry Joannes, Francois Milstein,  
Pierre Stassain, Christophe Geuzaine, Carl  
Emmereichs, Philippe Laurent


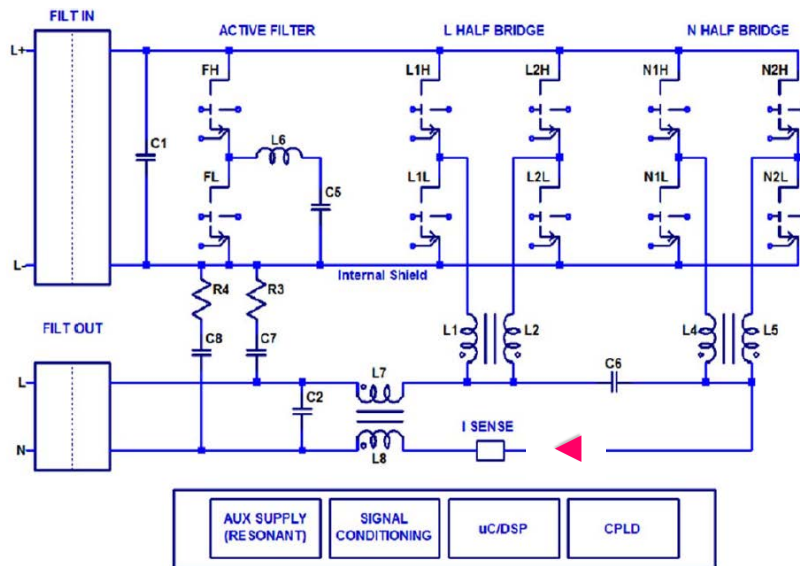
# 

★ 145 W/in<sup>3</sup>

- No Low-Frequ. Common-Mode Output Voltage Comp. →  $i_{\text{gnd}} < 5\text{mA}$  (!)
- Buck-Type DC-Side Active Power Pulsation Filter (MLCC Cap.  $< 150\mu\text{F}$ ,  $200\text{V}_{\text{pp}}$ )




- 2 x Interleaved Bridge Legs for Each Half-Bridge
- DM Inductors ( $L_1/L_2$  and  $L_4/L_5$ ) and Series Connected CM Inductor ( $L_7/L_8$ )
- Single Open-Loop Hall Sensor Outp. Curr. Measurement + Observer-Based Curr. Reconstruction


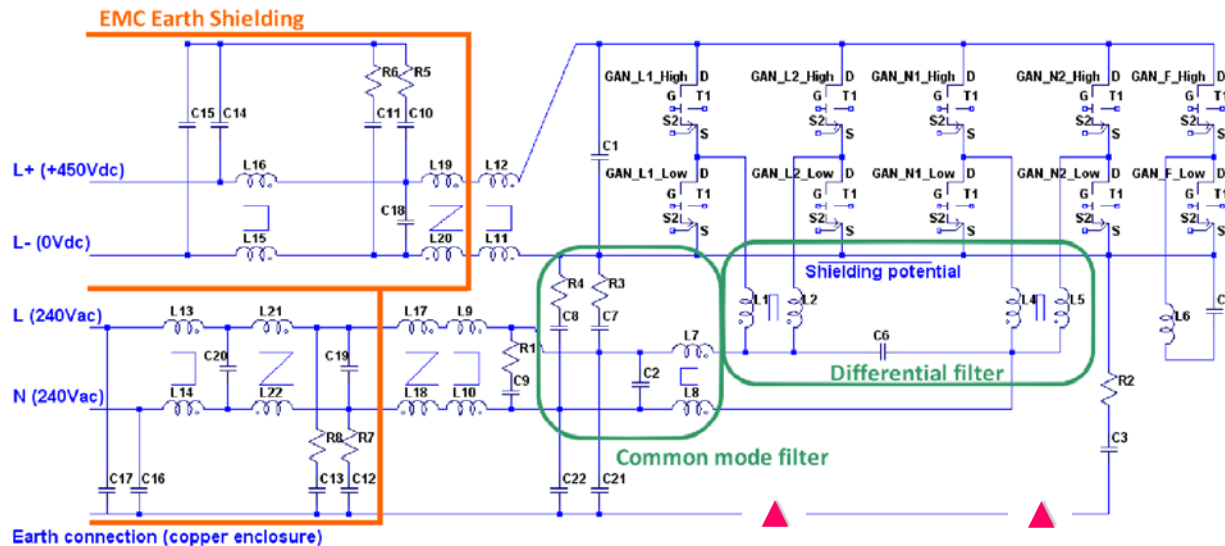
## Red Electric Devils

★ 145 W/in<sup>3</sup>

- No Low-Frequ. Common-Mode Output Voltage Comp. →  $i_{\text{gnd}} < 5\text{mA}$  (!)
- Buck-Type DC-Side Active Power Pulsation Filter (MLCC Cap.  $< 150\mu\text{F}$ ,  $200\text{V}_{\text{pp}}$ )





- DSP & CPLD Control
- GaN Systems @ ZVS (35kHz ... 240kHz)
- Shielded Multi-Stage EMI Filter @ DC Input & AC Output


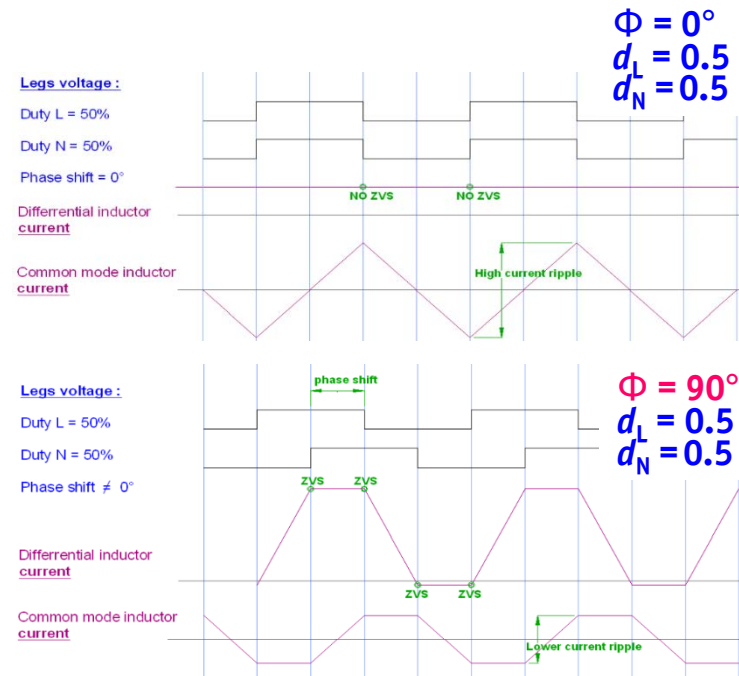 
## Red Electric Devils

★ 145 W/in<sup>3</sup>

- Variable Phase-Shift of the Half-Bridges (0° or 90°) Dep. on Duty Cycle





- Selection of Opt. Phase Shift & Sw. Frequency for ZVS & Min. Size of Filter Ind.  $L_{CM}$  &  $L_{DM}$


  
## Red Electric Devils

★ 145 W/in<sup>3</sup>

- 3D Sandwich Assembly
- Single Ultra-Thin PCB – Power / Control / Aux.
- Honeycomb Cu-Heatsink & Al Oxide Inductor Cooling
- MMLC Storage Caps Rows Utilized as Heatsink “Fins” (1mm Gaps)





- 145 W/in<sup>3</sup>
- 95.4 % CEC Efficiency
- $i_{\text{gnd}} < 5\text{mA}$  (!)
- CSPI = 22.6 W/(dm<sup>3</sup>.K) - Heatsink & Axial Fan


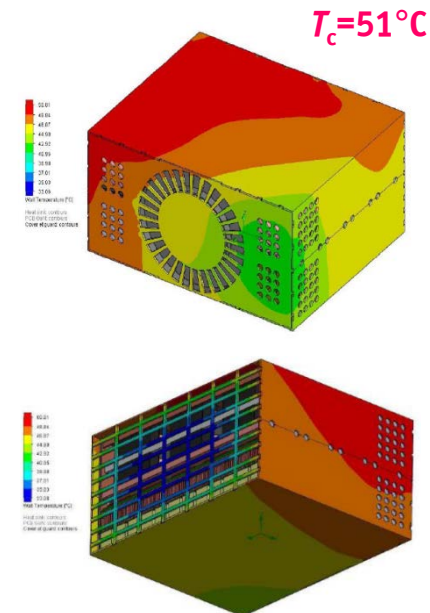 
## Red Electric Devils

★ 145 W/in<sup>3</sup>

- 3D Sandwich Assembly
- Single Ultra-Thin PCB – Power / Control / Aux.
- Honeycomb Cu-Heatsink & Al Oxide Inductor Cooling
- MMLC Storage Caps Rows Utilized as Heatsink “Fins” (1mm Gaps)



- 145 W/in<sup>3</sup>
- 95.4 % CEC Efficiency
- $i_{\text{gnd}} < 5\text{mA}$  (!)
- CSPI = 22.6 W/(dm<sup>3</sup>.K) - Heatsink & Axial Fan

**Google**  
**Little Box Challenge**  
**Top 3 Finalist**

**Schneider**  
**Electric Team**



Miao-xin Wang, Rajesh Ghosh, Srikanth  
Mudiyula, Radoslava Mitova, David Reilly,  
Milind Dighrasker, Sajeesh Sulaiman, Alain  
Dentella, Damir Klikic, Michael Hartmann



**Schneider** Global Team  
Electric

★ 100 W/in<sup>3</sup>

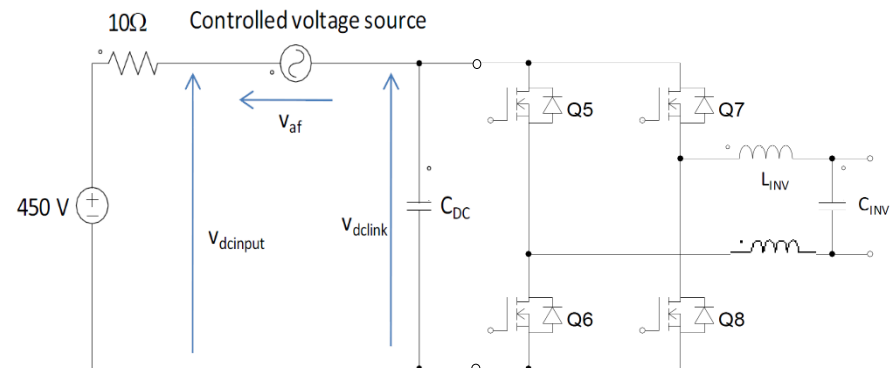 - High Efficiency & Robustness Preferred → Larger Size
- PWM of Both Legs of Output Full-Bridge → No Low. Freq. CM Output Voltage Comp.
- DC-Side Series (!) Active Power Puls. Filter → Compensates 120Hz DC Link Volt. Variation



- $C_{DC} = 400\mu\text{F} / 450\text{V}$
- 1/5 Volume Comp. to only Bulk Capacitors
- $V_{dcinput}$  Ripple <10% (<30V<sub>pp</sub>) @ Full Load


- Nanocrystalline CM Choke
- DC-Side & AC-Side EMI/RF Filter
- Q<sub>5...8</sub> – T0247 SiC MOSFETs, 45kHz of Both Legs




**Schneider** Global Team  
Electric

★ 100 W/in<sup>3</sup>

 - High Efficiency & Robustness Preferred → Larger Size
- PWM of Both Legs of Output Full-Bridge → No Low. Freq. CM Output Voltage Comp.
- DC-Side Series (!) Active Power Puls. Filter → Compensates 120Hz DC Link Volt. Variation



 - $i_{\text{gnd}} < 25\text{mA} (!)$
- 97.2 % CEC Efficiency




- $C_{\text{DC\_RF}} = 2 \times 1500\mu\text{F}/25\text{V}$ ,  $U_{\text{DC\_RF}} = 15\text{V}$
- Only 52VA Processed Ripple Filter Power @ Rated Output (!)
- $Q_1/Q_2$  &  $Q_3/Q_4$  -  $R_{\text{ds,on}} = 2.2\text{m}\Omega$  MOSFETs (40V, 100A), w/o Heatsink,  $f_s = 130\text{kHz}$  of Both Legs
- TI Piccolo DSP Control of Entire System / Open Loop Control of 120Hz Comp. Filter


 
## Optimization of Little-Box 1.0




Adv. Modulation / Circuit Concepts  
Measurement of Buffer Cap. Performance  
Measurement of GaN ZVS & On-State Losses  
Measurement of Multi-Airgap Core Losses  
 $\eta$ -Pareto Optimization



   
## Eff. Optimal $f_s$ -Modulation



- TCM  $\rightarrow$  ZVS but Large Current Ripple & Wide Frequency Variation
- PWM  $\rightarrow$  Const. Sw. Frequency but Hard Sw. @ Current Maximum
- Opt. Combination of TCM & PWM  $\rightarrow$  Optim. Frequ. Variation Over Output Period
- Exp. Determination of Loss-Opt. Sw. Frequency  $f_{\text{OFM}}$  Considering DC/DC Conv. Stage





 
- DC/AC Properties Calculated Assuming Local DC/DC Operation
- Loss-Optimal Local Sw. Frequ.  $f_{\text{OFM}}$  for Given  $V_{\text{DC}}$  & Local  $i_o$  &  $v_{\text{co}}$


   
# Eff. Optimal $f_s$ -Modulation




- TCM  $\rightarrow$  ZVS but Large Current Ripple & Wide Frequency Variation
- PWM  $\rightarrow$  Const. Sw. Frequency but Hard Sw. @ Current Maximum
- Opt. Combination of TCM & PWM  $\rightarrow$  Optim. Frequ. Variation Over Output Period
- Exp. Determination of Loss-Opt. Sw. Frequency  $f_{\text{OFM}}$  Considering DC/DC Conv. Stage



- DC/AC Properties Calculated Assuming Local DC/DC Operation
- Loss-Optimal Local Sw. Frequ.  $f_{\text{OFM}}$  for Given  $V_{\text{DC}}$  & Local  $i_o$  &  $v_{\text{co}}$
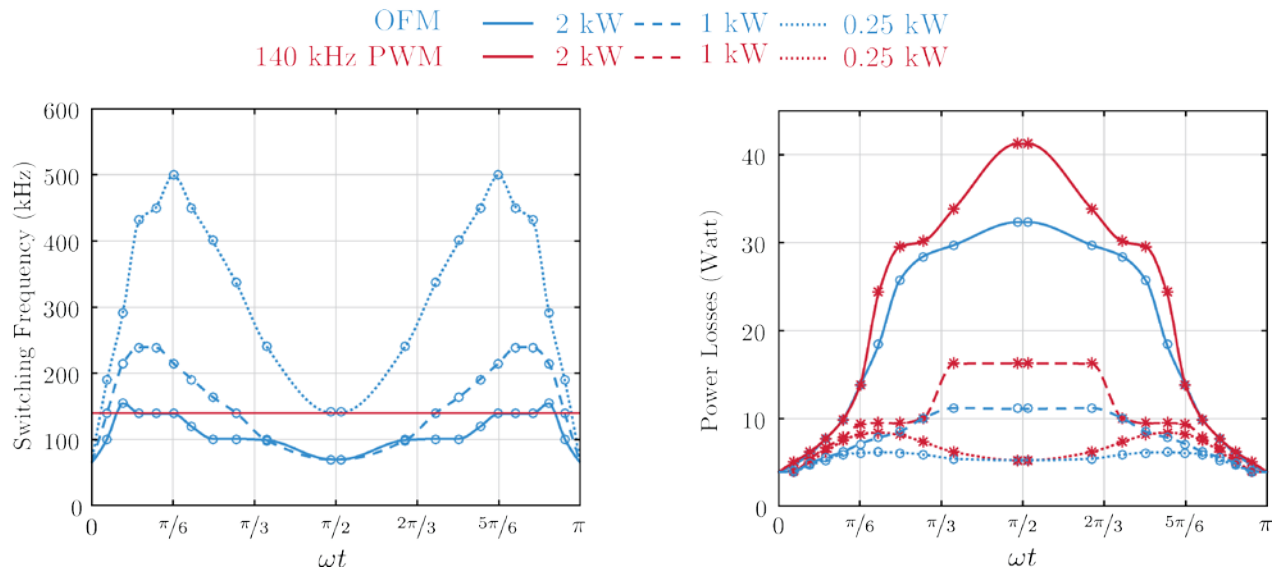
## Eff. Optimal $f_s$ -Modulation


- Resulting Time-Dependency of Optimal Sw. Frequ. & Power Loss
- Comparison with 140 kHz Const. Sw. Frequency PWM



- Higher Average Switching Frequency  $f_s$  @ Light Loads
- Reduction of  $f_s$  @ Mains Voltage Peak (for Ohmic Load) for Sustaining ZVS

## Eff. Optimal $f_s$ -Modulation

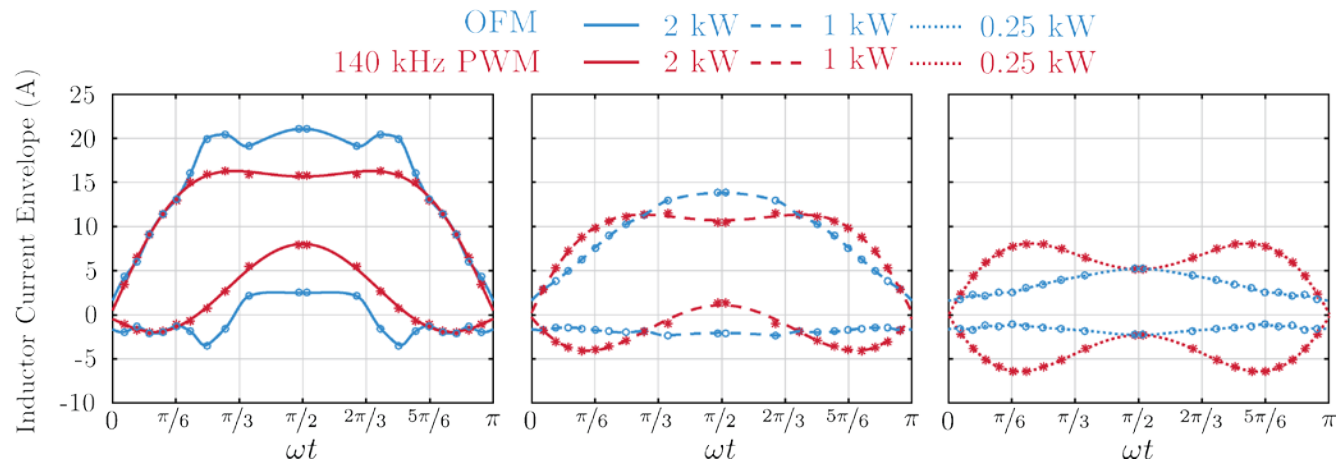
### Optimal Inductor Current Envelope for Diff. Output Power Levels



- Higher Average Switching Frequency  $f_s$  @ Light Loads
- Reduction of  $f_s$  @ Mains Voltage Peak (for Ohmic Load) for Sustaining ZVS


 
## Measurements

Buffer Capacitor Losses / Cap.  
Power Semicond. ZVS & On-State Losses  
Ferrite Multi-Airgap Core Losses



  
## CeraLink vs. X6S

- Electrolytic Capacitors → Limited by Lifetime Current Limit
- X6S MLCC, 2.2 $\mu$ F, 450 V Class II → Highest Energy Density but Low Cap. @ High DC Bias
- CeraLink™, 1 $\mu$ F / 2 $\mu$ F, 650 V → PLZT Ceramic, High Cap. @ High DC Bias
- CeraLink™ Allows Op. @ 125°C → Very Low ESR @ High Frequencies





 - PPB Design Optimiz. Requires Large-Signal Capacitance and Power Loss Data in All Operating Points



 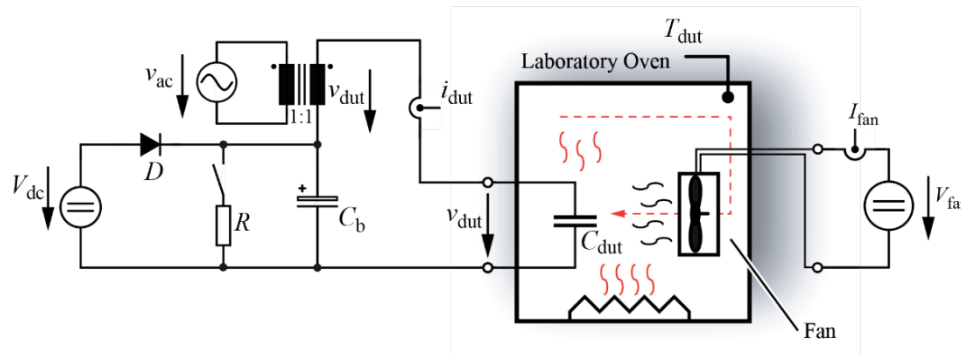
## CeraLink vs. X6S

- Electrolytic Capacitors → Limited by Lifetime Current Limit
- X6S MLCC, 2.2 $\mu$ F, 450 V Class II → Highest Energy Density but Low Cap. @ High DC Bias
- CeraLink™, 1 $\mu$ F / 2 $\mu$ F, 650 V → PLZT Ceramic, High Cap. @ High DC Bias
- CeraLink™ Allows Op. @ 125°C → Very Low ESR @ High Frequencies





 
### ■ Experimental Setup for Generation of DC Bias & Superimposed AC Voltage





   
## CeraLink vs. X6S

- CeraLink™**
  - Large-Signal 120Hz Excitation Reveals Large Hysteresis
  - Significantly Higher Losses @ 120Hz Comp. to X6S MLCC
  - ESR Drops Significantly @ Higher Temp.
  - 36 $\mu$ F (27 $\mu$ F) Blocks of Prepackaged Single Chips
  - Reliable Mech. Construction
- X6S MMLC**
  - Only Available as Single Chips
  - Complicated Packaging




 


## CeraLink vs. X6S



- Variation of DC Bias and Superimposed AC Voltage @ 60°C Operating Temp.

✗ Designed Op. Point

EPCOS/TKD  
CeraLink™ 2μF, 600V

  



TDK Class II  
X6S MLCC 2.2μF, 450V

  

- PPB Design Optimiz. Requires Large-Signal Capacitance and Power Loss Data in All Operating Points


 
## Measurement of GaN ZVS & On-State Losses →



 

  
## Analysis of GaN Power Transistor ZVS Losses

- Little-Box 1.0 Experiments Indicated *Residual ZVS Losses of GaN Power Transistors*
- Losses Cannot be Explained by Remaining  $i_D$ ,  $u_{DS}$  Overlap / Non-Ideal Gate Drive etc.





 - Potentially Large Measurement Error for Electric Double-Pulse Sw. Loss Measurement
- Accuracy only Guaranteed by **Direct Loss Measurement** → **Calorimetric Approach**



  
# Analysis of GaN Power Transistor ZVS Losses

- Little-Box 1.0 Experiments Indicated *Residual ZVS Losses* of GaN Power Transistors
- Losses Cannot be Explained by Remaining  $i_D$ ,  $u_{DS}$  Overlap / Non-Ideal Gate Drive






 - Potentially Large Measurement Error for Electrical Double-Pulse Sw. Loss Measurement
- Accuracy only Guaranteed by Direct Loss Measurement  $\rightarrow$  Calorimetric Approach



   
# Calorimetric Measurement of ZVS Losses

- “Inductor in the Box” → Accurate DC Inp. & Outp. Power Measurement, Subtr. on Ind. Losses
- “Bridge Leg in the Box” → Direct Measurement of the Sum of Cond. & Sw. Losses






 - “Bridge Leg in the Box” & Fast Measurement by  $C_{th} \cdot \Delta T / \Delta t$  Evaluation
- DC/DC Operation @ High Sw. Frequency for Large Ratio of Sw. and Conduction Losses
- Subtraction of the Cond. Losses from Datasheet or Dir. Measurement



   
# Calorimetric Measurement of ZVS Losses

- “Bridge Leg in the Box” & Fast Measurement by  $C_{th} \cdot \Delta T / \Delta t$  Evaluation
- Subtraction of the Cond. Losses from Datasheet or Direct Measurement
- DC/DC Operation @ High Sw. Frequency for Large Ratio of Sw. and Conduction Losses





 - Isolated Temp. Measurement with Optical Fiber (GaAs Crystal) Instead of Thermocouple
- Calibration by On-State of  $T_1$  and  $T_2$  & DC Current Operation / DC Power Loss Measurement



  
## Calibration of “Bridge Leg in the Box” Setup

- Calibration by On-State of  $T_1$  and  $T_2$  & DC Current Operation / DC Power Loss Measurement
- Identification of Thermal Cap.  $C_{th}$  and Thermal Resistance  $R_{th}$




 
- DC Power Loss Measurement Ensures High Accuracy
- Thermal Behavior for Short Measurement Times Mainly Determined by  $C_{th}$





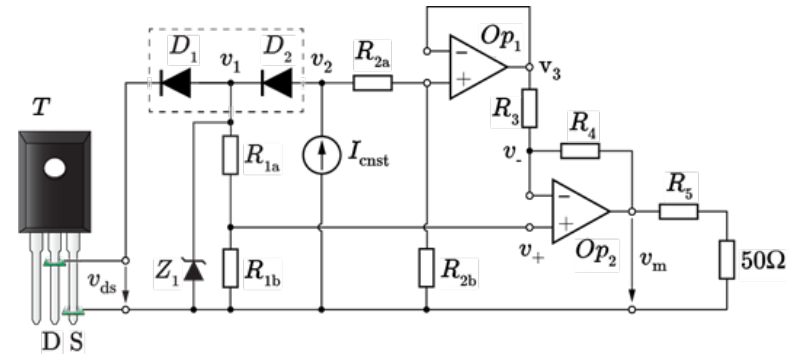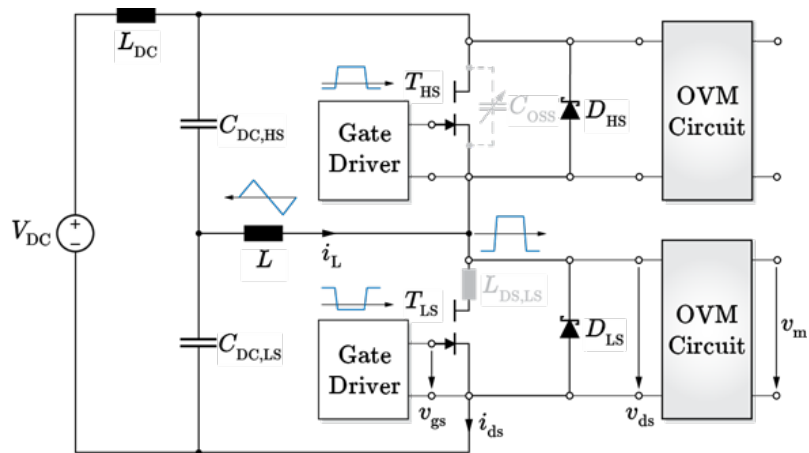
## Accurate On-State Voltage Measurement

- Clamping Diode for Limiting the On-State Voltage Measurement (OVM) to 2V
- Subtraction of the SiC Diode Forward Voltage Drop for High Accuracy (2mV)





 - Only 50ns Blanking Time – OVM Circuit Can also be Used for Dynamic  $R_{DS,on}$  Measurement



 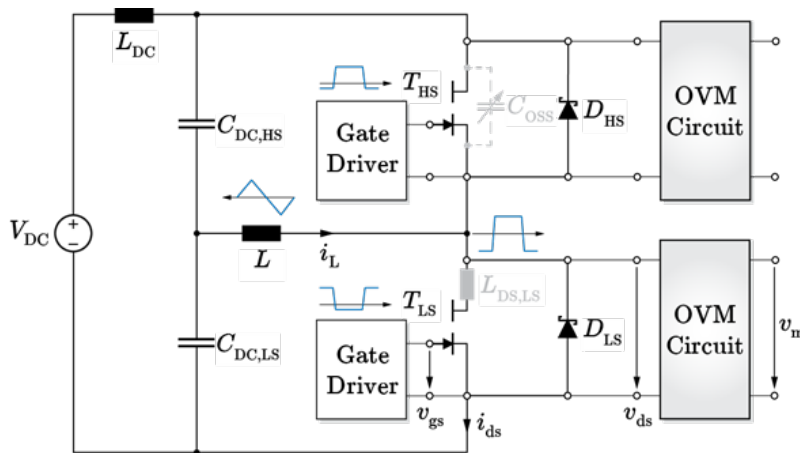
## Accurate On-State Voltage Measurement

- **Clamping Diode for Limiting the On-State Voltage Measurement (OVM) to 2V**
- **Subtraction of the SiC Diode Forward Voltage Drop for High Accuracy (2mV)**





 - **Only 50ns Blanking Time – OVM Circuit Can also be Used for Dynamic  $R_{DS,on}$  Measurement**



  
## ZVS Loss Measurement Results (1)

- Measurement of Energy Loss per Switch and Switching Period
- GaN Enhancement Mode Power Transistor (600V, 70mΩ@25°C)
- Antiparallel CREE SiC Schottky Freewheeling Diode (600V, 3.3A)





 - Switching w/ and w/o 100pF Parallel Low-Loss SMD Multilayer Ceramic Chip Capacitor (450V)
- $dv/dt$  Measured in 10%...90% of Turn-off Voltage, Behavior @ at Low  $dv/dt$  Still to be Clarified



  
## ZVS Loss Measurement Results (2)

- Analysis of a *Permanently-Off Half-Bridge* Excited with Switch Node Voltage
- Measurement of Energy Loss per Switch and Switching Period





 - Heating Indicates Losses in the Permanently-Off Devices
- Losses Comparable to the Losses of the Switching Half Bridge for Same dv/dt



  
## ZVS Loss Measurement Results (2)


- Analysis of a *Permanently-Off Half-Bridge* Excited with Switch Node Voltage
- Measurement of Energy Loss per Switch and Switching Period



- Heating Indicates Losses in the Permanently-Off Devices
- Losses Comparable to the Losses of the Switching Half Bridge for Same dv/dt


 
## Measurement of Ferrite Multi-Airgap Core "Mystery" Losses



 
  
## Multi-Airgap Inductor

- Ferrite E-Core with **50 x 0.3mm Thick Stacked Plates** as Center Post
- Power Loss of TCM Inductors Sign. Higher than Expected




- Analysis by **Fraunhofer IZM** Shows Up to Factor 10 High Core Losses (!) → “Mystery” Losses


 
## – Machining Increases Core Losses


- 1964 - E. Stern & D. Temme

→ Machining / Compressive Stress Changes BH-Loop of NiZn Ferrite




- 1974 - J. Knowles, E. Snelling

 → Compressive Stress Incr. Loss Fact., Reduces  $\mu_r$



- 1984 - E. Klokholm & H. Wolfe

 → 40  $\mu\text{m}$  Magn. Dead Surface Layer of MnZn Ferrite



- 1987 - S. Chandrasekar et al.


→ Lapping Causes Greater Residual Stress than Grinding



# Ferrite Machining Process


- Cutting of Thin Plates from Ferrite Rod with Diamond Saw
- Abrasive Machining Introduces Mech. Stress into Surface

Diamond Blade  
5000rpm

 


Machined  
Core

 
SEM Image of  
Machined MnZn  
Ferrite (3F4)



laboratory for  
*lmm*  
nanometallurgy

 

 - Ferrite Properties in Surface Altered → Increase of Loss Factor





## Subsurface Condition of Machined Ferrite




Empa

Materials Science and Technology

  - **Focused Ion Beam (FIB) Cut into Ferrite (3F4) Sample & Scanning Electron Microscopy (SEM)**
- **Polishing of Surface with Grain Sizes 2400 SiC → 4000 SiC → Colloidal Silica  $\text{SiO}_2$**




 - **Polishing Removes 500μm of Surface** → **Bulk Material Exposed**
- **Bulk Ferrite also Exhibits Cavities** → **Result of (Imperfect) Sintering Process**



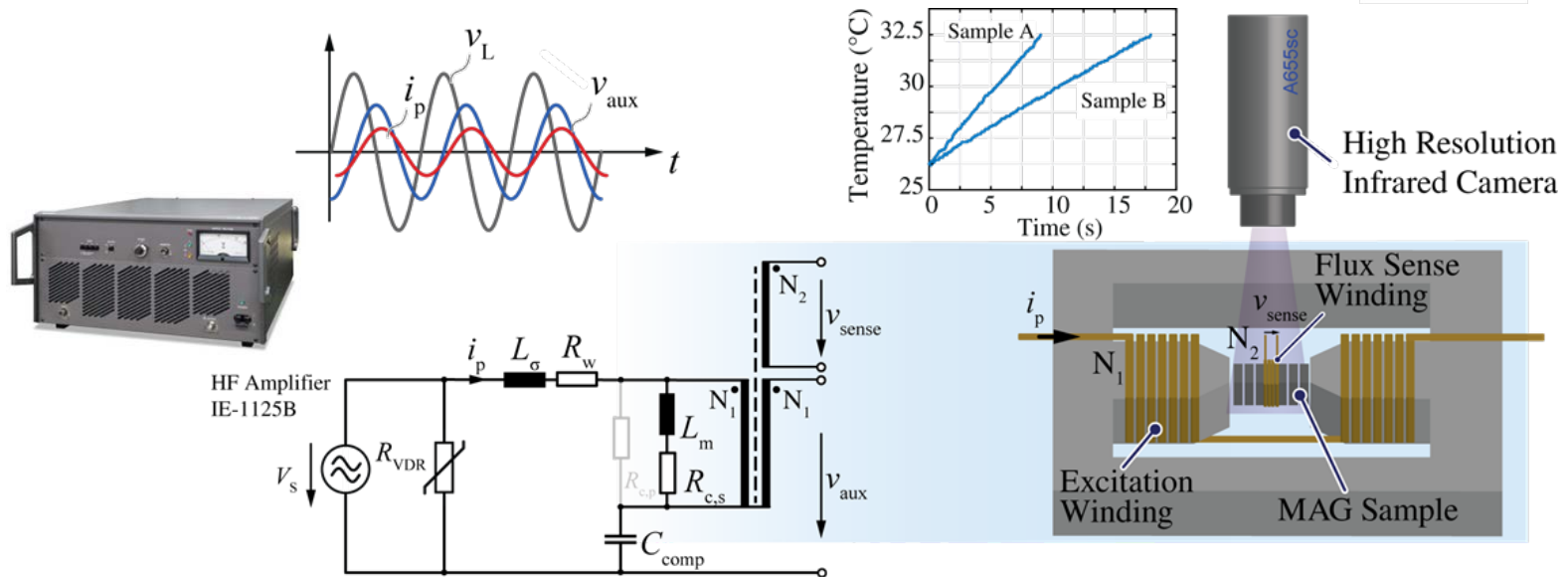
# Thermometric Surface Loss Measurement

- Impression of Homogeneous Sin. Flux Density of Desired Ampl. / Frequ.
- Cap. Series Comp. for Lowering Impedance @ High Frequencies
- Measurement of *Transient Temp. Change* → Calc. of Losses






 - Temperature Rise of  $\Delta T = 1.5^\circ \dots 5^\circ \text{C}$  Sufficient (Accuracy  $\pm 0.2^\circ \text{C}$ ), Fast Measurement (!)



   
## Test Fixture / Magnetic Circuit

- **E-Type Fixture** for Swift Installation of Diff. Samples (7mm x 6.4mm x 21.6mm)
- **FEM Optimiz. of Dimensions** – Large Core Cross Section / Tapered Outer Limbs






 - **Therm. Insul. & Airgap Lattice Ensure Low Heat Flux to Ambient**
- **Measurement of Temp. Increase Over Time Allows to Verify Homog. Flux Density in Sample**



  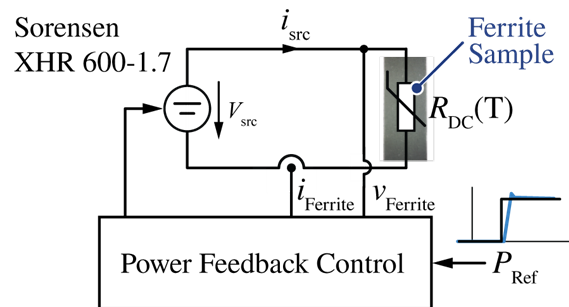
## Identification of Therm. Parameters $R_{th}$ , $C_{th}$

- DC Current Impressed in Ferrite, Voltage Control for Const. Power Dissipation as  $R_{DC}=R_{DC}(Temp.)$
- Temperature Response of Sample Recorded (FLIR A655sc W with Close-Up Lens)
- Emissivity of Ferrite Determined Using Heat Plate ( $\varepsilon=0.86$ )




 
- $R_{th} = 37.8 \text{ K/W}$  Can be Neglected
- Obtained Parameter  $C_{th}=3.83\text{J/K}$  Close to  $C_{th}$  Calc. Based on Vendor Data ( $C_{th} = 3.6\text{J/K}$ )


 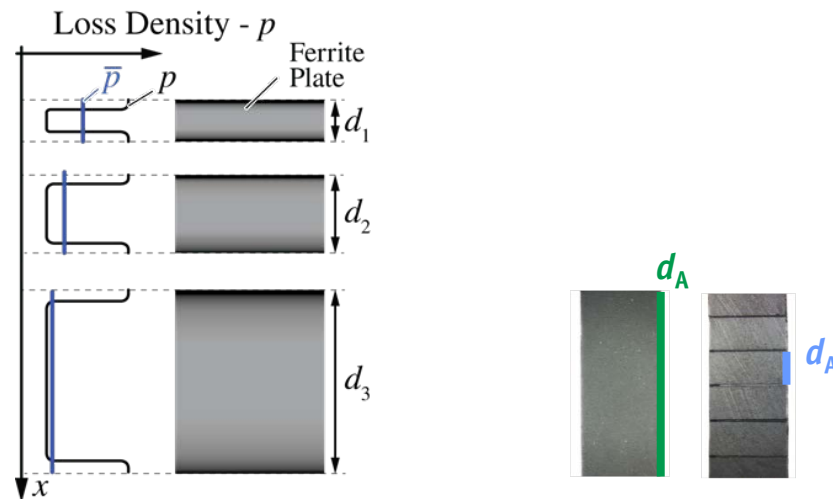
# Surface Loss Measurement Principle



- Hypothesis: Core Loss Density in Surface Layer Higher than in Bulk
- Thinner Plates  $\rightarrow$  Higher Average Losses / Faster Temp. Rise
- Stacking of Plates Does NOT Affect Temperature Rise (!)




- Surface Loss Density Can be Directly Calc. from Mat. Parameters / Geometry &  $\Delta t_A$  and  $\Delta t_B$


 
## Temperature Rise Recording


- Comparison of Solid 3F4 Sample (1 x 21.6mm) and Stacked Plates Sample (7 x 3mm)
- Sinusoidal Excitation *100mT / 400kHz*




3F4 Solid Sample / 21.6mm



7 Plates 3F4 / 3mm


 


 - Thermal Image shown *25 Seconds After Turn-On* of Magnetic Excitation


  
## Measurement Results – Bulk Losses

- Comparison of Measurement Results and Datasheet Values, 3F4 @ 25°C
- Measurement Error Approx.  $\pm 10\%$  (Worst Case)




- Good Agreement with Datasheet Values / Vendor Steinmetz Parameters




 
## Measurement Results – Surface Losses


- Measurement Error Approx.  $\pm 25\%$  (Worst Case)
- Error Determined by Meas. Time & Temp. Reading Accuracy


  
$$p_{Surf} = 0.0615 \times \left(\frac{f}{1\text{Hz}}\right)^{1.13} \times \left(\frac{\hat{B}}{1\text{T}}\right)^{3.47} \left(\frac{\text{mW}}{\text{cm}^2}\right)$$






 - Comp. of Steinmetz Parameters of Surface Losses & Bulk Losses  $BS > B$ ,  $aS < a$


   
## “Critical Thickness” of Ferrite Plates


- “Critical Thickness” Reached for **Equal Losses in Bulk & Surface**
- Critical Plate Thickness is **INDEPENDENT** of Cross Section (!)



- Dependence on Flux Density Ampl. & Frequency !
- Dependence on Material / Machining Process / Power Processing Treatment

 
## $\eta\rho$ -Pareto Optimization of Little Box 1.0

$\eta\rho$ -Pareto Front  
TCM vs. Large Ripple PWM  
**The Ideal Switch is Not Enough (!)**  
Design Space Diversity



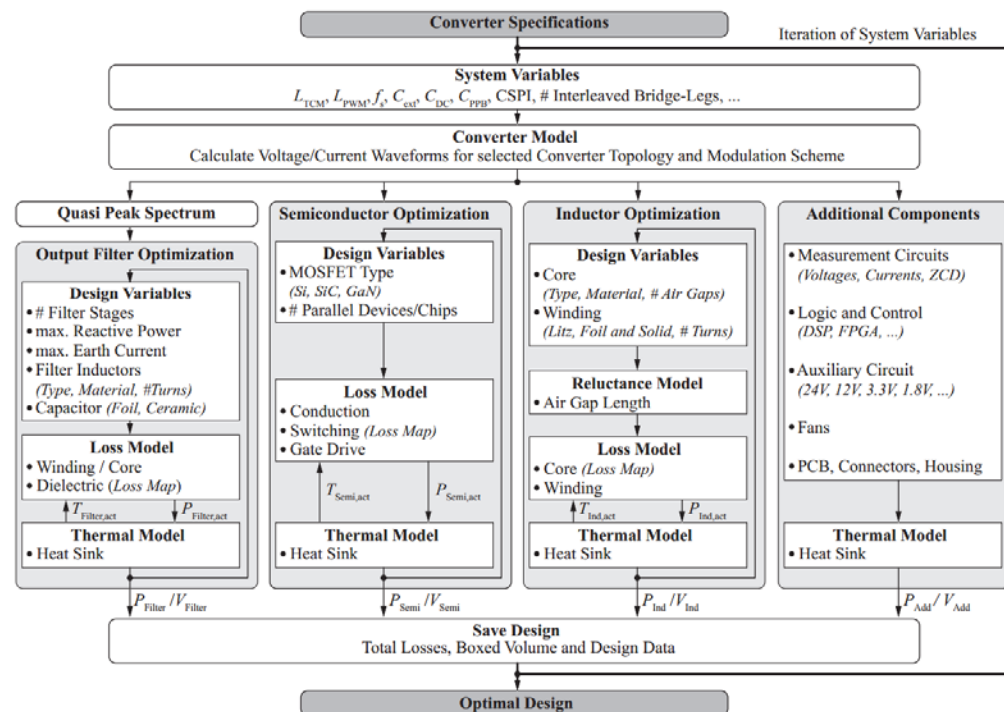
## Multi-Objective Optimization

- Detailed *System Models* → Power Buffer/Output Stage/EMI Filter
- Multi-Domain *Component Models* → Passives & GaN & SiC Semicond.
- Consideration of Very Large # of Degrees of Freedom




 ■ Pareto Optimization Shows Trade-Off Between Power Density and Efficiency


 
## Little Box 1.0 $\eta$ -Performance Limits


- Multi-Objective Optimization of Little-Box 1.0 (incl. CeraLink  $\rightarrow$  X6S)
- Absolute Performance Limits (I) - DSP/FPGA Power Consumption  
(II) - Heatsink Volume @  $(1-\eta)$



(a) ★ Realized Prototype

 
(b) CeraLink Power Pulsation Buffer  
(c) X6S Power Pulsation Buffer

- Further Performance Improvement for Triangular Current Mode (TCM)  $\rightarrow$  PWM



 
## Little Box 1.0 -- TCM $\rightarrow$ PWM

- Very High Sw. Frequency  $f_s$  of TCM Around Current Zero Crossings
- Efficiency Reduction due to Residual TCM Sw. Losses & Gate Drive Losses Reduction
- Wide  $f_s$ -Variation Represents Adv. & Disadvantage for EMI Filter Design



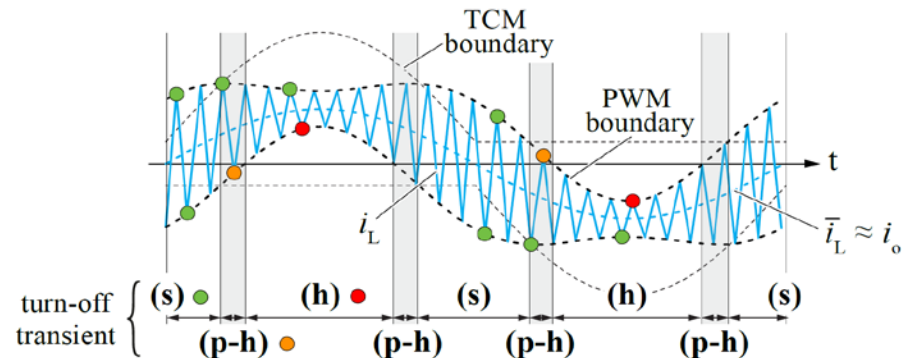(s) Soft-Switching (ZVS)  
(p-h) Partial Hard Switching  
(h) Hard-Switching






- PWM -- Const. Sw. Frequency & Lower Conduction Losses
- PWM @ Large Current Ripple -- ZVS in Wide Intervals



   
## Little Box 1.0 -- TCM → PWM

- Optimization for GaN GIT & No Interleaving
- Resulting Opt. Inductance of Output Inductor  $L=10\mu\text{H}$  (TCM),  $L=30\mu\text{H}$  (PWM@140 kHz)




 $\rho = 11.9 \text{ kW/dm}^3$   
 $\eta = 97.4\%$




$\rho = 12.5 \text{ kW/dm}^3$   
 $\eta = 97.4\%$

 ■ PWM vs. TCM → Slightly Higher Max. Power Density @ Same Efficiency


 
## Little Box 1.0 -- Electrolytic Cap. / Active PPB


- Analysis for Google Little Box Challenge Specification  $\Delta V/V < 3\%$
- Efficiency Benefit of PPB only for  $\rho > 9\text{kW/dm}^3$



- Electrolytics Favorable for High Efficiency @ Moderate Power Density ( $\Delta\eta = +0.5\%$ )
- Electrolytics Show Lower Vol. & Lower Losses if Large  $\Delta V/V$  is Acceptable (e.g. for PFC Rectifiers)





The Ideal Switch is  
Not Enough (!) →

 

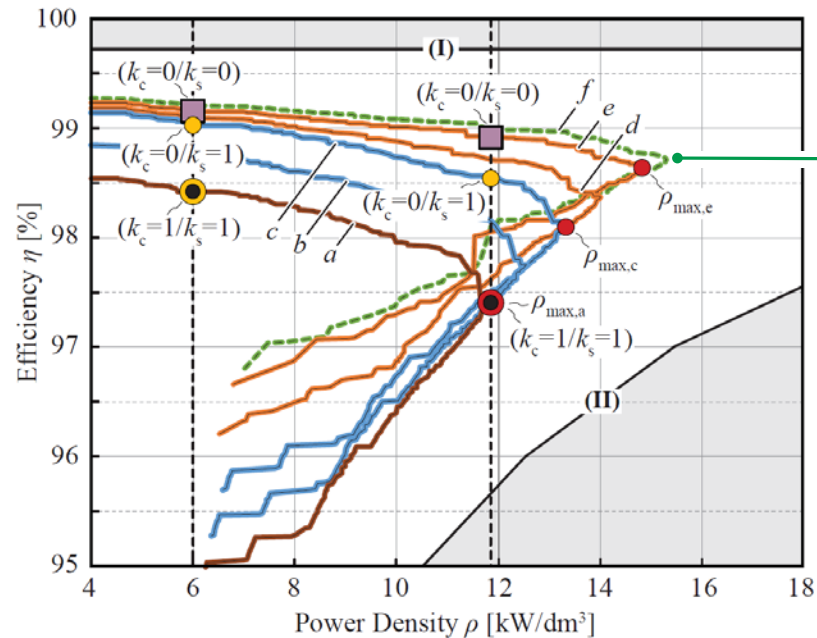 
## Little Box 1.0 @ Ideal Switches -- TCM

- Multi-Objective Optimization of Little-Box 1.0 (X6S Power Pulsation Buffer)
- Step-by-Step Idealization of the Power Transistors
- Ideal Switches:  $k_c = 0$  (Zero Cond. Losses);  $k_s = 0$  (Zero Sw. Losses)





Zero Output Cap.  
and Zero Gate  
Drive Losses
 
### ■ Analysis of Improvement of Efficiency @ Given Power Density & Maximum Power Density


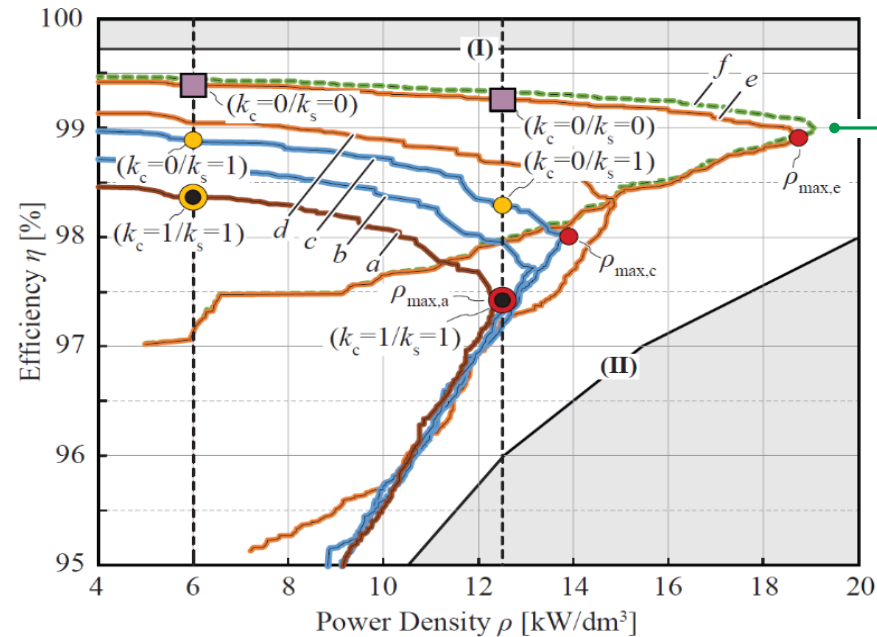 
## Little Box 1.0 @ Ideal Switches -- PWM

- Multi-Objective Optimization of Little-Box 1.0 (X6S Power Pulsation Buffer)
- Step-by-Step Idealization of the Power Transistors
- Ideal Switches:  $k_c=0$  (Zero Cond. Losses);  $k_s=0$  (Zero Sw. Losses)







Zero Output Cap.  
and Zero Gate  
Drive Losses

- Analysis of Improvement of Efficiency @ Given Power Density & Maximum Power Density


    
## Little Box 1.0 @ Ideal Switches -- PWM




$\rho = 6 \text{ kW/dm}^3$   
 $\eta \approx 99.35\%$

$L = 50 \mu\text{H}$   
 $f_s = 500 \text{ kHz or } 900 \text{ kHz}$

- $L$  &  $f_s$  are Independent Variables (Dependent for TCM)
- Large Design Space Diversity (Mutual Compensation of HF and LF Loss Contributions)

## Little Box 2.0

 


250 W/in<sup>3</sup>


DC/ | AC | Converter + Unfolder  
PWM vs. TCM incl. Interleaving  
 $\eta$ -Pareto Limits for Non-Ideal Switches  
Preliminary Exp. Results  
Final 3D-CAD

## Little Box 2.0 -- New Converter Topology (1)

- **Alternative Converter Topology → Only Single HF Bridge Leg + 60Hz-Unfolder**
- **DC/ | AC | - Buck Converter + Full-Bridge Unfolder OR HF Half-Bridge & Half-Bridge Unfolder**

 

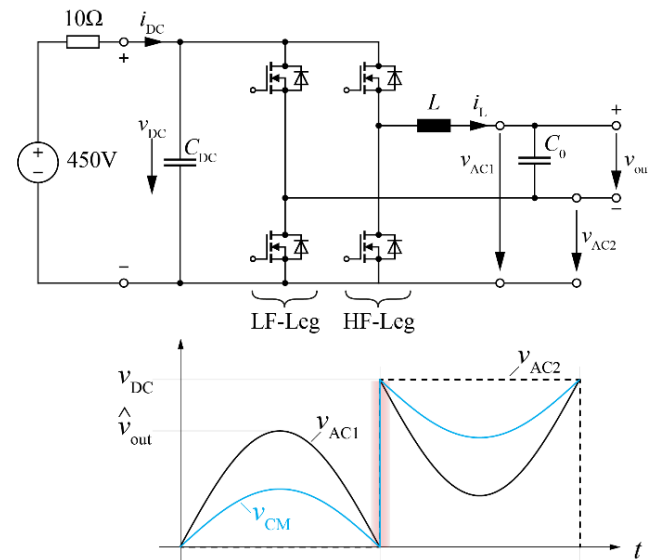- $V_{AC1}, V_{AC2}$  More Diff. to Gen. but Add. DOF
- Higher Sw. & Gate Drive Losses
- Zero Low-Frequ. CM-Noise (DC Comp. Only)
- $C_{CM}$  Not Limited by Allowed Gnd Current





- $V_{AC1}$  More Difficult to Generate/Control
- Lower Conduction Losses
- Higher CM-Noise (DC and  $n \times 120\text{Hz}$ -Comp.)
- $C_{CM}=150\text{nF}$  Allowed for 50mA Gnd Current





## Little Box 2.0 -- New Converter Topology (2)

- **Alternative Converter Topology** → Only Single HF Bridge Leg + 60Hz-Unfolder
- **DC/|AC| - Buck Converter + Full-Bridge Unfolder** OR **HF Half-Bridge & Half-Bridge Unfolder**

 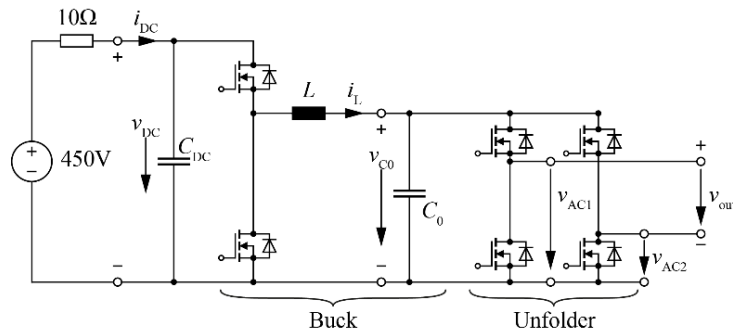

 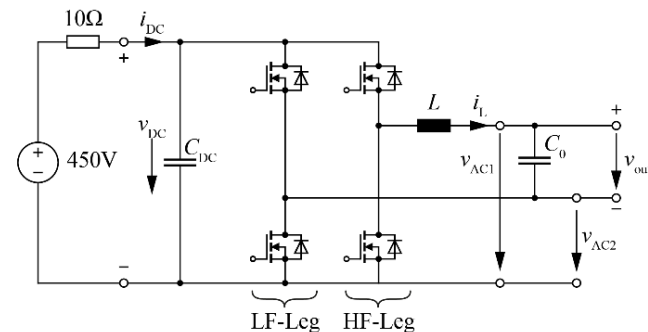- $v_{C0}$  Easy to Generate/Control
- **Higher** Cond. Losses Due to FB-Unfolder
- **Lower** CM-Noise (DC &  $n \times 120\text{Hz}$ -Comp.)
- $C_{CM}=700\text{nF}$  Allowed for 50mA Gnd Current




- $v_{AC1}$  More Difficult to Generate/Control
- **Lower** Cond. Losses
- **Higher** CM-Noise (DC and  $n \times 120\text{Hz}$ -Comp.)
- $C_{CM}=150\text{nF}$  Allowed for 50mA Gnd Current



## Little Box 2.0 -- New Converter Topology (3)

- **Alternative Converter Topology** - DC/|AC| - Buck Converter + Unfolder
- **60Hz-Unfolder** (Temporary PWM for Ensuring Cont. Current Control)
- **TCM** or **PWM** of DC/|AC| - Buck-Converter

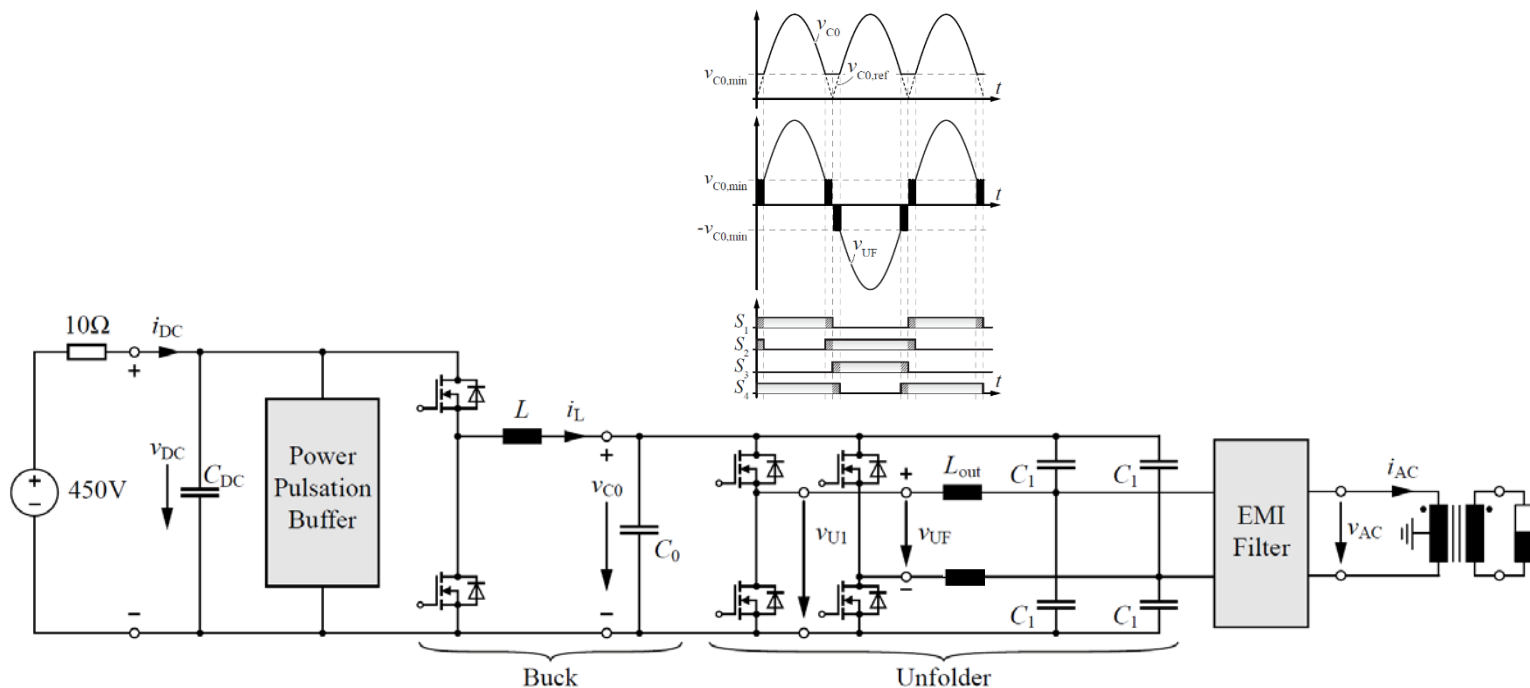


- **Full Optimization** of All Converter Options for **Real Switches** / X6S Power Pulsation Buffer




 
## Little Box 2.0 -- Multi-Objective Optimization

- DC/AC - Buck Converter (Single PWM Bridge Leg) + Unfolder Shows Best Performance
- Full-Bridge Would Employ 2 Switching Bridge Legs - Larger Volume & Losses
- Interleaving Not Advantageous - Lower Heatsink Vol. / Larger Vol. of Switches and Inductors



■  $\rho = 250\text{W/in}^3$  ( $15\text{kW/dm}^3$ ) @  $\eta = 98\%$  Efficiency Achievable for Full Optimization


*3D-CAD Construction  
of the Final System*



**250 W/in<sup>3</sup>**



 
## Little Box 2.0 -- Mechanical Construction (1)



■ 60 mm x 50 mm x 45 mm = 135 cm<sup>3</sup> (8.2 in<sup>3</sup>) → 14.8 kW/dm<sup>3</sup> (243 W/in<sup>3</sup>)



 
## Little Box 2.0 -- Mechanical Construction (2)



■ 60 mm x 50 mm x 45 mm = 135 cm<sup>3</sup> (8.2 in<sup>3</sup>) → 14.8 kW/dm<sup>3</sup> (243 W/in<sup>3</sup>)



 
## Little Box 2.0 -- Mechanical Construction (3)



■ 60 mm x 50 mm x 45 mm = 135 cm<sup>3</sup> (8.2 in<sup>3</sup>) → 14.8 kW/dm<sup>3</sup> (243 W/in<sup>3</sup>)



 
## Little Box 2.0 -- Mechanical Construction (4)



■ 60 mm x 50 mm x 45 mm = 135 cm<sup>3</sup> (8.2 in<sup>3</sup>) → 14.8 kW/dm<sup>3</sup> (243 W/in<sup>3</sup>)


 
## Little Box 2.0 -- Mechanical Construction (5)



■ 60 mm x 50 mm x 45 mm = 135 cm<sup>3</sup> (8.2 in<sup>3</sup>) → 14.8 kW/dm<sup>3</sup> (243 W/in<sup>3</sup>)






## Little Box 2.0 -- Demonstrator

★ 240 W/in<sup>3</sup>

Output Filter

Inductors  
(Buck-Stage &  
Unfolder)

Power Board  
Control Board

 

PPB Capacitor

Heat Sink + Fans

■ 60 mm x 50 mm x 45 mm = 135 cm<sup>3</sup> (8.2 in<sup>3</sup>) → 14.8 kW/dm<sup>3</sup> (243 W/in<sup>3</sup>)






## Little Box 2.0 -- Demonstrator

★ 240 W/in<sup>3</sup>

PPB Capacitor

Heat Sink + Fans

 

PPB Capacitor

Inductors  
(Buck-Stage &  
Unfolder)

Power Board

Control Board

■ 60 mm x 50 mm x 45 mm = 135 cm<sup>3</sup> (8.2 in<sup>3</sup>) → 14.8 kW/dm<sup>3</sup> (243 W/in<sup>3</sup>)

## Experimental Results


Control Block Diagram

Output Voltage / Input Current Quality

Efficiency



## Little Box 2.0 – Control Structure


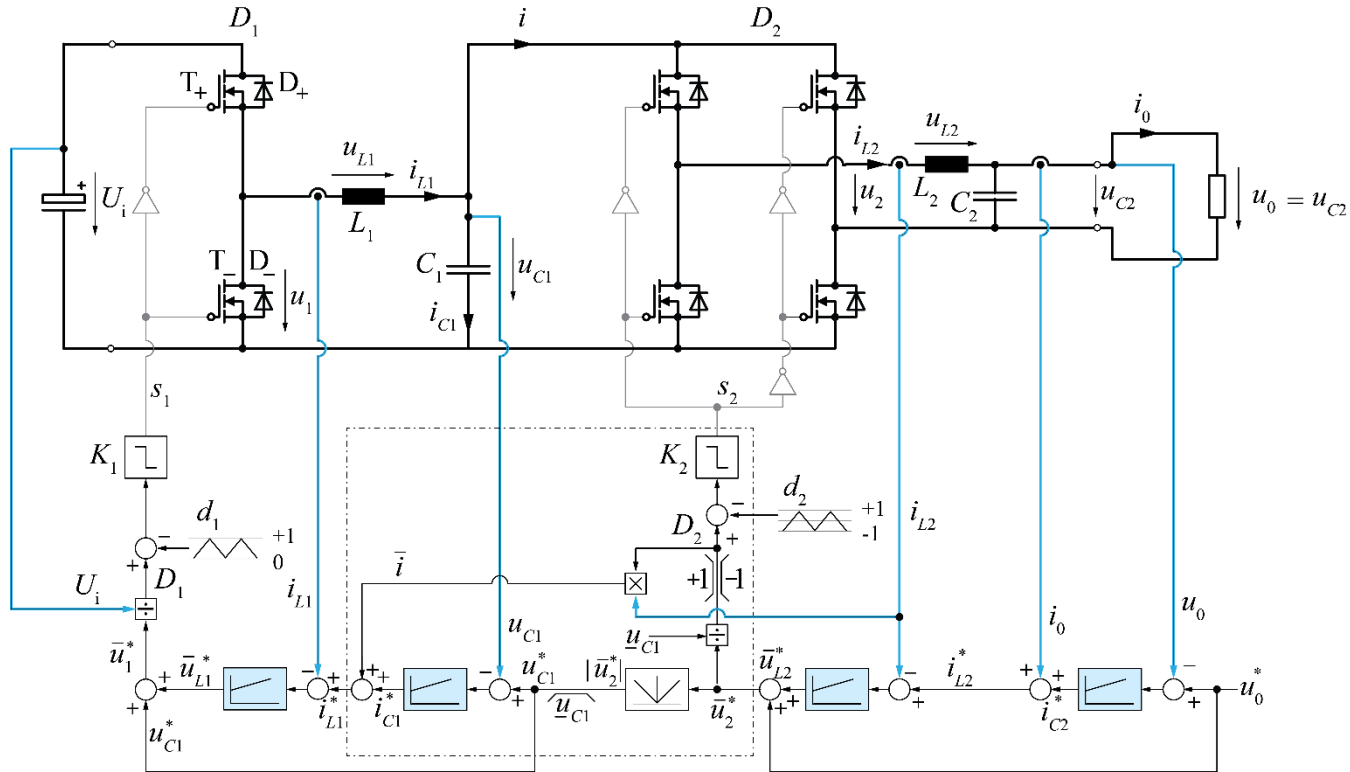


- Each Stage (Buck & Unfolder) Controlled with Cascaded Current and Voltage Loop
- Without Switching of Unfolder Control Like for Conventional Boost PFC Rectifier


  
## Little Box 2.0 – Experimental Results (1)

- Voltage Zero Crossing Behavior With (Right) & Without (Left) Switching of Unfolder




Output Voltage (200V/div)  
Output Current (10A/div)  
Buck Inductor Current (10A/div)  
Unfolder Output Voltage (200V/div)

- Output Voltage & Current Fully Controlled Around Voltage Zero Crossings
- Slope of Buck Conv. Outp. Curr. can be Decreased – Adv. for React. Loads (No Step-Change of DC Curr.)




## Little Box 2.0 – Experimental Results (2)


- DC/|AC| Buck-Stage Output Voltage & Inductor Current

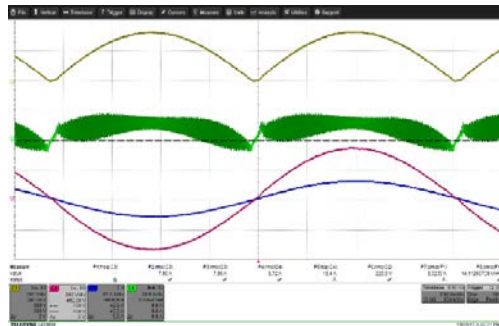

■ Resistive Load

 

■ Inductive Load

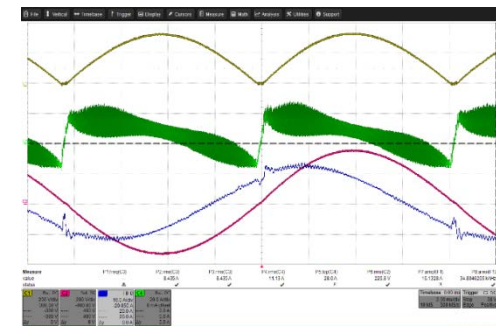


■ Capacitive Load



## Little Box 2.0 – Experimental Results (3)

- Performance of First DC/ | AC | - Buck Converter + Unfolder Prototype
- PWM Operation
- Without Power Pulsation Buffer

 


- 98% for Res. Load Achievable if Cond. Losses of PCB (Copper Cross Sect.) & Unfolder ( $R_{ds,on}$ ) are Red.


 
## Litte Box 2.0 – Performance Comparison


- 18 Finalists (3 No-Shows)
- 7 Groups of Consultants / 7 Companies / 4 Universities

**Note:** Numbering of Teams is Arbitrary



- (1) Virginia Tech
- (2) Schneider Electric
- (3) EPRI (Univ. of Tennessee)
- (4) Venderbosch
- (5) Energy Layer
- (6) ETH Zurich
- (7) Rompower
- (8) Tommasi-Bailly
- (9) Red Electric Devils
- (10) AHED
- (11) FH IISB
- (12) Univ. of Illinois
- (13) AMR

- 70...300  $\text{W}/\text{in}^3$
- 35 kHz...500kHz...1 MHz (up to 1MHz: 3 Teams)
- Full-Bridge or DC/|AC| Buck Converter + Unfolder
- Mostly Buck-Type Active Power Pulsation Filters (Ceramic Caps of Electrolytic Caps)
- GaN (11 Teams) / SiC (2 Teams) / Si (2 Teams)

 

Source: whiskeybehavior.info

## Overall Summary





## Performance Limits / Future Requirements

- 220...250W/in<sup>3</sup> for Two-Level Bridge Leg + Unfolder
- 250...300W/in<sup>3</sup> for Highly Integrated Multi-Level Approach
- Isol. Distance Requirements Difficult to Fulfill
- Fulfilling Industrial Inp. Overvoltage Requirem. would Signific. Reduce Power Density
  
- Low Frequency (20kHz...120kHz) SiC vs. HF (200kHz...1.2MHz) GaN
- Multi-Cell Concepts for LV Si (or GaN) vs. Two-Level SiC (or GaN)
  
- New Integr. Control Circuits and  $i=0$  Detection for Sw. Frequency >1MHz
- Integrated Gate Drivers & Switching Cells
- High Frequency Low Loss Magnetic Materials
- High Bandwidth Low-Volume Current Sensors
- Low Loss Ceramic Capacitors Tolerating Large AC Ripple
- Passives w. Integr. Heat Management and Sensors
- 3D Packaging
  
- New U-I-Probes Required for Ultra-Compact Conv. R&D
- Specific Systems for Testing → Devices Equipped with Integr. Measurement Functions
- Convergence of Sim. & Measur. Tools → Next Gen. Oscilloscope
- New Multi-Obj. Multi-Domain Simulation/Optim. Tools

**Thank You!**

# Questions







 
## Future Development 1/2

- Commoditization / Standardization
- Extreme Cost Pressure (!)




► Key Importance of Technology Partnerships of Academia & Industry



## Future Development 2/2

 
### ■ Extrapolation of Technology S-Curve



 
## Technology Progress – Technology Push

- WBG Semiconductor Technology
- Microelectronics

→ Higher Efficiency, Lower Complexity  
→ More Computing Power



→ + Advanced Packaging (!)


 


→ Moore's Law

## System / Smart Grid Drivers
  
### ■ Metcalfe's Law



- Moving from Hub-Based Concept to Community Concept Increases Potential Network Value Exponentially ( $\sim n(n-1)$  or  $\sim n \log(n)$ )







 
 
# Technology Sensitivity Analysis Based on $\eta$ - $\rho$ -Pareto Front

- Sensitivity to Technology Advancements
- Trade-off Analysis





# Converter Performance Evaluation Based on $\eta$ - $\rho$ - $\sigma$ -Pareto Surface

►  $\sigma$ : kW/\$

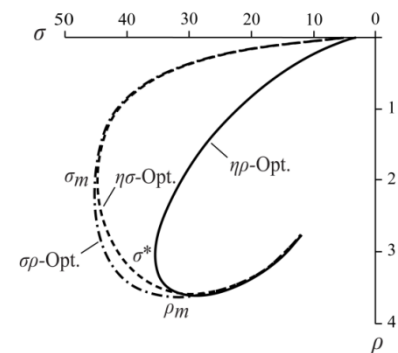   

# Converter Performance Evaluation Based on $\eta$ - $\rho$ - $\sigma$ -Pareto Surface

## ► 'Technology Node'

  

Technology Node:  $(\sigma^*, \eta^*, \rho^*, f_P^*)$

# Future Development

## “Devices”

- Minimize / Avoid Packages → (PCB) Embedding
- Integrate Driver Stage
- Integrate Sensors / Monitoring
- Multiple Use of Isolated Gate Drive Communication Channel
- Offer Test Devices with Integrated Measurement Function
- Facilitate (Double Sided) Heat Extraction

## Converters

- Standardized Very Low Cost Building Blocks
- “Application Specific” = Wide Operating Range Standardized Blocks
- Self-Parametrization
- Bidirectional Converters

## Systems

- AC and DC Distribution
- Single Converter vs. Combination of Modules / Cells
- Initial Costs / Life Cycle Cost Trade-off
- Grid 4.0

## Design

- Minimize Design Time / Fully Computerized
- Maximize Design Flexibility for Appl. Specific Solution (PCB)
- Maximize Design Insight for Trade-off Analysis
- Design for Manufacturing (Planar / PCB Based)

## Literature

- More & More “White Noise”