

Intelligente Transformatoren für das Energienetz der Zukunft


Konzepte – Herausforderungen – Anwendungen

Johann W. Kolar

Swiss Federal Institute of Technology (ETH) Zurich
Power Electronic Systems Laboratory
www.pes.ee.ethz.ch



Power Electronic Systems Laboratory

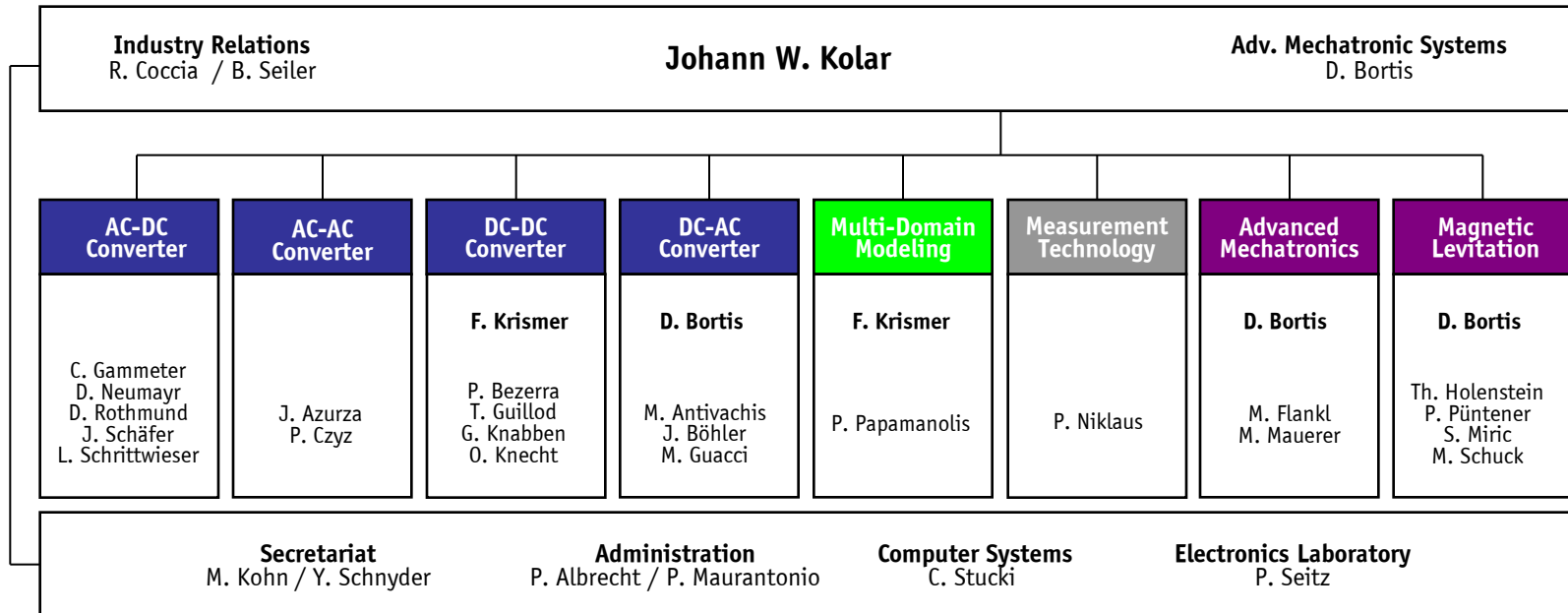

22 Ph.D. Students
2 Sen. Level Researchers



**Leading Univ.
in Europe**

Outline

- ▶ Transformer Basics
- ▶ Solid-State Transformer (SST) Concept
- ▶ Key SST Realization Challenges
 - #1 Power Semiconductors
 - #2 Topologies
 - #3 Medium Frequency Transformer
 - #4 Protection
 - #5 Reliability
- ▶ Industry Demonstrator Systems
- ▶ Potential Future Applications
- ▶ Conclusions

Acknowledgement:

Dr. J. Huber
Dr. G. Ortiz
P. Czyz
T. Guillod
D. Rothmund

Transformer Basics

History
Scaling Laws
—— *Efficiency / Power Density Trade-off* ——


► Classical Transformer (XFMR) – History (1)

- * 1830 - Henry/Faraday
- * 1878 - Ganz Company (Hungary)
- * 1880 - Ferranti
- * 1882 - Gaulard & Gibbs
- * 1884 - Blathy/Zipernowski/Deri

- Property of Induction
- Toroidal Transformer (AC Incandescent Syst.)
- Early Transformer
- Linear Shape XFMR (1884, 2kV, 40km)
- Toroidal XFMR (Inverse Type)

Europe

USA

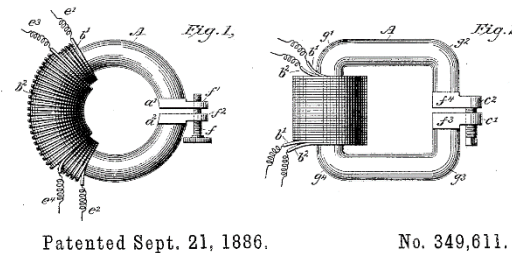

W. STANLEY, Jr.
INDUCTION COIL.



- * 1885 - Stanley & (Westinghouse)

- Easy Manufact. XFMR (1st Full AC Distr. Syst.)

► Classical Transformer – History (2)



UNITED STATES PATENT OFFICE.

MICHAEL VON DOLIVO-DOBROWOLSKY, OF BERLIN, GERMANY, ASSIGNOR TO
THE ALLGEMEINE ELEKTRICITÄTS-GESELLSCHAFT, OF SAME PLACE.

ELECTRICAL INDUCTION APPARATUS OR TRANSFORMER.

SPECIFICATION forming part of Letters Patent No. 422,746, dated March 4, 1890.

Application filed January 8, 1890. Serial No. 336,290. (No model.)


(No Model.)

M. VON DOLIVO-DOBROWOLSKY.

ELECTRICAL INDUCTION APPARATUS OR TRANSFORMER.

No. 422,746.

Patented Mar. 4, 1890.

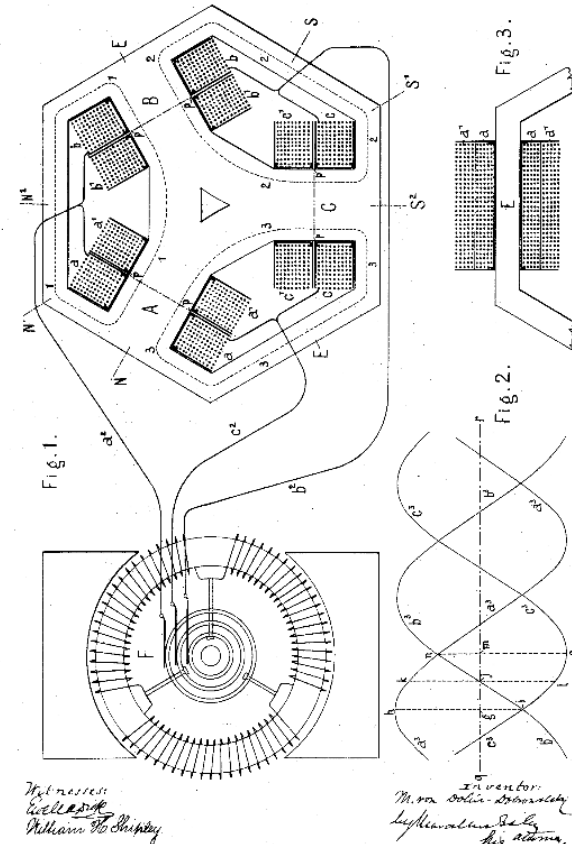

* 1890
* 1891

- Dobrowolski → 3-Phase Transformer
- 1st Complete AC System (Gen.+XFMR+Transm.+El. Motor+Lamps, 40Hz, 25kV, 175km)

► Classical Transformer – Basics (1)

- Magnetic Core Material * **Silicon Steel** / Nanocrystalline / Amorphous / Ferrite
- Winding Material * **Copper** or Aluminium
- Insulation/Cooling * **Mineral Oil** or Dry-Type

- Operating Frequency * **50/60Hz** (El. Grid, Traction) or **16²/3 Hz** (Traction)
- Operating Voltage * **10kV** or **20 kV** (6...35kV)
- * **15kV** or **25kV** (Traction)
- * **400V**



- **Voltage Transf. Ratio** * **Fixed**
- **Current Transf. Ratio** * **Fixed**
- **Active Power Transf.** * **Fixed** ($P_1 \approx P_2$)
- **React. Power Transf.** * **Fixed** ($Q_1 \approx Q_2$)
- **Frequency Ratio** * **Fixed** ($f_1 = f_2$)

- **Magnetic Core Cross Section**

$$A_{Core} = \frac{1}{\sqrt{2\pi}} \frac{U_1}{\hat{B}_{max}} \frac{1}{f N_1}$$

- **Winding Window**
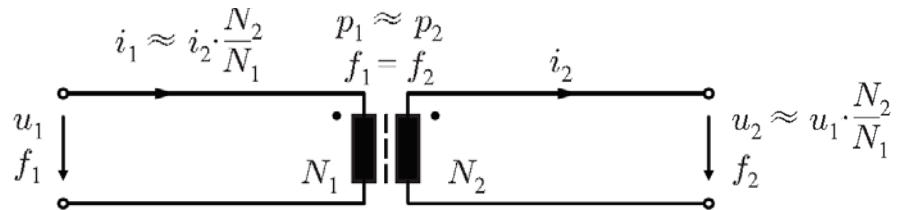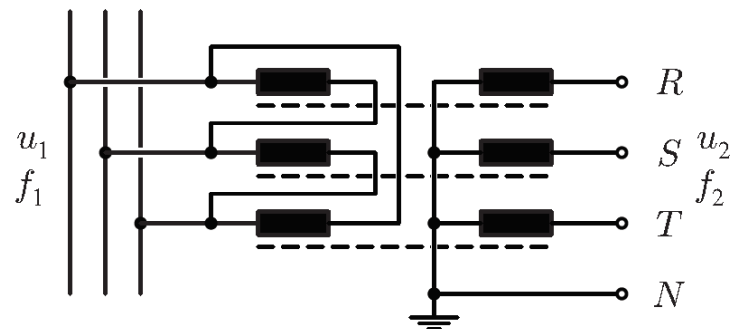
$$A_{Wdg} = \frac{2I_1}{k_W J_{rms}} N_1$$



► Classical Transformer – Basics (2)

Source: www.faceofmalawi.com

■ Advantages

- Relatively Inexpensive
- **Highly Robust / Reliable**
- Highly Efficient
- Short Circuit Current Limitation



► Classical Transformer – Basics (3)

■ Advantages

- Relatively Inexpensive
- Highly Robust / Reliable
- Highly Efficient (98.5%...99.5% Dep. on Power Rating)
- Short Circuit Current Limitation

■ Weaknesses

- Voltage Drop Under Load
- Losses at No Load
- Not Directly Controllable
- Dependency of Weight / Volume on Frequency
- Sensitivity to DC Offset Load Imbalances
- Sensitivity to Harmonics

• Construction Volume

P_t Rated Power

k_w Window Utilization Factor

B_{max} ... Flux Density Amplitude

J_{rms} ... Winding Current Density

f Frequency

$$A_{Core} A_{Wdg} = \frac{\sqrt{2}}{\pi} \frac{P_t}{k_w J_{rms} \hat{B}_{max} f}$$

↑ ↑ ↑

- Low Frequency → Large Weight / Volume

Vacuum Cast Coil Dry-Type
Distribution Transformer



1 MVA – 12kV/400V @ 2600kg
0.2%/1% Losses @ No/Rated Load

SST Motivation



*Next Generation
Traction Vehicles*



► Classical Locomotives

- Catenary Voltage **15kV or 25kV**
- Frequency **$16\frac{2}{3}$ Hz or 50Hz**
- Power Level **1...10MW typ.**

Source: www.abb.com

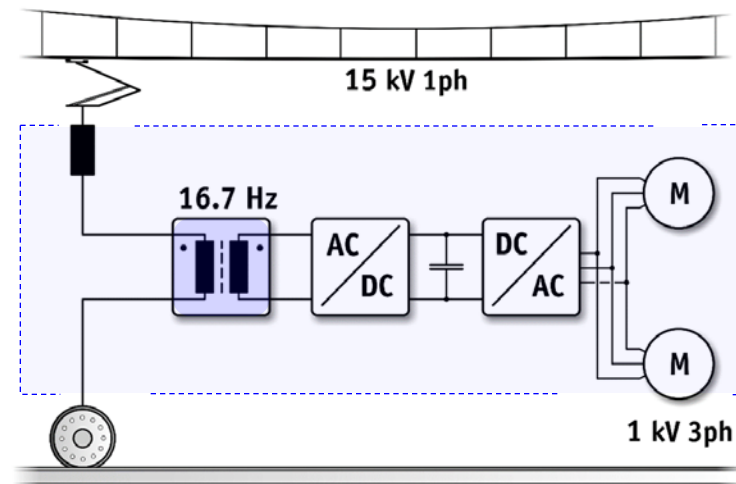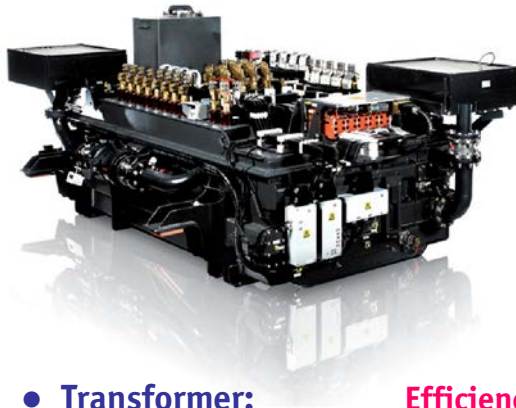

- Transformer:


Efficiency
Current Density
Power Density

90...95% (due to Restr. Vol., 99% typ. for Distr. Transf.)
6 A/mm² (2A/mm² typ. Distribution Transformer)
2...4 kg/kVA


► Next Generation Locomotives

- Trends
 - * Distributed Propulsion System → Volume Reduction (Decreases Efficiency)
 - * Energy Efficient Rail Vehicles → Loss Reduction (Requires Higher Volume)
 - * Red. of Mech. Stress on Track → Mass Reduction

Source: ABB

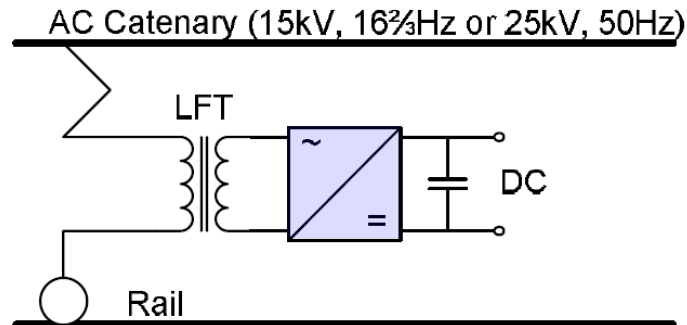

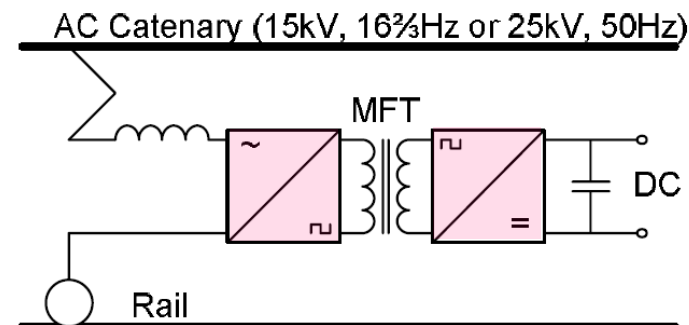Conventional AC-DC conversion with a line frequency transformer (LFT).





AC-DC conversion with medium frequency transformer (MFT).

- Replace LF Transformer by **Medium Frequency Power Electronics Transformer** → **SST**
- **Medium Frequency Provides Degree of Freedom** → **Allows Loss Reduction AND Volume Reduction**

► Next Generation Locomotives

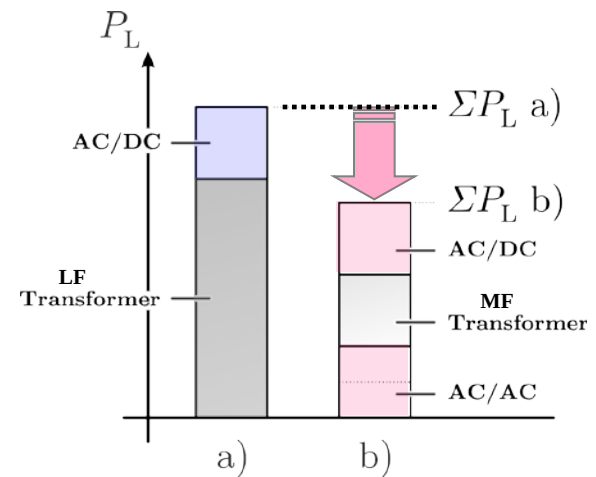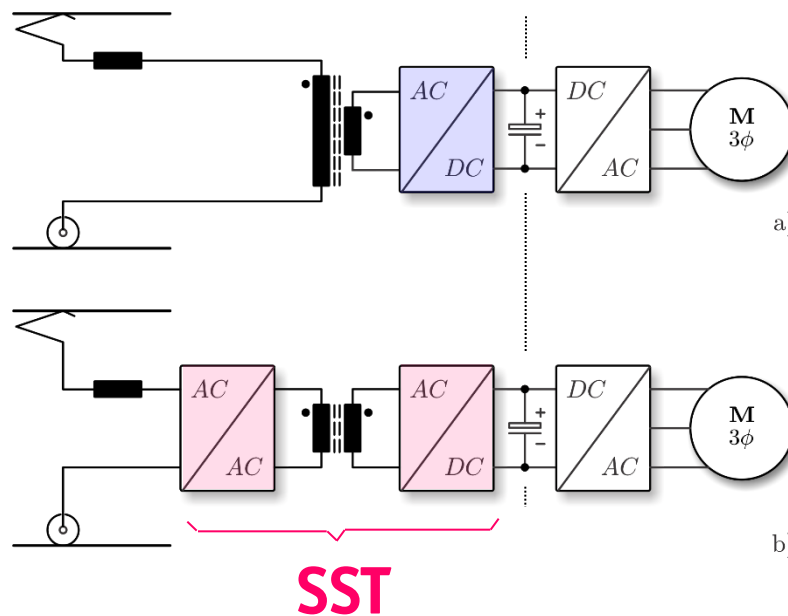- Loss Distribution of Conventional & Next Generation Locomotives



- Medium Freq. Provides Degree of Freedom → Allows Loss Reduction **AND** Volume Reduction


Future Smart EE Distribution



Source: TU Munich

► Advanced (High Power Quality) Grid Concept

- Heinemann / ABB (2001)

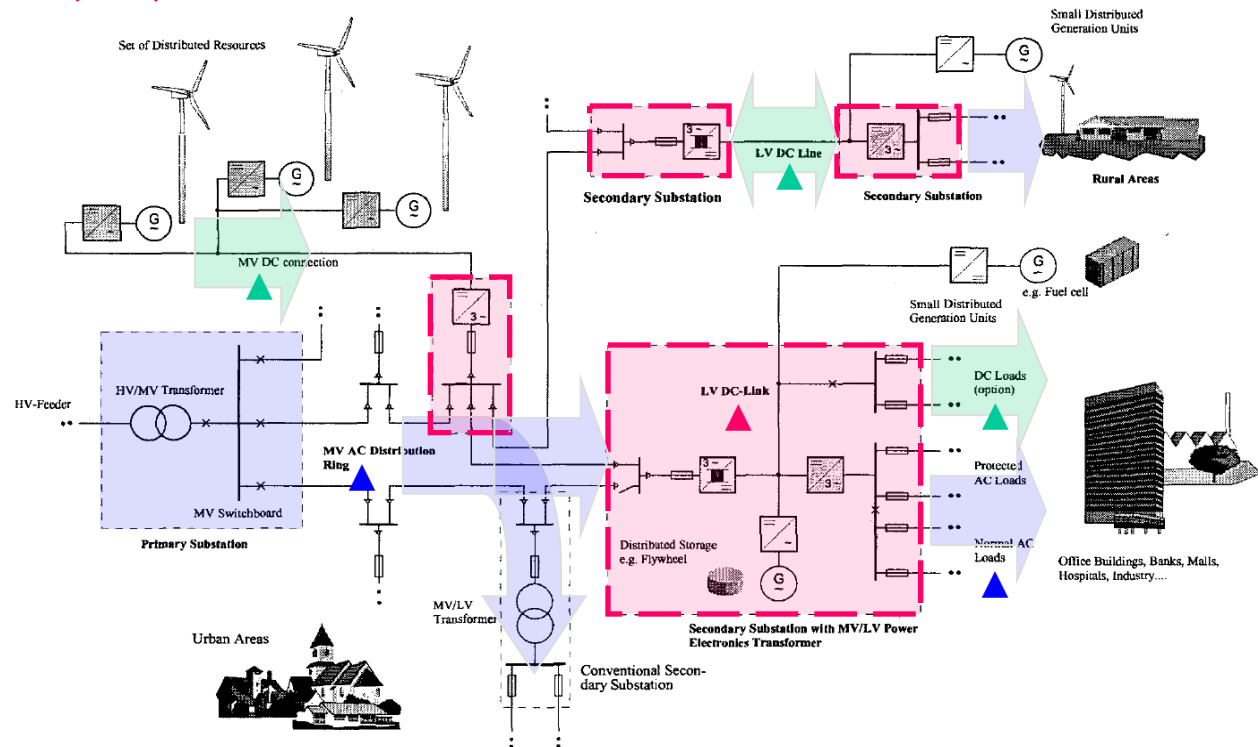

- MV AC Distribution with DC Subsystems (LV and MV) and Large Number of Distributed Resources
- MF AC/AC Conv. with DC Link Coupled to Energy Storage provide High Power Qual. for Spec. Customers

► Future Ren. Electric Energy Delivery & Management (FREEDM) Syst.


- Huang et al. (2008)

• SST as Enabling Technology for the “Energy Internet”

- Full Control of the Power Flow
- Integr. of DER (Distr. Energy Res.)
- Integr. of DES (Distr. E-Storage) + Intellig. Loads
- Protects Power Syst. From Load Disturbances
- Protects Load from Power Syst. Disturbances
- Enables Distrib. Intellig. through COMM
- Ensure Stability & Opt. Operation
- etc.
- etc.




IFM = Intellig. Fault
Management

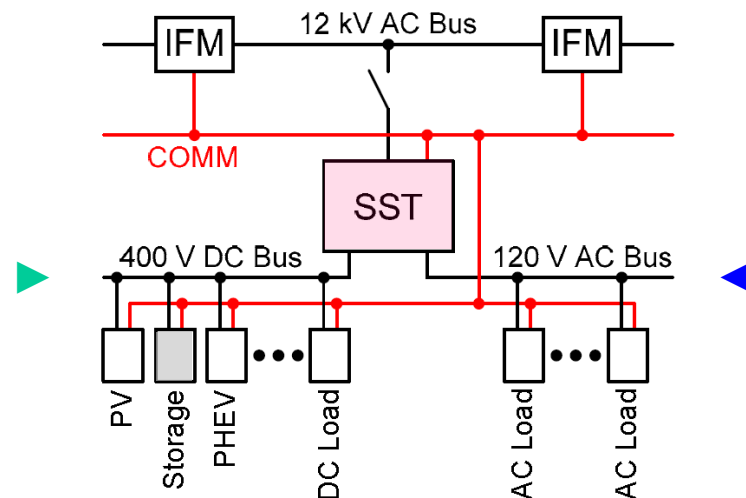

- Bidirectional Flow of Power & Information / High Bandw. Comm. → Distrib. / Local Autonomous Cntrl


► Passive Transformer → SST

- Efficiency Challenge

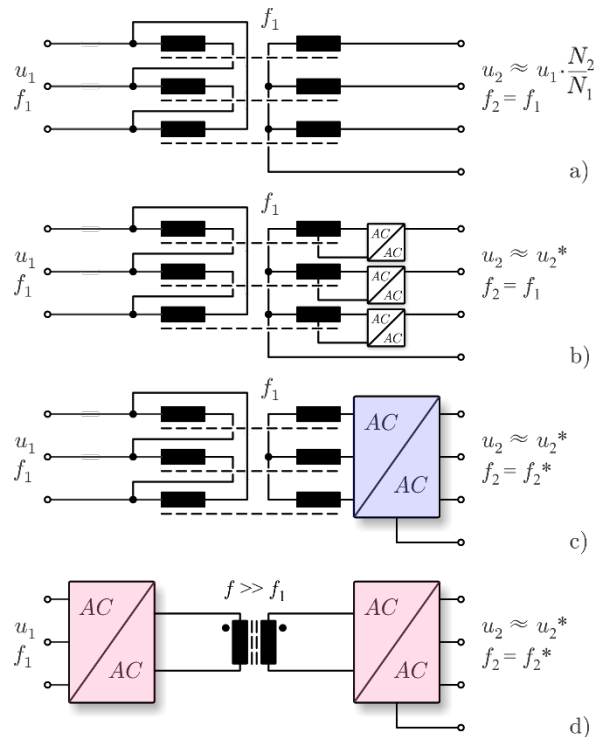

LF Isolation
Purely Passive (a)
Series Voltage Comp. (b)
Series AC Chopper (c)

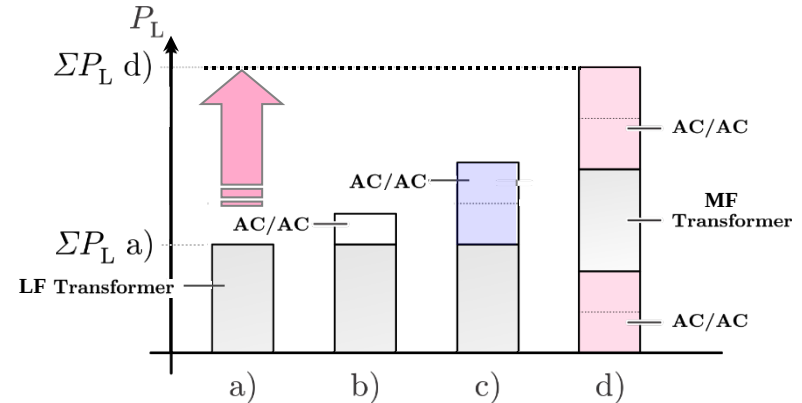MF Isolation
Active Input & Output Stage (d)



- Medium Freq. → Higher Transf. Efficiency Partly Compensates Converter Stage Losses
- Medium Freq. → Low Volume, High Control Dynamics

SST Concept Implementation

Challenge #1/5

*Availability / Selection of
Power Semiconductors*





► SiC Power Semiconductors

• Samples

- * 10kV & 15kV / 10A MOSFETs
- * 10kV & 15kV / 8A JBS Diodes
- * 15kV / 20A IGBTs

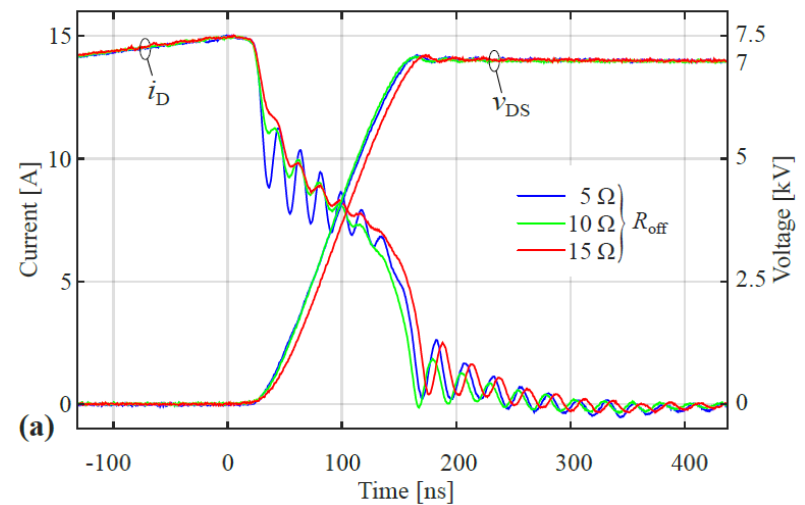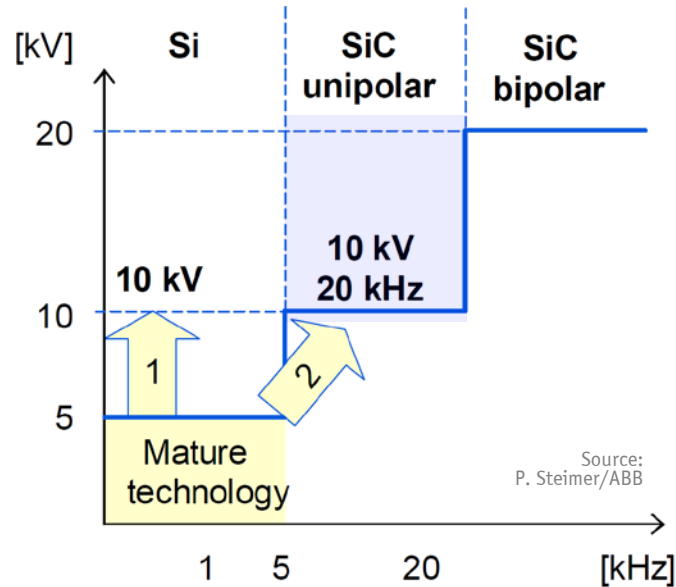
• Soft-Switching (ZVS) Performance 10kV MOSFET @ 15A (250uJ)



■ Interfacing to Medium Voltage → Two-Level OR Multi-Level Converter Topologies


► SiC Power Semiconductors

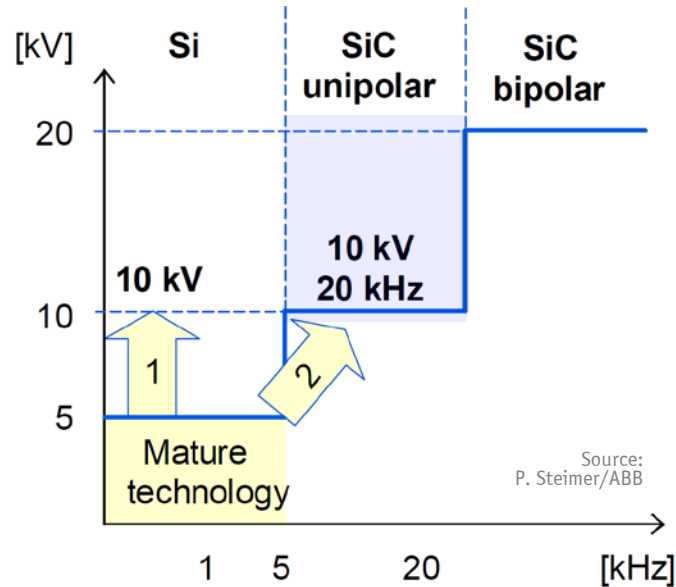- Samples *Wolfspeed*
- * 10kV & 15kV / 10A MOSFETs
- * 10kV & 15kV / 8A JBS Diodes
- * 15kV / 20A IGBTs



- Derating Requirement due to Cosmic Radiation for 100 FIT @ 25°C & 0 m AMSL
 $A_{\text{act}} = 7.2 \text{ cm}^2$



Source: P. Sandvik
R. Datta

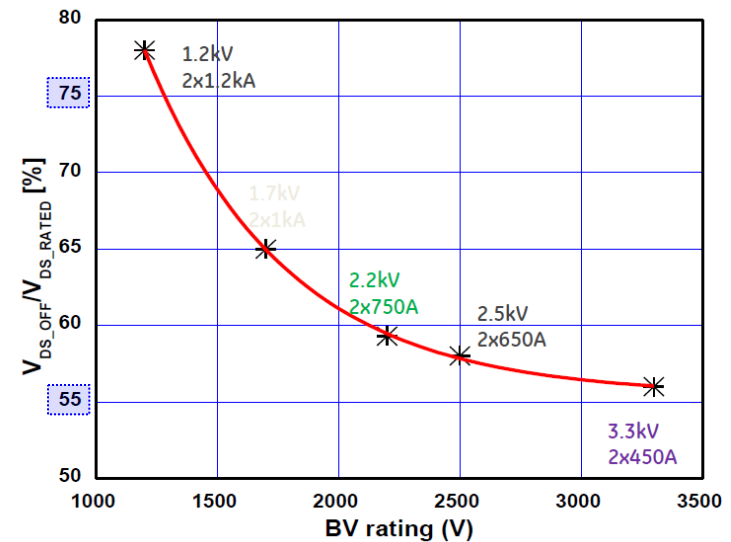

- Interfacing to Medium Voltage → Two-Level OR Multi-Level Converter Topologies

► Commercially Available SiC Power Semiconductors

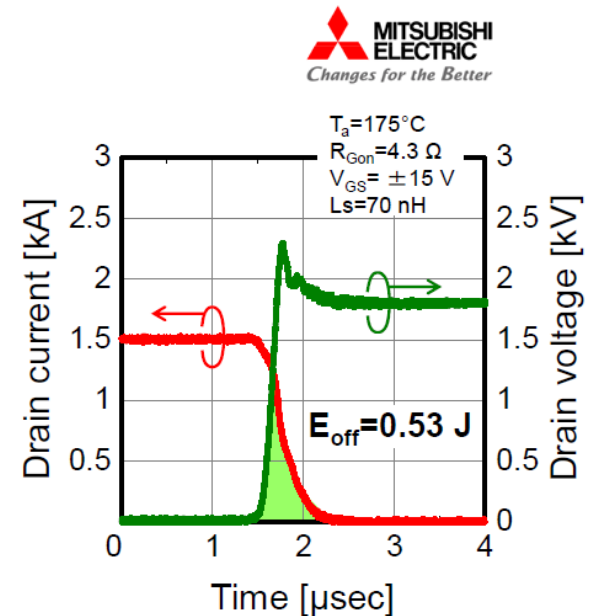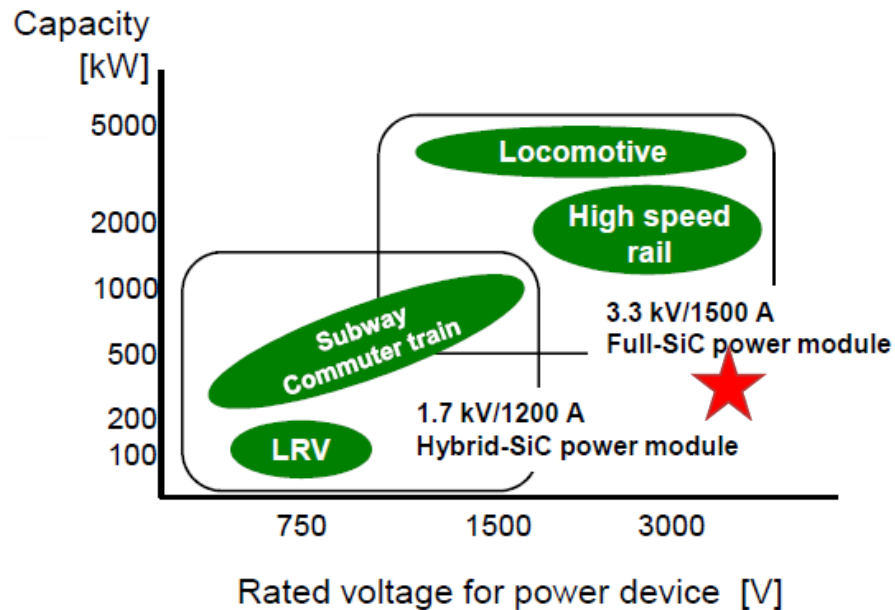- High Current 3.3kV / 1.7kV / 1.2 kV Power Modules
- Mitsubishi (CREE, ROHM, GE, etc.)




Challenge #2/5

*Creation of MV $\rightarrow$ LV
SST Topologies*




► Interfacing to Medium Voltage

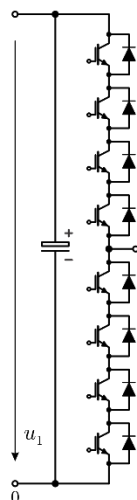- Partitioning of Blocking Voltage
- Series Connection or Multi-Cell and Multi-Level Approaches
- High Number N Cells $\rightarrow$ Quadratically Reduces Curr. Harmonics



* Two-Level Topology

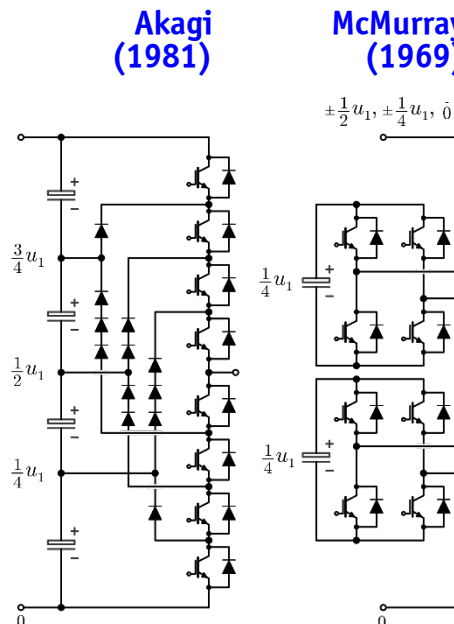


Akagi
(1981)

Marquardt



McMurray
(1969)

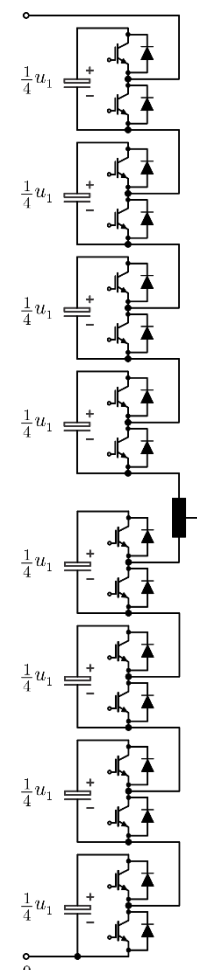



Alesina/
Venturini
(1981)




* Multi-Level/
Multi-Cell
Topologies

► Scaling of Series Interleaving of Converter Cells

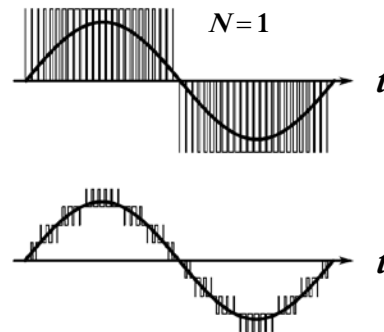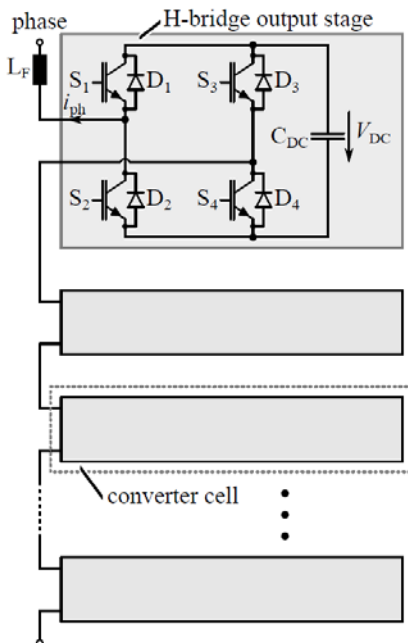■ Interleaved Series Connection Dramatically Reduces Switching Losses (or Harmonics)



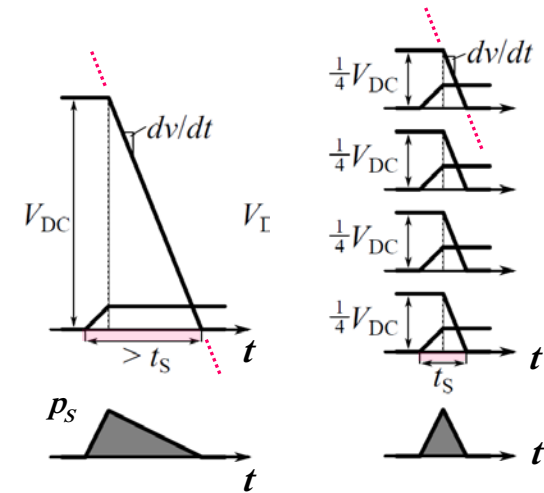– Scaling of Switching Losses for Equal $\Delta i/I$ and dv/dt






$$P_{S,N} \approx P_{S,N=1} \cdot \left(\frac{1}{2N^2} \cdots \frac{1}{N^3} \right)$$

- Converter Cells Could Operate at VERY Low Switching Frequency
- Minimization of Passives (Filter Components)

► Half-Cycle DCM Series Resonant Converter (HC-DCM-SRC)

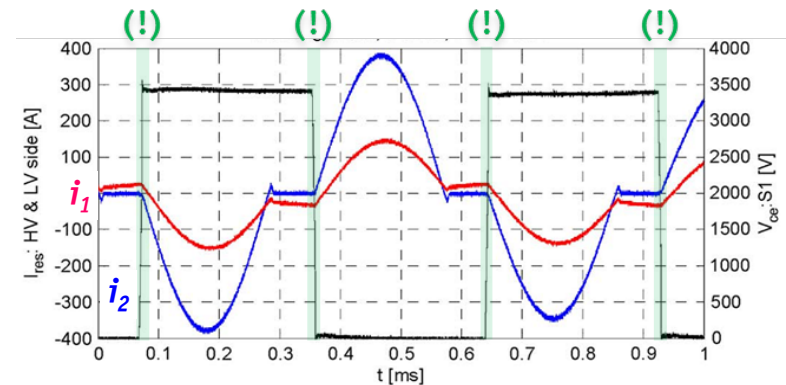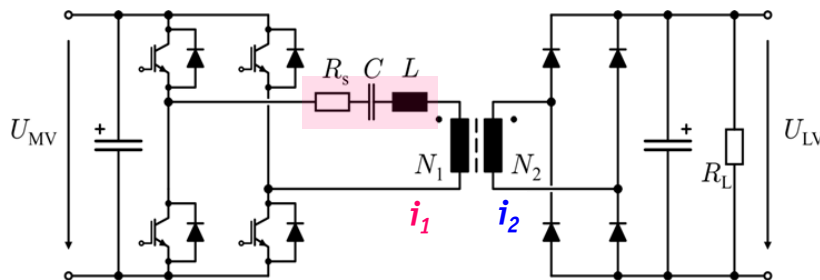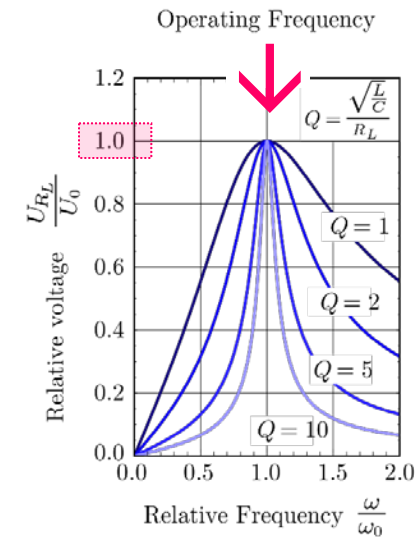- $f_s \approx$ Resonant Frequency $\rightarrow$ "Unity Gain"
- Fixed Voltage Transfer Ratio Independent of Transferred Power (!)
- Power Flow / Power Direction Self-Adjusting
- No Controllability / No Need for Control
- ZCS of All Devices



Combining the Basic Concepts I




Single-Phase AC-DC Conversion / Traction Applications



► Cascaded H-Bridges w. Isolated Back End


- Multi-Cell Concept (AC/DC Front End & Soft-Switching Resonant DC//DC Converter)
- Input Series / Output Parallel Connection – Self Symmetrizing (!)
- Highly Modular / Scalable
- Allows for Redundancy
- High Power Demonstrators: **ABB** **BOMBARDIER** **ALSTOM** etc.

Source: Zhao / Dujic (ABB / 2011)

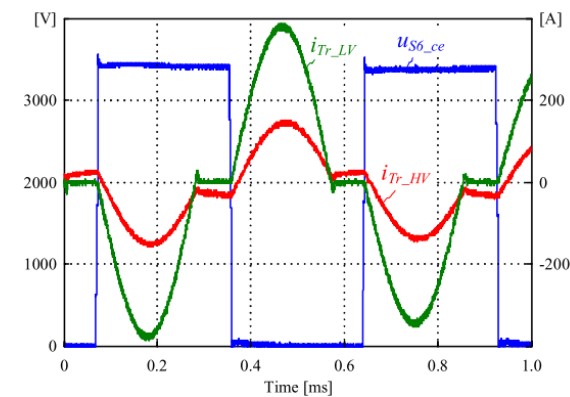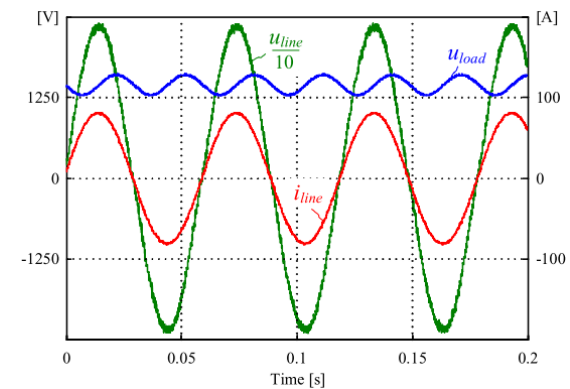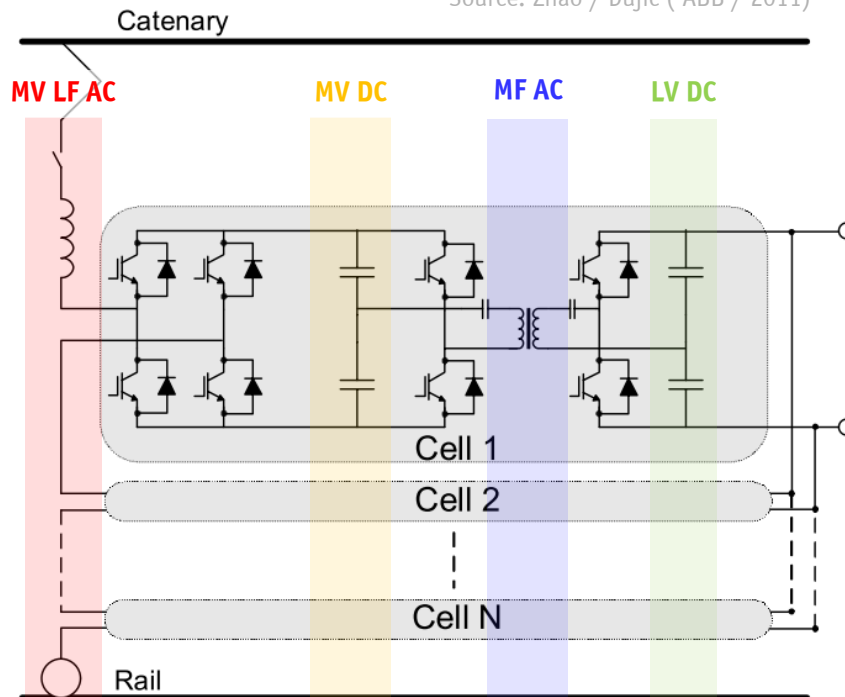


► Reversal of the Sequence of Current Shaping & Isolation

■ Isolated DC/DC Back End

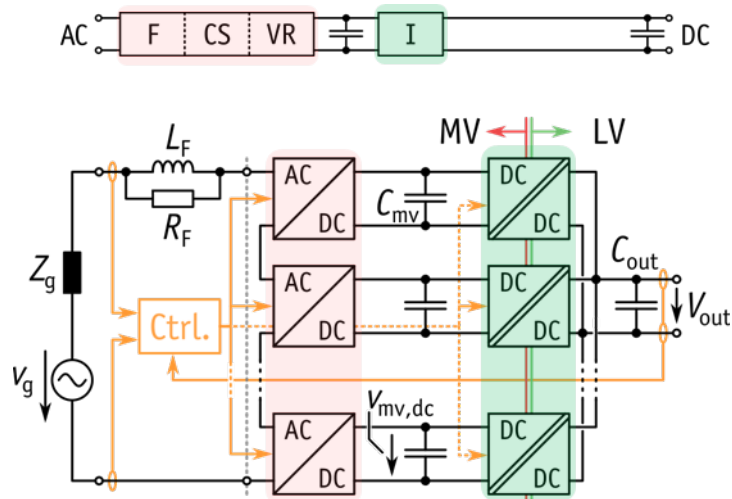

- Typical Multi-Cell SST Topology
- Two-Stage Multi-Cell Concept
- Direct Input Current Control
- Indirect Output Voltage Control
- High Complexity at MV Side


■ Isolated AC/AC Front End

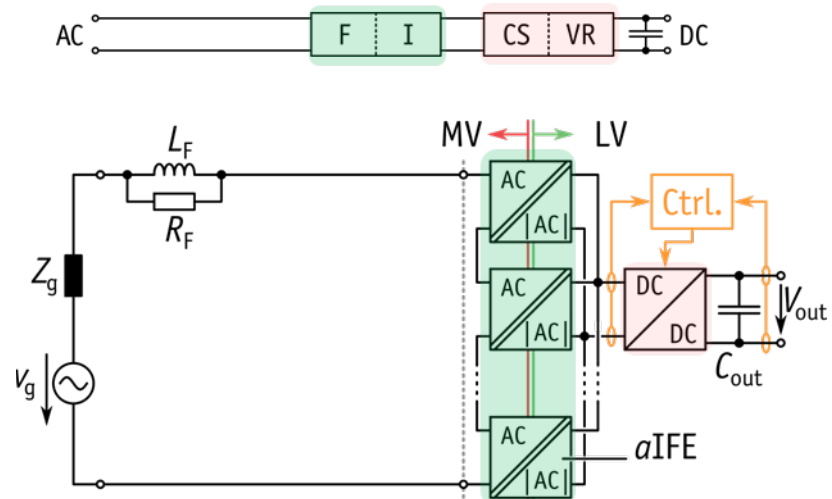

- Swiss SST (S3T)
- Two-Stage Multi-Cell Concept
- Indirect Input Current Control
- Direct Output Voltage Control
- Low Complexity on MV Side

Combining the Basic Concepts II

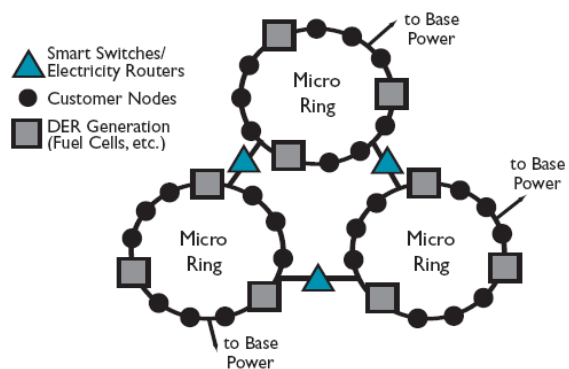
Three-Phase AC-AC Conversion / Smart Grid Applications



Source: **EPRI** | ELECTRIC POWER
RESEARCH INSTITUTE

► MEGALink @ ETH Zurich
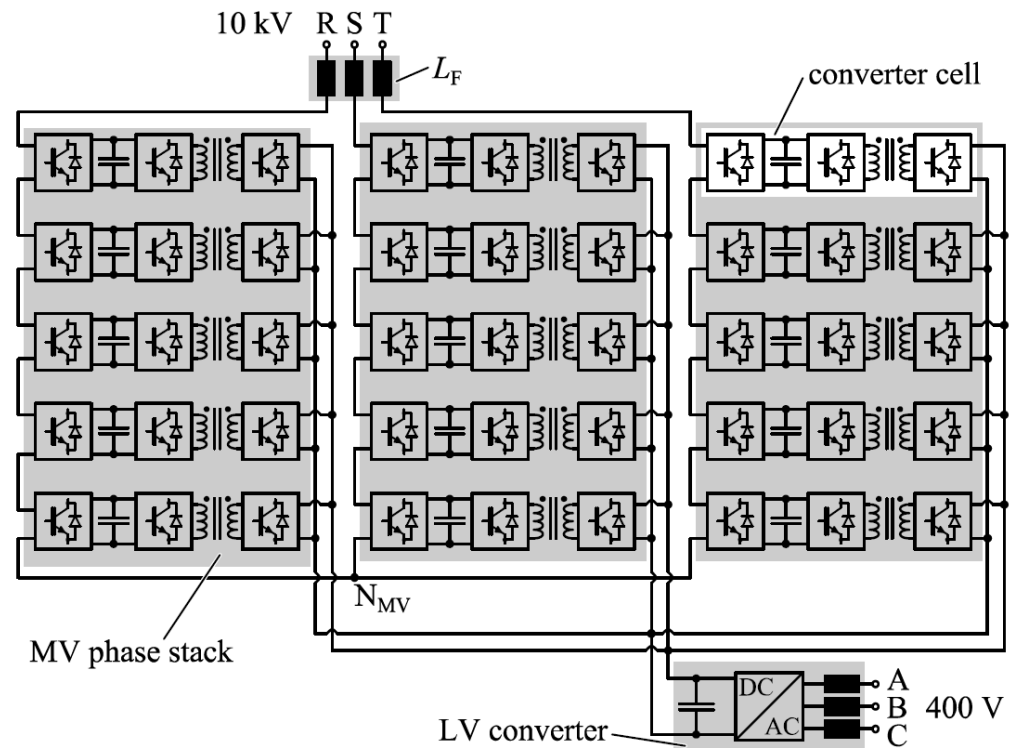
$$\begin{aligned} S_N &= 630 \text{ kVA} \\ U_{LV} &= 400 \text{ V} \\ U_{MV} &= 10 \text{ kV} \end{aligned}$$





- 2-Level Inverter on LV Side
- HC-DCM-SRC DC//DC Conversion
- Cascaded H-Bridge MV Structure – ISOP Topology

► 166kW / 20kHz HC-DCM-SRC DC-DC Converter Cell


- Half-Cycle DCM Series Resonant DC-DC Converter

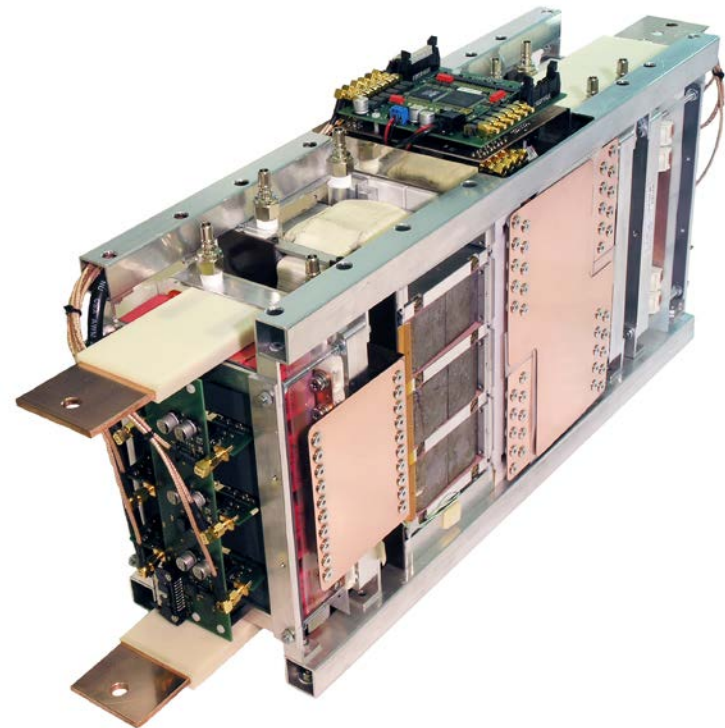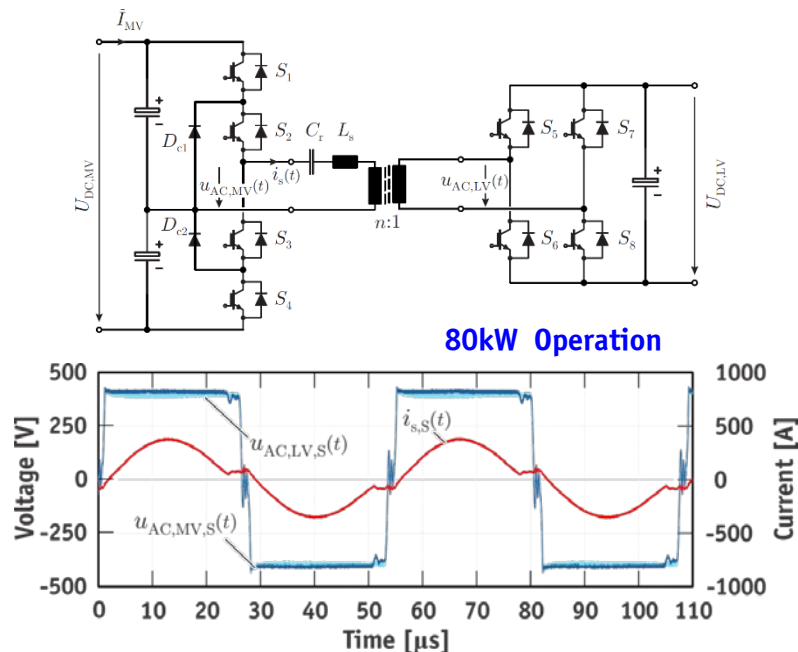- Medium-Voltage Side **2kV**
- Low-Voltage Side **400V**



► Single-Cell Structure

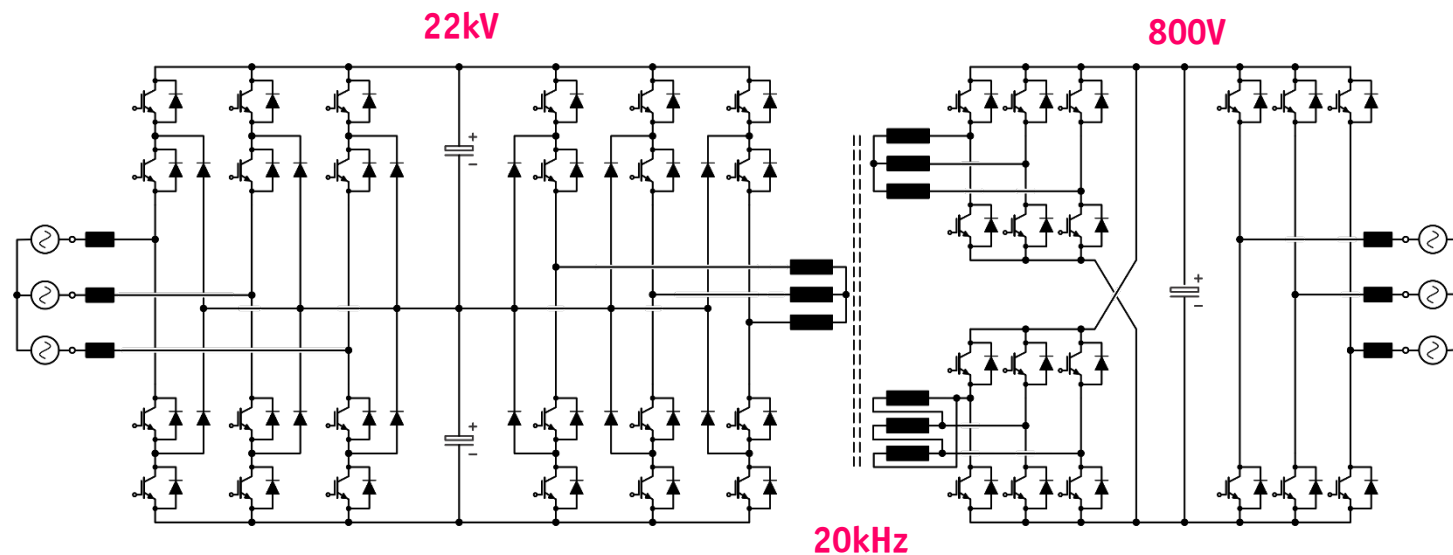- 13.8kV → 480V
- Scaled Prototype
- 15kV SiC-IGBTs, 1200V SiC MOSFETs



- Redundancy Only for Series-Connection of Power Semiconductors (!)

Challenge #3/5


Medium-Frequency Transformer Design

- *Heat Management*
- *Isolation*



► MF Transformer Design – Cold Plates/ Water Cooling

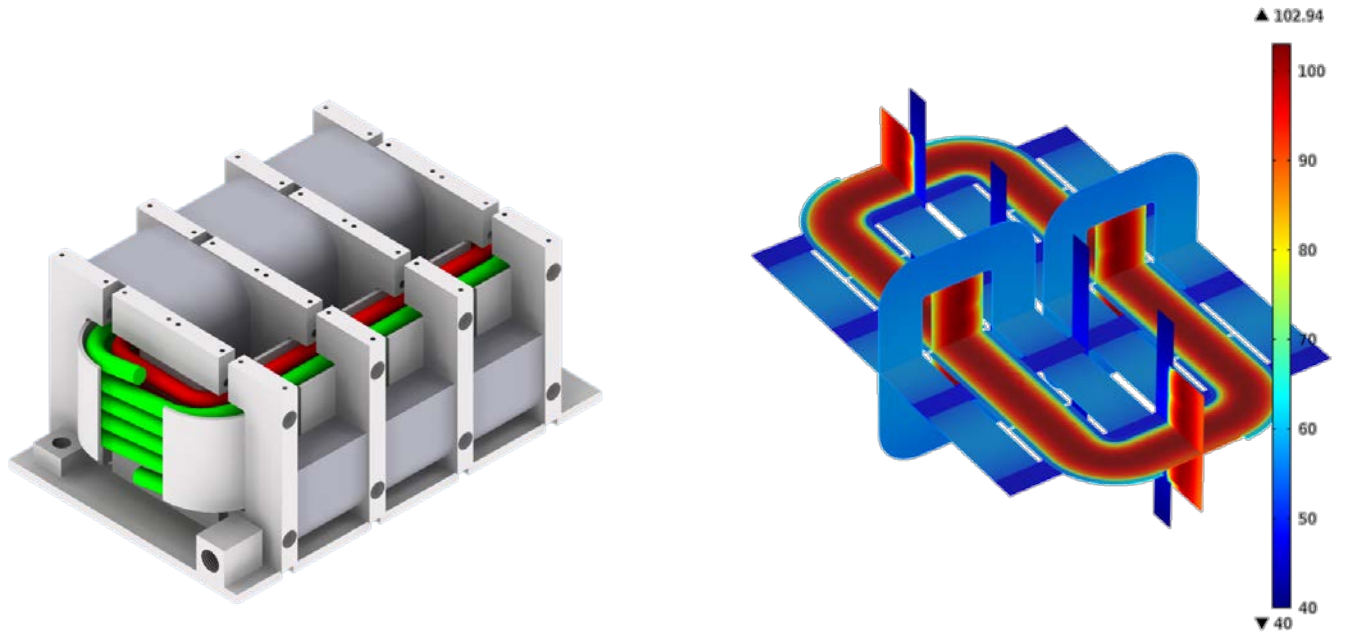- Nano-Crystalline 160kW/20kHz Transformer (ETH, Ortiz 2013)






- Combination of Heat Conducting Plates and Top/Bottom Water-Cooled Cold Plates
- FEM Simulation Comprising Anisotropic Effects of Litz Wire and Tape-Wound Core

► Water-Cooled 20kHz Transformer

- **Power Rating** 166 kW
- **Efficiency** 99.5%
- **Power Density** 32 kW/dm³

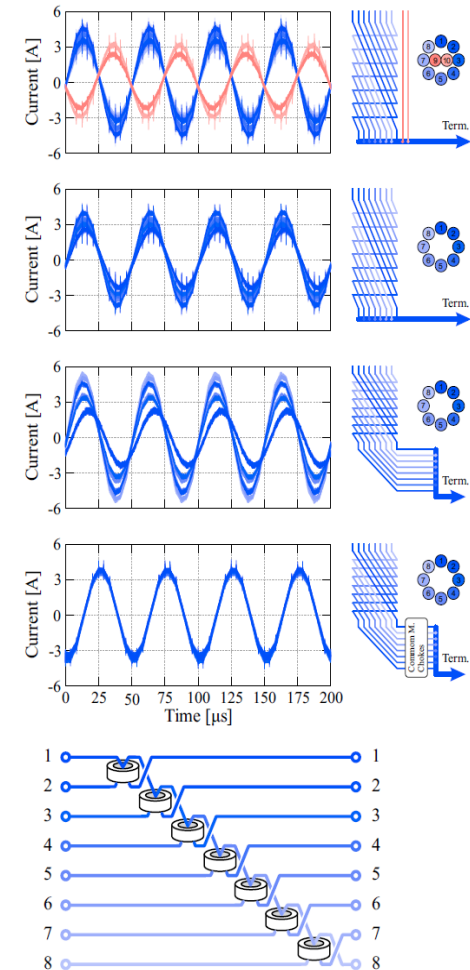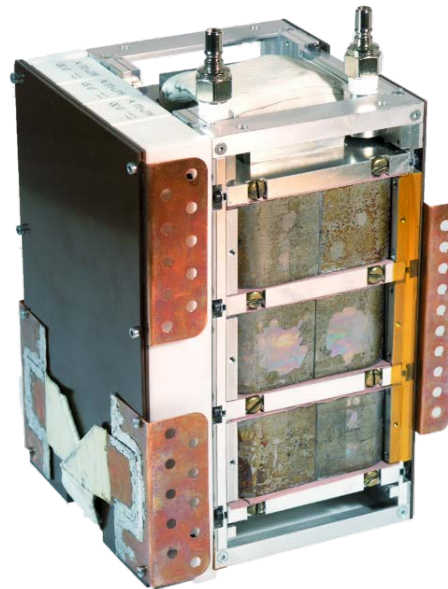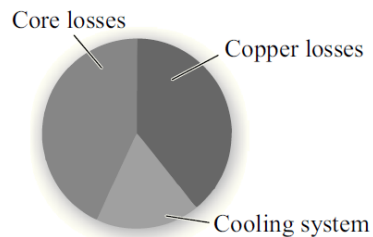- Nanocrystalline Cores with 0.1mm Airgaps between Parallel Cores for Equal Flux Partitioning
- Litz Wire (10 Bundles) with CM Chokes for Equal Current Partitioning



Challenge #4/5



*Mains $\leftarrow$ SST $\rightarrow$ Load
Protection / Grid Codes*



► Potential Faults of MV/LV Distribution-Type SSTs

- Extreme Overvoltage Stresses on the MV Side for Conv. Distr. Grids
- SST more Appropriate for Local Industrial MV Grids

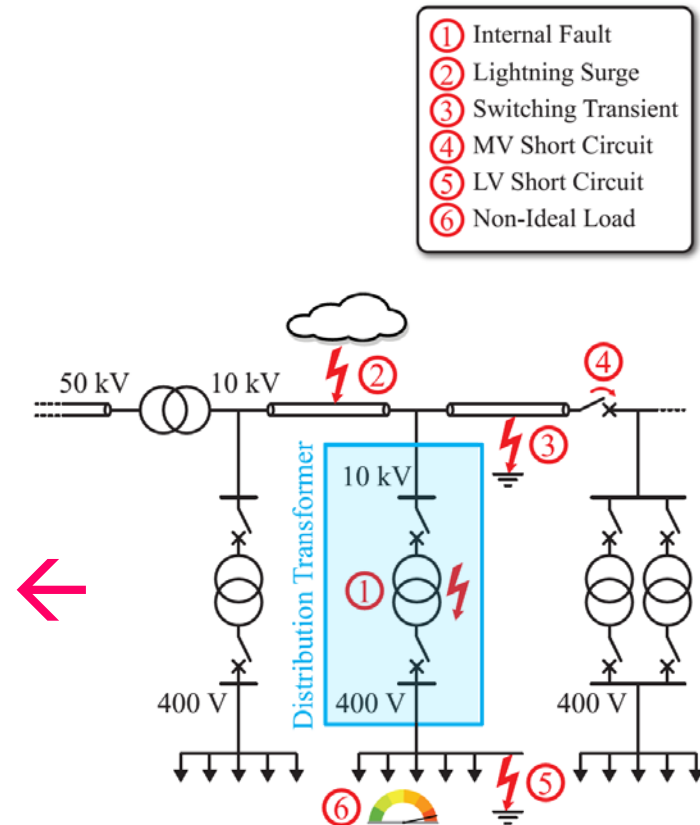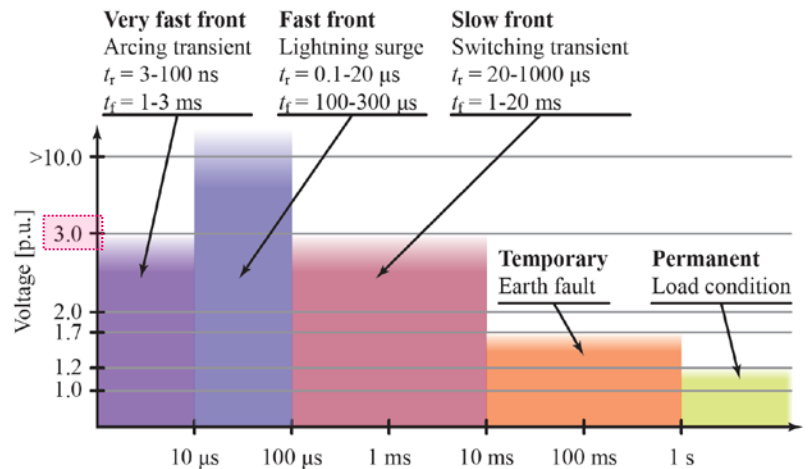
• Conv. MV Grid Time-Voltage Characteristic



► Protection of LF-XFRM vs. SST Protection


■ Missing Analysis of SST Faults (Line-to-Line, Line-to-Gnd, S.C., etc.) and Protection Schemes

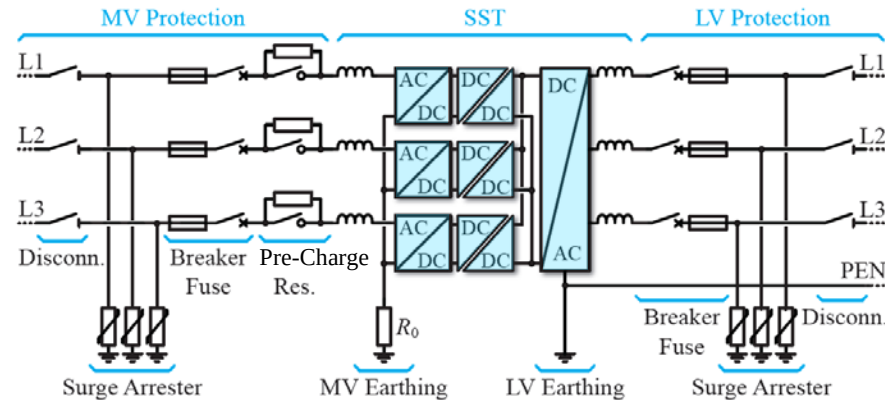• Proposed SST Protection Scheme with Minimum # of Protection Devices



• Overvoltage Protection (Lightning Strike)

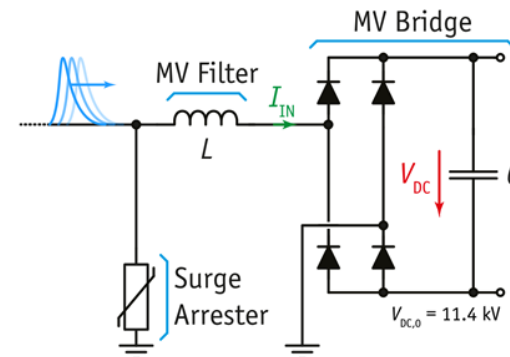
- * High Arrester Clamping Voltage
- * Filter Inductor $> 8\%$ for Current Limiting
- * Min. DC Link Capacitance
- * Sufficient Blocking Capability
- * Grounding – Lower Stress if Unearthed



■ Protection Scheme Needs to Consider: Selectivity / Sensitivity / Speed / Safety / Reliability

► Distribution Transformer Overcurrent Requirements

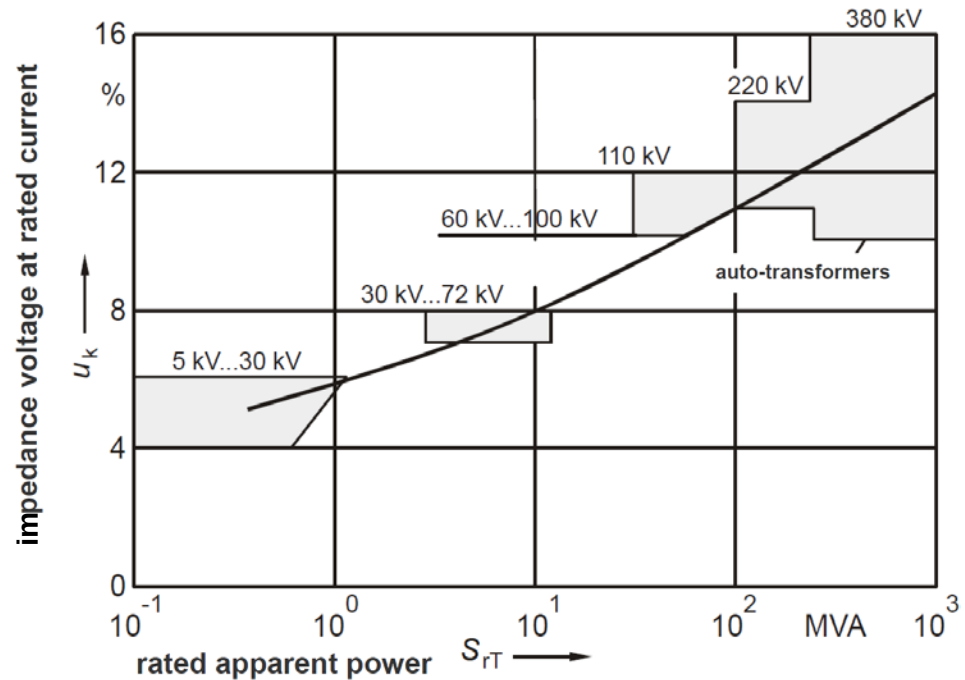- Low-Frequ. XFRM must Provide Short-Circuit Currents of up to **40 Times Nominal Current for 1.5 Seconds** (EWZ, 2009)
- Traction Transformers: **150% Nominal Power for 30 Seconds** (Engel 2003)



- Lower Grid Voltage Levels → Higher Relative Short Circuit Currents
- SST is NOT (!) a 1:1 Replacement for a Conventional Low-Frequency XFRM



Challenge #5/5

*Ensuring Reliability of Highly Complex
Multi-Cell Converter Topologies*



► Reliability Model (1) – Failure Rate

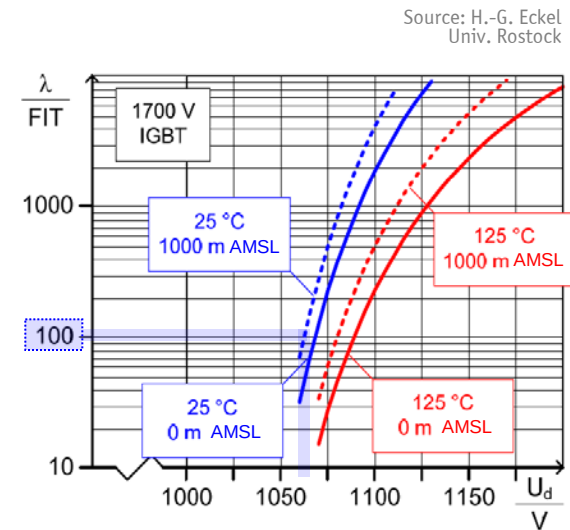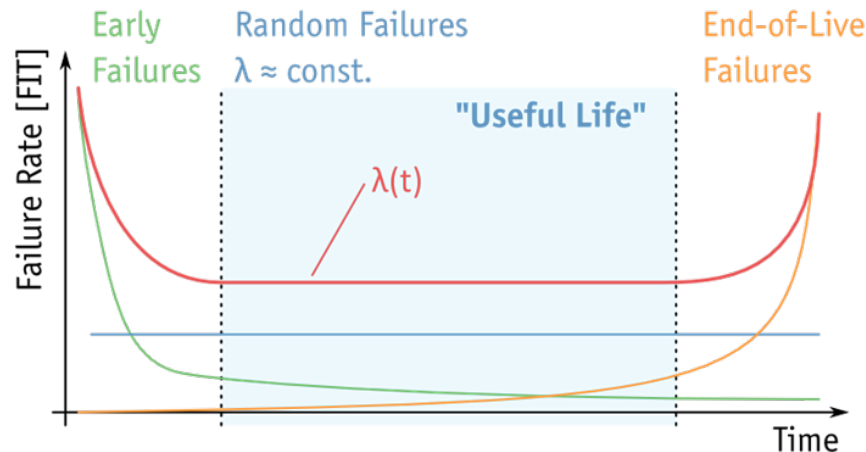- Failure Rate $\lambda(t)$ is a Function of Time – „Bathtub Curve“
- Useful Life Dominated by Random Failures $\rightarrow \lambda(t) = \text{const.}$
- $[\lambda] = 1 \text{ FIT}$ (1 Failure in 10^9 h)
- Typ. Value for IGBTs: 100 FIT




- Sources for Empirical Component Failure Rate Data : MIL-HDBK-217F, IEC Standard 62380, etc.

► Reliability Model (2) – Reliability Function

- **Reliability Function:** Probability of System being Operational after t :

$$R(t) = e^{-\int_0^t \lambda(x) dx} = e^{-\lambda t}$$

$\lambda(t) = \text{const.}$

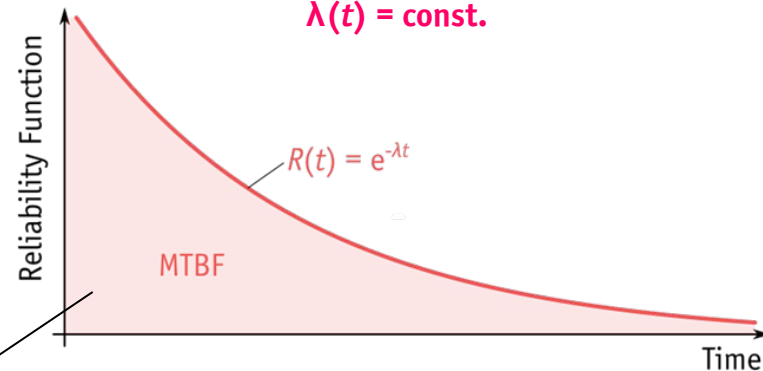


- **Mean Time Between Failures**


$$\text{MTBF} = \int_0^{\infty} R(t) dt = \int_0^{\infty} e^{-\lambda t} dt = \frac{1}{\lambda}$$

- **Series Structure**

$$\lambda_s = \sum_{i=1}^n \lambda_i$$

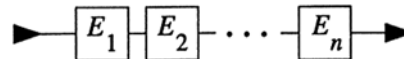


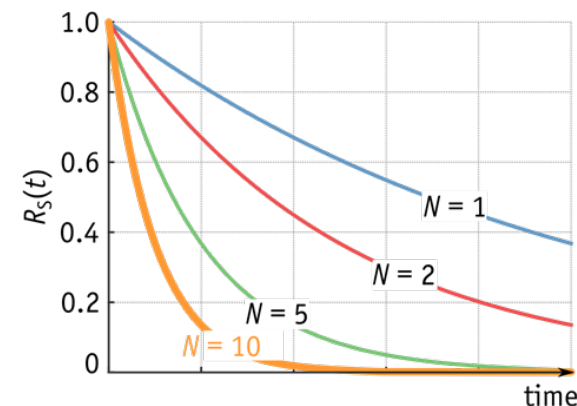
**Independent Cells
with Equal Failure Rate**





► Redundancy in Multi-Cell Converter Systems

■ k -out-of- n Redundancy Redundancy of Cells in Phase Stack

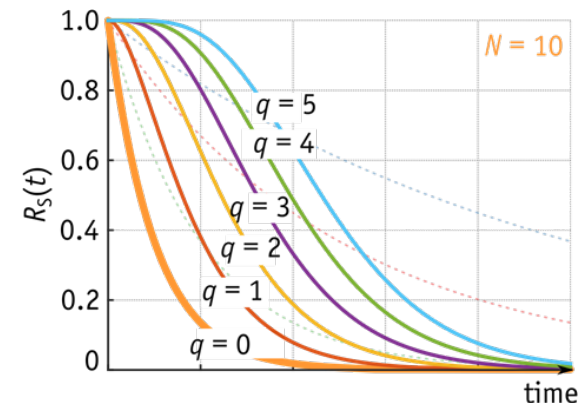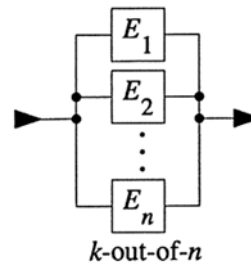System is Operational as Long as at Least k -out-of- n Subsystems are Working



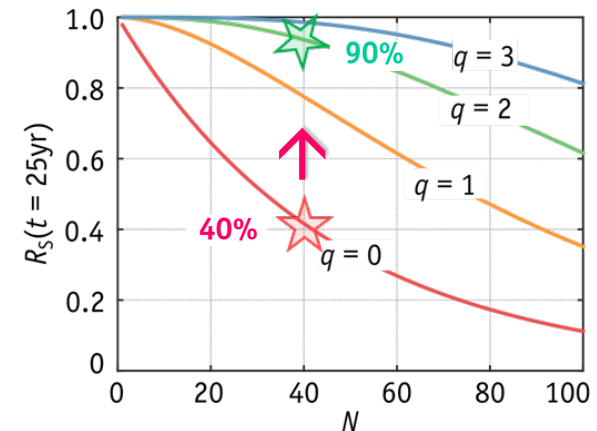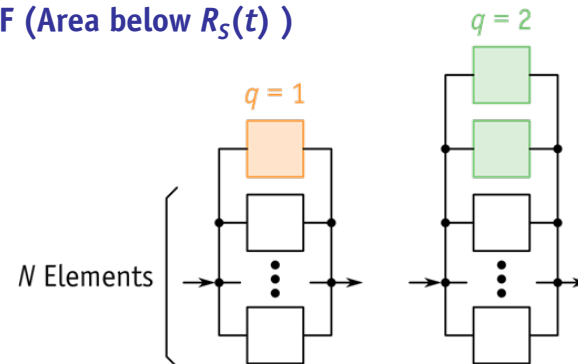■ Effect of q Redundant Cells on $R_S(t)$ and/or MTBF (Area below $R_S(t)$)




- Redundancy Significantly Improves System Level Reliability (!)

SST Demonstrator Systems

Future Locomotives
Smart Grid Applications

► 1ph. AC/DC Power Electronic Transformer - PET

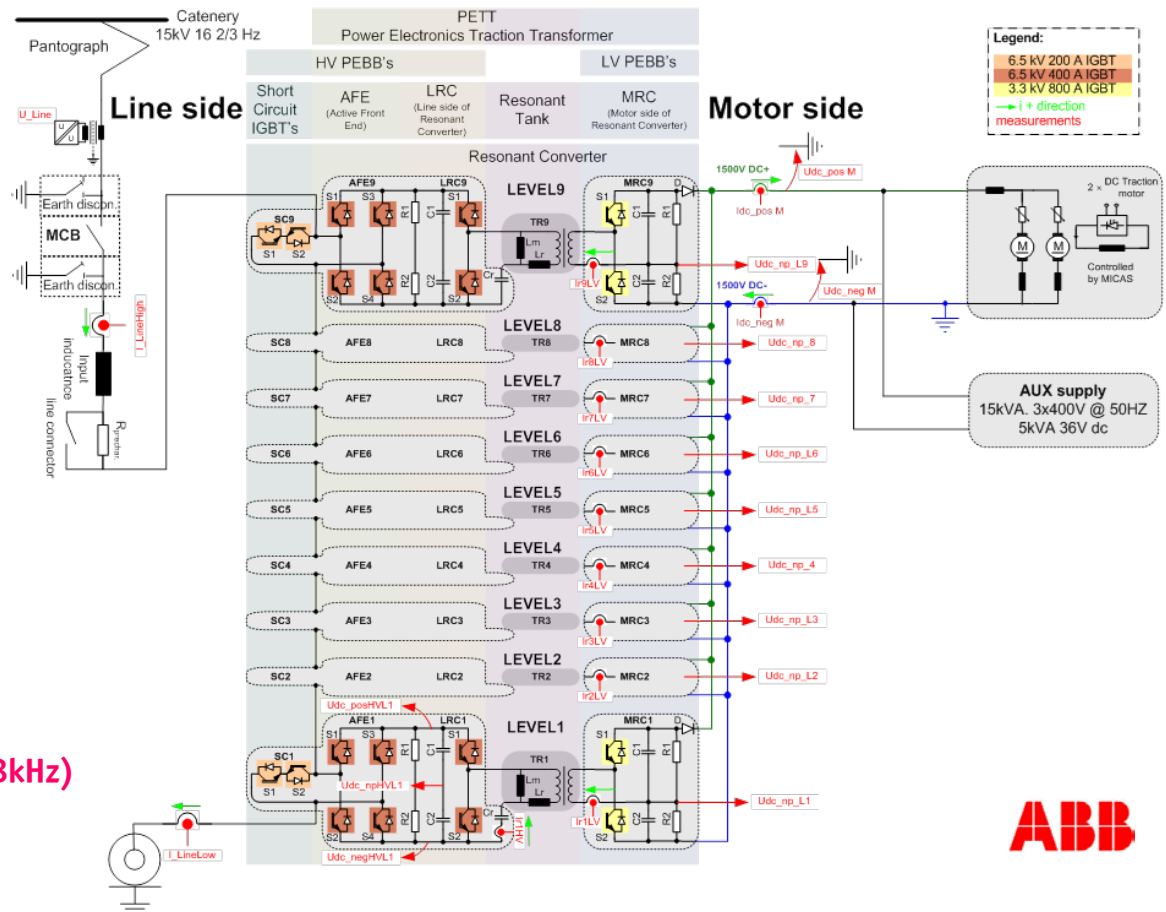- Dujic et al. (2011)
- Heinemann (2002)
- Steiner/Stemmler (1997)
- Schibli/Rufer (1996)





P = 1.2MVA, 1.8MVA pk
9 Cells (Modular)

54 x {6.5kV, 400A IGBTs}
18 x {6.5kV, 200A IGBTs}
18 x {3.3kV, 800A IGBTs}

9 x MF Transf. (150kVA, 1.8kHz)
1 x Input Choke

► 1.2 MVA 1ph. AC/DC Power Electronic Transformer

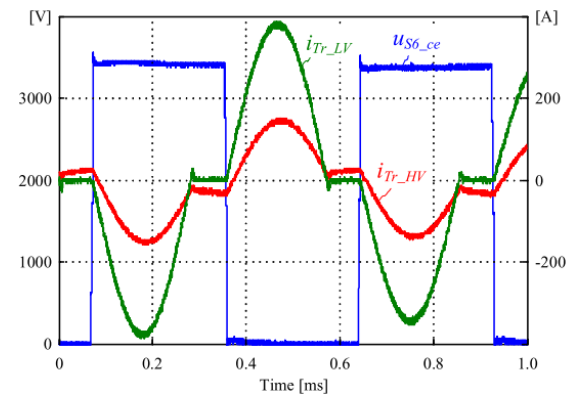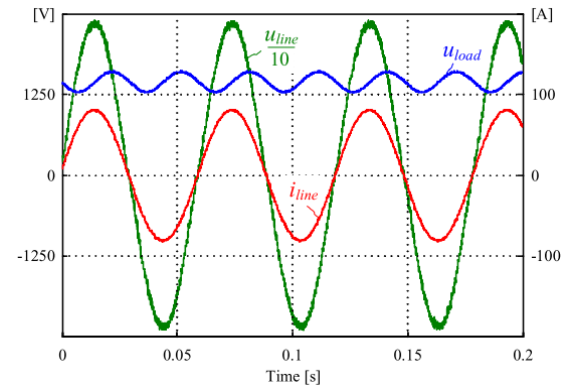- Cascaded H-Bridges – 9 Cells
- Resonant LLC DC/DC Converter Stages




► 1.2 MVA 1ph. AC/DC Power Electronic Transformer

- Cascaded H-Bridges – 9 Cells
- Resonant LLC DC/DC Converter Stages





Efficiency

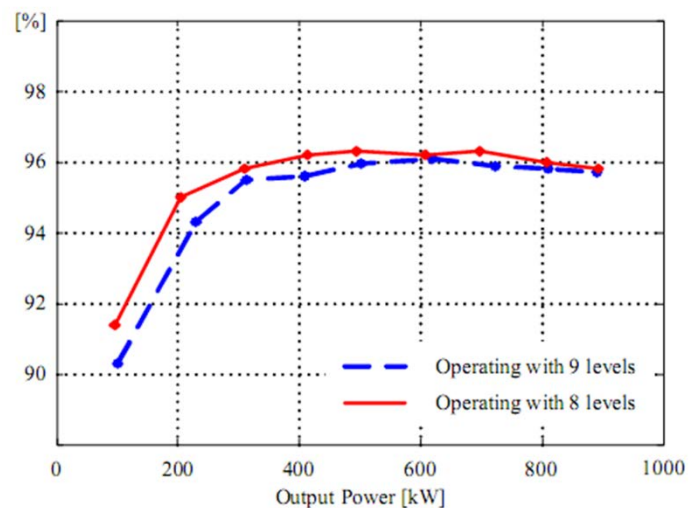

► SiC-Enabled Solid-State Power Substation



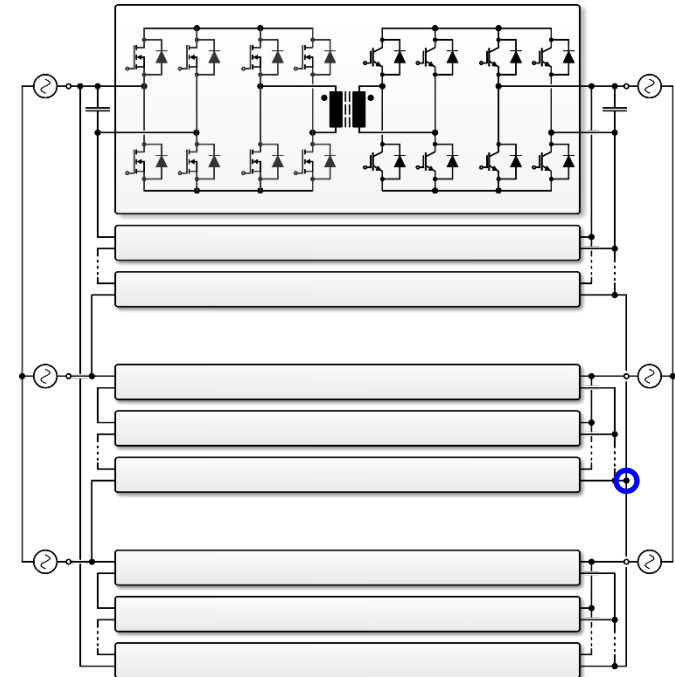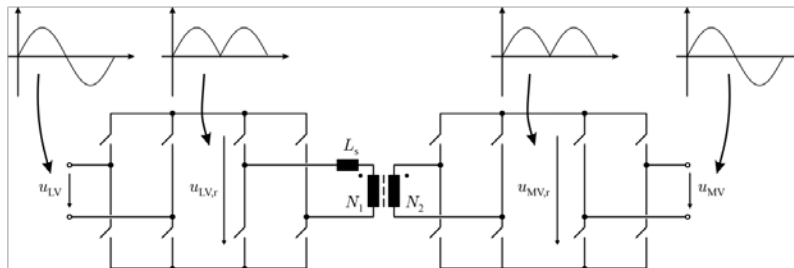- Das et al. (2011)
- Lipo (2010)
- Weiss (1985 for Traction Appl.)
- Fully Phase Modular System
- Indirect Matrix Converter Modules ($f_1 = f_2$)
- MV Δ -Connection (13.8kV_{l-l}, 4 Modules in Series)
- LV Y-Connection (265V, Modules in Parallel)




- SiC Enabled 20kHz/1MVA "Solid State Power Substation"
- 97% Efficiency @ Full Load / 1/3rd Weight / 50% Volume Reduction (Comp. to 60Hz)

► SiC-Enabled Solid-State Power Substation

- Das et al. (2011)

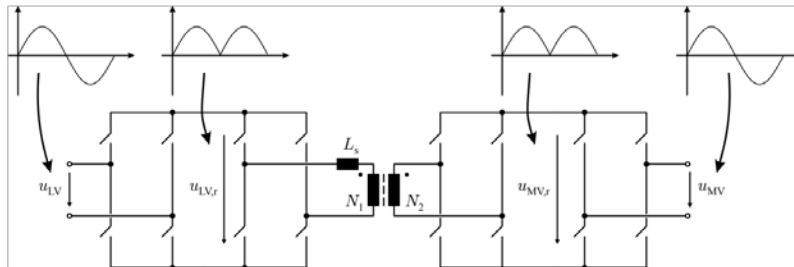- Fully Phase Modular System
- Indirect Matrix Converter Modules ($f_1 = f_2$)
- MV Δ -Connection (13.8kV_{l-l}, 4 Modules in Series)
- LV Y-Connection (265V, Modules in Parallel)





- SiC Enabled 20kHz/1MVA "Solid State Power Substation"
- 97% Efficiency @ Full Load / 1/3rd Weight / 50% Volume Reduction (Comp. to 60Hz)

► SST vs. LF Transformer + AC/AC or AC/DC Converter

- Specifications
 - 1MVA
 - 10kV Input
 - 400V Output
 - 1700V IGBTs (1kHz/8kHz/4kHz)

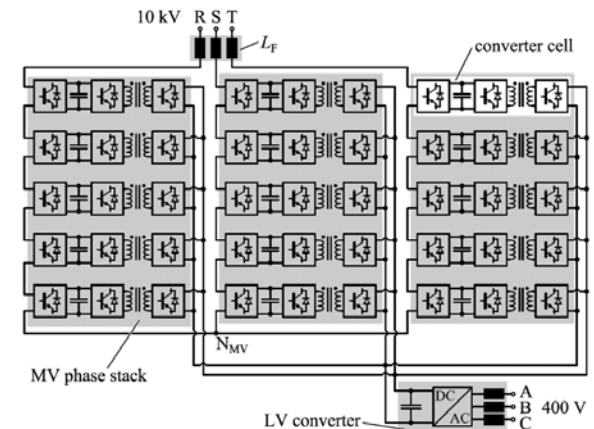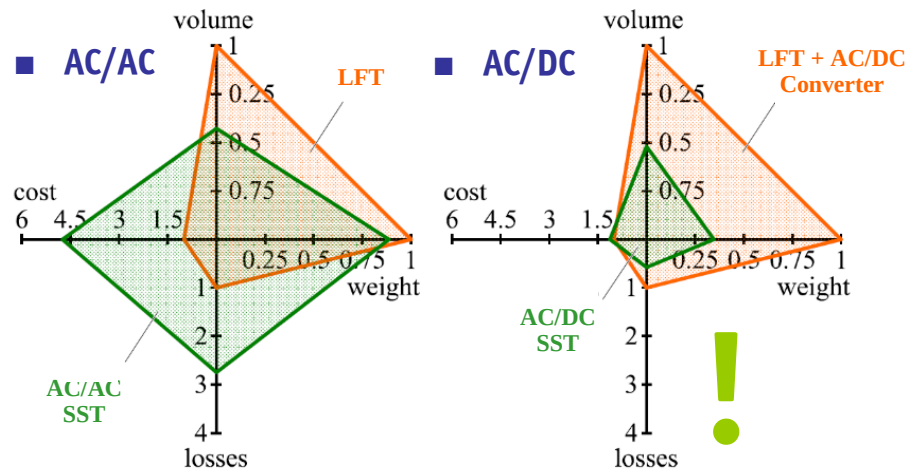- LF Transformer
 - 98.7 %
 - 16.2 kUSD
 - 2600kg (5700lb)



- Clear Efficiency/Volume/Weight Advantage of SST for DC Output (98.2%)
- Weakness of AC/AC SST vs. Simple LF Transformer (98.7%) - 5 x Costs, 2.5 x Losses

Potential Future SST Application Areas


Datacenters
Off-Shore Wind
Oil and Gas Industry
Power-to-Gas
All Electric Aircraft

► AC vs. Facility-Level DC Systems for Datacenters


- **Reduces Losses & Footprint**
- **Improves Reliability & Power Quality**

— Conventional US 480V_{AC} Distribution

Source: 2007

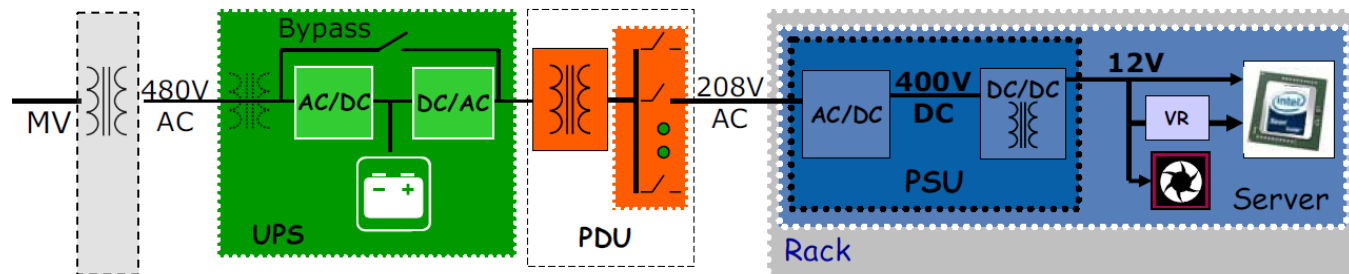


— Facility-Level 400 V_{DC} Distribution

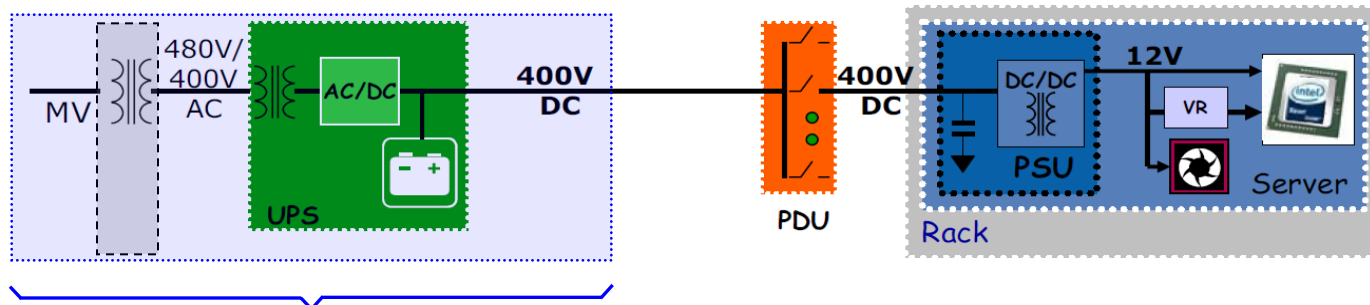

- **Future Concept: Unidirectional SST / Direct 6.6kV AC → 400V DC Conversion**


► DC Collection Grids for Offshore Wind Parks

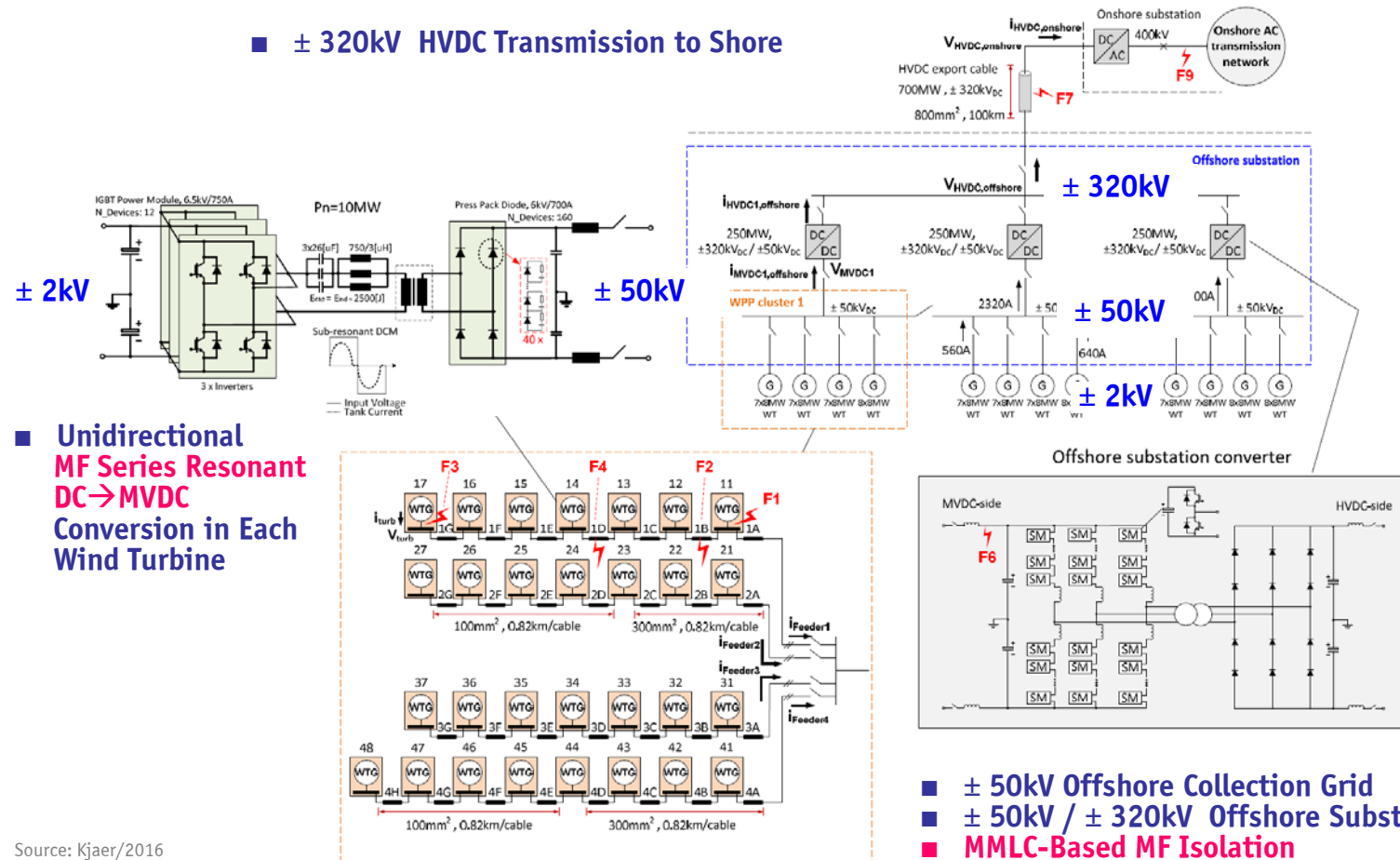■ $\pm 320\text{kV}$ HVDC Transmission to Shore



Source: Kjaer/2016

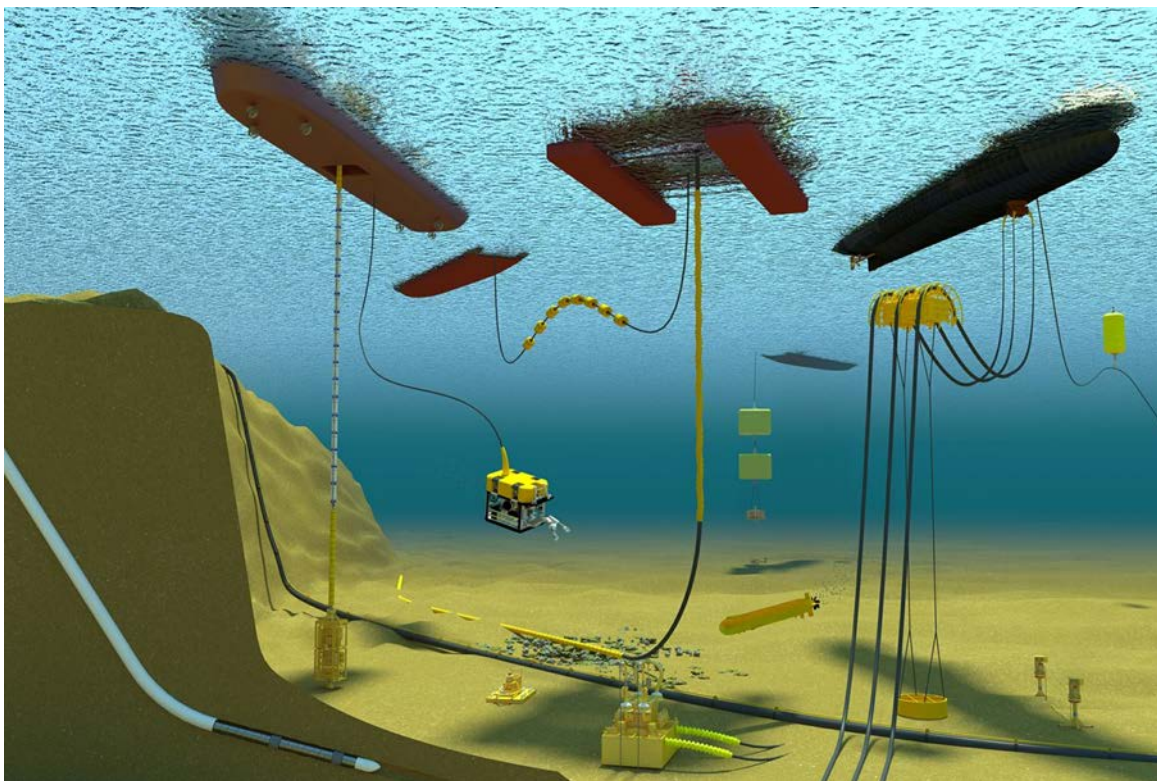► Subsea Applications – Oil & Gas Processing





- **ABB's Future Subsea Power Grid** → "Develop All Elements for a Subsea Factory"

► Future Subsea Distribution Network


- Transmission Over DC, No Platforms/Floaters
- Longer Distances Possible
- Subsea O&G Processing
- Weight Optimized Power Electronics

Source: Devold (ABB 2012)

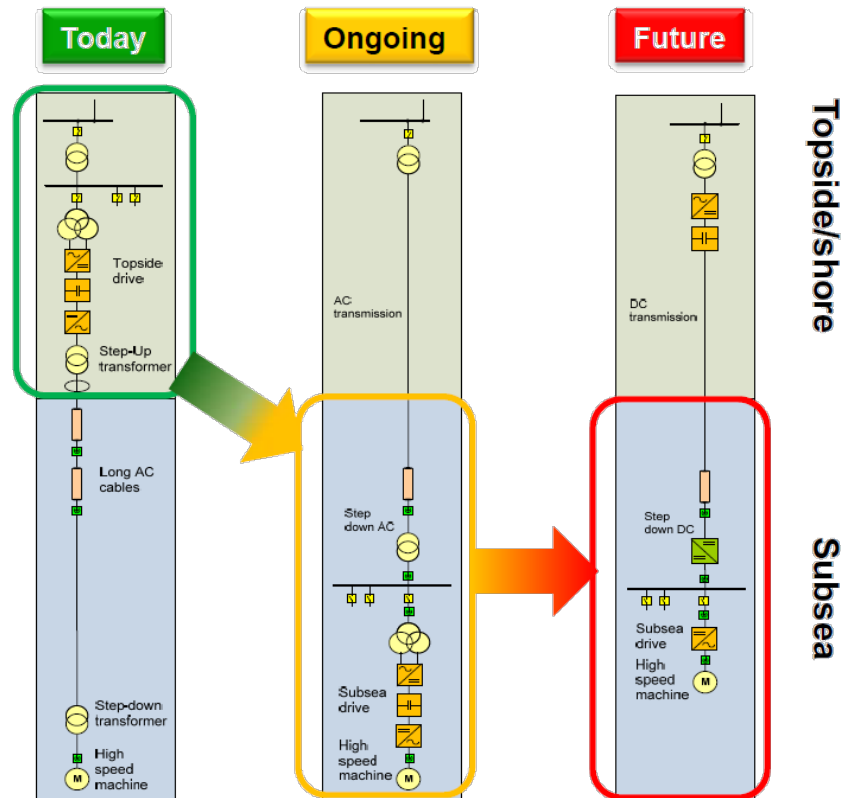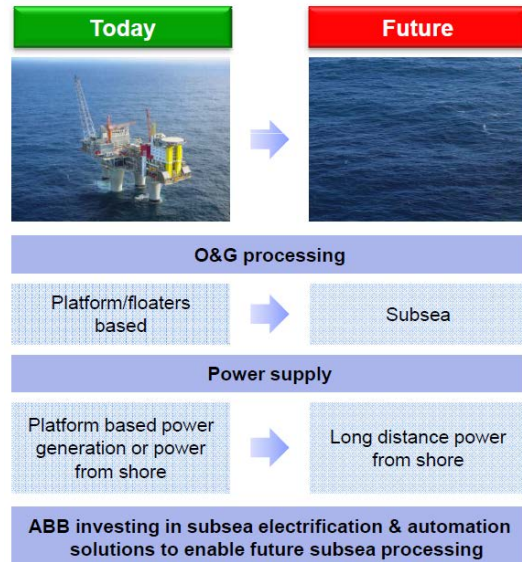

► Power-to-Gas

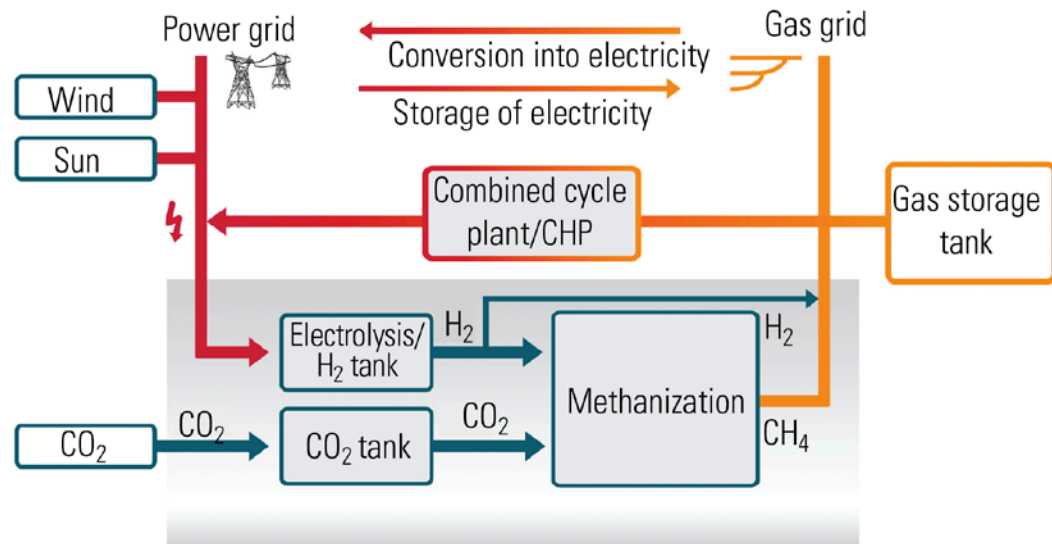- **Electrolysis for Conversion of Excess Wind/Solar Electric Energy** into
 - Hydrogen
 - Fuel-Cell Powered Cars
 - Heating
- **High-Power @ Low DC Voltage (e.g. 220V)**
- **Very Well Suited for MV-Connected SST-Based Power Supply**



– Hydrogenics 100 kW H₂-Generator ($\eta=57\%$)

Source: www.r-e-a.net


► Future Hybrid Distributed Propulsion Aircraft



Source:
EADS

- Powered by Thermal Efficiency Optimized Gas Turbine and/or Future Batteries (1000 Wh/kg)
- Highly Efficient Superconducting Motors Driving Distributed Fans (E-Thrust)
- Until 2050: Cut CO₂ Emissions by 75%, NO_x by 90%, Noise Level by 65%

► Future Distributed Propulsion Aircraft

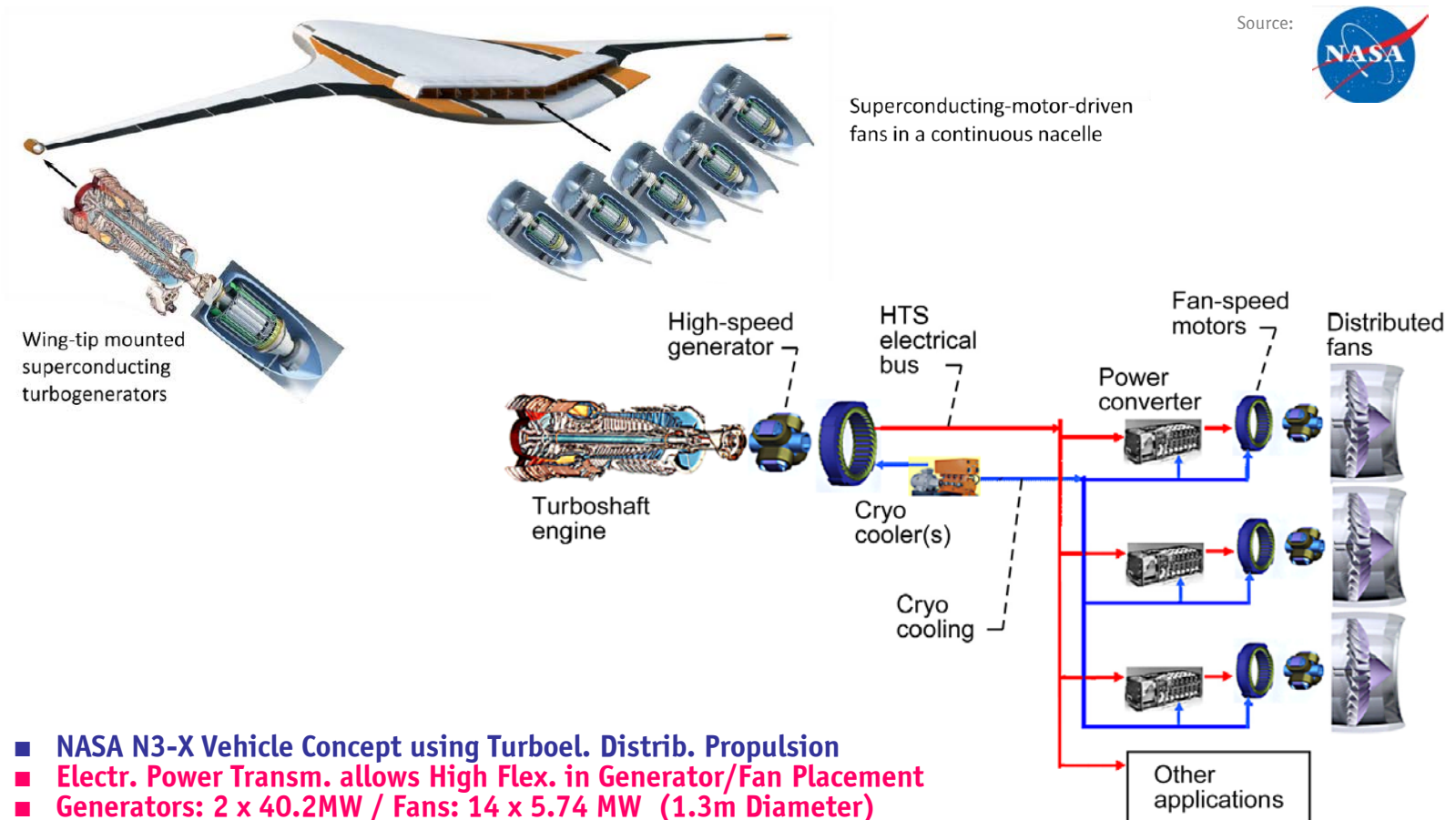

Conclusions

*SST Limitations / Concepts
Research Areas*

► SST Ends the “War of Currents”

THE CURRENT WAR
THE TALE OF AN EARLY TECH RIVALRY

DC

DIRECT CURRENT

The flow of electricity is in one direction only. The system operates at the same voltage level throughout and is not as efficient for high-voltage long distance transmission.

Direct current runs through:

- Battery-Powered Devices
- Fuel and Solar Cells
- Light Emitting Diodes

"(TESLA'S) IDEAS ARE SPLENDID, BUT THEY ARE UTTERLY IMPRACTICAL."

- THOMAS EDISON

THOMAS EDISON VS. NIKOLA TESLA

You would have never found two geniuses so spiteful of each other beyond turn-of-the-century inventors Nikola Tesla and Thomas Edison. They worked together—and hated each other. Let's compare their life, achievements, and embittered battles.

AC

ALTERNATING CURRENT

Electric charge periodically reverses direction and is transmitted to customers by a transformer that could handle much higher voltages.

Alternating current runs through:

- Car Motors
- Radio Signals
- Appliances

"IF EDISON HAD A NEEDLE TO FIND IN A HAYSTACK, HE WOULD PROCEED AT ONCE... UNTIL HE FOUND THE OBJECT OF HIS SEARCH. I WAS A SORRY WITNESS OF SUCH DOINGS, KNOWING THAT A LITTLE THEORY AND CALCULATION WOULD HAVE SAVED HIM 90 PERCENT OF HIS LABOR."

- NIKOLA TESLA

FALLING OUT

Edison promised Tesla a generous reward if he could smooth out his direct current system. The young engineer took on the assignment and ended up saving Edison more than \$100,000 (millions of dollars by today's standards). When Tesla asked for his rightful compensation, Edison declined to pay him. Tesla resigned shortly after, and the elder inventor spent the rest of his life campaigning to discredit his counterpart.

EDISON FRIES AN ELEPHANT

In order to prove the dangers of Tesla's alternating current, Thomas Edison staged a highly publicized electrocution of the three-ton elephant known as "Topsy." She died instantly after being shocked with a 6,600-volt AC charge.

LATE BLOOMER

Thomas Edison, the youngest in his family, didn't learn to talk until he was almost 4 years old.

WAR OF CURRENTS OFFICIALLY SETTLED

In 2007, Con Edison ended 125 years of direct current electricity service that began when Thomas Edison opened his power station in 1882. It changed to only provide alternating current.

NOBEL PRIZE CONTROVERSY

In 1915, both Edison and Tesla were to receive Nobel Prizes for their strides in physics, but ultimately, neither won. It is rumored to have been caused by their animosity towards each other and refusal to share the coveted award.

1847 BORN 1858

Edison: Milan, Ohio / Tesla: Smiljan, Croatia

NICKNAME Edison: Wizard of Menlo Park / Tesla: Wizard of the West

EDUCATION Edison: Home-schooled and self-taught / Tesla: Studied math, physics, and mechanics at The Polytechnic Institute at Graz

METHOD Edison: Mass communication and business / Tesla: Electromagnetism and electromechanical engineering

NOTABLE INVENTIONS Edison: Incandescent light bulb, phonograph, cement making technology, motion picture camera, DC motors and electric power / Tesla: Tesla coil, resonant transformer circuit, radio transmitter, fluorescent light, AC motors and electric power generation system

NUMBER OF US PATENTS Edison: 1,093 / Tesla: 112

NUMBER OF NOBEL PRIZES WON Edison: 0 / Tesla: 0

NUMBER OF ELEPHANTS ELECTROCUTED Edison: 1 / Tesla: 0

DEATH Edison: 1931—Passed away peacefully in his New Jersey home, surrounded by friends and family / Tesla: 1943—Died lonely and in debt in Room 3327 at the New Yorker Hotel

SOURCES: CHENNY WARDLAW "TESLA: MAN OUT OF TIME" | STEVE ROBERT "TESLA: MASTER OF LIGHTNING" | THOMAS.EDISON.COM | PBS.ORG | WEB.MIT.EDU | WIRED.COM

A COLLABORATION BETWEEN GOOD AND COLUMN FIVE

■ No “Revenge” of T.A. Edison but Future “Synergy” of AC and DC Systems !

► SST Applications - The Road Ahead

- **NOT (!) Weight / Space Limited**
- Smart Grid, Stationary Applications



- **AC/AC**
 - **Efficiency Challenge**
 - Controllability also by More Efficient Alternatives
 - * Tap Changers
 - * Series Regulators (Partial Power Processing)
 - Not Compatible w. Existing Infrastr.
 - **Cost / Robustness / Reliability**



- **AC/DC**
 - Efficiency Challenge more Balanced
 - "Local" Applic. (**Datacenters, DC Distr.**)
 - Cost / Robustness / Reliability




- **DC/DC**
 - **No Other Option (!)**
 - MV DC Collection Grids (Wind, PV)
 - Sw. Frequ. as DOF of Design




- **DC/DC**
- **AC/DC**
- **AC/AC**
 - Sw. Frequ. as DOF of Design
 - **Low Weight/Volume @ High Eff.**
 - Local Applic. (Load/Source Integr.)

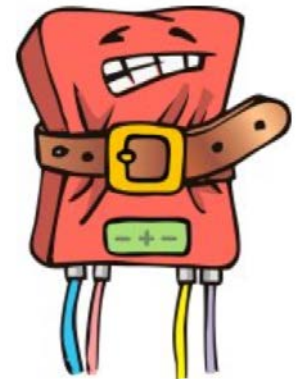- **Weight / Space Limited**
- Traction Applic. etc.



► SST Development Cycles - Outlook

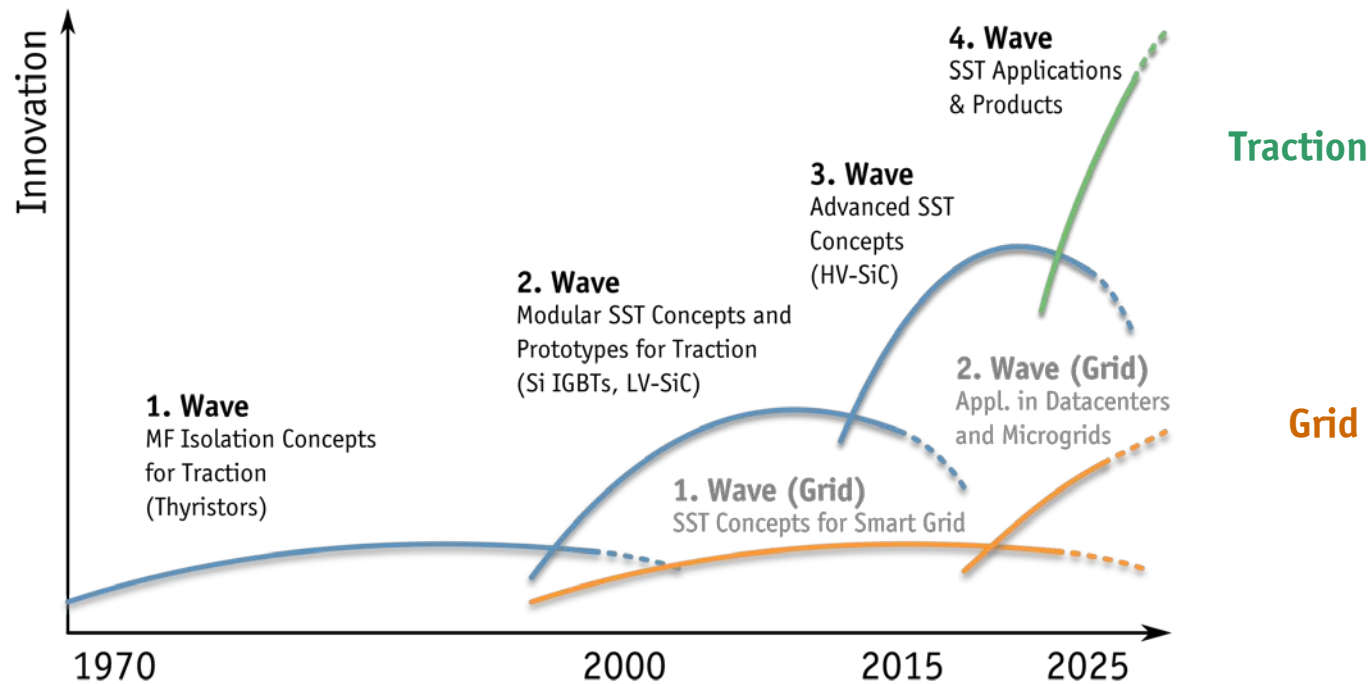

■ Development Reaching Over Decades – Matched to “Product” Life Cycle

Thank You!

Questions

