

# Derivation and Comparative Analysis of Multi-Cell Isolated Front End and Isolated Back End SSTs

**Jonas E. Huber & Johann W. Kolar**

Power Electronic Systems Laboratory  
ETH Zurich, Switzerland



# Agenda

Introduction

7 Slides

IFE vs. IBE Conclusions

3 Sl.

References

4 Sl.

1

S<sup>3</sup>T (IFE) Derivation  
and Operating Principle

*Appendix:*  
Other S<sup>3</sup>T Configurations

# Introduction

---

## ► Motivation: SSTs as MV AC to LV DC Power Interfaces

### ■ Emerging Low-Voltage DC Applications Could Benefit From Direct Connection to Medium-Voltage

- Datacenters with Internal 400V DC Distribution
- Larger PV Plants
- Fuel Cell or Battery Storage
- UPS
- ...

► MVAC ↔ LVDC Solid-State Transformers



FreeImages.com/Alta Leitus



www.powermag.com



FreeImages.com/Whirelf Siemens

### ■ Key Requirements:

- Galvanic Isolation and Voltage Scaling
- Unity Power Factor
- High Efficiency
- Low Complexity

► Isolated PFC Functionality

## ► Partitioning of Isolated AC//DC PFC Functionality


### ■ Required Functionality

- **F:** Folding of the AC Voltage Into a  $|AC|$  Voltage
- **CS:** Input Current Shaping
- **I:** Galvanic Isolation & Voltage Scaling
- **VR:** Output Voltage Regulation

### ■ Isolated PFC Functionality Partitioning Variants:
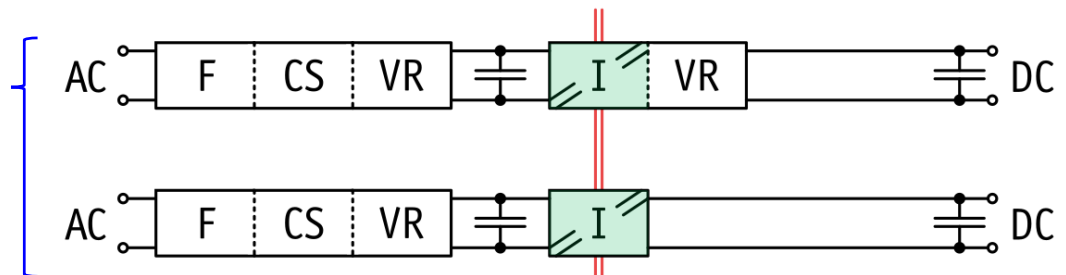
#### Isolated Back End (IBE) ►

→ Broadly Analyzed and  
Employed in SSTs



#### Fully Integrated ►





#### Isolated Front End (IFE) ►

→ Less Common,  
Interesting Alternative



## ► IBE and IFE Origins

### ■ Isolated Back End

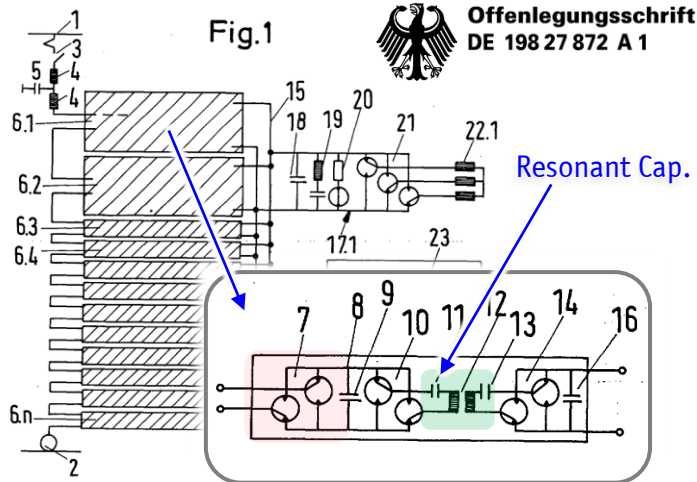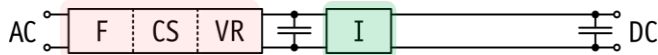

- Steiner, 1996 → Traction Applications
- **Primary Side** Active Rectification
- ISOP System Structure
- **Soft-Switched** Isolation Stage (HC-DCM Series Resonant Conv.)

[Steiner1998], [Steiner2000]

### ■ Isolated Front End

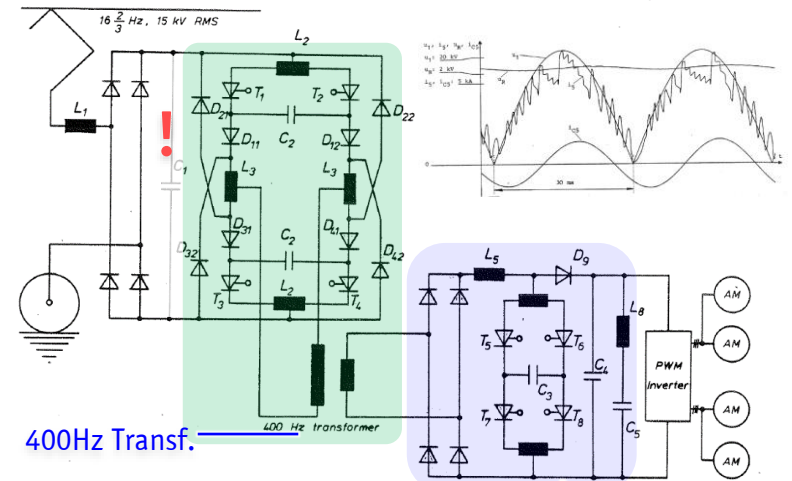
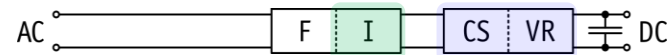


Fig. 3. Circuit diagram.



- Weiss, 1985 (!) → Traction Applications
- **Secondary Side** |AC|-DC Boost Converter for Sinusoidal Current Shaping and Volt. Reg.
- **Hard-Switched** Isolation Stage

- Han et al., 2014 → Ext. to **Resonant & Modular Concept**

[Weiss1985], [Han2014]

## ► IBE and IFE Status



### ■ Isolated Back End

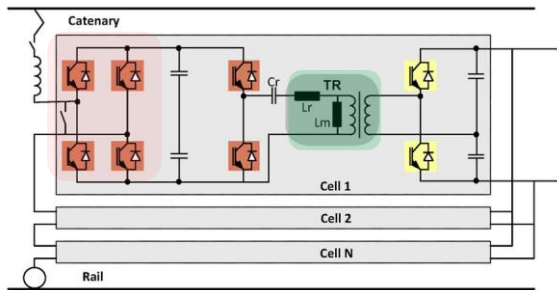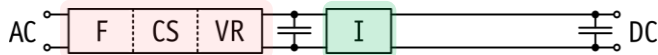

- **Fully Functional Traction SST** by ABB (Dujic, Zhao, et al.), ca. 2011-2014
- **Soft-Switched Isolation Stage** (HC-DCM Series Resonant Conv.)

[Dujic2013] & [Zhao2014]

### ■ Isolated Front End

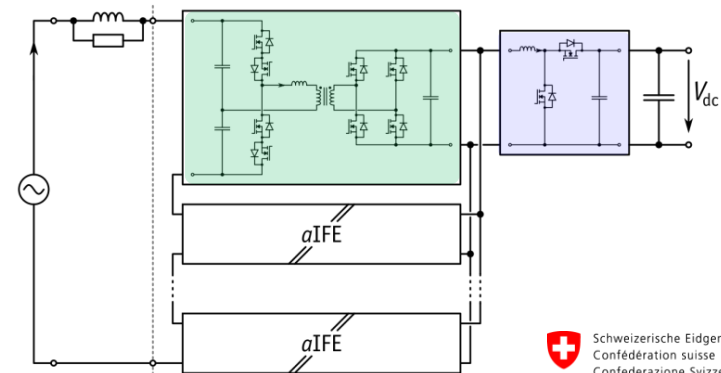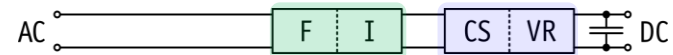

- ETH, 2015, in the Scope of




Schweizerische Eidgenossenschaft  
Confédération suisse  
Confederazione Svizzera  
Confederaziun svizra  
**Energy Turnaround**  
National Research Programme

► **"Swiss SST" (S<sup>3</sup>T)**

- All-SiC, Full ZVS Realization
- Simplified Input Stage
- Further Configurations: 3-Ph., AC/AC, etc.  
→ **Cf. Later!**
- **Soft-Switched Isolation Stage** (HC-DCM Series Resonant Conv.)

ETH / [Kolar2016]


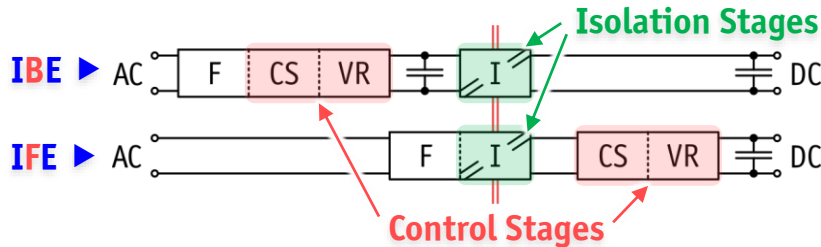
## ► Autonomous Isolation Stage: HC-DCM-SRC Review



- **Isolation Stage: No Control Required!**
  - Minimize Complexity
  - Autonomous Isolation Stage
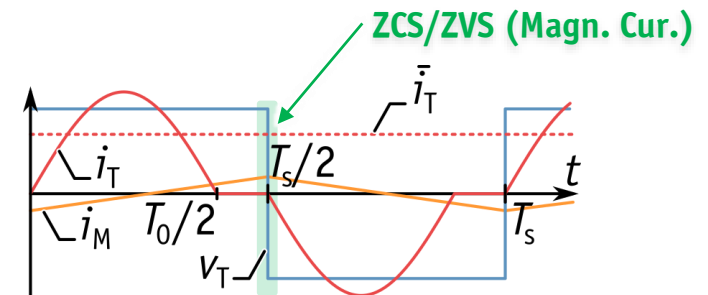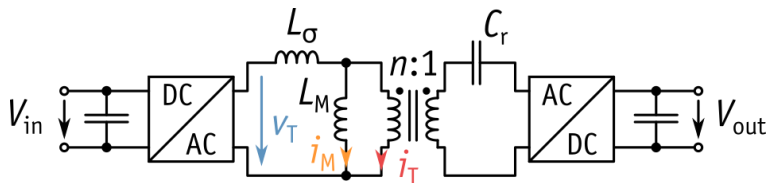
### ■ Enter HC-DCM SRC:

(Half-Cycle Discontinuous-Conduction-Mode Series-Resonant Converter)



- Source Side Actively Switched
- Each Switching Action Excites Resonant Tank → **Current Amplitude Depends on Ex. Volt. Step**

### ■ Automatically Tight Coupling of DC (or LF) Voltages!


$$V_{out} \approx V_{in} \quad (\text{Small Deviation Due to Losses})$$

► Autonomous “DC Transformer”

Further Reading: [McMurray1971], [Huber2015]

(!)

## ► IBE Example System

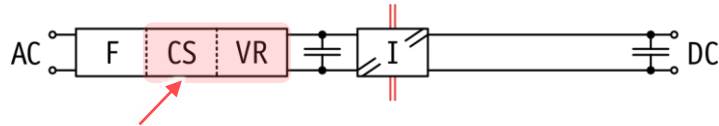


### MV Side Control Stage

#### ■ (Cascaded) AC/DC Boost (ARU)

- Approx. Const. MV DC Volt.
- Total Blocking Volt. Ca.  $1.2 \times v_{g,Pk}$
- Complexity (MV Side Meas. & Contr.)
- Hard Switching

• Transf. Cur. Envelope  $\propto \sin^2(t)$

• DC Buffer Caps.

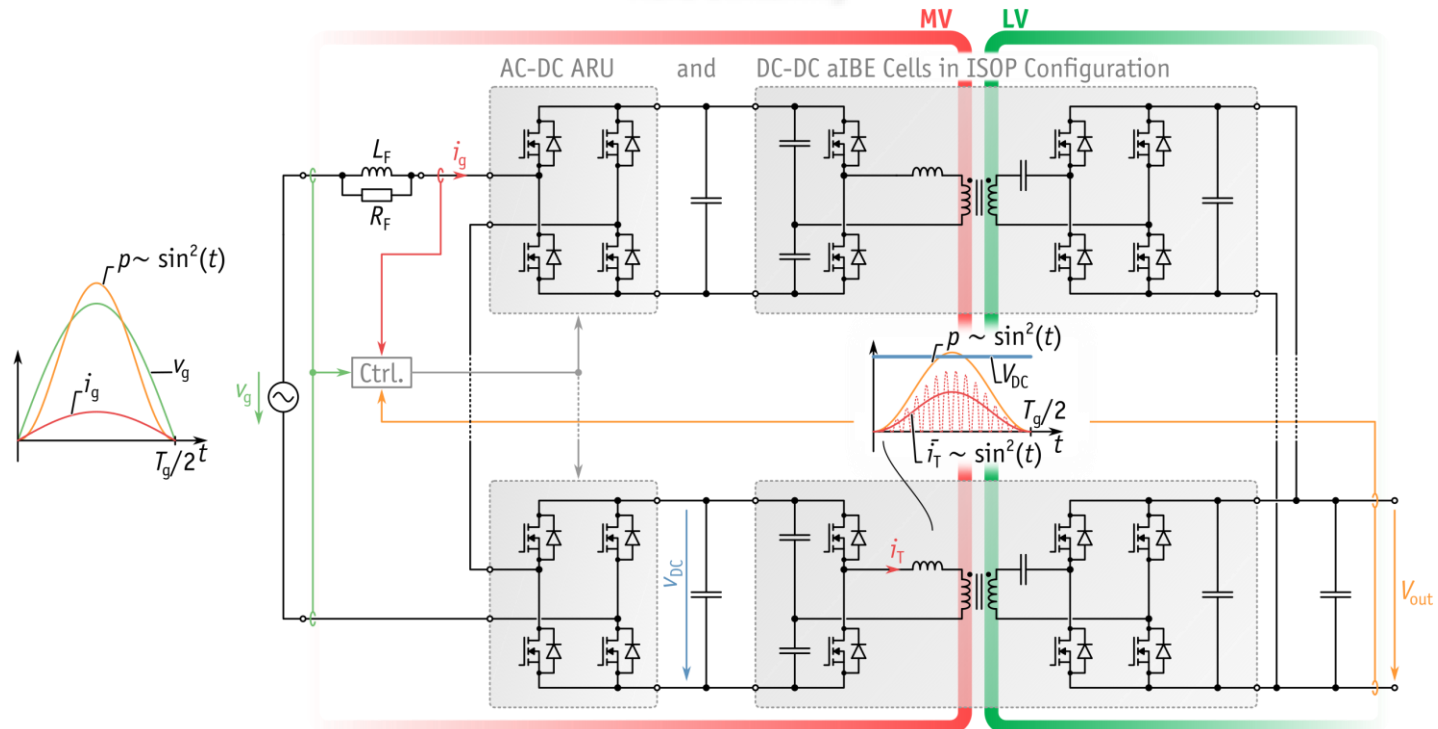

## ► IFE Example System: The Swiss SST (S<sup>3</sup>T)




LV Side Control Stage

■ (Interleaved) |AC|-DC Boost Conv.

S<sup>3</sup>T Specifications

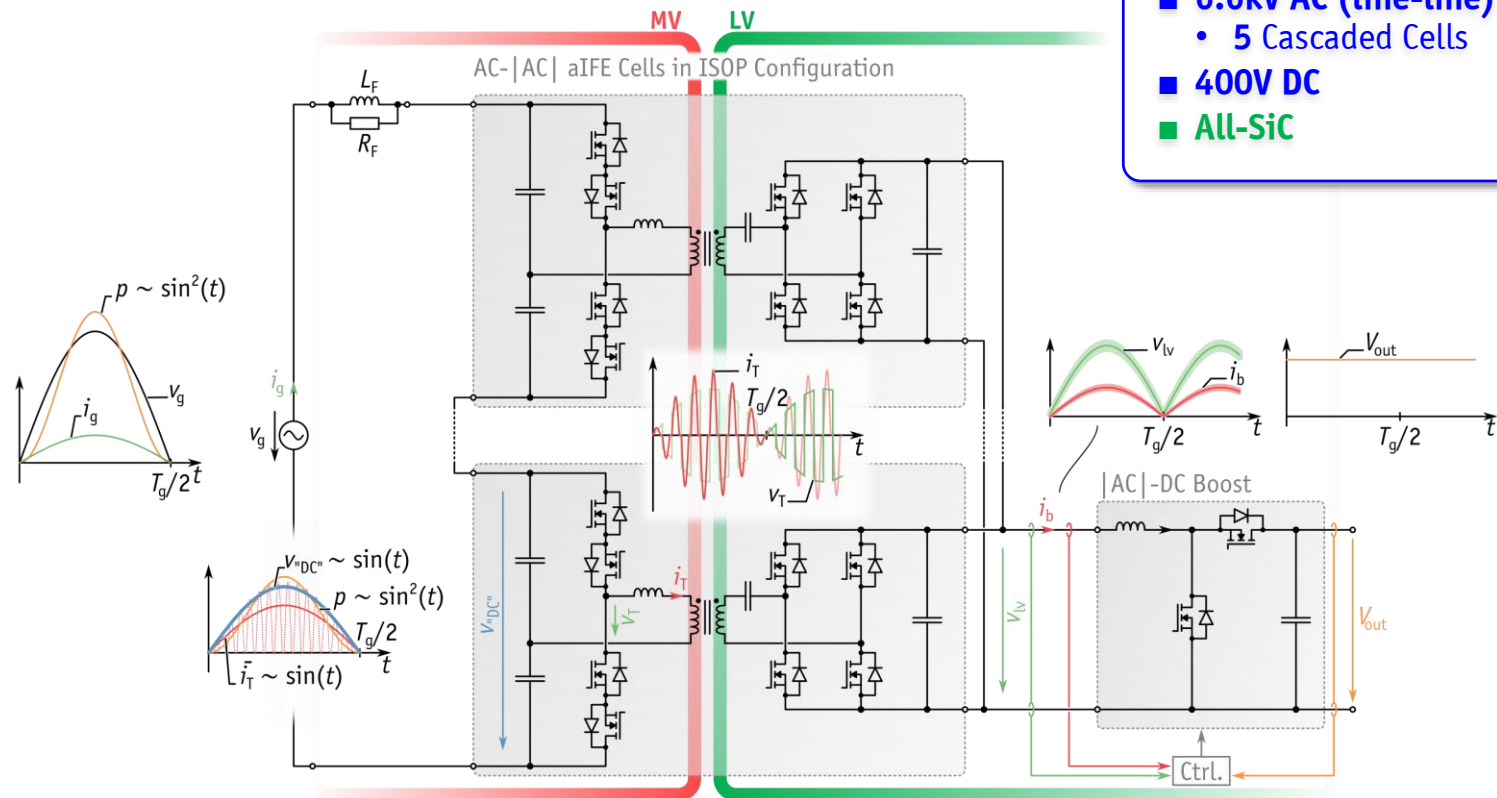- 25kW
- 6.6kV AC (line-line)
  - 5 Cascaded Cells
- 400V DC
- All-SiC




# **S<sup>3</sup>T Derivation and Operating Principle**


---

## ► Topology Derivation (1): *aIFE* Insertion

Non-Isolated, Unidirectional Boost PFC ►

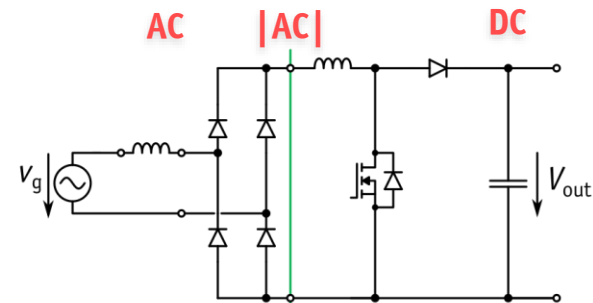


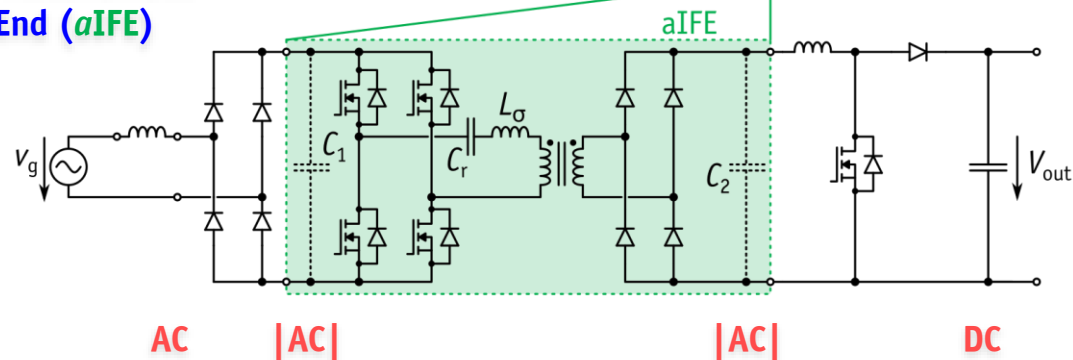Extension by an Autonomous  
Isolation Front End (*aIFE*) ►




- Note:  $C_1$  and  $C_2$  are **NOT** DC Buffer Capacitors!  
→ Commutation/Resonant Capacitors
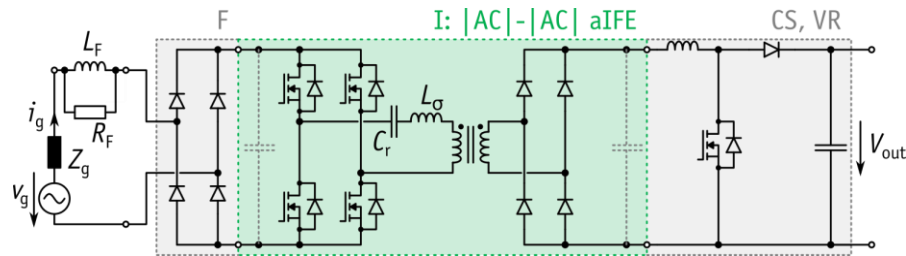
## ► Topology Derivation (2): Direct AC Input




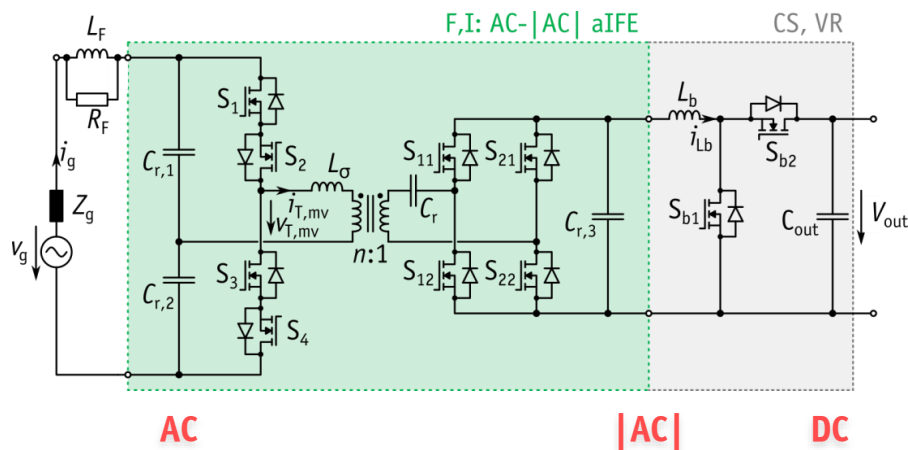- Bidirectional Switches on Primary Side  
→ SRC Switching And Folding of the Grid Voltage




- Note:  $C_{r1}$ ,  $C_{r2}$ , and  $C_{r3}$  are Resonant/Commutation Cap.!
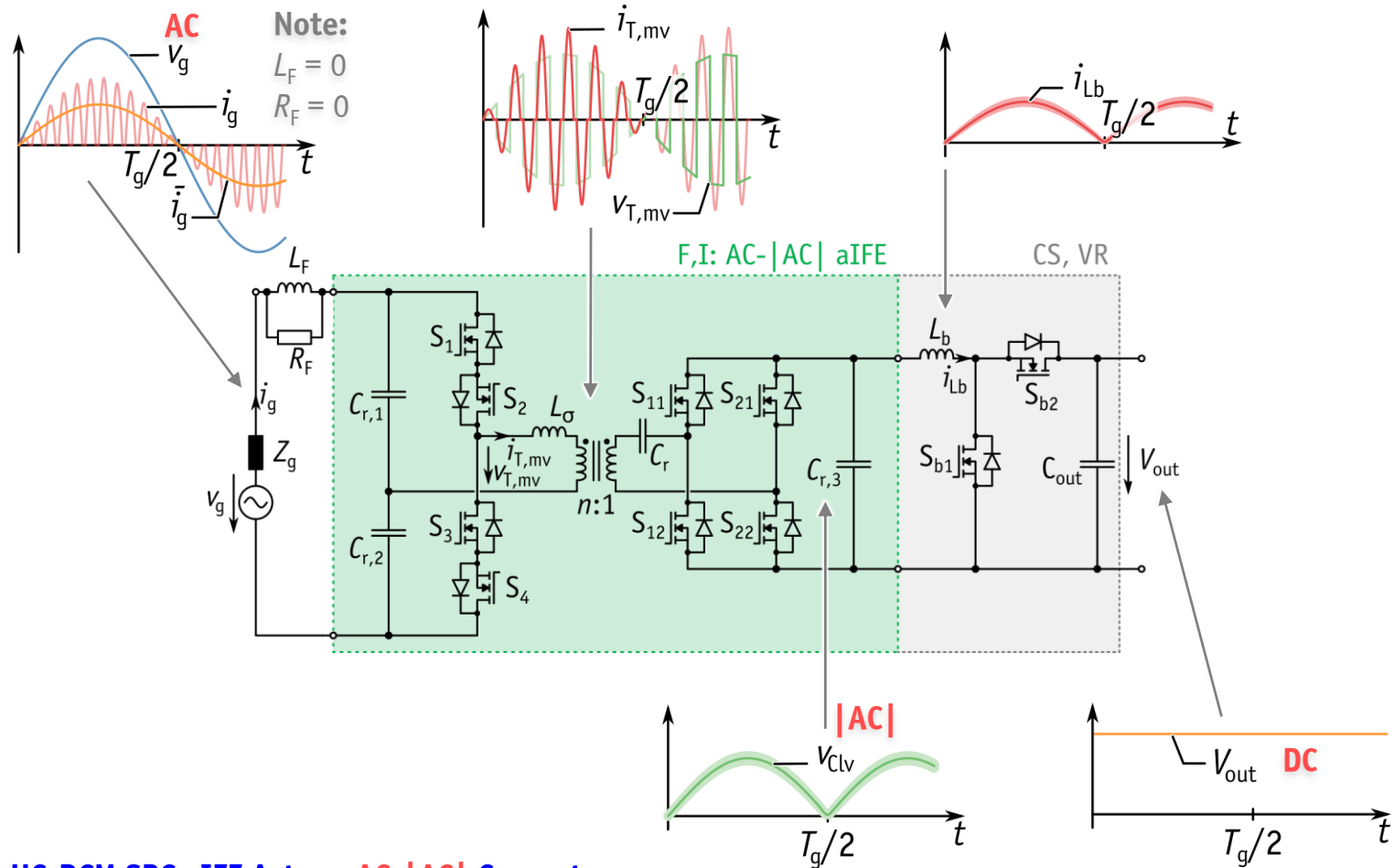
## ► Operating Principle of the Swiss SST (1)



- HC-DCM SRC aIFE Acts as AC-|AC| Converter

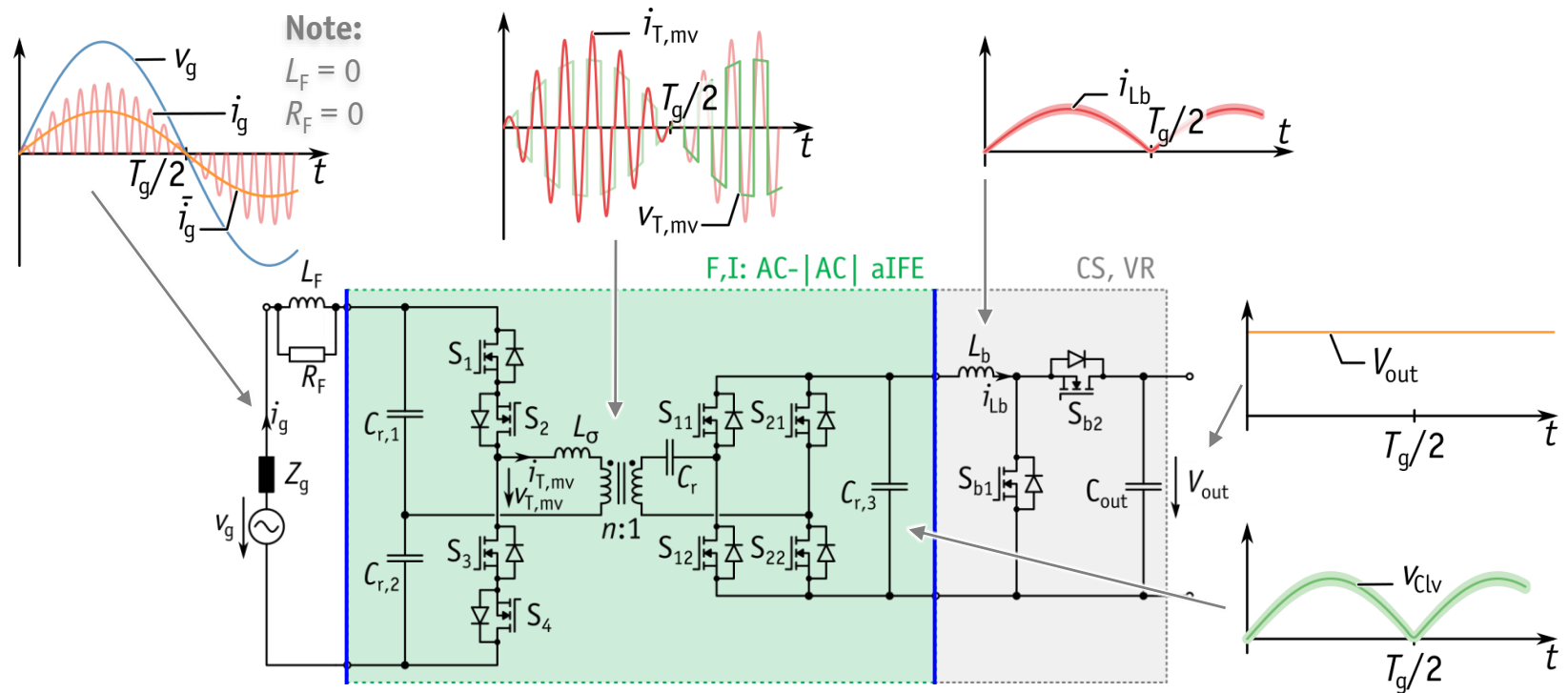
## ► Operating Principle of the Swiss SST (2)



←  $\bar{p}_{Boost}(t)$  Defined by Boost Control  
**No Energy Storage in aIFE**  
**→ Boost Stage Input Characteristics Are Translated to the Grid**


## ► Dynamic Behavior and Modeling
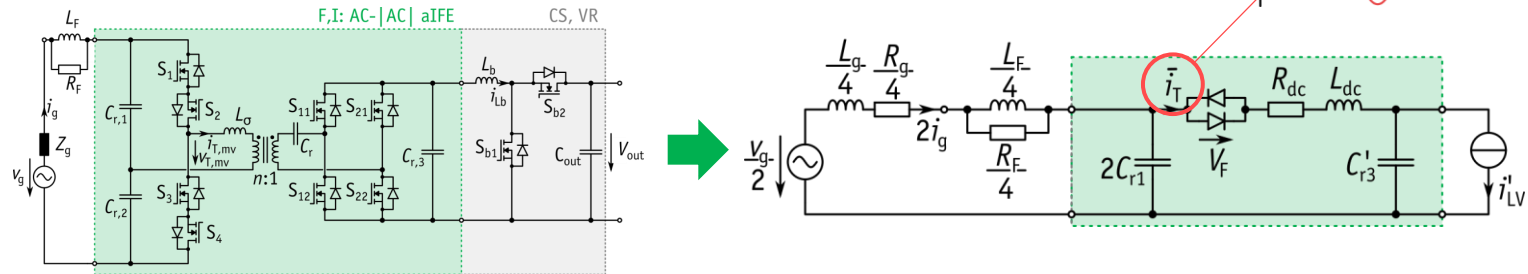
### ■ $\alpha$ IFE Terminal Behavior Can Be Modeled By Passive Equivalent Circuit<sup>1</sup>


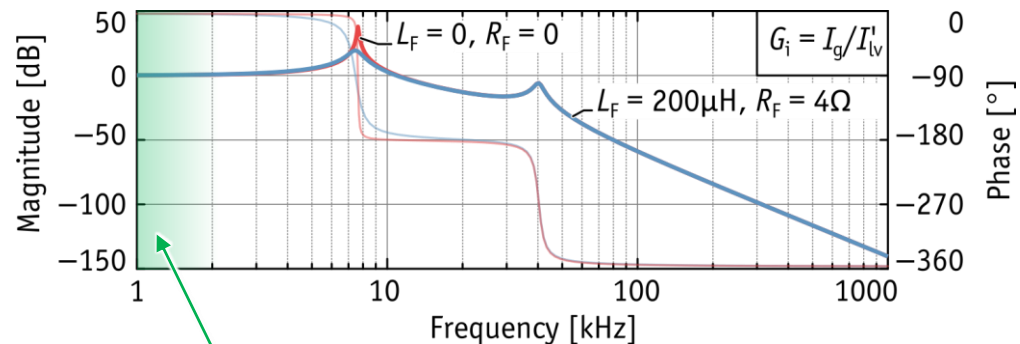
### ■ Transfer Function From Boost Current to Grid Current, $G_i$

- $\alpha$ IFE Translates Boost Stage Current to the Grid w/o Distortion or Delays
- Resonance Between Grid/Filter Impedance and Input Capacitance Requires Damping




Unity Gain For Low Frequencies!



<sup>1</sup> Background Reading: [Huber2015]
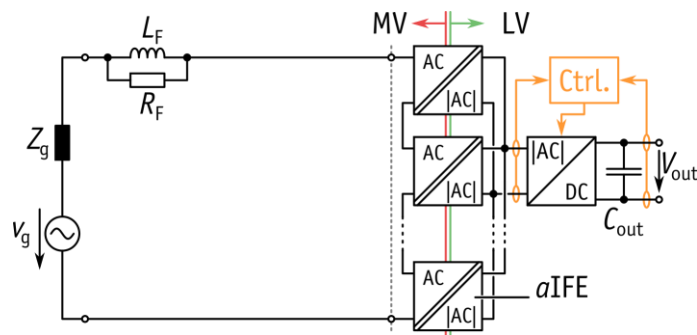
## ► Input-Series Output-Parallel (ISOP) Configuration

- Cascaded  $\alpha$ IFEs, Single (Interleaved) Boost Stage
- No MV Control or Meas. Required!



Interleaving of  $\alpha$ IFE Switching

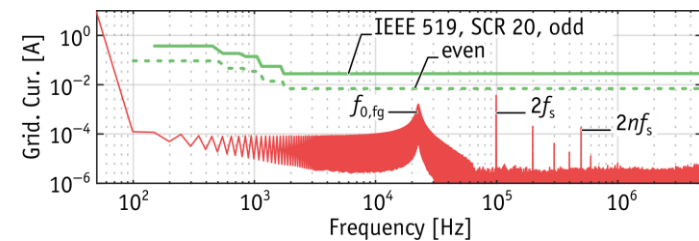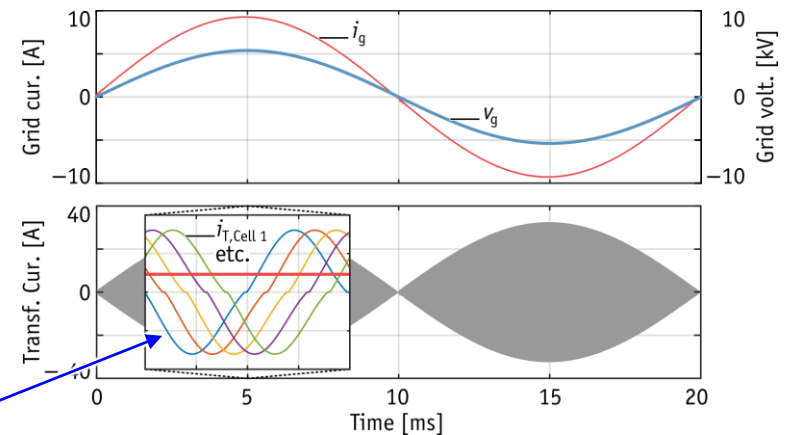

Note: Simulation with Booster  
Modeled as Current Source


- See Appendix For Other Configurations!

## ► ISOP: Balancing & Load Sharing

### ■ $\alpha$ IFE Tightly Couples Its Terminal Voltages


- All Cells Share Common LV Bus Voltage

→ MV Side Voltage Sharing is Ensured!

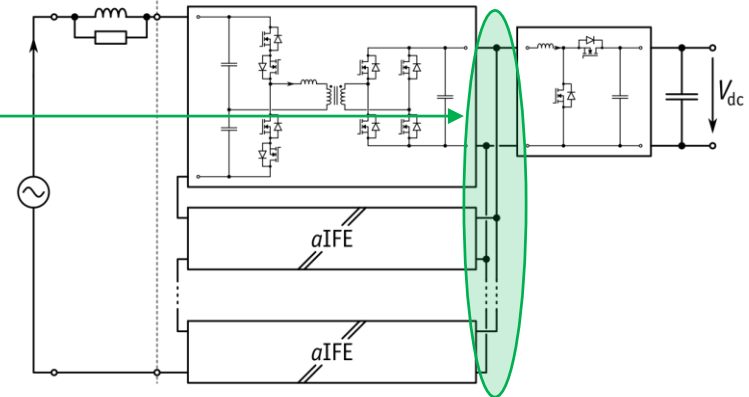

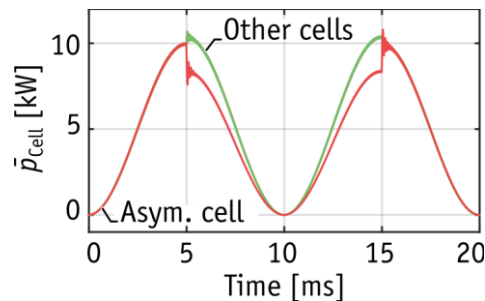
### ■ Example:

- Add. Load (10% nominal) On MV Side of One Cell




→ Redistribution of Power Transfer

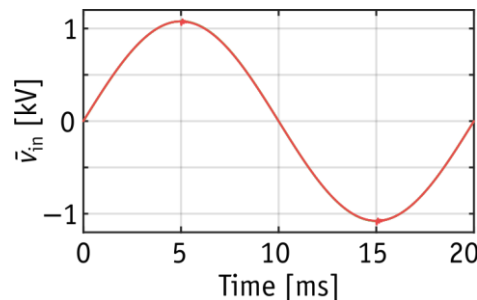


→ Voltage Sharing Ensured

- Also Simulated w/o Problems for Primary Resonant Capacitance Tolerances (20%)

## ► aIFE ZVS Considerations (1)

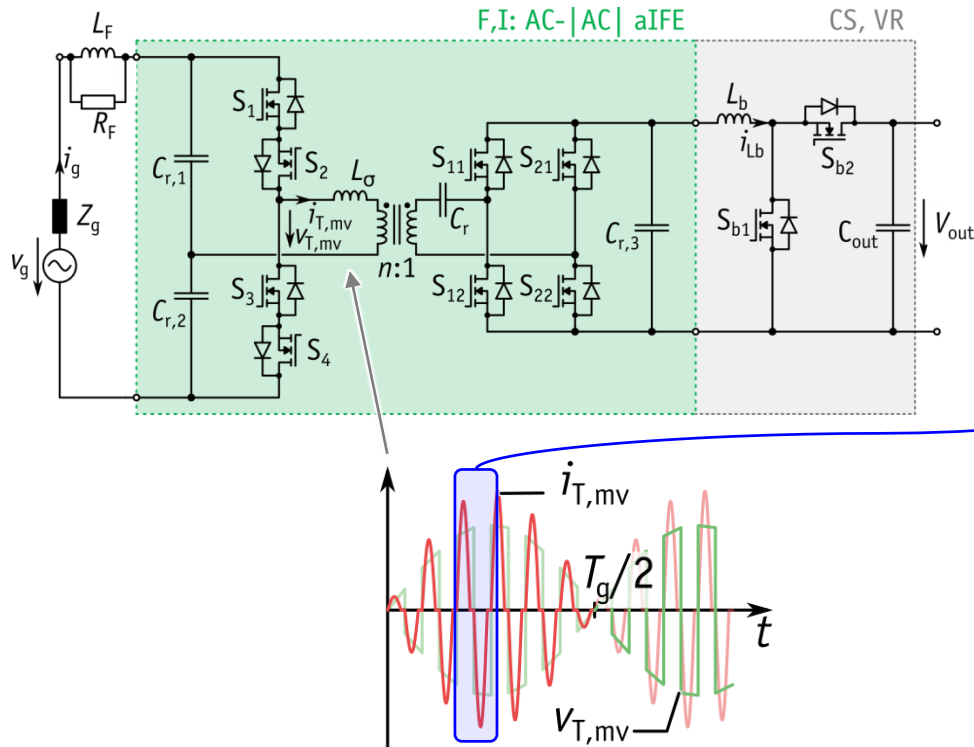


### ZVS Using Magnetizing Current

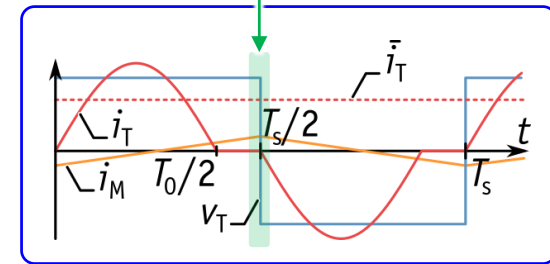


### ■ Magnetizing Current is Used for Load-Independent ZVS (LLC Operation)

- Transf. Volt. Envelope  $\propto \sin(t)$
  - Magn. Current Amplitude  $\propto \sin(t)$
  - Nonlinear Parasitic FET  $C_{oss}$
- ZVS Not Ensured Over Entire Grid Period!

## ► *a*IFE ZVS Considerations (2)

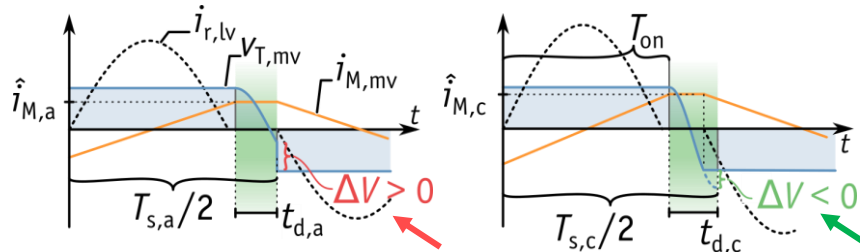

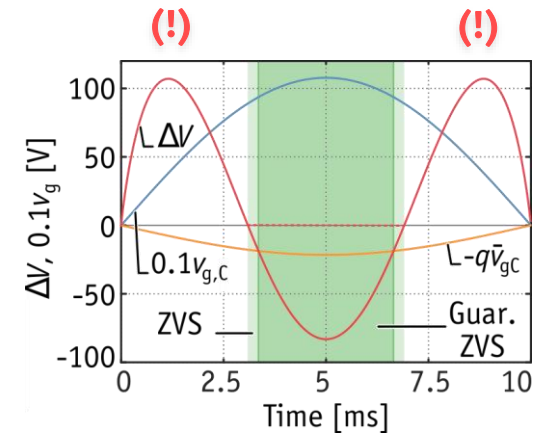
- **Optimize Magn. Ind. Value and Interlock Time for Min. Losses**
  - Partial ZVS Losses Are Very Small (Calc. for 1700V SiC FET)
  - ZVS Not Ensured Over Entire Grid Period!



- **Full-ZVS Still Desirable for EMI Noise Limitation**
  - Higher Losses With Adapted Magn. Ind. & Const. Dead Time
  - **Variable Interlock Time**

$$t_d^* = \frac{1}{\omega_0} \cdot \left[ \pi - \arctan\left(\frac{Z_0 \hat{i}_M}{V_{Cr1}}\right) - \arccos\left(\frac{V_{Cr2} + q\bar{v}_{g,C}}{\sqrt{\hat{i}_M^2 Z_0^2 + V_{Cr1}^2}}\right) \right]$$

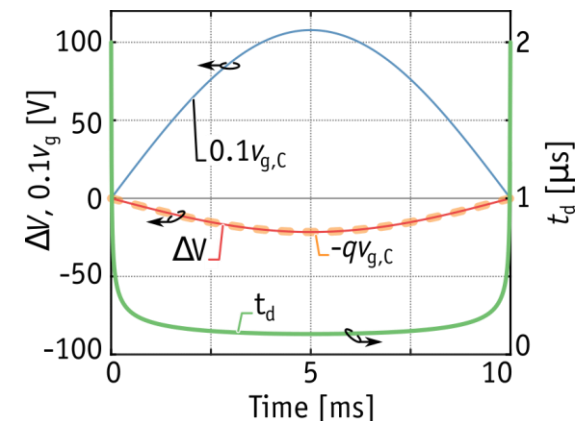- Potentially Compromises Interleaving – Analyses Ongoing!





## Control Stage ZVS

- **Known Concepts from Literature (TCM, Clamp Switch, etc.)**

## ► Control & Modulation With LV Meas. Only

- Sinusoidal Grid Current
- Unity Power Factor (0.99+)
- Output Voltage Regulation
- Grid. Volt. Polarity Est. for MV Side
- ZVS Modulation

Only LV-Side Meas.!

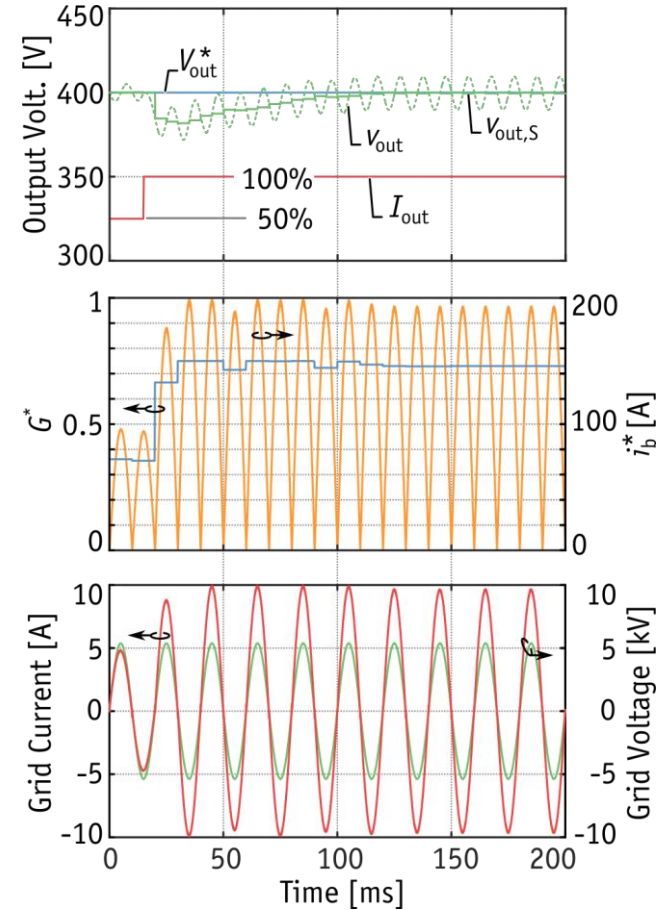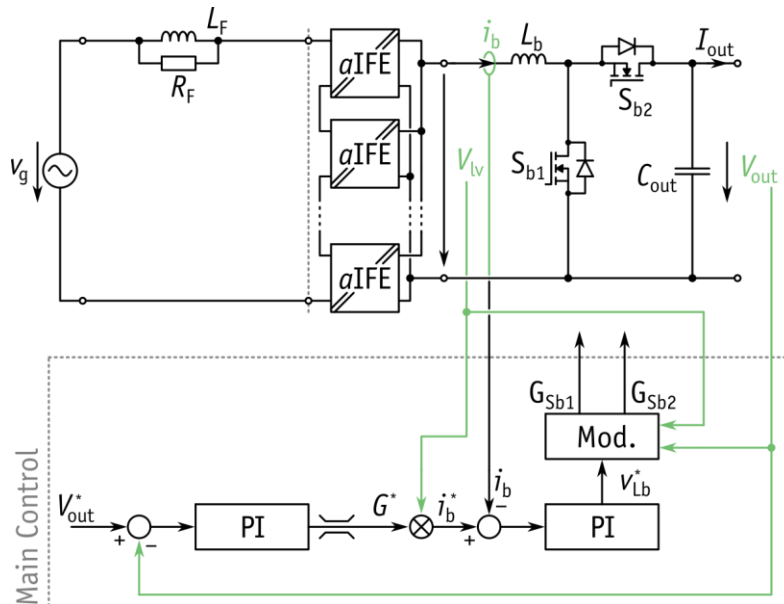

# **IBE and IFE** **Comparison & Conclusion**

---

## ► IFE Example System: The Swiss SST ( $S^3T$ )




Back Side


■ (Interleaved) |AC|-DC Boost

- MV "DC" Volt.  $\propto \sin(t)$
- Lower Total MV Block. Volt.
- Low MV Side Complexity and Smaller Floating Assembly
- Full ZVS Possible

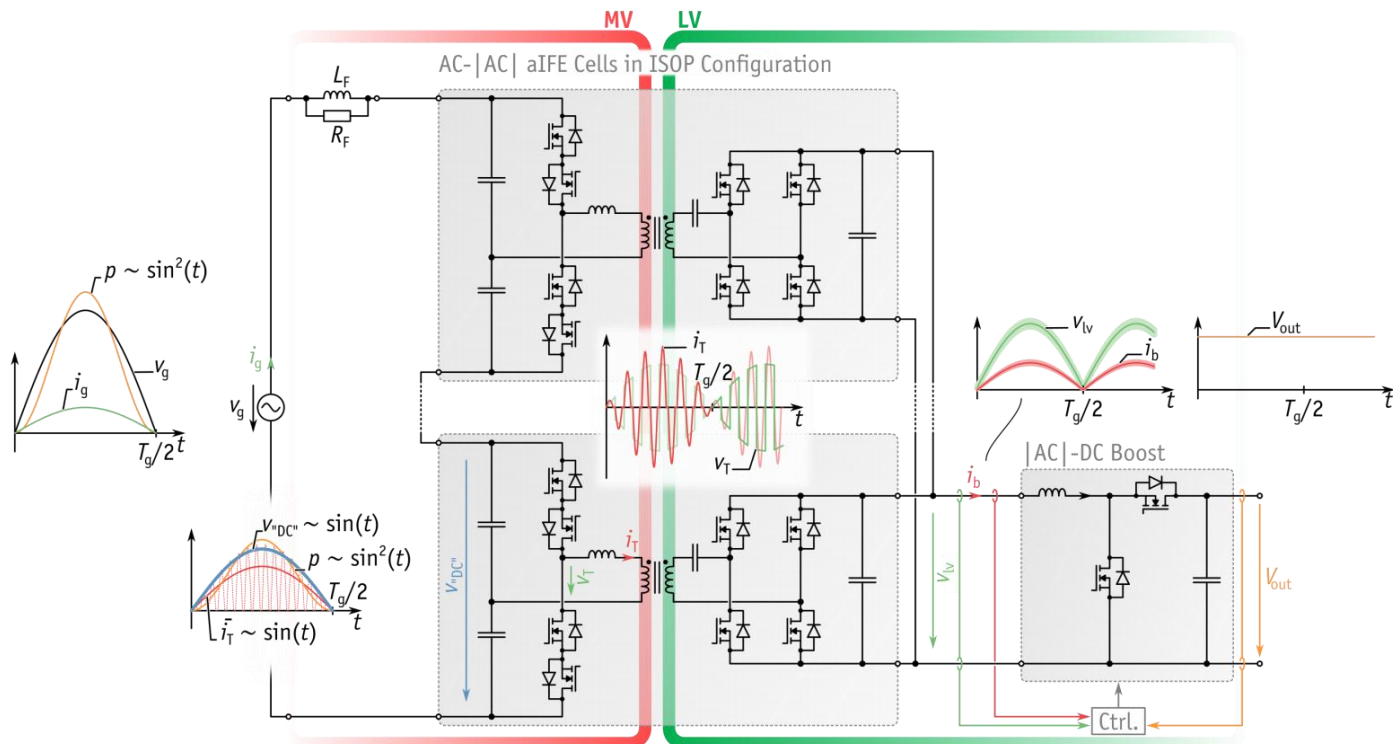- Transf. Cur. Envelope  $\propto \sin(t)$
- Larger SiC Area, More Copper
- Less Core Mat.


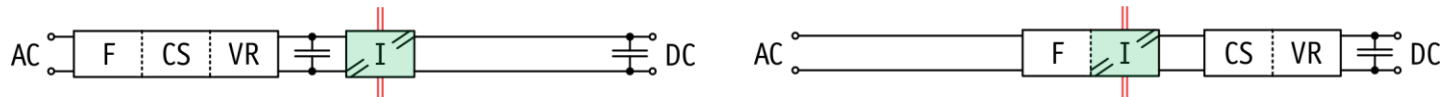
## ► Comparative Evaluation of IBE and IFE Concept



### Key Differences

#### ■ Control Stage (Boost) Location

**IBE**

MV Side

**IFE**

LV Side

### IFE (S<sup>3</sup>T) Features...



- Low MV Side Complexity  
(No Contr., Meas., Smaller Mech. Assem., etc.)
- Lower Total MV Blocking Voltage  
(5 Instead of 6 Casc. Cells for 6.6kV)
- No DC Buffering Per Cell (3-ph)
- Possibly Full ZVS of Contr. Stage
- Limitation To  $\cos\varphi \approx 1$  (Bidirectional)
- Higher SRC LV Side Cur. (Lower Volt.)

#### ■ Transf. Volt. Envelope

Const.  
→  $\tilde{I}_T$

$\propto \sin(t)$   
→  $1.44 \cdot \tilde{I}_T$

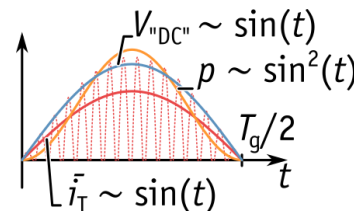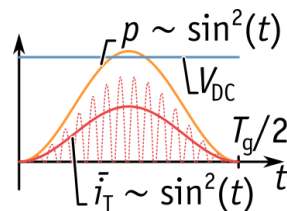- Higher Copper Usage
  - Higher SiC Area Usage
  - Lower Transf. Core Mat. Usage
- } Ca. 2...3x (!)



## ► (Preliminary) Conclusions

- Isolated **Back End** Main Advantage:  
Lower RMS Currents → Lower Semic. Area
- Isolated **Front End** Main Advantage:  
Lower MV Side Complexity

► Complexity vs. SiC Area Requirement Trade-Off




Img.: scanrail / 123RF Stock Photo

► IFE Concept (**S<sup>3</sup>T**) Has Potential for SST Appl. with Lower Power Ratings  
→ Higher Contrib. of Meas. And Control Electronics To Costs

### ■ Comparative Evaluation is Work in Progress:

- Grid Filter Requirements
- Control Stage Sw. Losses
- Full Multi-Objective Optimization
- ...

### S<sup>3</sup>T Research Status

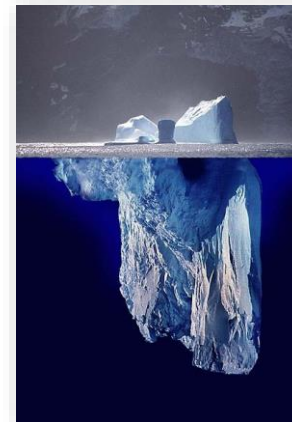

Img.: U. Kils / Wikimedia.org

Analyzed

To Be Analyzed (!)

# Thank You!



lightwise / 123RF Stock Photo


**Further Reading:** [Kolar2016]; **Upcoming:** [Huber2016a], [Huber2016b]

# *Appendix:* **Other S<sup>3</sup>T Configurations**

---


## ► Other Input-Series Output-Parallel Configurations
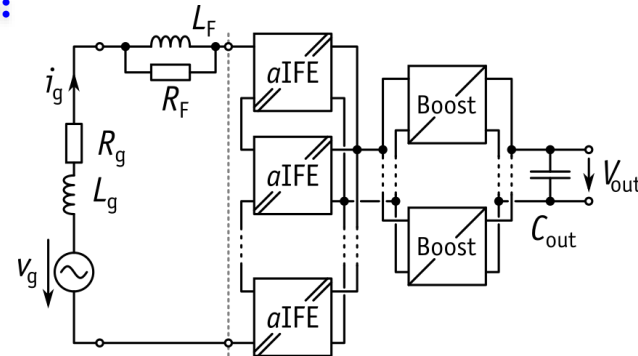
### ■ Cascaded $a$ IFEs, Single (Interleaved) Boost Stage:



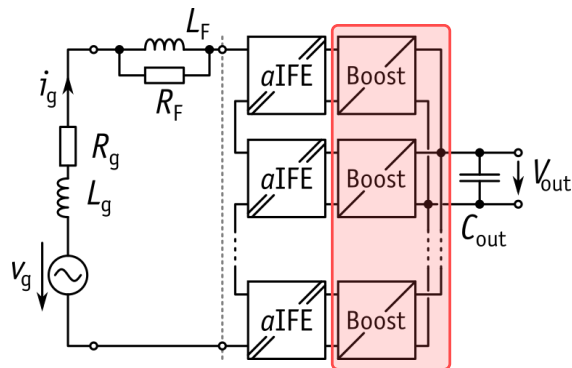
### ■ One Boost Stage Per Converter Cell

- Control for Equal Input Impedance Ensures MV Side Voltage Balancing





### ■ Common Folding Stage

- Passive or Active Grid Freq. Rectifier

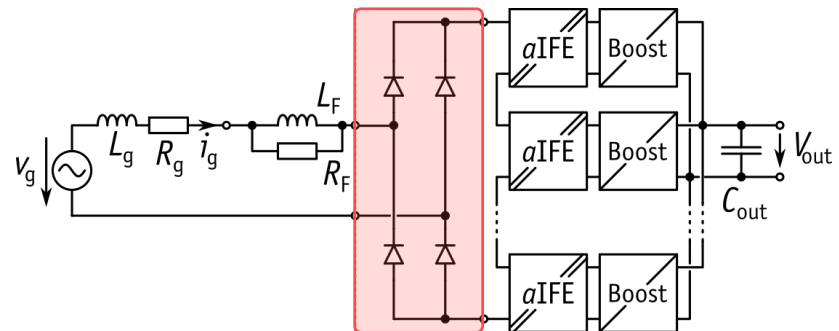
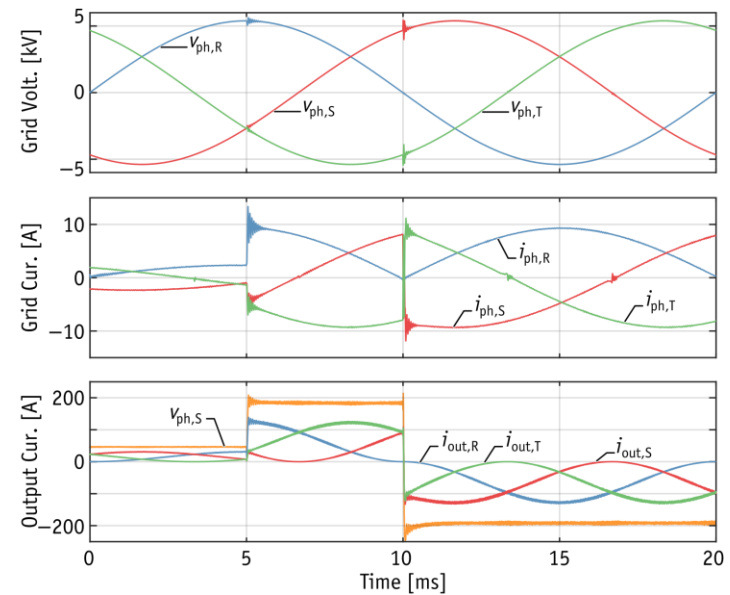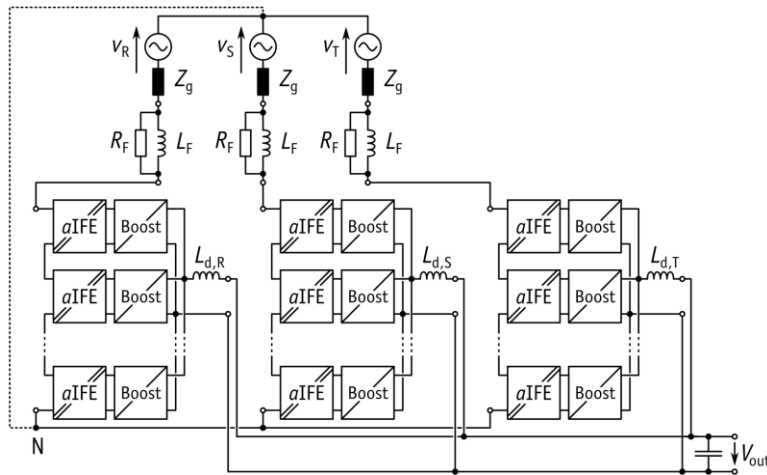
## ► Three-Phase System Configuration

- **Combination of Three Phase Stacks**  
(Example Realized With One Boost Stage Per Cell)




- **Benefit: In Theory No Need for Intermediate Energy Buffers in the Cells**

## ► Scott-Transformer Configuration

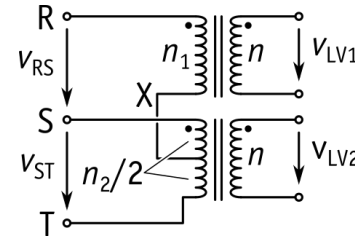
### ■ Magnetic Scott Transformer

- Three-Phase AC Input
- Two 90° Phase-Shifted AC Outputs
- Symmetric Grid Currents If Outputs Equally Loaded




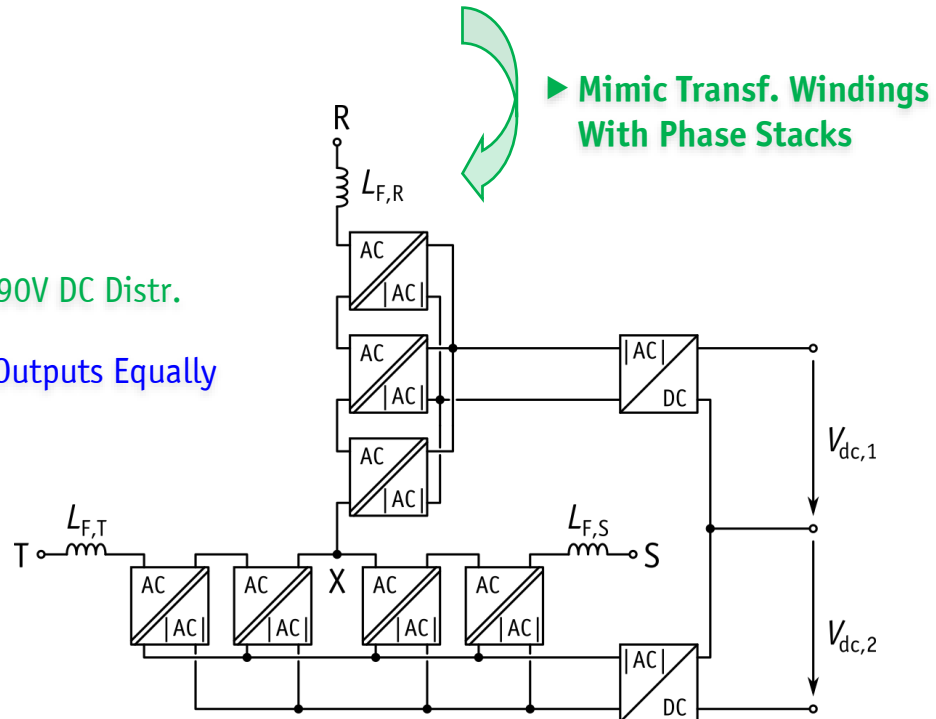
### ■ S<sup>3</sup>T Scott Transformer

- Three-Phase AC Input
- Two Isolated DC Outputs  
→ Series Connection for ±190V DC Distr.
- Symmetric Grid Currents If Outputs Equally Loaded (!)





## ► Direct AC/AC Operation

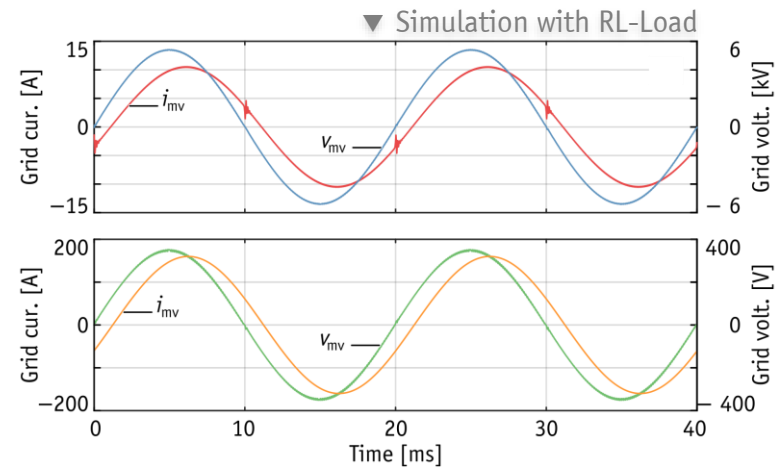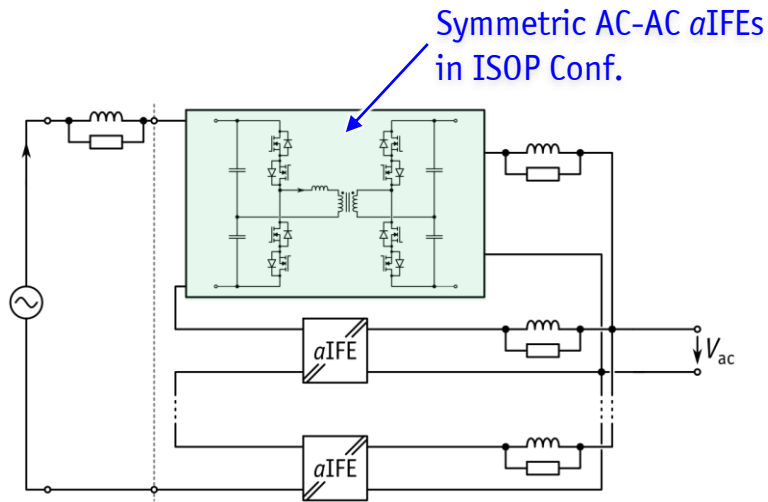

### ■ Optional Voltage Control with LV AC Chopper

### ■ Note: Back To The Roots!

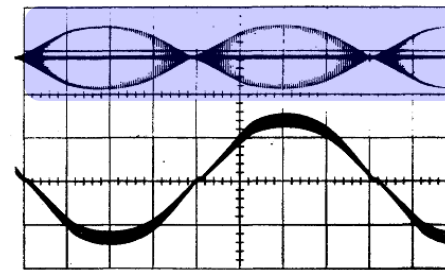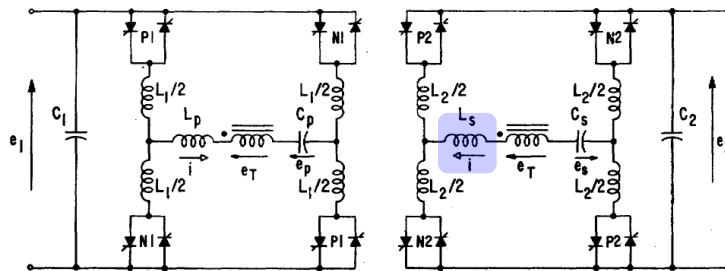

WILLIAM McMURRAY  
1971 (!)

[McMurray1971]

# References

---

## ► References: A-Z

**Dujic2013:** D. Dujic, C. Zhao, A. Mester, J. K. Steinke, M. Weiss, S. Lwedeni-Schmid, T. Chaudhuri, and P. Stefanutti, “**Power Electronic Traction Transformer—Low Voltage Prototype**,” *IEEE Trans. Power Electron.*, vol 28, no. 12, Dec. 2013.

**Han2014:** B. Han, N. Choi, and J. Lee, “**New bidirectional intelligent semiconductor transformer for smart grid application**,” *IEEE Trans. Power Electron.*, vol. 29, no. 8, pp. 4058-4066, Aug. 2014.

**Huber2015:** J. E. Huber and J. W. Kolar, “**Analysis and design of fixed voltage transfer ratio DC/DC converter cells for phase-modular solid-state transformers**,” in *Proc. IEEE Energy Conversion Congr. and Expo. (ECCE)*, Montréal, Canada, Sept. 2015.

**Huber2016a:** J. E. Huber, D. Rothmund, and J. W. Kolar, “**Derivation and comparative analysis of bidirectional multi-cell MV input PFC rectifier system**,” to be published/under review, 2016.

**Huber2016b:** J. E. Huber, D. Rothmund, and J. W. Kolar, “**Full-ZVS modulation and control considerations for all-SiC ISOP-type isolated front end (IFE) solid-state transformer (Swiss SST)**,” to be published/under review, 2016.

**Kolar2016:** J. W. Kolar and J. E. Huber, “**Konverter zur potentialgetrennten Übertragung elektrischer Energie**,” Swiss Patent Application, Jan. 12, 2016.

**McMurray1971:** W. McMurray, “**The thyristor electronic transformer: a power converter using a high-frequency link**,” *IEEE Trans. Ind. Gen. Appl.*, vol. 7, no. 4, pp. 451-457, Jul. 1971.

**Steiner1998:** M. Steiner and H. Reinold, “**Antriebsschaltung für ein Schienenfahrzeug**,” German Patent DE 198 27 872 A 1, 1998.

**Steiner2000:** M. Steiner, “**Seriegeschaltete Gleichspannungs-Zwischenkreisumrichter in Traktionsanwendungen am Wechselspannungsfahrdraht**,” PhD Dissertation, ETH Zürich, Switzerland, 2000.

**Weiss1985:** H. Weiss, “**Elimination of the 16 2/3 Hz 15kV main transformer on electrical traction vehicles**,” in *Proc. 1st Europ. Power Electronics and Applications Conf. (EPE)*, Brussels, Belgium, Nov. 1985.

**Zhao2014:** C. Zhao, D. Dujic, A. Mester, J. K. Steinke, M. Weiss, S. Lwedeni-Schmid, T. Chaudhuri, and P. Stefanutti, “**Power electronic traction transformer—medium voltage prototype**,” *IEEE Trans. Ind. Electron.*, vol. 61, no. 7, pp. 3257-3268, Jul. 2014.